 


## Decoder

The combinational circuit that change the binary information into  $2^N$  output lines is known as **Decoders**. The binary information is passed in the form of  $N$  input lines. The output lines define the  $2^N$ -bit code for the binary information. In simple words, the **Decoder** performs the reverse operation of the **Encoder**. At a time, only one input line is activated for simplicity. The produced  $2^N$ -bit output code is equivalent to the binary information.




There are various types of decoders which are as follows:

### 2 to 4 line decoder:

In the 2 to 4 line decoder, there is a total of three inputs, i.e.,  $A_0$ ,  $A_1$  and  $E$  and four outputs, i.e.,  $Y_0$ ,  $Y_1$ ,  $Y_2$ , and  $Y_3$ . For each combination of inputs, when the enable 'E' is set to 1, one of these four outputs will be 1. The block diagram and the truth table of the 2 to 4 line decoder are given below.

### Block Diagram:

 

Truth Table:

Enable	INPUTS		OUTPUTS			
E	$A_1$	$A_0$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	X	X	0	0	0	0
1	0	0	0	0	0	1
1	0	1	0	0	1	0
1	1	0	0	1	0	0
1	1	1	1	0	0	0

The logical expression of the term  $Y_0$ ,  $Y_1$ ,  $Y_2$ , and  $Y_3$  is as follows:


$$Y_3 = E \cdot A_1 \cdot A_0$$

$$Y_2 = E \cdot A_1 \cdot A_0'$$

$$Y_1 = E \cdot A_1' \cdot A_0$$

$$Y_0 = E \cdot A_1' \cdot A_0'$$

 
Logical circuit of the above expressions is given below:



### 3 to 8 line decoder:

The 3 to 8 line decoder is also known as **Binary to Octal Decoder**. In a 3 to 8 line decoder, there is a total of eight outputs, i.e.,  $Y_0, Y_1, Y_2, Y_3, Y_4, Y_5, Y_6,$  and  $Y_7$  and three inputs, i.e.,  $A_0, A_1,$  and  $A_2$ . This circuit has an enable input 'E'. Just like 2 to 4 line decoder, when enable 'E' is set to 1, one of these four outputs will be 1. The block diagram and the truth table of the 3 to 8 line encoder are given below.

Block Diagram:

 

Truth Table:

Enable	INPUTS			Outputs							
E	$A_2$	$A_1$	$A_0$	$Y_7$	$Y_6$	$Y_5$	$Y_4$	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

The logical expression of the term  $Y_0$ ,  $Y_1$ ,  $Y_2$ ,  $Y_3$ ,  $Y_4$ ,  $Y_5$ ,  $Y_6$ , and  $Y_7$  is as follows:

$$Y_0 = A_0' . A_1' . A_2'$$

$$Y_1 = A_0 . A_1' . A_2'$$

$$Y_2 = A_0' . A_1 . A_2'$$

$$Y_3 = A_0 . A_1 . A_2'$$


$$Y_4 = A_0' . A_1' . A_2$$

$$Y_5 = A_0 . A_1' . A_2$$

$$Y_6 = A_0' . A_1 . A_2$$

$$Y_7 = A_0 . A_1 . A_2$$

 Logical circuit of the above expressions is given below:



### 4 to 16 line Decoder

In the 4 to 16 line decoder, there is a total of 16 outputs, i.e.,  $Y_0, Y_1, Y_2, \dots, Y_{16}$  and four inputs, i.e.,  $A_0, A_1, A_2$ , and  $A_3$ . The 3 to 16 line decoder can be constructed using either 2 to 4 decoder or 3 to 8 decoder. There is the following formula used to find the required number of lower-order decoders.

$$\text{Required number of lower order decoders} = m_2 / m_1$$

$$m_1 = 8$$


$$m_2 = 16$$

Required number of 3 to 8 decoders =

$$\frac{16}{8}$$

$$= 2$$

Block Diagram:

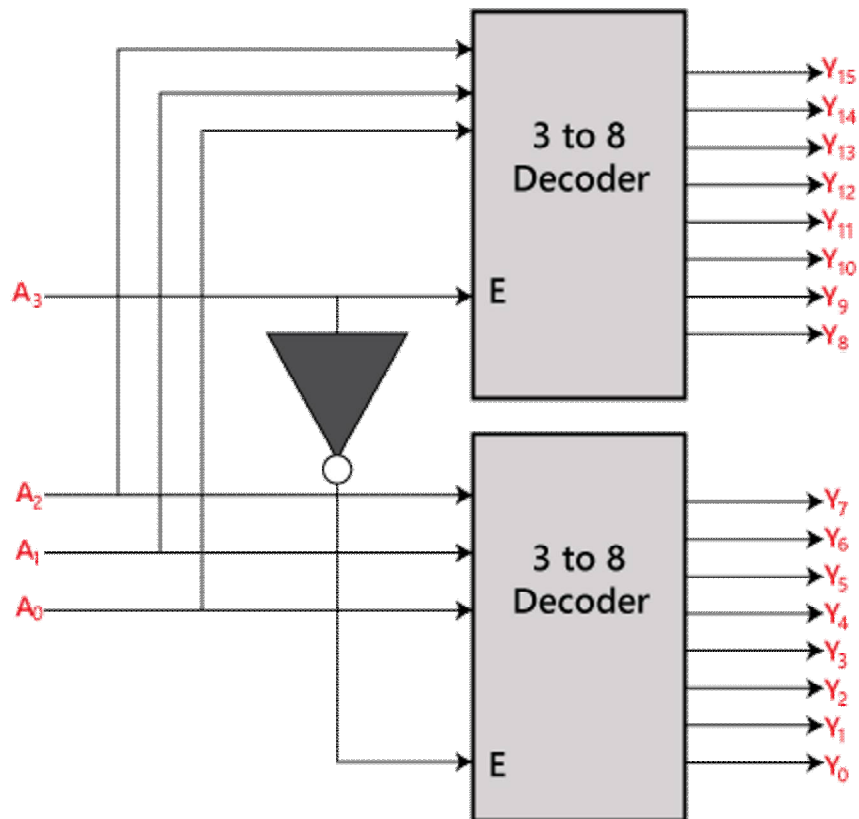

Truth Table:

INPUTS				OUTPUTS															
A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	Y <sub>15</sub>	Y <sub>14</sub>	Y <sub>13</sub>	Y <sub>12</sub>	Y <sub>11</sub>	Y <sub>10</sub>	Y <sub>9</sub>	Y <sub>8</sub>	Y <sub>7</sub>	Y <sub>6</sub>	Y <sub>5</sub>	Y <sub>4</sub>	Y <sub>3</sub>	Y <sub>2</sub>	Y <sub>1</sub>	Y <sub>0</sub>
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0
0	0	1	1	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0

The logical expression of the term A<sub>0</sub>, A<sub>1</sub>, A<sub>2</sub>, ..., A<sub>15</sub> are as follows:

$$Y_0 = A_0' . A_1' . A_2' . A_3'$$

$$Y_1 = A_0' . A_1' . A_2' . A_3$$

$$Y_2 = A_0' . A_1' . A_2 . A_3'$$

$$Y_3 = A_0' . A_1' . A_2 . A_3$$

$$Y_4 = A_0' . A_1 . A_2' . A_3'$$

$$Y_5 = A_0' . A_1 . A_2' . A_3$$

$$Y_6 = A_0' . A_1 . A_2 . A_3'$$

$$Y_7 = A_0' . A_1 . A_2 . A_3$$

$$Y_8 = A_0 . A_1' . A_2' . A_3'$$

$$Y_9 = A_0 . A_1' . A_2' . A_3$$

$$Y_{10} = A_0 . A_1' . A_2 . A_3'$$

$$Y_{11} = A_0 . A_1' . A_2 . A_3$$

$$Y_{12} = A_0 . A_1 . A_2' . A_3'$$

$$Y_{13} = A_0 \cdot A_1 \cdot A_2' \cdot A_3$$

$$Y_{14} = A_0 \cdot A_1 \cdot A_2 \cdot A_3'$$

$$Y_{15} = A_0 \cdot A_1 \cdot A_2' \cdot A_3$$

Logical circuit of the above expressions is given below:

