

Generally any network may be represented by a rectangular box.

A pair of terminals at which a signal may be enter (or) leave a network is called a port.

A port is defined as any pair of terminals into which energy is supplied (or) from which energy is withdrawn (or) where network variables may be measured.

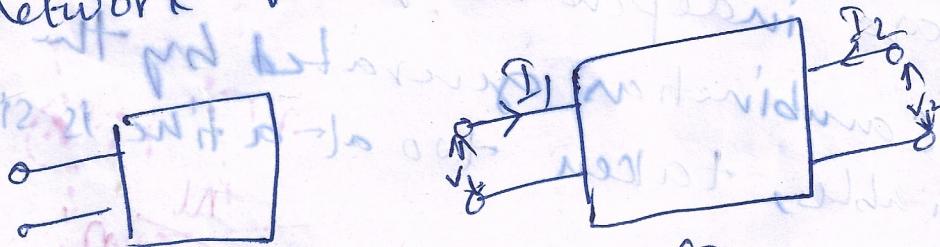


fig 1(b)

A two port network is simply a N/w inside a black box & the N/w has only two pairs of accessible terminals; usually one pair represents the R/p & the other represents the O/p. such a N/w is common in electronic, communication & tx & distribution system. fig 1.(b) is a two-port (O1) two-terminal pair N/w, in which the four terminals have been paired into ports 1-1 & 2-2.

Two ports containing no sources in their branches are called passive ports among them are power transmission lines & transformers.

Two ports containing sources in their branches are called active ports. A voltage (V_1) current assigned to each of the two ports.

The voltage & current at the 1/p terminals are V_1 & I_1 , whereas V_2 & I_2 are specified at the o/p port. It is also assumed that currents are entering into the N/W at the upper terminals 1 & 2 respectively. The variables of the two port N/W are V_1, V_2, I_1, I_2 . Two of them are dependent variable, the other two are independent variable. The no. of possible combinations generated by the four variables taken two at a time is 4C_2 .

$${}^4C_2 = \frac{4!}{2!(4-2)!}$$


$${}^4C_2 = \frac{4!}{(4-2)!}$$

$${}^4C_2 = \frac{4!}{2!}$$

$${}^4C_2 = 6$$

Open circuit Impedance (Z) parameters:-

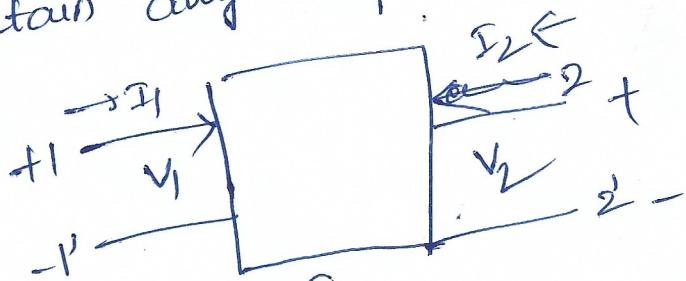A general two-port N/w which does not contain any independent sources is shown in fig(1).



fig(1)

The Z parameters of two-port for the positive directions of voltages & currents may be defined by expressing the port voltages V_1 & V_2 in terms of the current I_1 & I_2 .

Here V_1 & V_2 are dependent variables & I_1 , I_2 are independent variables.

The voltage at port 1-1' is the response produced by the two currents I_1 & I_2 . Thus,

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{--- (1)}$$

$$\text{similarly } V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{--- (2)}$$

Z_{11} , Z_{12} , Z_{21} & Z_{22} are the network functions and are called impedance (Z) parameters and are defined by eqns (1) & (2). These parameters can be represented by matrices.

The matrix equation $[V] = [Z] [I]$

V is the column matrix = $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

Z is the square matrix = $\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$

I is the column matrix = $\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Condition for Reciprocity :-



N/w for deriving condition for reciprocity.

A N/w is said to be reciprocal if the ratio of excitation at one port to response at the other port

Same if excitation & response are interchanged:

- (a) Voltage 'V_s' is applied at the '1/p' port with the output port short-circuited.

$$\text{i.e., } V_1 = V_s$$

$$V_2 = 0$$

$$I_2 = -I_1$$

from the $\begin{pmatrix} V \\ I \end{pmatrix}$ -parameter equation

$$V_s = Z_{11}I_1 - Z_{12}I_2$$

$$0 = Z_{21}I_1 - Z_{22}I_2 \Rightarrow I_1 = \frac{Z_{22}}{Z_{21}}I_2$$

$$V_s = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}}I_2$$

$$\frac{V_s}{I_2} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}}$$

- (b) Voltage V_s is applied at the '0/p' port with the input port short-circuited.

$$\text{i.e., } V_2 = V_s$$

$$V_1 = 0$$


$$I_1 = -I_2$$

from the $\begin{pmatrix} V \\ I \end{pmatrix}$ -parameter equation

$$0 = -Z_{11}I_1 + Z_{12}I_2$$

$$V_s = -Z_{21}I_1 + Z_{22}I_2$$

$$Z_{21} = \frac{Z_{11}}{Z_{12}}I_1$$

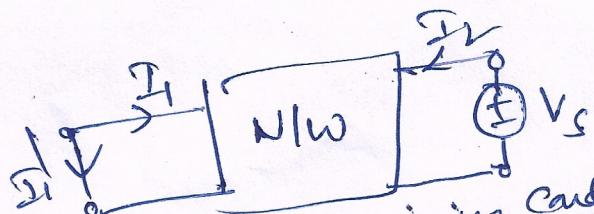

N/w for deriving condition for reciprocity.

$$V_s = -Z_{21}I_1 + Z_{22}\frac{Z_{11}}{Z_{12}}I_1$$

$$\frac{V_s}{I_1} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{12}}$$

For the N/w to be reciprocal

$$\frac{V_s}{I_1} = \frac{V_s}{I_2} \Rightarrow Z_{12} = Z_{21}$$

Condition for symmetry :-

for a network to be symmetrical, the voltage to current ratio at one port should be same as the voltage-to-current ratio at the other port with one of the ports open-circuited.

- (a) when the output port is open-circuited i.e., $I_2 = 0$ from the 2-parameter equation.

$$V_s = Z_{11} I_1$$

$$\frac{V_s}{I_1} = Z_{11}$$

- (b) when the input port is open-circuited i.e., $I_1 = 0$ from the 2-parameter equation.

$$V_s = Z_{22} I_2 \Rightarrow \frac{V_s}{I_2} = Z_{22}$$

For the network to be symmetrical

$$\frac{V_s}{I_1} = \frac{V_s}{I_2} \Rightarrow \boxed{Z_1 = Z_{22}}$$



problems on 2-parameters

1. Test results of a 2-port N/w are

(a) $I_1 = 0.1 \text{ LOA}$, $V_1 = 5.2 \text{ L}50\text{V}$, $V_2 = 4.1 \text{ L}25\text{V}$, with port 2 open circuited

(b) $I_2 = 0.1 \text{ LOA}$, $V_1 = 3.1 \text{ L}80\text{V}$, $V_2 = 4.2 \text{ L}60\text{V}$, with port 1 open circuited

Find 2 parameters.

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{5.2 \text{ L}50}{0.1 \text{ LOA}} = 52 \text{ L}50\text{Ω}$$


$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{4.1 \text{ L}25}{0.1 \text{ LOA}} = 41 \text{ L}25$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{3.1 \text{ L}80}{0.1 \text{ LOA}} = 31 \text{ L}80$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{4.2 \text{ L}60}{0.1 \text{ LOA}} = 42 \text{ L}60$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 52 \text{ L}50 & 31 \text{ L}80 \\ 41 \text{ L}25 & 42 \text{ L}60 \end{bmatrix}$$

2. Find the 2-parameters of the N/w below

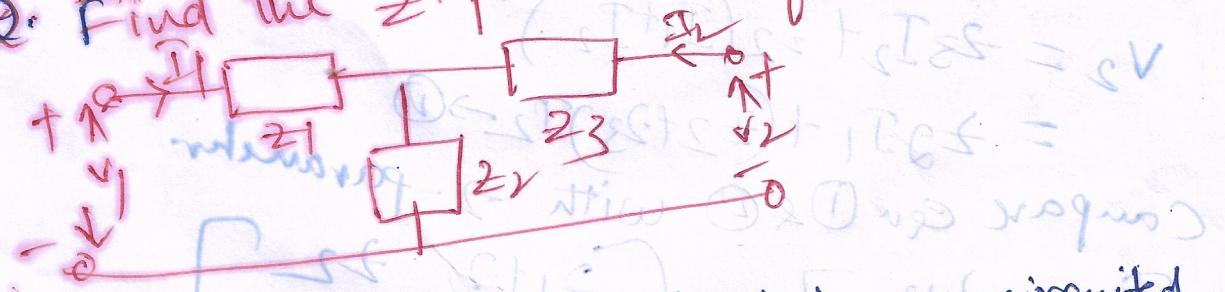

Method 1:-

When the 2nd port is open circuited $I_2 = 0$

$$V_1 = (Z_11 + Z_21)I_1$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = Z_11 + Z_21$$

$$V_2 = Z_22 I_1$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_22$$

CASE 2: When the 'input port' is open circuited i.e $I_F = 0$

Applying KVL to mesh 2

$$V_2 = (Z_{22} + Z_{23}) I_2$$

$$Z_{22} = \frac{V_2}{I_2} \quad |_{I_F=0} = Z_{22} + Z_{23}$$

$$V_1 = Z_{22} I_2$$

$$Z_{12} = \frac{V_1}{I_2} \quad |_{I_F=0} = Z_{12}$$

Hence, the 2-parameter are

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_{11} + Z_{22} & Z_{22} \\ Z_{22} & Z_{22} + Z_{23} \end{bmatrix}$$

Second method:-

KVL to mesh I

$$V_1 = Z_1 I_1 + Z_2 (I_1 + I_2)$$

$$V_1 = (Z_1 + Z_2) I_1 + Z_2 I_2 \rightarrow ①$$

KVL to mesh II


$$V_2 = Z_3 I_2 + Z_2 (I_1 + I_2)$$

$$= Z_2 I_1 + (Z_2 + Z_3) I_2 \rightarrow ②$$

Compare eqn ① & ② with 2-parameter

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Z_1 + Z_2 & Z_2 \\ Z_2 & Z_2 + Z_3 \end{bmatrix}$$

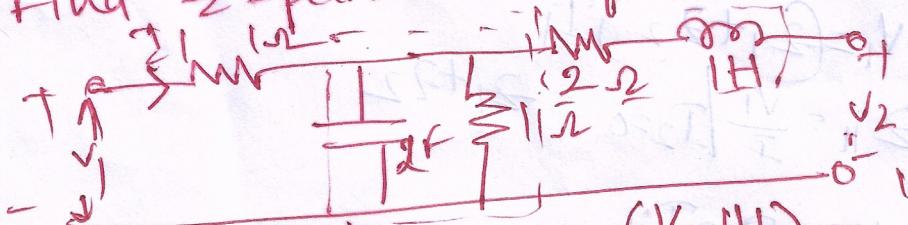3. Find 2-parameters of the network below.




$$Z_1 = 1 \quad Z_2 = (Y_{21} || 1) = \frac{Y_{21} \times 1}{Y_{21} + 1} = \frac{1}{2s+1} \quad Z_3 = s/2$$

$$Z_{11} = \frac{V_1}{I_1} \quad |_{I_2=0} = Z_1 + Z_2 = 1 + \frac{1}{2s+1} = \frac{2s+2}{2s+1}$$

$$Z_{12} = Z_{21} = Z_2 = \frac{1}{2s+1}$$

$$Z_{22} = \frac{V_2}{I_2} \quad |_{I_1=0} = Z_2 + Z_3 = \frac{1}{2s+1} + s/2 = \frac{2s^2 + 5s + 3}{2s+1}$$

4. Find 2 parameters of the network.

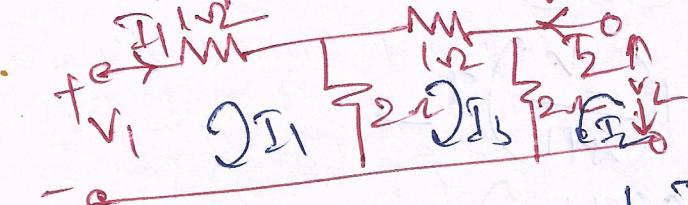

Apply KVL to mesh 1

$$V_1 = 3I_1 - 2I_3 \rightarrow ①$$

Apply KVL to mesh 2

~~$$V_2 = 2I_2 + 2I_3 \rightarrow ②$$~~

Apply KVL to mesh 3

~~$$-2I_1 + 2I_2 + 5I_3 = 0$$~~

$$I_3 = \frac{2I_1 - 2I_2}{5} \rightarrow ③$$

Substitute eqn ③ in ① & ②


$$V_1 = \frac{11}{5}I_1 + \frac{4}{5}I_2 \rightarrow ④$$

$$V_2 = \frac{4}{5}I_1 + \frac{6}{5}I_2 \rightarrow ⑤$$

Compare eqn ④ & ⑤ with 2 parameters

$$\begin{pmatrix} 211 & 212 \\ 221 & 222 \end{pmatrix} = \begin{pmatrix} 11/5 & 4/5 \\ 4/5 & 6/5 \end{pmatrix}$$

5. Find 2 parameters of the network

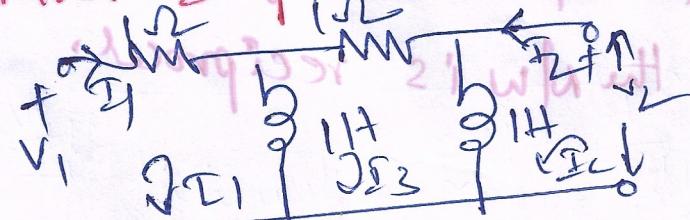

$$V_1 = (s+1)I_1 - sI_3 \rightarrow ①$$

$$V_2 = sI_2 + sI_3 \rightarrow ②$$

$$-sI_1 + sI_2 + (2s+1)I_3 = 0$$

$$I_3 = \frac{sI_1}{2s+1} - \frac{sI_2}{2s+1} \rightarrow ③$$


Substitute eqn ③ in ① & ②

$$V_1 = \left(\frac{s^2 + 3s + 1}{2s+1} \right) I_1 + \left(\frac{5V}{2s+1} \right) I_L$$

$$V_2 = \left(\frac{5V}{2s+1} \right) I_1 + \left(\frac{s^2 + s}{2s+1} \right) I_L$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{s^2 + 3s + 1}{2s+1} & \frac{5V}{2s+1} \\ \frac{5V}{2s+1} & \frac{s^2 + s}{2s+1} \end{bmatrix}$$

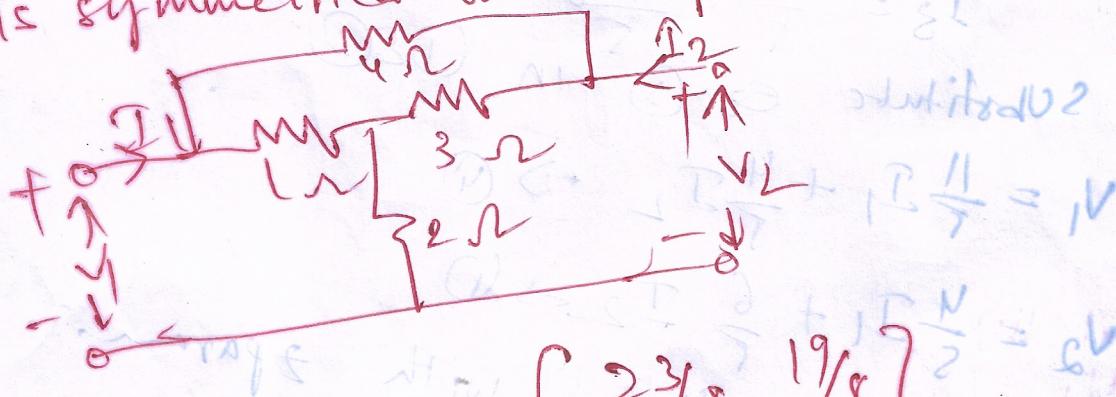6. find the open circuit impedance parameters for the N/w. Determine whether the network is symmetrical and reciprocal.



$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} 23/8 & 19/8 \\ 19/8 & 31/8 \end{bmatrix}$$

*From the above, the N/w is not symmetrical.
Z_{11} \neq Z_{22}, the N/w is not symmetrical.*

Z_{12} = Z_{21}, the N/w is reciprocal.

SHORT-CIRCUIT ADMITTANCE PARAMETERS (Y PARAMETERS)

The Y parameters of two-port network may be defined by expressing the two-port currents I_1 & I_2 in terms of the two-port voltages V_1 & V_2 (Independent Variables)

$$(I_1, I_2) = f(V_1, V_2)$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

In matrix form, we can write

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$[I] = [Y][V]$$

The individual Y parameters for a given N/w can be defined by setting each of the port voltages equal to zero (short circuit the ports)

Case 1:- when the o/p port short circuited i.e., $V_2=0$.

$$Y_{11} = \frac{V_1}{I_1} \quad | \quad V_2=0$$

Where Y_{11} is the driving point admittance with output - port short circuited. It is also called Short - circuit input admittance.

Similarly

$$Y_{21} = \frac{I_2}{V_1} \quad | \quad V_2=0$$

Where Y_{21} is the transfer admittance with o/p port short - circuited. It is also called short - circuit forward transfer admittance.

Case 2:-

When the i/p port is short-circuited i.e., $V_1 = 0$

$$Y_{12} = \frac{I_1}{V_2} \quad | V_1 = 0$$

Where Y_{12} is the transfer admittance with i/p port short-circuited. It is also called short-circuit reverse transfer admittance.


Similarly,

$$Y_{22} = \frac{I_2}{V_2} \quad | V_1 = 0$$

where Y_{22} is the short-circuit driving point admittance with input port short-circuited. It is also called the short circuit output admittance.

As these admittance parameters are measured with either input (or) output port short-circuited, they are called short-circuit admittance parameters.

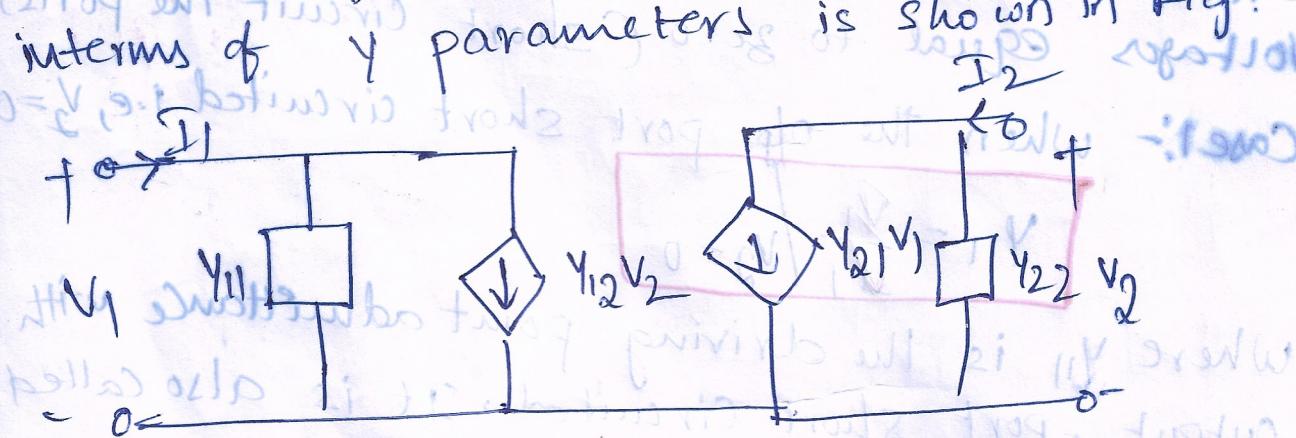The equivalent circuit of the two port N/w in terms of γ parameters is shown in Fig.



Fig① Equivalent C.R.T of the two port Network in terms of γ -parameters.

Condition for Reciprocity:

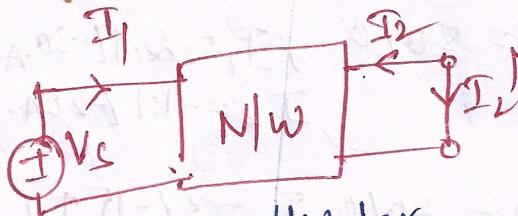


fig 2@ N/w for deriving condition for reciprocity.

From γ parameters

- (a) voltage V_s is applied at input port with output port short-circuited

$$V = V_s \quad I_L = -I_2$$

$$V_2 = 0$$

$$-I_2 = Y_{21} V_s$$

$$\frac{I_2}{V_s} = -Y_{21}$$



fig 2(b) N/w for deriving condition for reciprocity.

from the γ -parameters: $-I_1 = Y_{12} V_s$

- (b) Voltage V_s is applied at output port with the O/p port short-circuited i.e. $V_1 = 0$.

$$V_2 = V_s, I_1 = -I_1, V_1 = 0$$

$$\frac{I_1}{V_s} = -Y_{12}$$

for the N/w to be reciprocal

$$\frac{I_2}{V_s} = \frac{I_1}{V_s} \Rightarrow Y_{12} = Y_{21}$$

Condition for Symmetry:

- (a) when the O/p port short circuited i.e. $V_2 = 0$. from γ parameters

$$I_1 = Y_{11} V_s$$

$$\frac{V_s}{I_1} = Y_{11}$$

- (b) when the I/p port short circuited i.e. $V_1 = 0$. from γ -parameters.

$$I_2 = Y_{22} V_s$$

$$\frac{V_s}{I_2} = Y_{22}$$

for the N/w to be symmetrical $\frac{V_s}{I_1} = \frac{V_s}{I_2}$

problems on γ -parameters

- ① Test results of Δ -port N/W are
- ⓐ port-2 short-circuited; $V_1 = 50\text{V}$, $I_1 = 2.1 \angle -30^\circ \text{A}$
 $I_2 = -1.1 \angle -20^\circ \text{A}$

- (b) port-1 short-circuited: $V_2 = 50\text{V}$, $I_2 = 3 \angle -15^\circ \text{A}$
 $I_1 = -1.1 \angle 20^\circ \text{A}$

$$\gamma_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = 0.042 \angle -30^\circ$$


$$\gamma_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} = -0.022 \angle -20^\circ$$

$$\gamma_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -0.022 \angle -20^\circ$$

$$\gamma_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = 0.06 \angle -15^\circ$$

The Network is reciprocal ~~but~~ not symmetric.


- ② Find γ -parameters for the N/W

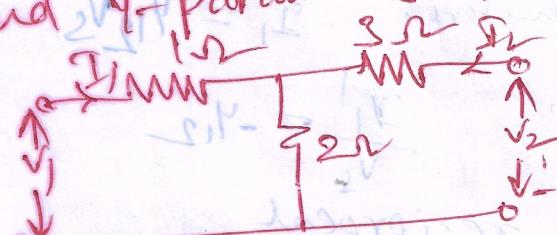

First method:-

Case 1:- When the opp port short-circuited $V_2 = 0$

$$\text{Req} = (3||2) + 1 = \frac{3+2}{3+2} \Omega = \frac{5}{3} \Omega$$

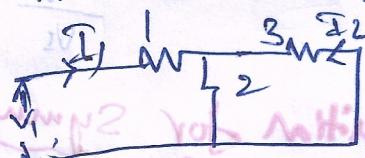


$$V_1 = \frac{I_1}{2} \quad \gamma_{11} = \frac{I_1}{V_1} = \frac{5}{11} \Omega$$

$$I_2 = -\frac{2}{2+3} I_1 = -\frac{2}{5} I_1 = -\frac{2}{5} \times \frac{5}{11} V_1 = -\frac{2}{11} V_1$$

$$\gamma_{21} = \frac{I_2}{V_1} = -\frac{2}{11} \Omega$$

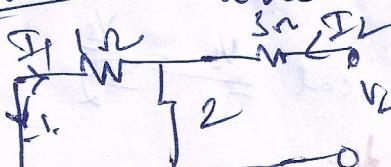Case 2:- when the 1st port short-circuited



$$\text{Req} = (1||2) + 3 = \frac{1}{3} \Omega$$

$$V_2 = \frac{1}{3} I_2 \Rightarrow \gamma_{22} = \frac{I_2}{V_2} \Big|_{V_1=0} = \frac{3}{1} \Omega$$

$$I_1 = -I_2 \times \frac{2}{2+1} = -\frac{2V_2}{3} \times \frac{2}{3} = -\frac{4V_2}{9}$$

$$Y_{12} = \frac{I_1}{V_2} = \frac{-2}{9} V$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} S/11 & -2/11 \\ -2/11 & 3/11 \end{bmatrix}$$

Second method:-

$$I_1 = \frac{V_1 - V_3}{N} = V_1 - \frac{V_3}{N} \rightarrow \textcircled{1}$$

$$I_2 = \frac{V_2 - V_3}{3} = \frac{V_2}{3} - \frac{V_3}{3} \rightarrow \textcircled{2}$$

~~(ii) KCL at node 3.~~

$$\textcircled{1} + \textcircled{2} = \frac{V_3}{2} \rightarrow \textcircled{3}$$

$$\textcircled{3} \quad V_1 - V_3 + \frac{V_2}{3} - \frac{V_3}{3} = \frac{V_3}{2}$$

$$V_3 = \frac{6}{11}V_1 + \frac{2}{11}V_2 \rightarrow \textcircled{4}$$

~~Sub ④ in ①~~


$$I_1 = \frac{V_1 - \frac{2}{11}V_2}{N}$$

$$\text{Sub ④ in ② } I_2 = \frac{-2}{11}V_1 + \frac{3}{11}V_2$$


~~Compare eqns ① & ⑥ with γ - parameter~~

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} S/11 & -2/11 \\ -2/11 & 3/11 \end{bmatrix}$$

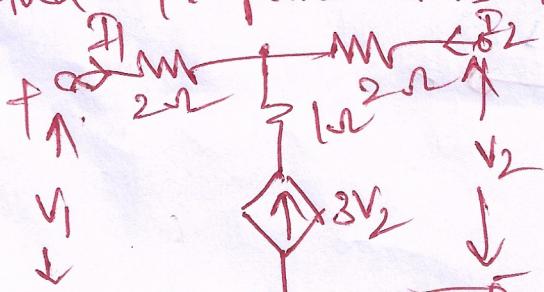3. find γ -parameters of the N/w shown below



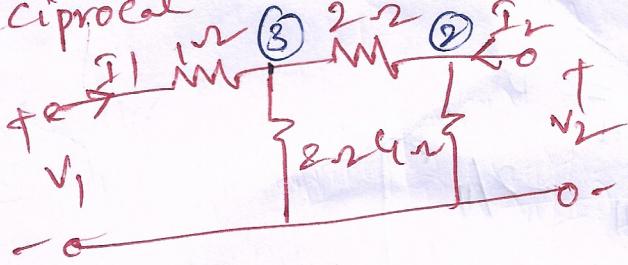4) Determine Y-parameters for the N/w shown below.
Determine whether the N/w is symmetrical and reciprocal.



$$I_1 = \frac{V_1 - V_3}{1} = V_1 - V_3 \rightarrow ①$$

$$I_1 = \frac{V_3}{2} + \frac{V_3 - V_2}{2} \rightarrow ②$$

$$V_1 - V_3 = V_3 - \frac{V_2}{2}$$

$$V_3 = \frac{V_1}{2} + \frac{V_2}{4} \rightarrow ③$$

$$\begin{aligned} I_2 &= \frac{V_2}{4} + \frac{V_2 - V_3}{2} \rightarrow ④ \\ \text{substituting } ③ &= \frac{V_2}{4} + \frac{V_2}{2} - \frac{1}{2} \left[\frac{V_1}{2} + \frac{V_2}{4} \right] \\ &= \cancel{\frac{3V_2}{4}} + \frac{V_1 + 5V_2}{8} \rightarrow ④(i) \end{aligned}$$

Substitute ③ in ①.


$$I_1 = V - \frac{V_1}{2} - \frac{V_2}{4} = \frac{V_1}{2} - \frac{V_1}{4} \rightarrow ④(ii)$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} Y_L - Y_4 & \\ -Y_4 & 5/8 \end{bmatrix}$$

$Y_{11} \neq Y_{22}$ the N/w is not symmetrical.
" " reciprocal.

$$Y_{12} = Y_{21}$$

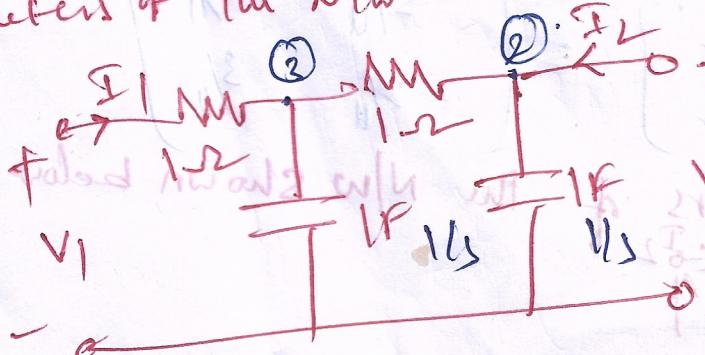5) Determine the short circuit admittance parameters of the N/w below.



$$I_1 = \frac{V_1 - V_3}{1} = V_1 - V_3 \rightarrow \textcircled{1}$$

$$I_1 = \frac{V_3}{V_5} + \frac{V_3 - V_2}{1} \rightarrow \textcircled{2}$$

equate \textcircled{1} & \textcircled{2}

$$V_1 - V_3 = V_3 + V_3 - V_2$$

$$V_3(2+s) = V_1 + V_2$$

$$V_3 = \frac{V_1 + V_2}{s+2} = \frac{V_1}{s+2} + \frac{V_2}{s+2}$$

$$I_2 = \frac{V_2}{1/s} + \frac{V_2 - V_3}{1} \rightarrow \textcircled{3}$$

Substitute eqn \textcircled{3} in \textcircled{4}

$$I_2 = sV_2 + V_2 - \frac{V_1}{s+2} - \frac{V_2}{s+2}$$

$$= -\frac{V_1}{s+2} + V_2 \left[s+1 - \frac{1}{s+2} \right]$$

$$= -\frac{V_1}{s+2} + \frac{s^2 + 3s + 1}{s+2} V_2 \rightarrow \textcircled{4}$$

Substitute eqn \textcircled{2} in \textcircled{1}


$$I_1 = \frac{V_1 - V_3}{s+2} - \frac{V_2}{s+2}$$

$$= \frac{s+1}{s+2} V_1 - \frac{1}{s+2} V_2$$

$$\begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{s+1}{s+2} & -\frac{1}{s+2} \\ -\frac{1}{s+2} & \frac{s^2 + 3s + 1}{s+2} \end{bmatrix}$$

Circuit is reciprocal.

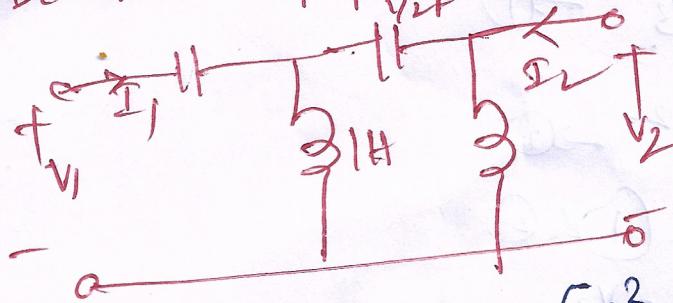
⑥ Determine γ -parameters for the N/w below



Ans:

$$\begin{bmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{bmatrix} = \begin{bmatrix} \frac{s^3 + 2s}{4(s^2 + 1)} & \frac{s^3}{4(s^2 + 1)} \\ -\frac{s^3}{4(s^2 + 1)} & \frac{s^4 + 6s^2 + 4}{4s(s^2 + 1)} \end{bmatrix}$$

⑦ Obtain γ -parameters of the N/w

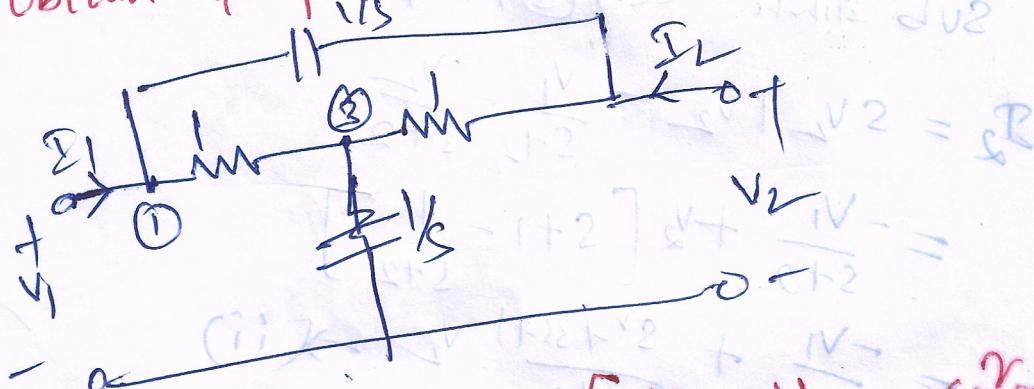

Ans:

$$\begin{bmatrix} \gamma_{11} & \gamma_{12} \\ \gamma_{21} & \gamma_{22} \end{bmatrix} = \begin{bmatrix} \frac{s^2 + 3st + 2}{s + 2} & \frac{(s^2 + st + 1)}{s + 2} \\ \frac{(s^2 + st + 1)}{s + 2} & \frac{s^2 + 3st + 1}{2} \end{bmatrix}$$

$$\begin{bmatrix} s+1 & 1/2 \\ 1/2 & s+2 \end{bmatrix} = \begin{bmatrix} s+1 & 1/2 \\ 1/2 & s+2 \end{bmatrix}$$

• 2009 question 21 part (a)