

JK Flip Flop

JK Flip Flop



The JK Flip Flop removes these two drawbacks of [SR Flip Flop](#).

The [JK flip flop](#) is one of the most used flip flops in digital circuits. The JK flip flop is a universal flip flop having two inputs 'J' and 'K'.


The JK flip flop work in the same way as the SR flip flop work. The JK flip flop has 'J' and 'K' flip flop instead of 'S' and 'R'. The only difference between JK flip flop and SR flip flop is that when both inputs of SR flip flop is set to 1, the circuit produces the invalid states as outputs, but in case of JK flip flop, there are no invalid states even if both 'J' and 'K' flip flops are set to 1.

The JK Flip Flop is a gated SR flip-flop having the addition of a clock input circuitry. The invalid or illegal output condition occurs when both of the inputs are set to 1 and are prevented by the addition of a clock input circuit. So, the JK flip-flop has four possible input combinations, i.e., 1, 0, "no change" and "toggle". The symbol of JK flip flop is the same as **SR Bistable Latch** except for the addition of a clock input.


Block Diagram:

  


Circuit Diagram:

 

+ve edge triggered JK flip flop

 


Clock	J	K	Q	Q(t+1)
1	0	0	0	0

 


Clock	J	K	Q	Q(t+1)
1	0	0	1	1

Clock	J	K	Q	Q(t+1)
1	0	0	0	0
1	0	0	1	1

} No change

 


Clock	J	K	Q	Q(t+1)
1	0	1	0	0

 


Clock	J	K	Q	Q(t+1)
↓	0	1	1	0

clock	J	K	Q	Q(t+1)
↓	0	1	0	0
↑	0	1	1	0


} Reset

 

Clock	J	K	Q	Q(t+1)
↑	1	0	0	1

 


Clock	J	K	Q	Q(t+1)
↑	1	0	1	1

 


Clock	J	K	Q	Q(t+1)
\uparrow	1	0	1	1

clock	J	K	Q	Q(t+1)
\uparrow	1	0	0	1
\uparrow	1	0	1	1

set

 

Clock	J	K	Q	Q(t+1)
\uparrow	1	1	0	1

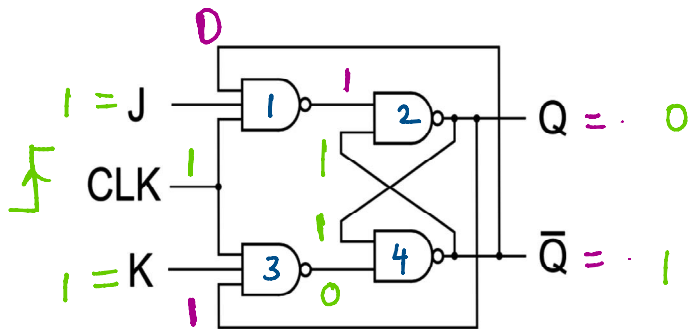


Clock	J	K	Q	Q(t+1)
\uparrow	1	1	1	0

clock	J	K	Q	Q(t+1)
\uparrow	1	1	0	1
\uparrow	1	1	1	0


Toggle

+ve edge triggered JK flip flop

 

Clock	J	K	Q	Q(t+1)	State
↓	0	0	0	0	No change state
↓	0	0	1	1	
↓	0	1	0	0	
↓	0	1	1	1	
↓	1	0	0	0	
↓	1	0	1	1	
↓	1	1	0	0	
↓	1	1	1	1	

+ve edge triggered JK

 

		I/p		O/p		
	Clock	J	K	Q	Q(t+1)	State
	↓	x	x	x	No change	
0	↑	0	0	0	0	No change
1	↑	0	0	1	1	
2	↑	0	1	0	0	Reset
3	↑	0	1	1	0	
4	↑	1	0	0	1	Set
5	↑	1	0	1	1	
6	↑	1	1	0	1	Toggle
7	↑	1	1	1	0	

$$Q(t+1) = J\bar{Q} + \bar{K}Q$$

Let us take $J=1, K=0, Q=0$

$$Q(t+1) = ?$$

$$Q(t+1) = J \bar{Q} + \bar{K} Q$$

$$1 \cdot 1 + 1 \cdot 0$$

$$1 + 0 = 1 \checkmark$$

Let us take $J=K=1$ & $Q=1$ then determine $Q(t+1)$

Characteristic equation for JK $\Rightarrow Q(t+1) = J \bar{Q} + \bar{K} Q$

$$1 \cdot 0 + 0 \cdot 1$$

$$0 + 0 = 0$$

$$Q(t+1) = 0 \checkmark$$

JK flip flop characteristic

Characteristic equation can be derived from the truth table

$Q(t+1)$

	$K \bar{Q}$	00	01	11	10
J	0	0	1	0	0
	1	1	1	0	1


$J \bar{Q}$

$\rightarrow \bar{K} Q$

$$Q(t+1) = J \bar{Q} + \bar{K} Q \checkmark$$

Propagation delay :- Time taken for the ckt

 
@ to change its o/p, ~~app~~ after application of i/p



$$A=1, B=1 \Rightarrow \overline{AB} = 0 \checkmark$$

Suddenly A=0, B=1

Then I will get my
o/p after 10 nsec

 


propagation time for AND is 50 nsec


JK flip flop, propagation delay $\Delta t = 10 \text{ nsec}$
clock pulse width $t_p = 40 \text{ nsec}$



$$t_p > \Delta t \checkmark$$

 

+ve edge triggered JK flip flop

 

If $t_p > \Delta t \rightarrow$ Race around condition


$$V_{in} = 5V \Rightarrow \frac{dV_{in}}{dt} = 0$$



Spike wave form (Edge triggered clock)



Differentiator circuit

 

RACE AROUND CONDITION

- The race around condition occurs if $t_p \gg \Delta t$.

clock pulse width t_h


↓ propagation delay

How we can avoid race-around condition?

We can avoid race around condition by the following way.

1. If $t_p < \Delta t$.
2. By using edge triggering flip-flop.
3. By using Master-Slave JK Flip-flop.

Edge triggered JK flip flop

 



$$\Delta t = 10 \text{ nsec}$$

$$t_p = 5 \text{ nsec}$$

1st clock
 $J=K=1$ $Q=0$
 $Q(t+1) = 1$

2nd clock
 $J=0, K=0, Q=1, Q(t+1)=0$

  - when $J=K=1$, output toggles recursively during active period of clock pulse
- This leads to unpredictable output state after active period of clock pulse
- This condition is known as race around condition



- Solution to race around condition

- Master slave FF: that gives a single trigger at slave output. However race around condition occurs in Master.
- **Edge triggered FF**: flip-flop triggers the 'edge' of clock pulse

1st clock

$$J=0, K=0, Q=0$$

$$Q(t+1) = 0$$

2nd clock

$$J=K=1, Q=0$$

$$Q(t+1) = \text{toggle}$$

3rd clock

$$J=K=0, Q=0$$

$$Q(t+1) = 1$$