

Two – Port Networks

Unit- IV

Analysis and Design of Small Signal Low Frequency BJT Amplifiers:

Transistor Hybrid model, Determination of h-parameters from transistor characteristics, Typical values of h-parameters in CE, CB and CC configurations, Transistor amplifying action, Analysis of CE, CC, CB Amplifiers and CE Amplifier with emitter resistance, low frequency response of BJT Amplifiers, effect of coupling and bypass capacitors on CE Amplifier.

Two Port Networks

Generalities:

The standard configuration of a two port:



The network ?

The voltage and current convention ?

* notes

Two Port Networks

Network Equations:

Impedance
Z parameters

$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

Admittance
Y parameters

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

Transmission
A, B, C, D
parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

Hybrid
H parameters

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

• Of these four variables V_1 , V_2 , i_1 and i_2 , two can be selected as independent variables and the remaining two can be expressed in terms of these independent variables. This leads to various two part parameters out of which the following three are more important.

Hybrid Parameters or h-parameters

If the input current i_1 and output Voltage V_2 are takes as independent variables,
Then input voltage V_1 and output current i_2 can be written as dependant variable:

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

The four hybrid parameters : h_{11} , h_{12} , h_{21} and h_{22} are defined as follows.

- $h_{11} = [V_1 / i_1]$ with $V_2 = 0$, : I/P Resistance with output port short circuited.
- $h_{12} = [V_1 / V_2]$ with $i_1 = 0$, : reverse voltage transfer ratio with i/p port open circuited.
- $h_{21} = [i_2 / i_1]$ with $V_2 = 0$, : Forward current gain with output part short circuited.
- $h_{22} = [i_2 / V_2]$ with $i_1 = 0$, : Output admittance with input part open circuited.

The dimensions of h – parameters are as follows:

h_{11} - Ω

h_{12} – dimension less.

h_{21} – dimension less.

h_{22} – mhos

as the dimensions are not alike, (i.e) they are hybrid in nature, and these parameters are called as hybrid parameters.

Two Port Networks

Hybrid Parameters:

The equations for the hybrid parameters are:

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$h_{11} = \frac{V_1}{I_1} \quad | \quad V_2 = 0$$

$$h_{12} = \frac{V_1}{V_2} \quad | \quad I_1 = 0$$

$$h_{21} = \frac{I_2}{I_1} \quad | \quad V_2 = 0$$

$$h_{22} = \frac{I_2}{V_2} \quad | \quad I_1 = 0$$

Hybrid Parameters:

The equations for the hybrid parameters are:

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$I_2 = h_{21} i_1 + h_{22} V_2$$

$$\downarrow \\ V_1 = h_i i_1 + h_r V_2$$

$$\downarrow \\ I_2 = h_f i_1 + h_o V_2$$


$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_i & h_r \\ h_f & h_o \end{bmatrix} \begin{bmatrix} i_1 \\ V_2 \end{bmatrix}$$

$$h_i = \frac{V_1}{I_1} \quad | \quad V_2 = 0$$

$$h_r = \frac{V_1}{V_2} \quad | \quad I_1 = 0$$

$$h_f = \frac{I_2}{I_1} \quad | \quad V_2 = 0$$

$$h_o = \frac{I_2}{V_2} \quad | \quad I_1 = 0$$

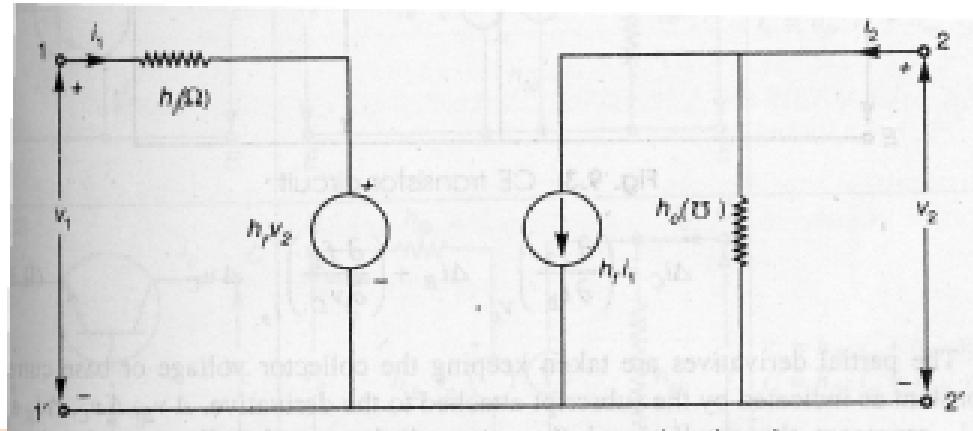

Transistor Hybrid Model CE Configuration

In common emitter transistor configuration, the input signal is applied between the base and emitter terminals of the transistor and output appears between the collector and emitter terminals. The input voltage (V_{be}) and the output current (i_c) are given by the following equations:

$$V_{be} = h_{ie} \cdot i_b + h_{re} \cdot V_c$$


$$i_c = h_{fe} \cdot i_b + h_{oe} \cdot V_c$$

$$h_{ie} = \text{input resistance} = \left. \frac{\Delta v_{be}}{\Delta i_b} \right|_{v_{ce} = \text{constant}}$$

$$h_{re} = \text{reverse transfer voltage ratio} = \left. \frac{\Delta v_{be}}{\Delta v_{ce}} \right|_{i_b = \text{constant}}$$


$$h_{fe} = \text{forward transfer current ratio} = \left. \frac{\Delta i_c}{\Delta i_b} \right|_{v_{ce} = \text{constant}}$$

$$h_{oe} = \text{output conductance} = \left. \frac{\Delta i_c}{\Delta v_{ce}} \right|_{i_b = \text{constant}}$$

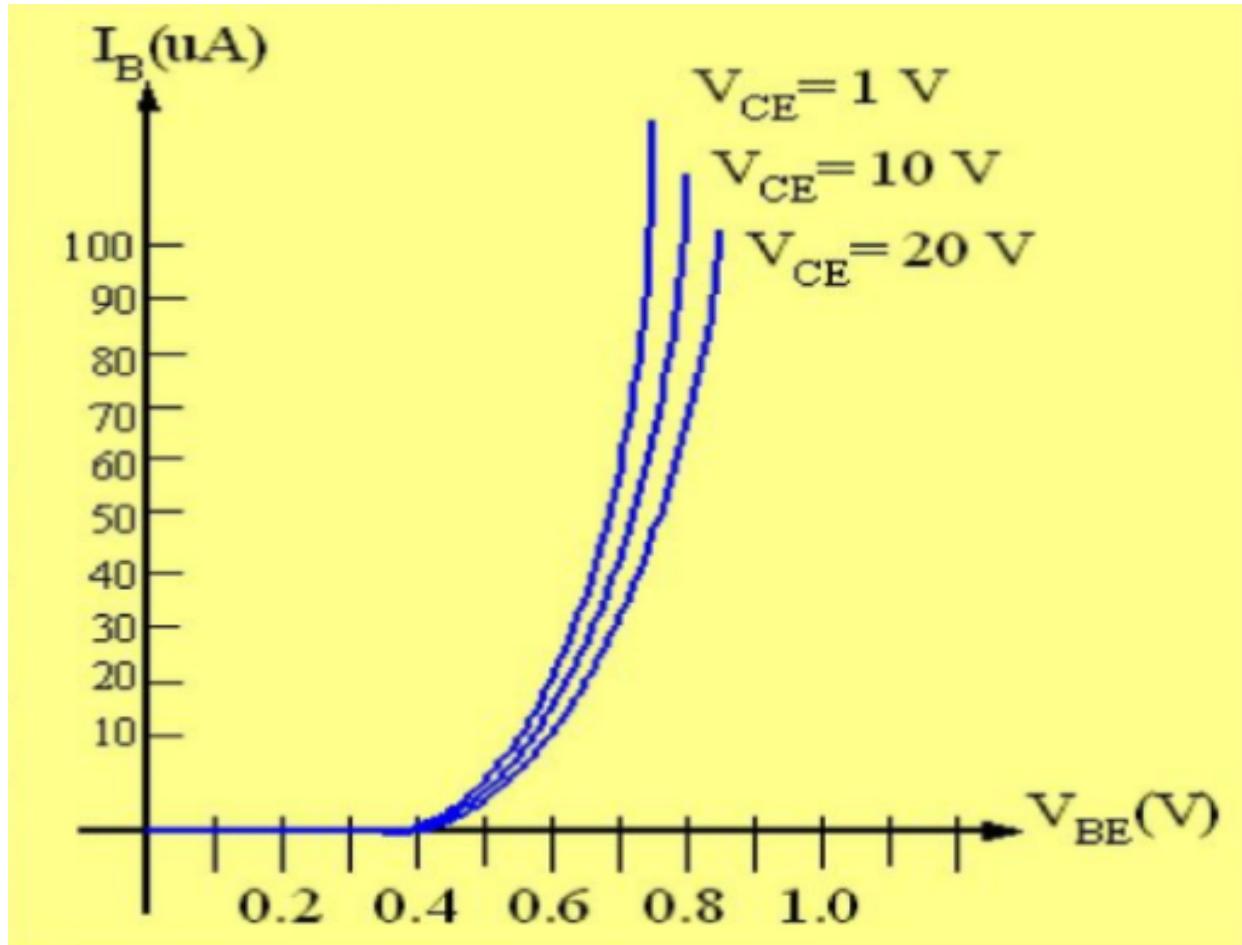



$$h_{ie} = \text{input resistance} = \left. \frac{\Delta v_{be}}{\Delta i_b} \right|_{v_{ce} = \text{constant}}$$

$$h_{re} = \text{reverse transfer voltage ratio} = \left. \frac{\Delta v_{be}}{\Delta v_{ce}} \right|_{i_b = \text{constant}}$$

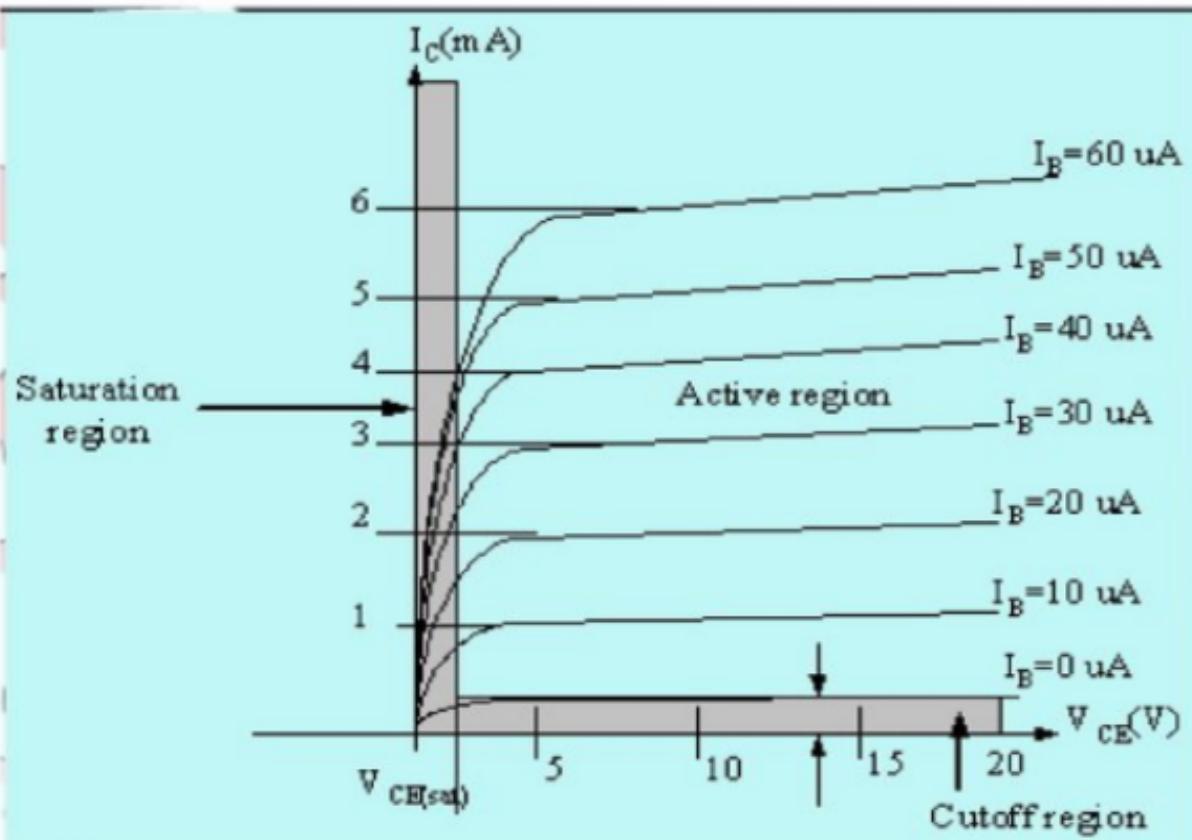

$$h_{fe} = \text{forward transfer current ratio} = \left. \frac{\Delta i_c}{\Delta i_b} \right|_{V_{ce} = \text{constant}}$$



$$h_{oe} = \text{output conductance} = \left. \frac{\Delta i_c}{\Delta V_{ce}} \right|_{i_b = \text{constant}}$$

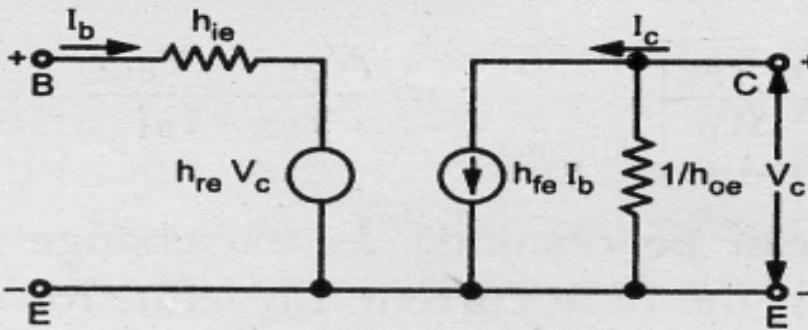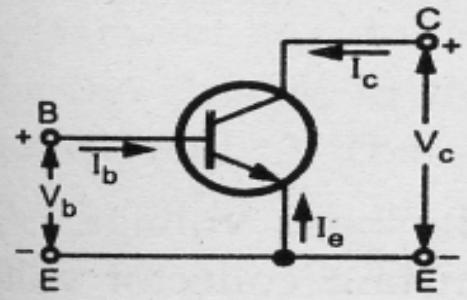

CE

$$V_b = h_{ie} I_b + h_{re} V_c$$



$$I_c = h_{fe} I_b + h_{oe} V_c$$

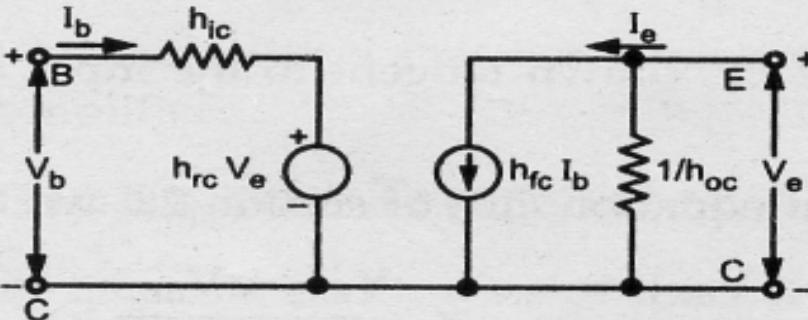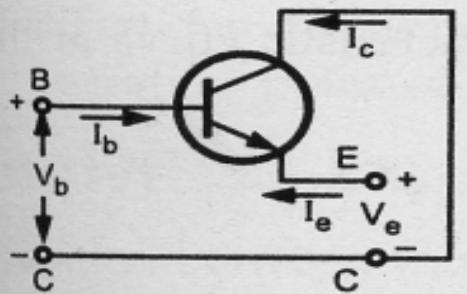

CC

$$V_b = h_{ic} I_b + h_{rc} V_e$$

$$I_e = h_{fc} I_b + h_{oc} V_e$$

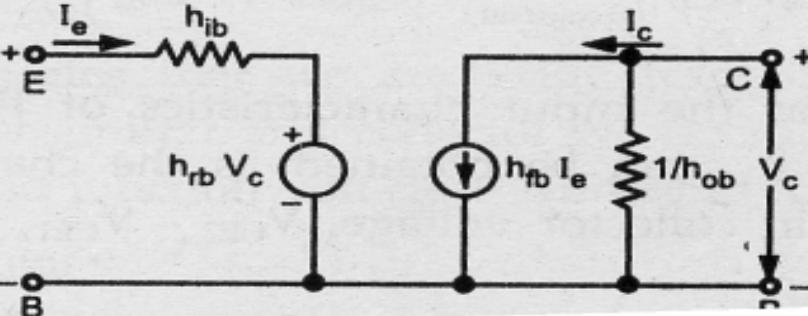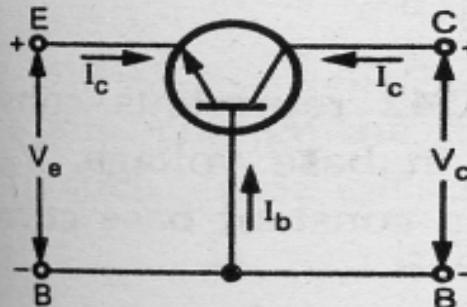

CB

$$V_e = h_{ib} I_e + h_{rb} V_c$$

$$I_c = h_{fb} I_e + h_{ob} V_c$$

Transistor Hybrid Model

Use of h – parameters to describe a transistor have the following advantages:

- h – parameters are real numbers up to radio frequencies .
- They are easy to measure
- They can be determined from the transistor static characteristics curves.
- They are convenient to use in circuit analysis and design.
- Easily convert able from one configuration to other.
- Readily supplied by manufacturiers.


Procedure for DC and AC analysis

The process of dc analysis is as follows :

1. Reduce ac signal source to zero.
2. Open all capacitors.
3. Analyse the resulting *dc equivalent circuit*.


The process of ac analysis is as follows :

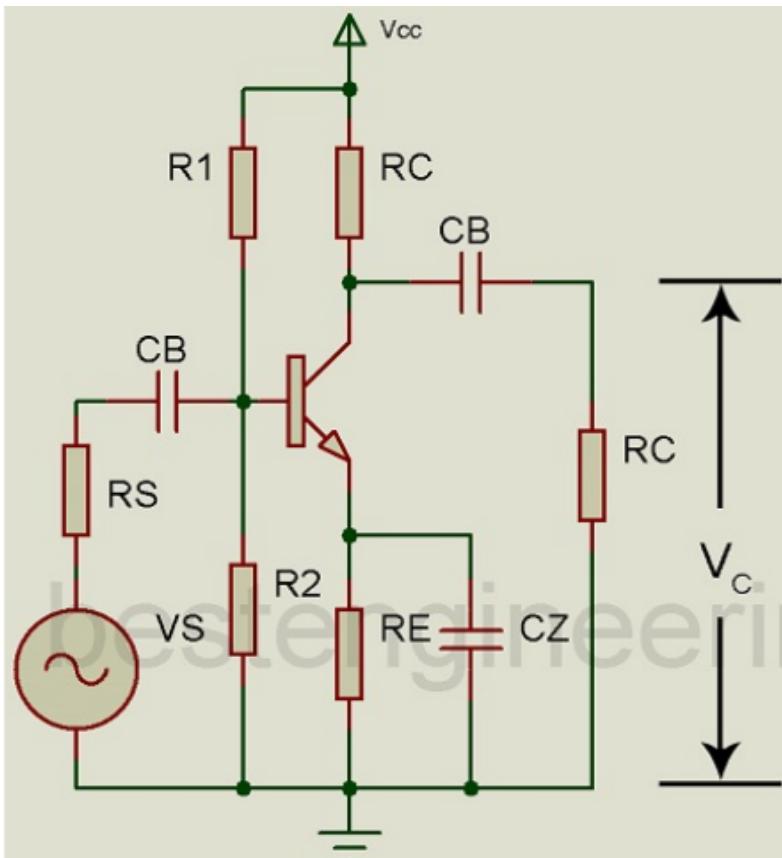1. Reduce the dc source to zero.
2. Short all capacitors.
3. Analyse the resulting *ac equivalent circuit*.




(a) Circuit of CE Amplifier

CE Amplifier

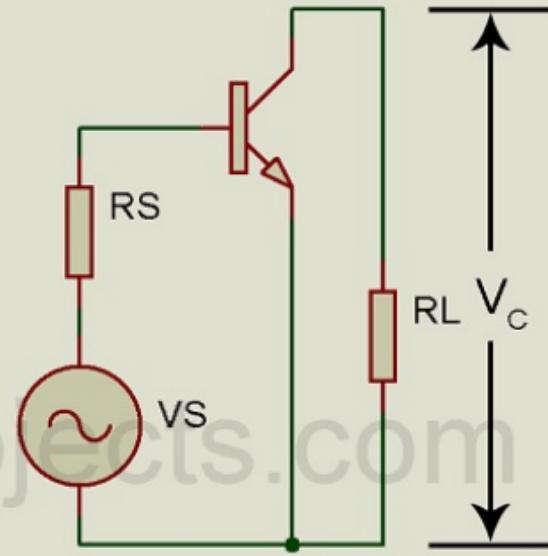


(b) a.c. equivalent circuit

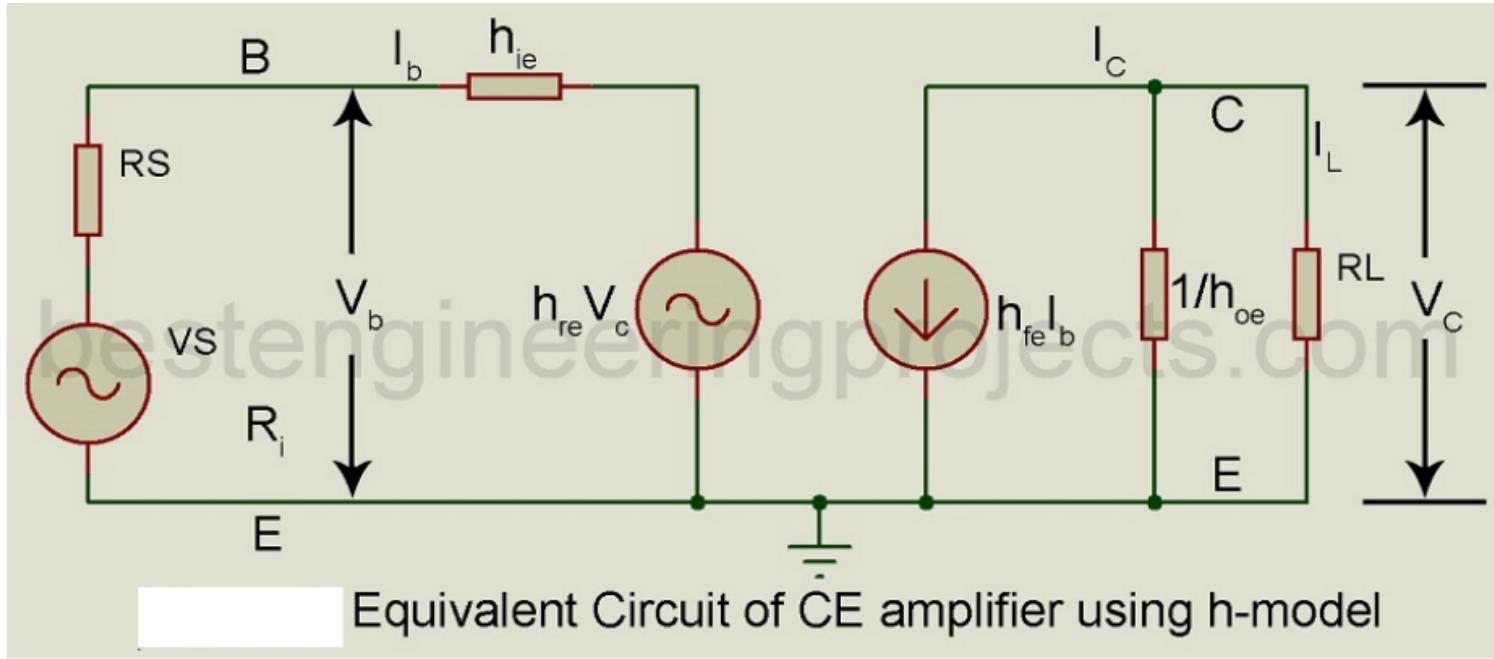

$$A_I = \frac{I_L}{I_b} = -\frac{I_c}{I_b} \quad I_c = h_{fe} \times I_b + h_{oe} \times V_c \quad V_c = I_L \times R_L = -I_c \times R_L$$

$$I_c = h_{fe}I_b - h_{oe} \times I_c \times R_L \text{ or } (1 + h_{oe} \times R_L)I_c = h_{fe} \times I_b$$

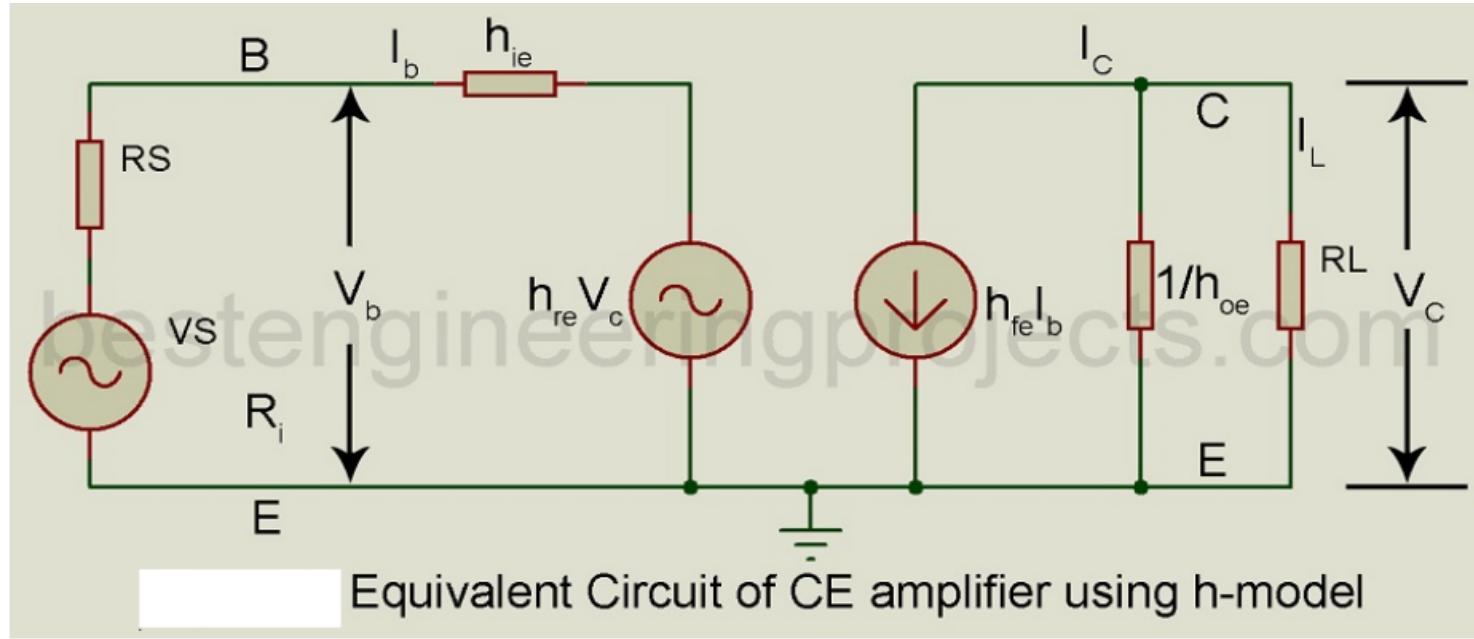Hence Current Gain A_I is $A_I = -\frac{I_c}{I_b} = -\frac{h_{fe}}{1 + h_{oe} \times R_L}$



Equivalent Circuit of CE amplifier using h-model

$$R_i = \frac{V_b}{I_b}$$


$$V_b = h_{ie} \times I_b + h_{re} \times V_c$$

$$V_c = -I_c \times R_L = A_I I_b R_L$$

$$V_b = h_{ie} \times +h_{re} A_I I_b R_L$$

$$R_i = \frac{V_b}{I_b} = h_{ie} + h_{re} A_I R_L = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + Y_L}$$


$$Y_L = \frac{1}{R_L}$$

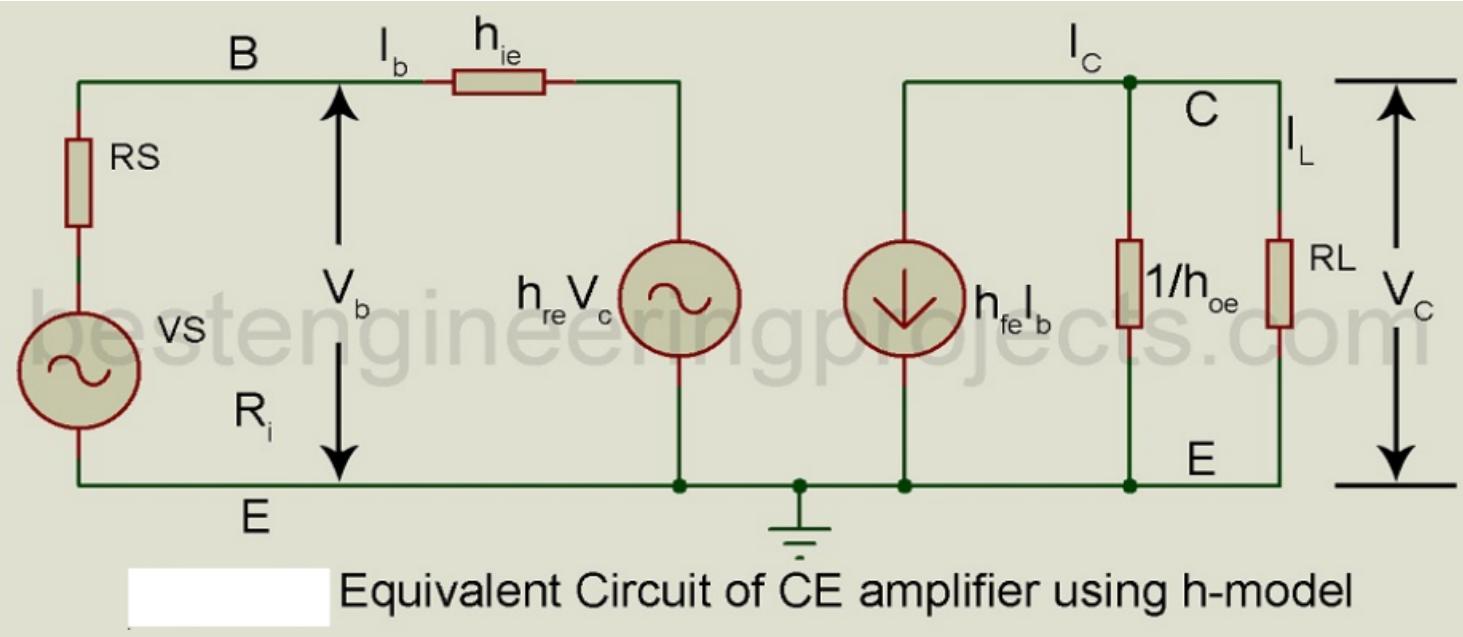

Equivalent Circuit of CE amplifier using h-model

Voltage Gain or Voltage Amplification:
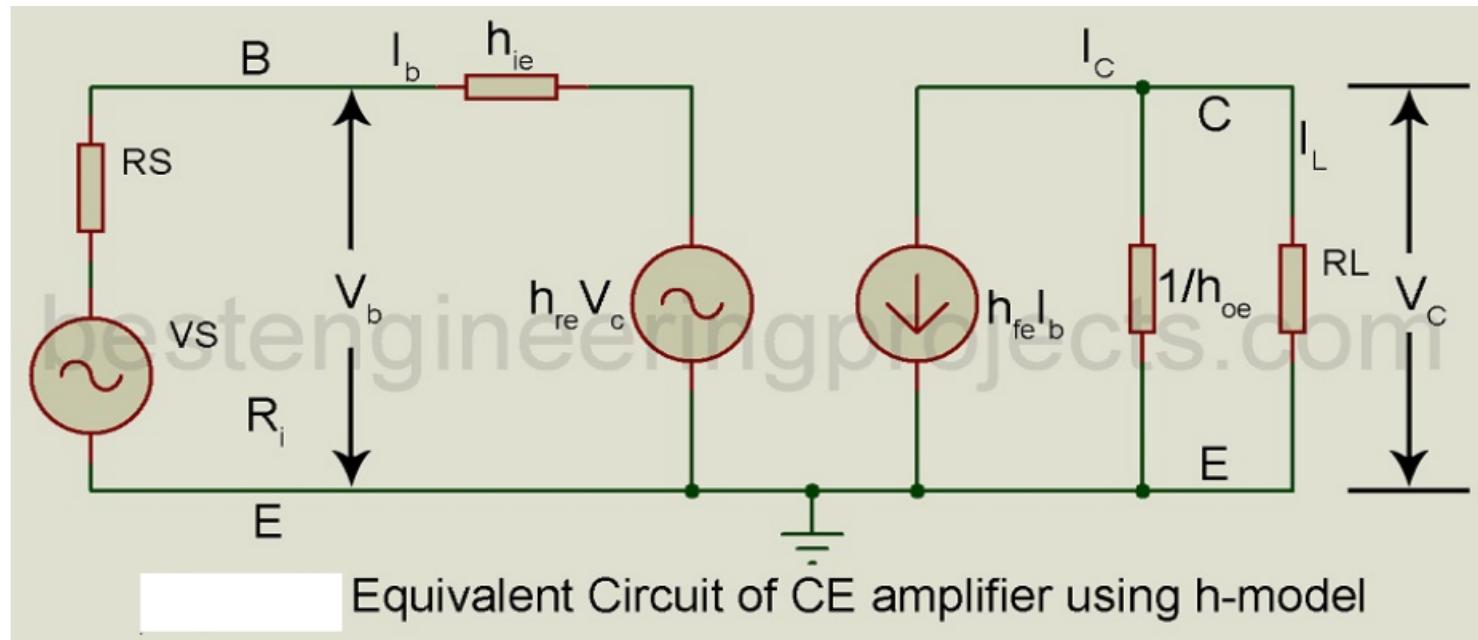
$$A_v = \frac{V_c}{V_b} = -\frac{I_c R_L}{I_b R_i} = \frac{A_I R_L}{R_i}$$



Equivalent Circuit of CE amplifier using h-model

Output Admittance Y_0 :

$$Y_0 = \frac{I_c}{V_c} \quad \text{With } V_s = 0 \quad Y_0 = h_{fe} \times \frac{I_b}{V_c} + h_{oe} \quad \text{But with } V_s = 0, \text{ Figure gives } (R_s + h_{ie}) I_b + h_{re} V_c = 0$$



$$\frac{I_b}{V_c} = -\frac{h_{re}}{h_{ie} + R_s}$$

$$Y_0 = h_{oe} - \frac{h_{fe} \times h_{re}}{h_{ie} + R_s}$$

$$R_0 = \frac{1}{Y_0}$$

In the calculation of Y_0 , R_L has been considered external to the amplifier. If we include R_L in parallel with R_0 , we get the output terminal impedance Z_t given by

$$Z_t = \frac{R_0 R_L}{R_0 + R_L}$$

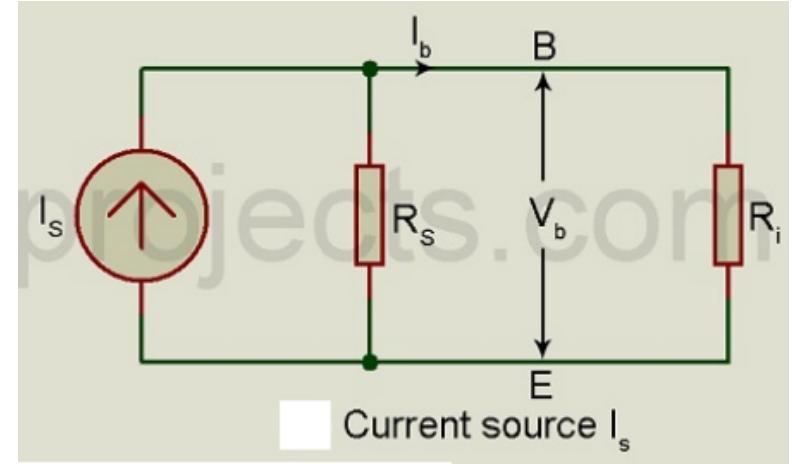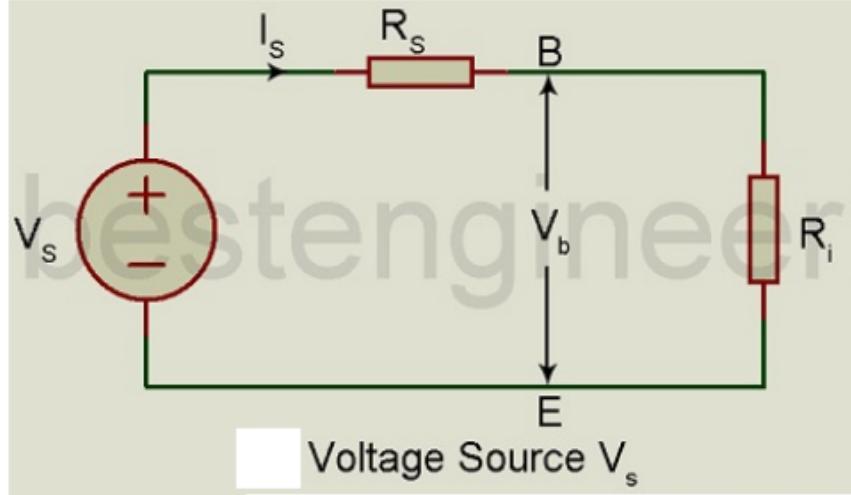

Overall Voltage Gain Considering R_s :

$$A_{VS} = \frac{V_c}{V_s} = \frac{V_c}{V_b} \times \frac{V_b}{V_s} = A_V = \frac{V_b}{V_s} \quad V_b = V_s \times \frac{R_i}{R_i + R_s}$$

$$A_{VS} = A_v \times \frac{R_i}{R_i + R_s}$$

If $R_s = 0$, then $A_{VS} = A_V$. Thus, A_V forms a special case of A_{VS} with $R_s = 0$.

Overall Current Gain Considering R_s :

$$A_{IS} = \frac{I_L}{I_s} = \frac{-I_C}{I_b} \times \frac{I_b}{I_s} = A_I \times \frac{I_b}{I_s}$$

$$I_b = I_s \frac{R_s}{R_s + R_i}$$

$$A_{VS} = A_{IS} \times \frac{R_i}{R_s}$$

$$A_I = -\frac{h_{fe}}{1+h_{oe}\times R_L}$$

$$A_V=\frac{A_I\times R_L}{R_i}$$

$$R_i=h_{ie}+h_{re}\times A_I \times R_L$$




$$A_{VS}\frac{A_V R_i}{R_i + R_s}$$

$$Y_0=h_{oe}-\frac{h_{re}h_{fe}}{h_{ie}+R_s}=\frac{1}{Z_0}$$

$$A_{IS}=\frac{A_I R_s}{R_i+R_s}$$


<i>Parameter</i>	<i>CE</i>	<i>CC</i>	<i>CB</i>
h_i	1,100 Ω	1,100 Ω	22 Ω
h_r	2.5×10^{-4}	1	3×10^{-4}
h_f	50	-51	-0.98
h_o	$25 \mu A/V$	$25 \mu A/V$	$0.49 \mu A/V$

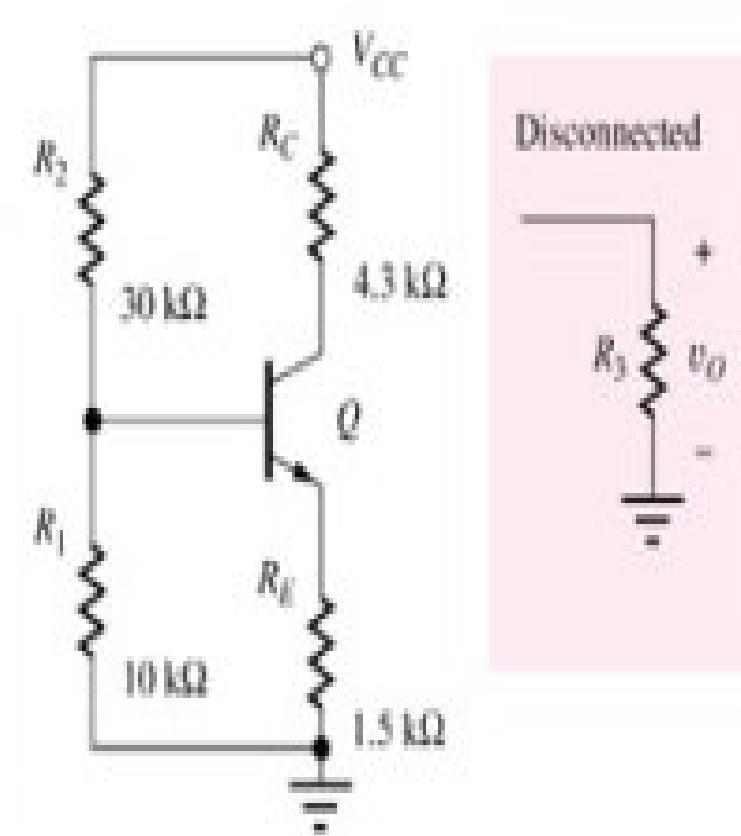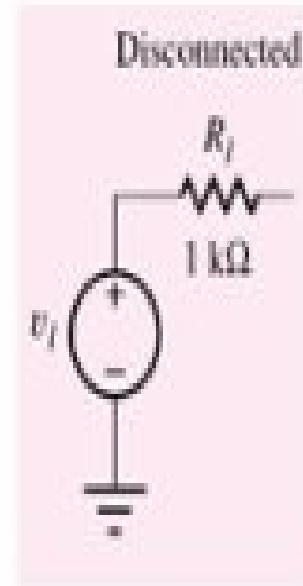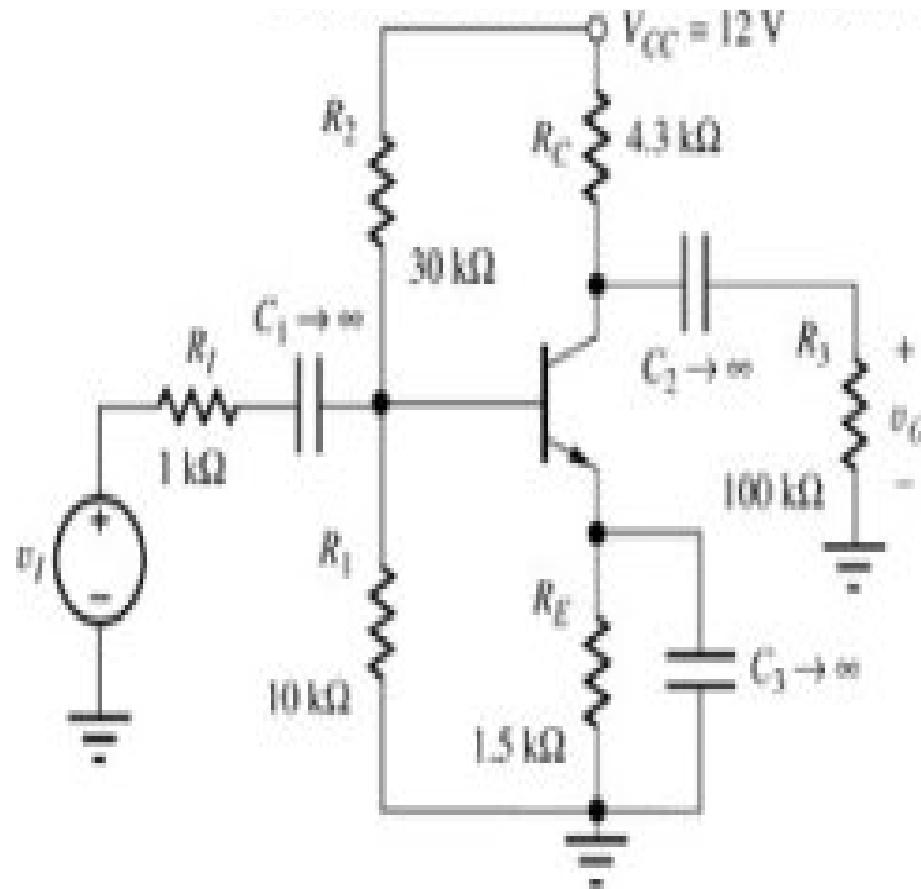D C Equivalent for the BJT Amplifier (Step1)




AC Equivalent Circuit

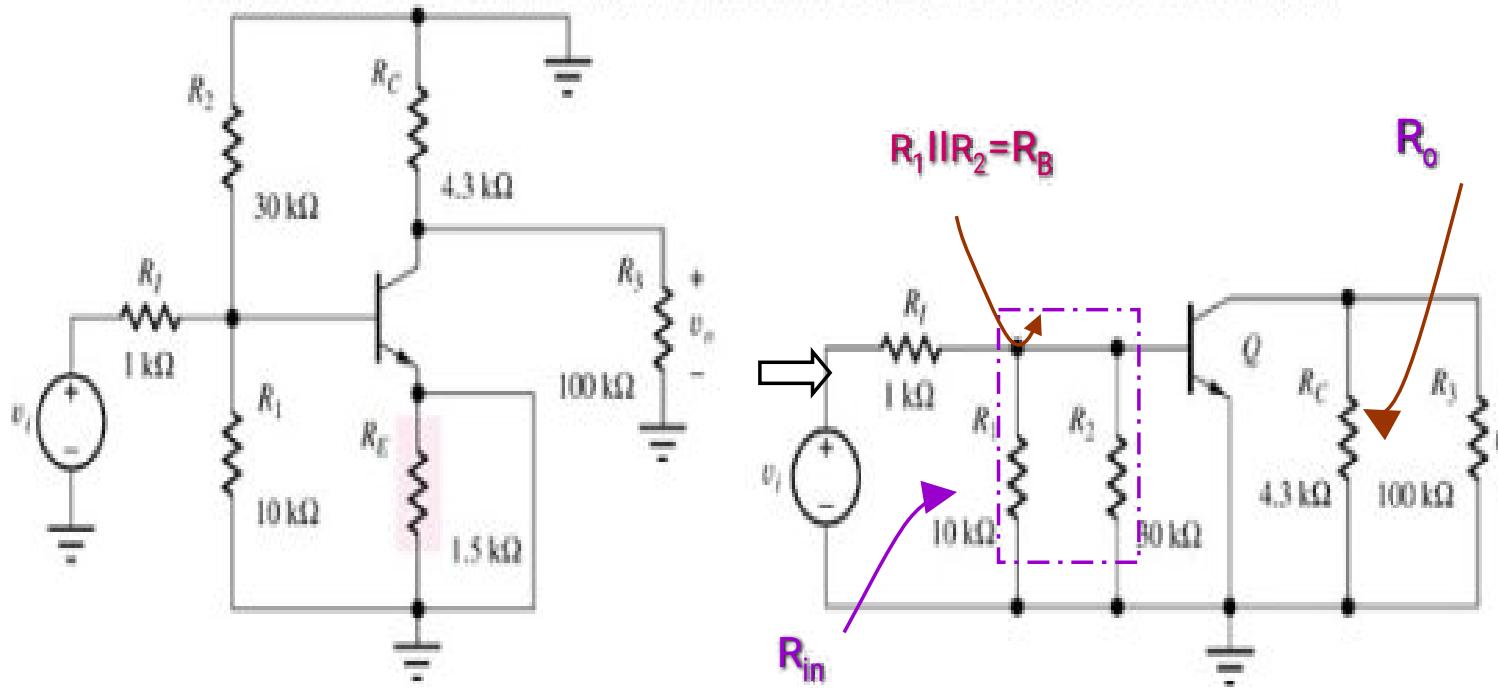A C Equivalent for the BJT Amplifier (Step 2)



- Coupling capacitor C_C and Emitter bypass capacitor C_E are replaced by short circuits.
- DC voltage supply is replaced with short circuits, which in this case is connected to ground.

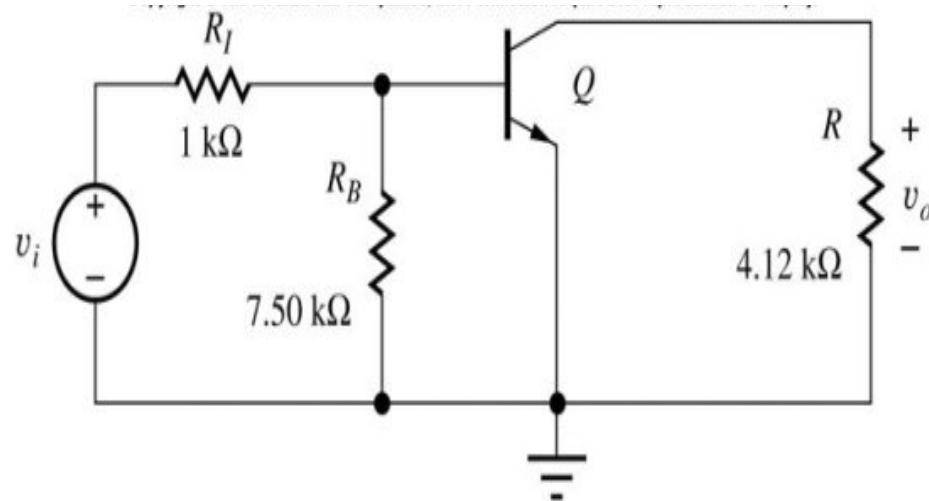A C Equivalent for the BJT Amplifier (continued)



All externally connected capacitors are assumed as short circuited elements for ac signal


$$R_B = R_1 \parallel R_2 = 10\text{k}\Omega \parallel 30\text{k}\Omega$$

$$R = R_C \parallel R_3 = 4.3\text{k}\Omega \parallel 100\text{k}\Omega$$

- By combining parallel resistors into equivalent R_B and R , the equivalent AC circuit above is constructed. Here, the transistor will be replaced by its equivalent small-signal AC model (to be developed).


A C Analysis of CE Amplifier

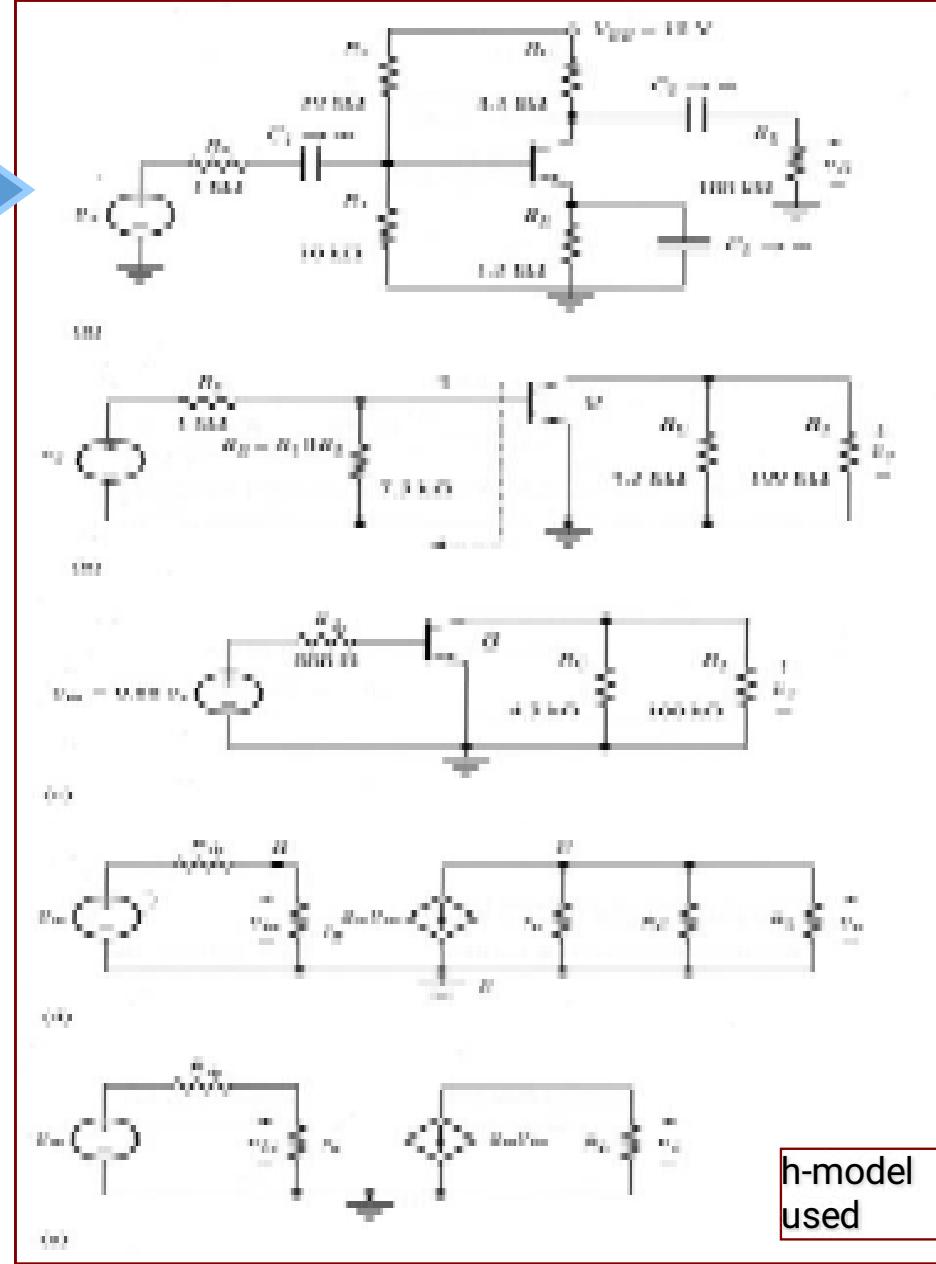- 1) Determine DC operating point and calculate small signal parameters
 - 2) Draw the AC equivalent circuit of Amp.
 - DC Voltage sources are shorted to ground
 - DC Current sources are open circuited
 - capacitors are short circuits
 - inductors are open circuits
 - 3) Find the simplified form of network which is a two port network
 - 4) Replace transistor with small signal model
 - 5) Simplify the circuit as much as necessary.
- Steps to Analyze a Transistor Amplifier
- 6) Calculate the small signal parameters and gain etc.




BJT Small Signal Analysis


Common Emitter Fixed Bias

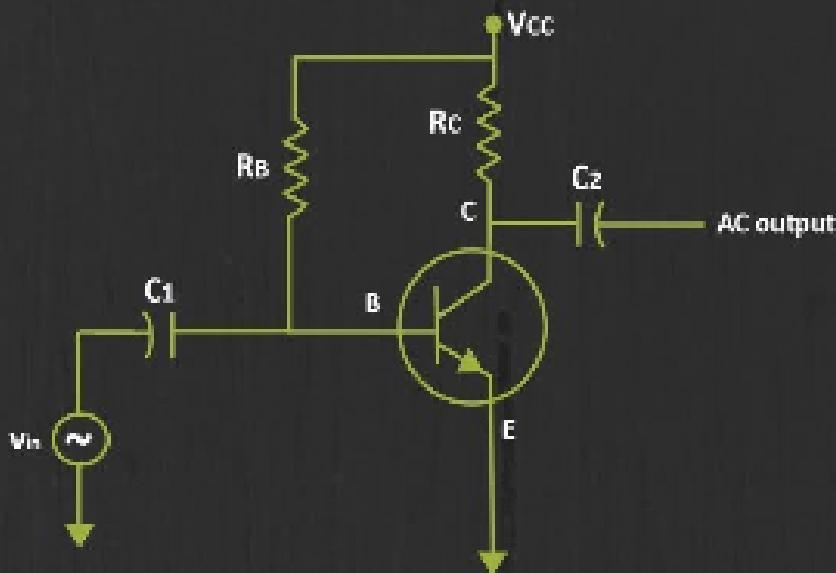

Small Signal Equivalent Circuit

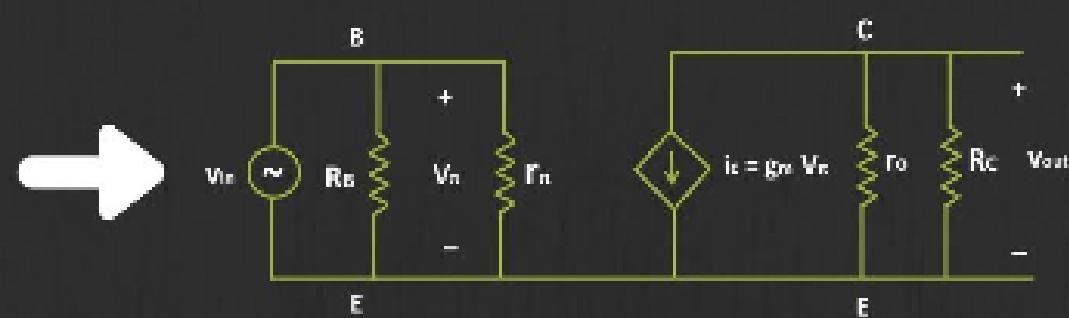

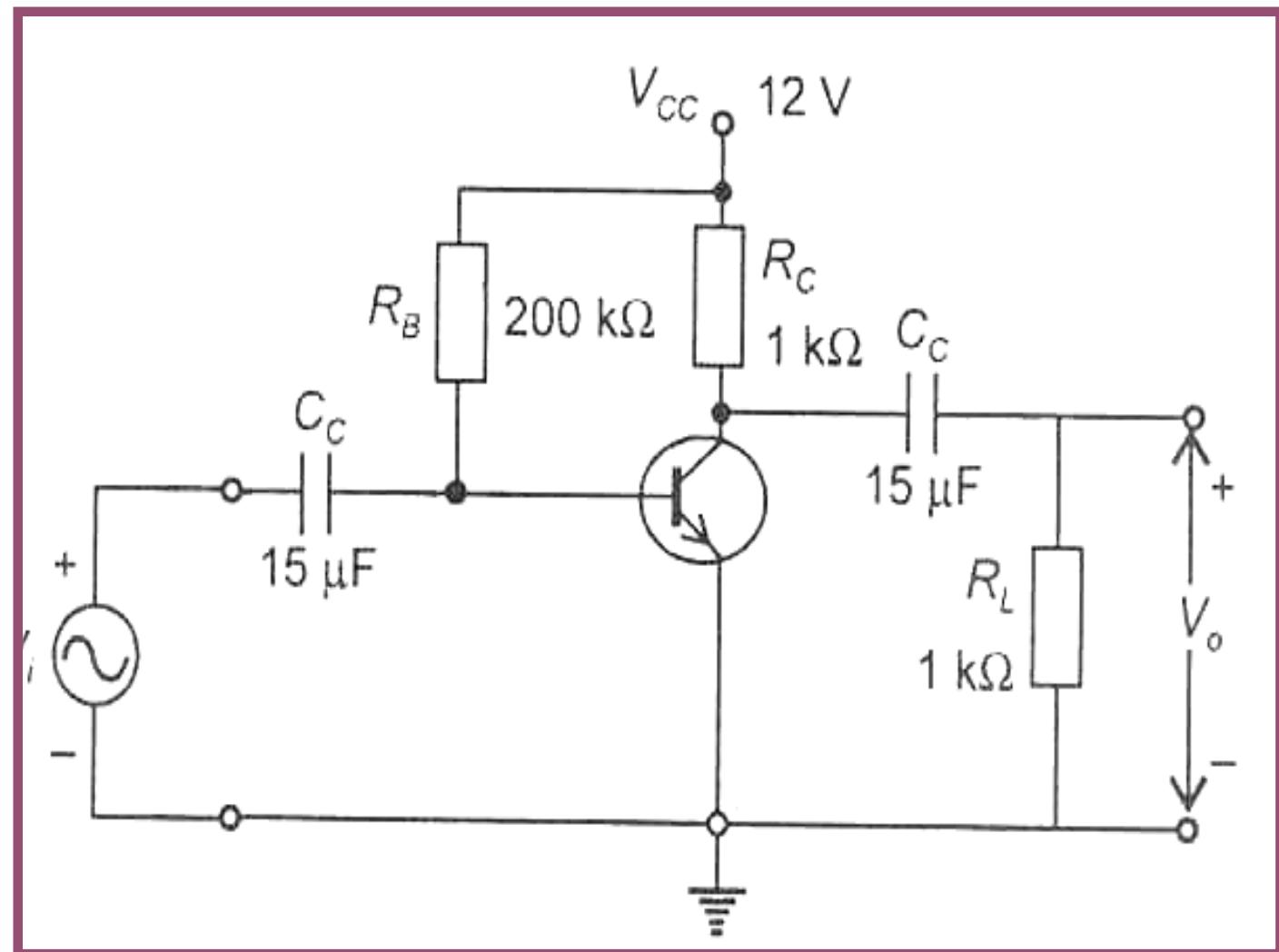Example : Analyze
the CE amplifier
circuit using h-
parameter model of
BJT. $h_{ie} = 2K$ $h_{fe} = \beta$
 $= 100$, $i/h_{oe} = 40K$ $h_{re} = .00025$



Solution : DC Analysis :


$$I_B = \frac{V_{CC}}{R_B} = \frac{12 \text{ V}}{200 \text{ k}\Omega} = 60 \mu\text{A}$$


$$\therefore I_C = \beta_0 I_B = 100 \times 60 \mu\text{A} = 6 \text{ mA};$$

$$I_{C(\text{sat})} = \frac{V_{CC}}{R_C} = \frac{12 \text{ V}}{1 \text{ k}\Omega} = 12 \text{ mA}$$

Thus, the transistor is not in saturation. Then
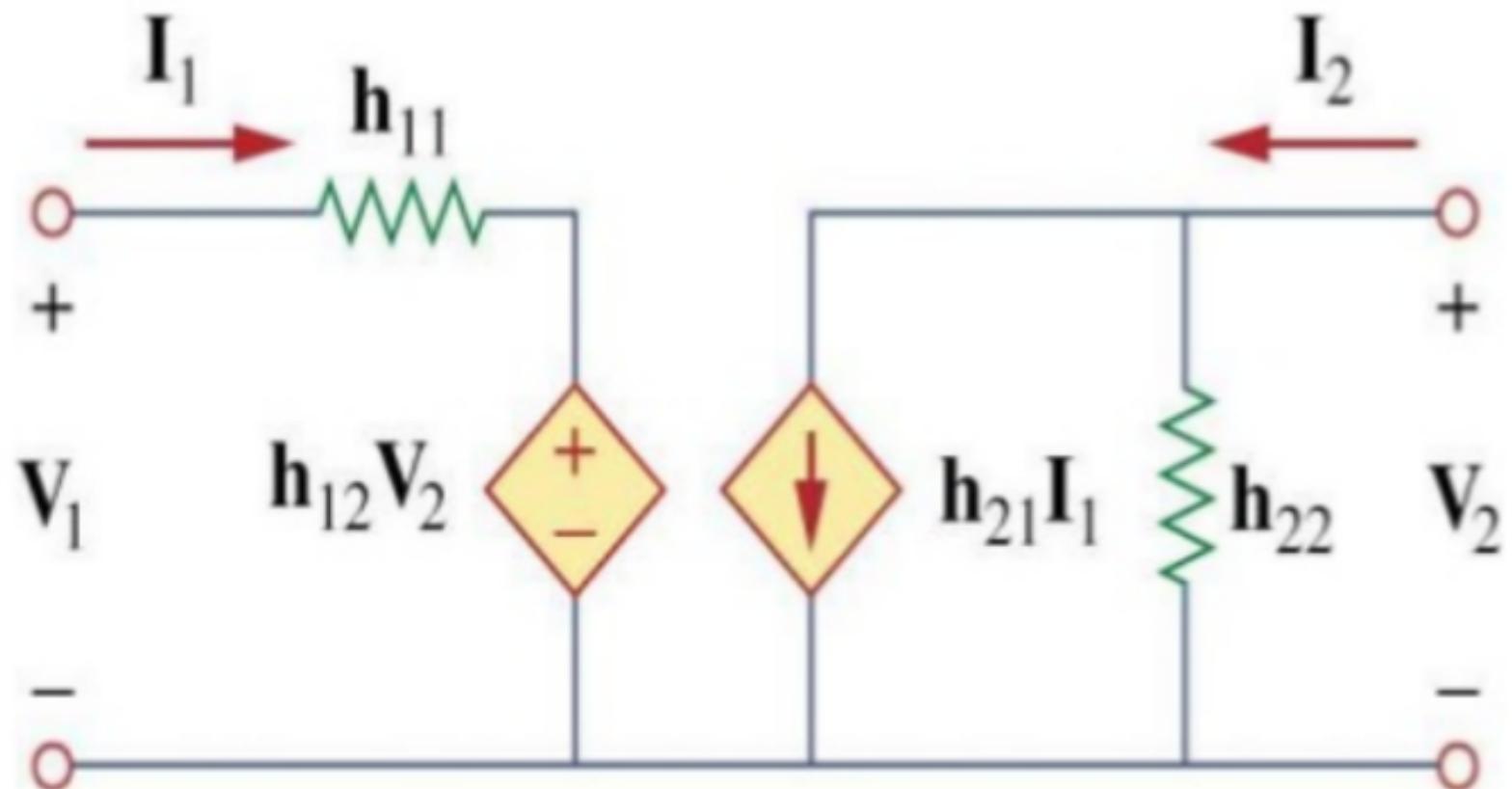
$$V_{CE} = V_{CC} - I_C R_C = 12 \text{ V} - 6 \text{ mA} \times 1 \text{ k}\Omega = 6 \text{ V}$$



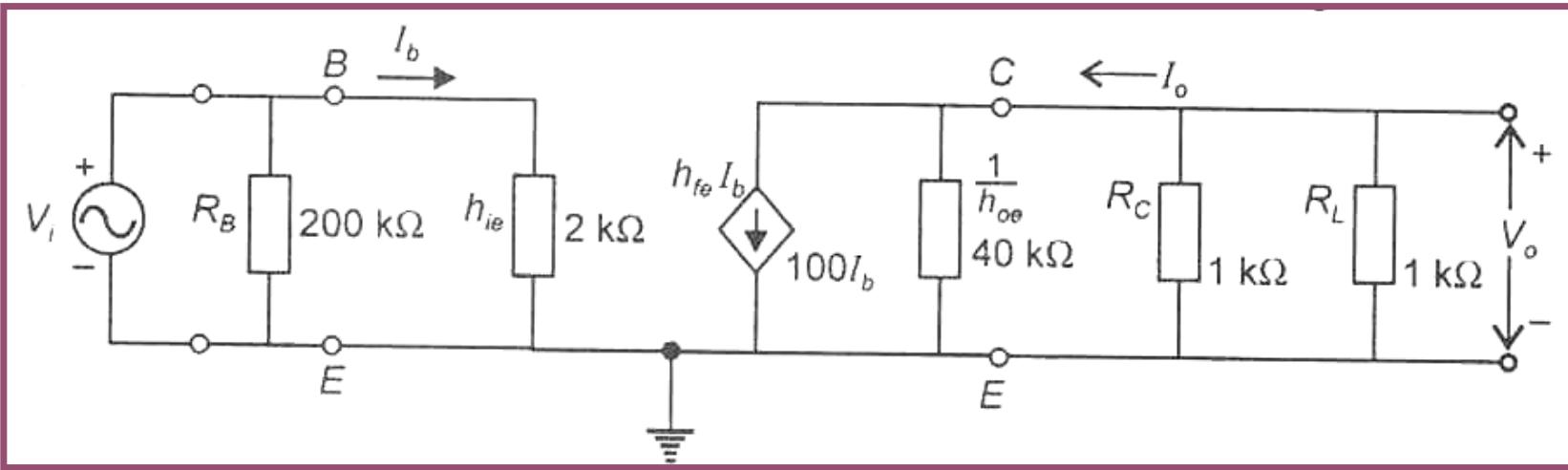

$$R_{ac} = R_C \parallel R_L = \frac{(1 \text{ k}\Omega)(1 \text{ k}\Omega)}{(1 \text{ k}\Omega + 1 \text{ k}\Omega)} = 0.5 \text{ k}\Omega$$

$$A_V = -\frac{h_{fe} R_{ac}}{h_{ie}} = -\frac{100 \times 0.5 \text{ k}\Omega}{2 \text{ k}\Omega} = 25$$

$$A_I = -\frac{h_{fe}}{1 + h_{oe} \times R_L}$$

$$A_V = \frac{A_I \times R_L}{R_i}$$

$$I_o = -100I_b$$

$$R_i = h_{ie} + h_{re} \times A_I \times R_L$$

$$\text{current gain} = \frac{I_o}{I_b} = -100$$

$$R_i = R_B \parallel h_{ie} = 200 \text{ k}\Omega \parallel 2 \text{ k}\Omega = \frac{(200 \text{ k}\Omega)(2 \text{ k}\Omega)}{(200 \text{ k}\Omega + 2 \text{ k}\Omega)} \approx 2 \text{ k}\Omega$$

$$\begin{aligned} R_o &= R_L \parallel R_C \parallel (1/h_{ve}) = (1 \text{ k}\Omega) \parallel (1 \text{ k}\Omega) \parallel (40 \text{ k}\Omega) \\ &= (0.5 \text{ k}\Omega) \parallel (40 \text{ k}\Omega) \approx 0.5 \text{ k}\Omega \end{aligned}$$

$$A_I = -\frac{h_{fe}}{1 + h_{oe} \times R_L}$$

$$A_V = \frac{A_I \times R_L}{R_i}$$

$$R_i = h_{ie} + h_{re} \times A_I \times R_L$$


$$Y_0 = h_{oe} - \frac{h_{re}h_{fe}}{h_{ie} + R_s} = \frac{1}{Z_0}$$

$$A_{VS} \frac{A_V R_i}{R_i + R_s}$$


$$A_{IS} = \frac{A_I R_s}{R_i + R_s}$$


Parameter	CE	CC	CB
h_i	1100Ω	1100Ω	22Ω
h_t	2.5×10^{-4}	1	3×10^{-4}
h_f	50	-51	-0.98
h_o	$25 \mu\text{A/V}$	$25 \mu\text{A/V}$	$0.49 \mu\text{A/V}$

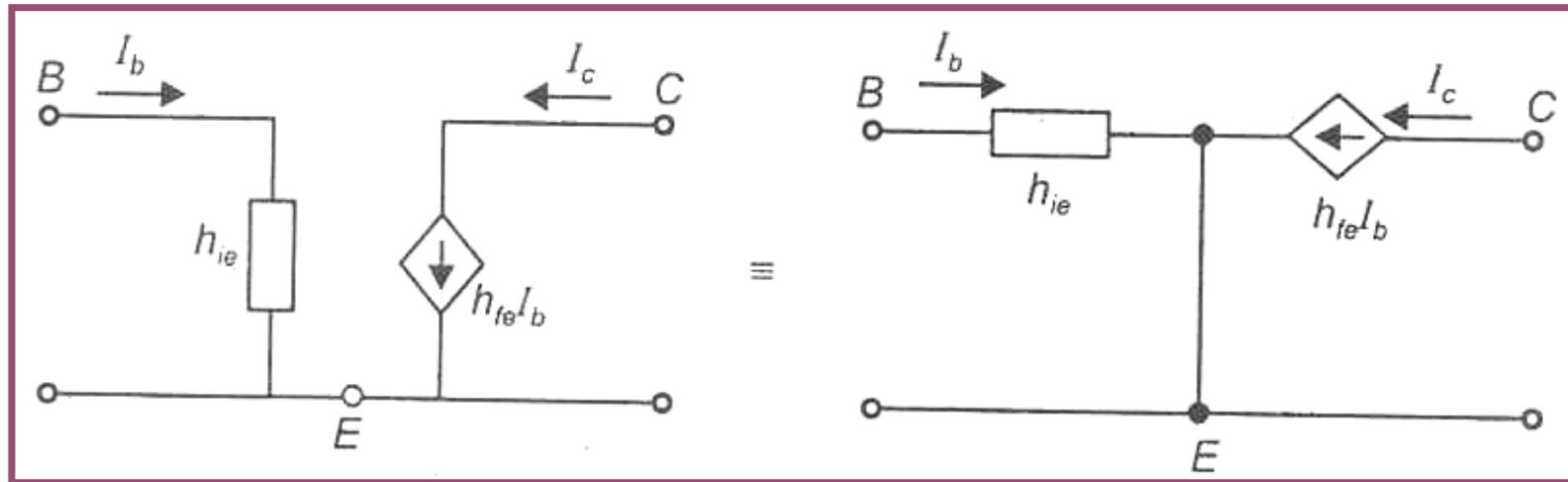Note : Since $1/h_{oe}$ can be ignored, the h – parameter model is further simplified.



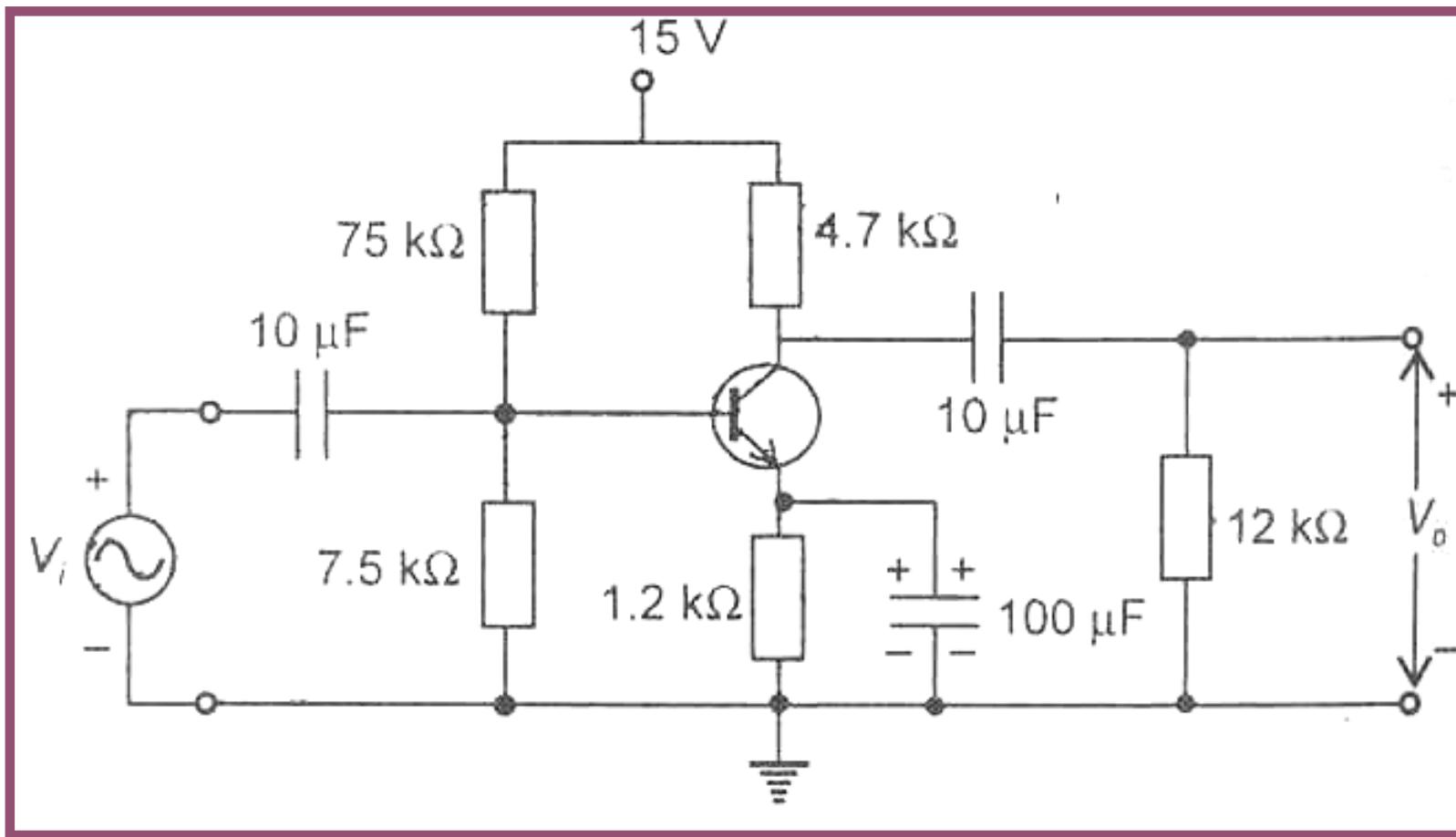Example 7.7 In the amplifier circuit of Fig. 7.31, the BJT used has $\beta = 150$ and $r_i = 2 \text{ k}\Omega$. Neglecting V_{BE} , determine its Q-point. Draw its ac equivalent circuit and calculate (a) the voltage gain, and (b) the input resistance.



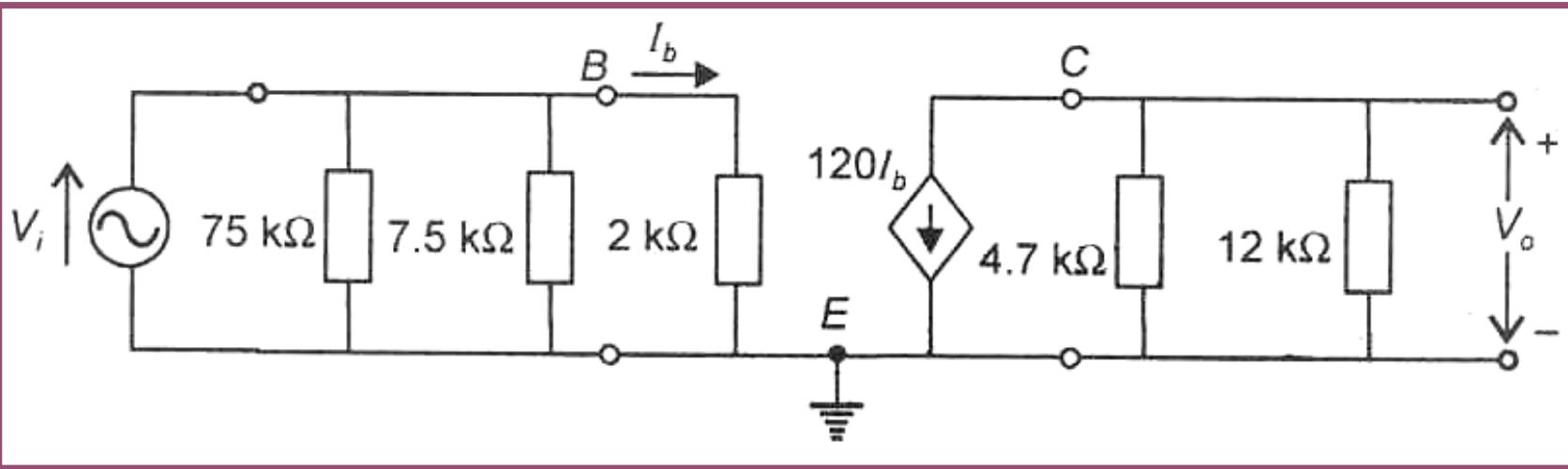


$$R_{ac} = (4.7 \text{ k}\Omega) \parallel (12 \text{ k}\Omega) = \frac{(4.7 \text{ k}\Omega)(12 \text{ k}\Omega)}{(4.7 \text{ k}\Omega + 12 \text{ k}\Omega)} = 3.38 \text{ k}\Omega$$

\therefore The voltage gain, $A_V = -\frac{\beta R_{ac}}{r_i} = -\frac{150 \times 3.38 \text{ k}\Omega}{2 \text{ k}\Omega} = -253.5$

$$R'_i = (75 \text{ k}\Omega) || (7.5 \text{ k}\Omega) || (2 \text{ k}\Omega) \simeq (7.5 \text{ k}\Omega) || (2 \text{ k}\Omega)$$


$$= \frac{(7.5 \text{ k}\Omega)(2 \text{ k}\Omega)}{(7.5 \text{ k}\Omega + 2 \text{ k}\Omega)} = 1.58 \text{ k}\Omega$$

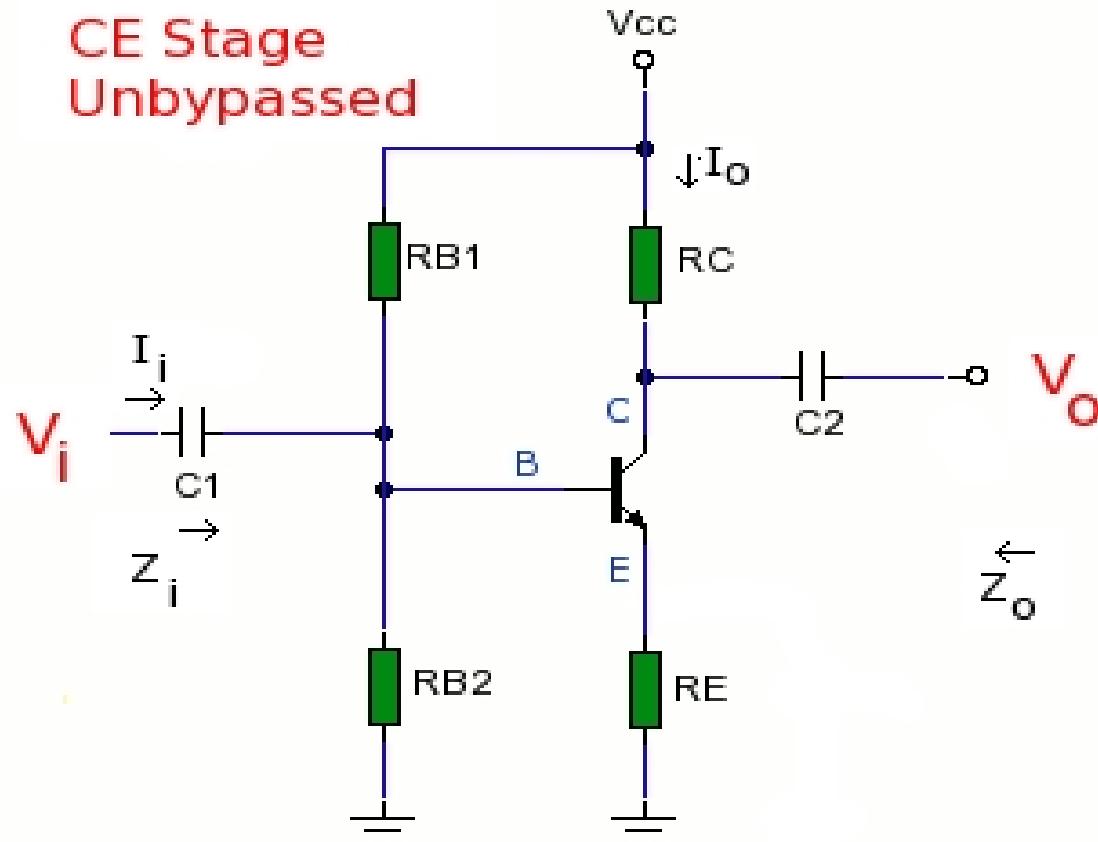The h-parameter model of a common emitter stage with the emitter resistor unbypassed is now shown. The model will be used to build equations for voltage gain, current gain, input and output impedance. The circuit is shown below:



As in the previous example, RB1 and RB2 are in parallel, the bias resistors are replaced by resistance R_{BB} , but as RE is now unbypassed this resistor appears in series with the emitter terminal. The hybrid small signal model is shown below, once again effects of small signal parameters h_{re} V_{ce} and h_{oe} have been omitted.


CE Stage RE Unbypassed

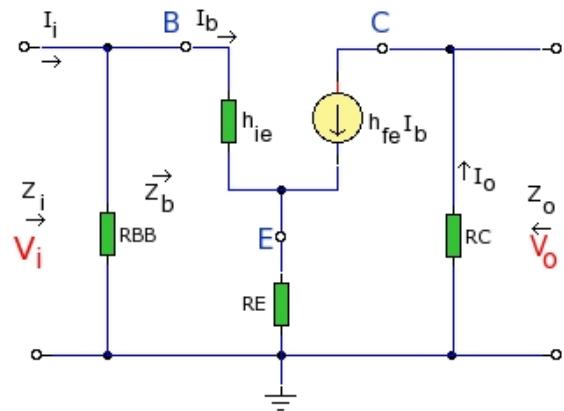


The input impedance Z_i is the bias resistors R_{BB} in parallel with the impedance of the base, Z_b . $Z_b = h_{ie} + (1 + h_{fe}) RE$ Since h_{fe} is normally much larger than 1, the equation can be reduced to: $Z_b = h_{ie} + h_{fe} RE$ $Z_i = R_{BB} \parallel (h_{ie} + h_{fe} RE)$ With V_i set to zero, then $I_b = 0$ and $h_{fe} I_b$ can be replaced by an open-circuit. The output impedance is: $Z_o = RC$ Note the - sign in the equation, this indicates phase inversion of the output waveform.

$$V_o = -I_o RC = -h_{fe} I_b RC$$

Example

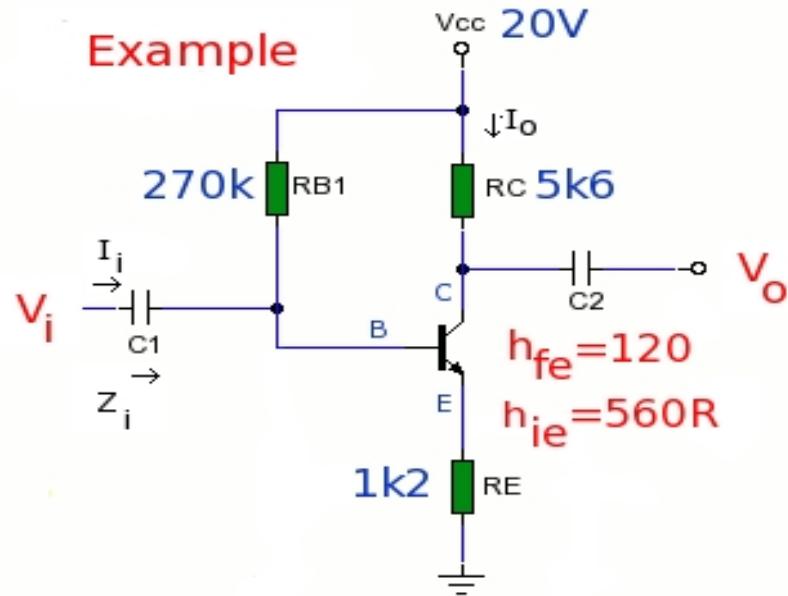


CE Stage RE Unbypassed

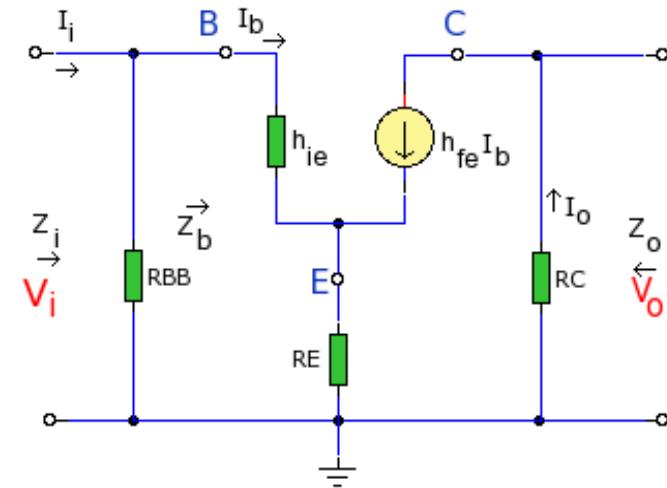

The hybrid parameters must be known to use the hybrid model, either from the datasheet or measured. In the above circuit, Z_i , Z_o , Av , and Ai will now be calculated.

Note that this CE stage uses a single bias resistor $RB1$ which is the value RBB .

Parameter	CE	CC	CB
h_i	1100Ω	1100Ω	22Ω
h_t	2.5×10^{-4}	1	3×10^{-4}
h_f	50	-51	-0.98
h_o	$25 \mu\text{A/V}$	$25 \mu\text{A/V}$	$0.49 \mu\text{A/V}$

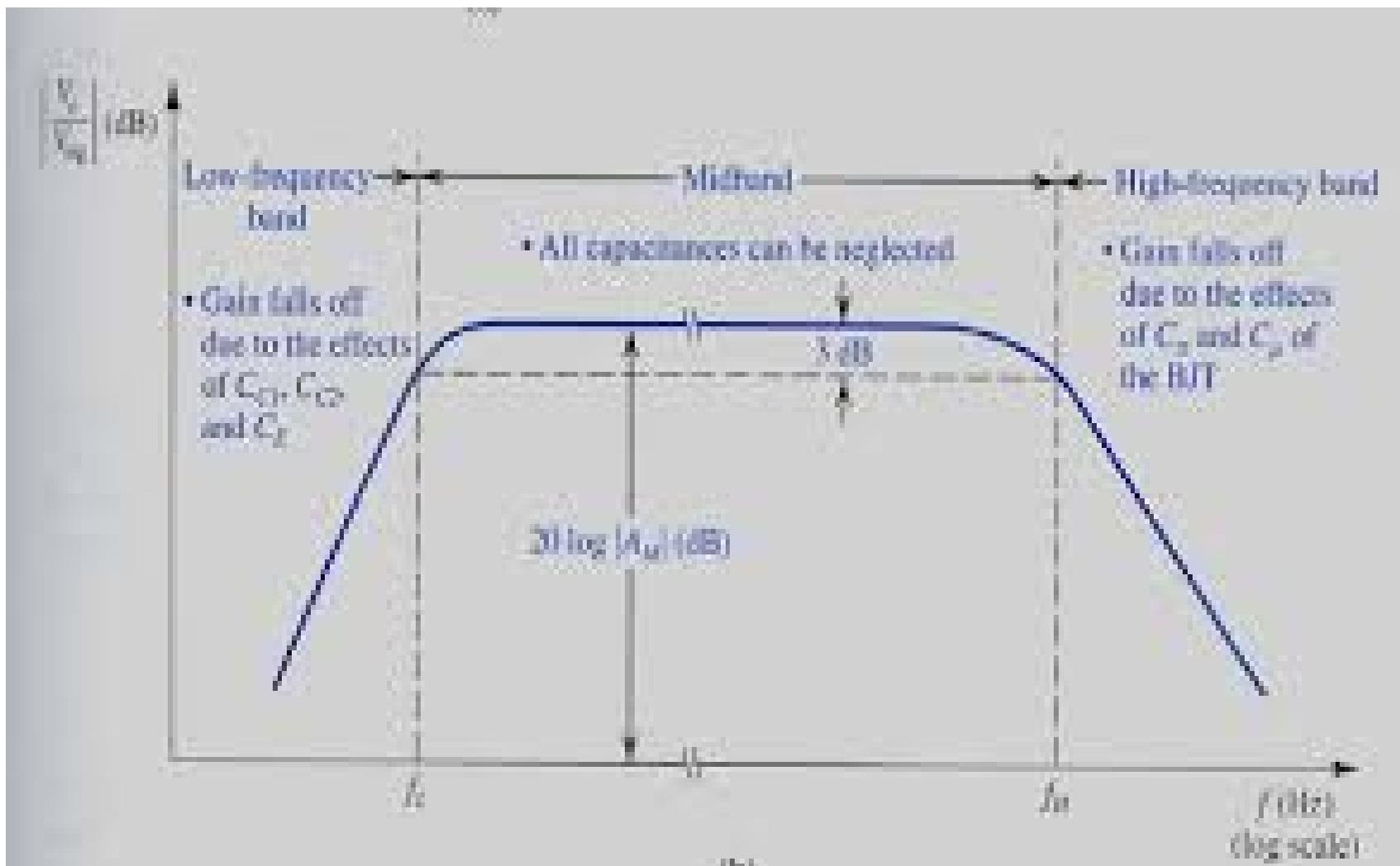

Conversion from CE h -parameters to CB and CC
 h -parameters, and to r -parameters.

CE to CB h -parameters	CE to CC h -parameters	CE h -parameters to r -parameters
$h_{ib} \approx \frac{h_{ie}}{1 + h_{fe}}$	$h_{ic} = h_{ie}$	$\alpha \approx \frac{h_{fe}}{1 + h_{fe}}$
$h_{rb} \approx \frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{re}$	$h_{rc} = 1 - h_{re}$	$r_c = \frac{1 + h_{fe}}{h_{oe}}$
$h_{fb} \approx \frac{h_{fe}}{1 + h_{fe}}$	$h_{fc} = 1 + h_{fe}$	$r_e = \frac{h_{ie}}{1 + h_{fe}} \approx r'_e$
$h_{ob} \approx \frac{h_{oe}}{1 + h_{fe}}$	$h_{oc} = h_{oe}$	$r_b = h_{ie} - \frac{h_{re}(1 + h_{fe})}{h_{oe}}$