

Code No: 45012

R07

Set No - 1

III B.Tech I Semester Regular Examinations, Nov/Dec 2009

Linear IC Applications

Electronics And Communication Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions

All Questions carry equal marks

1. (a) Why should cascading of differential amplifiers be done? Draw the circuit and explain the operation of cascaded differential amplifier stages.
(b) When a differential input of $1\text{mV} \sin \omega t$ is applied to a differential amplifier the differential output is $0.5\text{V} \sin \omega t$. When both inputs are joined together and $1\text{V} \sin \omega t$ is applied to the output is $200\text{mV} \sin \omega t$. Determine the CMRR. [8+8]
2. (a) With the help of circuit diagram and wave forms explain how IC 555 can be operated as monostable multi-vibrator.
(b) What is the importance of Pin5 of IC 555? Explain. [10+6]
3. (a) Find the resolution of 12-bit D/A converter.
(b) List the draw backs of binary weighted resistor technique D/A conversion.
(c) Explain the working of inverted R-2R ladder D/A converter. [6+4+6]
4. (a) With the help of circuit diagram explain staircase and pulse generator.
(b) Use $\pm 15\text{V}$ power supply and IC741 design wien bridge oscillator for 1 KHz frequency. [8+8]
5. (a) Discuss the stability of an op-amp by considering non-inverting amplifier with resistive feed back.
(b) For an op-amp $\text{PSRR} = 70\text{db}$ (min) $\text{CMRR} = 10^5$ and differential mode gain $A_d = 10^5$. The output voltage changes by 20V in $4\mu\text{Sec}$ calculate:
 - i. PSRR
 - ii. Common mode gain
 - iii. Slew Rate. [8+8]
6. (a) Draw the circuit diagram of a triangular wave generator using a comparator and integrator. Explain its operation by referring to the output waveform.
(b) What is window detector? Explain its operation. [8+8]
7. (a) What is an instrumentation amplifier? What are the basic requirements of a good instrumentation amplifier.
(b) Design an instrumentation amplifier whose gain can be varied continuously over the range $1 \leq A \leq 1000$ use $100\text{ k}\Omega$ potentiometer. [8+8]

Code No: 45012

R07

Set No - 1

8. (a) Draw the basic logarithmic multiplier circuit and explain how it multiplies two voltages
- (b) With the neat circuit diagram explain the operation of an op-amp based sample & hold circuit. [8+8]

★ ★ ★ ★ ★

III B.Tech I Semester Regular Examinations, Nov/Dec 2009**Linear IC Applications****Electronics And Communication Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions****All Questions carry equal marks**

1. Obtain the expressions for A_d , A_c , R_i and R_o for dual input unbalanced output differential amplifier configuration. [16]
2. (a) What is the name of the circuit that is used to detect the peak value of non-sinusoidal input wave forms? Explain its operation?
(b) Distinguish between positive and -ve clipper circuits. Explain the operation of +ve and -ve clippers with the help of circuit and wave form. [8+8]
3. (a) Define a filter? How filters are classified?
(b) Explain various types of filters alongwith their frequency response.
(c) Define the conditions on the feedback circuit of an amplifier to convert it into an oscillator. [6+6+4]
4. (a) Explain the operation of balanced modulator using diodes.
(b) Briefly explain the following.
 - i. Square circuit.
 - ii. Square rooting circuit. 8+8]
5. (a) Write a short notes on
 - i. Limitations of weighted resistor type D/A converters.
 - ii. Resolution of a converter circuit.
(b) Calculate the number of bits required to represent a full scale voltage of 10V with a resolution of 5 mV approximately. [8+8]
6. (a) An IC555 timer used as a monostable has $R=20\text{ K}\Omega$ and $C = 0.01\mu\text{f}$. What is the duration of output pulse?
(b) Explain how IC555 can be used as missing pulse detector. [8+8]
7. (a) Explain how the averaging circuit can be derived from the summer.
(b) Show that the output of the subtractor is proportional to the difference between the two input voltages.
(c) Design the op-amp circuit which can give the output as $V_o = 2V_1 - 3V_2 + 4V_3 - 5V_4$ [6+6+4]
8. (a) Explain the following parameters of an op-amp:
 - i. Input bias current

Code No: 45012

R07

Set No - 2

- ii. Input offset current
 - iii. Input offset voltage.
- (b) An op-amp is given 7 KHz sine wave input signal. Find the largest amplitude of undistorted output of the amplifier with I_{CQ} of $8\mu\text{A}$ and C_C of 27pF . [16]

★ ★ ★ ★ ★

III B.Tech I Semester Regular Examinations, Nov/Dec 2009**Linear IC Applications****Electronics And Communication Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions****All Questions carry equal marks**

1. (a) Using analog voltage multiplier circuit show that the output voltage is proportional to two analog input voltages V_1 and V_2 .
(b) Explain analog voltage divider circuit. [8+8]
2. (a) Compare monostable and astable multi-vibrators.
(b) What are the features of IC 555 timer.
(c) Design a timer, which should turn ON heater immediately after pressing a push button and should hold heater ON state for 5 seconds. [6+6+4]
3. (a) Explain the operation of a practical integrator with suitable mathematical expressions.
(b) Obtain the frequency response of a practical integrator. What are its applications? [8+8]
4. (a) Draw the circuit diagram of a symmetrical emitter coupled differential amplifier and show that a very high CMRR will result if the differential amplifier is supplied by a constant current bias.
(b) That parameters for the differential amplifier are given as $R_C = 1\text{k}\Omega$, $R_S = 1\text{k}\Omega$, $h_{fe} = 1$, $K\Omega$ and $R_E = 2\text{M}\Omega$ neglecting h_{oe} , calculate differential mode gain, common mode gain and CMRR. The amplifier is dual input, balanced output configuration. [8+8]
5. (a) Explain the following parameters of an op-amp.
 - i. CMRR
 - ii. PSRR
 - iii. Slew rate.
(b) For an op-amp having a slew rate of $3\text{V}/\mu\text{sec}$. What is the maximum closed loop voltage gain that can be used when the input signal varies by 0.4 in $12\mu\text{sec}$. [8+8]
6. (a) Write a note on multiplying DACs.
(b) List important specifications of a standard ADC IC.
(c) An 8 bit successive approximation Register type ADC is driven by a 1 MHz clock. Find its conversion time. [6+6+4]
7. (a) What is absolute value output circuit? How can it be used as a full wave rectification. [10]

- b) For an op-amp Comparator assume $\pm V_{CC} = \pm 12V$, $V_{sat} = 0.9V_{CC}$ If a sine wave of 10V is applied, calculate threshold level and plot input output waveforms [6]
8. (a) What is VCVS configuration. Explain.
- (b) Design a VCVS low pass butter worth second order filter with a cut off frequency of 4KHz assume necessary data. [8+8]

III B.Tech I Semester Regular Examinations, Nov/Dec 2009**Linear IC Applications****Electronics And Communication Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions****All Questions carry equal marks**

1. (a) Explain the performance parameters of a multiplier.
(b) List the applications of multiplier. [8+8]
2. (a) Describe any two application of 555 timer in
 - i. Astable multivibrator configuration.
 - ii. Monostable multivibrator configuration. [8+8]
3. (a) Explain successive approximation ADC with the help of block diagram. Also illustrate conversion process.
(b) An 8-bit successive approximation ADC is driven by a 1 MHz clock. Find its conversion time. [8+8]
4. (a) What are the limitations of comparator.
(b) In the square wave oscillator as shown in figure 1, calculate the frequency of oscillations. If $R_2 = 10\text{K}\Omega$ $R_1 = 8.6\text{K}\Omega$ $R_f = 100\text{K}\Omega$ and $C = 0.01\mu\text{f}$. [8+8]
5. (a) Draw the circuit diagram of emitter coupled differential amplifier and perform D.C. analysis.
(b) Determine the output-voltage of a differential amplifier for the input voltage of $300\mu\text{V}$ and $240\mu\text{V}$. the differential gain of the amplifier is 5000 and the value of CMRR is 100. [8+8]
6. (a) Explain the operation of voltage to current converter.
 - i. With floating load
 - ii. Grounded load.
(b) An inverting amplifier using op-amp has $R_1 = 10\text{ k}\Omega$ and $R_f = 47\text{ K}\Omega$. It is applied with 2V peak to peak sine wave. An AC voltmeter is used between the output terminal and ground to measure the output voltage calculate the reading on the voltmeter. Assume supply voltage to be $\pm 12\text{V}$. [8+8]
7. (a) Derive the expression for voltage to frequency conversion factor.
(b) Draw the pin diagram of 566 VCO IC and list important specifications of 566 VCO IC. [8+8]
8. Discuss Dominant pole, pole zero and Feed Forward compensation technique. What are its merits and demerits. [16]

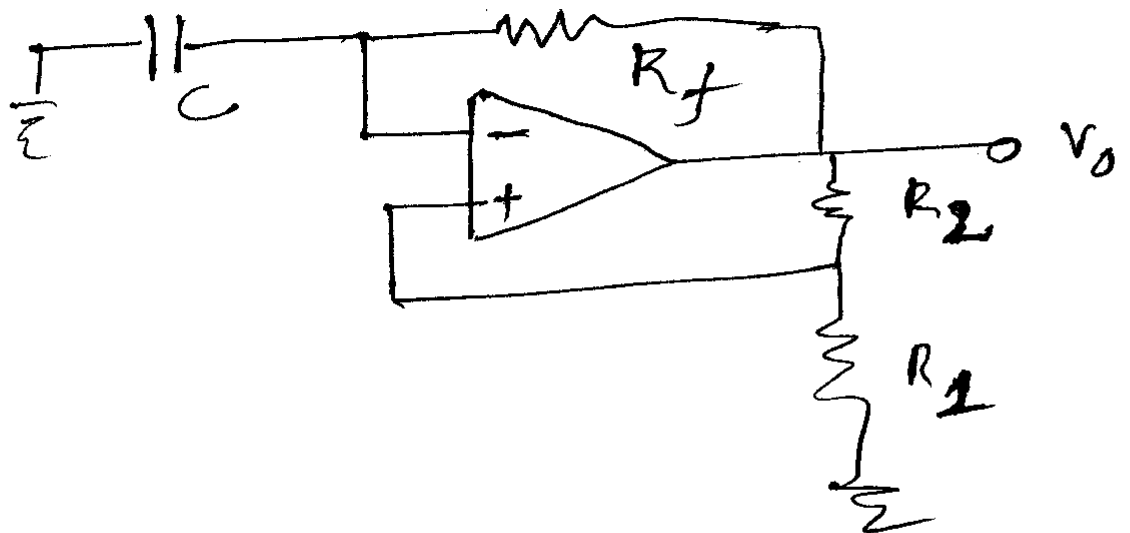


Figure 1: