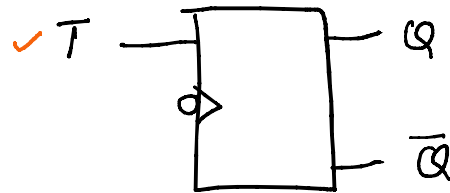


synchronous inputs & Asynchronous inputs

The normal data **inputs** to a **flip flop** (D, S and R, or J and K) are referred to as **synchronous inputs** because they have an effect on the outputs (Q and not-Q) only in step, or in sync, with the clock signal transitions.





-ve edge triggered T flip flop

Synchronous inputs (for example the *D* or *J-K* inputs) affect the output on the triggering edge of the clock. Most flip-flops also have other inputs that are *asynchronous*, meaning they affect the output independent of the clock.

Two such inputs are normally labeled PRE (preset) and CLR (clear). These inputs are usually active LOW, as shown here.

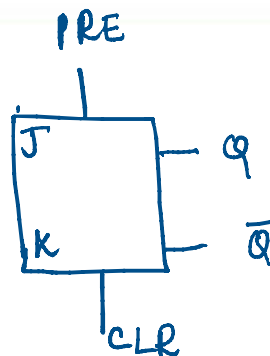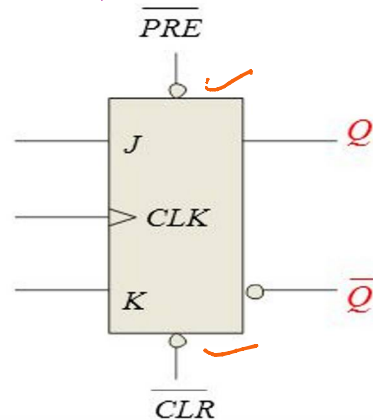Other common names for these pins are *SET* and *RESET*.



\overline{PRE}
 \overline{CLR} } Active low Asynchronous

PRE, CLR → Active high Asynchronous i/p


active high means, we need to give logic '1'
at asynchronous $\bar{i/p}$


active low means, we need to give logic '0'
at asynchronous $\bar{i/p}$.

Flip-flops with Asynchronous Preset and Clear


- It is often necessary to initialize a flip-flop to a known state before the circuit operation starts.
 - Preset* (sets $Q = 1$) and *Clear* (sets $Q = 0$).
 - These are asynchronous operations, and can be easily implemented by using additional inputs on the cross-coupled gates.
 - The term "*asynchronous*" means that it does not depend on the clock.

Active high Asynchronous $\bar{i/p}$ s

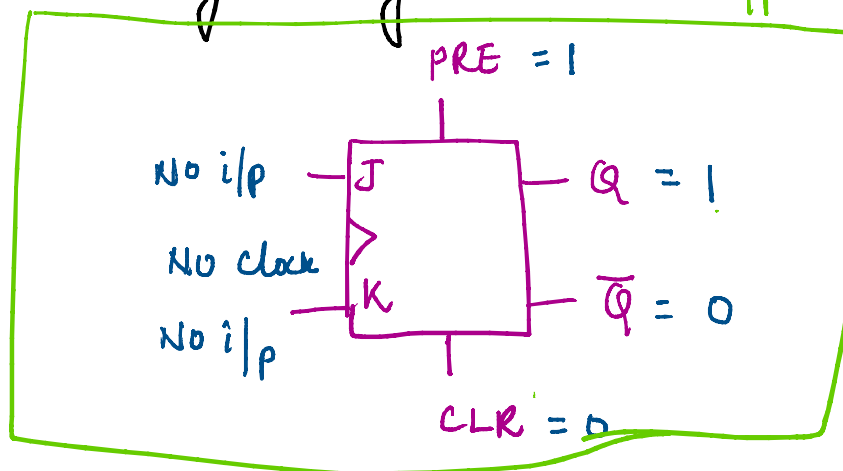


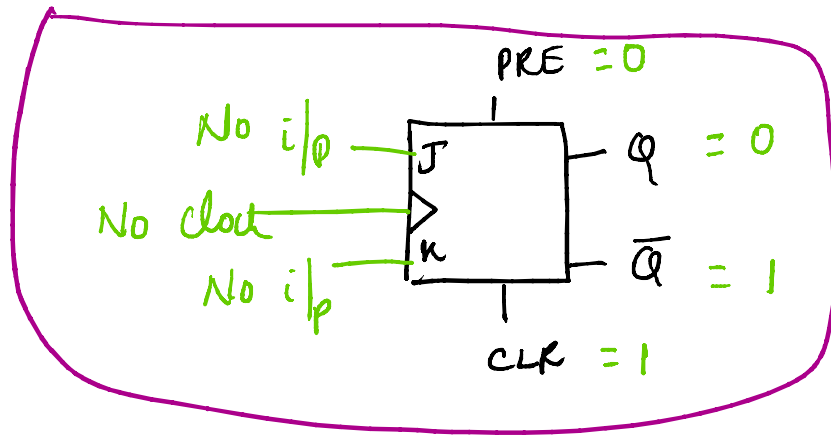

Active low Asynchronous Flip flop

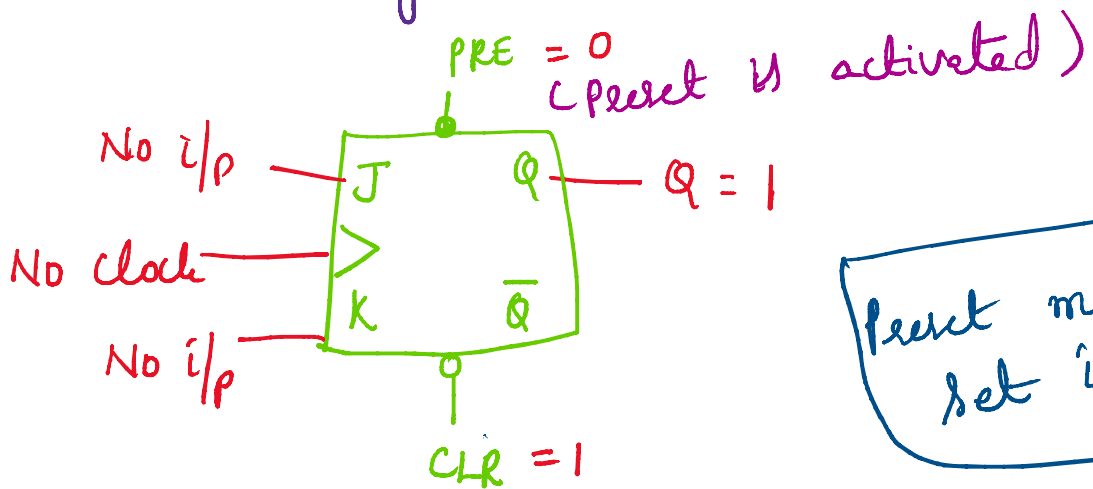


Preset means
set i.e. $Q=1$

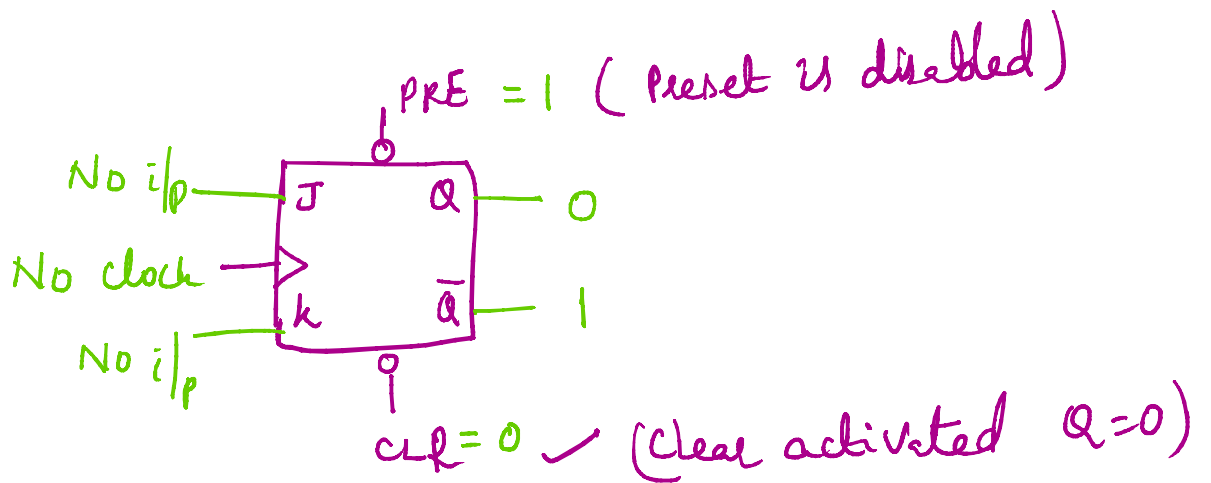

Asynchronous inputs (override inputs) operate independently of the synchronous inputs and clock and can be used to set the FF to 1/0 states *at any time*.

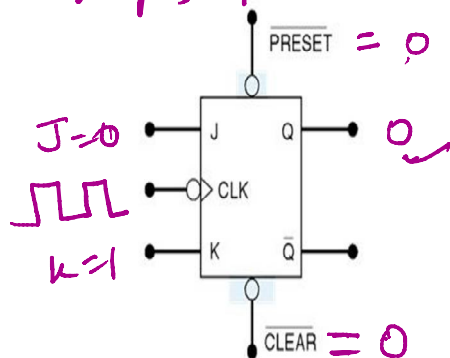JK flip flop with Active low Preset and clear




PRESET	CLEAR	FF response
1	1	Clocked operation*
0	1	Q = 1 (regardless of CLK)
1	0	Q = 0 (regardless of CLK)
0	0	Not used

*Q will respond to J, K, and CLK

Asynchronous will not be activated

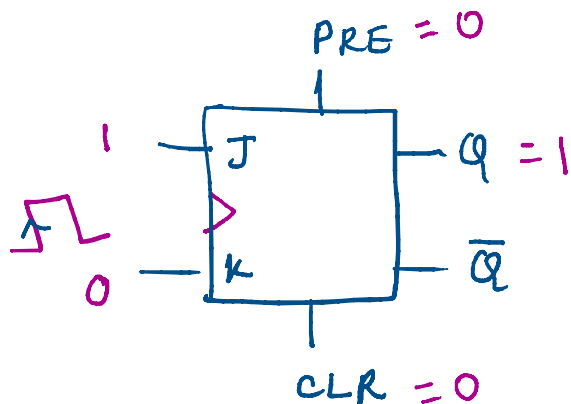logic diagram of basic JK flip flop with Active High Preset and clear



PRE	CLR	FF response
0	0	Clocked operation
0	1	Q = 0
1	0	Q = 1
1	1	Not used