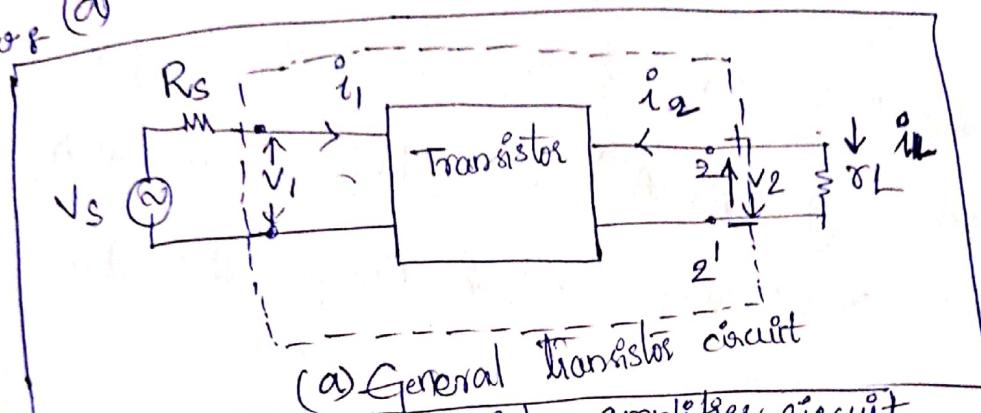


# Analysis of a transistor amplifier circuit using h-parameters (Amplifier Expressions)

Consider the general transistor amplifier circuit as shown below:

(a)



(b) Transistor amplifier circuit


The amplifier can be formed by connecting a signal source at its input terminals and load resistance at its output terminals and  $R_s$  is the internal resistance of the voltage source. The figure shows the hybrid equivalent circuit of a general transistor amplifier circuit (A) (B) (C)

The performance of the transistor can be analysed by calculating the four parameters, they are (i) current gain ( $A_i$ ) (ii) voltage gain ( $A_v$ ) (iii) input resistance ( $R_i$ ) (iv) output resistance ( $R_o$ )

10/01/15

The following figure shows the small signal hybrid equivalent circuit of general transistor amplifier.

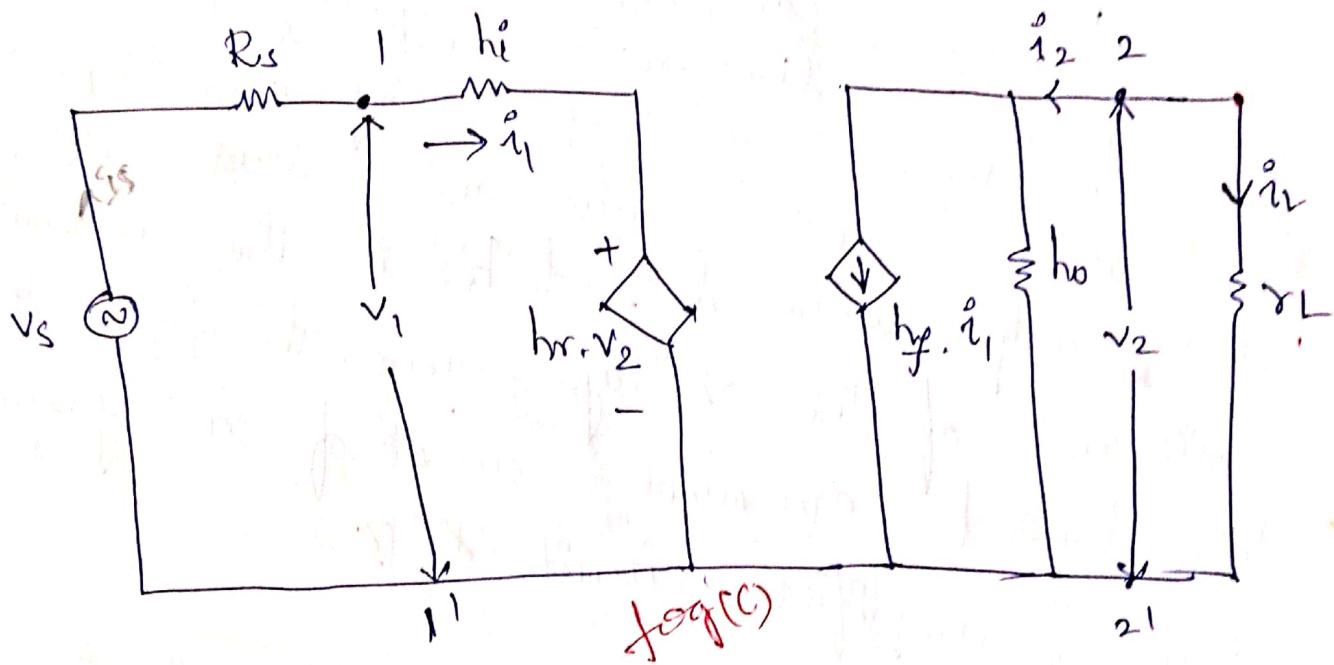We shall derive the expressions for current gain ( $A_i$ ), voltage gain ( $A_V$ ), input resistance ( $R_i$ ) & output resistance ( $R_o$ ).



Hybrid Equivalent circuit for general amplifier circuit.

The expressions can be obtained by using following relations

$$V_1 = h_i \cdot i_1 + h_{oV} \cdot V_2 \quad \text{--- (1)}$$

$$\dot{i}_2 = h_f \cdot i_1 + h_o \cdot V_2 \quad \text{--- (2)} \quad \checkmark$$

The voltage drop across ' $\gamma_L$ ' is equal to voltage across output terminals '2-2'.

$$\therefore V_2 = \dot{i}_L \cdot \gamma_L \quad (\because \dot{i}_L = -\dot{i}_2)$$

$$\boxed{V_2 = -\dot{i}_2 \cdot \gamma_L} \quad \checkmark$$

### (i) Current gain ( $-A_i$ )

The ratio of output to input current

$$-A_i = \frac{\dot{i}_L}{\dot{i}_1} = \frac{-\dot{i}_2}{\dot{i}_1}$$

Now substituting,  $V_2 = -\dot{i}_2 \cdot \gamma_L$  in equation (2)

$$\dot{i}_2 = h_f \cdot \dot{i}_1 + h_o \cdot V_2$$

$$\dot{i}_2 = h_f \cdot \dot{i}_1 + h_o \cdot (-\dot{i}_2 \cdot \gamma_L)$$

$$\dot{i}_2 = h_f \cdot \dot{i}_1 - h_o \dot{i}_2 \cdot \gamma_L$$

$$\dot{i}_2 + h_o \dot{i}_2 \gamma_L = h_f \cdot \dot{i}_1$$

$$\dot{i}_2 (1 + h_o \gamma_L) = h_f \cdot \dot{i}_1$$

$$\boxed{\therefore \frac{\dot{i}_2}{\dot{i}_1} = \frac{h_f}{1 + h_o \gamma_L}} \quad \checkmark$$

$$\therefore A_i^o = - \frac{i_2^o}{i_1}$$

$$\therefore A_i^o = \frac{-h_f}{1 + h_o \cdot r_L} \quad \text{--- } ③$$

### (ii) Input Resistance ( $R_i^o$ ):

Input resistance which we see looking into input terminals  $1-1'$  is called amplifier input resistance.

$$R_i^o = \frac{V_1}{i_1}$$

Substituting  $V_2 = -i_2 r_L$  in equation ①

$$V_1 = h_i \cdot i_1 + h_o \cdot V_2$$

$$V_1 = h_i \cdot i_1 + h_o \cdot (-i_2 r_L)$$

$$V_1 = h_i \cdot i_1 - h_o \cdot i_2 r_L$$

Divide this equation both sides by  $i_1^o$ .

$$\frac{V_1}{i_1^o} = h_i - \frac{h_o \cdot i_2 r_L}{i_1^o}$$

Replacing  $\frac{i_2^o}{i_1^o}$  with  $-A_i^o$

$$R_i = h_{ie} + h_{re} \cdot A_i \cdot r_L \quad \checkmark \quad (4)$$

Substituting  $-A_i = -\frac{h_f}{1+h_{re}r_L}$  in the above equation,

now, Substitute  $R_i = h_{ie} + h_{re} \left( -\frac{h_f}{1+h_{re}r_L} \right) r_L$

$$\therefore R_i = h_{ie} - \frac{h_{re}h_f}{h_{re} + \frac{1}{r_L}} \quad \checkmark \quad (5)$$

(ii) Voltage Gain ( $-Av$ ):

$g_t$  is defined as the ratio of output voltage  $v_2$  to input voltage  $v_1$ .

$$\therefore -Av = \frac{v_2}{v_1} = \frac{-i_2 r_L}{v_1}$$

we know  $-A_i = -\frac{i_2}{i_1}$

$$\Rightarrow i_2 = -A_i \cdot i_1$$

Sub. in  $-Av$  we get,

$$\therefore A_v = A_i \cdot \gamma_L \left( \frac{i_1}{v_1} \right)$$

$$A_v = \frac{A_i \cdot \gamma_L}{R_i} \quad \text{--- (6)}$$

Substituting  $A_i = -\frac{h_f}{1+h_o \gamma_L}$  in equation (6)

&  $R_i = h_i - \frac{h_r h_f}{h_o + 1/\gamma_L}$  in above equation

$$A_v = \frac{\left( -\frac{h_f \gamma_L}{1+h_o \gamma_L} \right)}{\left( h_i - \frac{h_r h_f}{h_o + 1/\gamma_L} \right)} \rightarrow \frac{h_r h_f \gamma_L}{h_o \gamma_L + 1}$$

$$A_v = \frac{-h_f \gamma_L}{h_i(h_o \gamma_L + 1) - h_r h_f \gamma_L / 1}$$

$$A_v = \frac{-h_f \gamma_L}{h_i + (h_i h_o - h_r h_f) \gamma_L}$$

Replace  $h_{iho} - h_{rf}h_f$  with  $\Delta h$  in above equation


$$\therefore A_v = -\frac{h_f \cdot r_L}{h_i + \Delta h \cdot r_L} \quad - \textcircled{7}$$

(iv) Output Resistance ( $R_o$ ):-

It is obtained by setting the voltage

Source  $V_s$  to '0' & Load resistance  $R_L$  to ' $\infty$ ' from  
and by driving the output terminals  $2-2'$  from  
a generator  $V_2$  as shown in the figure below:

12/01/15

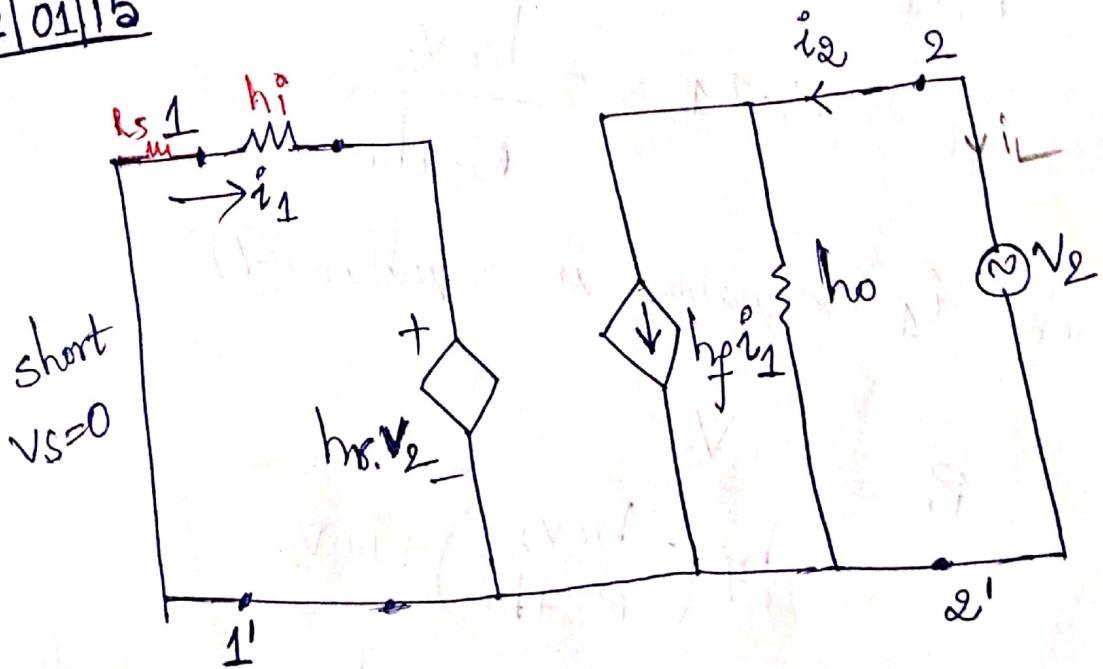

The output resistance ' $R_o$ ' is defined as output voltage ' $V_2$ ' to output current ' $i_2$ ' to the current drawn from  $V_2$ .

$$R_o = \frac{V_2}{i_2}$$

$$R_o = \frac{V_2}{h_f i_1 + h_o V_2} \quad \textcircled{7}$$

The current ' $i_1$ ' is obtained applying KVL to the input circuit.

$$R_s i_1 + h_i i_1 + h_o V_2 = 0$$

$$\therefore i_1 = -\frac{h_o V_2}{R_s + h_i}$$

Sub.  $i_1$  equation in equation  $\textcircled{7}$

$$R_o = \frac{V_2}{h_f \left( -\frac{h_o V_2}{R_s + h_i} \right) + h_o V_2}$$

$$R_o = \frac{R_s + h_i}{(R_s + h_i)h_o + h_o h_f}$$

$$R_o = \frac{R_s + h_i}{R_{sho} + (h_{ho} - h_r) h_f}$$

$$R_o = \frac{R_s + h_i}{R_{sho} + \Delta b} \quad \text{②} \quad \checkmark$$

if  $R_s = 0$ ;  $R_o = \frac{h_i}{\Delta b}$

Output admittance

$$Y_o = \frac{i_2}{V_2}$$

But  $i_2 = h_f i_1 + h_r V_2$

divide by  $V_2$ ; we get

$$\frac{i_2}{V_2} = \frac{h_f \frac{i_1}{V_2}}{1} + \frac{h_r V_2}{V_2}$$

Apply KVL to input,

$$R_s i_1 + h_i i_1 + h_r V_2 = 0$$

$$i_1 (R_s + h_i) + h_r V_2 = 0$$

From;  $\frac{i_1}{V_2} = -\frac{h_r}{R_s + h_i}$

$$y_0 = \frac{I_2}{V_2} = hf \left( \frac{-hr}{R_s + h_i} \right) + h_o$$

$$\boxed{y_0 = h_o - \frac{hr hf}{R_s + h_i}} \quad \text{--- (9)}$$

Note Output admittance is a function of Source resistance  $R_s$ .

### Power Gain & ( $A_p$ )

$A_p$  is defined as output power delivered to the load to the input power.  $= \frac{P_2}{P_1}$

$$P_2 = V_2 \times i_L \quad \Rightarrow \quad P_2 = V_2 \times i_2 \quad A_p = \frac{P_2}{P_1}$$

$$P_1 = V_1 \times i_1$$

$$\therefore A_p = \frac{-V_2 \times i_2}{V_1 \times i_1} = +A_v \times A_T$$

$$= -A_i \times \frac{r_L}{R_i} \times A_i$$

$$\boxed{\therefore A_p = (A_i)^2 \times \frac{r_L}{R_i}} \quad \text{--- (10)}$$

$A_v, A_T, \frac{r_L}{R_i}$

## Overall voltage Gain (Avs) / Voltage Amplification

- taking ~~into~~ account the resistance of source  $R_s$  /  
Effect of source resistance on voltage gains

It is important to take into account the source resistance  $R_s$  while calculating the voltage & current gains, results a ~~is~~ overall voltage gain ( $Avs$ ) and overall current gain ( $Ais$ ).


## Overall voltage Gain (Avs)

gt is defined as the ratio of output voltage  $V_2$  to source voltage  $V_s$ .

$$Avs = \frac{V_2}{V_s} \times \frac{V_1}{V_1}$$

$$Avs = Av \times \frac{V_1}{V_s}$$

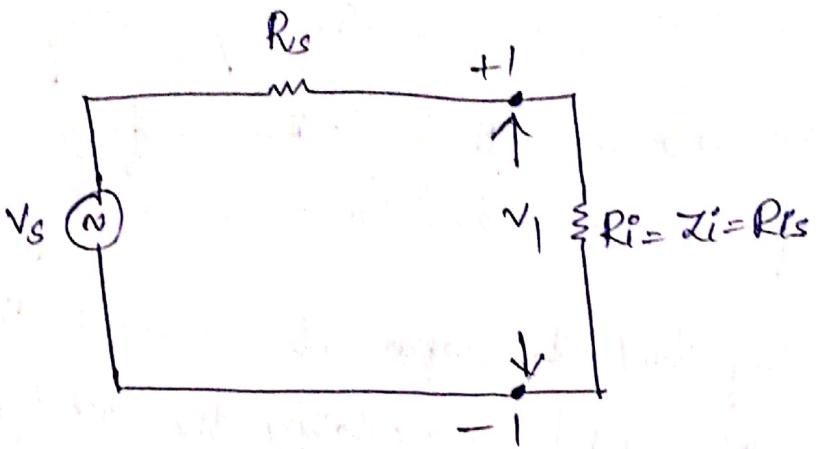consider the ~~network~~, equivalent circuit for the source as shown below:



voltage drop across input resistance ( $R_i^o$ ) is

$$V_1 = V_s \times \frac{R_i}{R_i + R_s}$$

$$\Rightarrow \frac{V_1}{V_s} = \frac{R_i}{R_i + R_s}$$

$$-A_{VS} = -A_V \times \frac{V_1}{V_s}$$

$$= A_V \times \frac{R_i}{R_i + R_s}$$

$$-A_{VS} = A_I \times \frac{\delta L}{R_i^o} \times \frac{R_i^o}{R_i^o + R_s}$$

$$-A_{VS} = \frac{A_I \times \delta L}{R_i + R_s}$$

NOTE: if voltage source is a ideal voltage source,

$$R_s = 0 \text{ then } A_{VS} = \frac{-A_I \delta L}{R_i} = -A_V$$

Overall Current Gain ( $A_{is}$ ) / Effect of Source resistance on Current gain / Current amplification taking into account the source resistance  $R_s$ :


$$A_{is}^o = \frac{i_L}{i_S} = -\frac{i_2}{i_S}$$

$$A_{is}^o = \frac{-i_2}{i_S} \times \frac{i_1}{i_1}$$

$$A_{is}^o = A_I \times \frac{i_1}{i_S}$$

$$A_I = \frac{i_2}{i_1}$$

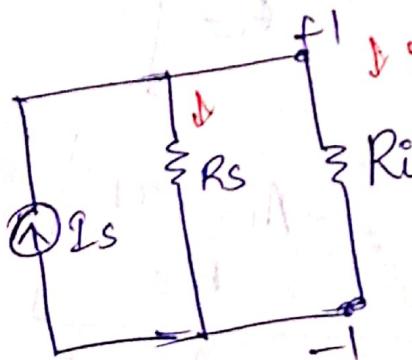Considering the Norton's equivalent circuit for source as shown below:



Current flowing through the amplifier input resistance may be written as

$$i_1 = i_S \times \frac{R_s}{R_s + R_i}$$

$$\Rightarrow \frac{i_1}{i_S} = \frac{R_s}{R_s + R_i}$$

$$-A_{is}^o = -A_i \times \frac{R_s}{R_s + R_i} \quad (12)$$

Relationship between  $A_{vs}$  &  $A_{is}$

we know that  $A_{vs} = \frac{-A_i \times \gamma L}{R_s + R_i}$

$$\epsilon - A_{is} = \frac{-A_i \times R_s}{R_s + R_i}$$

Taking the ratio of above two equations



$$\frac{A_{vs}}{A_{is}} = \frac{\gamma L}{R_s} \quad (13)$$

$$\Rightarrow A_{vs} = \frac{A_{is} \times \gamma L}{R_s}$$

$$\Rightarrow A_{is} = \frac{A_{vs} \times R_s}{\gamma L}$$

16/01/15

### C.E amplifier - Exact analysis:-

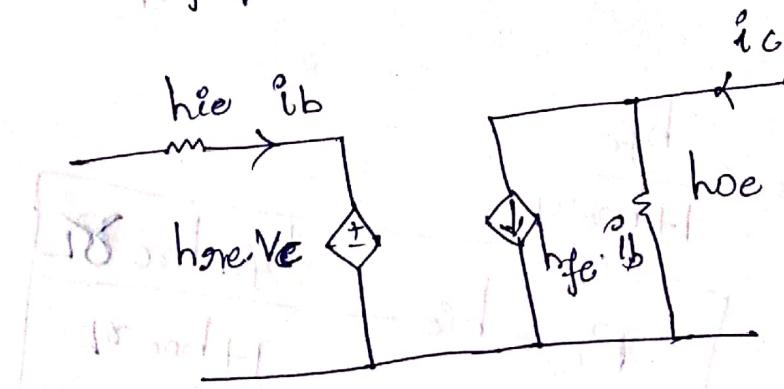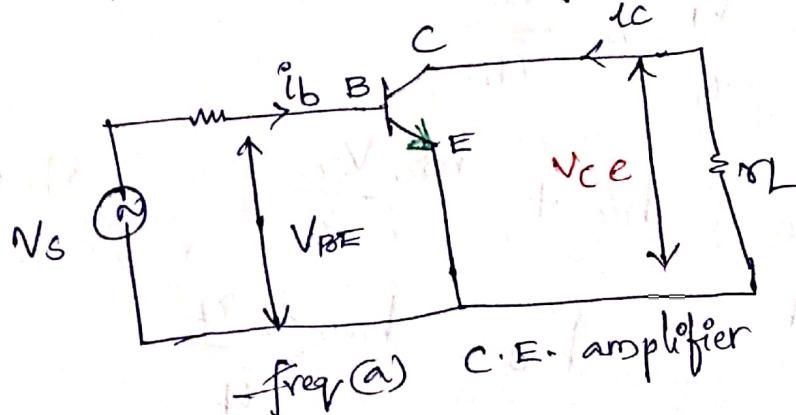

$$R_i = h_{ie} - \frac{h_{fe} h_{re} r_L}{1 + h_{oe} r_L}$$

Hybrid parameters equations

$$V_{be} = h_{ie} i_b + h_{re} V_{ce} \quad \textcircled{1}$$

$$i_{ce} = h_{fe} i_b + h_{oe} V_{ce} \quad \textcircled{2}$$

1) Current gain ( $A_i$ ): - 
$$-\frac{i_o}{i_b} = -\frac{i_c}{i_b}$$

$$-A_i = \frac{-h_{fe}}{1 + h_{oe} r_L} = \left( -\frac{i_c}{i_b} \right)$$

obtained by dividing  $\textcircled{2}$  by  $\textcircled{1}$

2) Input resistance ( $R_i$ ):-

$$R_i = \frac{V_1}{i_1} = \frac{V_{be}}{i_b}$$

$$\frac{V_{be}}{i_b} = h_{ie} + \frac{h_{re} \frac{V_{ce}}{i_b}}{i_b}$$

$$= h_{ie} - \frac{h_{re} \frac{i_c \gamma_L}{i_b}}{i_b}$$

$$-\frac{i_c}{i_b} = -\frac{h_{fe}}{1+h_{oe}\gamma_L}$$

$$R_i = h_{ie} - \frac{h_{fe} h_{re} \gamma_L}{1+h_{oe}\gamma_L}$$

$N_{ce} = -i_c$

3) Voltage gains ( $A_v$ ):-

$$A_v = \frac{V_2}{V_1} = \frac{V_{ce}}{V_{be}}$$

$$V_2 = +i_c \gamma_L$$

$$V_1 = i_1 \gamma_L$$

$$A_v = -\frac{i_c \gamma_L}{V_{be}}$$

$$A_v = -\frac{i_c}{i_b} \times \gamma_L \cdot \frac{i_b}{V_{be}}$$

$$A_v = \frac{-A_{ie} \gamma_L}{R_i}$$

4) Output admittance ( $y_o$ ):-

$$y_o = \frac{i_2}{v_2} = \frac{i_{ce}}{v_{ce}}$$

$$i_{ce} = h_{fe} i_b + h_{oe} v_{ce}$$

$$\frac{i_{ce}}{v_{ce}} = h_{fe} \frac{i_b}{v_{ce}} + h_{oe}$$

$$y_o = \frac{i_{ce}}{v_{ce}} = h_{oe} + h_{fe} \frac{i_b}{v_{ce}}$$


$$y_o = h_{oe} + h_{fe} \cdot \frac{i_b}{v_{ce}}$$

Applying KVL  $R_s \frac{i_b}{v_{ce}} + h_{ie} \frac{i_b}{v_{ce}} + h_{ic} v_{ce} = 0$


$$\frac{i_b}{v_{ce}} = -\frac{h_{ie}}{R_s + h_{ic}}$$

$$y_o = h_{oe} - \frac{h_{oe} \cancel{h_{fe}}}{R_s + h_{ie}}$$

2) C.B. amplifier exact analysis

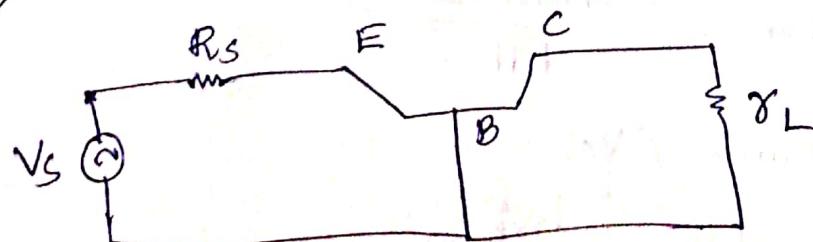

## Hybrid model

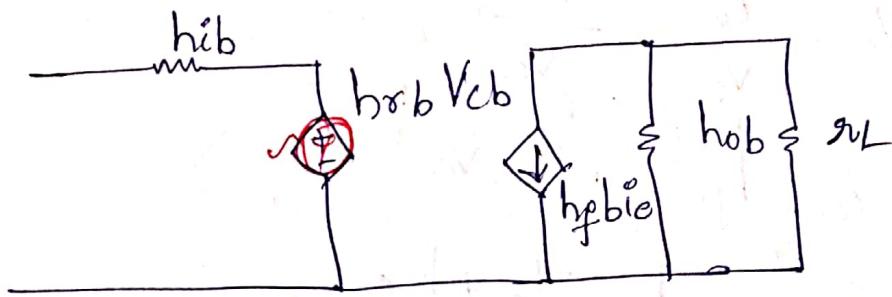

## Hybrid equations :-

$$V_{cb} = h_{ib} i_e + h_{rb} V_{cb}$$

$$i_{cb} = h_{fb} i_e + h_{ob} V_{cb}$$

### 1) current gain ( $A_{ib}$ )

$$A_{ib} = \frac{i_2}{i_1} = \frac{-i_{cb}}{i_e} = -\frac{h_{fb} r_L}{1 + h_{ob} r_L}$$

### 2) Input resistance ( $R_i$ )

$$R_i = h_{ib} - \frac{h_{fb} h_{rb} r_L}{1 + h_{ob} r_L}$$



### 3) voltage gain ( $A_{vb}$ )

$$A_{vb} = \frac{A_{ib} \cdot r_L}{R_i}$$

### 4) Output admittance ( $Y_o$ )

$$Y_o = h_{ob} - \frac{h_{rb} h_{fb}}{R_s + h_{ib}}$$
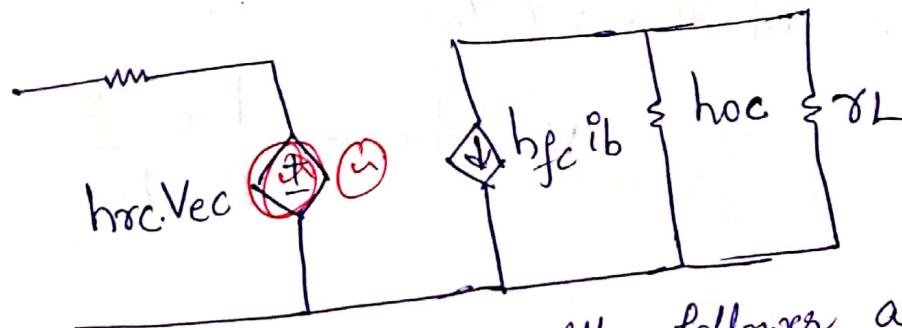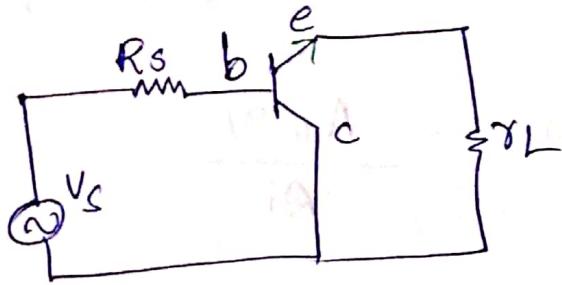
### 3) C.C exact analysis (emitter follower):-



C.C is also known as emitter follower as its voltage gain is unity and hence any change in the base voltage appears as an equal change across the load at the emitter ie the op signal at the emitter follows the input signal at the base.

-Hybrid equations of cc amplifier model

$$V_{bc} = h_{ic}^o i_b + h_{rc} V_{ec}$$

$$i_{ec} = h_{fc}^o i_b + h_{oc} V_{ec}$$

1) Current gain ( $A_i^o$ ) =  $\frac{-h_{fc}}{1+h_{oc} R_L}$


$$2) \text{ Input resistance } (R_i^o) = h_{ic} - \frac{h_{fe} h_{rc} r_L}{1 + h_{oc} r_L}$$

$$3) \text{ Voltage gain } (A_v) = \frac{-A_{ic} r_L}{R_i^o}$$

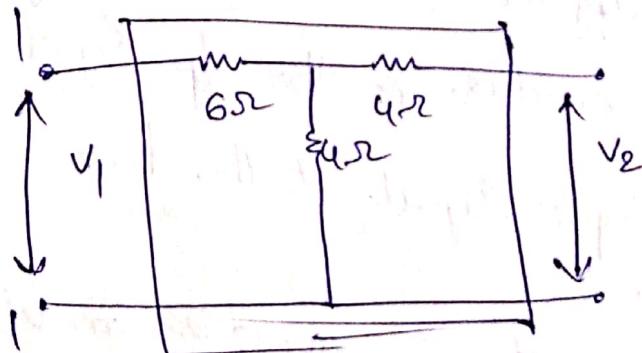4) Output admittance ( $Y_o$ )

$$Y_o = h_{oc} - \frac{h_{rc} \times h_{fe}}{R_s + h_{ic}}$$

Determine the value of h - parameters for the ckt shown below:



$$V_1 = 6I_1 + 4(I_1 + I_2) \Rightarrow V_1 = 10I_1 + 4I_2$$

$$V_2 = 4I_2 + 4(I_1 + I_2) \Rightarrow V_2 = 4I_1 + 8I_2$$

$$V_1 = 10I_1 \quad \Rightarrow \frac{V_1}{V_2} = 2.5$$

$$V_2 = 4I_1$$

$$h_{41} = \frac{V_1}{I_1} = 8\Omega \quad h_{21} = \frac{I_2}{I_1}$$

$$h_{12} = \frac{1}{2}, h_{21} = \frac{I_2}{I_p} = \frac{1}{2}$$

$$h_{22} = 18\Omega$$

2) A transistor is used in a CB amplifier has the following values of h-parameters  $h_{12} = 28.2$ ,  $h_{21} = -0.98A$ ,  $h_{22} = 5 \times 10^4$ ,

$$h_{ob} = 0.34 \times 10^6 S$$

Calculate the values of  $Z_{lp}$  resistance, O/p resistance, current & voltage gain if  $R_L = 1.2k\Omega$ . assumed  $R_s = 0$

$$\boxed{\text{Ans}} \quad A_i = \frac{-h_{21}}{1 + h_{21}R_L} = 0.98$$

$$R_i = h_{12} - \frac{h_{21}h_{ob}R_L}{1 + h_{21}R_L} = 28.6$$

$$A_v = \frac{A_i R_L}{Z_i} = 41.11$$

$$R_o = h_{ob} - \frac{h_{12}h_{21}}{R_s + h_{12}} = 56 k\Omega = 55.8 k\Omega$$

Q The h-parameters of a transistor used in a CE are  $h_{12} = 1k\Omega$ ,  $h_{21} = 1 \times 10^{-4}$ ,  $h_{fe} = 50$ ,  $h_{oe} = 100 \mu S$

Supplying  $R_L = 1k\Omega$ , the transistor is  $R_s = 100\Omega$

$$\boxed{\text{Ans}} \quad A_i = -\frac{h_{fe}}{1 + h_{fe}R_L} = -45.45$$

$$R_i = h_{ie} - \frac{h_{fe} \times R_L}{1 + h_{fe} \times R_L} = 995.45$$

$$A_v = -45.65$$

$$f_o = 10.2 \text{ kHz}$$

$$R_{os} = R_{in} \parallel R_L = 911 \Omega$$

$$\frac{A_i \times R_L}{R_i + R_S}$$

$$A_{vs} = \frac{A_i \times R_L}{R_i + R_S} = -28.63$$

$$A_{is} = \frac{A_i \times R_S}{R_S + R_i}$$

$$R_{os} = R_{in} \parallel R_L$$

$$R_{is} = R_i + R_S$$

3) A transistor used in a C.C circuit as shown below has the following set of h-parameters.

$$h_{ic} = 2 \text{ k}\Omega, h_{fc} = -51, h_{rc} = 1, h_{oc} = 25 \times 10^6 \text{ mhos.}$$

Find the values of I<sub>lp</sub> & o/p resistances current & voltage gain of amplifier stage. Use the exact hybrid formulas.

