

**Sol. :** Flip-flops required are

$$2^n \geq N$$

Here

$$N = 5$$

• • •


$$n = 3$$

i.e. three flip-flops are required.


$Q_n$	$Q_{n+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

**Table 9.25**[illegible]

— — —

 

100

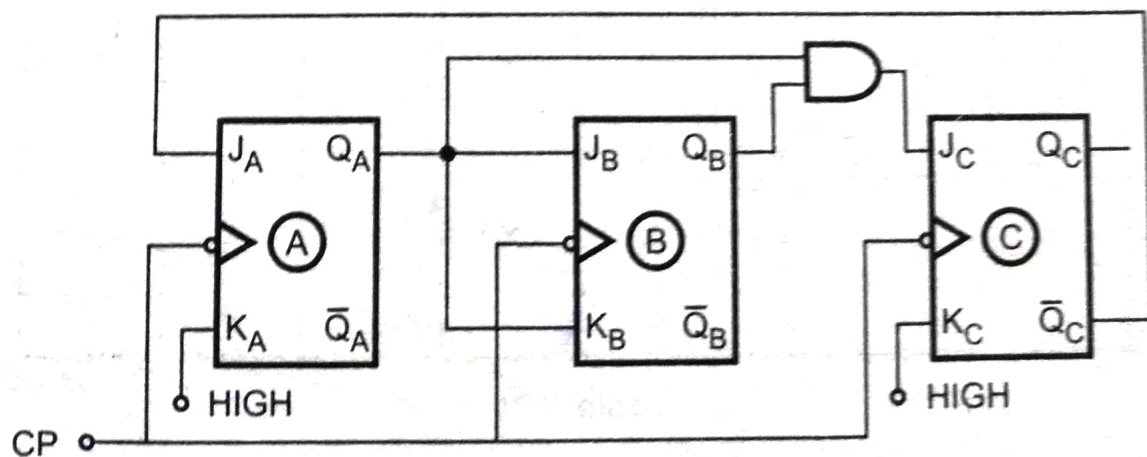

## Timing Diagram

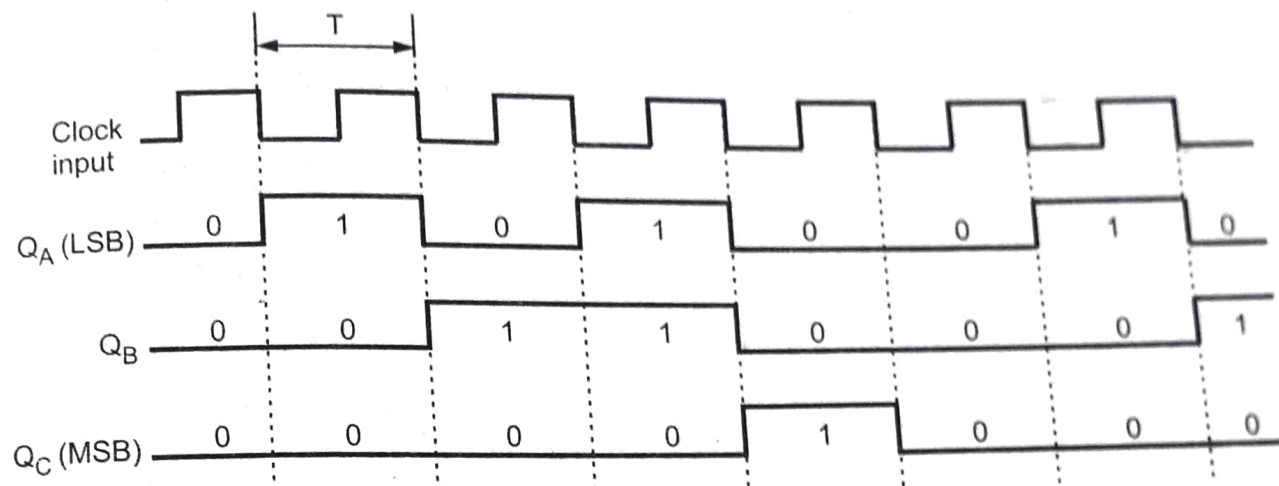


Fig. 9.77 Timing diagram

Ex. 9.11 : Design divide by 6 counter using T-flip-flop. Write state table and reduce the expression using K-map.

Sol. : For designing mod 6 counter using the formula

$$2^n \geq N$$

Here

$$N = 6$$

$\therefore$

$$n = 3$$

i.e. 3 flip-flops are required.

Excitation table for T-flip-flop

$Q_n$	$Q_{n+1}$	T
0	0	0
0	1	1
1	0	1
1	1	0

TABLE 9.27

State Table

CP	$Q_C$	$Q_B$	$Q_A$	$Q_{C+1}$	$Q_{B+1}$	$Q_{A+1}$	$T_C$	$T_B$	$T_A$
0	0	0	0	0	0	1	0	0	1
1	0	0	1	0	1	0	0	1	1
2	0	1	0	0	1	1	0	0	1
3	0	1	1	1	0	0	1	1	1
4	1	0	0	1	0	1	0	0	1
5	1	0	1	0	0	0	1	0	1

Table 9.28

## K-map Simplification

For  $T_C$

$Q_C$	$Q_B Q_A$			
	00	01	11	10
0	0	0	1	0
1	0	1	X	X

$$T_C = Q_C Q_A + Q_B Q_A$$

For  $T_B$

$Q_C$	$Q_B Q_A$			
	00	01	11	10
0	0	1	1	0
1	0	0	X	X

$$T_B = \overline{Q_C} Q_A$$

For  $T_A$

$Q_C$	$Q_B Q_A$			
	00	01	11	10
0	1	1	1	1
1	1	1	X	X

$$T_A = 1$$

## Logic Diagram

 


Fig. 9.79

## Synchronous Decade Counter

We know that in the decade counters we have to truncate normal counter sequence. Therefore, it is also called MOD-10 counter. Let us design the synchronous decade counter. Here, we will not use clear input to reset the counter after state 1010. Table 9.29 shows the excitation table for synchronous decade counter using T flip-flops.

## Excitation Table

Present State				Next State				Flip-flop Inputs			
$Q_D$	$Q_C$	$Q_B$	$Q_A$	$Q_{D+1}$	$Q_{C+1}$	$Q_{B+1}$	$Q_{A+1}$	$T_D$	$T_C$	$T_B$	$T_A$
0	0	0	0	0	0	0	1	0	0	0	1
0	0	0	1	0	0	1	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	1
0	0	1	1	0	1	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	1
0	1	0	1	0	1	1	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	1
0	1	1	1	1	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	1
1	0	0	1	0	0	0	0	1	0	0	1
1	0	1	0	X	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X	X



**For  $T_D$**

$Q_D \backslash Q_B Q_A$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	0	1	X	X

$T_D = Q_A Q_D + Q_A Q_B Q_C$

**For  $T_C$**

$Q_D \backslash Q_B Q_A$	00	01	11	10
00	0	0	1	0
01	0	0	1	0
11	X	X	X	X
10	0	0	X	X

$T_C = Q_A Q_B$

**For  $T_B$**

$Q_D \backslash Q_B Q_A$	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	X	X	X	X
10	0	0	X	X


$T_B = Q_A \bar{Q}_D$

**For  $T_A$**

$Q_D \backslash Q_B Q_A$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	X	X	X	X
10	1	1	X	X

$T_A = 1$

### Logic Diagram

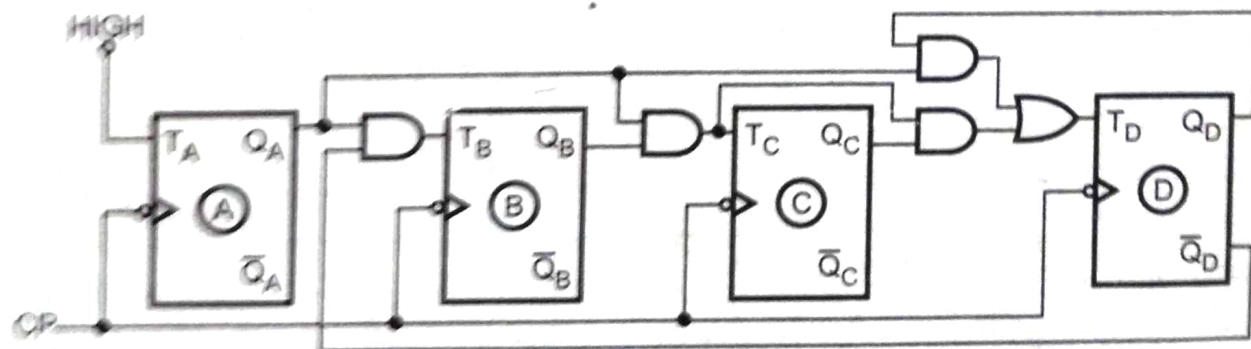

An up/down counter is one that is capable of progressing in increasing order or decreasing order through a certain sequence. An up/down counter is also called bidirectional counter. Usually up/down operation of the counter is controlled by UP/DOWN signal. When this signal is HIGH, counter goes through UP sequence, i.e. 0, 1, 2, 3, ..., n. When UP/DOWN signal is LOW counter follows reverse sequence i.e. n, n-1, n-2, ..., 1, 0. For 3-bit counters these sequences are : 0, 1, 2, 3, 4, 5, 6, 7 for up operation and 7, 6, 5, 4, 3, 2, 1, 0 for DOWN operation. This is illustrated in Table 9.31. The arrows in the Table 9.31 indicate the state-to-state movement of the counter for both its UP and its DOWN modes of operation.

State Table



CP	UP	$Q_C$	$Q_B$	$Q_A$	DOWN
0		0	0	0	
1		0	0	1	
2		0	1	0	
3		0	1	1	
4		1	0	0	
5		1	0	1	
6		1	1	0	
7		1	1	1	

Table 9.31

Let us design the 3-bit UP/  $\overline{\text{DOWN}}$  synchronous counter, using T flip-flops. Table 9.32 shows the excitation table for 3-bit UP/  $\overline{\text{DOWN}}$  synchronous counter.

Excitation Table

Input $\overline{\text{UP/DOWN}}$ (UD)	Present State			Next State			Flip-flop Inputs		
	$Q_C$	$Q_B$	$Q_A$	$Q_{C+1}$	$Q_{B+1}$	$Q_{A+1}$	$T_C$	$T_B$	$T_A$
0	0	0	0	1	1	1	1	1	1
0	0	0	1	0	0	0	0	0	1
0	0	1	0	0	0	1	0	1	1
0	0	1	1	0	1	0	0	0	1
0	1	0	0	0	1	1	1	1	1
0	1	0	1	1	0	0	0	0	1
0	1	1	0	1	0	1	0	1	1

0	1	1	1	1	1	0	0	0	1
1	0	0	0	0	0	1	0	0	1
1	0	0	1	0	1	0	0	1	1
1	0	1	0	0	1	1	0	0	1
1	0	1	1	1	0	0	1	1	1
1	1	0	0	1	1	0	0	0	1
1	1	0	1	1	1	0	0	1	1
1	1	1	0	1	1	1	0	0	1
1	1	1	1	0	1	1	1	0	1
1	1	1	1	1	0	0	1	1	1

Table 9.32

### K-Map Simplification


 


Fig. 9.87

### Logic Diagram

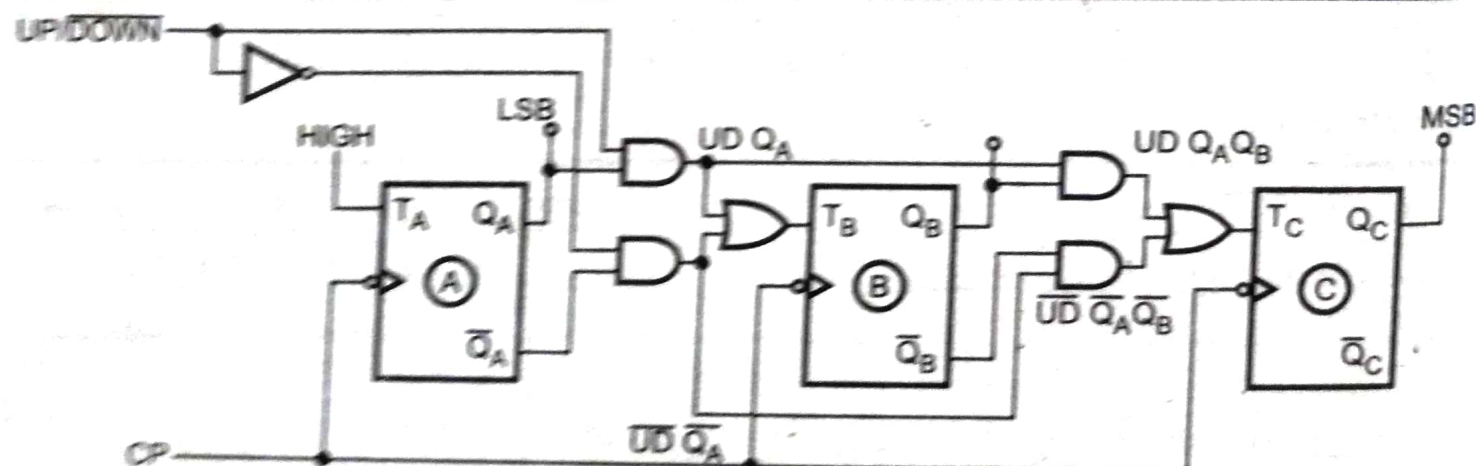



Design a asynchronous mod-6 gray code counter using T flip flops.

$$2^n \geq N$$

$$2^3 \geq 6$$

Deciml	present state			Next state			Excitation i/p's of		
	$Q_2$	$Q_1$	$Q_0$	$Q_{2H}$	$Q_{1H}$	$Q_{0H}$	$T_2$	$T_1$	$T_0$
0	0	0	0	0	0	1	0	0	1
1	0	0	1	0	1	1	0	1	0
3	0	1	1	0	1	0	0	0	1
2	0	1	0	1	1	0	1	0	0
6	1	1	0	1	1	1	0	0	1
7	1	1	1	0	0	0	1	1	1

101, 100 states are invalid i.e don't cares

for  $T_2$

$Q_1$	$Q_0$	00	01	11	10
0	0	0	0	0	1
1	X	X	1	0	

$$T_2 = Q_2 Q_0 + \bar{Q}_2 Q_1 \bar{Q}_0$$

for  $T_1$

$Q_1$	$Q_0$	00	01	11	10
0	0	0	1	0	0
1	X	X	1	0	


$$T_1 = Q_2 Q_0 + \bar{Q}_1 Q_0$$

for  $T_0$

$Q_1$	$Q_0$	00	01	11	10
0	0	1	0	1	0
1	X	X	1	1	

$$T_0 = Q_2 + \bar{Q}_1 \bar{Q}_0 + Q_1 Q_0$$

# Mod-6 gray code synchronous counter

 

## Parity bit generator

### odd parity bit generator

a	b	c	Parity bit (odd)
0	0	0	1

Ex. 9.37 : Design a 4-bit counter that counts either in binary or BCD depending on control line MODE. When MODE = 0, the counter is to count in binary, and when MODE = 1, the counter is to count in BCD. Select any flip-flops for implementation. Draw the logic diagram for realization.

Sol. : Table 9.40 shows the excitation table for BCD/Binary counter.

Input M	Present State				Next State				Flip-flop Inputs							
	Q <sub>A</sub>	Q <sub>B</sub>	Q <sub>C</sub>	Q <sub>D</sub>	Q <sub>A+1</sub>	Q <sub>B+1</sub>	Q <sub>C+1</sub>	Q <sub>D+1</sub>	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>	J <sub>D</sub>	K <sub>D</sub>
0	0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
0	0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
0	0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
0	0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
0	0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
0	0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
0	1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
0	1	0	0	1	1	0	1	0	X	0	0	X	1	X	X	1
0	1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
0	1	0	1	1	1	1	0	0	X	0	1	X	X	1	X	1
0	1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	X
0	1	1	0	1	1	1	1	0	X	0	X	0	1	X	X	1
0	1	1	1	0	1	1	1	1	X	0	X	0	X	0	1	X
0	1	1	1	1	0	0	0	0	X	1	X	1	X	1	X	1
1	0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
1	0	0	0	1	0	0	1	0	0	X	0	X	1	X	X	1
1	0	0	1	0	0	0	1	1	0	X	0	X	X	0	1	X
1	0	0	1	1	0	1	0	0	0	X	1	X	X	1	X	1
1	0	1	0	0	0	1	0	1	0	X	X	0	0	X	1	X
1	0	1	0	1	0	1	1	0	0	X	X	0	1	X	X	1
1	0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
1	0	1	1	1	1	0	0	0	1	X	X	1	X	1	X	1
1	1	0	0	0	1	0	0	1	X	0	0	X	0	X	1	X
1	1	0	0	1	0	0	0	0	X	1	0	X	0	X	X	1

Table 9.40



# K-Map Simplification

For  $J_A$

$M = 0$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	X	X	X	X

$M = 1$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	0	0	0
01	0	0	1	0
11	X	X	X	X
10	X	X	X	X

$$J_A = Q_B Q_C Q_D$$

For  $K_A$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	0	0	1	0
10	0	0	0	0

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	X	X
01	X	X	X	X
11	X	X	X	X
10	0	1	X	X

$$K_A = Q_B Q_C Q_D + Q_D M$$

For  $J_B$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	0	1	0
01	X	X	X	X
11	X	X	X	X
10	0	0	1	0

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	0	1	0
01	X	X	X	X
11	X	X	X	X
10	0	0	X	X

$$J_B = Q_C Q_D$$

For  $K_B$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	X	X
01	0	0	1	0
11	0	0	1	0
10	X	X	X	X

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	X	X
01	0	0	1	0
11	X	X	X	X
10	X	X	X	X

$$K_B = Q_C Q_D$$



For  $J_C$

$M = 0$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	1	X	X
01	0	1	X	X
11	0	1	X	X
10	0	1	X	X

$M = 1$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	0	1	X	X
01	0	1	X	X
11	X	X	X	X
10	0	0	X	X

$$J_C = Q_D \bar{M} + \bar{Q}_A Q_D$$

For  $K_C$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	1	0
01	X	X	1	0
11	X	X	1	0
10	X	X	1	0

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	X	1	0
01	X	X	1	0
11	X	X	X	X
10	X	X	X	X

$$K_C = Q_D$$

For  $J_D$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	1	X	X	1
10	1	X	X	1

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	1	X	X	1
01	1	X	X	1
11	X	X	X	X
10	1	X	X	X

$$J_D = 1$$


For  $K_D$

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	1	1	X
01	X	1	1	X
11	X	1	1	X
10	X	1	1	X

$Q_A Q_B \backslash Q_C Q_D$	00	01	11	10
00	X	1	1	X
01	X	1	1	X
11	X	X	X	X
10	X	1	X	X

$$K_D = 1$$

### Logic Diagram

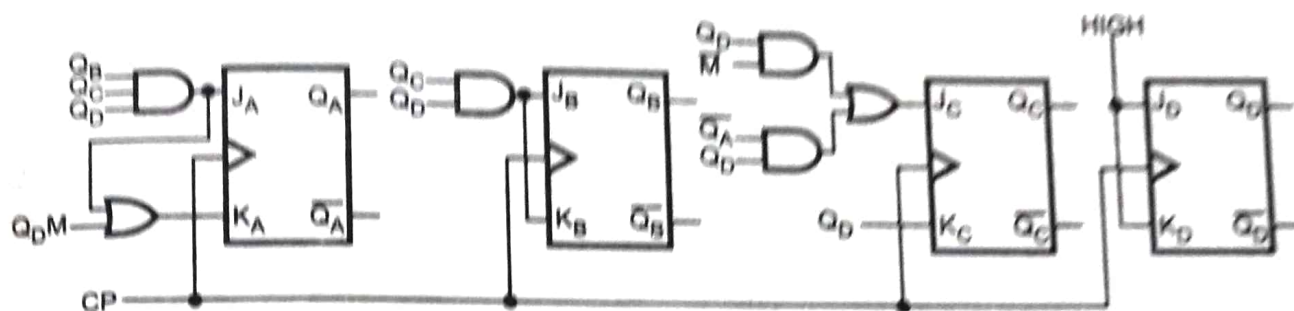**Fig. 9.103**

**Ex. 9.38 :** Design a synchronous Gray code up counter. Derive the expressions for the inputs of JK flip-flops.

**Sol. :** Table 9.41 shows the excitation table for synchronous Gray code up counter.

Present State				Next State				Flip-flop Inputs							
Q <sub>A</sub>	Q <sub>B</sub>	Q <sub>C</sub>	Q <sub>D</sub>	Q <sub>A+1</sub>	Q <sub>B+1</sub>	Q <sub>C+1</sub>	Q <sub>D+1</sub>	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>	J <sub>D</sub>	K <sub>D</sub>
0	0	0	0	0	0	0	1	0	X	0	X	0	X	1	X
0	0	0	1	0	0	1	1	0	X	0	X	1	X	X	0
0	0	1	0	0	1	1	0	0	X	1	X	X	0	0	X
0	0	1	1	0	1	1	0	0	X	0	X	X	0	X	1
0	1	0	0	1	1	0	0	1	X	X	0	0	X	0	X
0	1	0	1	0	1	0	0	0	X	X	0	0	X	X	1
0	1	1	0	0	1	1	1	0	X	X	0	X	0	1	X
0	1	1	1	0	1	0	1	0	X	X	0	X	1	X	0
1	0	0	0	0	0	0	0	X	1	0	X	0	X	0	X
1	0	0	1	1	0	0	0	X	0	0	X	0	X	X	1
1	0	1	0	1	0	1	1	X	0	0	X	X	0	1	X
1	0	1	1	1	0	0	1	X	0	0	X	X	1	X	0
1	1	0	0	1	1	0	1	X	0	X	0	0	X	1	X
1	1	0	1	1	1	1	1	X	0	X	0	1	X	X	0
1	1	1	0	1	0	1	0	X	0	X	1	X	0	0	X
1	1	1	1	1	1	1	0	X	0	X	0	X	0	X	1

**Table 9.41**

## K-Map Simplification

 


Fig. 9.104