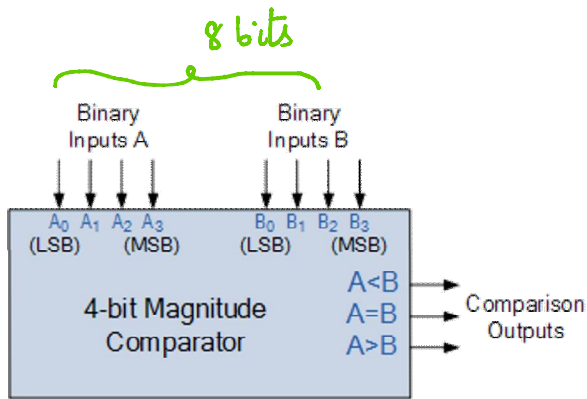


4-Bit Magnitude Comparator



2^8 combinations

$$\begin{array}{rcl}
 A & = & \overset{\text{MSB}}{A_3} A_2 A_1 \overset{\text{LSB}}{A_0} = 1110 \\
 B & = & B_3 B_2 B_1 B_0 = 0100
 \end{array}
 \left. \vphantom{\begin{array}{rcl} A \\ B \end{array}} \right\} A > B$$

The condition of $A=B$ is possible only when all the individual bits of one number exactly coincide with corresponding bits of another number.

$$A = B \Rightarrow AB + \bar{A}\bar{B} \Rightarrow A \odot B$$

$$x_i = A_i B_i + \bar{A}_i \bar{B}_i \Rightarrow A_i \odot B_i$$

where $i = 0, 1, 2, 3$.

$$x_0 = A_0 B_0 + \bar{A}_0 \bar{B}_0 \Rightarrow A_0 \odot B_0$$

$$x_1 = A_1 B_1 + \bar{A}_1 \bar{B}_1 \Rightarrow A_1 \odot B_1$$

$$x_2 = A_2 B_2 + \bar{A}_2 \bar{B}_2 \Rightarrow A_2 \odot B_2$$

$$x_3 = A_3 B_3 + \bar{A}_3 \bar{B}_3 \Rightarrow A_3 \odot B_3$$

In a 4-bit comparator the condition of $A > B$ can be possible in the following four cases:

in a 4-bit comparator the condition of $A > B$ can be possible in the following four cases:

1. If $A_3 = 1$ and $B_3 = 0 \Rightarrow A_3 \bar{B}_3$

2. If $A_3 = B_3$ and $A_2 = 1$ and $B_2 = 0 \Rightarrow (A_3 \odot B_3) \cdot A_2 \bar{B}_2$
 $\Rightarrow x_3 \cdot A_2 \bar{B}_2$

3. If $A_3 = B_3$, $A_2 = B_2$ and $A_1 = 1$ and $B_1 = 0 \Rightarrow (A_3 \odot B_3) \cdot (A_2 \odot B_2) \cdot A_1 \bar{B}_1$
 $\Rightarrow x_3 \cdot x_2 \cdot A_1 \bar{B}_1$

4. If $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$ and $A_0 = 1$ and $B_0 = 0$

$$(A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) A_0 \bar{B}_0$$

$$x_3 \cdot x_2 \cdot x_1 \cdot A_0 \bar{B}_0$$

$$A > B \Rightarrow A_3 \bar{B}_3 + x_3 \cdot A_2 \bar{B}_2 + x_3 \cdot x_2 \cdot A_1 \bar{B}_1 + x_3 x_2 x_1 \cdot A_0 \bar{B}_0$$

B) Similarly the condition for $A < B$ can be possible in the following four cases:

1. If $A_3 = 0$ and $B_3 = 1 \Rightarrow \bar{A}_3 B_3$

2. If $A_3 = B_3$ and $A_2 = 0$ and $B_2 = 1 \Rightarrow (A_3 \odot B_3) \bar{A}_2 B_2$
 $x_3 \cdot \bar{A}_2 B_2$

3. If $A_3 = B_3$, $A_2 = B_2$ and $A_1 = 0$ and $B_1 = 1$

$$(A_3 \odot B_3) (A_2 \odot B_2) \bar{A}_1 B_1$$

$$(x_3) (x_2) \bar{A}_1 B_1$$

4. If $A_3 = B_3$, $A_2 = B_2$, $A_1 = B_1$ and $A_0 = 0$ and $B_0 = 1$

$$(A_3 \odot B_3) (A_2 \odot B_2) (A_1 \odot B_1) \bar{A}_0 B_0$$

$$x_3 \cdot x_2 \cdot x_1 \cdot \bar{A}_0 B_0$$

$$A < B \Rightarrow \bar{A}_3 B_3 + x_3 \cdot \bar{A}_2 B_2 + x_3 \cdot x_2 \cdot \bar{A}_1 B_1 + x_3 x_2 x_1 \cdot \bar{A}_0 B_0$$

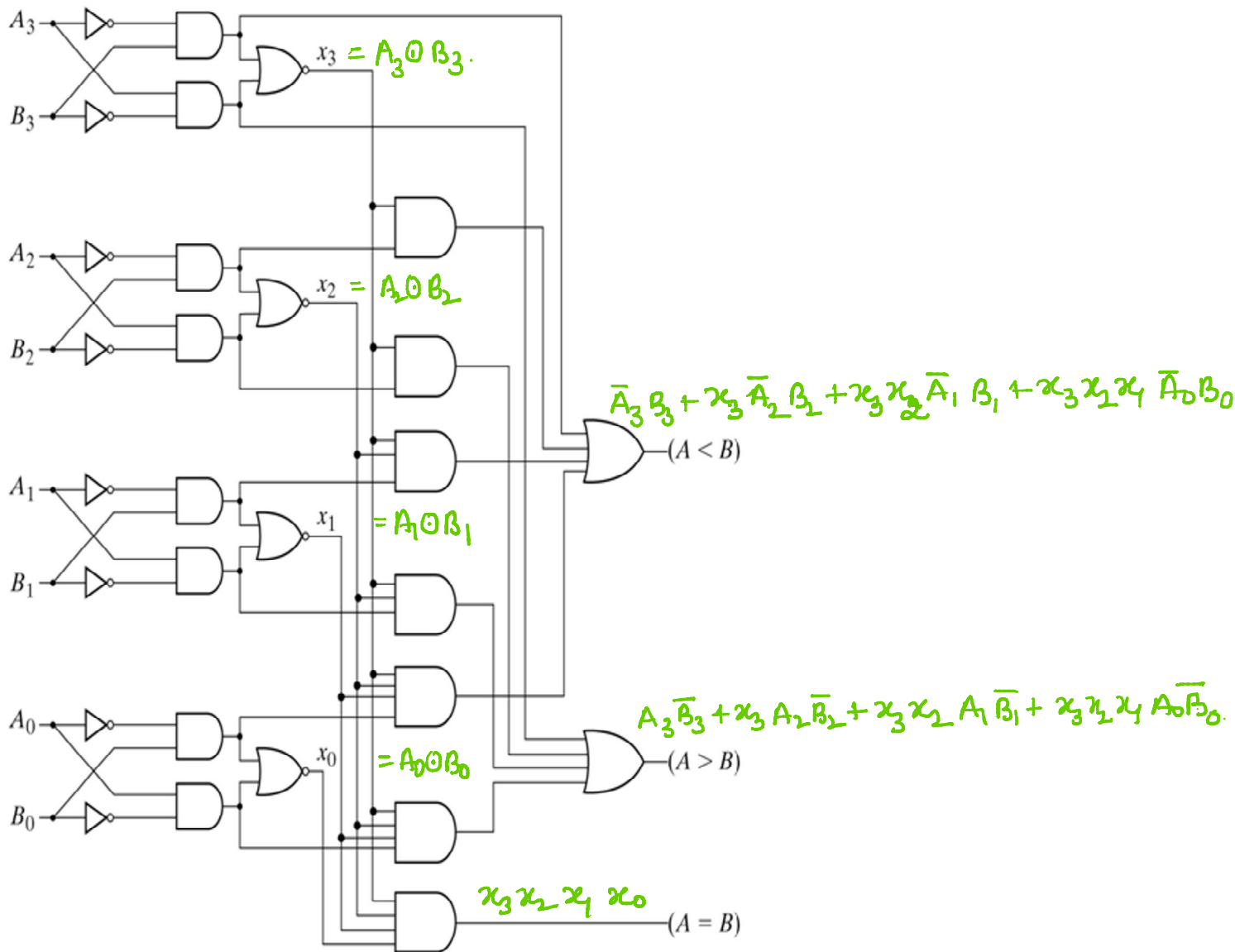


Fig. 4-17 4-Bit Magnitude Comparator