

## UNIT-1

## DC CIRCUITS

### → Electric Current :-

It is defined as a flow of charge per unit time. Denoted by 'I' or 'j'.  
i.e  $i = Q/t$  coulombs/sec (or) Ampera.

### → Electric Potential :-

It is the capacity of an element or conductor to do some work per unit charge.

Denoted with V.

$$\text{i.e } V = W/Q \text{ Joules/coulombs}$$

The difference between the potentials at both the ends of a conductor is known as Potential difference

(or) voltage.  $V_{AB}$

Units for voltage are volts (or), Joules/coulombs.

### → Electric Resistance :-

It is defined as the opposition offered by the conductor to the flow of charge. Denoted by R.

$R \propto \frac{l}{A} \rightarrow$  length  
 $A \rightarrow$  cross sectional area

$$\boxed{R = \frac{\rho l}{A}}$$

Units : OHMS ( $\Omega$ )

due to which the voltage across the terminals reduces as the current increases.

$$i = C \frac{dv}{dt}$$

$$dv = \frac{1}{C} i dt$$


$$\int_0^t dv = \frac{1}{C} \int_0^t i dt$$

$$v(t) - v(0) = \frac{1}{C} \int_0^t i dt$$

i.e.,

$$V_t = V_s - I_s R$$

$$V_t = V_s - I_s R$$

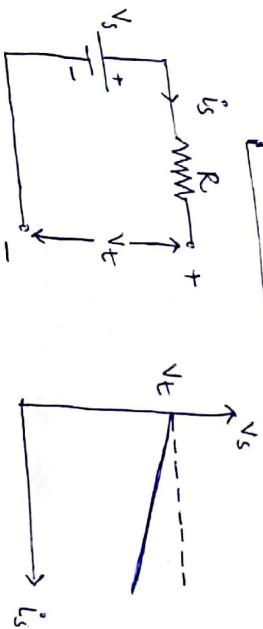



Expression for voltage.

$$W = \frac{1}{2} C V^2$$

- \* The energy stored in a capacitor
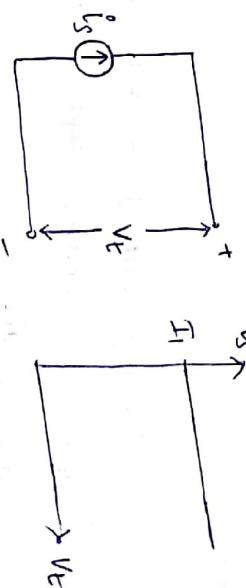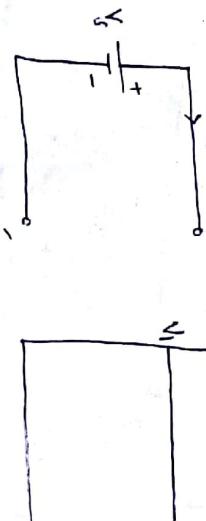
### Types of Sources


An ideal voltage source is an element in which the voltage  $V_s$  is completely independent of the current  $I_s$  flowing through its terminals.



→ An ideal current source is an element in which the source current is completely independent of the voltage across its terminals.

In practical case there exists an internal resistance in parallel with the current source due to which the current through its terminals reduces as the voltage is increased.

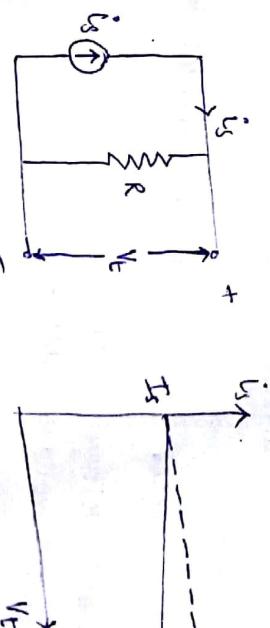
In practical case there exists an internal resistance in series with the voltage source,




The voltage & current sources are sub-divided into two types

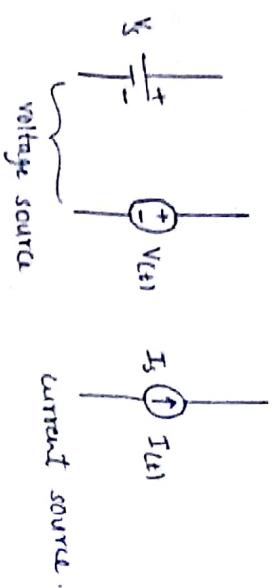1. Independent sources and
2. Dependent sources (voltage/current)

→ An Independent source is the one in which the voltage or current is completely independent of the other variables in the circuit.



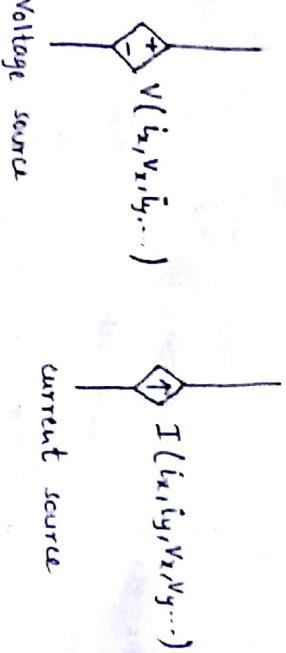→ A dependent source (voltage/current) is the one in which the voltage or current depends on other variables in the circuit




→ The dependent sources are further divided into

1. Voltage controlled voltage source
2. Current controlled voltage source.
3. Voltage controlled current source

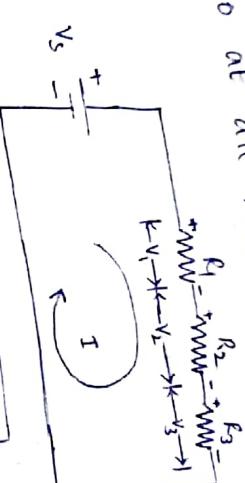4. Current controlled current source.

KIRCHOFF'S VOLTAGE LAW :- (KVL)

KVL states that the algebraic sum of the branch voltages around a closed path is equal to zero at all instants of time.



$$V_S - V_1 - V_2 - V_3 = 0$$


$$\Rightarrow V_S = V_1 + V_2 + V_3$$

KIRCHOFF'S CURRENT LAW (KCL) :-

KCL states that the algebraic sum of the currents at a node (or) junction is equal to zero.

(b)

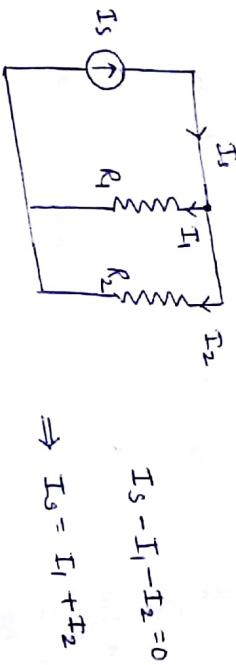KCL states that the sum of the currents entering into a node is equal to the sum of the currents leaving that node.




$$I_S - I_1 - I_2 = 0$$

→ Resistance in series  $\rightarrow R_T = R_1 + R_2 + R_3 + \dots$

$$\text{Resistance in parallel} \rightarrow \frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

- Q) Two lamps A and B takes current of 0.8A and 0.9A respectively when connected across 110V supply. If the lamps are connected in series across a 220V supply. Find the circuit current and the voltage across each lamp. Assume the filament resistance is unaltered.

Sol:-

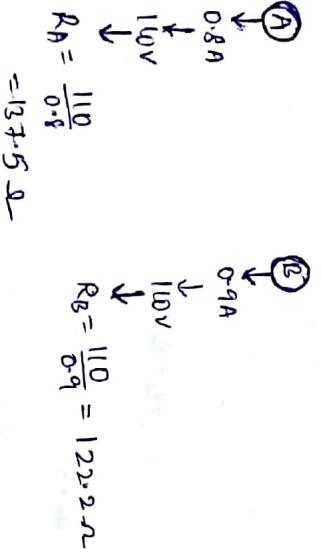

$$R_A = \frac{110}{0.8} = 137.5 \Omega$$

$$R_B = \frac{110}{0.9} = 122.2 \Omega$$

$$V_A = 159.5V$$

$$V_B = 97.5V$$

$$\boxed{R_T = 625}$$

$$I = \frac{V}{R_T} = \frac{220}{625} = 0.354A$$

across each lamp.

$$\boxed{\text{(A)} \quad P = i^2 R = \frac{V^2}{R}}$$


$$\boxed{\text{(B)} \quad P = \frac{V^2}{R}}$$

$$100 = \frac{220 \times 220}{R_T}$$

$$\boxed{R_T = 400}$$

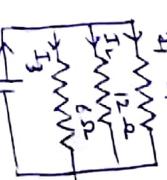- Q. 3 resistors  $4\Omega$ ,  $12\Omega$  and  $6\Omega$  are connected in parallel if the total current taken is 12A. Find the current through each resistor

$$\frac{1}{R_T} = \frac{1}{4} + \frac{1}{12} + \frac{1}{6}$$



$$\boxed{R_T = 2\Omega}$$

$$12A = I \Rightarrow I = \frac{V}{R_T}$$

$$\boxed{V = 24V}$$

$$I_1 = \frac{24}{4} = 6A$$

$$I_2 = \frac{24}{12} = 2A$$


$$I_3 = \frac{24}{6} = 4A$$

- Q. Two lamps of 250V, 100W and 200V, 100W are connected in series across a 250V supply

- calculate the circuit current and the voltage across each lamp.

- Q. In the circuit shown find the value of  $R_1$ .

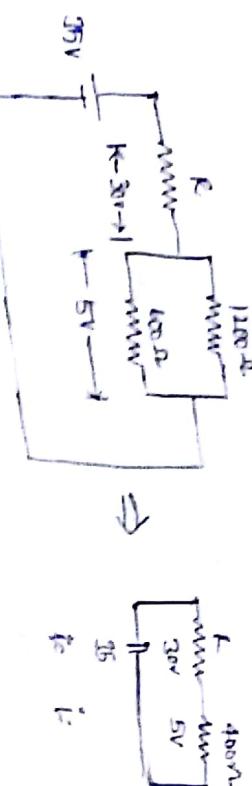Using Kirchhoff's law find the current through  $2\Omega$  resistor in the circuit shown




$$i = \frac{V}{R} = \frac{5}{400} = 0.0125$$

$$\frac{0.0125}{i} = \frac{30}{R}$$

$$[R = 2400\Omega]$$

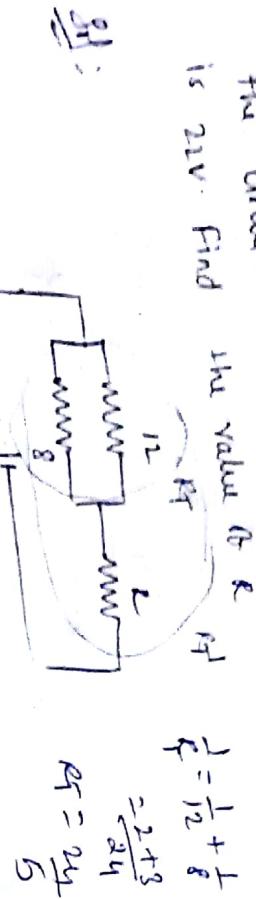- a. A resistance 'R' is connected in series with a parallel circuit comprising 2 resistors  $12\Omega$  and  $8\Omega$  respectively. The total power dissipated in the circuit is  $30W$  when the applied voltage is  $24V$ . Find the value of  $R$



$$\frac{1}{R} = \frac{1}{12} + \frac{1}{8}$$

$$= \frac{2+3}{24}$$


$$R = \frac{24}{5}$$

$$P = i^2 R = \frac{V^2}{R}$$

$$I_0 = \frac{24 \times 12}{R_{T1}}$$

$$R_{T1} = 6.914\Omega$$

$$[R = 2.11\Omega]$$

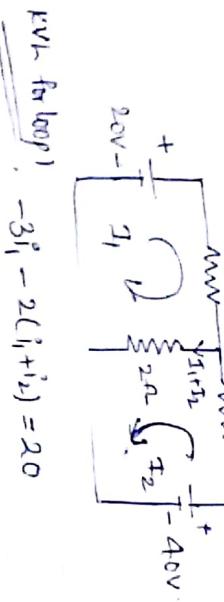

$$KVL \text{ for loop 1: } -3i_1 - 2(i_1 + i_2) = 20$$

$$-3i_1 - 2i_1 - 2i_2 = 20$$

$$-5i_1 - 2i_2 = 20 \quad \text{---(1)}$$

$$\begin{aligned} & KVL \text{ for loop 2:} \\ & -4i_2 - 2(i_1 + i_2) = 40 \\ & -4i_2 - 2i_1 - 2i_2 = 40 \\ & -2i_1 - 6i_2 = 40 \end{aligned}$$

$$+i_1 + 3i_2 = 20 \quad \text{---(2)}$$

$$(2) \times 5 = +5i_1 + 15i_2 = 100 \quad \text{---(3)}$$

$$\begin{aligned} & 13i_2 = 80 \\ & \text{Solve for } i_2: \\ & i_2 = \frac{80}{13} = 6.15 \end{aligned}$$

$$i_1 = 1.53$$

$$i_2 = 6.15$$

$$\begin{aligned} & \frac{i_1}{2} = \frac{i_2}{20} = \frac{1}{15-2} \\ & \frac{i_1}{20} = \frac{i_2}{80} = \frac{1}{13} \end{aligned}$$

$$[i_1 = 1.53]$$

$$[i_2 = 6.15]$$

$$[I = \pm 6.68]$$

Q Find the current through all the resistors in the

circuit shown by using KVL.

$$\text{Sol} : \quad \begin{array}{c} i_1 \quad 6\Omega \quad 3\Omega \quad i_2 \\ | \quad \diagdown \quad \diagup \quad | \\ \text{---} \quad \text{---} \quad \text{---} \\ i_{12} \quad 4\Omega \quad i_2 \end{array} - 45V$$

$$25V - \begin{array}{c} + \\ \text{---} \\ i_1 \end{array}$$

$$\text{Loop 1} : 25 - 6i_1 - 4(i_1 + i_2) = 0$$

$$25 - 10i_1 - 4i_2 = 0 \quad \text{---(1)}$$

$$\text{Loop 2} : 45 - 3i_2 - 4(i_1 + i_2) = 0$$

$$45 - 4i_1 - 7i_2 = 0 \quad \text{---(2)}$$

$$\begin{matrix} i_1 & i_2 & i & \\ -4 & 25 & -10 & -4 \\ -7 & 45 & -4 & -7 \end{matrix}$$

$$\frac{i}{-180+135} = \frac{i_2}{-160+450} = \frac{1}{70-16}$$


$$\frac{i}{-5} = \frac{i_2}{350} = \frac{1}{54}$$

$$i_1 = -0.092 \text{ A}$$

$$i_2 = -6.481 \text{ A}$$

$$i_1 + i_2 = 6.389 \text{ A}$$

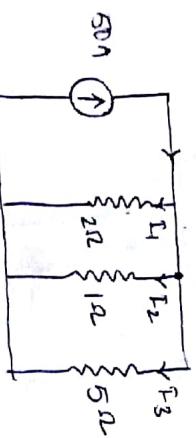Q. Find the currents flowing through all the resistors in the circuit shown



i.e. in a series circuit the voltage across any n<sup>th</sup> resistor is equal to the ratio of

$$S_D = I_1 + I_2 + I_3 \quad \text{---(1)}$$

$$I_1 = \frac{V}{R_1}, \quad I_2 = \frac{V}{R_2}, \quad I_3 = \frac{V}{R_3}$$

$$R_D = \frac{V}{2} + V + \frac{V}{5} = \frac{17V}{10}$$


$$R_D = 1.7V$$

$$[V = 29.411]$$

$$i_1 = 14.70 \text{ A}$$

$$i_2 = 29.41 \text{ A}$$

$$i_3 = 5.882 \text{ A}$$

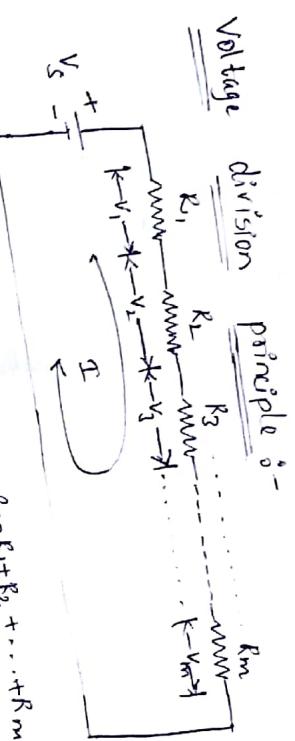

$$I = \frac{V_s}{R_T}$$

$$V_1 = I R_1$$

$$V_2 = I R_2$$


$$V_m = I R_m$$

$$V_m = \frac{R_m}{R_T} \times V_s$$

$$\boxed{V_m = \frac{R_m}{R_T} \times V_s}$$

its resistance to the total resistance multiplied by the source voltage

### Current division principle :-

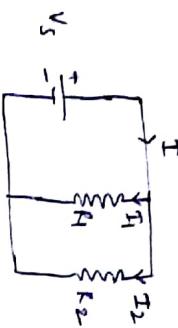

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

$$I_1 = \frac{V_s}{R_1} \Rightarrow V_s = I_1 R_1$$

$$I_2 = \frac{V_s}{R_2} \Rightarrow V_s = I_2 R_2$$

$$I = \frac{V_s}{R_T} = \frac{V_s}{R_1 + R_2} (R_1 + R_2)$$

$$= \frac{I_1 R_1 (R_1 + R_2)}{R_1 R_2}$$

$$\Rightarrow I = \frac{I_1 (R_1 + R_2)}{R_2}$$

$$\Rightarrow I_1 = \frac{R_2}{R_1 + R_2} \times I$$

Similarly,  $\Rightarrow I_2 = \frac{R_1}{R_1 + R_2} \times I$

### Generalised Equation

$$I_1 = \frac{R_2}{R_1 + R_2} \times I$$

$R_T$  = resultant opp. resistor in parallel



i.e. In a parallel circuit the current flowing through any 1<sup>st</sup> resistor is equal to the ratio of its opposite parallel resistance to the sum of

its all the resistances and opposite resistance multiplied by the total current entering into the circuit.
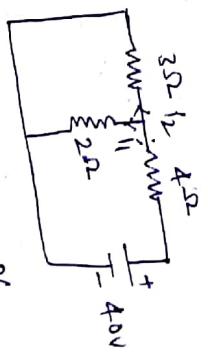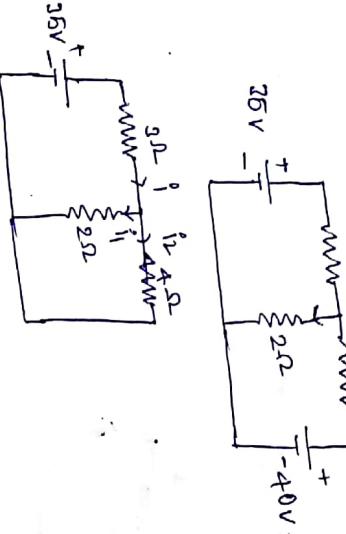
### Superposition theorem :-

Superposition theorem states that, in a linear circuit with two or more sources, any element is equal to the algebraic sum of the responses with individual sources acting alone, while the other sources are non-operative.

Q. By using superposition theorem, find the current following through  $2\Omega$  resistor in the circuit shown.



$$R_T = \frac{6}{5} + 4 = \frac{26}{5}$$

$$I = \frac{40}{26} = 1.538 A$$

$$X = \frac{i_1}{i_2} = \frac{R_2}{R_1}$$

$$\frac{X}{8.045-X} = \frac{4}{2}$$

$$7.69 - X = \frac{3}{2}$$

$$2X = 23.04 - 3X$$


$$5X = 23.04$$

$$X = 4.61 A$$

$$I = 16.15 - 2X$$

$$I = 5.38 A$$

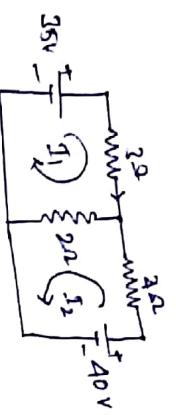Verify superposition theorem for the above circuit



$$35 - 3i_1 - 2(i_1 + i_2) = 0$$


$$40 - 5i_1 - 2(i_1 + i_2) = 0 \quad \text{--- (1)}$$

$$40 - 4i_2 - 2(i_1 + i_2) = 0$$

$$40 - 2i_1 - 5i_2 = 0 \quad \text{--- (2)}$$


$$\begin{cases} i_1 = 5A \\ i_2 = 5A \end{cases}$$

$$i_1 + i_2 = 10A$$

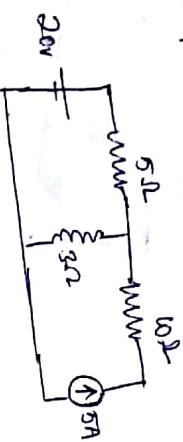

Find the current through  $3\Omega$  resistor by using super. pos. theorem.

Thevenin's theorem states that linear circuit with two terminals having no. of voltage, current sources and resistors can be replaced by a simple equivalent circuit consisting of a single voltage source in series with a single resistance, where source value is equal to the open circuit voltage measured across the terminals and resistance value is equal to the equivalent resistance measured through the terminals with all the energy sources deactivated. Thevenin's equivalent circuit is shown below:

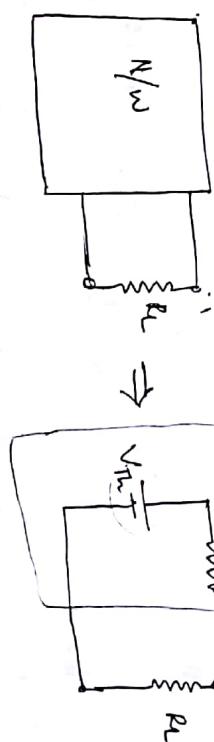


$$R_T = \frac{15}{8} + 10 = \frac{95}{8}$$

$$\frac{i_1}{i_2} = \frac{R_2}{R_1}$$

$$\frac{2}{3} = \frac{5}{3}$$

$$5 = 25 - 5R$$

$$\text{Ans: } R = 5.625\Omega$$

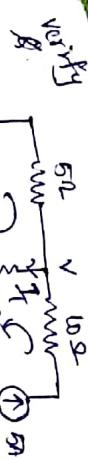

$$5 = \frac{5V + 10V}{15}$$

$$\frac{5}{5+10} \times 5 = \frac{5}{15} \times 5 = 1.67A$$

$$13.5 = 8V$$

$$\frac{13.5 - 8V}{8} =$$

$$I = V_3 = \frac{16.8 - 5}{3} = 5.625$$

### THEVENIN'S THEOREM

Verify




$$5 = \frac{5V + 10V}{15}$$


$$13.5 = 8V$$

$$\frac{13.5 - 8V}{8} =$$

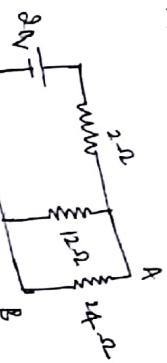
Q. Find the Thvenin's equivalent circuit across AB  
for the circuit shown.



Given

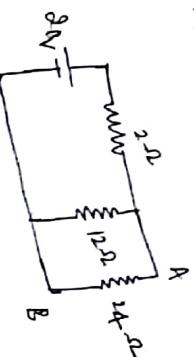

To find  $V_{TH}$

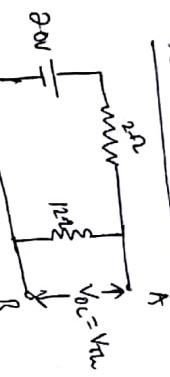


$$i = \frac{20}{14} = 1.428$$

$$20 - 2.856 = \boxed{V_{TH} = 17.136}$$

$$= 17.14 \text{ V}$$

To find  $R_{TH}$

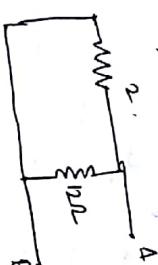

$$R_{TH} = 1.714 \Omega$$

$$17.136 \text{ V} \rightarrow I_2 = \frac{17.14}{25.714} = 0.66 \text{ A}$$


To find  $I_L$



Q. Verify Thvenin's theorem for the above circuit?

For the circuit shown below.

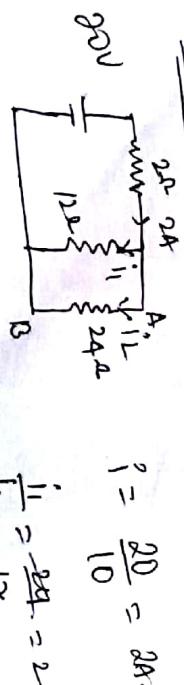
Q. Determine Thvenin's equivalent circuit across AB



$$i = \frac{20}{10} = 2 \text{ A}$$

$$\frac{1}{i} = \frac{24}{12} = 2$$

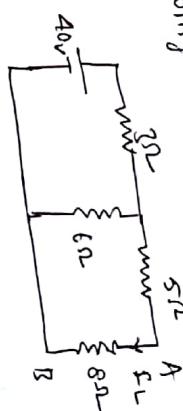Q. By using Thvenin's theorem find the current flowing in 8Ω resistor



To find  $V_{TH}$




$$i = \frac{40}{9} = 4.44 \text{ A}$$

$$V_{TH} = 26.64 \text{ V}$$



$$\boxed{R_{TH} = 1.714 \Omega}$$


To find  $R_{TH}$

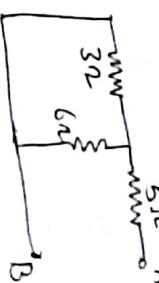

$$R_{TH} = 1.714 \Omega$$

$$\boxed{I_L = 1.714 \text{ A}}$$
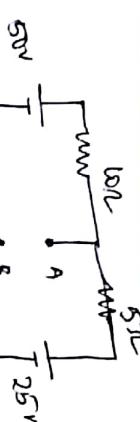
$$\begin{aligned} \frac{i_1}{i_2 - i_1} &= 2 \\ i_1 &= 4 - 2i_1 \\ i_1 &= 2 \\ \frac{i_1}{i_2} &= \frac{4}{3} \\ i_2 &= \frac{2}{3} \end{aligned}$$




To find  $V_{RN}$ .


$$25 - 5i = \frac{25}{25} i$$

$$25 - 10i - 25 = 0$$

$$25 = 10i \\ i = \frac{25}{10} = 2.5A$$

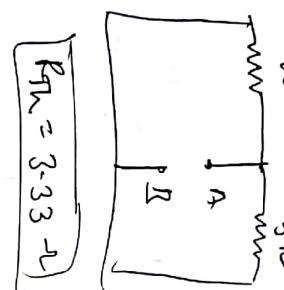

To find  $R_{RN}$

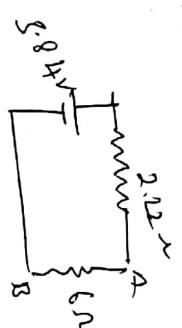


$$R_N = 2.12 + 6 \\ R_N = 8.22 \Omega$$

$$I = \frac{3.84}{8.22} = 0.467A$$


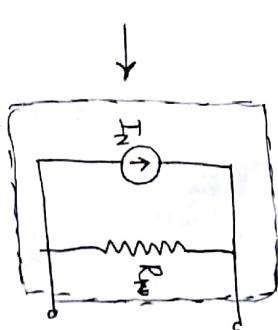
### NORTON'S THEOREM :-

Norton's theorem states that any linear circuit with no dc voltage, current sources and resistors can be replaced by an equivalent circuit consisting of single current source in parallel with a single resistor, where the current value through the terminals and the resistance value is equal to the short circuit current measured through the terminals with all the energy sources deactivated.



↳ Norton's equivalent circuit

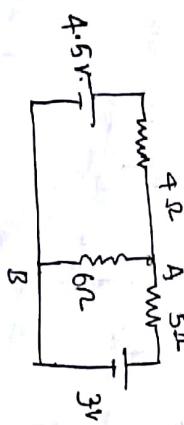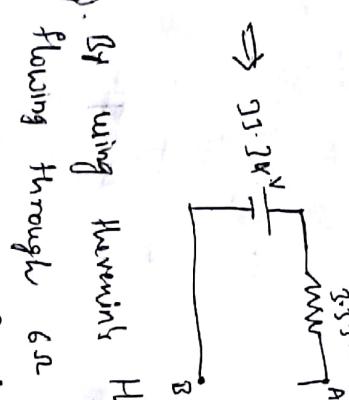- Q. By using Norton's theorem find the current flowing through  $6\Omega$  resistance




To find  $V_{RN}$

$$4.5 - 5i = \frac{5}{6} i \\ i = \frac{4.5}{9} = 0.5A$$


$$5 - 5i = \frac{5}{6} i \\ i = \frac{5}{11} = 0.455A$$

- Q. Find the Norton's equivalent circuit across AB for the ckt shown.


$$V_RN = 4.5 - 0.66 \\ = 3.84V$$

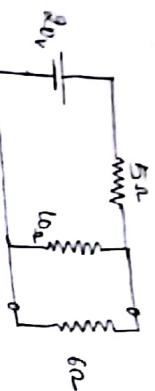


To find  $T_N$

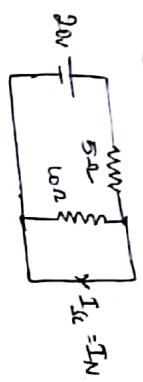

$$I_N = \frac{20}{5} = 4A.$$

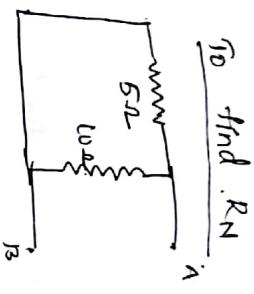
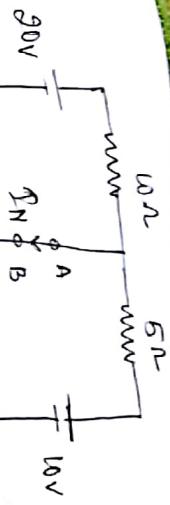
$$R_N = \frac{10 \times 5}{15} = 3.33\Omega$$



To find  $T_N$ .

$$I_1 = \frac{10}{10} = 1A$$


$$I_2 = \frac{10}{5} = 2A$$

$$T_N = 4A$$

To find  $R_N$ .

$$\frac{10 \times 5}{10+5} = 3.33\Omega$$

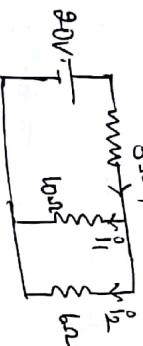Verify Norton's theorem for the above circuit



$$I = \frac{20}{8.75} = 2.285$$


$$\frac{20 \times 2}{x} = \frac{6}{10}$$

$$20 \cdot 8.75 - 10x = 6x$$


$$16x = 20 \cdot 8.75$$

$$x = 1.4285A$$

Determine the circuit shown.

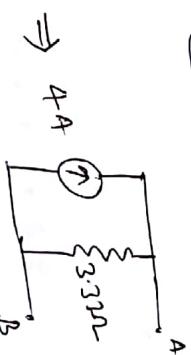

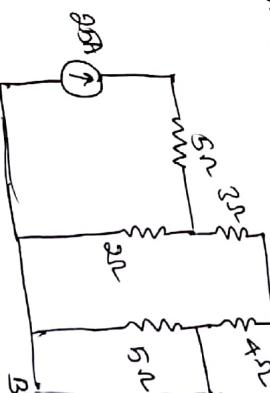Determine the Norton's equivalent circuit across AB



To find  $T_N$ .


$$\frac{1}{2} = \frac{2}{4}$$

$$\frac{x}{6.55-x} = \frac{2}{4}$$

$$x = 1.21 - 2x$$

$$3x = 1.21$$

$$x = 0.4035$$

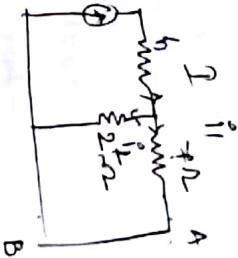

$$\frac{1}{2} = \frac{2x}{4+x}$$

$$6.55-x = \frac{2x}{4+x}$$

$$x = 1.21 - 2x$$

$$3x = 1.21$$

$$x = 0.4035$$

- Q8. Determine the Norton's equivalent circuit at terminals AB for the circuit shown.

- Q9. Determine the Norton's equivalent circuit at terminals AB.

$$x = 5\Omega$$


$$I_N = 5A$$

$$R_N = 5\Omega$$

To find  $R_N$



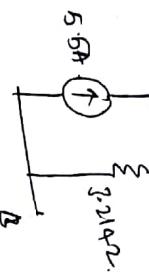
$$R_N = \frac{9 \times 5}{14} = 3.214 \Omega$$



loop

(or) Mesh Analysis :-

for voltage source (KVL)

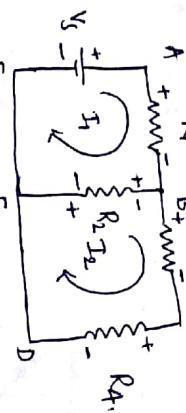

KVL  $\rightarrow$  ABCEDA

$$V_S - I_1 R_1 - (I_1 - I_2) R_2 = 0$$

$$-I_1(R_1 + R_2) + I_2 R_2 + V_S = 0 \quad \text{--- (1)}$$

KVL  $\rightarrow$  BCDEFB


$$-I_2 R_3 - R_4 I_2 - (I_2 - I_1) R_2 = 0$$

$$-I_2 R_3 - R_4 I_2 - I_2 R_2 + I_1 R_2 = 0$$

$$-I_1 R_2 + I_2(R_2 + R_3 + R_4) = 0 \quad \text{--- (2)}$$

By solving eqns (1) & (2) the currents  $I_1$  and  $I_2$  can be determined.

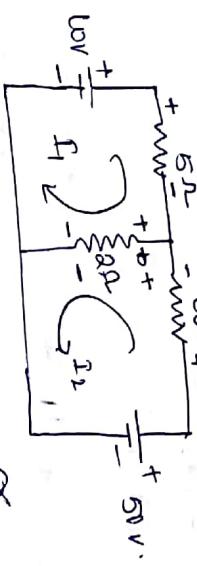Q. Find the currents  $I_1$  &  $I_2$  by using mesh analysis in the circuit shown.



$$\boxed{ax + by = c}$$

$$10 - 5I_1 - 2(I_1 + I_2) = 0 \quad \text{--- (1)}$$

$$50 - 10I_2 - 2(I_1 + I_2) = 0 \quad \text{--- (2)}$$

$$I_1 = +\frac{V_S}{4} \quad I_2 = +\frac{33}{8}$$


$$\begin{matrix} I_1 & I_2 & 1 \\ 1 & 2 \\ 12 & -50 & I_2 \\ & & 12 \end{matrix}$$

$$\frac{I_1}{-100 + 120} = \frac{I_2}{-20 + 350} = \frac{1}{84 - 4}$$

$$\frac{I_1}{20} = \frac{I_2}{330} = \frac{1}{80}$$

$$I_1 = \frac{V_S}{4} \quad I_2 = \frac{33}{8} \Omega$$

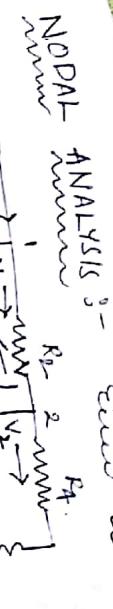Q. Calculate the current through 6Ω resistor by using loop analysis.



$$\underline{\text{Loop 1}} \quad 10 - 2I_1 - 4(I_1 + I_2) = 0$$

$$-6I_1 - 4I_2 + 10 = 0 \quad \text{---} \textcircled{1}$$

$$6I_1 + 4I_2 = 10$$

$$\underline{\text{Loop 2}} \quad -I_2 - 4(I_1 + I_2) - 6(I_2 - I_3) = 0$$

$$-I_2 - 4I_2 - 4I_2 - 6I_2 + 6I_3 = 0 \quad \text{---} \textcircled{2}$$

$$-4I_1 - 11I_2 + 6I_3 = 0$$

$$\begin{cases} -4I_2 + 6I_3 = 0 \\ 8I_3 = 11I_2 \end{cases} \quad \text{---} \textcircled{2}$$

Loop 3

$$20 - 4I_3 - 6(I_3 - I_2) = 0$$

$$-6I_2 + 10I_3 + 20 = 0 \quad \text{---} \textcircled{3}$$

By solving equations  $\textcircled{1}$  &  $\textcircled{2}$  the node voltages  $V_1$  &

$$I_1 = \frac{65}{41} = 0.915A$$

$$I_2 = \frac{50}{41} = 1.126A$$

$$I_3 = \frac{190}{41} = 2.0676A$$

$$I_3 - I_2 = 1.55A$$


KCL at node 1

$$10 = \frac{V_1}{5} + \frac{V_1 - V_2}{3}$$

$$10 = \frac{V_1}{5} + \frac{V_1}{3} - \frac{V_2}{3}$$

$$10 = \frac{8V_1}{15} - \frac{V_2}{3} \quad \text{---} \textcircled{1}$$

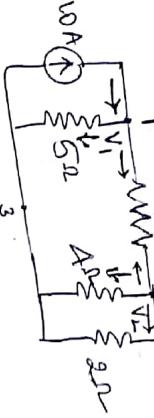Q. By using nodal analysis find the current flowing through  $3\Omega$  resistance in the circuit shown



KCL at node 1

$$10 = \frac{V_1}{5} + \frac{V_1 - V_2}{3}$$

node 2

$$\frac{V_2 - V_1}{3} + \frac{V_2}{4} + \frac{V_2}{2} = 0$$

$$\frac{V_2}{3} + \frac{V_2}{4} + \frac{V_2}{2} - \frac{V_1}{3} = 0$$

$$\frac{4V_2 + 3V_2 + 6V_2}{12} - \frac{V_1}{3} = 0$$

$$13V_2 = \frac{V_1}{3}$$

$$13V_2 = 4V_1$$

$$V_0 = \frac{8V_1}{4} - \frac{4V_1}{13 \times 3}$$

$$V_0 = \frac{8V_1}{15} - \frac{4V_1}{39} = V_1 (0.53 - 0.10)$$


$$V_1 = \frac{10}{0.431}$$

$$V_1 = 23.201 V$$

$$V_2 = 4.139 V$$

$$I = 6.354 A$$

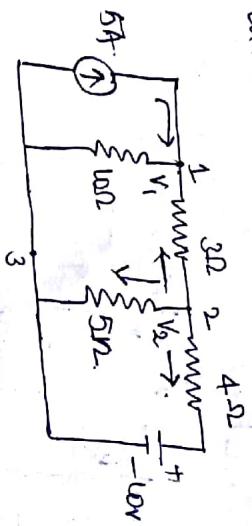- Q. Write the node voltage equation and determine the current through  $3\Omega$  resistance.



KCL at 1:

$$5 = \frac{V_1}{10} + \frac{V_1 - V_2}{3}$$

$$5 = \frac{V_1}{10} + \frac{V_1}{3} - \frac{V_2}{3}$$

node 2

$$5 = \frac{13V_1 - V_2}{30} - 1$$

$$\frac{V_2 - V_1}{3} + \frac{V_2}{5} + \frac{V_2 - 10}{4} = 0$$

$$\frac{V_2}{3} + \frac{V_2}{5} + \frac{V_2}{4} - \frac{V_1}{3} - \frac{10}{4} = 0$$

$$\frac{4\frac{7}{5}V_2}{60} - \frac{V_1}{3} = \frac{5V_2}{12} - 2$$

$$= \frac{4\frac{7}{5}V_2 - 20V_1}{60} = \frac{5}{2}$$

$$\frac{13V_1 - 10V_2}{30} = 5$$

$$13V_1 - 10V_2 = 150$$

$$-20V_1 + 4\frac{7}{5}V_2 = 150 - 1$$

$$20V_1 - 4\frac{7}{5}V_2 = -150 - 1$$

$$\begin{cases} V_1 = 20.802 V \\ V_2 = 12.043 V \end{cases}$$

$$I = 2.99 A$$

Time domain analysis :-

R\_L series circuit :-




$$KVL \rightarrow -V_s + V_R + V_L(t) = 0$$

$$\Rightarrow -V_s + I_L(t)R + L \frac{dI_L(t)}{dt} = 0$$

$$I_L(t) = k_1 + k_2 e^{-t/\tau}$$

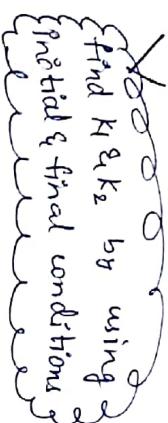~~At t=0~~  
find  $k_1$  &  $k_2$  by using  
{initial & final conditions}



$$\therefore I_L(t)(0^+) = I_L(t)(\infty) = 0$$

The solution for the above eqn is

$$I_L(t) = k_1 + k_2 e^{-t/\tau}$$

At the moment of switching the inductor the current does not change  
i.e.,  $I_L(0^-) = I_L(\infty) = 0$

Substituting the initial condn's we get

$$0 = k_1 + k_2$$

$$\Rightarrow \boxed{k_2 = -k_1}$$

when  $t \rightarrow \infty$  the inductor acts as short circuit

$$\text{and } I_L(\infty) = V_s/R.$$

Substituting the final conditions we get


$$k_1 = V_s/R$$

Substituting the constants  $k_1$  &  $k_2$  values

$$\boxed{I_L(t) = \frac{V_s}{R}(1 - e^{-t/\tau})} *$$

where  $\tau = \frac{L}{R}$

RC SERIES CKT

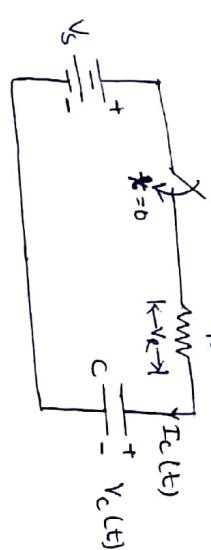

$$KVL \rightarrow -V_s + I_C(t)R + V_C(t) = 0$$

$$\Rightarrow -V_s + I_C(t)R + V_C(t) = 0$$

$$\Rightarrow -V_s + RC \times \frac{dV_C(t)}{dt} + V_C(t) = 0$$

The solution for above equation is  $V_C(t) = A + B e^{-t/\tau}$

$$\text{At } t(0^+), V_C(t) = 0$$

$$0 = A + B \Rightarrow B = -A$$

$$\text{At } t \rightarrow \infty, V_C(t) = V_s$$

$$\therefore V_s = A$$

Substituting the constant values  $A$  and  $B$


$$\boxed{V_C(t) = V_s(1 - e^{-t/\tau})}$$

where  $\tau = RC$  (time constant.)

UNIT-IAC CIRCUITS

Alternating Quantity :-

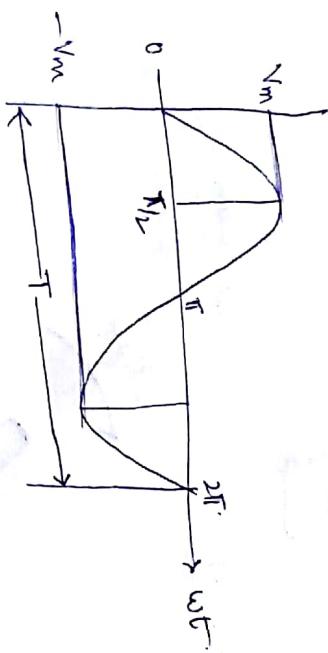An alternating quantity changes in magnitude and alternates in the direction at regular intervals of time. See any quantity.



The terms related to an alternating quantity are

- ① Amplitude :-  
 $\frac{V_m}{\Omega t}$  is defined as the maximum value attained by the alternating quantity.

It is also known as peak value or maximum value.

- ② Time period :-

The time taken for an alternating quantity to complete one cycle is known as its Time period.

### ③ Frequency :-


It is defined as the no. of cycles of an alternating quantity in one second, is known as its frequency. Hertz (Hz) or cycles/second. Units are

$$T = \frac{1}{f}$$

Representation of a Sinusoidal wave :-

$\omega \text{ rad/sec}$

$\rightarrow \omega t$

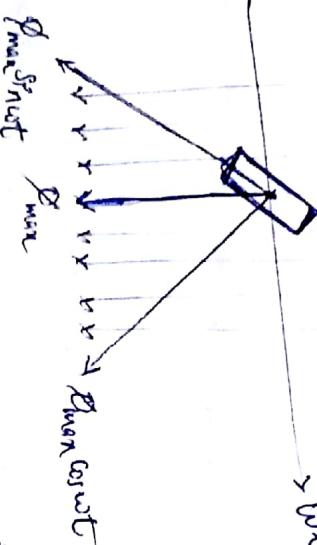

Consider a conductor with 'N' turns is rotating at  $\omega$  rad/sec in a stationary magnetic field.

$$e \text{ (or) } v = -N \frac{d\phi}{dt}$$

$$\text{or, } v = -N \frac{d}{dt} (\text{constant current})$$

$$\text{or, } v = +N \times \Phi_{max} \times \omega \sin \omega t$$

$$\Rightarrow \boxed{v = V_m \sin \omega t}, \quad V_m = N \Phi_{max}$$

The maximum flux  $\Phi_{max}$  can be divided into two components,  $\Phi_{max} \sin \omega t$  which acts in parallel to the conductor and  $\Phi_{max} \cos \omega t$  which is in  $L$  to the conductor and which is responsible to induce an emf in the conductor.

i.e.  $v' \text{ or } e' = -n$

i.e. the emf induced in a current carrying conductor placed in a stationary magnetic field is a sinusoidal wave. Hence the currents induced will also have a sinusoidal in shape, which is represented by  $\boxed{i = I_m \sin \omega t}$

Average Value :-

The arithmetic sum of all the values of an alternating quantity over a period of cycle is known as its Average value.

i.e., Average value =  $\frac{\text{Area of the wave over full cycle}}{\text{Base}}$

Since a symmetrical alternating quantity has an average value of zero, only half of the cycle is considered while measuring the average value of an alternating quantity.

i.e. Average value =  $\frac{\text{Area of the wave over half cycle}}{\text{Base}}$

$$\text{For a sinusoidal wave } V_{avg} = \frac{1}{\pi} \int_0^{\pi} V d(\omega t)$$

$$= \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t d(\omega t)$$

$$= \frac{V_m}{\sqrt{2\pi}} \int_0^{\pi} \left( \frac{1 - \cos \omega t}{2} \right) d(\omega t)$$

$$= \frac{V_m}{\pi} \int_0^{\pi} \sin \omega t d(\omega t)$$

$$= \frac{V_m}{\pi} \left[ -\cos \omega t \right]_0^{\pi}$$

$$= \frac{V_m}{\pi} \left[ -\cos \pi + \cos 0 \right]$$

$$\Rightarrow \frac{V_m}{\pi} [ +1 + 1 ]$$

$$V_{avg} = \frac{2V_m}{\pi}$$

$$V_{avg} = 0.636 V_m$$

$$11^{\text{th}} \quad T_{avg} = 0.636 T_m$$

RMS Value :-

C

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V^2 d(\omega t)}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \sin^2 \omega t d(\omega t)}$$

Form factor :-

It is defined as the ratio of RMS value to the average value of an alternating quantity.

$$\text{For a sinusoidal wave form factor} = \frac{0.707 V_m}{0.636 V_m}$$

$$= 1.11$$

Peak factor :-

It is defined as the ratio of the maximum value to the RMS value of an alternating quantity.

$$\text{For a sinusoidal wave peak factor} = \frac{V_m}{0.707 V_m}$$


$$= 1.414$$

## PHASE :-

The phase of an alternating quantity is the advancement of the wave from the starting point (or zero ref. reference point).
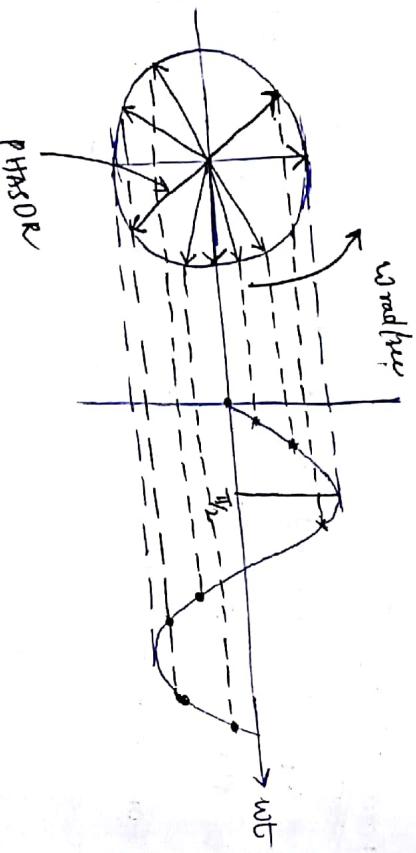
## PHASOR :-

A phasor is straight line with fixed length rotating in anti clockwise direction with a constant angular velocity.




## PHASOR

→ When two wave forms with same frequency have same starting points, then they are said to be in phase.

→ When the two wave forms with same frequency has different starting points, then they are said to be out of phase.

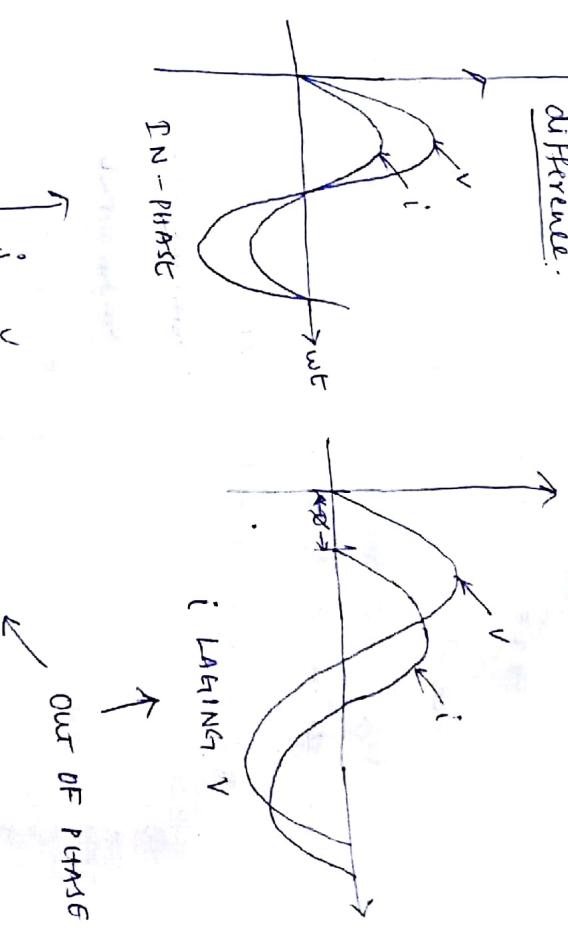
## PHASOR

The difference in the phase of the two wave forms starting at different points is known as Phase difference.



## ANALYSIS OF AC CIRCUITS :-

1. With Pure resistance ( $R$ ) :

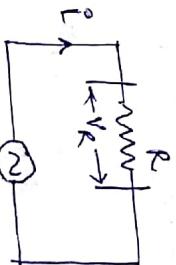

$$v = V_m \sin \omega t$$

Consider  $V = V_m \sin \omega t$  as reference.

The current flowing in the circuit  $i = \frac{V}{R} = \frac{V_m \sin \omega t}{R}$

$$\Rightarrow i = I_m \sin \omega t \quad (2) \quad I_m = \frac{V_m}{R}$$

From equations ① & ② in a pure resistive circuit the voltage and current are in phase. So the phase difference is zero.

The instantaneous power  $P = VI$

$$= V_m \sin \omega t \cdot I_m \sin \omega t$$

$$= V_m I_m \sin^2 \omega t$$

$$= V_m I_m \left( \frac{1 - \cos 2\omega t}{2} \right)$$

$$P = \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t$$

$\downarrow$   
Constant power  
 $\downarrow$   
fluctuating power

The average power over a full cycle  $P_{av}$

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} \left[ \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t \right] dt$$


$$= \frac{1}{2\pi} \left[ \frac{V_m I_m}{2} [2\pi] - \frac{V_m I_m}{2} \left( \frac{\sin 2\omega t}{2} \right)_0 \right]$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m}{4\pi} (\sin 4\pi - \sin 0)$$

$$= \frac{V_m I_m}{2}$$

$$P_{av} = V_{rms} \times I_{rms} = \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}$$

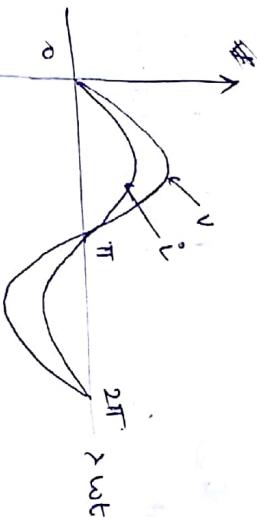i.e. In a pure resistive circuit the average power is equal to the product of the rms voltage and rms current.



phasor representation

wave representation

with Pure Inductance:-

$$V = V_m \sin \omega t \quad (1)$$

$$V = V_m \sin \omega t = V_L$$

$$= L \cdot \frac{di}{dt}$$

$$V = V_m \sin \omega t$$

$$\Rightarrow V_m \sin \omega t = L \frac{di}{dt}$$

$$di = \frac{V_m \sin \omega t}{L} dt$$

Integrating on both sides

$$i = \frac{V_m}{L} \left[ -\frac{\cos \omega t}{\omega} \right]$$

$$\Rightarrow i = \frac{V_m}{\omega L} \sin(\omega t - \pi/2) \quad \text{--- (2)}$$

$$i = I_m \sin(\omega t - \pi/2) \quad \text{--- (2)}$$

$$\text{where } I_m = \frac{V_m}{\omega L}$$


$$I_m = \frac{V_m}{\omega L} = \omega \frac{V_m}{X_L}$$

$$\text{The average power } P = \frac{1}{2\pi} \int_{-\frac{V_m I_m}{2}}^{\frac{V_m I_m}{2}} V_m \sin \omega t dt = 0$$

where  $X_L$  is known as inductive reactance.

From equations ① & ② in a pure inductance circuit, the current lags the voltage by an angle  $\pi/2$  or  $90^\circ$

$$i^\circ$$

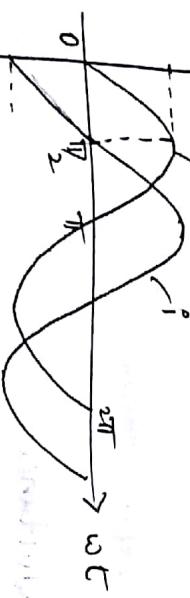

Phasor diagram :-

$$i = \frac{d\varphi}{dt} = \frac{d}{dt}(C V_m \sin \omega t)$$

$$\Rightarrow i = C V_m \cos \omega t \times \omega$$

$$\Rightarrow i = \omega C V_m \cos \omega t$$

$$\Rightarrow i = I_m \sin(\omega t + \pi/2)$$

The

$$\text{instantaneous power } 'P' = V_i i^\circ$$

$$= V_m \sin \omega t \times I_m \sin(\omega t - \pi/2)$$

$$= -\frac{V_m I_m}{2} \sin 2\omega t$$

i.e. In a pure inductive circuit the power consumed is zero.

3. With pure capacitance :-



$$V = V_m \sin \omega t$$

Consider  $V = V_m \sin \omega t \quad \text{--- (1)}$  as preference

$$\therefore Q = C V = C V_m \sin \omega t$$


$$i = \frac{dQ}{dt} = \frac{d}{dt}(C V_m \sin \omega t)$$

$$\text{where } I_m = \omega C V_m = \frac{V_m}{X_C}, X_C = \frac{1}{\omega C}$$

where  $X_C$  is known as capacitive reactance.

i-e The power consumed in a pure capacitive circuit is always zero.

R-L series circuit :-

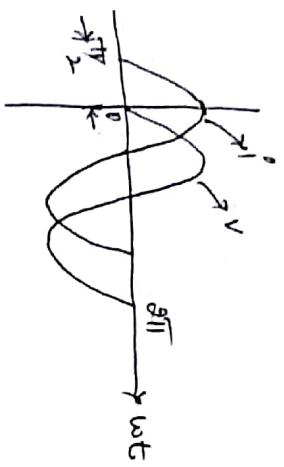


from equations ① & ②, in a pure capacitive circuit the current always leads the voltage by an angle  $\frac{\pi}{2}$ .

The instantaneous power  $p = VI^2$


$$= V_m \sin \omega t \times I_m \sin \omega t$$

$$= V_m I_m \sin \omega t \times \cos \omega t$$

$$= \frac{V_m I_m}{2} \sin 2\omega t.$$

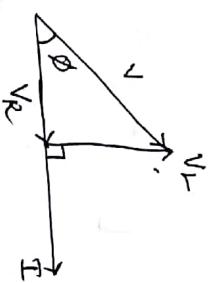

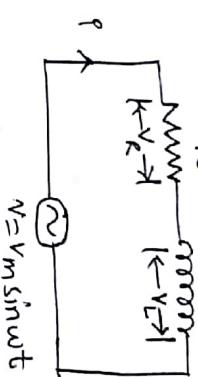Let  $V_R = IR$   $\rightarrow$  In phase with  $I$   
 $V_L = I X_L \rightarrow$  leads  $I$  by  $\frac{\pi}{2}$ .



From the phasor diagram the resultant voltage:  $V = \sqrt{V_R^2 + V_L^2} = \sqrt{(IR)^2 + (IX_L)^2}$

$$= I \sqrt{R^2 + X_L^2}$$

$$\boxed{V = IZ}$$

$$\tan \phi = \frac{V_L}{V_R} = \frac{I X_L}{IR}$$

$$= \frac{X_L}{R}$$

$$\tan \phi = \frac{\omega L}{R}$$

The average power  $P = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \sin 2\omega t dt$

$$= \frac{1}{2\pi} \times \frac{V_m I_m}{2} \left[ -\cos 2\omega t \right]_0^{2\pi}$$

$$= \frac{1}{2\pi} \frac{V_m I_m}{4} \left[ -\cos 2\pi + \cos 0 \right]$$

$\Rightarrow 0$

$$\Rightarrow \boxed{\phi = \tan^{-1} \left( \frac{wL}{R} \right)}$$

The instantaneous power  $P = V^2 = V_m^2 = V_m \sin \omega t \times I_m \sin(\omega t - \phi)$

$$= V_m I_m \sin \omega t \left[ \sin \omega t \cos \phi - \cos \omega t \sin \phi \right]$$

$$= V_m I_m \left[ \sin^2 \omega t \cos \phi - \frac{\sin 2\omega t \cdot \sin \phi}{2} \right]$$

$$= \frac{V_m I_m}{2} \left[ \cos \phi - \cos 2\omega t \cos \phi - \sin 2\omega t \sin \phi \right]$$

$$= \frac{V_m I_m}{2} \left[ \cos \phi - \cos 2\omega t \cos \phi - \sin 2\omega t \sin \phi \right]$$




$$\text{The average power } P = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \left[ \cos \phi - \cos 2\omega t \cos \phi \right] d\omega t$$

$$= \frac{1}{2\pi} \frac{V_m I_m}{2} \left[ \cos \phi - \int_0^{2\pi} [\cos 2\omega t \cos \phi] d\omega t \right]$$

$$= \frac{V_m I_m}{4\pi} \left[ \cos \phi \left[ \frac{1}{2} \int_0^{2\pi} \sin(2\omega t - \phi) d\omega t \right] \right]$$

$$= \frac{V_m I_m}{4\pi} \left[ \cos \phi - \left[ \frac{\sin(4\pi - \phi)}{2} + \frac{\sin(-\phi)}{2} \right] \right]$$
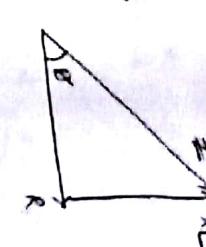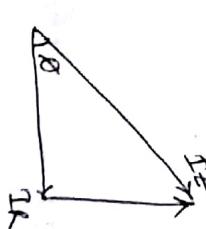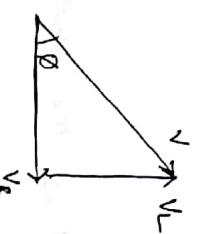
$$= \frac{V_m I_m}{4\pi} \left[ \cos \phi + \frac{\sin \phi}{2} + \frac{\sin \phi}{2} \right]$$



$$\boxed{P = VI \cos \phi}$$

Power factor :-

i.e. In an R-L series circuit the power consumed

$$\cos \phi = \frac{P}{VI}$$

$\phi$  is equal to  $I^2 R$ , since the power consumed in an inductor is zero.

Power factor :- (no units)

It is defined as the cosine of the phase angle between the voltage and current in an A-C circuit.

$$= \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}} \times \cos \phi$$

$$\cos \phi = \frac{R}{Z}$$

$$\tan \phi = \frac{X_L}{R} \Rightarrow \phi = \tan^{-1}\left(\frac{X_L}{R}\right)$$

i.e power factor ( $\cos \phi$ ) can also be defined by the ratio of resistance to the impedance of the A-C circuit.

A-C circuit :-

Power in an A-C circuit :-


The power in an A-C circuit consists of an active (or) real power and reactive power.

$\Rightarrow$  The power which do some useful work in the circuit is known as active power.

$\Rightarrow$  The power which doesn't do any useful work is known as Reactive power.

$\Rightarrow$  The total power available in an A-C circuit is known as Apparent power.

Known as Active components

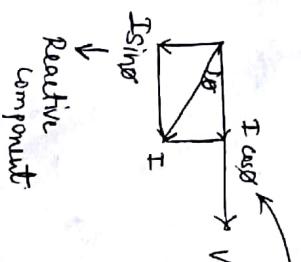

Ising  
Reactive  
component

Active power ( $P_A$ ). It is defined as the power

in an A-C circuit due to the active compo-

of the current. Units are watts.  
i.e  $P = V I \cos \phi$  watts

$$\Rightarrow V = I Z$$

$$P = I Z \times I \times \frac{R}{Z} = I^2 R \text{ watts}$$

Reactive power (Q) :-

It is defined as the power in an A-C circuit due to their reactive component of the current.

Units are VARs

$$\text{i.e } Q = V I \sin \phi \text{ VARs}$$

$$= I Z \times I \times \frac{X_L}{Z} = I^2 X_L \text{ VARs.}$$

Apparent power (S) :-

$P_A$  is defined as the total power available in an A-C circuit. Units are VA.


$$\text{i.e } S = \sqrt{P^2 + Q^2}$$

$$P^2 = (I^2 R)^2, Q^2 = (I^2 X_L)^2$$


$$S = \sqrt{(I^2 R)^2 + (I^2 X_L)^2}$$

$$= I^2 \sqrt{R^2 + X_L^2}$$

$$S = I^2 Z \quad \text{VA}$$

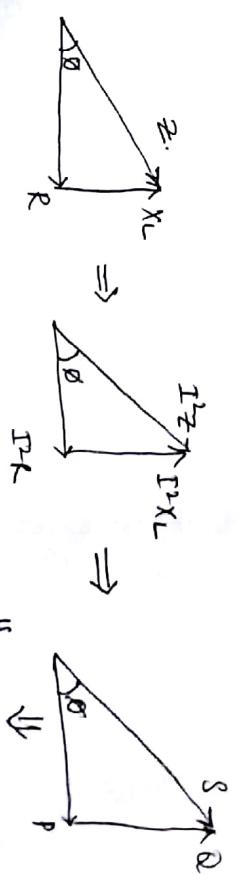


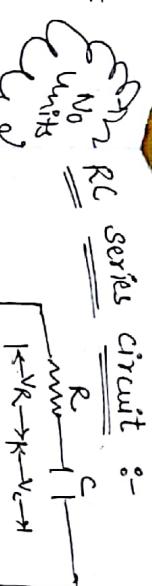from power triangle,  ~~$\cos\phi = P/S$~~   $\cos\phi = \frac{\text{real power / Active}}{\text{apparent power}}$



i.e. Power factor can also be defined as the ratio of active / real power to the apparent power in an A-C circuit.
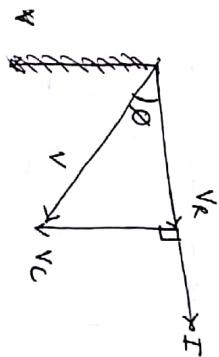
$$\begin{aligned} \text{No. units} &= \frac{\text{real power / Active}}{\text{apparent power}} \\ \text{In phase with } I & \quad V_R = IR \\ V_C &= Ix_C \quad \text{lags current by } \pi/2. \end{aligned}$$



from the phasor diagram the resultant is

$$\begin{aligned} V &= \sqrt{V_R^2 + V_C^2} \\ &= \sqrt{(IR)^2 + (Ix_C)^2} \\ &= I \sqrt{R^2 + x_C^2} \\ \boxed{V = IZ} \quad Z &= \sqrt{R^2 + x_C^2} \end{aligned}$$

$Z \rightarrow \text{impedance.}$

$$\tan\phi = \frac{V_C}{V_R} = \frac{I x_C}{I R} = \frac{x_C}{R} = \frac{1}{wCR}$$

$$\boxed{\phi = \tan^{-1}\left(\frac{1}{wCR}\right)}$$

The instantaneous power  $P = V I \cos\phi$

$$= V_m \sin\omega t I_m \sin(\omega t + \phi)$$

$$= V_m I_m \sin \omega t [ \sin \omega t \cos \phi + \cos \omega t \sin \phi ]$$

$$= V_m I_m [ \sin^2 \omega t \cos \phi + \sin \omega t \cos \omega t \sin \phi ]$$

$$= V_m I_m \left[ \frac{1 - \cos 2\omega t}{2} \cos \phi + \frac{\sin 2\omega t}{2} \sin \phi \right]$$

$$= \frac{V_m I_m}{2} [\cos \phi - \cos \phi \cos 2\omega t + \sin \phi \sin 2\omega t]$$

$$\boxed{P = \frac{V_m I_m}{2} [\cos \phi - \cos(\phi + 2\omega t)]}$$

$\rightarrow$  The average power  $P = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t + \phi)] dt$

$$= \frac{V_m I_m}{2} \times \frac{1}{2\pi} \int_0^{2\pi} \left[ \cos \phi - \frac{\sin 2\omega t + \phi}{2} \right] dt$$

$$= \frac{V_m I_m}{2} \times \frac{1}{2\pi} [\cos \phi 2\pi]$$

$$= \frac{V_m I_m}{2} \cos \phi$$

$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} \cdot \cos \phi$$

$$\boxed{P_{avg} = V_{rms} I_{rms} \cos \phi}$$

Pure resistor  $\phi = 0^\circ$

$$\boxed{P = V I}$$

max

Pure capacitor / Inductor  $\phi = 90^\circ$


$$\boxed{P = 0}$$

from phasor diagram

$$\cos \phi = \frac{V_R}{V}$$


$$= \frac{I R}{I Z} = \frac{R}{Z}$$
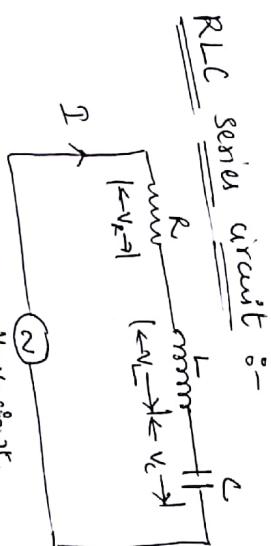
$$\boxed{P = \frac{I^2 Z \times I \times R}{I^2 \times Z}}$$




Let  $V_R = I R \rightarrow$  in phasor with  $I$   
 $V_L = I X_L \rightarrow$  Leads current by  $90^\circ$   
 $V_C = I X_C \rightarrow$  Lags  $I$  by  $90^\circ$

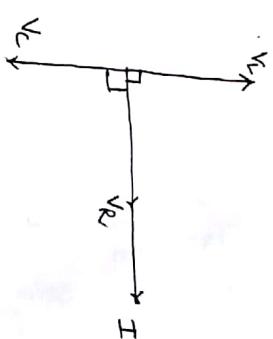Case (ii) :- Inductor dominant ( $X_L > X_C$ )



$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

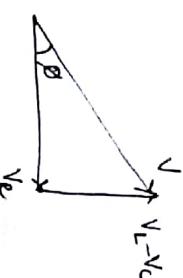

$$V = \sqrt{(IR)^2 + (Ix_L - Ix_C)^2}$$

$$V = I \sqrt{R^2 + (x_L - x_C)^2}$$

$$V = IZ, \quad Z = \sqrt{R^2 + (x_L - x_C)^2}$$

case(iii) if  $x_L = x_C$ , The total impedance of the circuit will be equal to the resistance  $R$  and the circuit acts like a pure resistive circuit, in which the voltage and current are in phase.

$$\tan \phi = \frac{V_L - V_C}{V_R} = \frac{x_L - x_C}{R}$$

$$\Rightarrow \boxed{\phi = \tan^{-1} \left( \frac{x_L - x_C}{R} \right)}$$

case(iii)  
~ 'C' DOMINANT ( $x_C > x_L$ )



$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$V = \sqrt{(IR)^2 + (Ix_C - Ix_L)^2}$$

$$V = I \sqrt{R^2 + (x_L - x_C)^2}$$

$$V = IZ, \quad Z = \sqrt{R^2 + (x_L - x_C)^2}$$

$$\tan \phi = \frac{V_C - V_L}{V_R} = \frac{x_C - x_L}{R}$$

$$\phi = \tan^{-1} \left( \frac{x_C - x_L}{R} \right)$$

- Q. A coil having a resistance of  $31.8$  mH is connected to an inductance of  $31.8$  mH is connected to  $230$  V  $50\text{Hz}$  ac supply. Calculate  
 (i) the circuit current.  
 (ii) Power factor  
 (iii) Power consumed.

$$R = 31.8 \quad x_L = \omega L = 31.8 \cdot \frac{9900 \cdot 2\pi \cdot 50}{1000} = 9.99026$$

$$I_p = \frac{230}{9.99026} = 23.026 \text{ A} = 23.026 \text{ A}$$

$$\phi = \tan^{-1} \left( \frac{x_L}{R} \right) = 54.98^\circ$$

$$\cos \phi = \frac{R}{Z} = 0.57386.$$

$$\text{Power} = P = 2489.89 \text{ Watts}$$

- Q A  $200$  V  $50\text{Hz}$  inductive circuit takes a current of  $10$  A lagging by  $30^\circ$ . Find  
 (i) Resistance

iii, resistance  
iii, inductance of the coil

$$\tan \phi' = \frac{X_L}{R} \Rightarrow \tan 30^\circ = \frac{X_L}{R} = \frac{1}{\sqrt{3}} \Rightarrow R = X_L$$

$$I = \frac{V}{\sqrt{R^2 + X_L^2}} \Rightarrow I\phi = \frac{200}{\sqrt{R^2 + X_L^2}}$$

$$R^2 + X_L^2 = 400$$

$$3X_L^2 + X_C^2 = 400$$

$$\frac{4X_L^2 = 400}{X_L = 10}$$

$$\text{Reactance} = 10$$

$$\lambda = \frac{L}{2\pi f} = 0.03141$$

$$R = 10\sqrt{3}$$

$$I = \frac{V}{Z} = \frac{100}{19.43} = 5.146 \text{ A} \approx 5.1$$

$$\text{Power factor} = \cos \phi = \frac{R}{\sqrt{R^2 + (X_L - X_C)^2}}$$

$$= \frac{12}{19.43}$$

$$A \neq Q =$$

Q. A series RLC circuit containing a resistance of  $100\ \Omega$  and a capacitor of  $100\ \mu F$  are connected to an AC source of  $100\sqrt{2}\ V$  at  $50\ Hz$ . The current in the circuit is

of  $12\ \Omega$ ,  $0.15\text{H}$  and a capacitor of  $0.01\mu\text{F}$  connected in series across a  $100\text{V}$   $50\text{Hz}$  supply.

calculate.

in the usual

power factor.

Also draw the voltage phasor diagram

$$R = 12 \Omega$$

$$X_C = \frac{1}{\omega C} = \frac{1}{600} = 31.83 \Omega$$


Q. An ac circuit composed of a series connect  
 of  $R = 50\Omega$ ,  $L = 0.34$  and  $C = 15\mu F$ . The  
 circuit is connected to an ac voltage source  
 of 25V and 60Hz. Find the current in the  
 circuit & phase difference b/w voltage and  
 current.

$$X_L = 94.24 \Omega \quad X_C = 212.31 \Omega$$

$$r = \frac{25}{\sqrt{50^2 + (212.31 - 94.24)^2}} = 0.1949 \text{ A.}$$


$$\tan \phi = \frac{x_c - y_L}{R} = \frac{212.31 - 94.24}{150}$$

R L parallel circuit :-

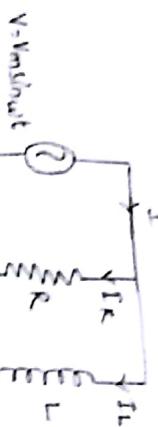

Let  $I_R = \frac{V}{R}$  in phase with V
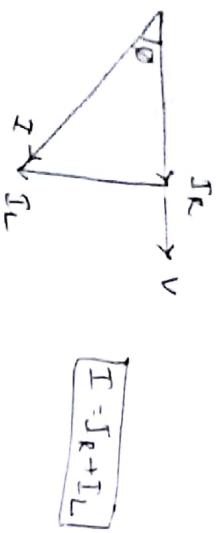
$$I_L = \frac{V}{X_L} \text{ lags V by } 90^\circ$$



$$I = \sqrt{I_R^2 + I_L^2}$$

From the phasor diagram

$$I = \sqrt{I_R^2 + I_L^2}$$

$$= \sqrt{\left(\frac{V}{R}\right)^2 + \left(\frac{V}{X_L}\right)^2}$$

$$\boxed{Z = \frac{V}{I} = \frac{1}{\left[\frac{1}{R^2} + \frac{1}{X_L^2}\right]^{1/2}}}$$

$$\vartheta = \tan^{-1}\left(\frac{I_L}{I_R}\right) = \tan^{-1}\left(\frac{R}{X_L}\right) = \tan^{-1}\left(\frac{R}{\omega L}\right)$$


$$\cos \vartheta = \frac{I_R}{I} = \frac{(VR)}{\frac{V}{R}} = \frac{V}{\frac{V}{R}} = R$$

$$\cos \vartheta = \frac{V}{R}$$

$$\vartheta = \tan^{-1}\left(\frac{I_L}{I_R}\right) = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}(R\omega C)$$


For instantaneous power P = VI = V sin theta

R C parallel circuit :-

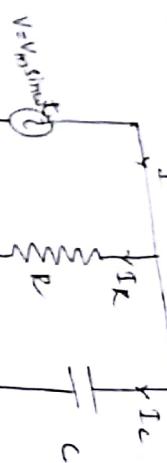

Let  $I_R = \frac{V}{R}$  in phase with V
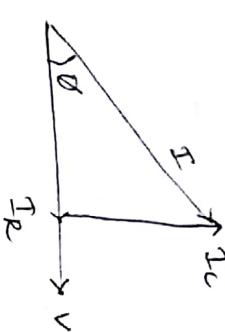
$$I_C = \frac{V}{X_C} \text{ leads V by } \pi/2$$



From the phasor diagram

$$I = \sqrt{I_R^2 + I_C^2}$$

$$= \sqrt{\left(\frac{V}{R}\right)^2 + \left(\frac{V}{X_C}\right)^2}$$

$$= \sqrt{\frac{1}{R^2} + \frac{1}{X_C^2}}$$

$$\boxed{\frac{V}{I} = Z = \left[\frac{1}{R^2} + \frac{1}{X_C^2}\right]^{1/2}}$$


$$\cos \vartheta = \frac{V}{R}$$

$$\cos \vartheta = \frac{V}{R}$$

$$\alpha = \cos^{-1} \left( \frac{I_R}{I} \right) \quad \phi = \tan^{-1} \left( \frac{X_L - X_C}{R} \right)$$

$$\boxed{\cos \phi = \frac{R}{Z}}$$



RLC Parallel circuit :-

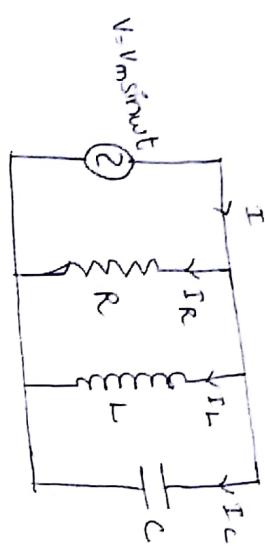

Let  $I_R = \frac{V}{R}$  lags  $V$  by  $\pi/2$

$$I_L = \frac{V}{X_L} \text{ leads } V \text{ by } \pi/2$$

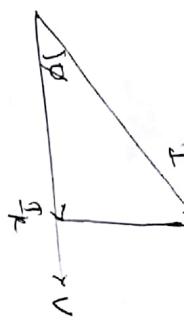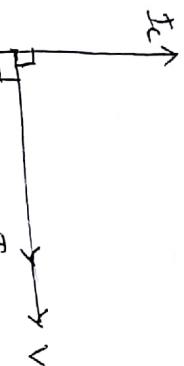Case (i) Capacitor dominant ( $X_C < X_L$ )



$$I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

(Case ii) Inductor dominant ( $X_L \gg X_C$ )

$\approx$

$$I = \sqrt{I_R^2 + (I_L - I_C)^2}$$

$$\frac{V}{I} = Z = \frac{1}{R^2 + \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2}$$

$$\phi = \tan^{-1} \left( \frac{T_L - T_C}{R} \right) = \tan^{-1} \left( \frac{\frac{1}{X_L} - \frac{1}{X_C}}{R} \right)$$

$$I = \sqrt{\left(\frac{V}{R}\right)^2 + \left(\frac{V}{X_L} - \frac{V}{X_C}\right)^2}$$

$$\frac{V}{I} = Z = \frac{1}{\left[\frac{1}{R^2} + \left(\frac{1}{X_C} - \frac{1}{X_L}\right)^2\right]}$$

$$\phi = \tan^{-1} \left( \frac{\frac{1}{X_L} - \frac{1}{X_C}}{R} \right) = \tan^{-1} \left[ R \left( \frac{1}{X_C} - \frac{1}{X_L} \right) \right]$$

Caseiii) :- If  $X_L = X_C$  (The total impedance of the circuit will be equal to the resistance  $R$  and the circuit acts like a pure resistance circuit, in which the voltage and current are in phase.




### Pr. Three Phase Balanced System :-

The three phase balanced system (Voltage/current) is a combination of 3 single phase systems (Voltage (or current) of which the three voltages (or currents) differ in phase by  $120^\circ$  electrical degrees from each other in a particular sequence.

### Advantages :-

- (i) The three phase power supplied to a three phase balanced circuit is constant at every instant of time and hence three phase motors have uniform torque.
- (ii) To transmit a given amount of power over a given length a three phase transmission circuit requires less conductor material than a single phase circuit.
- (iii) In a given frame size a three phase motor (or) generator produces more output than its single phase counter part.

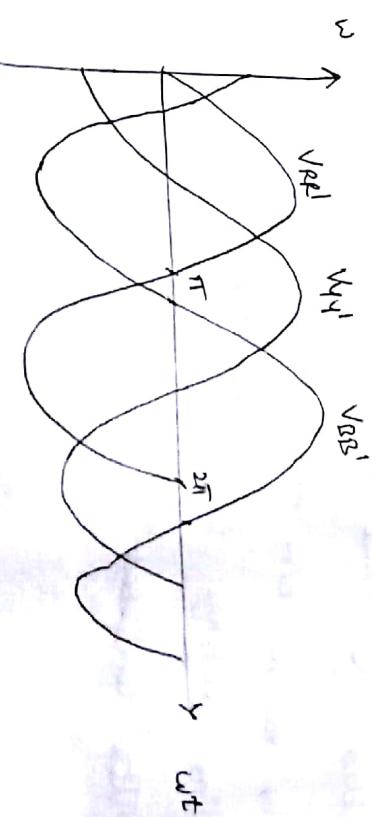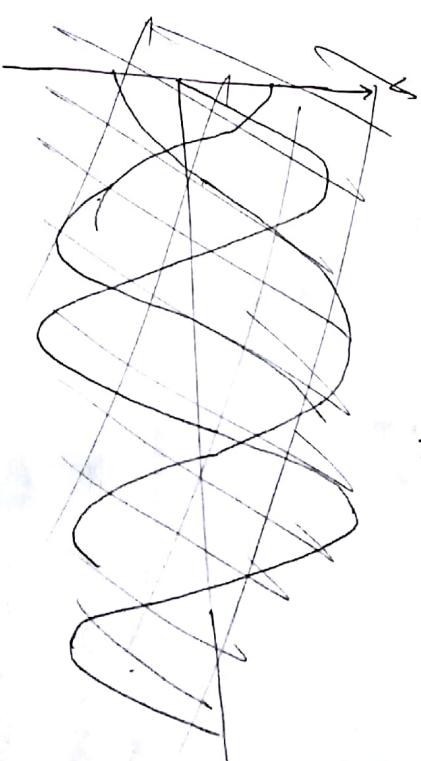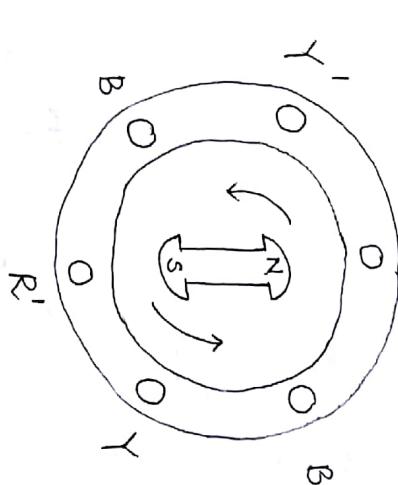(iv) Three phase machines control equipment are smaller, cheaper, lighter in weight and more efficient.




A three phase balanced system can be represented by


1. Star connected system

2. Delta connected system.

### Star connected System:

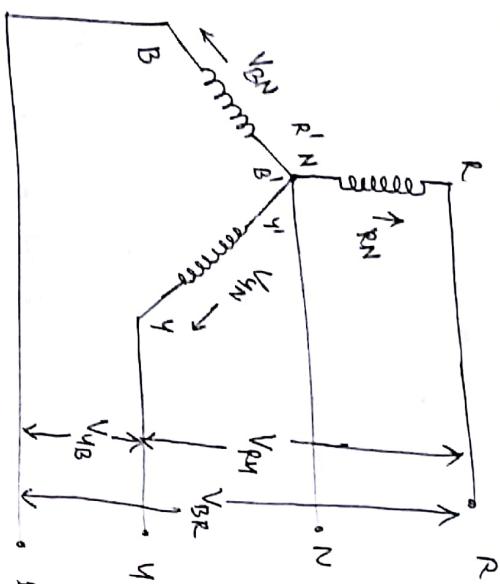

### Delta connected System:-

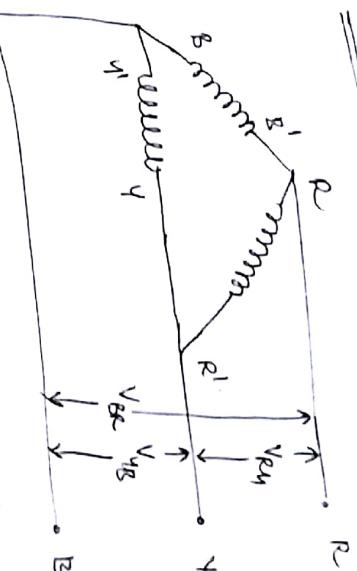

→ In this system the dissimilar ends of the windings are joined together i.e. R' to Y, Y to B and B' to R.

→ Since there is no common terminal, only three line voltages  $V_{RY}$ ,  $V_{YB}$ ,  $V_{BR}$  are available and these are also referred as phase voltages in delta connected system.



- In this system similar ends of the three phases are joined together. The
- The voltage b/w any line and the neutral point is called the phase voltage ( $V_{RN}$ ,  $V_{YN}$ ,  $V_{BN}$ )
- The voltage b/w any two lines is called the line voltage ( $V_{RY}$ ,  $V_{YB}$ ,  $V_{BR}$ ).

Delta connected

~~Energy~~

Voltage and Current Relations in Three phase balanced Systems:

① Star connected System :-

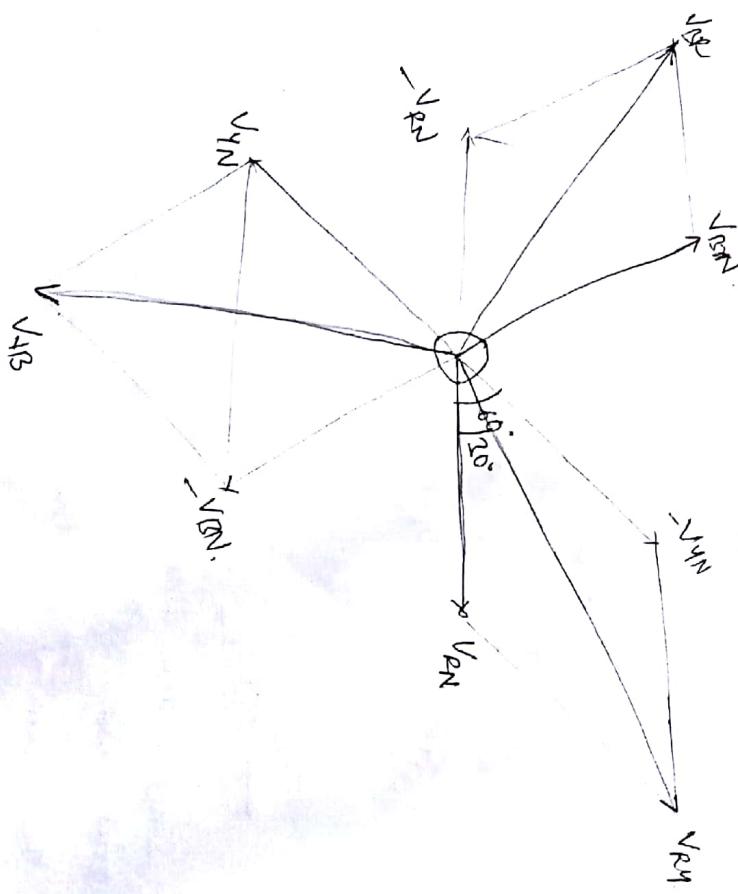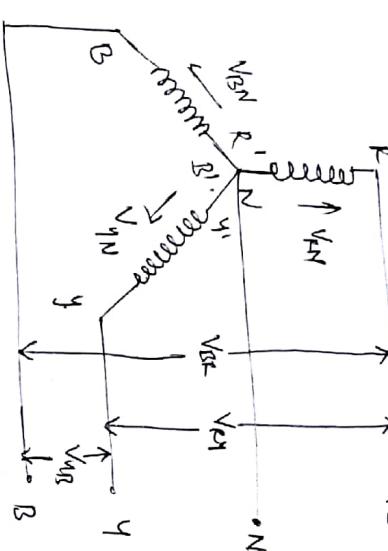

$$|V_{RN}| = |V_{YN}| = V_{ph}$$

$$\sqrt{P_h} = 2 V_{ph} \times \cos 30^\circ$$

$$\Rightarrow \boxed{\sqrt{P_h} = \sqrt{3} V_{ph}}$$


Similarly  $V_{YB} = \sqrt{3} V_{ph}$  and

$$V_{BR} = \sqrt{3} V_{ph}$$



i.e. in a balanced star connected

System  
i) line voltage =  $\sqrt{3}$  phase voltage

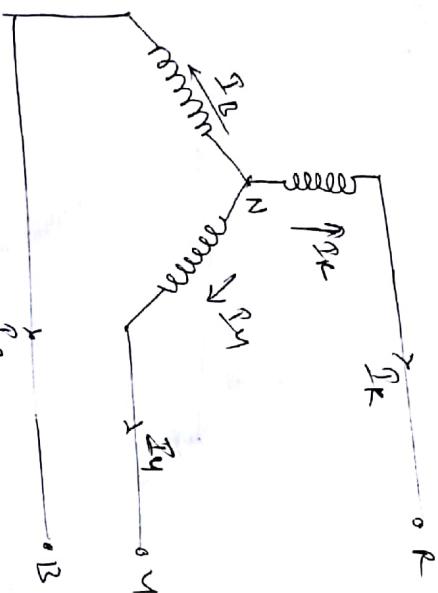ii) All line voltages are equal in magnitude and displaced by  $120^\circ$



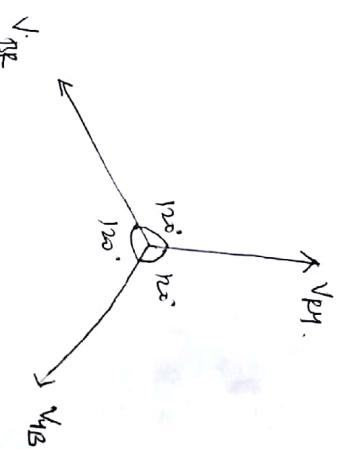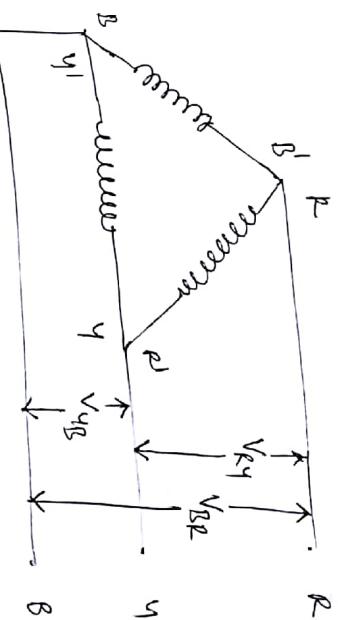Since the system is balanced all the phase voltages are equal in magnitude, displaced by  $120^\circ$  and are equal to the line voltages



$$\boxed{V_L = V_{ph} = V_{YB} = V_{BY} = V_{BR}}.$$

Since each line conductor is connected in series with its individual phase winding, the current in the line conductor is same as that in the phase to which it is connected.

i.e.  $I_L = I_{ph} = I_E = I_Y = I_B$

Q) Delta connected System :-



## UNIT-III

### TRANSFORMER

16/10/18

A transformer is a static device which converts the power from one level to another level without any change in the frequency.

Construction :-

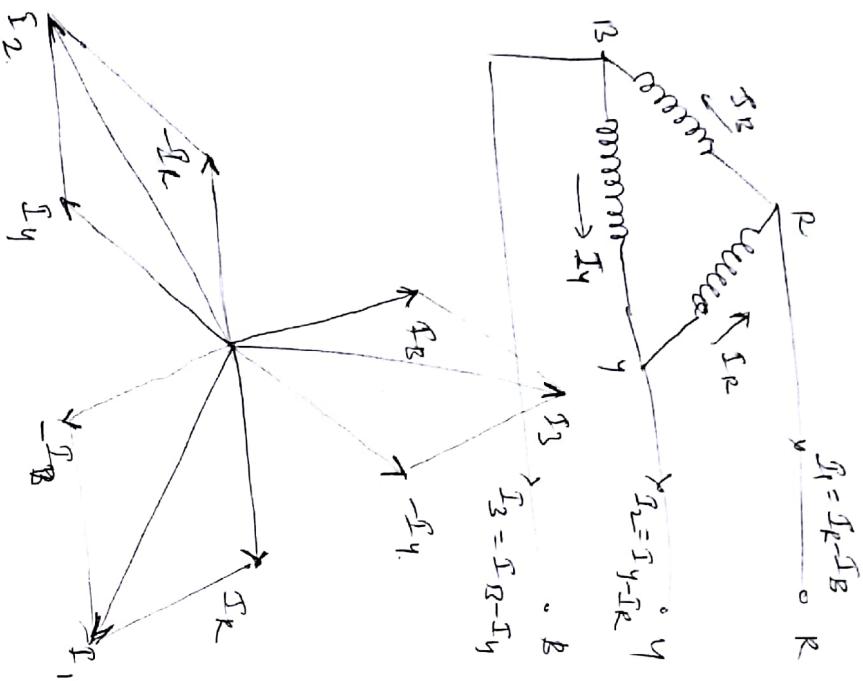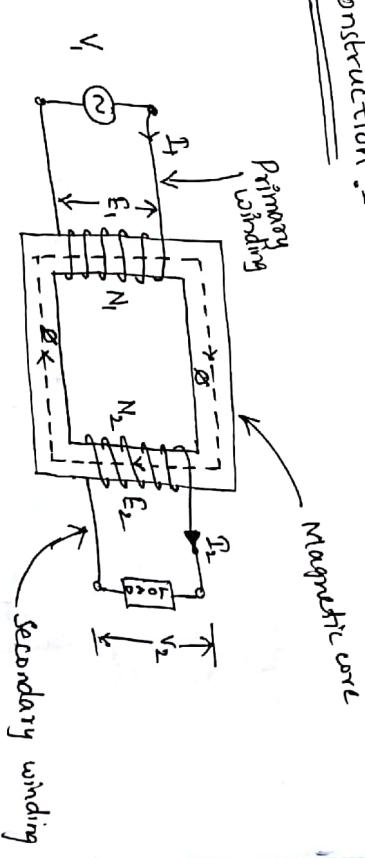

$$I_L = \sqrt{I_{ph}^2 + I_{ph}^2} = \sqrt{2} I_{ph}$$

$$I_1 = 2 I_{ph} \times \cos 30^\circ$$

$$\boxed{I_1 = \sqrt{3} I_{ph}}$$

$$I_2 = \sqrt{3} I_{ph}$$


- In a balanced three phase delta connected system,  $I_L = \sqrt{3} I_{ph}$ .
- The load current  $I_L$  develops a magnetic flux  $\phi$  in the primary winding which in turn induces an emf  $E_1$  in the primary.
- The change in current  $I_1$  develops a magnetic flux  $\phi$  in the primary winding inducing an emf  $E_2$ .  $I_2$  &  $V_2$  are the load current and voltage.

In a balanced three phase delta connected system,  $I_L = \sqrt{3} I_{ph}$ .

### Working principle :-

A transformer works on the principle of mutual induction, which states that the change in current in a coil or winding induces an emf in its neighbouring coil, when the two coils are inductively coupled with each other.

EMF equation :-

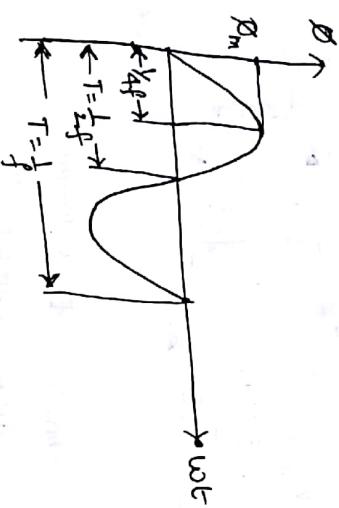

Average EMF per turn =  $\frac{d\Phi}{dt}$

$$= \frac{\Phi_m - 0}{T} = \frac{d\Phi}{dt} \quad [:: N=1]$$

Since there is alternating flux, the emf induced will also be alternating in nature.

Therefore, for a sinusoidal wave form factor

$$PF = \frac{V_{RMS}}{V_{AVG}} = 1.11$$

$$\Rightarrow V_{RMS} = 1.11 \times V_{AVG}$$

Therefore the RMS value of the emf induced =  $1.11 \times 4.44f\Phi_m$  =  $4.44f\Phi_m$  volts

i.e. EMF induced in the primary winding

$$E_1 = N_1 \cdot 4.44f\Phi_m$$

Similarly

$$E_2 = N_2 \times 4.44f\Phi_m$$

$$\frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$

VOLTAGE  
TRANSFORMATION  
RATIO

$$\therefore E_2 = K \cdot E_1 \quad \& \quad \frac{N_2}{N_1} = K$$

(i) If  $N_2 > N_1$ ,  $K > 1$ ,  $E_2 > E_1 \rightarrow$  'STEP-UP' TR

(ii) If  $N_2 < N_1$ ;  $K < 1$ ;  $E_2 < E_1 \rightarrow$  'STEP-DOWN' TR

(iii) If  $N_2 = N_1$ ;  $K = 1$ ;  $E_2 = E_1 \rightarrow$  'Isolation' TR

Ideal Transformer is said to be ideal if it satisfies the following conditions.

(i) No losses

(ii) Winding resistance is zero.


(iii) Leakage flux is zero.

(iv) Permeability of the magnetic core is high

$$E_1 = V_1 \quad \& \quad E_2 = V_2$$

$$V_1 I_1 = V_2 I_2$$

Ideal transformer - no load.

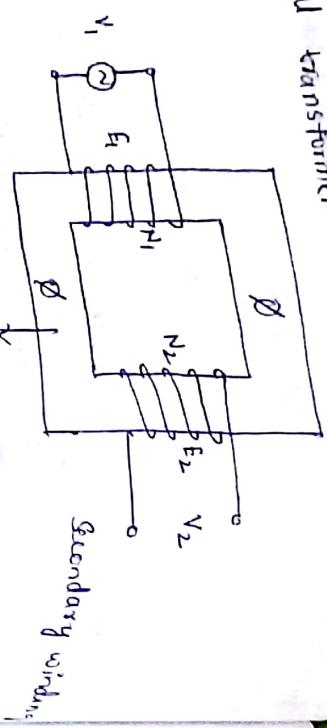


Primary winding

magnetic core

Secondary winding

Phasor diagram:

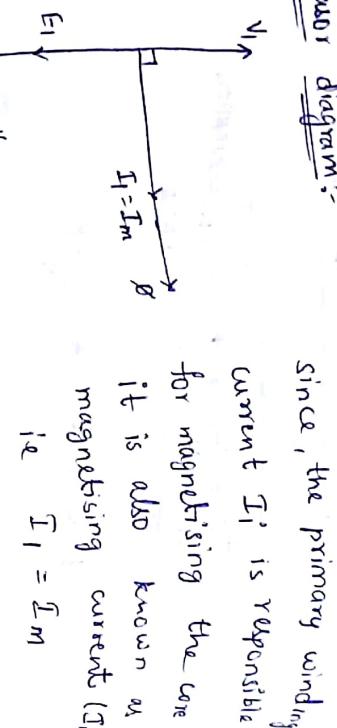

since, the primary winding current  $I_1$  is responsible for magnetising the core it is also known as magnetising current ( $I_m$ )

$$\text{i.e. } \vec{I}_1 = \vec{I}_m$$

Since the transformer is ideal, the winding is purely inductive in nature and hence the primary current  $I_1$  lags  $V_1$  by  $90^\circ$ .

According to lenz law the emf induced  $E_1$  in the primary winding acts exactly opposite to the cause of producing it.

i.e.  $E_1$  i.e. in anti phase with  $V_1$  but equal in magnitude.

The secondary induced emf  $E_2$  is also in anti phase with  $V_1$  but the magnitude depends on  $N_2$  since there are no losses  $E_2 = V_2$

$E_1$  and  $E_2$  are in phase.

\* Practical transformer - no load (same as previous diagram)

Phase diagram:



In a practical transformer with no load, the primary winding current ( $I_1$ ) is termed as no load current ( $I_o$ ).  $I_o$  is responsible to produce the losses in the transformer.

and to magnetise the core

∴ The no load current is split into the components:  $I_m$  - magnetising component  $I_w$  - iron loss component

$$\text{i.e. } \vec{I}_o = \vec{I}_m + \vec{I}_w$$




Since the winding has some resistance the no load current  $I_o$  lags  $V_1$  by an angle  $\phi$  ( $\phi < 90^\circ$ ) Since there are losses the primary induced emf  $E_1$  will never be equal to  $V_1$  and if by  $E_2 \neq V_2$

is known as no load power factor from the phasor diagram,

$$\boxed{\text{Power Factor} = \frac{V_1 I_o \sin \phi}{V_1 I_o \cos \phi}}$$

$$\text{Power Factor} = \frac{E_1 I_o \sin \phi}{E_1 I_o \cos \phi}$$

## Equivalent circuit of a Transformer

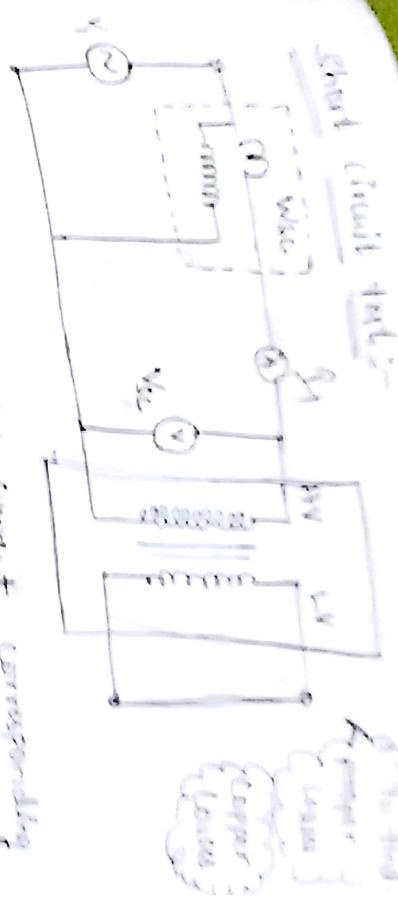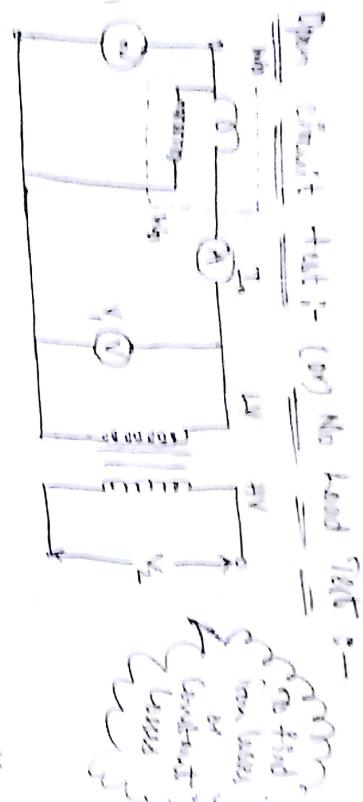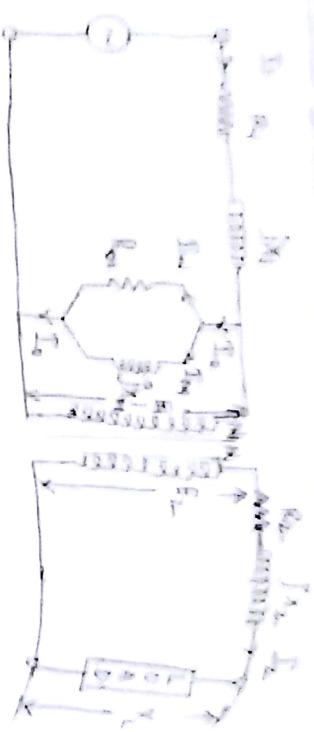

$$Z_{eq} = \text{Leaking Reactance}$$

$$\text{Voltage drop} = V_1 - V_{eq} = \sqrt{I_1^2 R_1 + I_1^2 Z_{eq}}$$

$$V_{eq} = \sqrt{Z_{eq}^2 + R_1^2}$$

Impedance referred to primary side

$$Z_{eq} = \frac{V_{eq}}{I_1}$$

$$\text{Primary side voltage} = \text{Primary rated voltage} (V_1)$$

- For this test, the rated current corresponding to the rated voltage is applied on the primary side ( $I_1$ )
- the primary side ( $V_1$ ) is scaled as the input voltage.

- Primary resistance ( $R_1$ ) = primary rated current ( $I_1$ )  $\times$  primary resistance ( $R_p$ )
- Wattmeter reading = primary rated current ( $I_1$ )  $\times$  primary rated voltage ( $V_1$ )

$$\text{Efficiency} = \eta = \frac{\text{Output Power}}{\text{Input Power}} = \frac{P_o}{P_i}$$

$$P_i = \text{Power Input}$$

$$P_o = \text{Power Output}$$

$$P_i = \frac{V_1 I_1}{\sqrt{2}}$$

Efficiency of a Transformer :-

The output of a transformer = Output + losses

The input of the transformer = Output + losses

$$\frac{S}{P} = V_2 T_2 \cos \theta_2 + P_i + P_c$$

$$\frac{dN}{dT_2} = 0 \Rightarrow (V_2 T_2 \cos \theta_2 + P_i + P_c) \frac{d(V_2 T_2 \cos \theta_2)}{dT_2}$$

$$= V_2 T_2 \cos \theta_2 - V_2 T_2 \cos \theta_2 \frac{\frac{d(V_2 T_2 \cos \theta_2)}{dT_2}}{V_2 T_2 \cos \theta_2 + P_i + P_c}$$

$$(V_2 T_2 \cos \theta_2 + P_i + P_c) (V_2 \cos \theta_2) = V_2 T_2 \cos \theta_2 \times V_2 \cos \theta_2$$

$$+ 2 T_2 R_2$$

$$\times V_2 \cos \theta_2$$

$$V_2^2 \cos^2 \theta_2 T_2 + P_i V_2 \cos \theta_2 + T_2^2 R_2 V_2 \cos \theta_2 \\ = V_2^2 \cos^2 \theta_2 T_2 + 2 T_2 R_2 V_2 \cos \theta_2$$

$$P_i V_2 \cos \theta_2 + T_2^2 R_2 V_2 \cos \theta_2 = 2 T_2 R_2 V_2 \cos \theta_2$$

$$P_i + P_c = 2 T_2 R_2.$$

$$\boxed{P_i = P_c}$$

$$P_c = n T_2 \quad \text{and}$$

$$T_2 = n T_1$$

$$P_c = (n T_2)^2 R_2$$

$$\therefore \% \text{ efficiency} = \frac{V_A \text{ Rating} \times \cos \theta_2}{V_A \text{ Rating} \times \cos \theta_2 + P_i + P_c} \times 100$$

$$\text{let } n = \frac{\text{Actual Load}}{\text{Full Load}}$$

Condition for minimum efficiency :-

$$\text{for max } N. \quad n = \frac{V_2 T_2 \cos \theta_2}{V_2 T_2 \cos \theta_2 + P_i + P_c}$$

$\Rightarrow$  To obtain the minimum efficiency of transformer, the iron losses should be equal to copper losses.

Q. A 150 kVA transformer has iron losses of 3000 watts and full load copper losses of 800 w. Find the efficiency of the transformer at

75% full load

i) for unity power factor lagging  
 ii) 0.8 power factor lagging

$$\eta = \frac{3}{4}$$

$$= \frac{8}{9} \times 100 \\ = 88.88\%$$

$$\eta_1' = \eta_c$$

$$\eta_0 = 100\%$$

$$(i) \eta = \frac{\frac{3}{4} \times 150000 \times 1}{\frac{3}{4} \times 160000 \times 1 + 3000 + 800 \times (\frac{3}{4})^2} \times 100$$

$$\therefore \text{max } \eta = 88.88\%.$$

$$= \frac{\frac{1125000}{1000} \times 100}{\frac{3}{4} \times 150000 \times 0.8} \times 100 \\ = 97.024\%$$

Q A 4 kVA, 200/400 volts, 50Hz single phase transformer has the following test results.

OC Test - 200V, 0.8A, 50W  
 SC Test - 17.5V, 9A, 50W  
 calculate the full load efficiency at 0.8 power factor lagging and unity power factor.

$$\eta = \frac{1 \times 4000 \times 0.8}{4000 \times 0.8 + 50 + 50} \times 100$$

$$= 96.96\%$$

- Q. A 2kV transformer has iron losses 50W and full load copper losses 200W, what will be efficiency at half of the full load and also determine its maximum efficiency and also determine its minimum efficiency.

$$\text{Loss}_3 = 0.8$$

$$\eta = \frac{3}{4}$$


$$\eta = \frac{1 \times 4000}{4000 + 50} \times 100 \\ = 97.50\%$$

$$\eta = \frac{\frac{1}{2} \times 2000 \times 0.8}{\frac{1}{2} \times 2000 \times 0.8 + 50 + 200 \times (\frac{1}{2})^2} \times 100$$
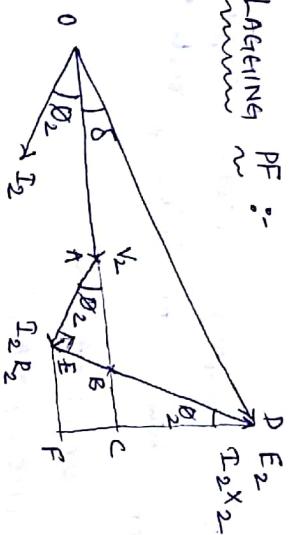
## Voltage regulation of a Transformer

Voltage regulation is defined as the percentage of difference in no load and full load voltage of a transformer with respect to its full load voltage.

$$\text{i.e., } \% \text{ Regulation} = \frac{E_2 - V_2}{V_2} \times 100$$



Let  $\theta_2$  is phase angle b/w the secondary voltage ( $V_2$ ) and secondary current ( $I_2$ ). Since the angle ( $\delta$ ) b/w  $OB$  and  $OC$  is negligibly small  $OD \approx OC$ .

$$\therefore E_2 = OC = OA + AB + BC$$

$$\Rightarrow E_2 = V_2 + I_2 R_2 \cos \theta_2 + I_2 X_2 \sin \theta_2$$

$$\therefore \% R = \frac{E_2 - V_2}{V_2} \times 100$$

$$= \frac{V_2 + I_2 R_2 \cos \theta_2 + I_2 X_2 \sin \theta_2 - V_2}{V_2} \times 100$$

$$\text{Voltage regulation corresponding to the primary side is expressed as } \% R = \frac{(I_2 R_{01} + I_2 X_{01}) \cos \theta_2 + I_2 X_{01} \sin \theta_2}{V_1} \times 100$$

Q. A 15kVA, 450/120 V 50Hz transformer gave the following test results.  

DC	120V	4.2A	30W
SC	9.65V	22.2A	120W

(use only this result for voltage regulation)

Find the voltage regulation at 0.8 PF lagging

$$R_{01} = \frac{P_c}{I_1^2} = \frac{120}{(22)^2} = 0.243 \Omega$$

$$Z_{01} = \frac{V_{sc}}{I_1} = \frac{9.65}{22.2} = 0.4346 \Omega$$

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = 0.359 \Omega$$

$$\boxed{\% R = \frac{I_2 R_2 \cos \theta_2 + I_2 X_2 \sin \theta_2}{V_2} \times 100}$$

$$\frac{15 \times 1000}{450} = 33.33$$

$$\frac{1}{\rho} R = \frac{T_1 R_{D1} \cos \phi + T_1 x_{D1} \sin \phi}{\sqrt{1 + x_{D1}^2}} + w_0$$

$$= \underline{37.3 \times 0.24 \times 0.8 + 33.3 \times 0.36 \times 0.6} \quad \wedge \quad \underline{\text{450}} \quad \wedge \quad \underline{100}$$

$$= 3.019\%.$$

Q. The primary and secondary winding resistances of a 40KVA, 6000/250 V single phase transformer are  $10\Omega$  and  $0.02\Omega$  respectively. The equivalent leakage reactance as referred to primary winding is  $35\Omega$ . Find the full load voltage regulation.

for  $P_F = 0.8$  lagging and leading

$$X_{01} = 35\Omega$$

$$R_{01} = 1.0 + \frac{0.0012}{(0.037)^2}$$

$$I_1 = \frac{40x^{1000}}{6600} = 6.06 A$$

$$\text{for lagging} \\ \% R = \frac{6.06 \times 24.6 \times 0.8 + 6.06 \times 35 \times 0.6}{6600} \times 100$$

for leading  $\chi R = -0.1212 \cdot \%$


Q. The following test data were taken on  $\mu$ -A transformer

4400/440 V 300W

OC Test : 440  
SC Test : 18V  
Find the efficiency and voltage regulation at 200A, 2000W

Unity power factor

## Auto Transformers :-

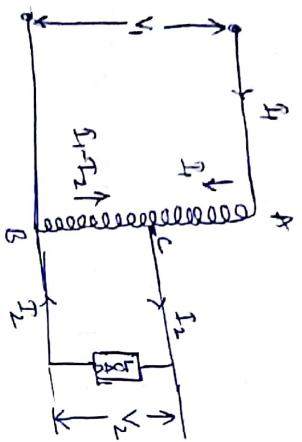

An auto transformer shares the common single winding as both primary and secondary.

AB → primary winding

BC → secondary winding

Let  $N_1$  &  $N_2$  are No. of turns of primary and secondary winding.

If  $V_1$  is voltage applied across primary,

The voltage per turn =  $\frac{V_1}{N_1}$


∴ The voltage across secondary

$$V_2 = \frac{V_1}{N_1} \times N_2 = N_2$$

$$\Rightarrow \boxed{\frac{V_2}{V_1} = \frac{N_2}{N_1} = k}$$

## ★ UNIT-4 ★

### D.C - GENERATORS

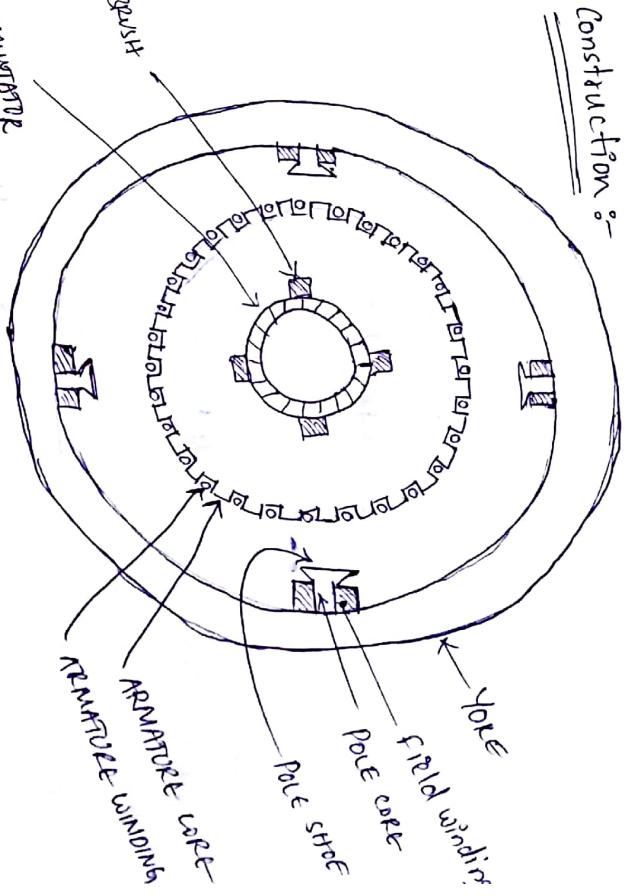

→ The main parts of a dc generator are :

- (i) YOKE
- (ii) POLES
- (iii) FIELD WINDING
- (iv) ARMATURE
- (v) COMMUTATOR
- (vi) BRUSHES

### Yoke:-

It serves the purpose of outermost cover of the dc generator so that the machine gets protected from moisture, dust and gases.

→ It also provides mechanical support to the poles.

→ It is made by cast iron which provides a low reluctance path for a magnetic flux.

### Pole:-

Each pole is divided into two parts

#### i) Pole core

#### ii) Pole shoe

→ Pole core carries the field winding which is used to produce the flux.

→ Pole shoe enlarges the area of armature core to come across the flux which produces the induced emf.

### Field Winding:-

The field winding is placed on the pole core which behaves as an electromagnet producing the necessary flux.

### Armature:-

Armature consists of

#### i) Armature core

#### ii) Armature winding

→ Armature core is cylindrical in shape consisting of slots on its periphery and air ~~ducts~~ ducts which permits air-flow through armature for cooling purpose. It is made up of cast iron or cast steel.


→ The armature winding is an inter connection

of armature conductors placed in the slots provided on the armature core periphery. It is made up of copper and the generation of emf takes place in it.

→ The armature winding is of two types

#### i) Lap winding

$Z_P$

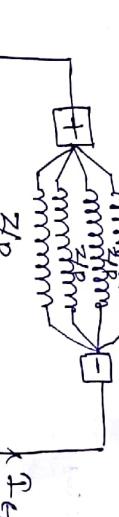


$R_L$

→ It is made up of a conducting material such as aluminum or copper.

In this type the armature coils / conductors are connected in series through commutator segments in such a way that the armature winding is divided into as many parallel paths as the no. of poles of the machine.

→ If there are  $\frac{z}{2}$  conductors and 'p' pole, then there will be  $\frac{z}{2p}$  no. of parallel paths each containing  $\frac{z}{2p}$  conductors in series.

Wave winding :-

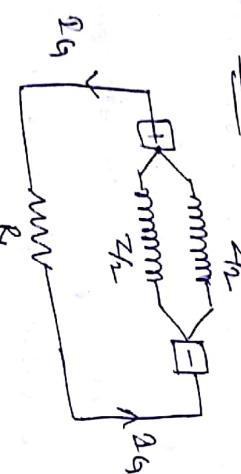

In this type the armature conductors are connected in series through commutator segments in such a way that the armature winding is divided into two parallel paths irrespective of the no. of poles of the machine.

→ If there are  $\frac{z}{2}$  conductors then their will be  $\frac{z}{2}$  conductors in series in each parallel path.

COMMUTATOR :- The emf induced in the armature winding is alternating, which needs rectification


into direct emf, which is done by the commutator brushes :-

These are used to collect the emf from the commutator segments and is made available to the stationary external loads. There are made of copper.

WORKING PRINCIPLE :-

The working principle of a dc generator is based on the dynamically induced emf or

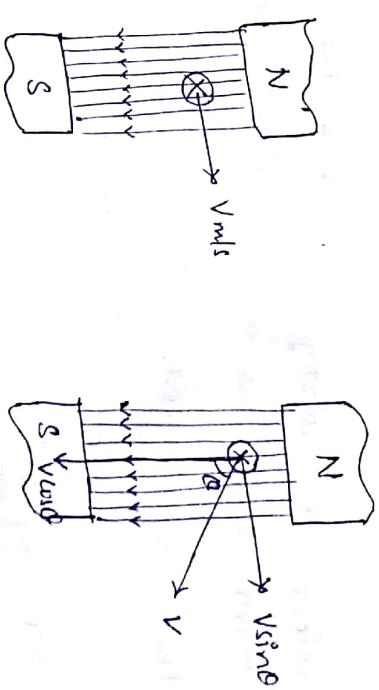Faraday's law of electromagnetic induction, which states that "when the flux linking the conductor or coil changes an emf is induced in it".



Consider a conductor of length 'l' mts moving in a uniform magnetic field within a velocity of  $v$  m/s.

Let the conductor move through a distance  $dx$  in  $dt$  sec, the area swept by the conductor is equal to  $l dx$ .

Therefore the magnetic flux cut by the conductor =  $B \cdot l dx$

where  $B$  = magnetic flux density.

Therefore, according to Faraday's law

$$e = N \frac{d\phi}{dt}$$

$$e = N \frac{B l dx}{dt}$$

$$\Rightarrow e = N \frac{B l dx}{dt}$$

$$\Rightarrow e = B l v \text{ volts}$$

Since the velocity with which the conductor moves across the magnetic field is  $v \sin \theta$ ,

the emf induced in the conductor =  $B l v \sin \theta$

$$[e = B l v \sin \theta] \text{ volts}$$

EMF equation:-

Let  $\phi$  = magnetic flux per pole in webres.  
 $Z$  = total no. of armature conductors.

$$\begin{aligned} P &= \text{No. of poles of the generator} \\ A &= \text{No. of parallel paths.} \\ N &= \text{Speed of armature in RPM.} \end{aligned}$$

The magnetic flux cut by one conductor in one revolution of the armature

$$d\phi = P \times \phi \text{ Wb}$$

$$\text{Time taken for one revolution} = \frac{60}{N} \text{ sec.}$$

Therefore the emf induced in one conductor in one revolution  $e = N \frac{\phi}{\frac{60}{N}}$

$$e = \frac{P \times \phi}{60/N}$$

$$\Rightarrow e = \boxed{\frac{P \times \phi \times N}{60}} \text{ Volts}$$

∴ The total emf of the generator = emf per conductor  $\times$  no. of conductors in series per parallel path.

$$\text{i.e. } E_g = \frac{P \times \phi \times N}{60} \times \frac{Z}{A}$$

$$\boxed{E_g = \frac{P \times \phi \times N}{60A} Z \text{ Volts}}$$

For LAP WINDING,

$$A = P$$

$$\therefore \boxed{E_g = \frac{P \times \phi \times N}{60} Z \text{ Volts}}$$

FOR WAVE WINDING  $A=2$

$$E_g = \frac{\phi Z N P}{120} \text{ volts}$$

(i)

- Q. Calculate the emf generated by a four pole DC generator having 65 slots wound wave with 12 conductors per slot when driven at 1200 rpm.

$$Z = 65 \times 12$$

$$\phi = 0.02$$

$$P = 4$$

$$N = 1200 \text{ rpm}$$

$$A = 2$$

$$E_g = \frac{0.02 \times 65 \times 12 \times 1200 \times 4}{60 \times 2}$$

$$= 624 \text{ volts.}$$

- Q. An 8 pole wave connected armature has 800 conductors and the flux per pole is 0.04 wb. At what speed it must be driven to generate 400 volts.

$$Z = 800 \times 8$$

$$\phi = 0.04$$

$$E = 400$$

$$N = ?$$

$$A = 2$$

$$400 = \frac{0.04 \times 800 \times 8 \times N \times 8}{60 \times 2}$$

$$N = 187.5 \text{ rpm}$$

Q. A six pole lap wound DC generator has 600 conductors on the armature. The flux per pole is 0.02 wb. Calculate

(i) The speed at which the generator must run to generate 300 volts

(ii) What would be the speed of the generator if it is wave wound.

$$(i) E_g = \frac{\phi Z N}{60} \Rightarrow 300 = \frac{0.02 \times 600 \times N \times 6}{60 \times 30}$$

$$N = 1500 \text{ rpm}$$

$$(ii) E_g = \frac{\phi Z N P}{120} \Rightarrow E = \frac{0.02 \times 600 \times N \times 8}{120 \times 10}$$

$$N = 500 \text{ rpm}$$

- Q. An 8 pole lap wound armature rotated at 350 rpm is required to generate 260 volts. The magnetic flux per pole is 0.05 wb. If the armature has 120 slots find the no. of conductors per slot.

$$Z = 120 \times 8$$

$$\phi = 0.05$$

$$P = 8$$



$$N = 350$$

$$260 = \frac{0.05 \times 120 \times 8 \times 350}{60 \times 8}$$


$$\alpha = 7.4 \Rightarrow 7 \text{ conductors}$$

## Types of DC generators :-


### DC GENERATOR

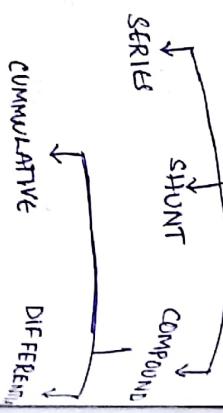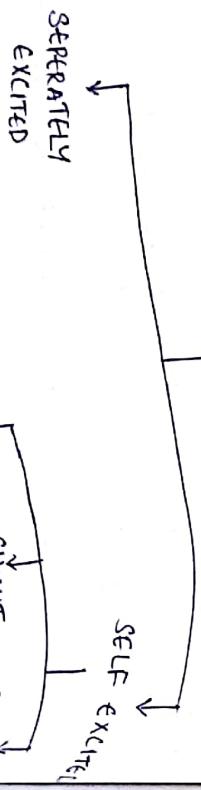

Separately excited DC-generator :-

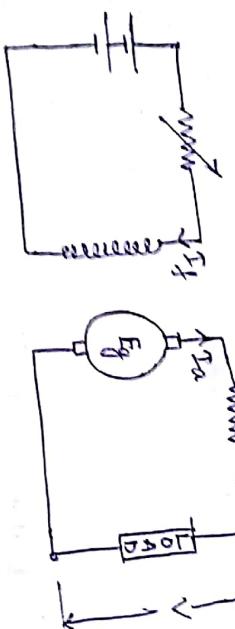

① Series DC-generator :-

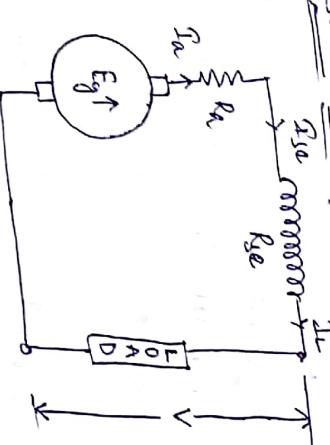

→ The DC generator whose field winding is excited from an independent external DC source is called Separately excited DC-generator.

→ Armature current.  $I_a = I_L$

→ Terminal voltage  $V = E_g - I_a R_a$

→ Power developed by the generator  $P_g = E_g I_a R_a$

$$P_g = (V + I_a R_a) I_a$$

→ Power supplied to the load  $P_L = V I_a$  or  $V I_L$

$$P_L = (E_g - I_a R_a) I_a$$

SELF EXCITED DC GENERATOR :-

The DC generator whose field winding is excited by the current from the output of the generator itself, is called as self excited DC-generator.

→ In a series DC-generator the field winding is connected in series with the armature winding so that the whole armature current flows through the field winding as well as the load.

$$I_a = I_{sc} = I_L$$

$$V = E_g - I_a R_a - I_{sc} R_{se}$$


$$= E_g - I_a (R_a + R_{se})$$

$$P_g = E_g I_a = E_g [V + I_a (R_a + R_{se})] I_a$$

$$P_L = V\Gamma_L$$

$$= [E_g - I_a(R_a + R_{se})]\Gamma_L$$

### ② Shunt DC generator :-

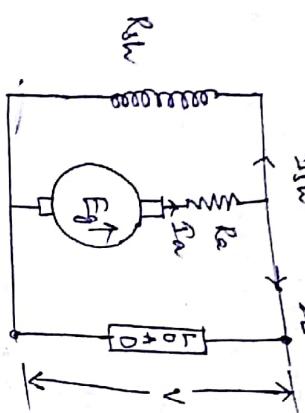

In a DC-shunt generator the field winding is connected in parallel with the armature winding so that the terminal voltage is supplied across it.

$$\Omega_a = I_{sh} + I_L \quad ! \quad I_{sh} = \frac{V}{R_{sh}}$$

$$V = E_g - I_a R_a$$


$$= I_{sh} R_{sh}$$

$$P_g = E_g I_a = (V + I_a R_a) I_a$$

$$P_L = V\Gamma_L = (E_g - I_a R_a) \Gamma_L = I_{sh} R_{sh} \Gamma_L$$
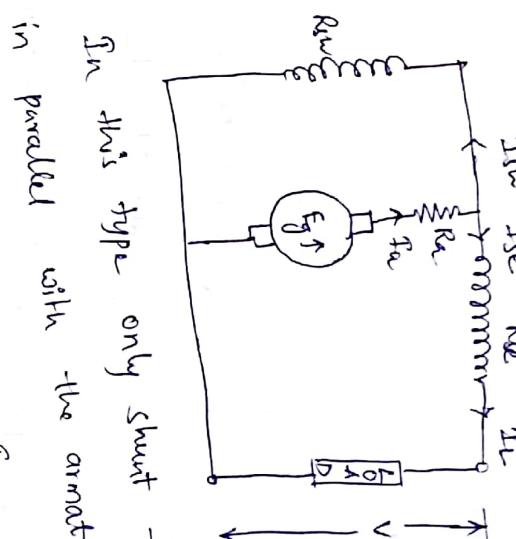
### ③ Compound generator :-

In a DC-compound generator there are two sets of field winding on each pole one in series and the other in parallel with the armature winding.



$$\text{i) Commutative compound DC generator :-}$$

$$\Omega_a = I_{sh} + I_{se} \quad ! \quad I_{sh} = \frac{V + I_{se} R_{se}}{R_{sh}}$$


$$I_{se} = \Omega_L$$

$$V = E_g - I_a R_a - I_{se} R_{se} = I_{sh} R_{sh}$$

$$P_g = E_g I_a = (V + I_a R_a + I_{se} R_{se}) I_a$$

$$P_L = V\Gamma_L = (E_g - I_a R_a - I_{se} R_{se}) \Gamma_L$$
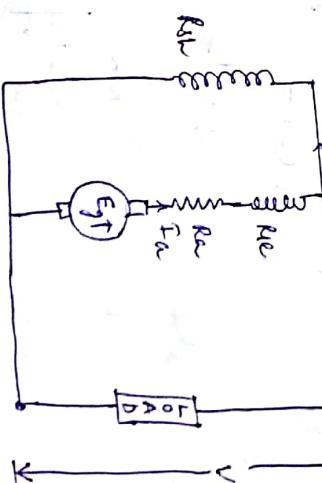
### ii) Differential compound DC generator :-



In this type the shunt field winding is parallel with both series field and armature.

$$I_a = I_A = I_{Sh} + I_L, \quad I_{Sh} = \frac{V}{R_{Sh}}$$


$$V = E_g - I_a (R_a + R_{se})$$

$$P_g = E_g I_a = [V + I_a (R_a + R_{se})] I_a$$

$$P_L = V I_L = [E_g - I_a (R_a + R_{se})] I_L$$

Q. A 100kW 240V DC shunt generator has shunt generator has

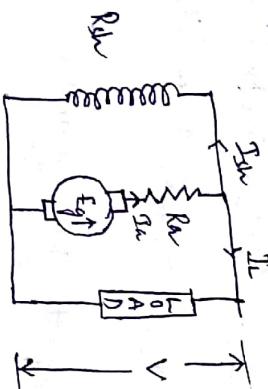field resistance of  $55\Omega$  and armature resistance of  $0.067\Omega$ . Find full load generated voltage.



$$P_L = 100 \text{ kW}$$

$$R_{sh} = 55\Omega$$

$$E_g = ?$$

$$V = 240V$$

$$R_a = 0.067\Omega$$

$$\sqrt{E_g} = V + I_a R_a$$

$$I_a = I_{sh} + I_L$$

$$\left[ I_a = \frac{V}{R_{sh}} + \frac{P_L}{V} \right]$$

$$I_{sh} = 421A$$

Q. A 30kW 300V DC shunt generator has armature and field resistances of  $0.05\Omega$  and  $100\Omega$  respectively calculate the total power developed by the armature when it delivers full load output.

$$R_a = 0.05$$

$$V = 300$$

$$R_{sh} = 100$$

$$P_g = E_g I_a$$


$$I_a = \frac{V}{R_{sh}} + \frac{P_L}{V} = 103$$

$$E_g = V + I_a R_a \\ = 300 + 103 \times 0.05$$

$$E_g = 305.15$$

$$P_g = 305.15 \times 103 \\ = 31430.45 \text{ W}$$

### ARMATURE REACTION

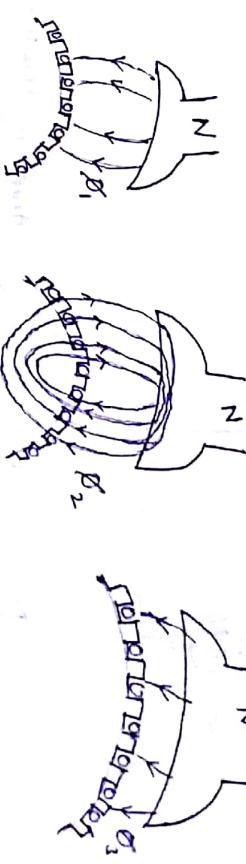



In a dc machine the current flowing through armature conductors creates a magnetic flux known as Armature flux which distorts and weakens the magnetic

flow (main flux) from the poles. This action of armature flux over the main flux is known as Armature reaction.

DC generator characteristics :-



- i) Open ckt characteristics ( $E$  vs  $I_f$ )
- ii) Internal characteristics ( $V$  vs  $I_a$ )
- iii) External characteristics ( $V$  vs  $I_a$ )

① Series generator characteristics :-

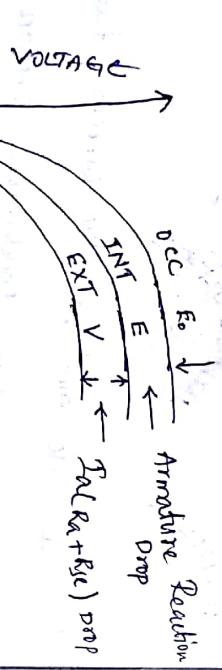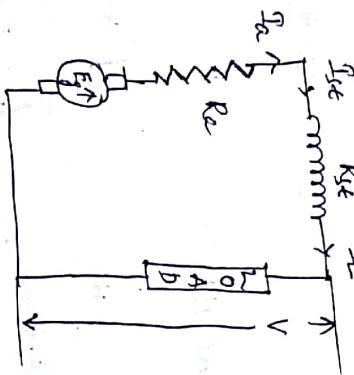

Ohmic drop.

② Shunt generator characteristics :-

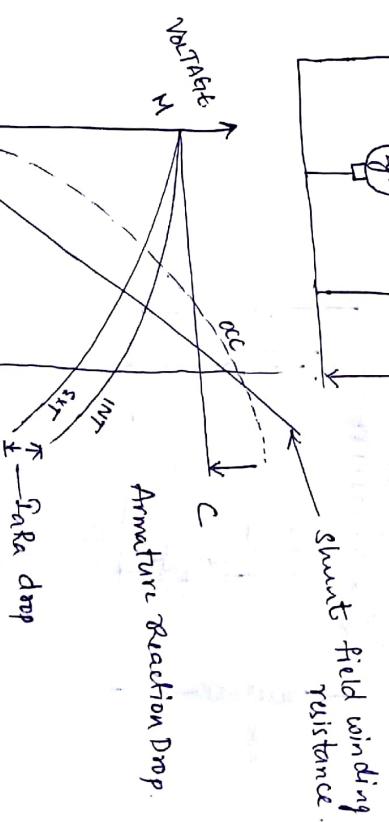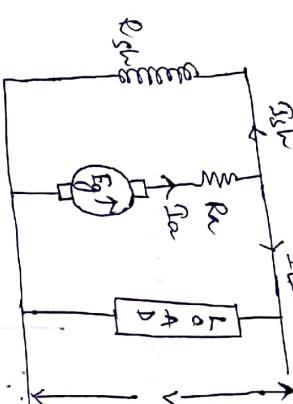

→ OC is obtained by disconnecting the field winding and exciting the machine from a separate dc source.

→ The emf generated ( $E$ ) under load conditions will be less than Emf ( $E_0$ ) under no load conditions due to the armature reaction. Therefore the internal characteristic lies below OC.

→ Since  $V = E - I_a R_a - I_a R_{se}$ , the external characteristic lies below the internal by an amount equal to  $I_a (R_a + R_{se})$ , known as

→ when the generator is run at normal speed it will represent by line

constant current generator is

will be similar

the O.C.C. of a shunt generator



to that of series is loaded the flux

→ when the generator is reduced due to the armature pole is reduced hence the emf generated reaction and hence the emf generated at is less than the emf generated at no load.

(1) no load. the external characteristics

→ Since  $V = E - IaRa$  by an amount equal to below the internal voltage drop.

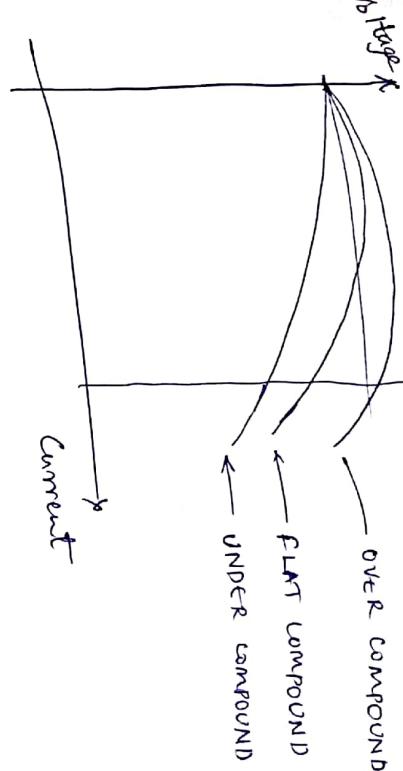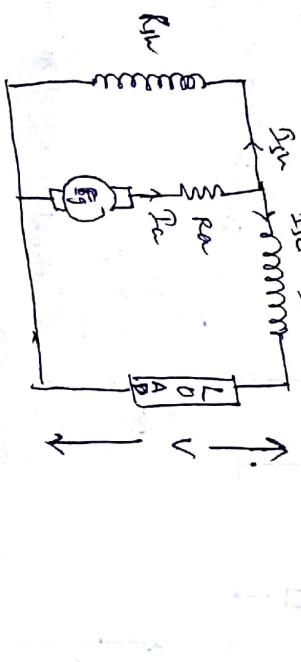(2) compound generator characteristics :-



# Star Delta Connection

$$S = \frac{70.7 \times 70.7}{509.9} = 9.802 \text{ watt-Amperes}$$

$I_{RN}$ ,  $I_{VN}$ ,  $I_{BN}$  are phase currents.  
 $I_R$ ,  $I_Y$ ,  $I_B$  are line currents.

$$\begin{aligned} & V_R \propto J \\ & V_R = I R \\ & R = \frac{70.7}{509.9} \times 500 = 69.327 \end{aligned}$$

Find current at 2 seconds.


$$\begin{aligned} I &= \frac{I_m}{\sqrt{2}} \Rightarrow I_m = \sqrt{2} I \\ & = \sqrt{2} \times \frac{70.7}{509.9} \end{aligned}$$

$$I = \frac{100}{509.9} \cdot \sin(100\pi t + 41.309) = -0.172037 \text{ Amp}$$

For parallel

$$\text{for capacitors } Z = -jX_C$$

$$\text{for inductors } Z = +jX_L$$

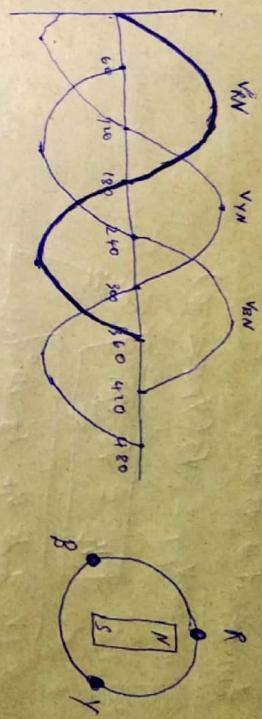

Apply KCL across load

$$I_{RN} = I_R$$

→ line current will be equal to phase current.

Here all the 'I' taken are RMS values of currents.

Apply KVL across  $V_{RN}$ ,  $V_{RN}$ ,  $V_{RN}$

$$-V_{RN} + V_R + V_{RN} = 0$$

$$\boxed{V_{RN} = V_{RN} - V_{RN}}$$

$$V_R = V_m \sin \omega t - V_m \sin(\omega t - 120)$$

$$= V_m (\sin \omega t - \sin(\omega t - 120))$$

$$= V_m \times 2 \cos \left( \frac{\omega t + \omega t - 120}{2} \right) \sin \left( \frac{\omega t - (\omega t - 120)}{2} \right)$$

$$\Rightarrow V_m \times 2 \cos(\omega t - 60) \sin 60$$

$$\Rightarrow V_m \times 2 \times \cos(\omega t - 60) \times \frac{\sqrt{3}}{2}$$

$$\Rightarrow V_m \sqrt{3} \sin(\omega t - 60)$$

$$= \sqrt{3} V_m \cos(\omega t - 60 + 90 - 90)$$

Three Phase Circuits :

Star

$$I_{RN}^m$$

$$V_{RN}$$

$$V_m(1+i_1) V_{RY} = \sqrt{3} V_m \sin(\omega t + 30^\circ)$$

Line current is  $\sqrt{3}$  times the phase current

$$V_{RY} = \sqrt{3} (V_{RN} < +30^\circ)$$

$$V_L = \sqrt{3} V_{ph}$$

$$\boxed{V_L \text{ leads } V_{ph} \text{ by } 30^\circ}$$

Phasor Diagrams

$$\boxed{V_{RN}}$$

$$V_{RN}$$

$$V_R = \sqrt{(V_{RN})^2 + (V_{RY})^2 + 2 V_{RN} V_{RY} \cos 60^\circ}$$

$$V_L = \sqrt{V_R^2 + V_B^2 + 2 \times V_{RN} \frac{V_R}{2}}$$

$$\begin{aligned} &\Rightarrow \sqrt{V_R^2 + V_{ph}^2 + V_B^2} \\ &= \sqrt{3} V_{ph} \end{aligned}$$

Phasor Diagram for  $V_{RK}$

$$\begin{aligned} V_{RK} &= \sqrt{(V_{RN})^2 + (V_{RY})^2 + 2 V_{RN} V_{RY} \cos 60^\circ} \\ &= \boxed{V_{ph}} \end{aligned}$$

$$\begin{aligned} &= \sqrt{3} V_{ph} \\ &= \boxed{\sqrt{3} V_{ph}} \end{aligned}$$

$$\begin{aligned} &V_{RN} \\ &V_{RN} \end{aligned}$$


Phasor Diagram for  $V_{RYR}$

$$\boxed{i_1 = \sqrt{3} I_m \sin(\omega t - 30^\circ)}$$

Delta Connection:

$V_{RN}, V_{RY}, V_{RN} \rightarrow$  phase voltages  
 $i_1, i_2, i_3$  are phase currents

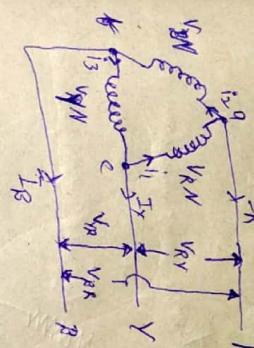$V_{RY}, V_{RP}, V_{RR}$  are line voltages  
 $I_R, I_Y, I_B$  are line currents



$$V_{RN} = V_m \sin \omega t$$

$$V_{RY} = V_m \sin(\omega t - 120^\circ)$$

$$i_2 = I_m \sin(\omega t - 120^\circ)$$

$$\begin{aligned} V_{RN} &= V_m \sin(\omega t - 120^\circ) \\ i_3 &= I_m \sin(\omega t - 240^\circ) \end{aligned}$$

$$i_1 = I_m \sin \omega t$$

$$\begin{aligned} \text{Applying KVL} \\ -V_{RN} + V_{RY} = 0 \end{aligned}$$

$$V_{RY} = V_{RN}$$

$$\boxed{V_L = V_{ph}}$$

Applying KCL at node a

$$i_1 = I_R + i_2$$

$$I_R = i_1 - i_2$$

$$I_m \sin \omega t - I_m \sin(\omega t + 120^\circ)$$

$$\begin{aligned} &= I_m \cdot 2 \cos \left( \frac{\omega t + \omega t - 120^\circ}{2} \right) \cdot \sin \left( \frac{\omega t + \omega t - 120^\circ}{2} \right) \\ &\Rightarrow I_m \cdot 2 \cos(\omega t - 120^\circ) \sin(120^\circ) \end{aligned}$$


$$\Rightarrow \sqrt{3} \cdot 2 \cos(\omega t - 120^\circ)$$

$$\begin{aligned} i_1 &\Rightarrow \sqrt{3} \cdot I_m \cos(\omega t - 120^\circ) \\ i_1 &\Rightarrow \sqrt{3} I_m \sin(\omega t - 30^\circ) \end{aligned}$$


line current lag phase current by  $30^\circ$

Phasor Diagrams:  $+30^\circ$  connection  
 $-30^\circ$  connection
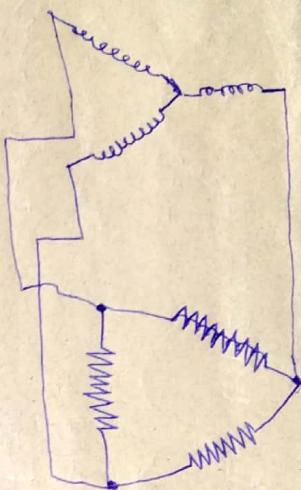
$$I_R > \sqrt{i_1^2 + i_3^2 + 2i_1i_3 \cos(120^\circ)} \\ = \sqrt{I_{ph}^2 + I_{ph}^2 + I_{ph}^2} \Rightarrow I_L = \sqrt{3} I_{ph}$$



$-30^\circ$  connection

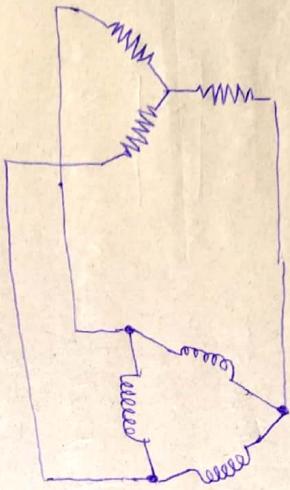

$$\begin{aligned} i_1 &= I \angle 0^\circ \\ i_2 &= I \angle -120^\circ \\ i_3 &= I \angle -240^\circ \\ i_R &= i_1 - i_3 \\ i_Y &= i_2 - i_1 \\ i_B &= i_3 - i_2 \end{aligned}$$

3 phase power =  $\sqrt{3} V_L I_L \cos \phi$

per.

$$i_3 - \phi = 3 P_1 - \phi$$

$$= 3 (V_h) (I_{ph}) \cos \phi$$

$$= 3 \times \frac{V_L}{\sqrt{3}} \cdot I_L \cos \phi \Rightarrow \sqrt{3} I_L V \cos \phi$$

For star:


$$3 - \phi = 30^\circ - \phi$$

$$3 \# T \sin \phi$$

$$= \sqrt{3} \cdot V_L I_L \sin \phi$$

$$\text{per.} \\ V_L = V_h \quad \text{if } I_L = \sqrt{3} I_{ph}$$

$$I_{ph} = I_L \sqrt{3}$$

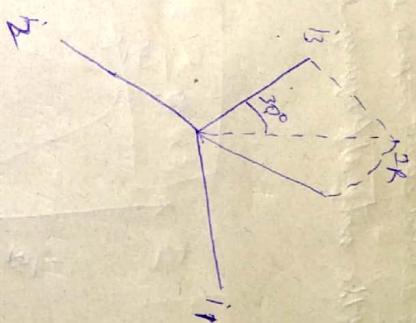

For  $i_2$  and  $i_3$ .

R

R

Subtract the phase angle of the R-phase from all the phase angles

$$\angle V_R' = 27^\circ - 27^\circ = 0^\circ$$

$$\angle V_Y' = 27^\circ - 147^\circ = -120^\circ$$

$$\angle V_B' = 27^\circ + 93^\circ = 120^\circ$$

Therefore, the phase sequence is 'RYB'

- (ii) First, convert the cosine waveforms into phasors

$$v_{an} = 200 \cos(\omega t + 10^\circ) \Rightarrow V_{an} = 200 \angle 10^\circ$$

$$v_{bn} = 200 \cos(\omega t - 230^\circ) \Rightarrow V_{an} = 200 \angle -230^\circ$$

$$v_{cn} = 200 \cos(\omega t - 110^\circ) \Rightarrow V_{an} = 200 \angle -110^\circ$$

Subtract the phase angle of the a-phase from all the phase angles

$$\angle V_{an}' = 10^\circ - 10^\circ = 0^\circ$$

$$\angle V_{bn}' = 10^\circ + 230^\circ = 240^\circ$$

$$\angle V_{cn}' = 10^\circ + 110^\circ = 120^\circ$$

Therefore, the phase sequence is 'abc'

## 4.5 Three Phase Balanced System Connections

### 4.5.1. Star Connection

When three similar polarity terminals of three sources are connected at a single point as shown in Figure (4.5) it is known as a star connection. The point of connection is known as source neutral and represented by 'N'. Similarly, three loads are joined at a single point known as load neutral and represented by 'n'. The wire joining source neutral point 'N' and load neutral point 'n' is known as neutral wire or simply neutral. After connecting three similar terminals at the neutral point, the remaining three free terminals of the source are joined to the load by means of individual conductors known as lines R, Y and B as shown in figure (4.5). Three lines carry the currents from the source to the load and neutral carries all the return currents from load to source. Therefore neutral current,  $I_N$  is the sum of three currents.

$$\therefore I_N = I_R + I_Y + I_B \quad (4.4)$$

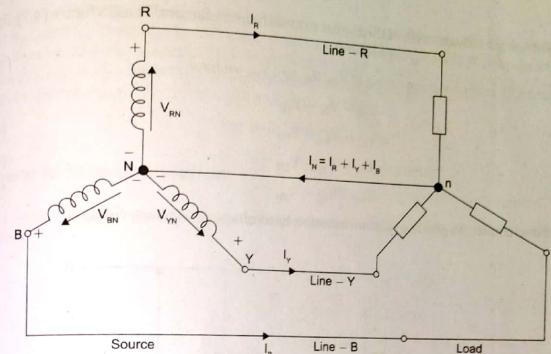


Figure (4.5): Star connection

In 3-phase balanced system if the loads in all the 3-phases are balanced, then three currents  $I_R$ ,  $I_Y$ ,  $I_B$  constitute balanced system of currents.

$$\therefore I_R = I \angle 0^\circ, I_Y = I \angle -120^\circ, I_B = I \angle 120^\circ$$

$$I_N = I_R + I_Y + I_B = I \angle 0^\circ + I \angle -120^\circ + I \angle 120^\circ = 0$$

From the above calculations, it is clear that neutral current  $I_N$  is zero. Hence, in a balanced system neutral wire is not required. Such a system is known as 3-phase 3-wire system.

**Line Voltages and Phase Voltages:** Phase voltage is a voltage measured between any line conductor and the neutral. Thus, in figure (4.6), three phase voltages  $V_{RN}$ ,  $V_{YN}$  and  $V_{BN}$  are shown.

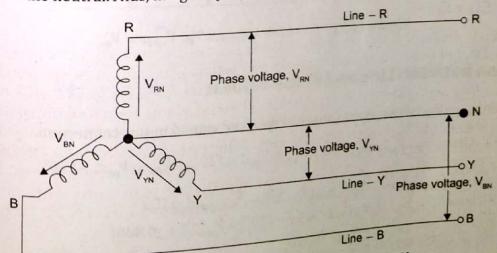


Figure (4.6): Three phase voltages  $V_{RN}$ ,  $V_{YN}$  and  $V_{BN}$

Line voltage is a voltage measured between any two line conductors. Thus in figure (4.7), the line voltages  $V_{RY}$ ,  $V_{YB}$  and  $V_{BR}$  are shown.

Applying KVL to the loop consisting of  $V_{RN}$ ,  $V_{RY}$  and  $V_{YN}$  we have

$$V_{RN} - V_{RY} - V_{YN} = 0$$

$$\Rightarrow V_{RY} = V_{RN} - V_{YN}$$

$$\text{Similarly, } V_{YB} = V_{RN} - V_{BN}$$

$$V_{BR} = V_{BN} - V_{RN}$$

The above equations give the relation between line voltages and phase voltages.

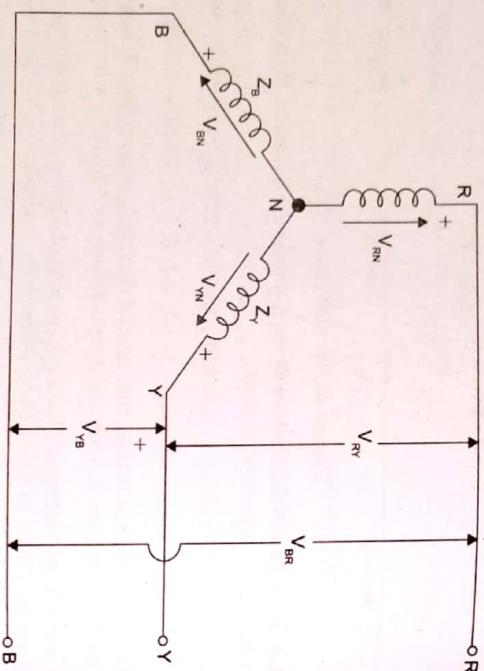


Figure (4.7): Three line voltages  $V_{RY}$ ,  $V_{YB}$  and  $V_{BR}$

### Relation between Line and Phase Values:

Let  $V_{RN} = V_{YN} = V_{BN}$  be the phase voltage of balanced system in star connection.

$$\therefore V_{RN} = V_{ph} \angle 0^\circ, \quad V_{YN} = V_{ph} \angle -120^\circ, \quad V_{BN} = V_{ph} \angle +120^\circ$$

$$\therefore V_{RY} = V_L = V_{RN} - V_{YN} = V_{ph} \angle 0^\circ - V_{ph} \angle -120^\circ \\ = V_{ph} [1 \angle 0^\circ - 1 \angle -120^\circ] = V_{ph} [1.5 + j0.866]$$

$$= 1.732 \angle 30^\circ \times V_{ph}$$

$$\Rightarrow V_L = \sqrt{3} V_{ph}$$

(4.8)

therefore, the magnitude of the line voltage  $V_{RY}$  is  $\sqrt{3}$  times the magnitude of the phase voltage  $V_{RN}$ , and  $V_{RY}$  leads  $V_{RN}$  by  $30^\circ$ . Same is the case with the other two line voltages. From the star connected 3-phase system, it is clearly observed that whatever current flows through the lines R, Y and B also flows through the respective phase windings or coils. Hence in a star connected system the phase currents and line currents are equal.

For star connected  $I_L = I_{ph}$

$$(4.5) \quad P = 3 \times \text{per phase power} = 3 \times V_{ph} I_{ph} \cos\phi$$

$$= 3 \times \frac{V_L}{\sqrt{3}} \times I_L \cos\phi = \sqrt{3} V_L I_L \cos\phi$$

$$(4.6) \quad P = \sqrt{3} V_L I_L \cos\phi$$

### 4.5.2 Delta or Mesh Connection

In a delta or mesh connection, the dissimilar ends of the 3-phase windings are joined together i.e. the starting end of one phase is joined to the finishing end of other phase and so on as shown in figure(4.8).

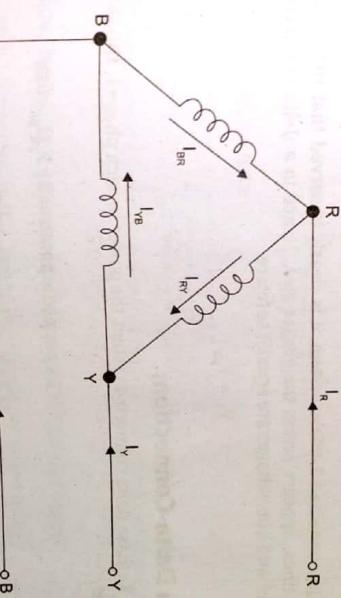


Figure (4.8): Delta connection

In the above figure,  $I_{RY}$ ,  $I_{YB}$  and  $I_{BR}$  represents phase values of currents and  $I_R$ ,  $I_Y$  and  $I_B$  represents line values of currents.

From the above figure (4.8), by applying KCL at node R

$$-I_{BR} - I_R + I_{RY} = 0 \quad (4.11)$$

$$\Rightarrow I_R = I_{RY} - I_{BR} \quad (4.12)$$

$$\text{Similarly } I_Y = I_{YB} - I_{RY} \quad (4.13)$$

$$I_B = I_{BR} - I_{YB}$$

### Relation Between Line and Phase Values:

Let  $I_{RY} = I_{YB} = I_{BR} = I_{ph}$  be the phase current of balanced system in delta connection.

$\therefore I_{RY} = I_{ph} \angle 0^\circ, I_{YB} = I_{ph} \angle -120^\circ, I_{BR} = I_{ph} \angle +120^\circ$

Line current flowing through the R-phase

$$\begin{aligned} I_R &= I_L = I_{RY} - I_{BR} = I_{ph} \angle 0^\circ - I_{ph} \angle 120^\circ \\ &= I_{ph} [1 \angle 0^\circ - 1 \angle 120^\circ] = I_{ph} [1.5 - j0.866] \\ &= 1.732 \angle -30^\circ \times I_{ph} \\ \therefore I_L &= \sqrt{3} I_{ph} \end{aligned} \quad (4.14)$$

From the above equation, it is clear that the line current  $I_L$  is  $\sqrt{3}$  times the phase current and current  $I_R$  lags  $I_{RY}$  by  $30^\circ$ .

From the delta connected 3-phase system, it is clearly observed that the voltage that exists between the lines, appears across the phases also.. Hence in a delta connected system the phase voltages and line voltages are equal. Therefore

$$V_L = V_{ph} \quad (4.15)$$

### Power in a Delta-Connection:

In a balanced 3-phase delta connected system, the power in each phase is the same. Therefore 3-phase power

$$P = 3 \times \text{per phase power} = 3 \times V_{ph} I_{ph} \cos \phi$$

$$= 3 \times V_L \times \frac{I_L}{\sqrt{3}} \cos \phi = \sqrt{3} V_L I_L \cos \phi$$

$$P = \sqrt{3} V_L I_L \cos \phi \quad (4.16)$$

From eqns. (4.10) and (4.16), it is clear that irrespective of star connection or delta connection

$$\text{3-phase power, } P = \sqrt{3} V_L I_L \cos \phi \quad (4.17)$$

### 4.5.3 Balanced Star/Delta and Delta/Star Conversions

Any balanced star connected system can be converted into an equivalent delta connected system and vice versa.

For a balanced star connected load, let

$$\text{Line voltage} = V_L$$

$$\text{Line current} = I_L$$

$$\text{Impedance per phase} = Z_Y$$

$$V_{ph} = \frac{V_L}{\sqrt{3}}$$

$$I_{ph} = I_L$$

$$Z_Y = \frac{V_{ph}}{I_{ph}} = \frac{V_L}{\sqrt{3}I_L} \quad (4.18)$$

For an equivalent delta connected system, the line voltages and currents must have the same values as in the star connected system, i.e.,

$$\text{Line voltage} = V_L$$

$$\text{Line current} = I_L$$

$$\text{Impedance per phase} = Z_\Delta$$

$$V_{ph} = V_L$$

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$Z_\Delta = \frac{V_{ph}}{I_{ph}} = \frac{V_L}{I_L / \sqrt{3}} = \frac{\sqrt{3}V_L}{I_L} \quad (4.19)$$

From eqns. (4.18) & (4.19), we have

$$Z_Y = \frac{V_L}{\sqrt{3}I_L} = \frac{Z_\Delta}{\sqrt{3} \times \sqrt{3}} = \frac{Z_\Delta}{3} \quad (4.20)$$

Thus, when three equal impedances are connected in delta, the equivalent star impedance is one third of the delta impedance.

### 4.5.4 Relation between power in Delta and Star systems

Let a balanced load be connected in star having impedance per phase as  $Z_{ph}$ .

For a star connected load,

$$V_{ph} = \frac{V_L}{\sqrt{3}}$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{V_L}{\sqrt{3}Z_{ph}}$$

$$I_L = I_{ph} = \frac{V_L}{\sqrt{3}Z_{ph}}$$

Now  $P_Y = \sqrt{3}V_L I_L \cos\phi = \sqrt{3}V_L \times \frac{V_L}{\sqrt{3}Z_{ph}} \times \cos\phi = \frac{V_L^2}{Z_{ph}} \times \cos\phi$

$$\Rightarrow P_Y = \frac{V_L^2}{Z_{ph}} \times \cos\phi$$
(4.2)

For a delta connected load,

$$V_{ph} = V_L$$

$$I_{ph} = \frac{V_{ph}}{Z_{ph}} = \frac{V_L}{Z_{ph}}$$

$$I_L = \sqrt{3}I_{ph} = \sqrt{3} \times \frac{V_L}{Z_{ph}}$$

Now  $P_\Delta = \sqrt{3}V_L I_L \cos\phi = \sqrt{3}V_L \times \sqrt{3} \frac{V_L}{Z_{ph}} \times \cos\phi = 3 \frac{V_L^2}{Z_{ph}} \times \cos\phi$

$$\Rightarrow P_\Delta = 3 \frac{V_L^2}{Z_{ph}} \times \cos\phi$$
(4.2)

From eqns. (4.21) & (4.22), we have

$$P_Y = \frac{P_\Delta}{3} \Rightarrow P_\Delta = 3P_Y$$
(4.2)

Thus power consumed by a balanced delta connected load is three times that in the case of star connected load.

#### 4.5.5 Comparison between Star and Delta Connections

S. No	Star Connection	Delta Connection
1	Similar ends are joined	Dissimilar ends are joined
2	$V_L = \sqrt{3}V_{ph}$ & $I_L = I_{ph}$	$V_L = V_{ph}$ & $I_L = \sqrt{3}I_{ph}$
3	Possible to carry neutral current	Neutral wire is not available
4	Provides 3-phase 4-wire arrangement	Provides 3-phase 3-wire arrangement
5	The phasor sum of all the phase currents is zero	The phasor sum of all the phase voltages is zero
6	Can be used for lighting as well as power loads	Can be used for power loads only