

logic families basic

Logic Families  
Logic family explains, how to implement a logic device using active device

→ Logic families classification is based on the active device used

→ propagation delay is related to internal capacitance effects

→ In MOSFET, internal capacitance is on the range of  $1\text{f}$

→ In BJT, internal capacitance is on the range of  $\text{nF}$  and  $\text{pF}$

→ As capacitance increases, charging and discharging time increases and hence propagation delay is more in BJT

→ BJT logic family having less propagation delays with more power consumption compared to unipolar (FET) logic family

→ power consumption is higher in BJT Bipolar logic family

Saturated logic family

↓  
BJT operating b/w cutoff & saturation regions

Non Saturated logic family

↓  
BJT operating b/w cutoff & active region

Modes of operation of Transistor


- ① Active mode  $\rightarrow (BE \rightarrow FB) (BC \rightarrow RB) \rightarrow$  Amplifier
- ② Saturation mode  $\rightarrow (BE \rightarrow FB) (BC \rightarrow FB) \rightarrow$  <sup>ON</sup> Switch
- ③ Cut off mode  $\rightarrow (BE \rightarrow RB) (BC \rightarrow RB) \rightarrow$  <sup>off</sup> switch

BJT logic families (Saturated logic)


uses saturation & cut off mode.

Non-saturated logic families uses active & cut off mode.

## n p n (Transistor)


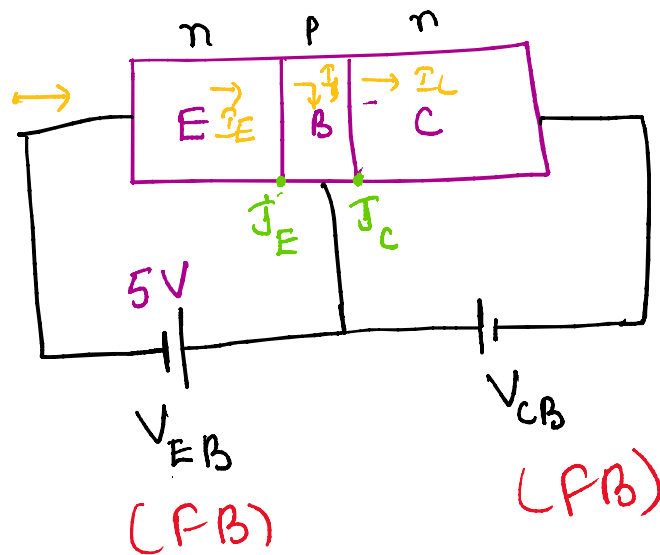


## Saturation mode

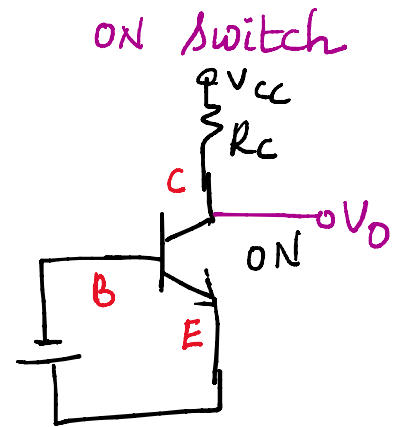

NPN transistor as ON switch apply 5V to the base of the transistor

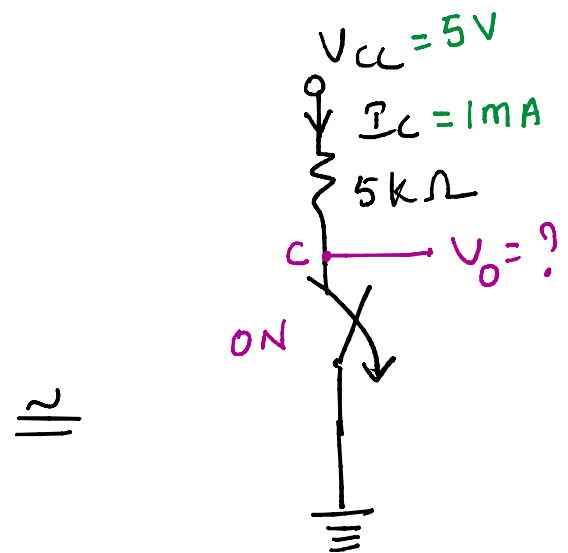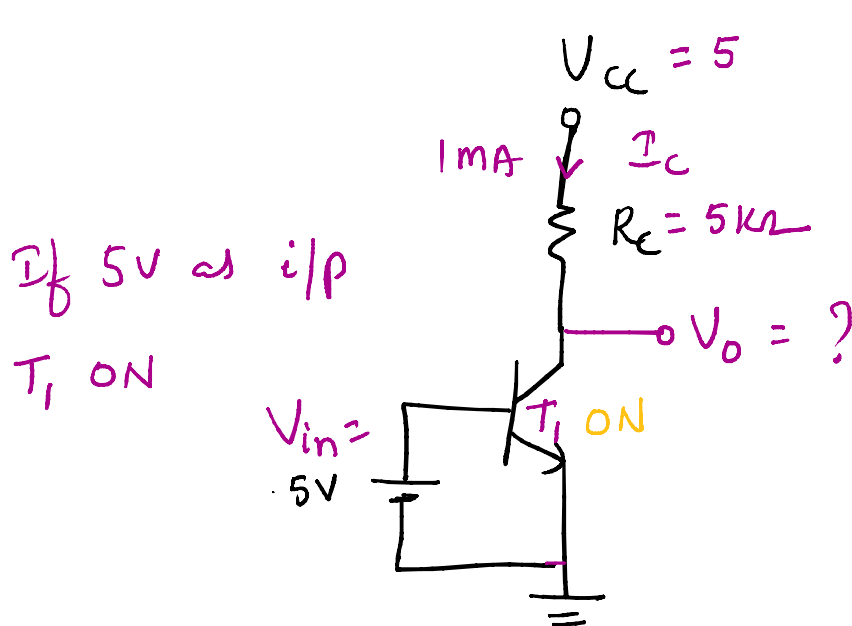NPN  $\rightarrow$  off switch,  $V_B = 0V$



$$V_{CC} = I_C R_C + V_O$$


$$V_O = V_{CC} - I_C R_C$$

$$= 5 - 1 \times 10^{-3} \times 5 \times 10^3$$


$$= 0\text{V}$$

Here  $V_{in} = 5\text{V}$  then  $V_O = 0$



Cut off mode (off switch)

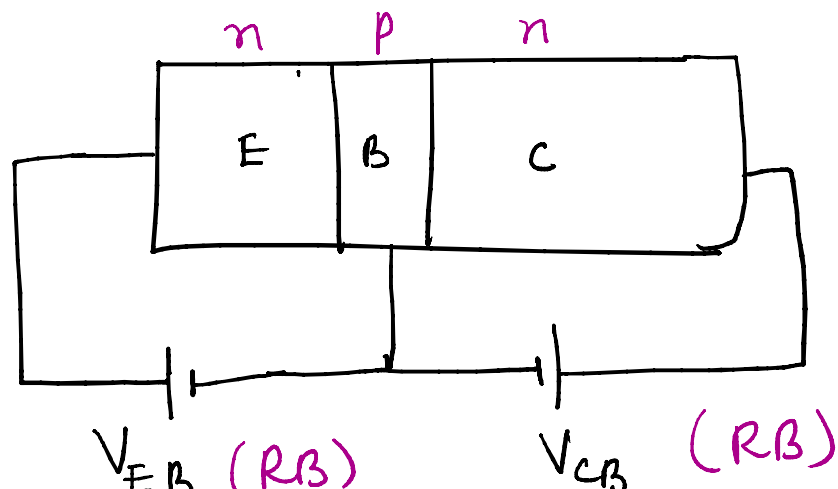

$V_{EB} (RB)$

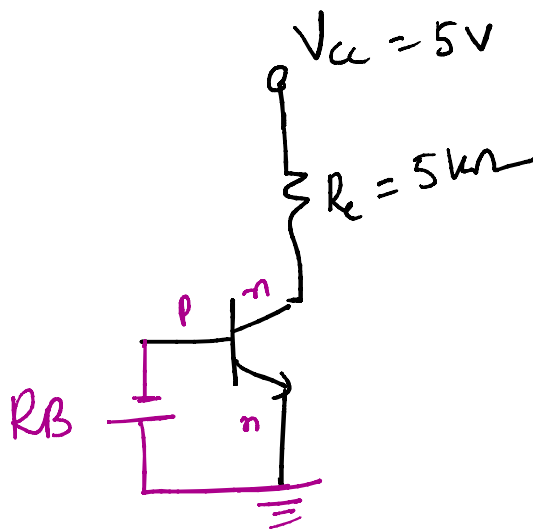

$V_{CB} (RB)$

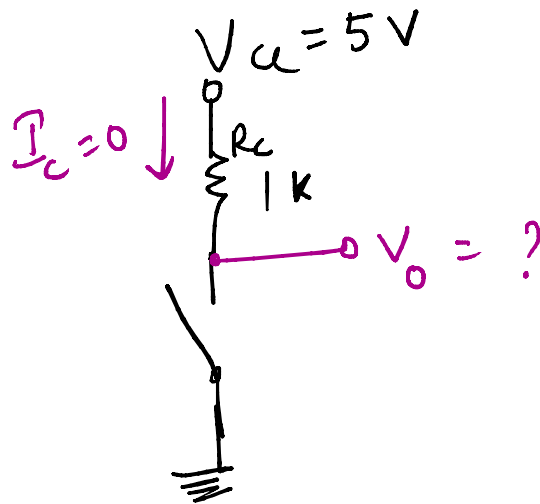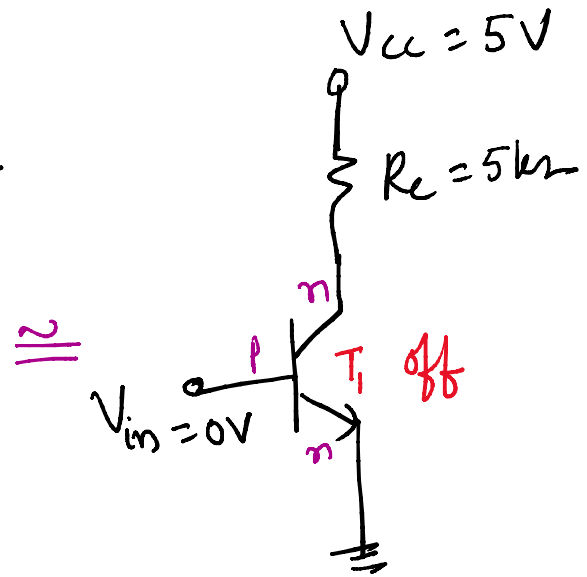

$$V_{cc} = I_c R_c + V_o$$

$$V_o = V_{cc} - \underbrace{I_c R_c}_0$$


$$= 5 - 0$$

$$V_o = 5V$$

If  $V_{in} = 0 \Rightarrow$  then  $V_o = 5V$

## Truth table (NOT)

$V_{in}$	$V_o$
5	0
0	5V

NOT symbol  


$5V \cong \text{logic '1'}$   
 $0V \cong \text{logic '0'}$

$V_{in}$	$V_o$
1	0
0	1