

$$R_i = h_{ie} - \frac{h_{fbc} R_L}{1 + h_{oerL}} = 995.45$$

$$-A_v = -45.65$$

$$R_o = 10.2k\Omega$$

$$R_{os} = R_{ol} \| R_L = 911\Omega$$

$$\frac{A_i + L}{R_i + R_s}$$

$$-A_{vs} = \frac{-A_v \cdot R_L}{R_i + R_s} = -22.63$$

$$-A_{ys} = \frac{A_i \times R_s}{R_s + R_i}$$


$$R_{os} = R_{ol} \| R_L$$


$$R_{is} = R_i + R_s$$

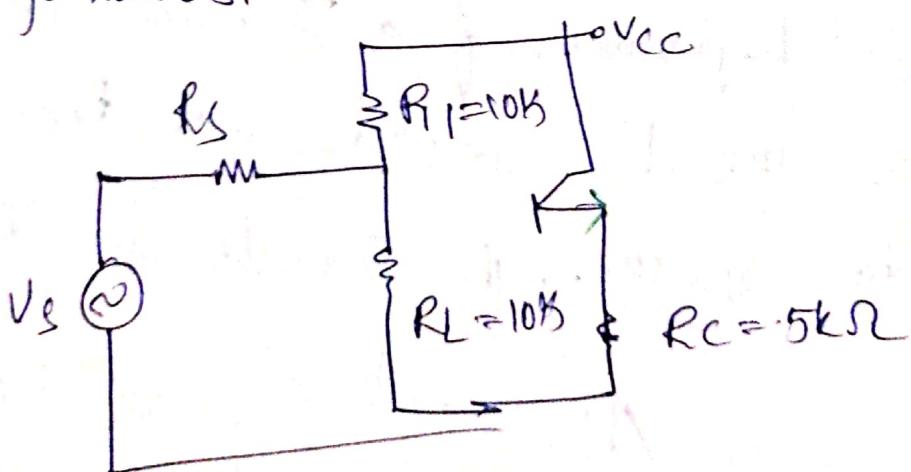3) A transistor used in a C.C circuit as shown below has the following set of h-parameters.

$$h_{ic} = 2k\Omega, h_{fc} = -5, h_{rc} = 1, h_{oc} = 25 \times 10^{-6} \text{ mhos.}$$

Find the values of I_D & o/p resistances current & voltage gain of amplifier stage. Use the exact hybrid formulas.



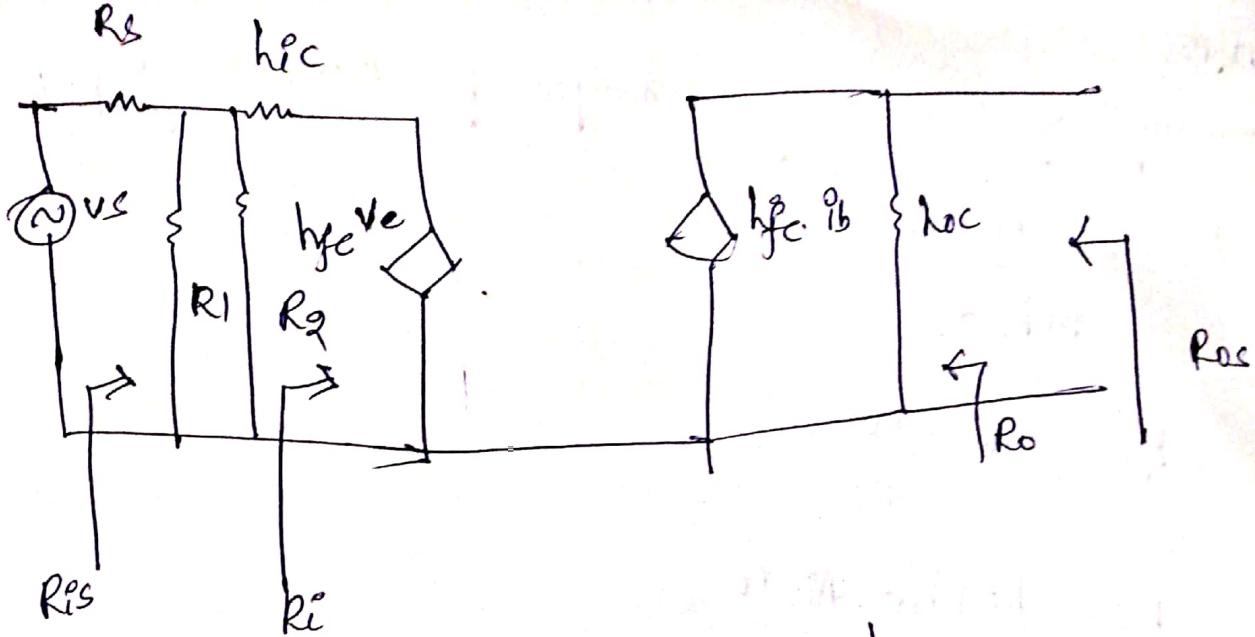

$$r_e = r_L = 5\text{ k}\Omega$$

$$A_i^o = \frac{-h_{fe}}{1 + h_{oc} r_L} = 45.33$$

$$r_i = h_{ic} - \frac{h_{fe} h_{rc} r_L}{1 + h_{oc} r_L} = 228.7\text{ k}\Omega$$

$$-A_v = \frac{A_i^o r_L}{r_i} = 0.994$$

$$r_{is} = R_i \parallel R_1 \parallel R_2 = R_i \parallel 5\text{ k}\Omega = 4.892\text{ k}\Omega$$

$$r_o = \frac{R_s + h_i}{R_{shot} + h_o} = 58.67$$

$$-A_{ic}^o = 4.644$$

$$-A_{vs} = \frac{-A_v \cdot R_s}{R_{is} + R_s} = 0.833$$

17/01/15

Summary of small signal analysis of transistor amplifiers

$$-A_i^o = -\frac{h_f}{1+h_{o\beta}r_L}$$

$$-A_v = -A_i^o \cdot \frac{r_L}{R_i}$$

$$R_i = h_{i\beta} + h_{ir} \cdot A_i^o \cdot r_L$$

$$R_i = h_{i\beta} + \frac{h_{rf}h_f}{h_{o\beta} + r_L} \quad \text{or} \quad \frac{h_{i\beta} - h_{rf}h_f r_L}{h_{o\beta} + r_L}$$

$$R_o = \frac{R_s + h_{i\beta}}{R_{short} + \Delta b} \quad \Delta b = h_{i\beta}h_o - h_{rf}h_o$$

$$Y_o = h_o - \frac{h_{rf}h_f}{R_s + h_{i\beta}}$$

$$-A_p = -A_v \cdot A_i^o = -A_i^o \cdot \frac{r_L}{R_i}$$

$$-A_{vs} = \frac{-A_v \cdot R_i}{R_s + R_i} = \frac{-A_i^o \cdot r_L}{R_s + R_i} = \frac{-A_{is} \cdot r_L}{R_s}$$

$$-A_{is} = \frac{-A_i^o \cdot R_s}{R_s + R_i} = A_{vs} \cdot \frac{R_s}{r_L}$$

NOTE The above formulae are applicable for all transistor configurations, only we have to add the appropriate subscript to h-parameters i.e; e for CE

'b' for CB & 'c' for CC results such as h_{ie} , h_{fe} , h_{oe} , etc.

Typical h-parameter values for a transistor

Parameter	CE	CC	CB
$h_{11} = h_i$	1100Ω	1100Ω	$\approx 22\Omega$
$h_{12} = h_{re}$	2.5×10^4	≈ 1	3×10^4
$h_{21} = h_f$	50	-51	-0.98
$h_{22} = h_o$	<u>$25 \mu A/V$</u>	$25 \mu A/V$	$0.49 \mu A/V$

Standardized values at room temperature.

Comparison of 3-transistor configurations

The quantities A_i , A_v , R_i , R_o & A_p are calculated for a typical transistor whose h-parameters are shown in previous table.

The values of R_L & s taken as $3k\Omega$.

Quantity	CE	CC	CB
A_i	$0.98(L)$	$47.5(H)$	$-46.5(H)$
A_v	$131(H)$	$0.989(L)$	$-131(H)$
A_p	128.38	46.98	6091.5
R_i	$22.6\Omega(H)$	$144 k\Omega(H)$	$1065\Omega(H)$
R_o	$1.72 m\Omega(H)$	$80.55\Omega(L)$	$45.5 k\Omega(H)$

OBSERVATIONS

CF configuration This configuration gives high current gain and high voltage gain also medium input resistance and high ~~input~~^{output} resistance is a good compromise value.

Due to this features, the CF configuration is most versatile and widely used.

CC configuration the most important feature of this configuration is high input resistance and low output resistance.

The high input resistance makes it suitable for used high impedance loads.

The low output resistance allows to be used with low impedance loads.

Thus this configuration is widely used buffer stage.

CB configuration


The low input resistance and high output resistance of the ckt makes of a choice for use with low impedance source and a high impedance load.

This configuration is not widely used.




guidelines for analysis of a transistor circuit -
(or) small signal equivalent circuit &
the actual circuit diagram.

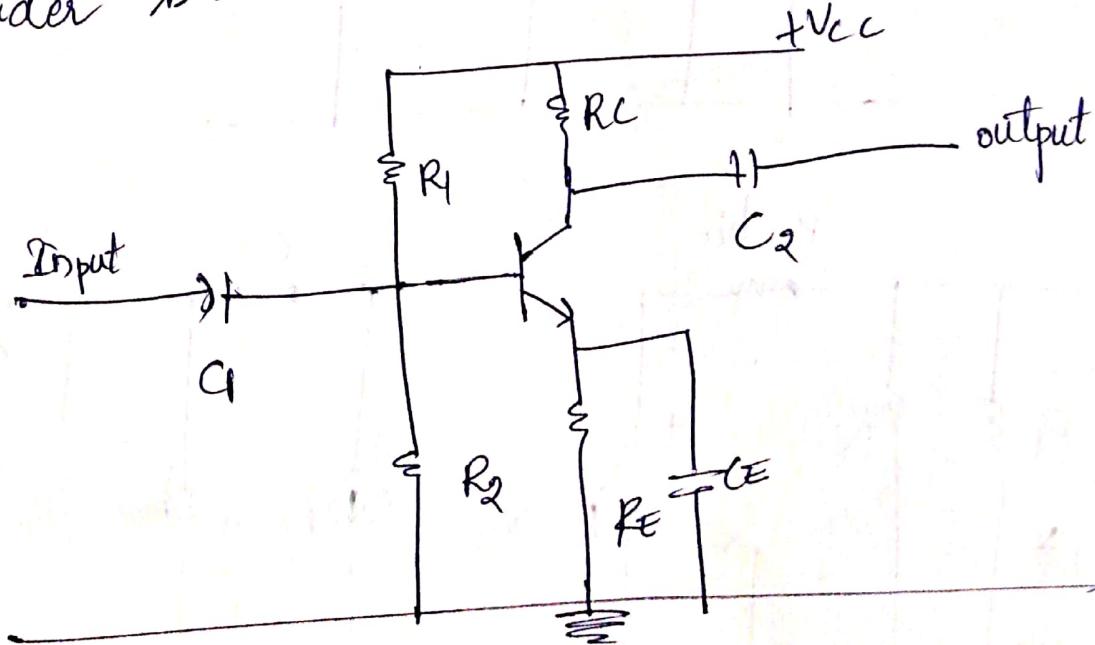- 1) Draw the actual circuit diagram.
- 2) Replace coupling capacitors and emitter bypass capacitors by short circuit.
- 3) Replace DC source by a short circuit. In other words short V_{cc} and ground lines.
- 4) make the points B , C & E on the circuit diagram
- 5) Replace the transistor by its h-parameter model

The following example explains us how to use guidelines for analysis of a transistor circuit:-
consider CE amplifier with voltage divider bias circuit.



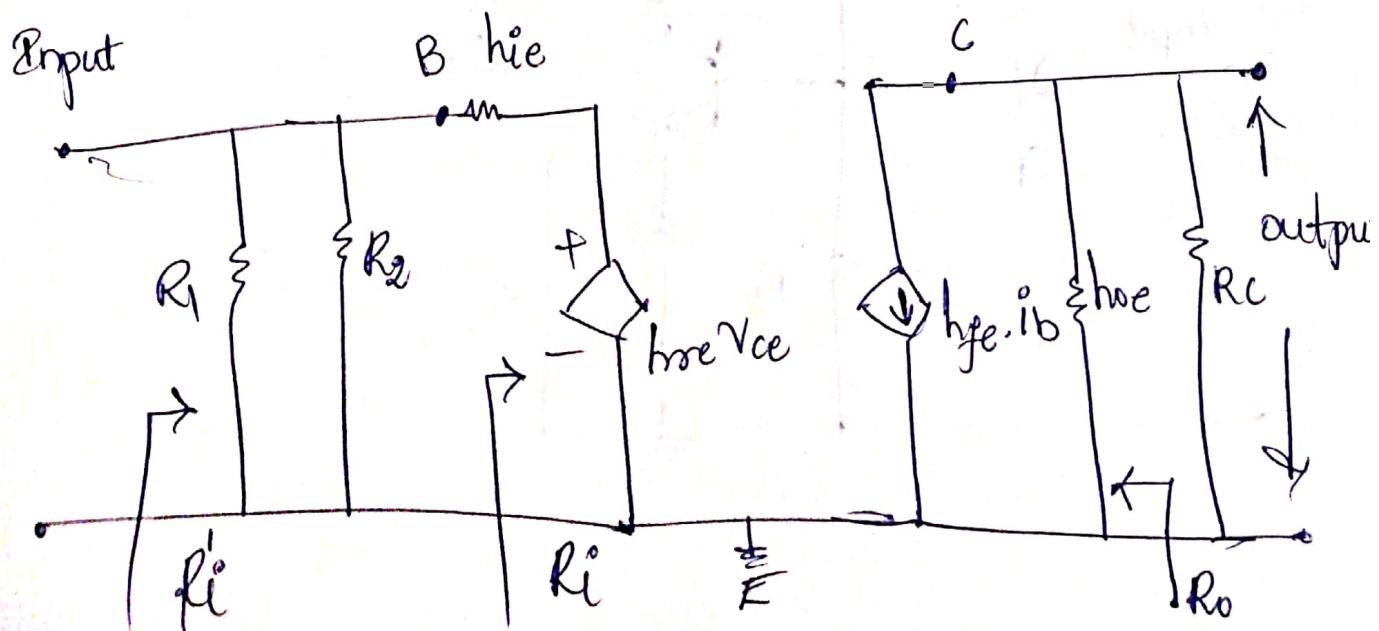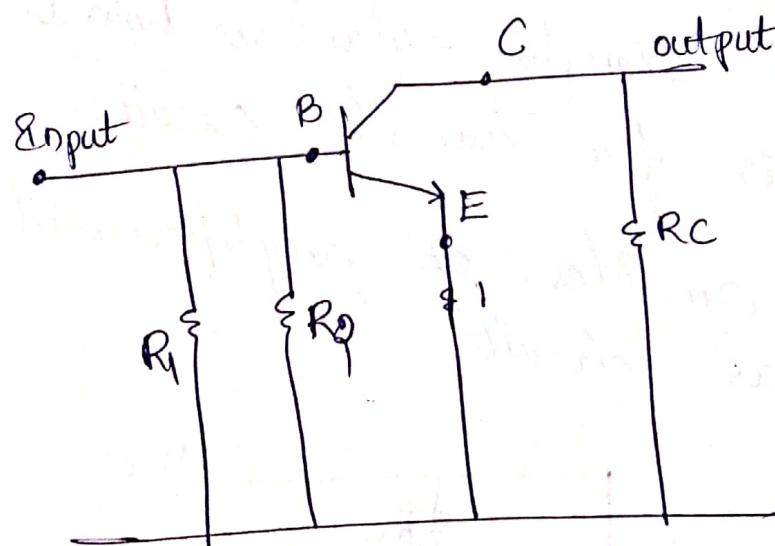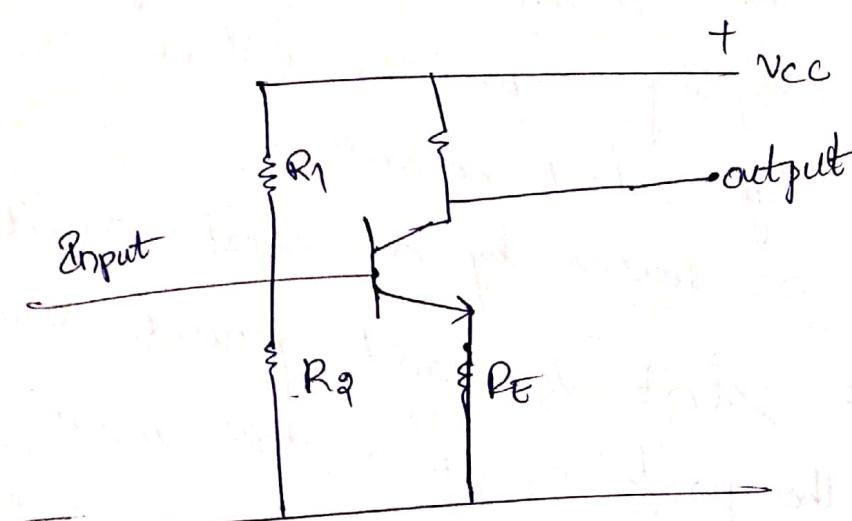C_1 & C_2 are coupling capacitors & CE emitter bypass capacitor.



$$R_i^i = R_1 \parallel R_1 \parallel R_2 \quad \& \quad R_o^i = R_0 \parallel R_C$$

Consider a single stage CE amplifier with $R_S = 1K\Omega$, $E_R = 50V$

$R_2 = 2K\Omega$, $R_C = 1K\Omega$, $R_L = 1.2K\Omega$, $\beta_{FE} = 50$, $h_{ie} = 1.1K\Omega$,

$h_{oe} = 25 \mu A/V$ & $h_{re} = 2.5 \times 10^{-4}$ as shown below.

$$\text{Sol} \quad R_i^i = R_1 \parallel R_2 \parallel R_i^i = (1.92K\Omega) \parallel 1.1K\Omega \\ = 0.700K\Omega$$

$$R_o^i = R_0 \parallel R_C = 1\Omega$$

19/01/15


Analysis of Transistor Amplifier using Simplified ~~(or)~~ Approximate hybrid model

So far we have seen that exact calculations of current gain, voltage gain, input resistance, output resistance of transistor amplifier circuits. In most practical cases, it is appropriate to obtain the approximate values. (Simplified values) of A_i , A_v ,

A_f , R_i , R_o rather than to carry out more lengthy exact calculations.

The condition for approximate analysis is
 $h_{oe} \cdot R_L \ll 0.1$, otherwise solve with exact analysis

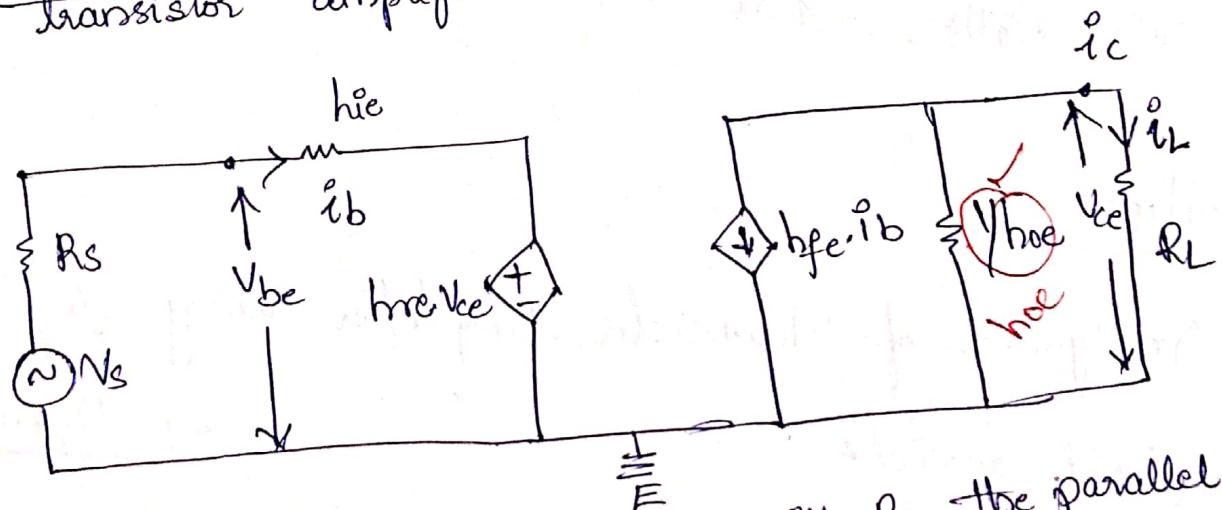- Analysis of common emitter transistor amplifier using simplified hybrid model & consider the hybrid equivalent circuit of CE transistor amplifier &



Since V_{hoe} is in parallel with R_L , the parallel combination of two unequal impedances i.e., V_{hoe} & R_L is approximately equal to lower value i.e., R_L . Hence V_{hoe} is very much greater than R_L .

i.e;

$$\frac{1}{h_{oe}} \gg R_L$$

$$\Rightarrow h_{oe} \cdot R_L \ll 1$$

$$\frac{1}{h_{oe}} \approx 10^6 \text{ S}$$

$$h_{oe} \approx \frac{1}{10^6 \text{ S}}$$

Then the term h_{oe} may be neglected. If we neglect h_{oe} , the collector current $i_c = h_{fe} \cdot i_b$

The magnitude of voltage of the generator in emitter circuit is $h_{re} \cdot V_{ce}$ i.e; $V_{re} = 2.5 \times 10^4 \text{ mV}$



$$h_{re} \cdot V_{ce} = -h_{re} \cdot i_c \cdot R_L$$

$$h_{re} \cdot V_{ce} = -h_{re} \cdot h_{fe} \cdot i_b \cdot R_L$$


$$h_{re} = 5$$

~~Since~~ Since $h_{re} \cdot h_{fe} \approx 0.01$. This voltage may be neglected in comparison with voltage drop across h_{ie} i.e; $h_{ie} \cdot i_b$

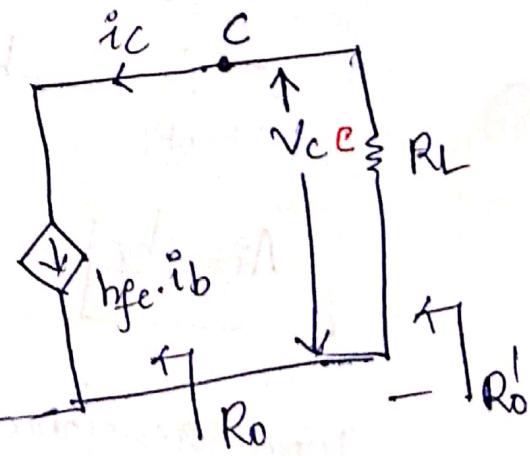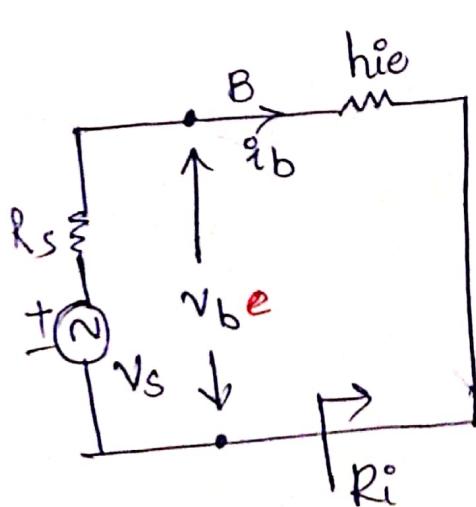To conclude if the load resistance R_L is too small, it is possible to neglect the parameters h_{re}, h_{ie} and obtain the hybrid equivalent circuit as shown below



Generalised approximate models

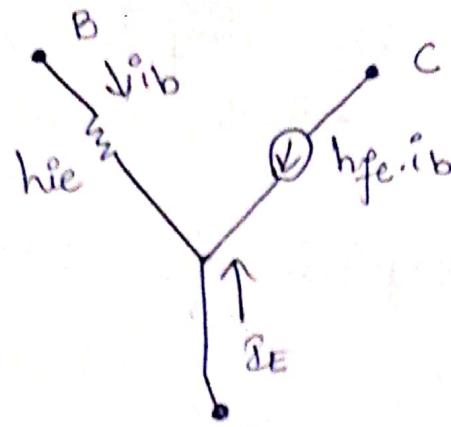

the above figure is valid for any configuration by simply grounding the appropriate terminal.

the input is applied between input and ground and the load is connected between output and ground.

21/01/15

Current gain (A_i)

$$-A_i = \frac{-h_f}{1+h_{oRL}} = -h_f$$

$$\boxed{-A_i = -h_f}$$

$$A_i = -h_f$$

Input resistance R_i

$$R_i = h_{ie} + h_{re} - A_i R_L$$

$$\boxed{R_i = h_{ie}}$$

$$R_i \approx h_{ie}$$

③ Voltage gain (A_v)

$$A_v = A_i \frac{R_L}{R_i}$$

$$A_v = A_i \cdot \frac{R_L}{h_i} = \boxed{\frac{-h_f R_L}{h_i} = A_v}$$

④ Output resistance R_o

$$R_o = \frac{V_{CE}}{i_C} = \frac{V_{CE}}{i_L}$$

while obtaining the output resistance, the condition is $R_L = \infty$

$$\Rightarrow i_L = 0$$

$$R_o = \infty$$

$$(or) Y_o = h_{oe} - \frac{h_f b_{re}}{h_{ie} + R_s}$$

$$Y_o = 0$$

$$R_o = 1/Y_o = \infty$$

① CE amplifier is drawn by a voltage source of $R_s = 8\Omega$
 $R_L = 1000\Omega$, $h_{ie} = 1k\Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 50$, $h_{oe} = 25 \times 10^6 \mu A$

Compute $-A_i$, A_v & R_i . Exact
 Approximate
 $A_i = -50$
 $R_i = h_i = 1k\Omega$
 $A_v = -50$
 $R_o = \infty$

$$A_i = -48.78$$

$$A_v = -49.26$$

$$R_i = 990.24\Omega$$


$$R_o = 51.28k\Omega$$

$h_{re} \cdot R_L \ll 0.1$
 approx. Approximate

$$25 \times 10^6 \times 10$$

$$\approx 25 \times 10^3$$

$$0.025$$

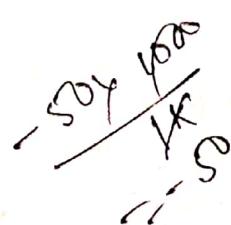

② CE amplifier is driven by voltage source of $R_s = 600\Omega$, $R_L = 1900\Omega$,
 $h_{ie} = 1100\Omega$, $h_{re} = 2.4 \times 10^4$, $h_{fe} = 52$, $h_{oe} = 90 \times 10^6 \mu\text{mhos}$.

Sol^F $-A_i = -50.7815$


$R_i = 1085.375\Omega$

$-A_v = -56.14$

$R_o = 78.996 \text{ k}\Omega$

$R_L || R_o = R_{OT} = 1182.04\Omega$

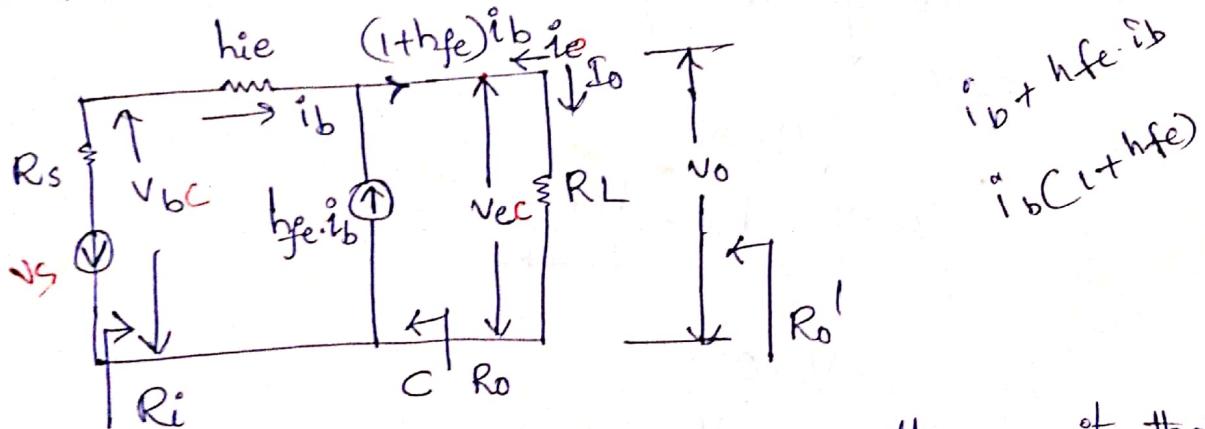Simplified Model of Common Collector Circuit



The $h_{fe} \cdot i_B$ current direction is now exactly opposite that of CE model. Since the current $h_{fe} \cdot i_B$ is always pointing towards emitter. In this, C is grounded. Input is applied between base & collector, load is connected between emitter & collector.

Simplified hybrid model of CC amplifier is shown in the figure

$$A_V = \frac{V_O}{V_B} = \frac{R_L I_O}{V_B} = \frac{R_L (1+h_{fe}) i_B}{V_B}$$

$$A_V = \frac{R_L (1+h_{fe}) i_B}{h_{ie} i_B + (1+h_{fe}) i_B \cdot R_L} = \frac{(1+h_{fe}) R_L}{h_{ie} + (1+h_{fe}) R_L} = \frac{h_{ie} + (1+h_{fe}) R_L - h_{ie}}{h_{ie} + (1+h_{fe}) R_L} = \frac{1 - h_{ie}}{1 + h_{ie}}$$

Current gain - A_i

$$-A_i = \frac{I_o}{I_b} = -\frac{i_e}{i_b} = \frac{(1+h_{fe})i_b}{i_b} = 1+h_{fe}$$

$$\boxed{-A_i = h_{fe}}$$

Input resistance R_i

$$R_i = \frac{V_b}{I_b} = \frac{h_{ie}I_b + (1+h_{fe})i_b R_L}{I_b}$$

$$\boxed{R_i = h_{ie} + (1+h_{fe})R_L}$$

$$\boxed{R_i = h_{ie} + A_i R_L}$$

$$I_o = (1+h_{fe})i_b$$

Voltage gain A_v


$$-A_v = \frac{V_o}{V_b} = \frac{R_L I_o}{V_b} = \frac{R_L (1+h_{fe}) i_b}{V_b}$$

$$R_i = \frac{V_b}{i_b}$$

$$= \frac{R_L}{R_i} (1+h_{fe})$$

(or)

$$\boxed{A_v = 1 - \frac{h_{ie}}{R_i}}$$

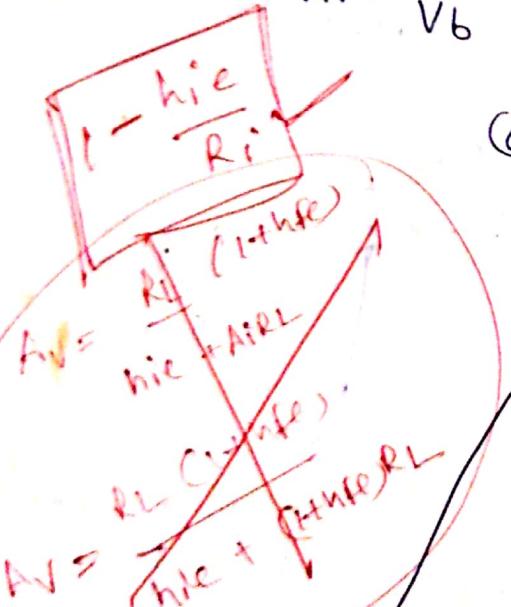

Output resistance (R_o)

$$R_o = \frac{V_o}{I_e}$$

$$R_o = \frac{V_o}{2\alpha} = \frac{V_o}{-i_e}$$

Apply KVL

$$V_s - i_b R_s - i_b h_{ie} - V_o = 0$$

To obtain R_o , we have to make $V_s \geq 0$

$$\frac{V_B}{V_S} = \frac{R_s + h_{ie}}{h_{fe}(1+h_{fe})}$$

$$V_S = 0$$

$$V_O = -i_B R_S - i_B h_{ie}$$

$$V_O = -i_B (R_s + h_{ie})$$

$$i_E = -(1+h_{fe}) i_B$$

$$R_o = \frac{R_s + h_{ie}}{1+h_{fe}}$$

$$R'_o = R_{OT} = R_o \parallel e^l R_L$$


$$R_o = \frac{V_O}{-i_E} = \frac{V_O}{(1+h_{fe}) i_B}$$

27/01/15

Analysis of CB amplifier using the approximate models

In the case of CB, the input is applied between emitter and base and load is connected between collector and base. The figure shown below is a simplified CB amplifier.

Simplified CB amplifier

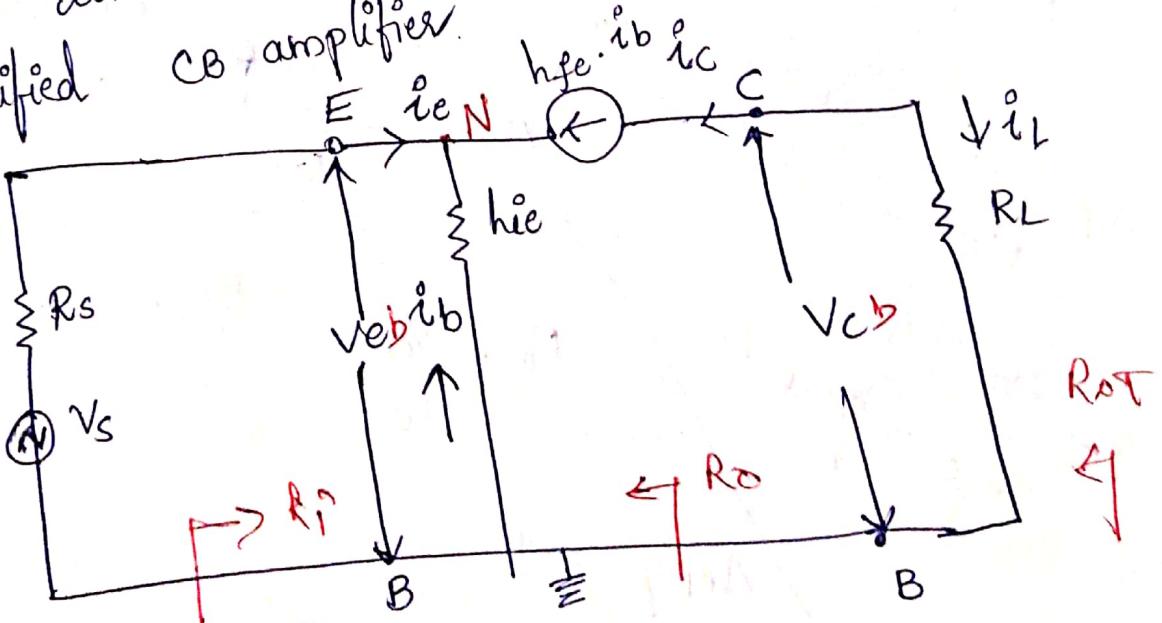

Current gain $A_i = \frac{i_L}{i_e} = \frac{-i_C}{i_e} = \frac{-h_{fe} \cdot i_b}{i_e}$

Apply KCL at point 'N';

$$i_e + i_b - h_{fe} \cdot i_b = 0$$

$$\Rightarrow i_e = -(1+h_{fe}) i_b$$

$$\therefore A_i = \frac{h_{fe} \cdot i_b}{-(1+h_{fe}) i_b}$$

$$A_i^o = \frac{h_{fe}}{1+h_{fe}}$$

$$i_e + i_b + h_{fe} i_b = 0 \\ i_e = -\epsilon^{(1+h_{fe}) i_b}$$

Input Resistance $R_i^o = \frac{V_e}{i_e}$

$$V_e = -i_b \cdot h_{ie}$$

$$\therefore i_e = -(1+h_{fe}) i_b$$

$$R_i^o = \frac{h_{ie}}{1+h_{fe}}$$

Voltage Gain $A_v = \frac{V_c}{V_e}$

$$V_c = i_L \cdot R_L = -i_C \times r_L = -h_{fe} \cdot i_b \cdot r_L$$

$$V_e = -i_b \cdot h_{ie}$$

$$A_v = \frac{h_{fe} R_L}{h_{ie}}$$

To obtain the value of R_o , the output must be open circuited.

$$\therefore i_C = 0$$

$$R_o = \frac{V_C}{i_C} = \frac{V_C}{0} = \infty$$

$$R_o \text{ (terminal resistance)} = R_o \parallel R_L = \infty \parallel R_L = R_L$$

Conversion of h-parameters of different configurations

Conversion		formulae
From	To	
CE	CB	$h_{ib}^o = \frac{h_{ie}}{1+h_{fe}}, h_{fb}^o = -\frac{h_{fe}}{1+h_{fe}}$ $h_{rb}^o = \frac{h_{ie} \cdot h_{oe}}{1+h_{fe}} - h_{re}, h_{ob}^o = \frac{h_{oe}}{1+h_{fe}}$
CE	CC	$h_{ic}^o = h_{ie}, h_{fc}^o = -1/(1+h_{fe})$ $h_{rc}^o = 1, h_{oc}^o = h_{oe}$
CB	CE	$h_{ie}^o = \frac{h_{ib}^o}{1+h_{fb}^o}, h_{fe}^o = -\frac{h_{fb}^o}{1+h_{fb}^o}$ $h_{re}^o = \frac{h_{ib}^o h_{ob}^o}{1+h_{fb}^o} - h_{rb}^o, h_{oe}^o = \frac{h_{ob}^o}{1+h_{fb}^o}$

→ voltage source of internal resistance $r_s = 900\Omega$, drives a cc amplifier using load resistance $R_L = 2000\Omega$, the CE h-parameters are $h_{ie} = 1200\Omega$, $h_{oe} = 2 \times 10^{-4}$, $h_{fe} = 60$ & $h_{oc} = 25\text{mA/V}$. compute the current gain A_i , A_v , R_i & R_o using approximate analysis and exact analysis.

Ques the conversion formulae for $CE \rightarrow cc$ are

$$h_{ic} = h_{ie} = 1200\Omega$$

$$h_{fc} = -(1+h_{fe}) = -61$$

$$h_{rc} = 1$$

$$h_{oc} = h_{oe} = 25\text{mA/V}$$

exact analysis

$$A_i = \frac{-h_{fc}}{1+h_{oc} \cdot R_L} = 58.095$$

$$A_v = A_i \cdot \frac{R_L}{R_i} = 0.99897$$

$$R_o = \frac{1}{Y_0} = h_{oe} - \frac{h_{oc} h_{fe}}{R_s h_{ie}} = \cancel{34.39\Omega} \quad 0.0290\Omega$$

$$R_i = h_{ic} + h_{rc} \cdot A_i \cdot R_L$$

$$= 1200 + (1)(58.095)(2000)$$

$$= 117.39\text{K}\Omega$$

Approximate analysis

$$A_i = -h_f = 61 \checkmark$$

$$A_v = \frac{-h_f R_L}{h_i} = 101.67$$

$$R_i = \frac{1200\Omega}{h_{ie} + (1+h_{fe}) R_L}$$

$$= 123.2\text{K}\Omega \checkmark$$

$$A_v = 1 - \frac{h_{ic}}{R_i} = 0.9903$$

$$R_o = \frac{R_s h_{ie}}{1+h_{fe}} = 34.43\Omega \checkmark$$

Consider - the h-parameter values of CE configuration.
 $h_{ie} = 1\text{ k}\Omega$, $h_{fe} = 100$, $h_{re} = 10^{-4}$, $h_{oe} = 50 \times 10^{-6}\text{ V}$ correct
(a) these parameters for CC configuration (b) Derive the expressions for A_v , A_i , R_o , R_i^o for CC configuration by using the above parameters if $R_L = 5\text{ k}\Omega$. and

$$R_S = 100\text{ k}\Omega$$

$$h_{ic} = h_{ie} = 1\text{ k}\Omega$$

$$h_{fc} = -(1 + h_{fe}) = -101$$

Exact

$$A_{if} = 80.8$$

$$A_v = 0.997$$

$$R_i = h_{ic} + h_{re} \cdot A_i \cdot R_L \\ = 40500\Omega$$

$$R_o = 952.38\Omega$$

$$h_{rc} = h_{re} = 1$$

$$h_{oc} = h_{oe} = 50 \times 10^{-6}\text{ V}$$

Approximate

$$A_i^o = 101$$

$$A_v = 0.998$$

$$R_i^o = 506\text{ k}\Omega$$

$$R_o = 1000\Omega$$

Draw the circuit diagram of CC amplifier
Draw the equivalent circuit using approximate model & derive the expressions for A_v , $A_i^o R_i^o$

Ques. It is given that, the source resistance $R_S = 600\Omega$ & the load resistance $R_L = 8\text{ k}\Omega$. The CE h parameters are $h_{ie} = 1100\Omega$, $h_{re} = 2.6 \times 10^{-4}$, $h_{fe} = 54$


$\text{V}_{\text{in}} = 26 \text{ mV}$ compute A_i , A_v , R_i , R_o & R_{ot} using the approximate analysis.

28/01/15


$A_i = 55$
 $A_v = 0.9901$
 $R_i = 111.1 \text{ k}\Omega$
 $R_o = 29.9$
 $R_{\text{ot}} = 2 \text{ k}\Omega$

28/01/15

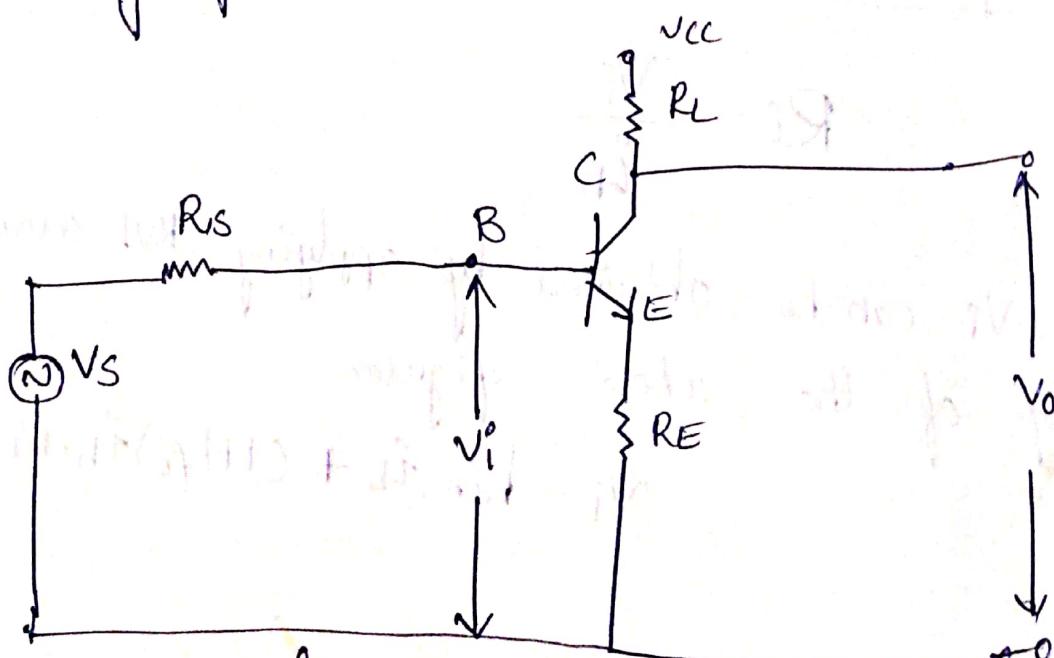Analysis of CE amplifier using Emitter Resistor (R_E) &
An effective way of providing voltage gain stabilization in a CE amplifier is to add an Emitter resistor R_E in the circuit as shown below. By using this resistor, (R_E) the circuit stability can be improved however the use of R_E results substantial reduction of voltage gain.



fig(a) CE amplifier with R_E

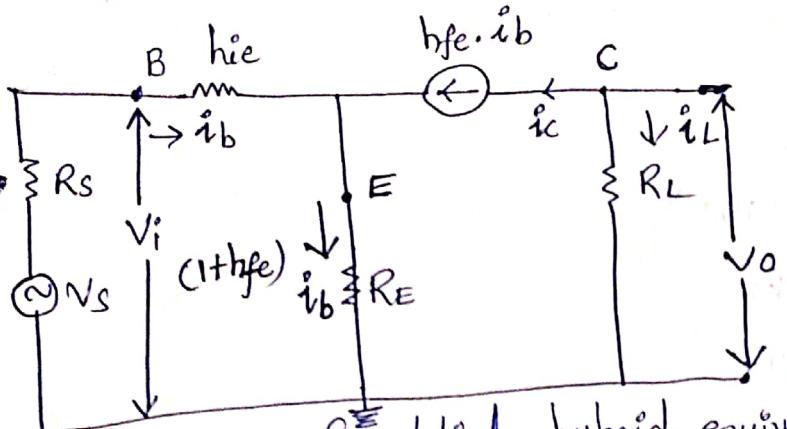

fig(b): Simplified hybrid equivalent circuit of fig(a).

(a) Current Gain (\$A_i\$)

$$A_i = \frac{i_L}{i_b} = \frac{-i_c}{i_b} = \frac{-h_{fe} \cdot i_b}{i_b}$$

$$\boxed{A_i = -h_{fe}}$$

NOTE: The current gain remains unchanged inspite of putting a resistor in emitter circuit.

(b) Input Resistance (\$R_i\$)

$$R_i = \frac{V_i}{i_b}$$

\$V_i\$ can be obtained by applying KVL around LHS loop of the above figure.

$$V_i = h_{ie} \cdot i_b + (1+h_{fe}) i_b \cdot R_E$$

$$R_i = h_{ie} + (1+h_{fe})R_E$$

NOTE & The input resistance of CE amplifier is only h_{ie} , thus input resistance is greatly increased due to the use of R_E .

(c) Voltage Gain (A_v)

we know that $A_v = \frac{-A_i \cdot R_L}{R_i}$

Substitute for A_i & R_i

$$A_v = \frac{-h_{fe} \cdot R_L}{h_{ie} + (1+h_{fe})R_E}$$

The $-A_v$ for a CE amplifier is $\frac{-h_{fe} \cdot R_L}{h_{ie} + (1+h_{fe})R_E}$ only.

\therefore It indicates that $-A_v$ is drastically reduced since R_i is increased greatly.

if $(1+h_{fe})R_E \gg h_{ie}$, then $A_v = \frac{-h_{fe} \cdot R_L}{(1+h_{fe})R_E}$

$\therefore h_{fe} \gg 1 ; \therefore A_v = \frac{-h_{fe} \cdot R_L}{h_{fe} \cdot R_E} = -\frac{R_L}{R_E}$

thus A_v is independent of all transistor parameters and so on etc.

and is governed by R_L and R_E , if the above conditions met.


(d) Output Resistance (R_o)

$$R_o = \infty$$


- Analysis of CE amplifier with R_E bypassed by a capacitor C_E &

We know that the use of resistor ~~and~~^{in the} emitter has major disadvantage ie; drastic reduction in voltage gain. However, if we connect a capacitor C_E in parallel to the resistor R_E as shown in the figure, the voltage gain does not get reduced.

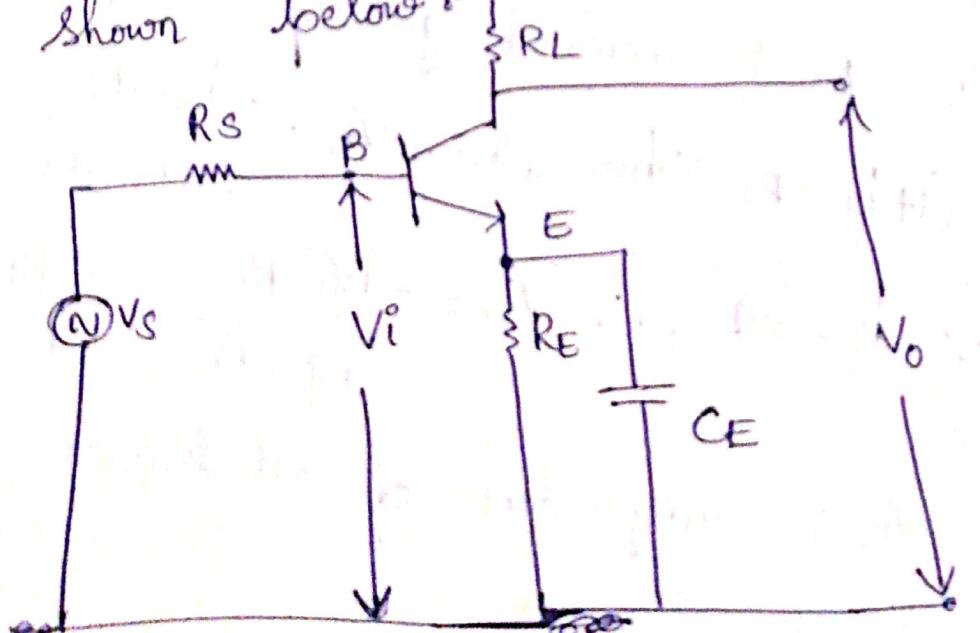The CE amplifier with unbypassed R_E is shown below:



fig(a) CE amplifier with bypass R_E

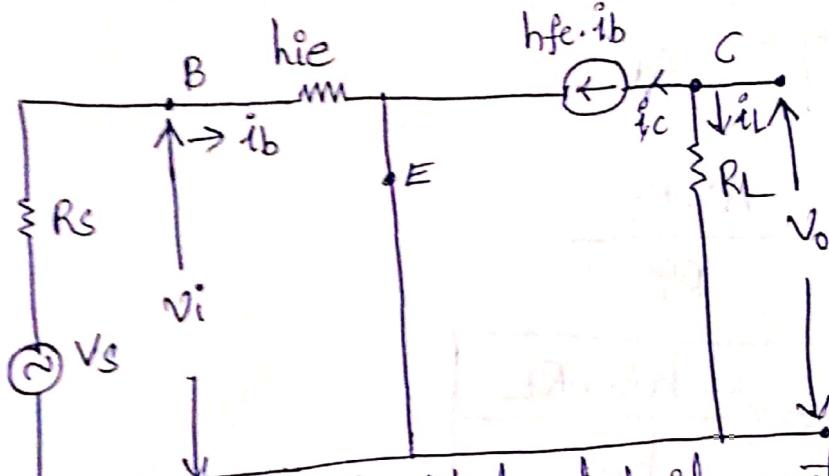

fig(b) + Simplified hybrid equation ckt of fig(a).

(a) Current Gain A_i^o

$$-A_i^o = \frac{i_L}{i_b} = \frac{-i_c}{i_b} = -\frac{h_{fe} \cdot i_b}{i_b}$$

$$\boxed{-A_i^o = -h_{fe}}$$

(b) Input Resistance (R_i^o)

$$R_i^o = \frac{V_i}{i_b}$$

$$V_i = h_{ie} \cdot i_b$$

$$R_i^o = \frac{h_{ie} \cdot i_b}{i_b}$$

$$\boxed{R_i^o = h_{ie}}$$

(c) Voltage Gain A_v

$$A_v = \frac{-A_i \cdot R_L}{R_i}$$

$$A_v = \frac{-h_{fe} \cdot R_L}{h_{ie}}$$


(d) Output Resistance R_o

$$R_o = \infty$$

NOTE :- All the four characteristics are same as that of an ordinary CE amplifier.

(*) Draw the ckt diagram of CB amplifier, draw its equivalent circuit using approximate h-model. Derive the expressions for A_i , A_v , R_i , & R_o . It is given that $R_S = 900\Omega$, $R_L = 2k\Omega$. CE h parameters are $h_{ie} = 12000$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 60$, $h_{oe} = 10\mu V$. Compute A_i , A_v , R_i & R_o and R_{ot} using approximate model.

Sol

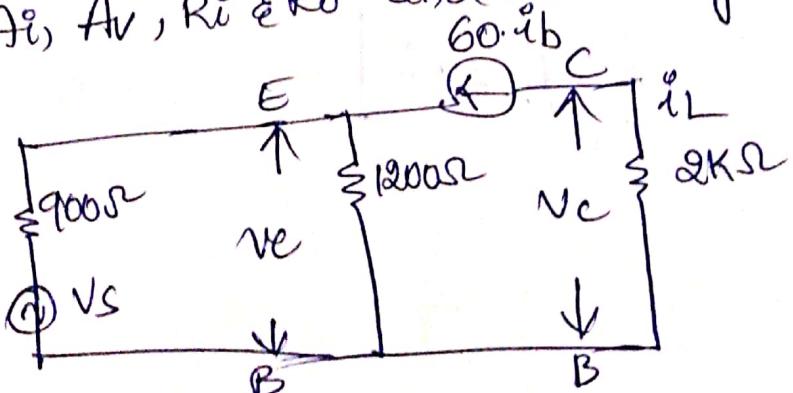

$$-A_i = \frac{60}{61} = 0.983$$

$$-A_i^o =$$

$$-A_v = R_i^o = \frac{1200}{61} = 19.67$$

$$-A_v = \frac{60 \times 2k\Omega}{1200} = 100$$

$$R_o = \infty$$

$$R_{ot} = 2k\Omega$$

A CE amplifier uses load resistor $R_L = 2k\Omega$ in the collector Ckt and is given by Voltage source

\checkmark ~~Given~~ $R_s = 1k\Omega$, $h_{ie} = 1300\Omega$, $h_{re} = 2 \times 10^{-4}$, $h_{fe} = 55$ & $h_{oe} = 22.4k\Omega$. Compute A_i , A_v , R_i , R_o & R_{ot} for the following values of R_E (1) 2000Ω (2) 4000Ω (3) 10000Ω by approximate analysis.

Soln (i) 2000Ω

$$-A_i = -55$$

(ii) 4000Ω

$$-A_i = -55$$

(iii) 10000Ω

$$-A_i = -55$$

$$R_i^o = 11.5k\Omega \text{ or } 12.1k\Omega$$

$$-A_v = 9.56$$

$$-A_v = 4.64$$

$$R_o = \infty$$

$$R_i^o = 23.7k\Omega$$

$$R_o = \infty$$

$$R_i^o = 57.3k\Omega$$

$$-A_v = 1.919 \approx -1.92$$

$$R_o = \infty$$

approximate model is
permissible

NOTE: $h_{oe}(R_E + R_C) \ll 0.1$,

29/01/15

Miller's Theorem

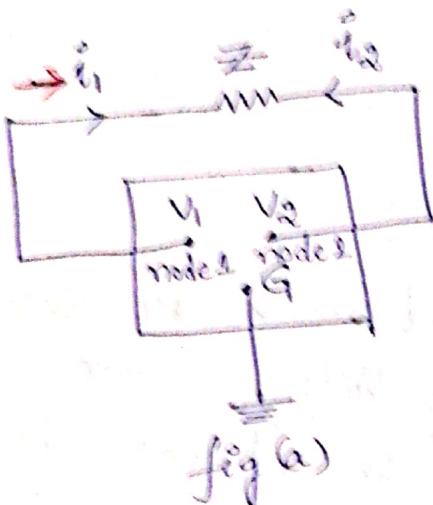


fig (a)

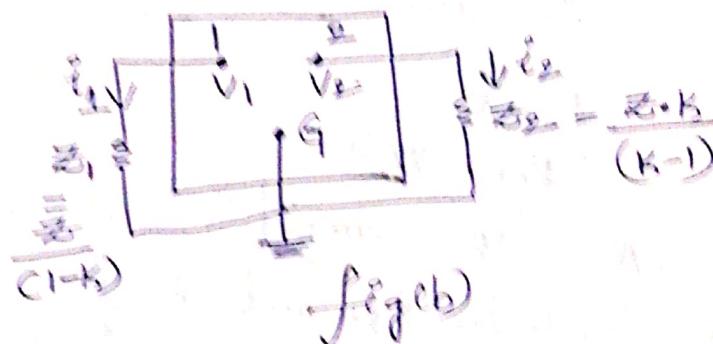


fig (b)

Miller's theorem is useful in converting any circuit having configuration in figure (a) to another configuration shown in fig (b). The impedance Z is connected between two nodes namely node 1 and node 2 can be replaced by two separate impedances.

$$Z_1 = \frac{Z}{1-K} \quad \text{and} \quad Z_2 = \frac{ZK}{(K-1)}$$

where Z_1 is connected between node 1 and ground and Z_2 is connected between node 2 and ground as shown in fig (b).

Proof: Let the voltages of nodes 1 and 2 be V_1 & V_2 respectively. The node G is grounded.

Note: The remaining part of the circuit is represented by a box which remains unchanged, even after the application of miller's theorem on the impedance Z .

$$\text{Let } \frac{V_2}{V_1} = K$$

$$\text{From fig(a), } i_1 = \frac{V_1 - V_2}{Z},$$

$$K = \frac{V_2}{V_1}$$

$$V_2 = KV_1$$

$$i_1 = \frac{V_1 - KV_1}{Z} = \frac{V_1(1-K)}{Z}$$

$$i_1 = \frac{V_1}{Z(1-K)} \quad \text{--- (1)}$$

From fig(b) current through Z_1

$$i_1 = \frac{V_1}{Z_1} \quad \text{--- (2)}$$

Equating equations (1) & (2)

$$Z_1 = \frac{Z}{1-K}$$

From fig @

$$i_2 = \frac{V_2 - V_1}{Z}$$

$$i_2 = \frac{V_2 - V_2/K}{Z} = \frac{V_2(1-1/K)}{Z}$$

$$i_2 = \frac{V_2}{Z/(K-1)} \quad \text{--- (1)}$$

From fig(b)

$$i_2 = \frac{V_2}{Z_2} \quad \text{--- (2)}$$

$$\frac{V_2}{Z_2} = \frac{V_2}{\frac{Z}{K}(K-1)}$$

$$Z_2 = \frac{Z \cdot K}{(K-1)}$$

It must be emphasized that this theorem is useful in making calculations only if it is possible to find the value of 'K' by some independent means.


Dual of Miller's theorem


The dual of miller's theorem helps us to transform any impedance 'z' which is common to both input and output loop into two separate impedances Z_1 & Z_2 .

$$Z_1 = z (1 - A_i)$$

$$Z_2 = \frac{(A_i - 1)}{-A_i} z$$

Figure (a) shows the impedance 'z' through which the input current i_1 and output current i_2 flows.

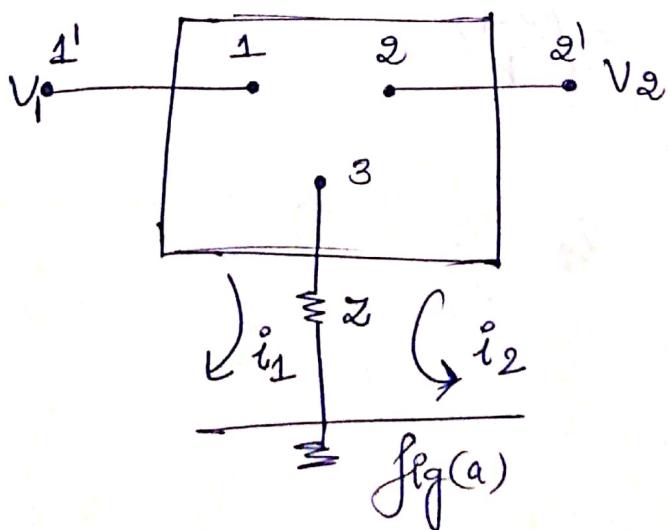

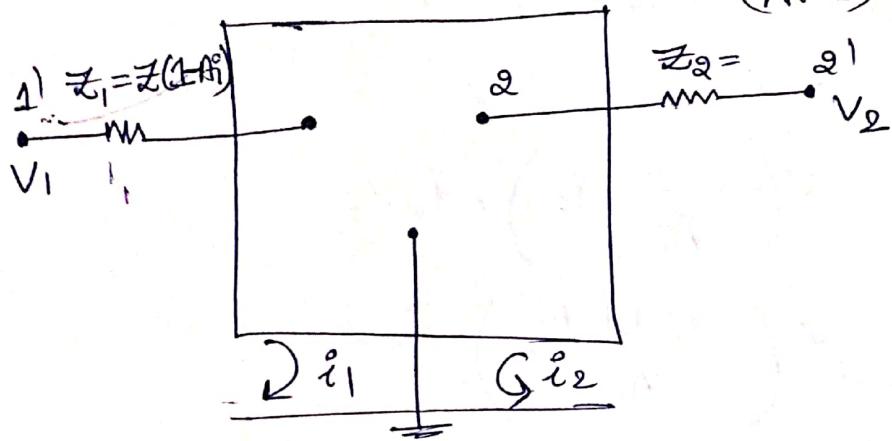

After transformation by the dual of miller's theorem, this Z' is removed and replaced by two separate impedances Z_1 in the input side loop and Z_2 in the output side loop. The currents i_1 & i_2 remains unchanged as shown in the figure below.

$$\text{from fig(a)} \quad A_i = \frac{i_2}{i_1}$$

$$\text{from fig(b)} \quad V_1 = i_1 Z_1 \quad \rightarrow \textcircled{1}$$

$$\text{from fig(a)} \quad V_1 = Z (i_1 + i_2) \quad \rightarrow \textcircled{2}$$

equating \textcircled{1} \& \textcircled{2}

$$i_1 Z_1 = Z (i_1 + i_2)$$

$$= Z (i_1 - A_i i_1)$$

$$Z_1 = \frac{i_1}{Z} (1 - A_i)$$

$$Z_1 = Z (1 - A_i)$$

Similarly for mesh 2

$$\text{from fig(a)} \quad V_2 = Z_2 (i_1 + i_2) \quad \rightarrow \textcircled{3}$$

$$\text{from fig(b)} \quad V_2 = i_2 Z_2 \quad \rightarrow \textcircled{4}$$

~~Equating equations ① & ②~~

$$Z(i_1 + i_2) = i_2 Z_2$$

$$Z\left(-\frac{i_2}{A_i} + i_2\right) = i_2 Z_2$$

$$Z\left(\frac{-i_2 + i_2 A_i}{A_i}\right) = i_2 Z_2$$


$$Z_2 = \frac{Z i_2 (A_i - 1)}{i_2 - A_i}$$

$$\boxed{Z_2 = \frac{Z (A_i - 1)}{A_i}}$$

NOTE: The theorem is used for analysis of circuits such as CE configuration with unbypassed R_E where R_E is common for both input and output loops.

30/01/15

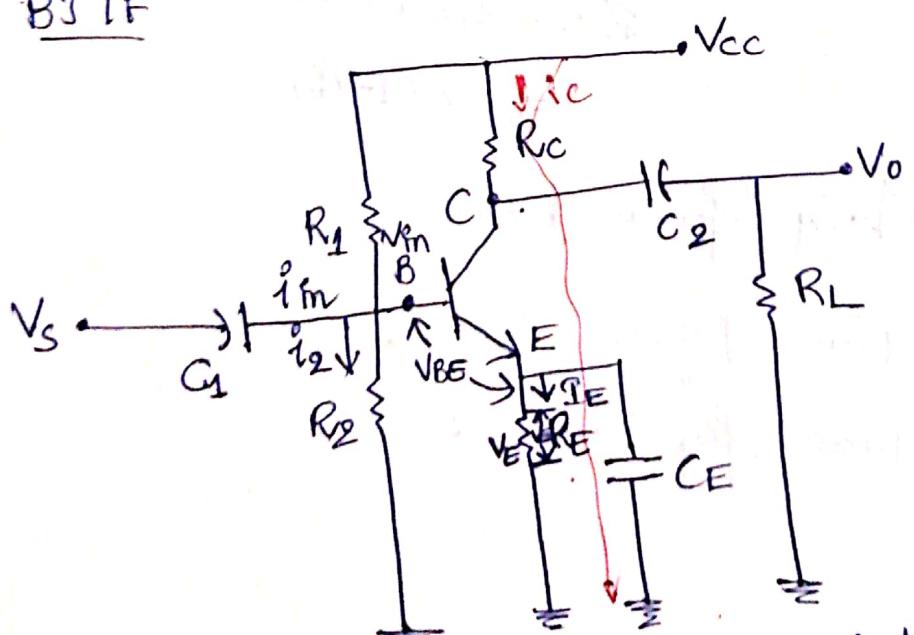Design of single stage RC coupled Amplifier
using BJT



fig(a). Single stage RC coupled BJT amplifier

The circuit diagram of single stage RC coupled amplifier is shown in figure. The design of resistor values involves application of ohms law after selecting suitable voltage and current values throughout the circuit. The design of capacitor values are based on the lower cut off frequency of the circuit. (f_L).

The biasing is provided by the resistors R_1 & R_2 . R_1, R_2 acts as a potential divider giving a fixed voltage.

Designing of R_C & R_E

The voltage gain of the CE amplifier is given by

$$-A_v = \frac{-h_{fe} \cdot R_L}{h_{ie}} = \frac{-h_{fe} \cdot (R_C \parallel R_L)}{h_{ie}}$$

$-A_v$ is directly proportional to $R_C \parallel R_L$, the design of large $-A_v$ requires selection of the largest possible collector resistance. The R_C can be obtained by applying KVL around the collector to emitter circuit.

$$V_{CE} = i_C R_C + V_{CE} + V_E$$

$$\Rightarrow R_{cE} = \frac{V_{cc} - V_{CE} - V_E}{i_C}$$

$$V_E = I_E R_E$$

To get the large value of R_{cE} , let us assume $V_{CE} = \frac{V_{cc}}{2}$ & $V_E = \frac{V_{cc}}{10}$

for good bias stability, $V_E \gg V_{BE}$
 $(V_E = V_B - V_{BE})$

Hence i_E & i_C remains stable at

$$I_E = I_C = \frac{V_E}{R_E}$$

Analysis of voltage divider bias circuit

By applying Ohm's law, the input resistance

$$R_{in} (\text{base}) = \frac{V_{in}}{i_{in}}$$

$$V_{in} = V_{BE} + V_E$$

$$V_{in} = V_{BE} + I_E R_E$$

$\because V_{BE}$ is very much less than $N_E @ 0 I_E R_E$

$$V_{in} = I_E R_E$$

$$(I_E = I_C)$$

$$V_{in} = \beta I_B R_E$$

$$I_C = \beta I_B$$

$$i_{in} = I_B$$

$$\therefore R_{in(base)} = \frac{\beta \beta RE}{R_B} = \beta RE$$

the total resistance from base to ground is

$$R_2 \parallel \beta RE$$

The voltage divider is formed by

R_1 and Resistance from base to ground

ie,

$$R_2 \parallel \beta RE$$

$$V_B = V_{cc} \times \frac{(R_2 \parallel \beta RE)}{R_1 + (R_2 \parallel \beta RE)}$$

for good bias stability;

$$\beta RE \gg R_2$$

(atleast 10 times)

neglect βRE

$$\therefore V_B = V_{cc} \times \frac{R_2}{R_1 + R_2}$$

Design to Bias Resistor:

The voltage divider current i_2 is selected as $\frac{i_c}{10}$ (for good bias stability).

Hence, the bias resistors are

Calculated as,

$$R_2 = \frac{V_{BE}}{I_E}$$

$$\therefore R_1 = \frac{V_{CC} - V_B}{I_E}$$

where $V_B = V_E + V_{BE}$ (or) $V_B = \frac{V_{CC} \times R_2}{R_1 + R_2}$

Design of bypass and coupling capacitors
the reactance offered by bypass capacitor

CE is $X_{CE} = \frac{1}{2\pi f C_E}$

$$\therefore C_E = \frac{1}{2\pi f X_{CE}}$$

The voltage gain for CE circuit with unbypassed R_E resistance is given by

$$-A_V = \frac{-h_{FE} \cdot R_L}{h_{IE} + R_E (1+h_{FE})}$$

But $R_L = R_E \parallel R_L$

and including the bypass Capacitor reactance
(in parallel with R_E)

$$A_v = \frac{-h_{fe} \cdot (R_C || R_L)}{h_{ie} + R_E (1+h_{fe}) (R_E || X_{CE})}$$

X_{CE} should be
fixed & one tenth
of R_E

$R_E \gg X_{CE}$ ($\because R_E$ neglecting)

Hence $A_v = \frac{-h_{fe} \cdot (R_C || R_L)}{h_{ie}^2 + [(1+h_{fe}) \times X_{CE}]^2}$

$$|A_v| = \sqrt{h_{fe}} \approx h_{fe}$$

Let $h_{ie} = (1+h_{fe}) \times X_{CE}$

$$|A_v| = \frac{-h_{fe} (R_C || R_L)}{h_{ie} \sqrt{1^2 + 1^2}}$$

$$A_v = \frac{-h_{fe} (R_C || R_L)}{h_{ie} \sqrt{2}} = \frac{-A_{vm}}{\sqrt{2}}$$

where $A_{vm} = \frac{-h_{fe} (R_C || R_L)}{h_{ie}}$

A_{vm} is the mid frequency gain,

$$h_{ie} = (1+h_{fe}) X_{CE}$$

hence $X_{CE} = \frac{h_{ie}}{1+h_{fe}} = h_{ib}$

Conventional
formal

$$\therefore C_E = \frac{1}{2\pi f_L X_{CE}}$$

$$\therefore C_E = \frac{1}{2\pi f_L \cdot h_{ib}}$$

The Coupling Capacitors C_1 & C_2 are obtained by following equations:

$$C_1 = \frac{1}{2\pi f_L \cdot X_{C_1}} \quad \&$$

$$X_{C_1} = \frac{R_i}{10} \quad \left[\text{for good stability of bias} \right]$$

[the reactance of each coupling capacitor is selected to be approximately equal to $\frac{1}{10}$ of the impedance]

$$R_i = R_{in} \parallel R_{out} \parallel h_{ie}$$


$$C_2 = \frac{1}{2\pi f_L \cdot X_{C_2}}$$

$$X_{C_2} = \frac{R_o}{10}$$

$$R_o = R_C \parallel R_L$$

01/02/15

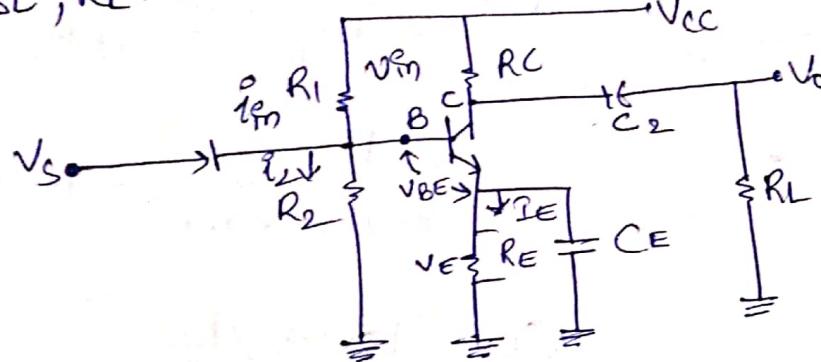Design a single stage RC coupled BJT amplifier circuit shown in figure below. Assume that $V_{CC} = 10V$, $I_C = 4mA$, $\beta = 100$, $h_{ie} = 1k\Omega$, $R_L = 100k\Omega$ & $f_L = 100Hz$, $\beta = 100$



$$R_C = \frac{10 - 5 - 1}{4mA} = \frac{4V}{4mA} = 1k\Omega \quad \text{---}$$

$$R_E = \frac{V_E}{I_C} = \frac{1V}{4mA} = 0.25k\Omega \quad \text{---}$$

$$V_E = \frac{V_{CC}}{10} = \frac{10}{10} = 1V \quad \text{---}$$

$$V_B = 0.7 + (V_{BE} + V_E) = 1.7V \quad \text{---}$$

$$V_B = V_{CC} \times \frac{R_2}{R_1+R_2} \Rightarrow 10 \times \frac{R_2}{R_1+R_2} = 1.7$$

$$R_2 = 0.17(R_1+R_2)$$

$$5.88R_2 = R_1+R_2 \quad \Rightarrow \quad \frac{R_2}{R_1+R_2} = 0.17 \quad \Rightarrow \quad R_1 = 4.12R_2 \quad \text{---}$$

$$R_1 = 4.12R_2 \quad \text{---}$$

$$\beta = 100, R_E = 250\Omega, \beta R_E = 25k\Omega \quad \text{---}$$

In order to satisfy the condition $\beta R_E \gg 10$ times atleast

$$\beta R_E \gg R_2$$

so R_2 is selected as $2k\Omega$. When $R_2 \approx 2k\Omega$

$$\text{then } R_1 = 4.12 \times 2 = 8.24k\Omega \quad \text{---}$$

$$R_1 = 4.12 \times 2 \approx 8.24k\Omega \quad \text{---}$$

$$= 8.24k\Omega \quad \text{---}$$

$$\approx 10k\Omega \quad \text{---}$$

$$\text{Calculation of } C_E = \frac{1}{2\pi f \times C_E}$$

$$X_{CE} = \frac{h_{ie}}{1 + h_{fe}} = \frac{1k\Omega}{1 + 100} = 9.9 \text{ m}\Omega$$

$$C_E = \frac{1}{2\pi f \times 100 \times 9.9} = 1.61 \times 10^{-4} \text{ F} \approx 160.8 \mu\text{F}$$


$$C_E = 160.8 \mu\text{F}$$

$$C_1 = \frac{1}{2\pi f_L \times \frac{R_i}{10}} = \frac{1}{2\pi \times 10^3 \times 10} \times (24.5) \text{ nF} = 6.47 \mu\text{F}$$

$$C_2 = \frac{1}{2\pi f_L \times \frac{R_o}{10}} = \frac{1}{2\pi \times 10^3 \times 10} \times (1.98) \text{ nF} = 16.06 \mu\text{F}$$

Analysis of cascaded RC coupled BJT amplifiers

Two stage cascaded amplifier

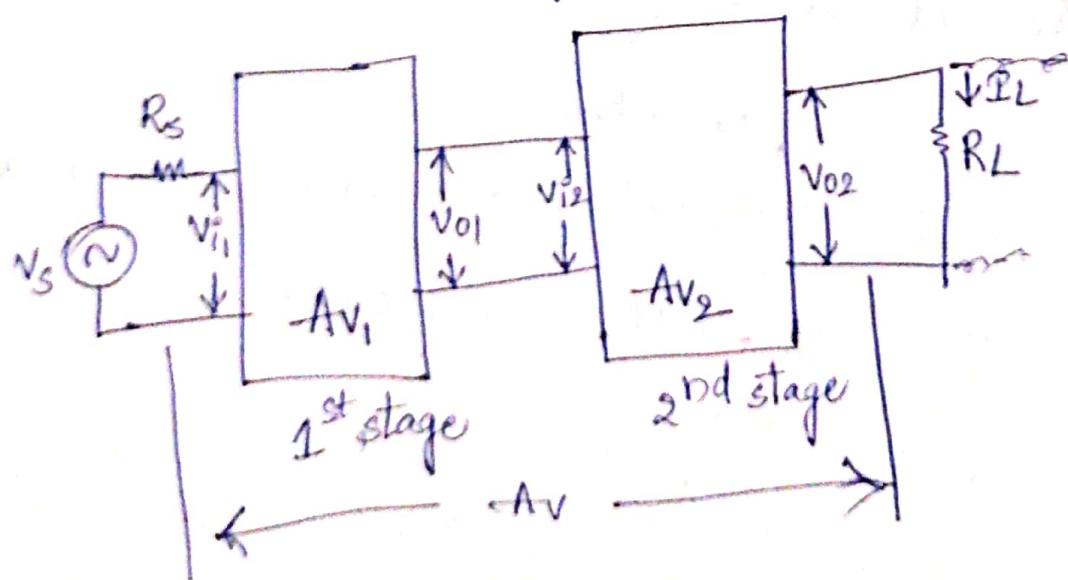


Overall voltage gain; $\rightarrow A_v \Rightarrow \frac{V_{o_2}}{V_{i_1}} = \frac{V_{o_2}}{V_{i_2}} \cdot \frac{V_{i_2}}{V_{i_1}}$

$$A_v = -A_{v_2} \cdot A_{v_1}$$

\therefore the overall voltage gain of the multistage amplifier is the product of the gains of individual stages.

n-stage cascaded amplifier

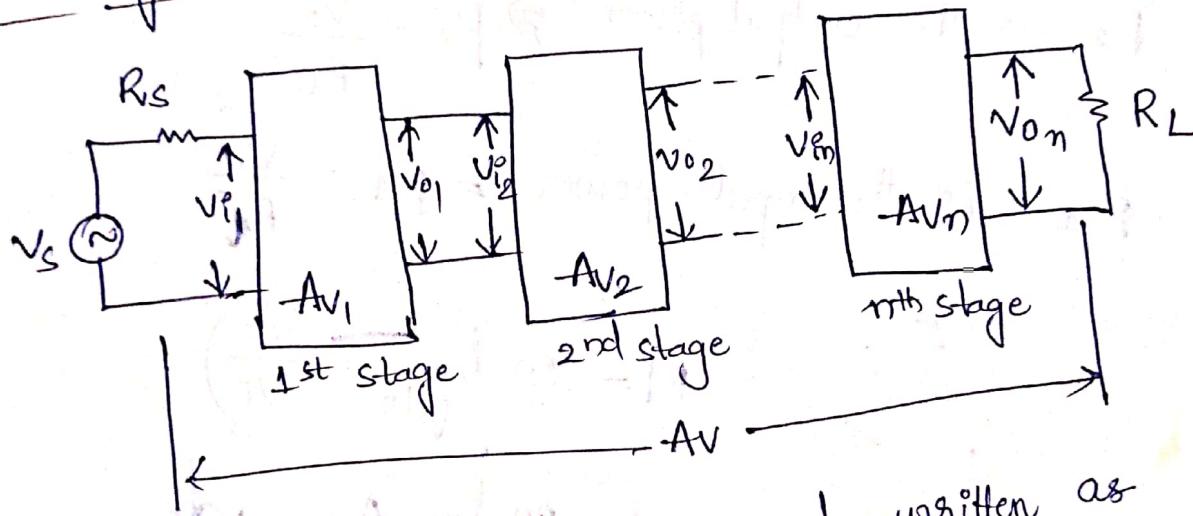

Overall voltage gain A_v can be written as

$$A_v = A_{v_1} \cdot A_{v_2} \cdots A_{v_n}$$

$$A_v = \sum_{i=1}^n A_{v_i}$$

\times the voltage gain of the k^{th} stage $\Rightarrow A_{v_k} = \frac{A_{i_k} \cdot R_{L_k}}{R_{i_k}}$

and R_{L_k} is the effective load resistance of k^{th} stage.

Gain in decibels +


It is most convenient to compare the two powers on a logarithmic scale rather than normal scale. The unit of logarithmic scale is 'dB'. The number of dB by which power P_2 exceeds the power P_1 ;

$$N = 10 \log_{10} \left(\frac{P_2}{P_1} \right)$$

$$P_2 \text{ is the output power } \Rightarrow P_2 = \frac{V_o^2}{R_o}$$

$$N = 10 \log_{10} \left(\frac{V_o^2}{V_i^2} \right)$$
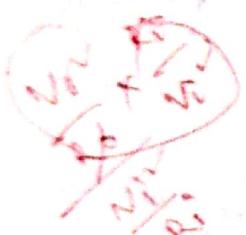
$$P_1 \text{ is the input power } = P_1 = \frac{V_i^2}{R_i}$$



$$N = 20 \log_{10} \left(\frac{V_o}{V_i} \right)$$

$$N = 20 \log_{10} A_v \rightarrow \text{dB}$$

10^{c} common
 c^{n} natural

Q2) Q2/15

$$N = G_V = 20 \log_{10} (A_v)$$

We know that $A_v = A_{v1} \cdot A_{v2} \cdot A_{v3} \dots A_{vn}$

$$G_V = 20 \log_{10} A_v$$

$$G_V = 20 \log_{10} (A_{v1} \cdot A_{v2} \cdot A_{v3} \dots A_{vn})$$

$$G_V = 20 \log_{10} A_{v1} + 20 \log_{10} A_{v2} + 20 \log_{10} A_{v3} + \dots + 20 \log_{10} A_{vn}$$

$$G_V = G_{V1} + G_{V2} + \dots + G_{Vn}$$

the overall voltage gain in dB of multistage amplifier is sum of decibel voltage gains of individual stages.


Advantages of Gain in dB

- (i) It allows to denote both very small as well as very large quantities of linear scale by considerably small figures.
- (ii) It permits to add individual gains of this stages to calculate overall gain.
(logarithmic changes multiplication to addition)

Different Coupling Schemes used in Amplifiers


Depending upon the type of coupling, the multistage amplifiers classified as

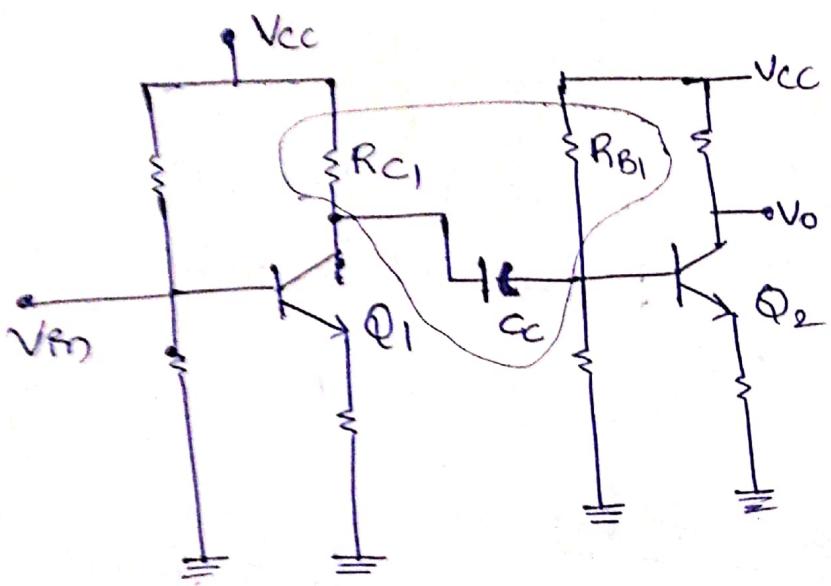- ✓ ① Resistance - Capacitance Coupling (RC coupled amplifier)
- ✓ ② Transformer coupled amplifier
- ✓ ③ Direct coupled amplifier




The signal developed across the collector resistor of each stage is coupled through capacitor into the base of the next stage.

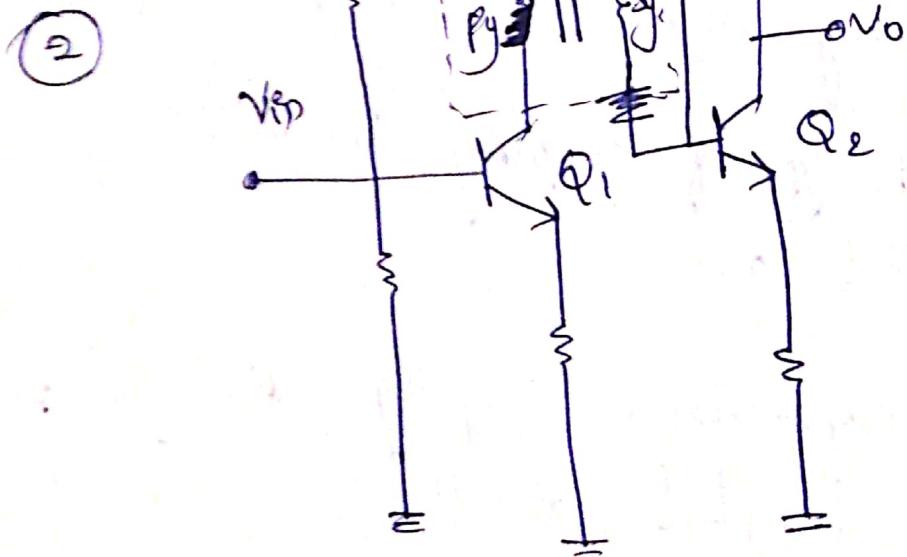The cascaded stages amplify the signals and the overall voltage gain is equal to the product of the individual stage gains.





Transformer
coupled

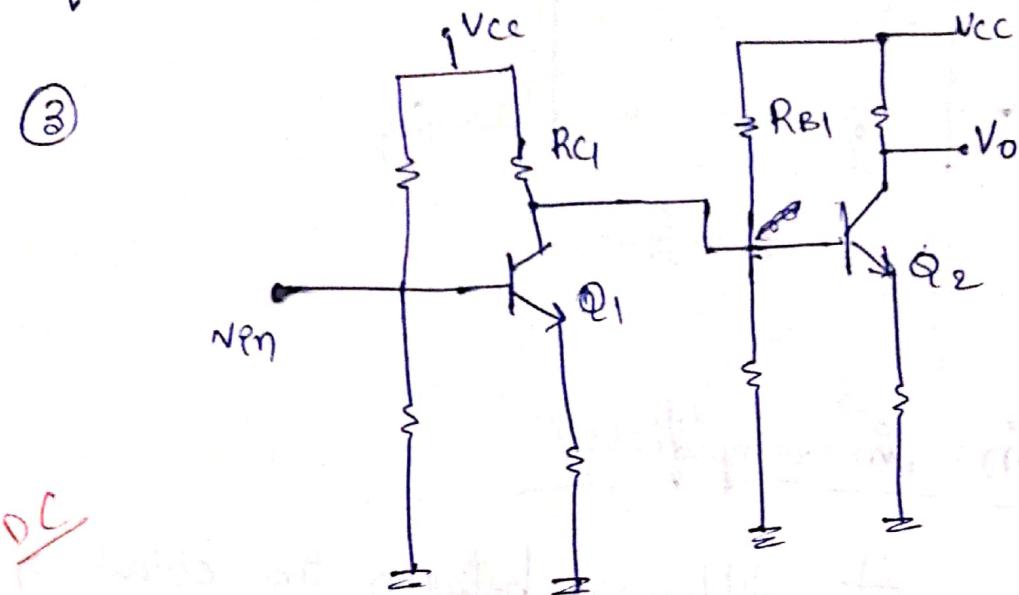In this method primary winding of a transformer acts as a collector load and the collector load conveys the ac output signal directly to the base of the next stage.



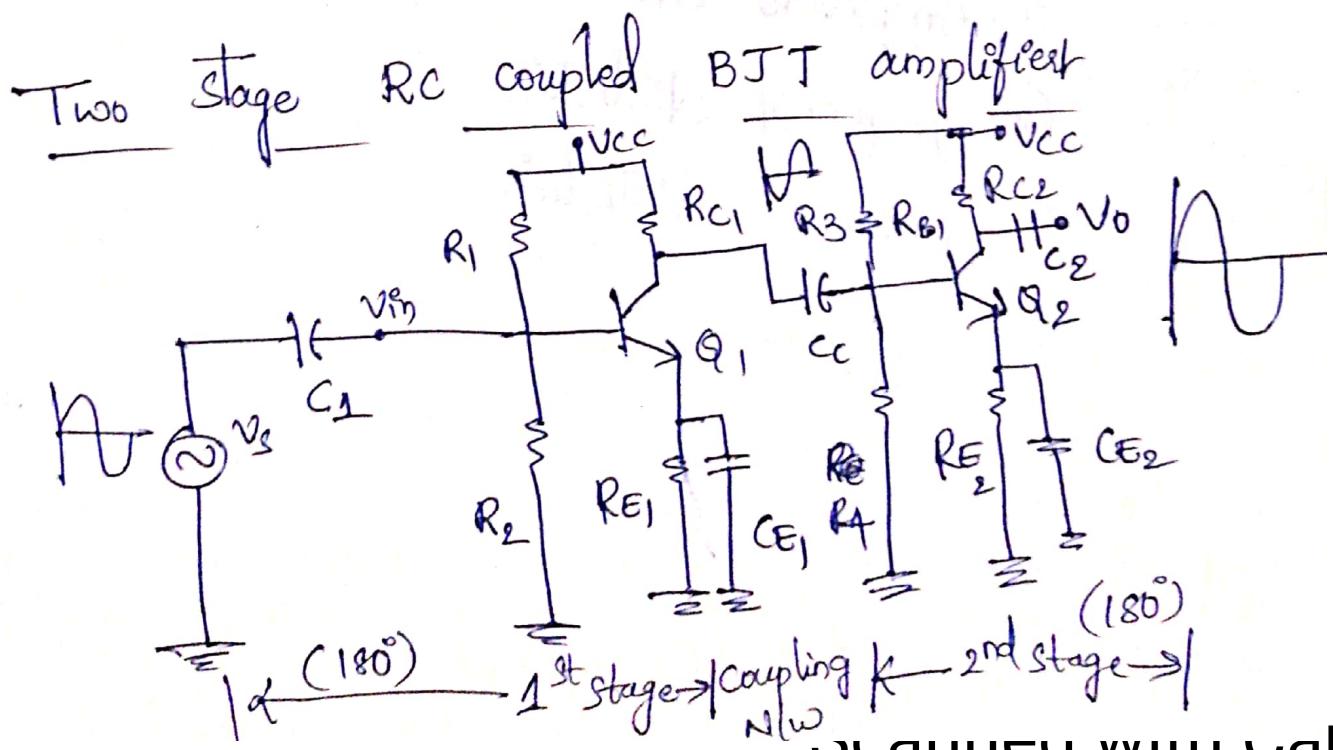In this method the a.c output signal of Stage one is fed directly to the base of the next stage. This type of coupling is used where low frequency signals are to be amplified.



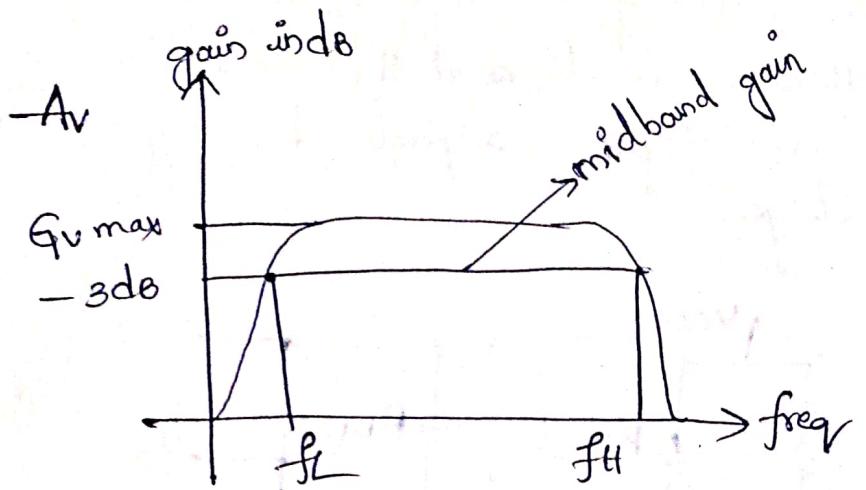

$$BW = f_2 - f_1$$

$$BW = f_H - f_L$$

Distortion in amplifiers

Distortion is the difference between the output signal to the input signal.

There are 3 types of distortion


① Amplitude distortion

② Frequency distortion


③ phase distortion

03/02/15

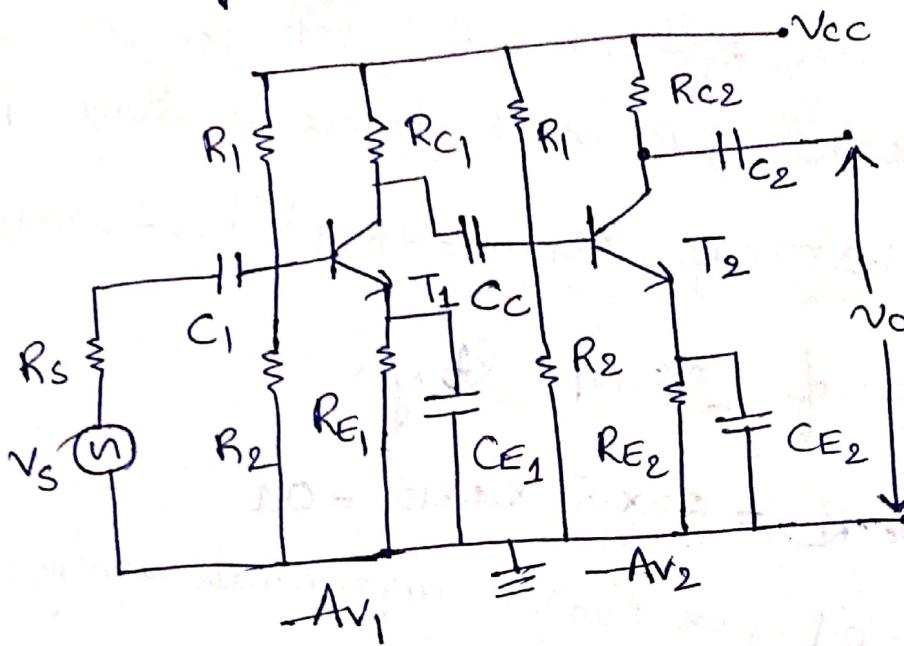Two stage RC coupled CE-CE Cascaded amplifiers



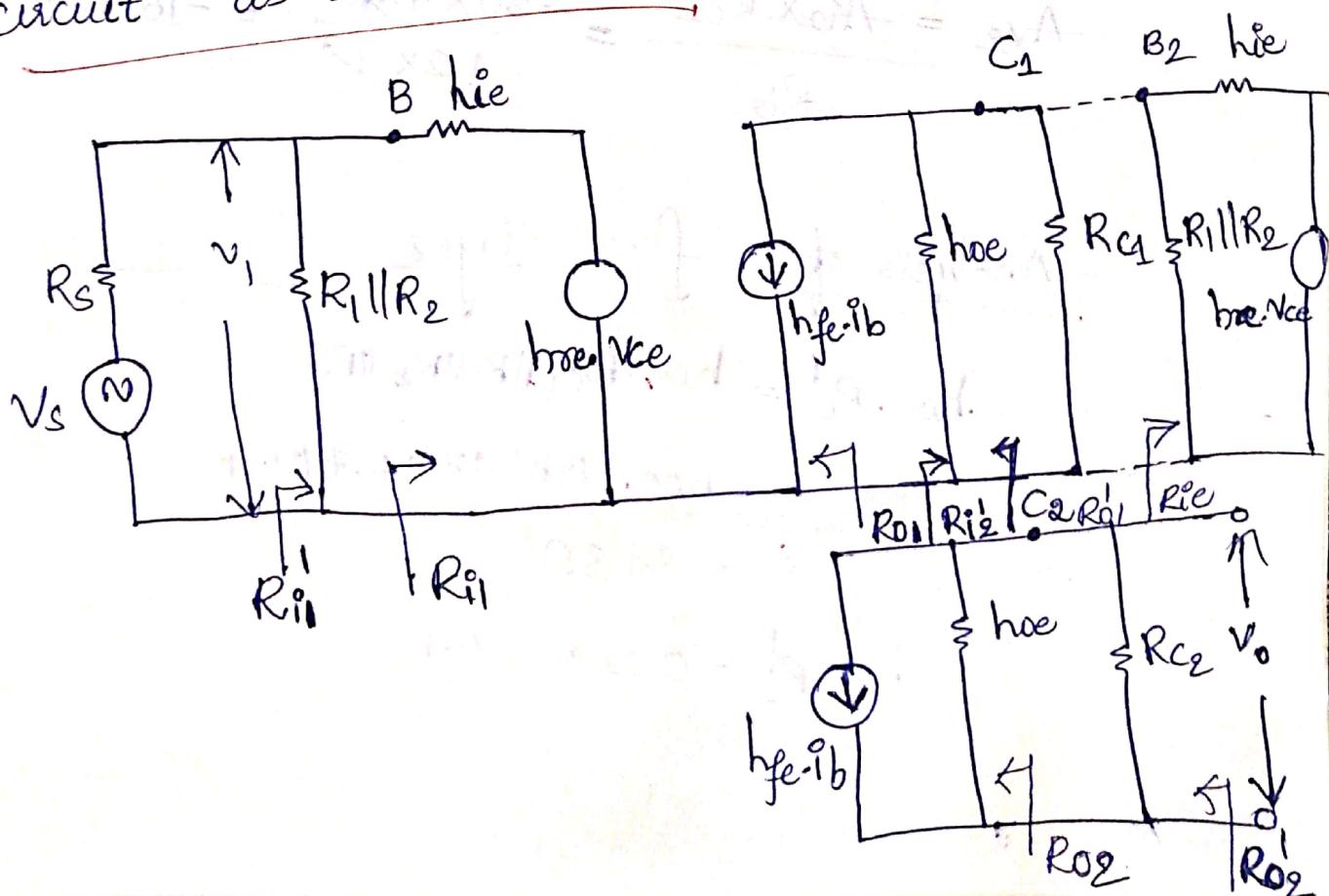- Assuming all capacitors acts a short circuit for A.C signal. we draw the h-parameter equivalent circuit as shown below.



Let us calculate R_i^o , A_v , A_i , A_{vs} if circuit parameters are

$$R_s = 1\text{ k}\Omega, R_{C_1} = 15\text{ k}\Omega, R_{E_1} = 0.1\text{ k}\Omega, R_{C_2} = 4\text{ k}\Omega,$$

$$R_{E_2} = 33\text{ k}\Omega, \text{with } R_1 = 200\text{ k}\Omega \text{ & } R_2 = 20\text{ k}\Omega \text{ for first stage}$$

$$\text{and } R_1 = 4.7\text{ k}\Omega \text{ & } R_2 = 4.7\text{ k}\Omega \text{ for Second stage. Assume}$$
$$\text{that } h_{ie} = 1.2\text{ k}\Omega, h_{fe} = 50, h_{oe} = 2.5 \times 10^{-4}, h_{ce} = 25 \times 10^6 \text{ A/V.}$$

Sol: Analysis of Second Stage

$$h_{oe} \cdot R_L = \frac{2.5 \times 10^{-4} \times 4 \times 10^3}{1.2 \times 10^3} = 0.1$$

$h_{oe} \cdot R_L = 0.1$, we can use approximate analysis.

$$A_{i2} = -h_{fe} = -50$$

$$R_{i2} = h_{ie} = 1.2\text{ k}\Omega$$

$$A_{v2} = \frac{-A_{i2} \times R_{C_2}}{R_{i2}} = \frac{-50 \times 4 \times 10^3}{1.2 \times 10^3} = -166.67$$

Analysis of first stages

$$h_{oe} \cdot R_L' = h_{oe} (R_{C_1} || R_1 || R_2 || R_{i2})$$

$$= h_{oe} (15\text{ k} \parallel 4.7 \parallel 4.7 \parallel 1.2\text{ k})$$

$$= 881.8\Omega$$

$$h_{oe} \cdot R_L' = 0.022 < 0.1$$

$$-A_{i1} = -h_{fe} = -50 \quad \checkmark$$

$$R_{i1} = h_{ie} = 1.2 \text{ k}\Omega \quad \checkmark$$

$$-Av_1 = \frac{-A_{i1} \times R_L'}{R_{i1}} = \frac{-50 \times 881.8}{1.2 \times 10^3} = -36.74$$

Overall voltage gain \checkmark

$$Av = Av_1 \cdot Av_2$$

$$= -166.67 \times -36.74$$

$$\boxed{Av = 6123.45}$$

$$Av_s = \frac{Av \cdot R_{i1}'}{R_{i1}' + R_s}$$

$$R_{i1}' = R_{11} \parallel R_{22} \parallel R_{11}$$

$$= 7227.4$$


$$Av_s = \frac{6123.45 \times 7227.4}{(7227.4 + 1000)} = 3248.6$$

$$R_{o1}' = \infty / R_C = \infty / 15 \text{ k} = 15 \text{ k}$$

Cascode amplifier

The cascode amplifier consists of common Emitter amplifier stage in series with the common ^{Collector} Source amplifier stage. It is used to solve the low impedance problem of circuit.

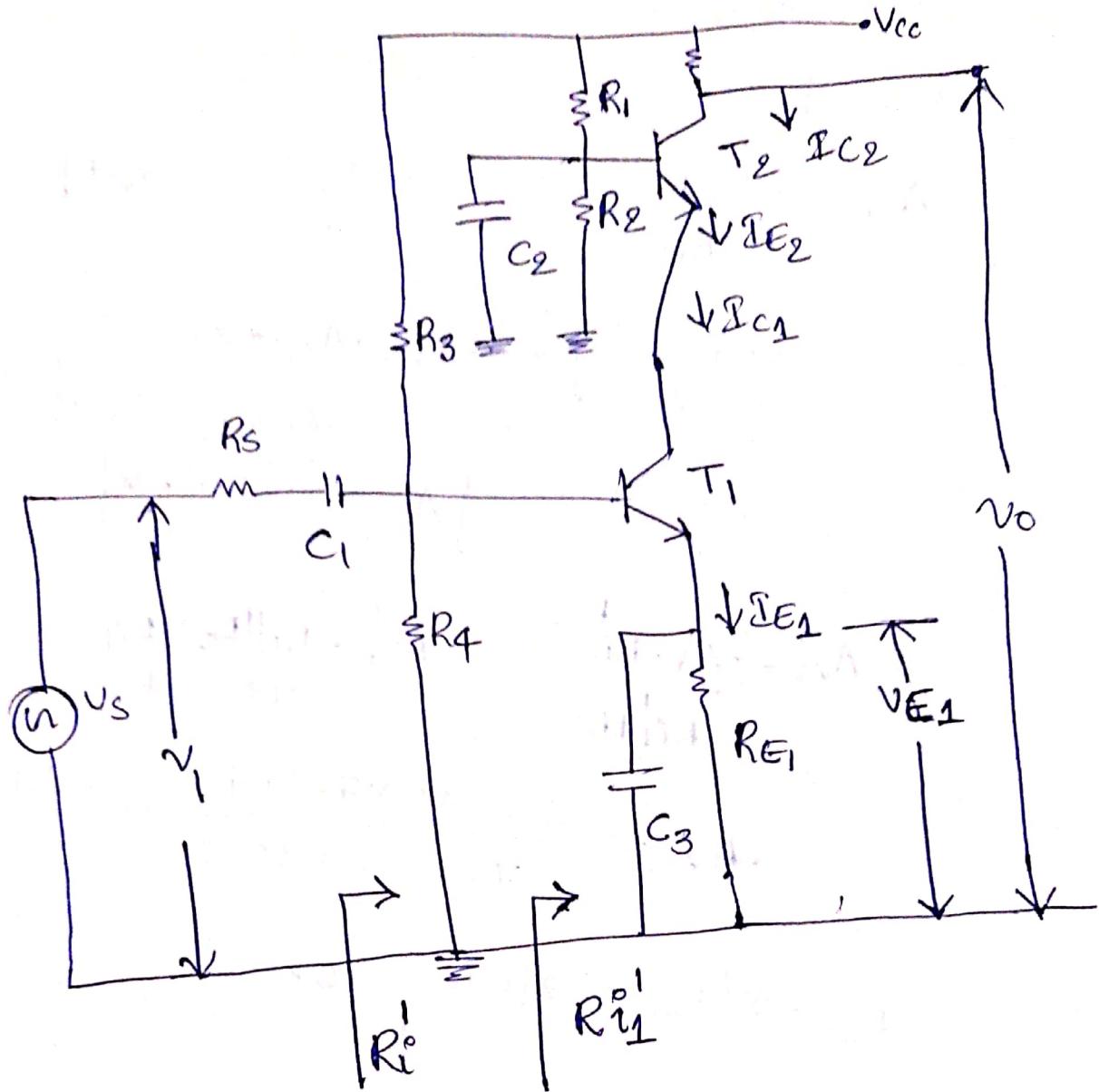The cascoding amplifier gives the high input impedance and good voltage gain.




$$R_S = 1\text{ k}\Omega, R_3 = 200\text{ k}\Omega, R_4 = 10\text{ k}\Omega, R_L = 3\text{ k}\Omega, h_{ie} = 1.1\text{ k}\Omega,$$

$$h_{fe} = 50$$

The Simplified hybrid equivalent circuit for Cascode amplifier is drawn by replacing their transistors with their Simplified equivalent circuit.


calculate $-A_v, R_i, R_o \& A_p$.

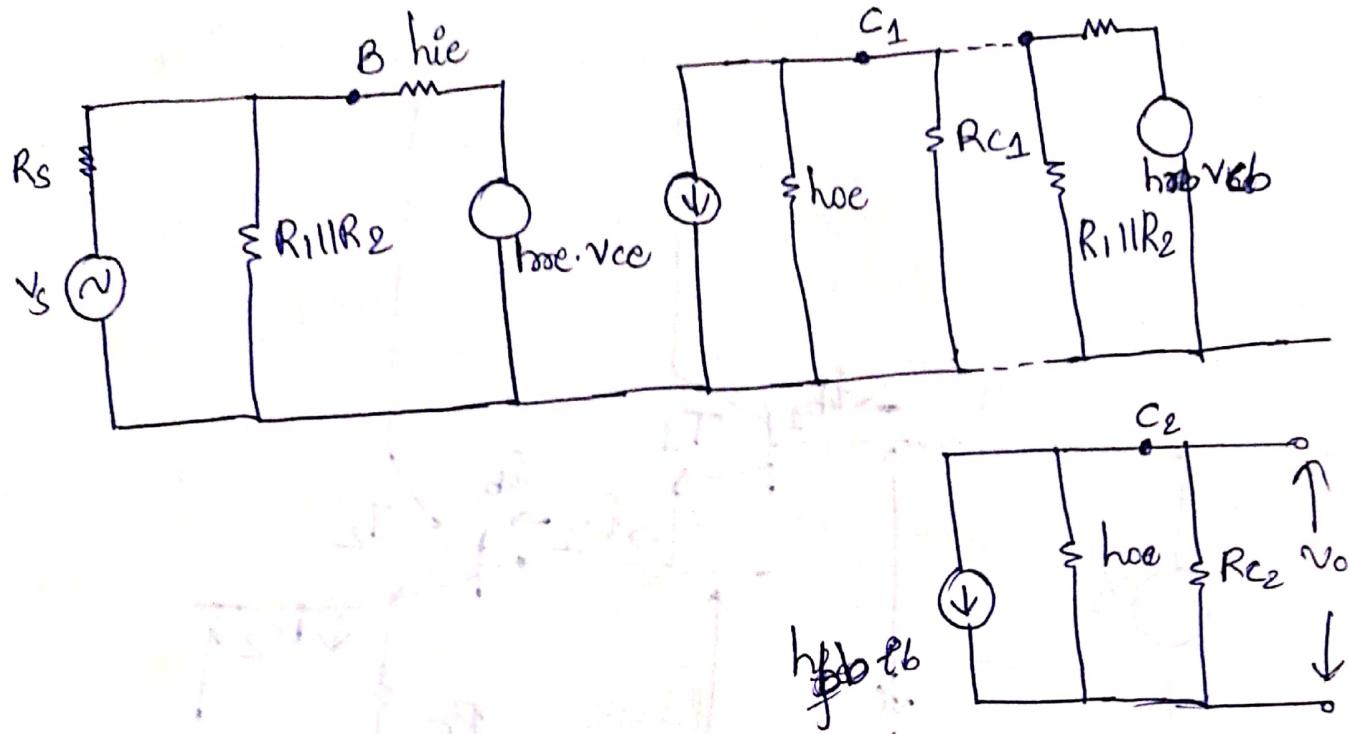

04/02/15

— A

Darlington pairs

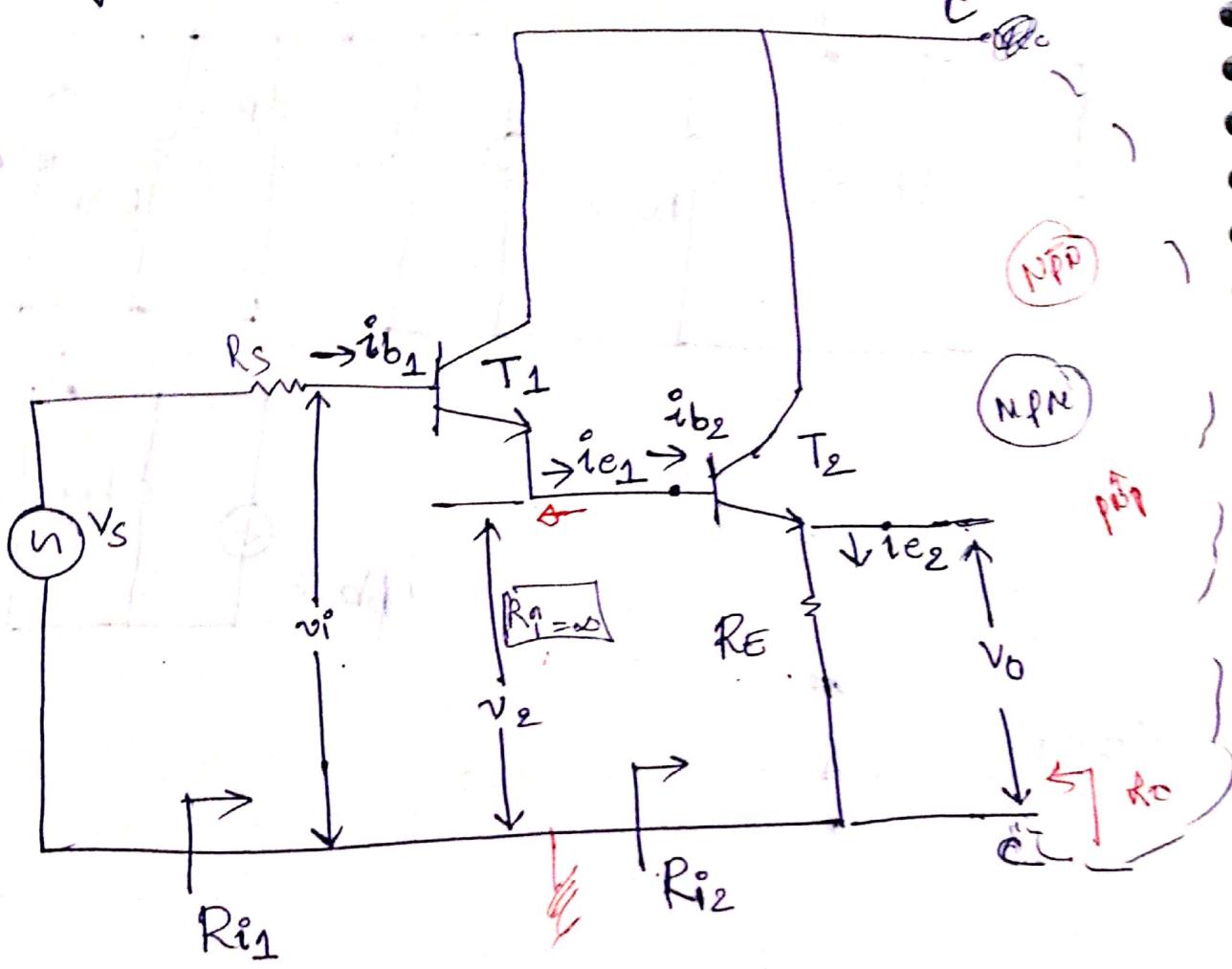

Darlington pair is used to improve the input impedance of the amplifier circuit. Direct coupling of two emitter followers (Emitter of stage 1 - Base of stage 2) results a darlington emitter follower amplifier. The above figure shows the cascaded connection of two emitter followers called the darlington connection.

Analysis of 2nd stage

Assume that $R_E \ll R_L$ is small such that

$$\text{h.o. } R_L < 0.1.$$

So we can use the approximate analysis for this stage (2).

Current gain $A_{i2} = (1+h_{fe}) \rightarrow q$ - cc config.

Input Resistance $R_{i2} = h_{ie} + (1+h_{fe})R_E$

If $h_{ie} \ll (1+h_{fe})R_E$


$$R_{i2} = (1+h_{fe})R_E \rightarrow = R_L$$

The load resistance of the first stage is the input resistance of the R_{i2} . As R_{i2} is very high, usually it does not meet the requirement.

Hence we have to use exact analysis for the first stage.

the hybrid equivalent circuit of cc-configuration for Stage 1 is shown below.

$$R_{i2} = R_L, \text{ very high}$$

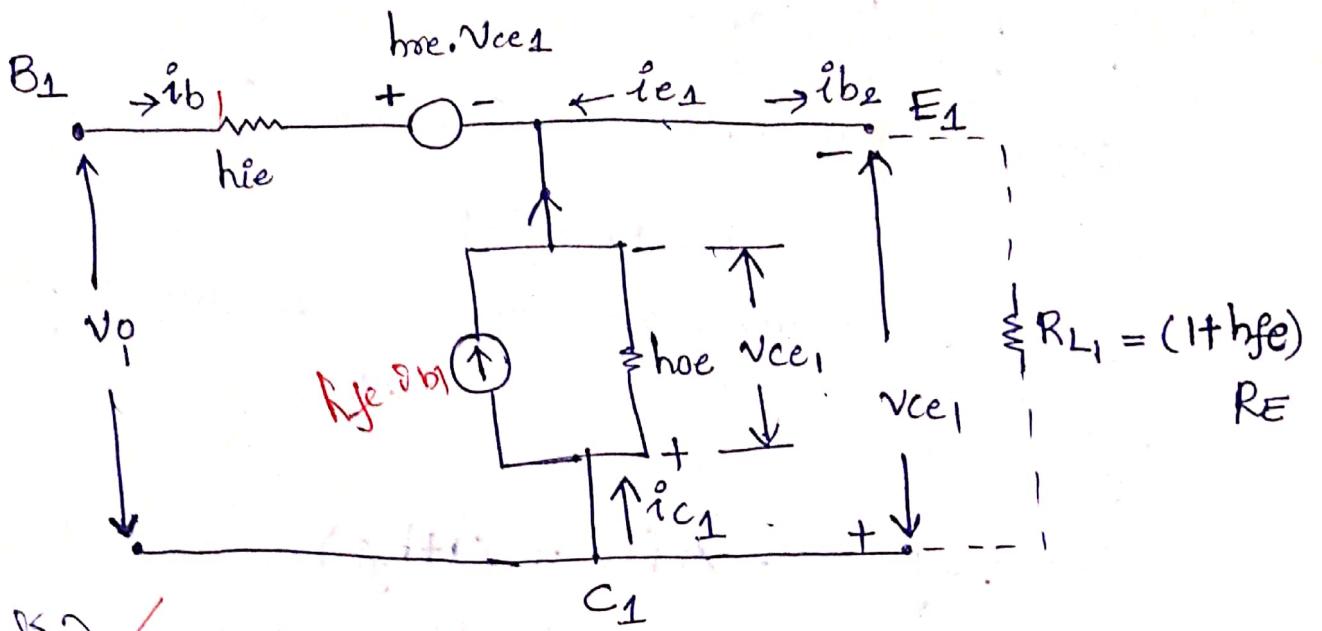

(Breaks
Analogies) ✓

$$A_{V1} = \frac{i_{B2}}{i_{B1}} = \frac{-i_{e1}}{i_{B1}}$$

$$i_{B2} = -i_{e1}$$

$$i_{e1} = -(i_{B1} + i_{C1})$$

$$i_{C1} = h_{FE} \cdot i_{B1} + h_{OE} \cdot V_{CE1}$$

$$= h_{FE} \cdot i_{B1} + h_{OE} \cdot (-i_{B2} \cdot R_{L1})$$

$$i_{C1} = h_{FE} \cdot i_{B1} + h_{OE} \cdot i_{e1} \cdot R_{L1}$$

Sub. i_{C1} in i_{e1}

$$i_{e1} = -(i_{B1} + h_{FE} i_{B1} + h_{OE} (-i_{B2} \cdot R_{L1}))$$

$$h_{OE} i_{e1} \cdot R_{L1}$$

$$i_{e1} + h_{OE} R_{L1} i_{e1} = -i_{B1} (1 + h_{FE})$$

$$-\frac{i_{e1}}{i_{B1}} = \frac{(1 + h_{FE})}{1 + h_{OE} \cdot R_{L1}}$$

we know that

$$R_{L1} = (1+hfe) R_E \quad \text{sub. in above equation}$$

$$-A_{i1}^o = -\frac{i_{e1}}{i_{b1}} = \frac{(1+hfe)}{1+hoe(1+hfe)R_E}$$

$$\boxed{-A_{i1}^o = \frac{1+hfe}{1+hoe \cdot hfe \cdot R_E}}$$

~~hfe > 1~~
~~hoe > 1~~
hoe: in Amhos
 $hoe R_E \ll 1$
 $1 + hoe R_E + hoe hfe \ll 1$

Input Resistance (R_{i1}) &

$$R_{i1} = \frac{V_i}{i_{b1}}$$

Apply KVL to output loop, we get

$$V_i - i_{b1} hie - hre V_{ces1} + V_{ces1} = 0$$

$$V_i = i_{b1} hie + hre V_{ces1} - V_{ces1}$$

the term $hre \cdot V_{ces1}$ is negligible. Since

hre is the order of 2.5×10^{-4} ✓ $V_{ces1} = -i_{b2} R_{L2}$

$$V_i = i_{b1} hie - (V_{ces1})$$

$$V_i = i_{b1} hie - (-i_{b2} R_{L2})$$

$$V_i = i_{b1} hie + i_{b2} R_{L2}$$

÷ by i_{b1}

$$R_{i1} = \frac{V_i}{i_{b_1}} = h_{ie} + \frac{i_{b_2}}{i_{b_1}} R_{L1}$$

$$= h_{ie} + A_{i1} \cdot R_{L1}$$

A_{i1}
 $i_{b_2} \approx R$
 i_{b_1}
 $(1+hfe) R_E$
 $R_{L1} =$

$$R_{i1} = h_{ie} + A_{i1} (1+hfe) R_E$$

Sub. - the value of A_{i1}

$$R_{i1} = h_{ie} + \frac{(1+hfe)(1+hfe) R_E}{1+hfe h_{oe} R_E}$$

$$R_{i1} = h_{ie} + \frac{(1+hfe)^2 R_E}{1+h_{oe} hfe R_E}$$

$$\therefore h_{ie} \ll \frac{(1+hfe)^2 R_E}{1+h_{oe} hfe R_E}$$

$$\therefore R_{i1} = \frac{(1+hfe)^2 R_E}{1+h_{oe} hfe \cdot R_E}$$

(A_i) overall current gain &

$$A_i = A_{i1} \cdot A_{i2} = \frac{(1+hfe)}{1+h_{oe}(1+hfe)R_E} \times (1+hfe)$$

$$-A_i^o = \frac{(1+h_{fe})^2}{1+h_{oe}(1+h_{fe})R_E}$$

Parameter Stage ① Darlington

$$\text{Input Resistance} \quad (1+h_{fe})R_E \quad \frac{(1+h_{fe})^2 R_E}{1+h_{oe}h_{fe}R_E}$$

$$\text{Current Gain} \quad -A_I(1+h_{fe}) \quad \frac{(1+h_{fe})^2}{1+h_{oe}(1+h_{fe})R_E}$$

Take $R_E = 3.3\text{ k}\Omega$ and $h_{ie} = 110\text{ m}\Omega$, $h_{re} = 2.5 \times 10^4$

$$h_{fe} = 50, h_{oe} = 25 \text{ mA/V}$$

Stage ②

$$R_i = 168.3\text{ k}\Omega$$

$$R_i^o = 1.67\text{ M}\Omega$$

$$-A_i^o = 51$$

$$-A_i^o = 499.47$$

QD

overall voltage gain (A_v)

$$-A_v = A_i \frac{R_L}{R_i}$$

subtracting 1 on both sides

$$1 - A_v = 1 - \frac{A_i R_L}{R_i}$$

$$1 - A_v = \frac{R_i - A_i R_L}{R_i}$$

$A_i = h_{ie}$
 $R_i = h_{re} + h_{ie} + h_{ce}$
(not simplified)

$$1 - A_v = \frac{h_{ie} + h_{re} \cdot A_i R_L - A_i R_L}{R_i}$$

$$1 - A_v = \frac{h_{ie} + h_{re} \cdot A_i R_L - A_i R_L}{h_{ie} + h_{re} \cdot A_i R_L}$$

From convergence
we have
Table

$$1 - A_v = \frac{h_{ie} + h_{re} \cdot A_i R_L - A_i R_L}{h_{ie} + h_{re} \cdot A_i R_L}$$

$$1 - A_v = \frac{h_{ie}}{R_i}$$

$$-Av = 1 - \frac{h_{ie}}{R_i}$$

∴ overall voltage gain is the product of individual voltage gains.

$$\therefore -Av = -Av_1 \cdot Av_2$$

$$-Av = \left(1 - \frac{h_{ie1}}{R_{i1}}\right) \left(1 - \frac{h_{ie2}}{R_{i2}}\right)$$

$$-Av = 1 - \frac{h_{ie2}}{R_{i2}} - \frac{h_{ie1}}{R_{i1}} + \left(\frac{h_{ie1} h_{ie2}}{R_{i1} R_{i2}}\right)$$

we know that $R_{i1} \gg R_{i2}$

$$-Av = 1 - \frac{h_{ie2}}{R_{i2}}$$

$$-Av = 1 - \frac{h_{ie2}}{R_{i2}}$$

$$1 - \frac{h_{ie}}{R_{i2}}$$

Output impedances R_o

$$R_o = \frac{1}{y_0} =$$

$$y_{01} = h_{oe} + \frac{(1+h_{fe})}{h_{ie} + R_s} \quad (\because y_{01} = h_{oe} - \frac{h_{fe} + h_{re}}{h_{ic} + R_s})$$

$$y_{01} = h_{oe} + \frac{(1+h_{fe})}{h_{ie} + R_s} \quad (\because h_{re} = 1) \quad h_{ic} = h_{ie}$$

$$y_{01} = \frac{1+h_{fe}}{h_{ie} + R_s}$$

$$h_{oe} \ll \frac{1+h_{fe}}{h_{ie} + R_s}$$

$$h_{oe} \approx h_{re} \quad h_{fe} = -(1+h_{fe})$$

$$R_{o1} = 1/y_{01}$$

$$R_{o1} = \frac{h_{ie} + R_s}{1+h_{fe}}$$

$$(\because R_{s2} = R_{o1})$$

$$R_{o2} = \frac{R_{s2} + h_{ie2}}{1+h_{fe}} = \left(\frac{h_{ie1} + R_s}{1+h_{fe}} \right) + \frac{h_{ie2}}{1+h_{fe}}$$

Since current times h_{ie1} is \approx current times h_{ie2}
 $h_{ie1} = (1+h_{fe})h_{ie2}$

$$R_{o2} = \frac{h_{ie1} + R_s}{(1+h_{fe})^2} + \frac{h_{ie2}}{1+h_{fe}}$$

$$(\because h_{ie1} \approx (1+h_{fe})h_{ie2})$$

$$R_{o2} = \frac{(1+h_{fe})h_{ie2} + R_s}{(1+h_{fe})^2} + \frac{h_{ie2}}{1+h_{fe}}$$

or expand by
x get

$$R_{o2} = R_s(1+h_{fe})^2 + 2h_{ie2}/(1+h_{fe})$$