
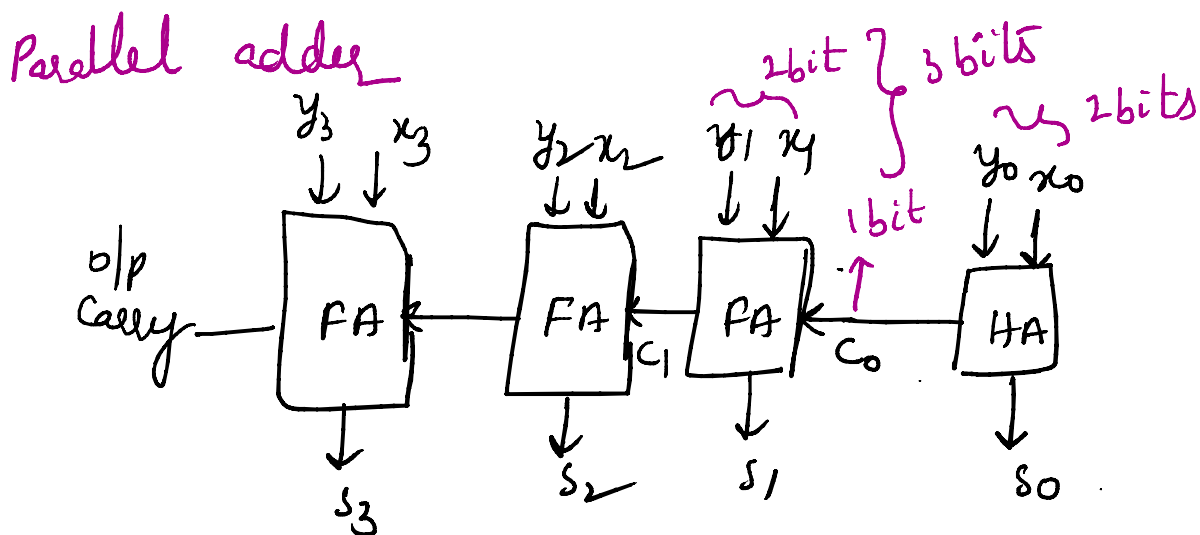



4 bit adder
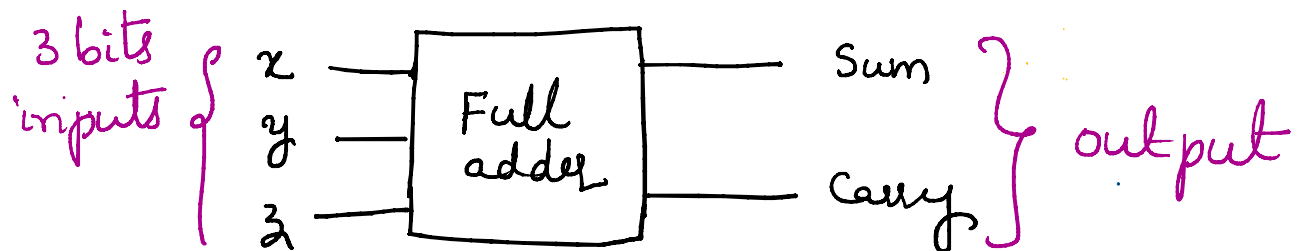
$$\begin{array}{r}
 \text{Carry} \quad \text{MSB} \leftarrow \text{LSB} \\
 x = 1001 \\
 y = 1011 \\
 \hline
 \text{Carry} \rightarrow 10100
 \end{array}$$



Serial adder

✶✶

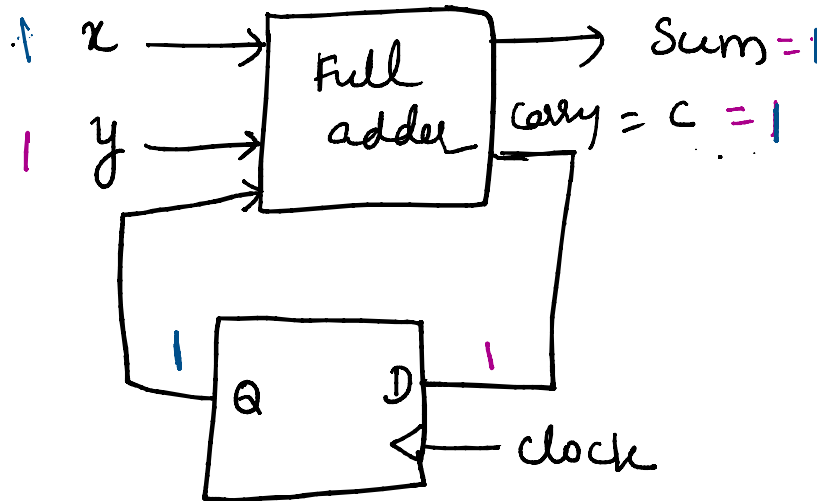

Carry 1 1 1 1
 $x = 1011$
 $y = 1111$
 Carry 1 1 0 1 0
 LsB


D	N-S Q(t+1)
0	0
1	1

① Design serial adder sequential circuit using D flip flop.

state table

Present state ✓	x	y	Next State Carry=D	Output Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

state diagram

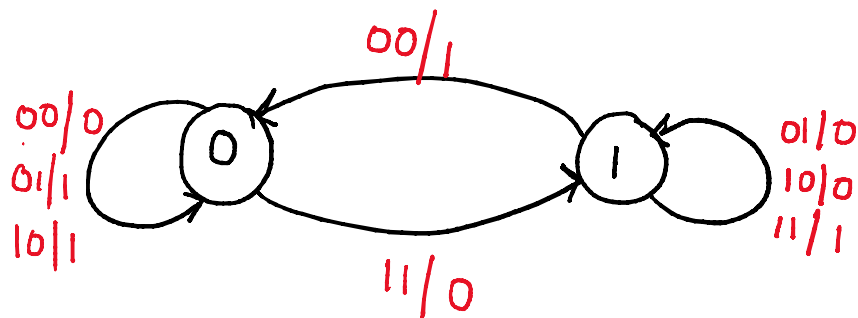


To design sequential circuit, need to follow these steps

1. State diagram
2. State table
3. Excitation table for sequential circuit
4. From excitation table, need to determine reduced form of boolean expressions.
5. Draw logic diagram for the boolean expression.

D flip flop excitation table

Q Present state	Q(t+1) Next state	D
0	0	0
0	1	1
1	0	0
1	1	1

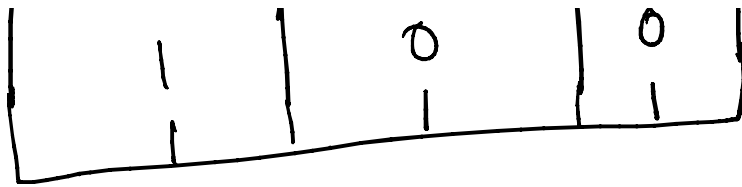


Excitation table for Serial adder (sequential ckt)

Excitation

D Flip flop

Full Adder

Decim	Present state Z	x	y	Next State Carry=D	Output Sum	
0	0	0	0	0	0	0
1	0	0	1	0	1	0
2	0	1	0	0	1	0
3	0	1	1	1	0	1
4	1	0	0	0	1	0
5	1	0	1	1	0	1
6	1	1	0	1	0	1
7	1	1	1	1	1	1

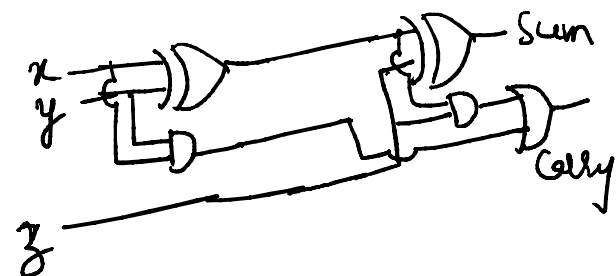

K map for D

xy \ yz	00	01	11	10
0	0	0	1	0
1	0	1	1	1

ABC

Carry out = $AB + BC + CA$

$\checkmark D = zx + xy + zy \checkmark$

logic diagram

