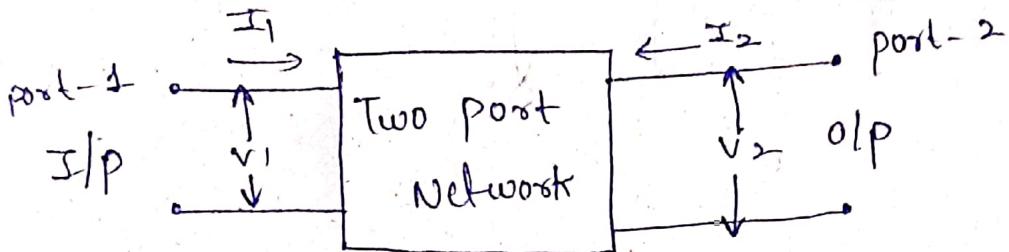


19/12/19 Electronic Circuit Analysis

* Two Port Network



$$V_1 = h_{11} I_1 + h_{12} V_2 \rightarrow ①$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \rightarrow ②$$

Eq ① $V_2 = 0 \quad I_1 = 0$

$$V_1 = h_{11} I_1 \quad V_1 = h_{12} V_2$$

$$h_{11} = \frac{V_1}{I_1} = h_o \quad h_{12} = \frac{V_1}{V_2}$$

Eq ②

$$V_2 = 0 \quad I_1 = 0$$

$$I_2 = h_{21} I_1 \quad I_2 = h_{22} V_2$$

$$h_{21} = \frac{I_2}{I_1} \quad h_{22} = \frac{I_2}{V_2} = h_o$$

$h_{11} \rightarrow h_o \rightarrow$ Input Impedance

$h_{22} \rightarrow h_o \rightarrow$ Output admittance


$h_{21} \rightarrow h_f \rightarrow$ Forward current gain

$h_{12} \rightarrow h_r \rightarrow$ Reverse voltage gain


$$V_1 = h_o I_1 + h_f V_2 \rightarrow ③$$

$$I_2 = h_f I_1 + h_o V_2 \rightarrow ④$$

Equivalent ckt

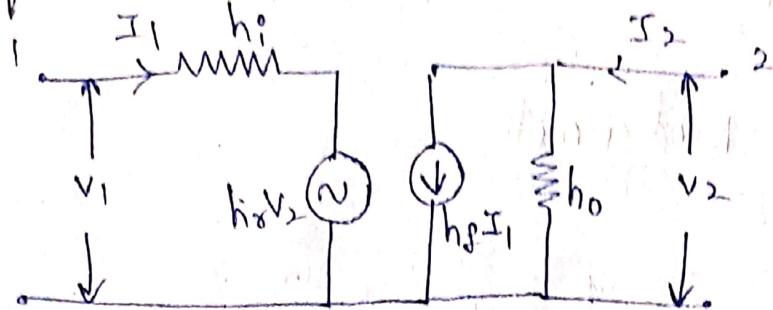


Common Base

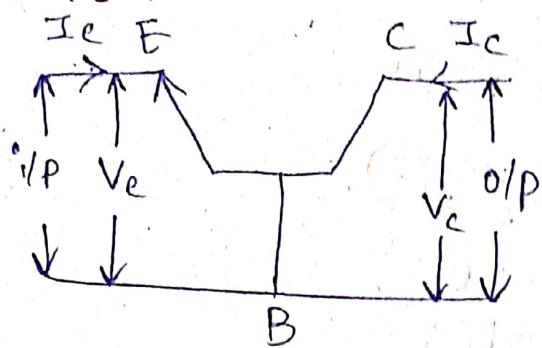


$$V_e = h_{1b} I_e + h_{2b} V_c$$

$$I_c = h_{2b} I_e + h_{3b} V_c$$

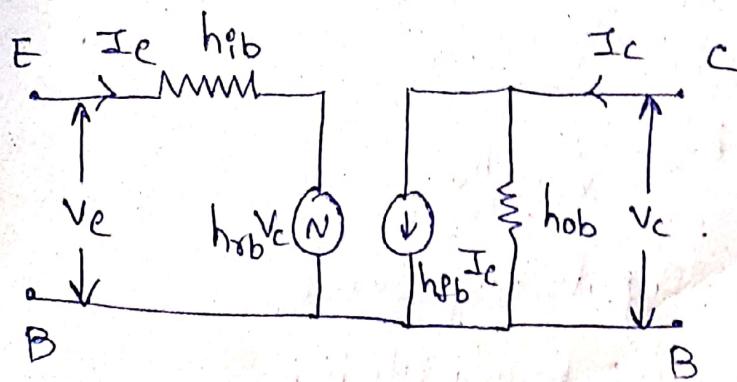


Common ~~emitter~~ collector :-

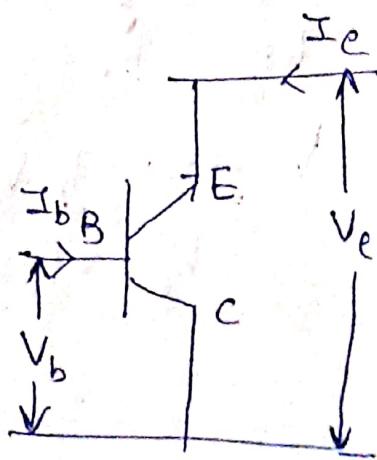


$$V_b = h_{ie} I_b + h_{re} V_C$$

$$I_C = h_{fe} I_b + h_{oe} V_C$$

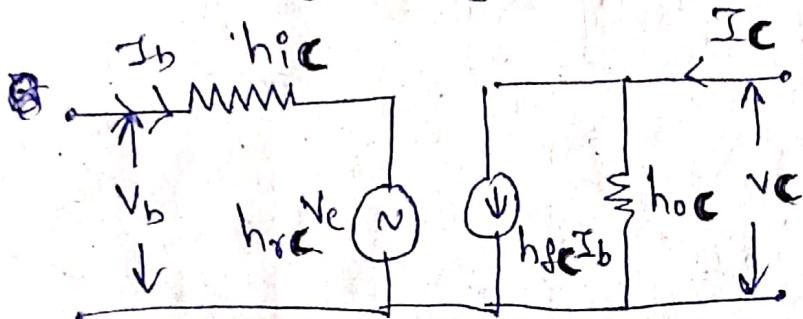


Common ~~base~~ emitter:-

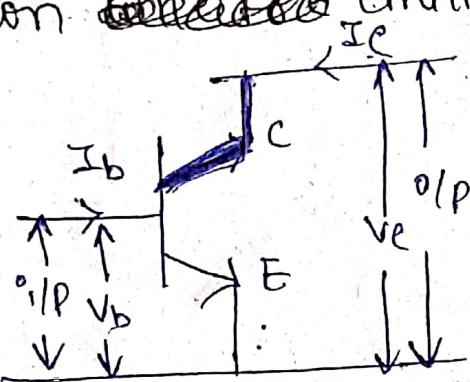


$$V_b = h_{ie} I_b + h_{re} V_e$$


$$I_e = h_{fe} I_b + h_{oe} V_e$$

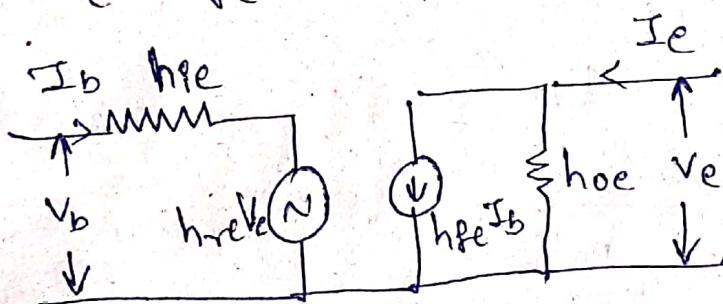

* Analysis of two port network using h-parameter

Model:

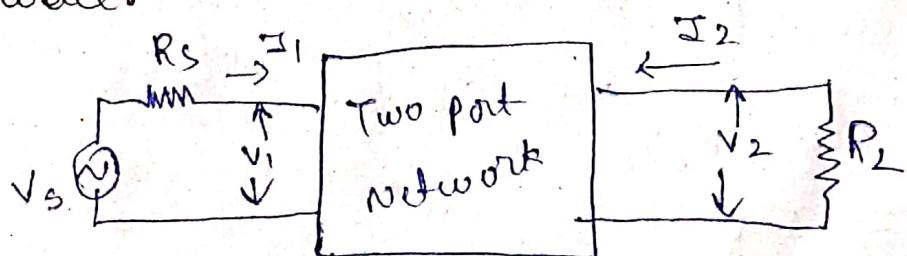

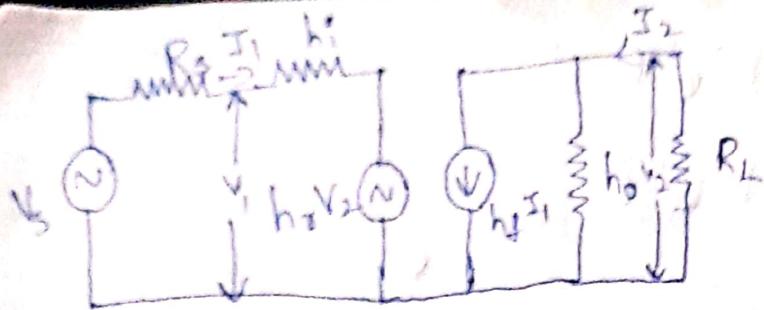

$$V_1 = h_i I_1 + h_r V_2 \quad \text{--- (1)}$$

$$I_2 = h_f I_1 + h_o V_2 \quad \text{--- (2)}$$

$$\text{Current gain} \therefore A_I = \frac{-I_2}{I_1}$$

From Eq. (2)

$$I_2 = h_f I_1 + h_o V_2$$

$$V_2 = -I_2 R_L$$

$$I_2 = h_f I_1 - h_o I_2 R_L$$

$$I_2 + h_o I_2 R_L = h_f I_1$$

$$I_2 [1 + h_o R_L] = h_f I_1$$

$$\frac{I_2}{I_1} = \frac{h_f}{1 + h_o R_L}$$

$$\frac{-I_2}{I_1} = \frac{-h_f}{1 + h_o R_L}$$

$$A_I = \frac{-h_f}{1 + h_o R_L}$$

$$\text{Input Resistance} \therefore R_i = \frac{V_1}{I_1}$$

$$V_1 = h_i I_1 + h_r V_2$$

$$V_2 = -I_2 R_L$$

w, k, T

$$-I_2 = A_I I_1$$

$$\frac{V_1}{I_1} = \frac{h_i I_1 + h_r A_I I_1 R_L}{I_1}$$

$$R_i = h_f + h_o A_I R_L$$

Voltage gain: $A_v = \frac{V_2}{V_1}$

$$V_2 = -I_2 R_L$$

$$V_2 = A_I I_1 R_L$$

$$\frac{V_2}{V_1} = \frac{A_I I_1 R_L}{V_1}$$

$$A_v = A_I \left(\frac{I_1}{V_1} \right) R_L$$

$$A_v = \frac{A_I R_L}{R_i}$$


Output Admittance: $Y_o = \frac{I_2}{V_2}$

$$\frac{I_2}{V_2} = \frac{h_f I_1}{V_2} + \frac{h_o V_2}{V_2}$$

$$Y_o = h_f \left(\frac{I_1}{V_2} \right) + h_o$$

$$Y_o = h_f \left(\frac{-h_o}{R_s + h_i} \right) + h_o$$
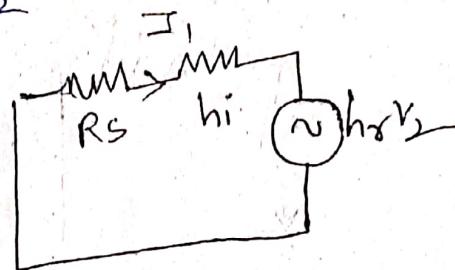
$$Y_o = h_o - \frac{h_f h_o}{R_s + h_i}$$



apply KV_L

$$0 = (R_s + h_i) I_1 + h_o V_2$$

$$h_o V_2 = -(R_s + h_i) I_1$$

$$\frac{I_1}{V_2} = -\frac{h_o}{R_s + h_i}$$

CE

CB, CC, CC

* 8

$$A_I = \frac{-h_f}{1+h_o R_L}$$

$$A_I = \frac{-h_{fe}}{1+h_{oc} R_L}$$

$$A_I = \frac{-h_{fb}}{1+h_{ob} R_L}$$

$$A_I = \frac{-h_{fc}}{1+h_{oc} R_L}$$

$$R_i = h_i + h_o A_I R_L$$

$$R_i = h_{ie} + h_{re} A_I R_L$$

$$R_i = h_{ib} +$$

$$R_i = h_{ic} + h_{re}$$

$$A_v = \frac{A_I R_L}{R_i}$$

$$A_v = \frac{A_I R_L}{R_i}$$

$$A_v = \frac{A_I R_L}{R_i}$$

$$A_v = \frac{A_I R_L}{R_i}$$

$$Y_o = h_o - \frac{h_f h_r}{R_s + h_i}$$


$$Y_o = h_{oc} - \frac{h_{fe} h_{re}}{R_s + h_{ie}}$$

$$Y_o = h_{ob} -$$

$$Y_o = h_{oc} - \frac{h_{fb} h_{rb}}{R_s + h_{ib}}$$

$$Y_o = h_{oc} - \frac{h_{fe} h_{ic}}{R_s + h_{ic}}$$

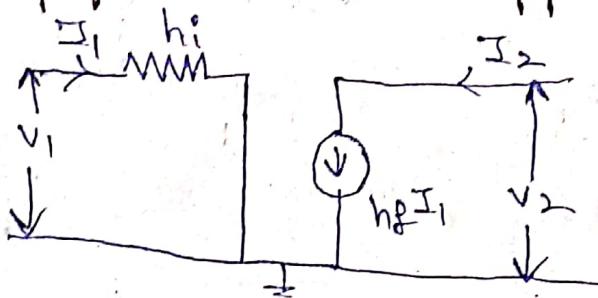* Simplified Model or Approximation model



T^r \rightarrow IIP F.B \rightarrow Dep J \rightarrow MR \downarrow
 \rightarrow O/P R.B \rightarrow Dep \uparrow \rightarrow MR \uparrow

$$A_I = \frac{-h_f}{1+h_o R_L} \Rightarrow -h_f$$

CB

CE

CC

$$-h_{fb}$$

$$-h_{fe}$$

$$-h_{ec}$$

$$R_i = h_i + h_o A_I R_L \Rightarrow h_i$$

$$h_{ib}$$

$$h_{ie}$$

$$h_{ic}$$

$$A_v = \frac{A_I R_L}{R_i} = \text{same}$$

$$\frac{A_I R_L}{R_i}$$

$$\frac{A_I R_L}{R_i}$$

$$\frac{A_I R_L}{R_i}$$

$$Y_o = h_o - \frac{h_f h_r}{R_s + h_i} \Rightarrow 0$$

$$0$$

$$0$$

$$0$$

* Classification of Amplifiers

1. According to the number of stages

(a) Single stage amplifier

(b) Multi stage amplifier.

2. According to the couplings

(a) RC coupled Amplifier

(b) Direct coupled Amplifier

(c) Transformer ~~coupled~~ Amplifier

3. According to the load impedance

(a) Tune amplifiers

(b) Un-Tune amplifiers

4. According to the frequencies

(a) Audio Amplifier

(b) Radio ^{frequency} Amplifier

(c) Very high frequency amplifier.

(d) ultra high frequency amplifier.

(e) Micro wave frequency amplifier.

5. According to the large signal

(a) class-A power amplifier


(b) class-B power "

(c) class-C power "

(d) class-AB power "

(e) class-D power amplifier

* Analysis of multi stage Amplifier.


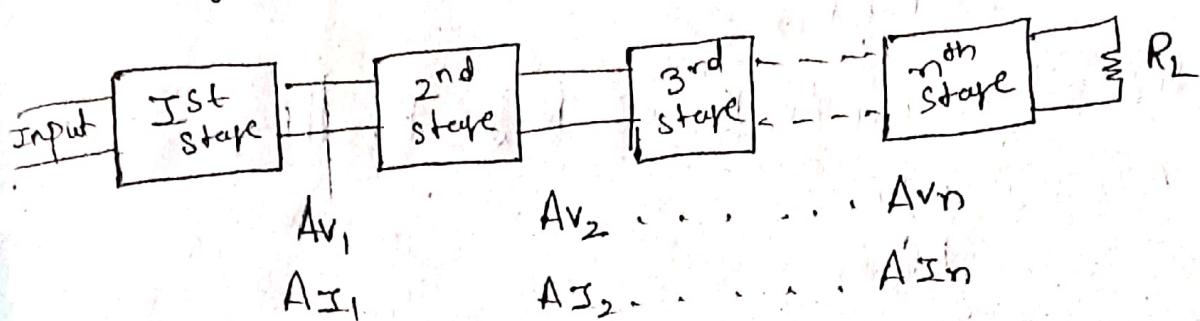


$$A_v = A_{v1} \times A_{v2} \times \dots \times A_{vn}$$

$$A_I = A_{I1} \times A_{I2} \times \dots \times A_{In}$$

The analysis is done from output to the input.

Two Stage CE RC coupled Amplifier

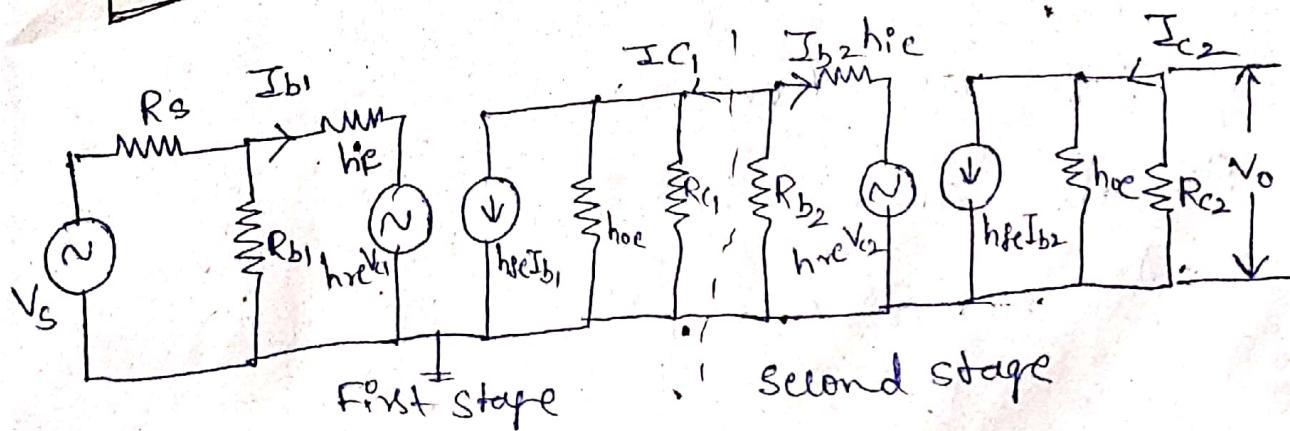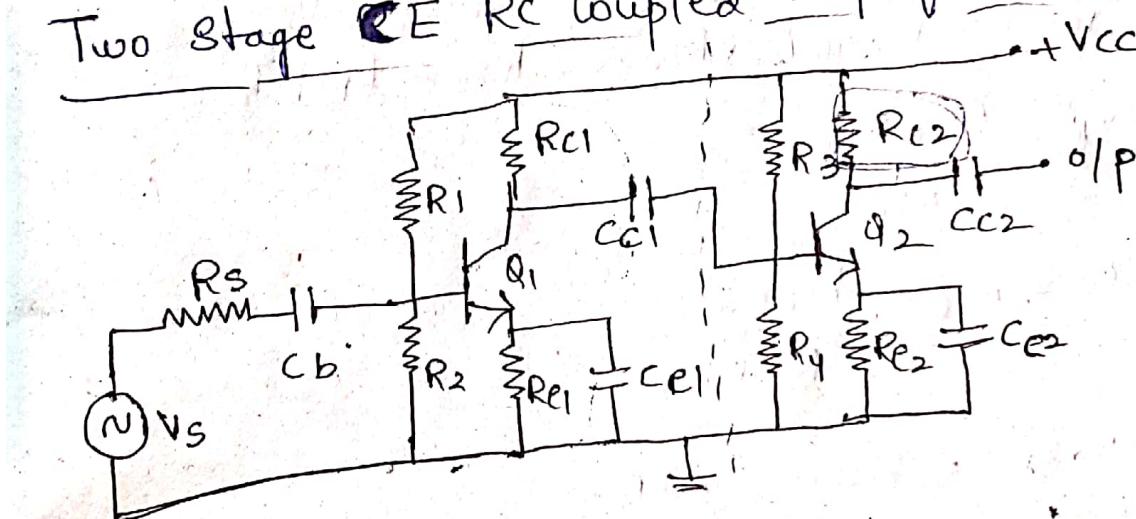

$$R_{b1} = R_1 \parallel R_2$$

$$R_{b2} = R_3 \parallel R_4$$

Second Stage Analysis

$$A_{I2} = \frac{-h_{fe}}{1 + h_{fe} R_{C2}}$$

$$R_{o2}^i = h_{ie} + h_{re} A_{I2} R_{C2} \Rightarrow R_{o2}^i = R_{b2} \parallel R_{i2}$$

$$Av_2 = \frac{A_{I2} R_{C2}}{R_{o2}^i}$$

$$Y_{o2} = h_{oe} - \frac{h_{fe} h_{re}}{R_s + h_{ic}}$$

First Stage Analysis

$$A_{I1} = \frac{-h_{fe}}{1 + h_{fe} R_{C1}}$$

$$R_{o1}^i = h_{ie} + h_{re} A_{I1} R_{C2} \Rightarrow R_{o1}^i = R_{b1} \parallel R_{i1}$$

$$Av_1 = \frac{A_{I1} R_{C1}}{R_{o1}^i}$$

$$Y_{o1} = h_{oe} - \frac{h_{fe} h_{re}}{R_s + h_{ie}}$$


Overall voltage gain

$$Av = Av_2 \times Av_1$$

Overall current gain

$$A_I = A_{I2} \times A_{I1}$$

* Simplified Model

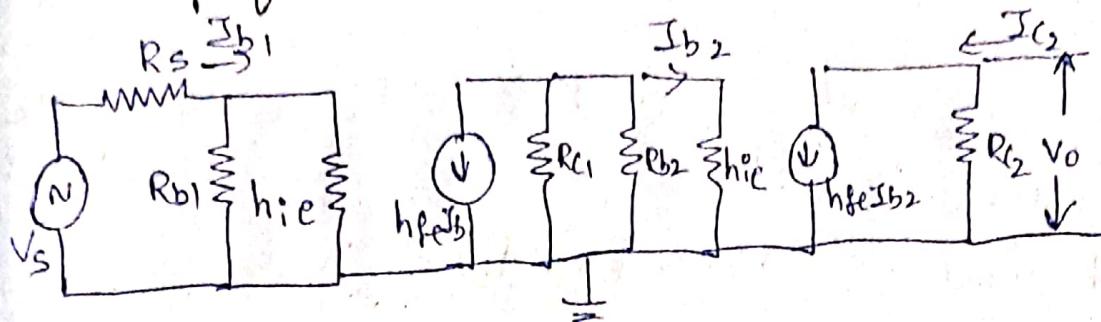

Approximate Analysis

Second stage Analysis

$$A_{I2} = -h_{fe}$$

$$R'_{i2} = R_{b2} \parallel h_{ie}$$

$$A_{V2} = \frac{A_{I2} R_{C2}}{R'_{i2}}$$

$$Y_{O2} = \frac{1}{R_{C2}}, R_o = R_{C2}$$

First stage Analysis

$$A_{I1} = -h_{fe}$$

$$R'_{i1} = R_{b1} \parallel h_{ie}$$

$$A_{V1} = \frac{A_{I1} R_{C1}}{R'_{i1}}$$

$$Y_{O1} = \frac{1}{R_{C1}}, R_o = R_{C1}$$

$$A_V = A_{V2} \times A_{V1} \rightarrow \text{Voltage gain}$$

$$A_I = A_{I2} \times A_{I1} \rightarrow \text{Current gain}$$

① For a CE, CE cascade amplifier find

~~\$R_{out}~~, \$R_i, A_I, A_V, R'_i, R'_o\$ & \$R_o\$ with
the following parameters

$$R_s = 1k$$

$$hie = 1.2 k \cdot \Omega$$

$$R_1 = 200k \quad \text{first stage}$$

$$R_2 = 20k \quad \text{second stage}$$

$$R_{C1} = 15k$$

$$hre = 2.5 \times 10^{-4}$$

$$R_{e1} = 100 \Omega$$

$$hoe = 25 \mu A/V$$

$$R_{C2} = 4k$$

$$R_{e2} = 33 \Omega$$

$$R_1 = 44k \quad \text{second stage}$$

$$R_2 = 44k$$

(Q): Second stage Analysis

$$A_{IZ2} = \frac{-50}{1 + 25 \times 10^6 \times 4 \times 10^3} = -45.45$$

$$R_{i2}^1 = R_{b2} \parallel R_{i2}$$

$$\begin{aligned} R_{i2} &= hie + hre A_{IZ2} R_{C2} \\ &= 1.2 \times 10^3 + 2.5 \times 10^{-4} (-45.45) 4 \times 10^3 \\ &= 1154.55 \end{aligned}$$

$$\begin{aligned} R_{b2} &= R_1 \parallel R_2 = \frac{44 \times 10^3 \times 44 \times 10^3}{44 \times 10^3 + 44 \times 10^3} \\ &= 23500 \end{aligned}$$

$$\begin{aligned} R_{i2}^1 &= 23500 \parallel 1154.55 \\ &\approx 1100.48 \end{aligned}$$

$$A_{V2} = \frac{A_{IZ2} R_{i2}}{R_{i2}^1} = \frac{(-45.45)(4 \times 10^3)}{1100.48}$$

$$A_{V_2} = -165.200$$

$$R_o = R_{C2} = 4 \times 10^3$$

$$\cancel{R_o = R_{C2} = \frac{50 \times 2.5 \times 10^{-4}}{1 \times 10^{-6} + 1.2 \times 10^{-3}}} = 1.931 \times 10^{-5}$$

$$R_o = \frac{1}{Y_o} = 51786.63$$

First stage Analysis

$$A_{I1} = \frac{-50}{1 + 25 \times 10^{-6} (15 \times 10^3)} = -36.36$$

$$R_{o1} = 1.2 \times 10^3 + 2.5 \times 10^{-4} (-36.36) (4 \times 10^3)$$

$$R_{o1} = 1163.64$$

$$R'_{i1} = R_{b1} || R_{o1}$$

$$R_{b1} = 200K || 20K$$

$$R_{b1} = \frac{200 \times 10^3 \times 20 \times 10^3}{200 \times 10^3 + 20 \times 10^3} = 18181.81$$

$$R'_{i1} = 18181.81 || 1163.64$$

$$R'_{i1} = 1093.64$$

$$A_{V1} = \frac{(-36.36)(15 \times 10^3)}{1093.64} = -498.7$$

$$R_o = R_{C2} = 330 \Omega$$

$$Y_o = \frac{1}{330} = 3.03 \times 10^{-3}$$

Simplified Model

$$A_{I2} = -h_{Fe} = -50$$

$$R'_{i2} = R_{b2} \parallel hie$$

$$R_{b2} = R_1 \parallel R_2 = \frac{470 \times 10^3 \times 470 \times 10^3}{470 \times 10^3 + 470 \times 10^3} = 23500$$

$$hie = 1.2 \times 10^3$$

$$R'_{i2} = \frac{23500 \times 1.2 \times 10^3}{23500 + 1.2 \times 10^3} = 1141.700$$

$$A_{V2} = \frac{A_{I2} R_{C2}}{R'_{i2}} = \frac{(-50)(4 \times 10^3)}{1141.700} = -175.177$$



$$R_o = 4 \times 10^3$$

1. Cascade Amp → CE-CE
CE-CC

2. Cascode Amp → CE-CB

3. Darlington Amp

1. Cascade Amplifier (CE-CC) +V_{CC}

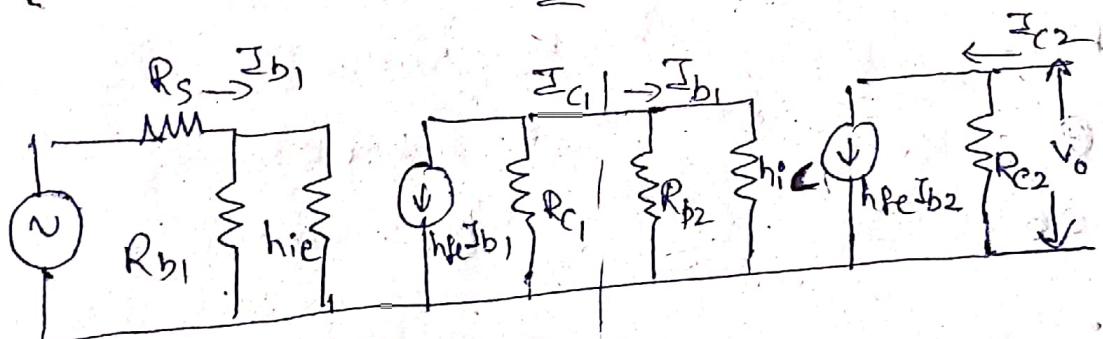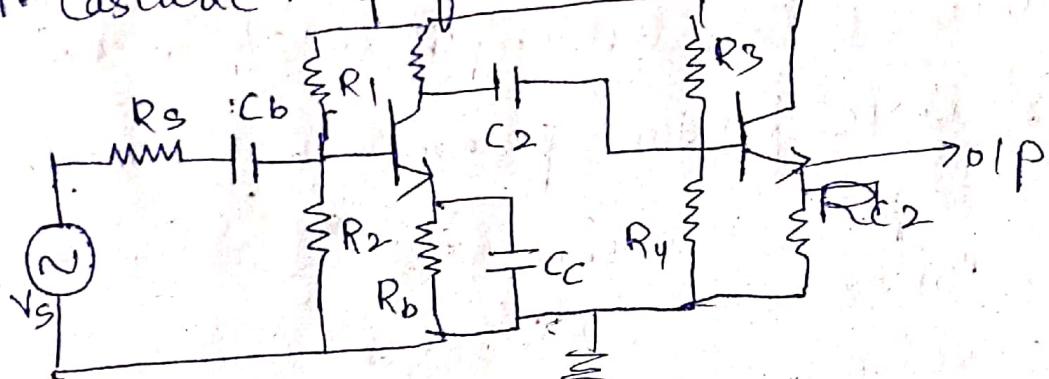

$$A_{I2} = -h_{fc}$$

$$A_{I1} = -h_{fc}$$

$$R_{i2}' = R_{b2} \| h_{ie} \quad R_{i1}' = R_{b1} \| h_{ie}$$

$$A_{V2} = \frac{A_{I2} R_C2}{R_{i2}'} \quad A_{V1} = \frac{A_{I1} R_C1}{R_{i1}'}$$

$$R_o = R_{C2}$$

$$R_o = R_{C1}$$

Note:-

① $R_L = R_{C1} \parallel R_{B2} \parallel h_{ie}$ (output stage of first resistance)

② $R_{C1} \parallel R_{B2} \parallel h_{ie} \rightarrow I/p$ of 2nd stage.

① For a CE-CE cascade amplifier find the A_v, A_I, R_i, R_o for the parameters given below

First stage

$$R_{C1} = 10k\Omega$$

$$R_1 = 20k\Omega$$

$$R_2 = 200k\Omega$$

$$R_{B1} = 10k\Omega$$

$$R_{S1} = 1k\Omega$$

$$h_{ie} = 1.2k\Omega$$

$$h_{re} = 2.5 \times 10^{-4}$$

$$h_{oe} = 25 \mu A/V$$

$$h_{fe} = 50$$

$$h_{oe} R_L = h_{oe} = 25 \mu A/V \quad R_L = R_{C2} = 5k\Omega$$

$$h_{oe} R_L = 25 \times 10^{-6} \times 5 \times 10^3$$

$$h_{oe} R_L = 0.125$$

$$h_{oe} R_L < 1$$

Approximation mode
 $h_{oe} R_L \ll 1$

$h_{oe} R_L \gg 1 \rightarrow$ exact model

$h_{oe} R_L \ll 1 \rightarrow$ Approx. model

we can use approximate model
Second stage Analysis

$$A_{I2} = -h_{fe} = -50$$

$$R_{i2}^e = h_{ie} = 1.2k\Omega$$

$$\text{Voltage gain } A_{v2} = \frac{A_{I2} R_{C2}}{R_{i2}^e}$$

$$= \frac{-50 \times 5 \times 10^3}{1.2 \times 10^3} = -208.3$$

$$\text{Output impedance } R_{o1} = R_{C1} = 10k\Omega$$

First stage Analysis:

$$\text{Current gain } A_{I1} = -h_{fe} \\ = -50$$

$$\text{Input impedance } R_{i1}^e = h_{ie} = 1.2k\Omega$$

$$A_{v1} = \frac{A_{I1} (R_{C1} \parallel R_b1 \parallel h_{ie})}{R_{i1}^e}$$

$$h_{oe} = R_{b1} = R_1 \parallel R_2$$

$$R_1 = 20k\Omega$$

$$R_2 = 200k\Omega$$

$$R_{C1} = 10k\Omega$$

$$h_{ie} = 1.2k\Omega$$

$$= \frac{-50 (10k\Omega \parallel 20k\Omega \parallel 200k\Omega \parallel 1.2k\Omega)}{1200}$$

$$= \frac{-50 \times 102.14}{1200}$$

$$A_{v1} = 42.14$$

⑧ Output impedance $R_{o2} = R_{c2} = 5k\Omega$

Overall voltage gain $A_v = A_{v1} A_{v2}$
 $= (208.3)(42.1)$

$$A_v = 8785.2$$

⑨ The CE-CC amplifier uses $R_s = 1k\Omega$, $R_C = 2k\Omega$,
 $R_{e2} = 1.2k\Omega$, the h-parameters are $h_{ie} = 1k\Omega$,
 $h_{fe} = 50$, $h_{re} = 1 \times 10^{-4}$, $h_{oc} = 10^4 \text{ A/V}$, $h_{ic} = 1k\Omega$,
 $h_{fe} = 50$, $h_{re} = 1$, $h_{oc} = 10^{-4} \text{ A/V}$. Compute

- Input impedance
- Output admittance
- A_I , A_v for individual stages
- Overall (A_I , A_v)

Sol: $A_{I2} = \frac{-h_{fe}}{1 + h_{oc}R_{e2}} = \frac{-51}{1 + 10^{-4} \times 1.2 \times 10^3}$

$$A_{I2} = -45.54$$

$$R_{i2} = h_{ic} + h_{oc} A_{I2} R_{e2}$$

$$R_{i2} = 1 \times 10^3 + (1 \times 45.54) \times 1.2 \times 10^3$$
$$= -53.64$$

$$A_{v2} = \frac{A_{I2} R_{e2}}{R_{i2}} = \frac{-45.54 \times 1.2 \times 10^3}{-53.6 \times 10^3}$$

$$A_{v2} = 1.018$$

$$R_{o1} = h_{oc} - \frac{h_{fe} h_{re}}{h_{ie} + R_s}$$

$$= 1 \times 10^{-4} - \frac{50 \times 10^{-4}}{1 \times 10^3 + 1 \times 10^3}$$

$$R_{o1} = 9.75 \times 10^{-5} \text{ A/V}$$

$$Y_{o1} = \frac{1}{R_{o1}} = \frac{1}{9.75 \times 10^{-5}}$$

$$Y_{o1} = 10.26 \text{ k}\Omega$$

First stage Analysis:-

The net load impedance R_{L1} of first stage is

obtained by

$$R_{e1} = R_{C1} \parallel R_{i2}$$

$$= \frac{2k \times 53.6k}{2k + 53.6k} = 1.92 \times 10^3$$

$$\text{Current gain } A_{I1} = \frac{-h_{fe}}{1 + h_{oc} R_{e1}}$$

$$= \frac{-50}{1 + 10^{-4} + 1.92k} = -41.91$$

$$R_{i1} = h_{ie} + h_{re} A_{I1} R_{e1}$$

$$= 1k + 10^{-4} \times -41.91 \times 1.93k$$

$$R_{i1} = 991.91$$

$$A_{V1} = \frac{A_{I1} R_{e1}}{R_{i1}} = \frac{-41.91 \times 1.93k}{991.91} = -81.5$$

$$\text{Output impedance} = h_{oc} - \frac{h_{fe} h_{re}}{R_s + h_{ie}}$$

$$= 10^{-4} - \frac{50 \times 10^{-4}}{10^3 + 10^3}$$

$$R_{o2} = 9.75 \times 10^{-5} \text{ A/V}$$

$$Y_{o2} = \frac{1}{R_{o2}}$$

$$= \frac{1}{9.75 \times 10^{-5}} = 10026 \text{ k}\Omega$$

*Effect of cascading of gain

In the earlier sections, gain of a single stage amplifier is computed. In this section, we will compute the overall gain for coupled amplifier using 'n' identical stages.

Let A_{mid} be the individual mid frequency gain of each stage, then overall mid frequency gain of n identical stages will be given by

$$|A_{mid}(\text{overall})| = |A_{mid}| \cdot |A_{mid}| \dots n \\ = |A_{mid}|^n$$

But gain in low-frequency region is given by,

$$A_{VL} = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}}$$

so, overall low frequency gain will be

$$\left| \frac{A_{VL}}{A_{mid}} \right|^n = \frac{1}{\left(\sqrt{1 + \left(\frac{f_L}{f}\right)^2} \right)^n}$$

$$\Rightarrow |A_{VL}|^n = \frac{|A_{mid}|^n}{\left[1 + \left(\frac{f_L}{f} \right)^2 \right]^{n/2}}$$

Hence, in general, the gain of a multistage

amplifier at any frequency below lower cut-off. Frequency can be computed using the above equation.

The overall gain of n identical multistage amplifier at any frequency is defined as

$$|A_{VH}|^n = \frac{|A_{mid}|^n}{\left[1 + \left(\frac{f}{f_H}\right)^2\right]^{n/2}}$$

CC

$$h_{ic} = h_{ie}$$

$$h_{fc} = -(1 + h_{fe})$$

$$h_{re} = 1$$

$$h_{oc} = \bullet h_{oe}$$

CB

$$h_{ib} = \frac{h_{fe}}{1 + h_{fe}}$$

$$h_{fb} = \frac{-h_{fe}}{1 + h_{fe}}$$

$$h_{rb} = \frac{h_{ie} h_{oe}}{1 + h_{fe}} - h_{re}$$

$$h_{ob} = \frac{h_{oe}}{1 + h_{fe}}$$

① Determine voltage gain, A_I , input resistance output resistance

$$R_S = 1k\Omega$$

$$R_C_1 = 8k\Omega$$

$$R_C_2 = 1.2k\Omega$$

h-parameter's

ce

$$h_{ie} = 1k\Omega$$

$$h_{fe} = 50$$

$$h_{fe} = 1 \times 10^{-4}$$

$$h_{oe} = 10^{-4} A/V \quad h_{rc} = 1$$

cc

$$h_{ie} = 1k\Omega$$

$$h_{fe} = 51$$

$$h_{rc} = 1$$

$$h_{oc} = 10^{-4} A/V$$

Q1: Second stage Analysis


$$\begin{aligned}
 A_{I2} &= \frac{-h_{fe}}{1 + h_{oe} R_{e2}} = \frac{1 + h_{fe}}{1 + h_{oe} R_{e2}} \\
 &= \frac{1 + 50}{1 + 10^{-4} (1.2 \times 10^3)} \\
 &= 45.53
 \end{aligned}$$

$$\begin{aligned}
 R_{i2} &= h_{ic} + h_{rc} A_{I2} R_{e2} \\
 &= h_{ie} + (1)(45.53)(1.2 \times 10^3) \\
 &= 1 \times 10^3 + (45.53)(1.2 \times 10^3) \\
 &= 55636
 \end{aligned}$$

$$\begin{aligned}
 AV_2 &= \frac{A_{I2} R_{L2}}{R_{i2}} \\
 &= \frac{(45.53) R_{e2}}{(55636)} = \frac{(45.53)(1.2 \times 10^3)}{55636} \\
 &= 0.982
 \end{aligned}$$

$$\begin{aligned}
 Y_o &= h_{oc} - \frac{h_{fe}h_{rc}}{R_s + h_{ie}} \\
 &= h_{oc} + \frac{(51)(1)}{10^3 + 10^3} \\
 &= 10^{-4} + \frac{51}{10^6} \\
 &= 0.0256
 \end{aligned}$$

* Cascode Amplifier [CE-CB]

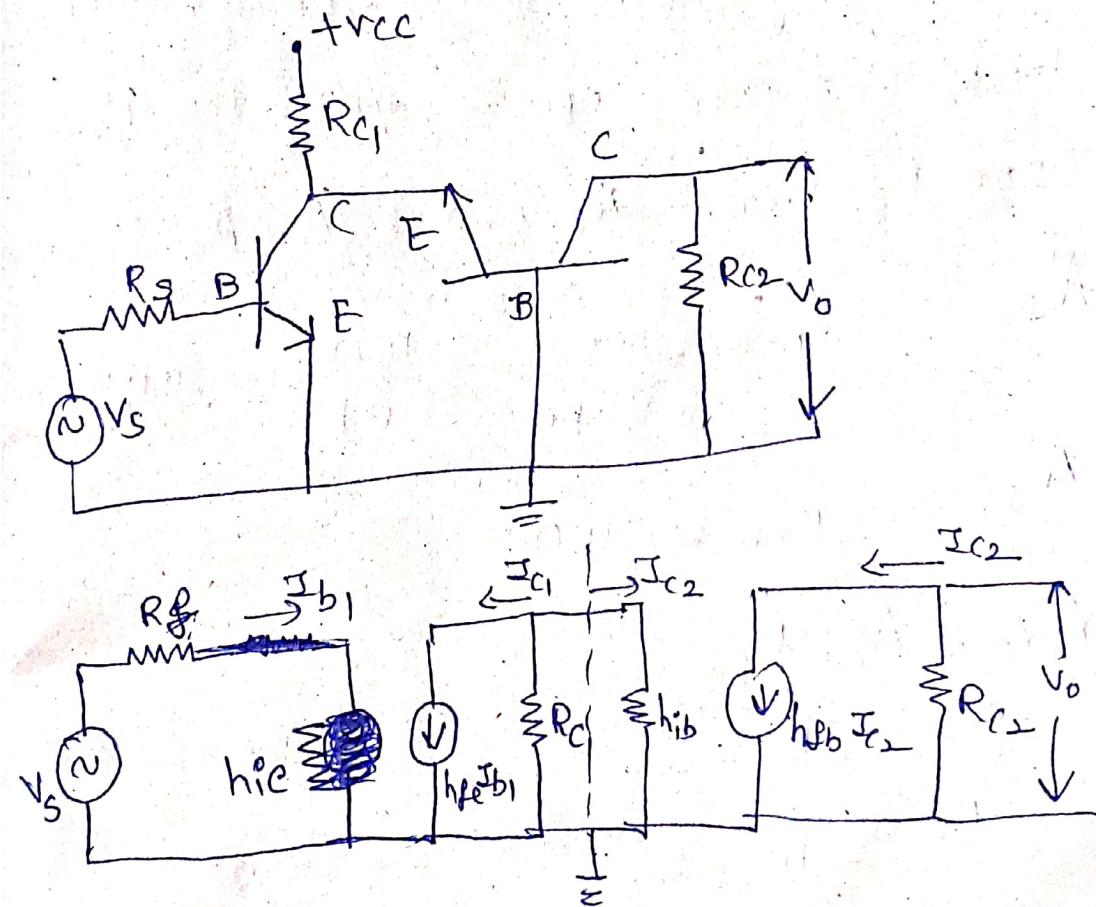

Second stage

$$A_i I_2 = -h_{fb} \quad R_{O2} = R_{C2} \rightarrow CB \text{ } h_{fb} \text{ value}$$

$$R_{i2} = h_{ib} \rightarrow CB \text{ } h_{ib} \text{ Val}$$

$$A_{V2} = \frac{A_{i2} \times R_{C2}}{R_{i2}} \rightarrow CB \text{ } h_{ib} \text{ Val}$$

First stage

$$A_{I_1} = -h_{FE} \Rightarrow A_{I_1} = -h_{FE} = \frac{h_{FE}}{1+h_{FE}}$$

$$R_{i_1} = h_{IE} \Rightarrow R_{i_1} = h_{IE} = \frac{h_{FE}}{1+h_{FE}}$$

$$A_{V_1} = \frac{A_{I_2} R_{C_1}}{R_{i_1}} \Rightarrow 1$$

$$R_o = R_{C_1} \parallel h_{OB}$$

① For the cascode Amplifier $R_C = 2.2$

$R_L = 2.7$ having transistors identical with $h_{IE} = 1.2k$ and $h_{FE} = 100$ neglecting the effect of R_1 and R_2 Derive overall (A_V, A_I)

$$A_{I_2} = -h_{FB} = \frac{h_{FE}}{1+h_{FE}} = \frac{100}{101} = 0.99$$

$$A_{I_1} = -h_{FE} = -100$$

$$A_{V_2} = \frac{A_{I_2} R_{C_2}}{R_{i_2}}$$

$$R_{i_2} = h_{OB} = \frac{h_{IE}}{1+h_{FE}} = \frac{1.2 \times 10^3}{1+100}$$

$$R_{i_2} = 11.88$$

$$(ORD) \quad A_{V_2} = \frac{(0.99)(2.2)}{11.88} = 0.183$$

Given

$$R_C = 2.2 \Omega$$

$$R_L = 2.4 \Omega$$

$$h_{ie} = 1.2 k\Omega$$

$$h_{fe} = 100$$

Second stage Analysis

$$A_{I2} = \frac{h_{fe}}{1+h_{fe}}$$

$$= \frac{100}{101} = 0.99$$

$$R_{i2} = \frac{h_{fe}}{1+h_{fe}} = \frac{100}{101} = 0.99$$

$$Av_2 = \frac{A_{i2} \times R_{C2}}{R_{i2}} = \frac{0.99 \times 2.2}{0.99} \\ = 2.2$$

$$R_{o2} = 2.2$$

First stage Analysis

$$A_{I1} = -h_{fe} = -100$$

$$R_{i1} = h_{ie} = 1.2 k\Omega$$


$$Av_1 = \frac{A_{I1} R_C}{R_{i1}} = \frac{-100}{1.2 \times 10^3} \times 2.2 = -0.183$$

$$R_o = R_C \parallel \frac{h_{fe}}{1+h_{fe}} = 2.2 \parallel 10.99 \\ = 1.3724$$

$$\begin{aligned}\text{Overall voltage gain} &= A_{V_2} \times A_{V_1} \\ &= 2.4 (-0.18) \\ &= -0.468\end{aligned}$$

$$\begin{aligned}\text{Overall current gain} &= A_{I_2} \times A_{I_1} \\ &= 0.99 \times (-100) \\ &= -99\end{aligned}$$

* Cascode Amplifier (CE-CE)

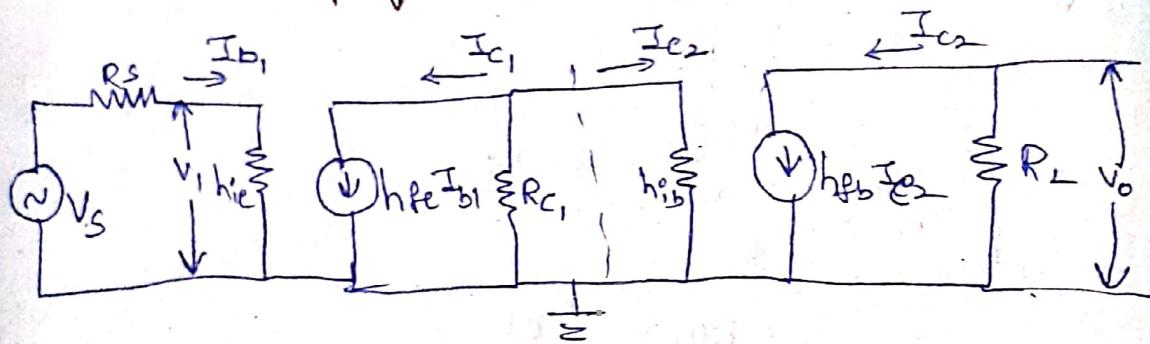

Voltage gain: $A_V = \frac{V_o}{V_i}$

$$V_o = I_o R_L$$

$$= -I_{C_2} R_L$$

$$V_o = -h_{fb} I_{C_2} R_L$$

$$I_2 = I_{C_1} \times \frac{R_{C_1}}{R_{C_1} + h_{ib}}$$

$$I_{C_2} = h_{fe} I_{b_1} \frac{R_{C_1}}{R_{C_1} + h_{ib}}$$

$$V_o = h_{fb} h_{fe} I_{b_1} R_{C_1} R_L$$

$$V_o = \frac{h_{fb} h_{fe} I_{b_1} R_{C_1} R_L}{R_{C_1} + h_{ib}}$$

$$V_i = I_{b1} h_{ie}$$

$$A_v = \frac{h_{fb} h_{fe} I_{b1} R_c R_L}{R_c + h_{ib}} / I_{b1} h_{ie}$$

$$= \frac{h_{fb} h_{fe} I_{b1} R_c R_L}{(R_c + h_{ib})(I_{b1} h_{ie})}$$

$$A_v = \frac{h_{fb} h_{fe} R_c R_L}{(R_c + h_{ib}) h_{ie}}$$

$$h_{fb} = \frac{h_{fe}}{1 + h_{fe}}$$

$$h_{fb} = \frac{-h_{fe}}{1 + h_{fe}}$$

$$= \frac{\left(\frac{-h_{fe}}{1 + h_{fe}}\right) h_{fe} R_c R_L}{\left(\frac{R_c + h_{fe}}{1 + h_{fe}}\right) h_{ie}}$$

$$= \frac{\frac{-h_{fe}}{1 + h_{fe}} h_{fe} R_c R_L}{\frac{R_c (1 + h_{fe}) + h_{fe}}{1 + h_{fe}} h_{ie}}$$

$$= \frac{-h_{fe} R_c R_L}{R_c + R_c h_{fe} + h_{fe} h_{ie}} = \frac{-h_{fe} R_c R_L}{R_c (1 + h_{fe}) + h_{ie}}$$

$$\text{Current gain: } A_I = \frac{I_o}{I_i}$$

$$A_I = \frac{-I_{e2}}{I_{b1}}$$

$$I_{e2} = -h_{fb} I_{c2}$$

$$I_{c2} = I_{c1} \times \frac{R_c}{R_c + h_{ib}}$$

$$I_{c2} = \frac{-h_{fe} I_{b1} R_c}{R_c + h_{ib}}$$

$$I_{c2} = \frac{-h_{fb} h_{fe} I_{b1} R_c}{R_c + h_{ib}}$$

$$A_I = \frac{-h_{fb} h_{fe} I_{b1} R_c}{R_c + h_{ib}}$$

$$A_I = \frac{-h_{fb} h_{fe} I_{b1} R_c}{(R_c + h_{ib}) I_{br}}$$

$$A_I = \frac{-h_{fb} h_{fe} R_c}{(R_c + h_{ib})}$$

* Frequency Analysis of CE Amplifier


① A Two Stage RC coupled Amplifier shown in the ckt find A_v , A_I , R_i , R_o

$$h_{ie} = 1.2 \text{ k}\Omega$$

$$h_{re} = 2.5 \times 10^{-4}$$

$$h_{oc} = 25 \mu\text{A/V}$$

$$\beta = 50$$

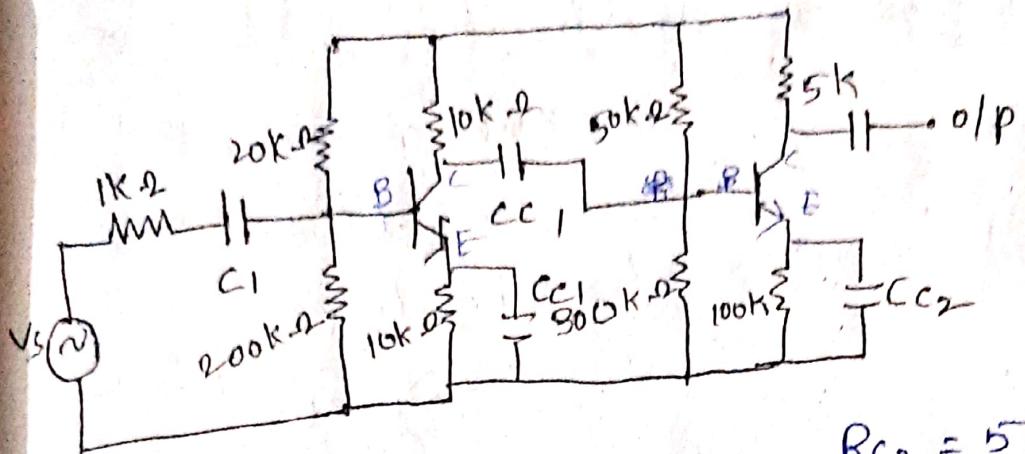

Second stage Analysis

$$A_{I2} = -h_{fe} = -50$$

$$R_{i2} = h_{ie} = 1.2k\Omega$$

$$R_{c2} = 5k\Omega$$

$$R_1 = 50k\Omega$$

$$R_2 = 300k\Omega$$

$$R_{e2} = 100k\Omega$$

$$AV_2 = \frac{A_{I2} R_{c2}}{R_{i2}}$$

$$= \frac{(-50)(5 \times 10^3)}{1.2 \times 10^3} = -208.3$$

$$R_{o2} = R_{c2} = 5 \times 10^3$$

First stage Analysis:-

$$A_{I1} = -h_{fe} = -50$$

$$R_{i1} = h_{ie} = 1.2k\Omega$$

$$AV_1 = \frac{A_{I1}(R_{c1} || R_{b1} || h_{ie})}{R_{i1}}$$

~~$$h_{oe} = R_{b1} = R_i || R$$~~

~~$$= \frac{-50(10k\Omega || 20k\Omega || 200k\Omega || 1.2k\Omega)}{1200}$$~~

$$AV_1 = 42.17$$

$$R_{o1} = R_{c1} = 10k\Omega$$

overall voltage gain $A_v = A_{v2} \cdot A_{v1}$

$$= 142.11 \cdot (200.3)(42.1)$$

$$\approx 8785.2$$

overall current gain $A_I = A_{I2} \cdot A_{I1}$

$$= (-50)(-50)$$

$$\approx 2500$$

* Frequency Response of an Amplifier

Effect of cascading on bandwidth

For a single stage amplifier the lower cut off frequency is given by

$$A_{VL} = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f_L}{f}\right)^2}} \quad \textcircled{1}$$

$A_{VL} \rightarrow$ Gain at low Frequency

$$A_{VH} = \frac{A_{mid}}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} \quad \textcircled{2}$$

$A_{VH} \rightarrow$ Gain at high frequency

* Considering multi stage amplifiers

(a) Lower cutoff frequency at 3dB

$$|A_{\text{mid}}|_{\text{overall}} = |A_{\text{mid}1}| \cdot |A_{\text{mid}2}| \cdots \cdot |A_{\text{mid}n}|$$

$$= |A_{\text{mid}}|^n$$

$$|A_n|^n = \frac{|A_{\text{mid}}|^n}{\left[1 + \left(\frac{f_L}{f} \right)^2 \right]^n}$$

$$\left| \frac{A_{VL}}{A_{\text{mid}}} \right|^n = \frac{1}{\left[1 + \left(\frac{f_L}{f} \right)^2 \right]^{n/2}}$$

$$\sqrt{\frac{1}{2}} = \frac{1}{\left[1 + \left(\frac{f_L}{f} \right)^2 \right]^{n/2}}$$

$$\left[1 + \left(\frac{f_L}{f} \right)^2 \right]^n = 2$$

$$1 + \left(\frac{f_L}{f} \right)^2 = 2^{1/n}$$

$$\left(\frac{f_L}{f} \right)^2 = 2^{1/n} - 1$$

$$\frac{f_L}{f_L(n)} = \sqrt{2^{1/n} - 1}$$

$$f_L(n) = \frac{f_L}{\sqrt{2^{1/n} - 1}} \rightarrow \textcircled{3}$$

(b) Higher cutoff frequency at 3 dB

$$|A_{vH}|^n = \frac{|A_{mid}|^n}{\left[1 + \left(\frac{f}{f_H} \right)^2 \right]^n}$$

$$\frac{|A_{vH}|^n}{|A_{mid}|} = \frac{1}{\left[1 + \left(\frac{f}{f_H} \right)^2 \right]^{n/2}}$$

$$\left(\frac{1}{\sqrt{2}} \right) = \frac{1}{\left[1 + \left(\frac{f}{f_H} \right)^2 \right]^{n/2}}$$

$$\left[1 + \left(\frac{f}{f_H} \right)^2 \right]^n = 2$$

$$1 + \left(\frac{f}{f_H} \right)^2 = 2^{1/n}$$

$$\left(\frac{f}{f_H} \right)^2 = 2^{1/n} - 1$$

$$\left(\frac{f}{f_H} \right)^2 = 2^{1/n} - 1 \Rightarrow \frac{f_H(n)}{f_H} = \left(\sqrt{2^{1/n} - 1} \right)$$

$$f_H(n) = f_H \left(\sqrt{2^{1/n} - 1} \right) \rightarrow ④$$

It is clearly observed from the above equations ③ & ④ the low frequency


will increased and the high frequency will decreased due to the bandwidth is decreased.

Distortion in Amplifiers

- Amplitude Distortion
- Frequency Distortion
- Phase Distortion

① Amplitude changes w.r.t time

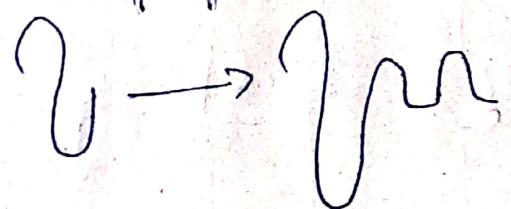
② we give one ilp the o/p get different types of cycles




③ change in angle is called phase distortion.

* Hybrid π -Model:-

CE amplifier:

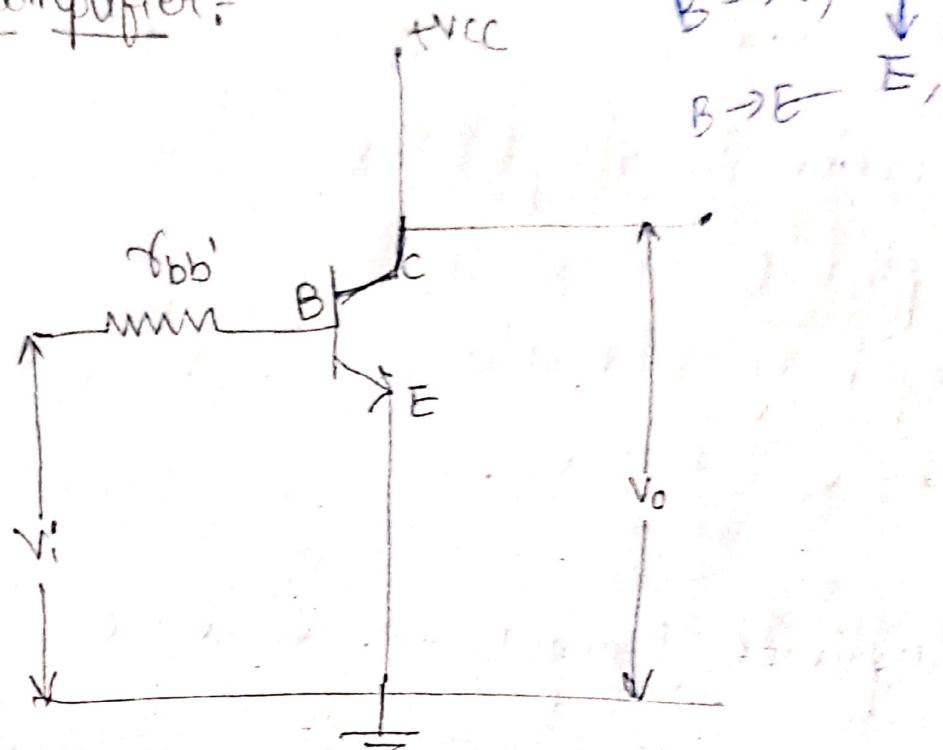


Low frequency

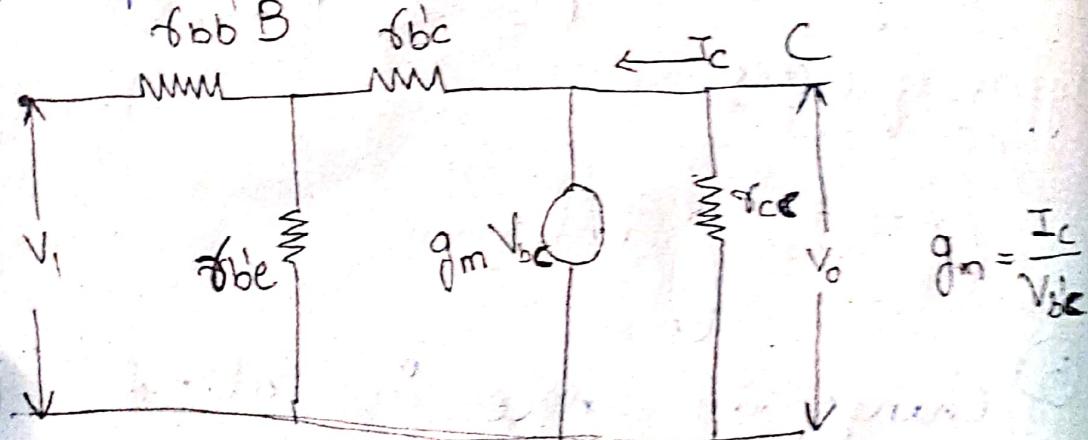


Low frequency \rightarrow only resistor

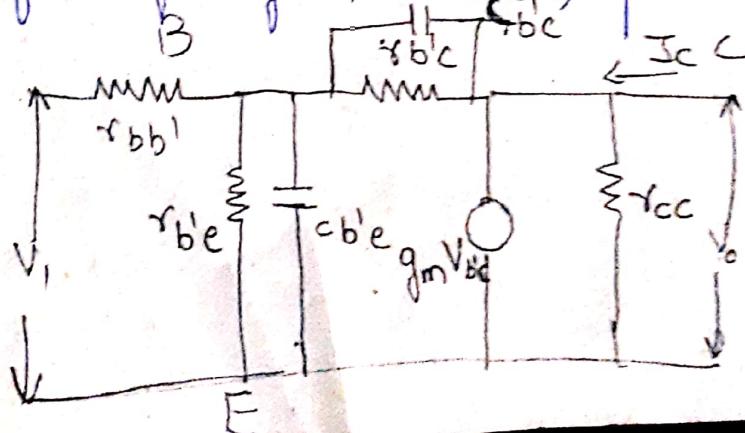High frequency \rightarrow resistor, capacitor



Base Spreading Resistance:

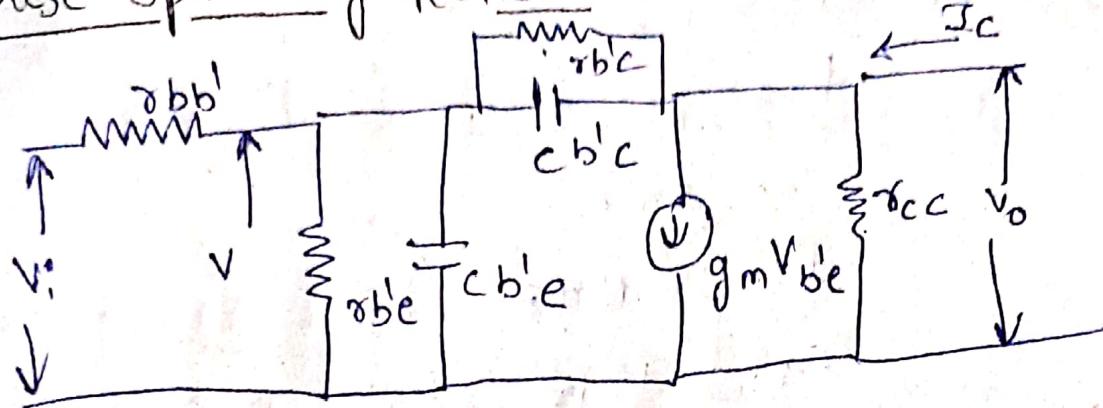

$$\textcircled{1} \quad r_{bb'} = h_{ie} - r_{be}$$

Input conductance:

$$g_{be} = \frac{g_m}{h_{fe}}$$

Feed back conductance:

$$g_{bc} = \frac{h_{re}}{r_{be}}$$

Output conductance:

$$g_{ce} = h_{oe} - g_m h_{re}$$

Collector Junction Capacitances $V_T = 26mV$

$$C_E = \frac{g_m}{2\pi f_T}$$

$$g_m = \frac{I_C}{V_T}$$

\textcircled{1} A BJT has $h_{ie} = 6k\Omega$, $h_{fe} = 224$, ~~but~~

$I_C = 1mA$ with $f_T = 80MHz$, $C_{bc} = 12pF$.

Determine

- (i) g_m (ii) r_{be} (iii) $r_{bb'}$ (iv) C_{be} at room temp & a collector current of 1mA.

Q2. Given $h_{ie} = 6k\Omega$

$$h_{fe} = 224$$

$$I_C = 1 \text{ mA}$$

$$f_T = 80 \text{ MHz}$$

$$C_{b'e} = 12 \text{ pF}$$

$$(i) g_m = \frac{I_C}{V_T} = \frac{1 \times 10^{-3}}{26 \times 10^3} = 0.03$$

$$(ii) \gamma_{b'e} = \frac{h_{fe}}{g_m} = \frac{224}{0.03} = 5894.43$$

$$(iii) \gamma_{bb'} = h_{ie} - \gamma_{b'e}$$
$$= 6 \times 10^3 - 5.89 \times 10^3$$
$$= 0.11 k\Omega$$

$$(iv) C_{b'e} = CE = \frac{g_m}{2\pi f_T} = \frac{0.03}{2\pi \times 80 \times 10^6}$$
$$= 4.563 \times 10^{-11}$$

Reasonable values of CE and $C_{b'e}$ are
3 pF & 100 pF respectively.

The following low frequency parameters
are known ^{for a given transistor} at $I_C = 10 \text{ mA}$, $h_{ie} = 500 \Omega$

$$h_{fe} = 100, I_C = 10 \text{ mA}, f_T = 50 \text{ Hz}, h_{oe} = 10^{-5}$$

$$V_{ce} = 10 \text{ V}, h_{re} = 10^{-4}, C_{ob} = 3 \text{ pF}$$

Find hybrid π -model parameters.

$$\text{Q1. } g_m = \frac{2I_c}{V_T} = \frac{10 \times 10^{-3}}{26 \times 10^{-3}} = 0.38$$

$$g_{b'e} = \frac{g_m}{8\pi f_T} = \frac{0.38}{8\pi \times 50} = 1.22 \text{ mF}$$

$$g_{be} = \frac{g_m}{h_{fe}} = \frac{0.38}{100} = 3.8 \times 10^{-3} = 3.8 \text{ mA}$$

$$g_{b'c} = \frac{h_{re}}{\gamma_{b'e}} = \frac{10^{-4}}{263.15} = 3.80 \times 10^{-7}$$

$$\gamma_{b'e} = \frac{h_{fe}}{g_m} = \frac{100}{0.38} = 263.15$$

$$g_{ce} = h_{oe} - g_m h_{re}$$

$$= 10^{-5} - (0.38)(10^{-4})$$

$$= -2.8 \times 10^{-5}$$



$$\begin{aligned}\gamma_{bb'} &= h_{ie} - \gamma_{b'e} \\ &= 500 - 263.15 \\ &= 236.85\end{aligned}$$

$$C_{ob} \rightarrow I_o$$

* Miller's Theorem

Statement: In any linear bilateral two port network, if an impedance Z is connected between the input and output terminal of the network with a voltage gain A_v , an equivalent ckt that gives the same effect can be drawn by removing Z and connecting an impedance ~~at~~ the o/p and connecting an impedance ~~at~~ the i/p
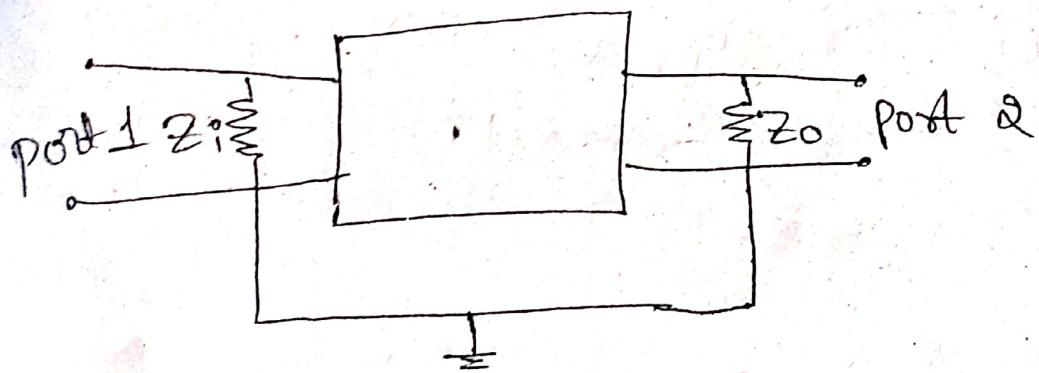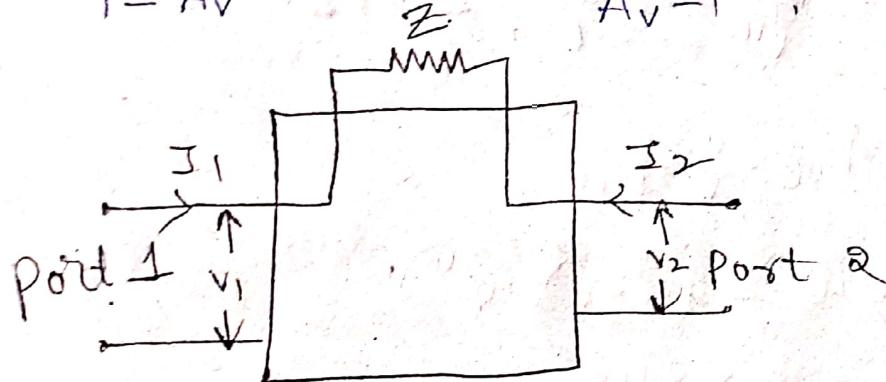
$$Z_i = \frac{Z}{1 - A_v} \quad \text{and} \quad Z_o = \frac{Z A_v}{A_v - 1} \quad \text{across the o/p}$$




~~$$K_1 = \frac{\gamma b' c}{1 - A_v}$$~~



~~$$K_1' = \frac{\gamma b' c A_v}{A_v - 1}$$~~

~~$$K_2 = \frac{\gamma b' c}{1 - A_v}$$~~
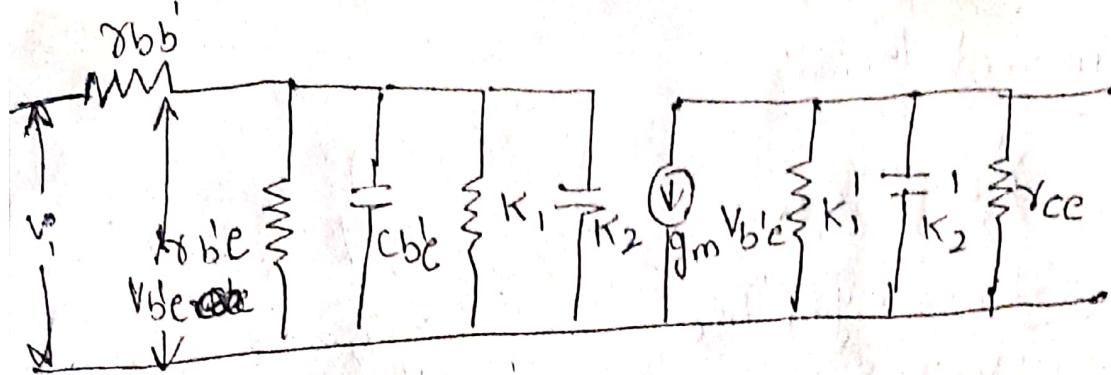
$$K_2' = \frac{\gamma b' c A_v}{A_v - 1}$$



CE short ~~kt~~ current gain :-

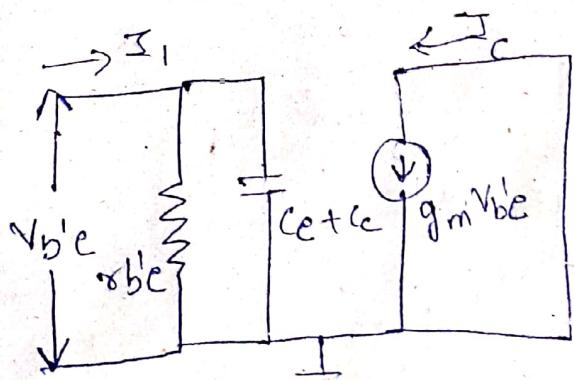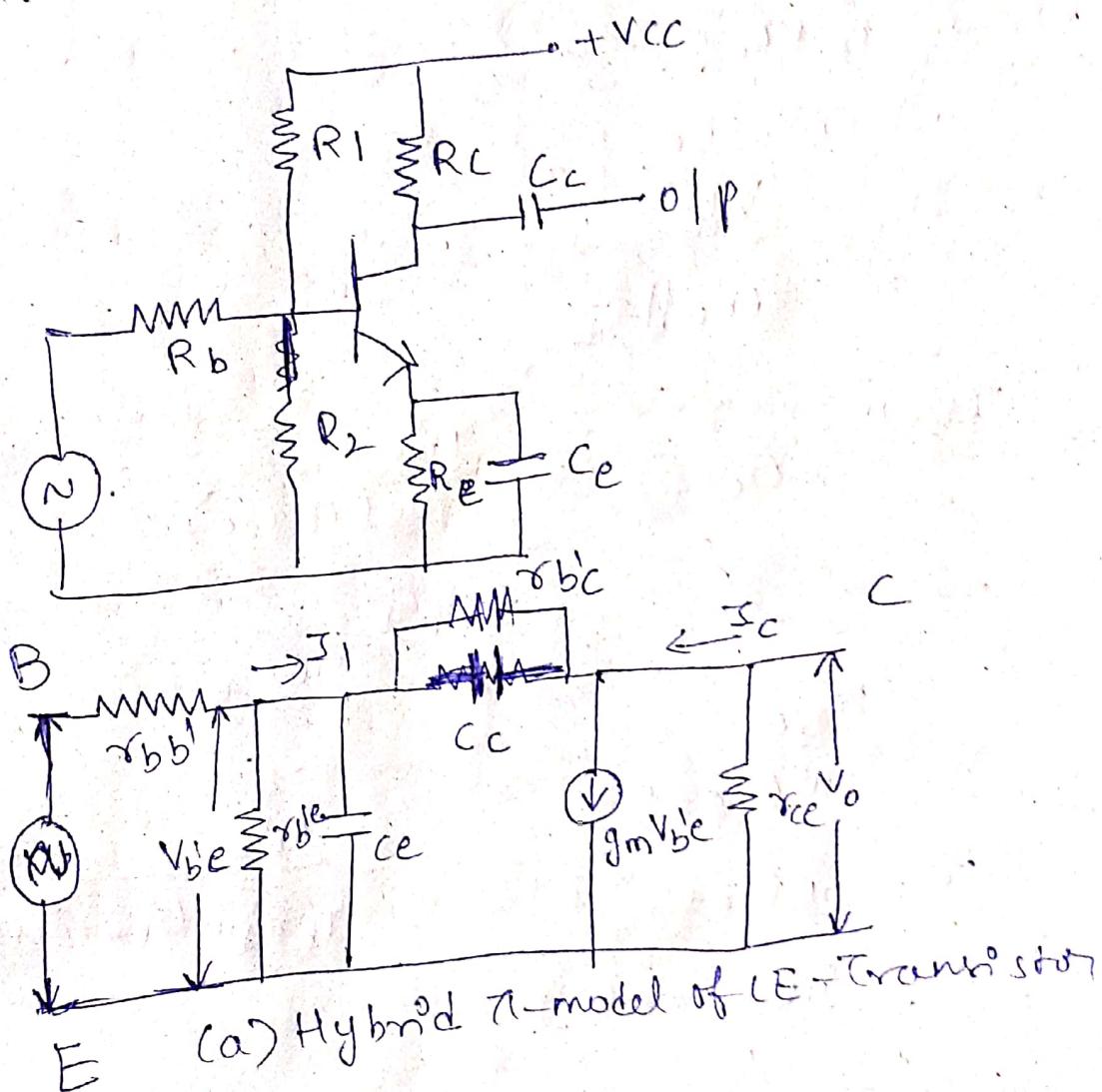

(b) Approximation model

* Current Gain:

$$A_I = \frac{I_1}{I_1}$$

$$I_C = g_m V_{BE}$$

$$V = IR$$

$$V_{BE} = I_1 \times \gamma_{BELL} \frac{1}{j\omega C}$$

$$C = C_E + C_C$$

$$\gamma_{BELL} + C_{BELL}$$

$$I_1 = \frac{V_{BE}}{\gamma_{BELL} \frac{1}{j\omega(C_E + C_C)}}$$

$$\gamma_{BELL} \frac{1}{j\omega(C_E + C_C)} = \frac{\gamma_{BE}}{j\omega(C_E + C_C)}$$

$$\gamma_{BE} + \frac{1}{j\omega(C_E + C_C)}$$

$$= \frac{\gamma_{BE}}{j\omega(C_E + C_C)}$$

$$= \frac{\gamma_{BE}}{\gamma_{BE} j\omega(C_E + C_C) + 1}$$

$$I_1 = \frac{V_{BE}}{\gamma_{BE} j\omega(C_E + C_C) + 1}$$

$$I_1 = \frac{V_{BE} [\gamma_{BE} j\omega(C_E + C_C) + 1]}{\gamma_{BE}}$$

$$V_{be} = \frac{I_1 \gamma_{be}}{\gamma_{be} j\omega (C_e + C_c) + 1}$$

$$I_c = -g_m V_{be}$$

$$I_c = -g_m \left[\frac{I_1 \gamma_{be}}{\gamma_{be} j\omega (C_e + C_c) + 1} \right]$$

$$-\frac{I_c}{I_1} = \frac{g_m \gamma_{be}}{\gamma_{be} j\omega (C_e + C_c) + 1}$$

$$A_I = \frac{g_m \gamma_{be}}{\gamma_{be} j\omega (C_e + C_c) + 1}$$

$$A_I = \frac{-h_f}{1 + h_f j \omega (C_e + C_c)}$$

where $\omega_B = \frac{1}{\gamma_{be} (C_e + C_c)}$, $f_B = \frac{1}{2\pi \gamma_{be} (C_e + C_c)}$

$$A_I = \frac{-h_f e}{1 + j \left(\frac{\omega}{\omega_B} \right)}$$

$$= \frac{-h_f e}{1 + j \left(\frac{f}{f_B} \right)}$$

$f_B \rightarrow$ cutoff frequency

* f_R (cutoff Frequency for CE)

$$A_I = \frac{I_2}{I_1}$$

$$= \frac{-h_{FE}}{1 + j\left(\frac{f}{f_P}\right)}$$

$$f_R = \frac{1}{2\pi \gamma b'e(1+h_{FE})C_{BE}}$$

$$f_2 = \frac{h_{FE}}{2\pi \gamma b'e C_{BE}}$$

$$f_P = \frac{1}{2\pi \gamma b'e (C_{BE} + C_C)}$$

~~$$A_I = \frac{I_2}{I_1} = \frac{-h_{FE}}{1 + j\left(\frac{f}{f_P}\right)}$$~~

$$f_2 = \frac{f \cdot C_{BE}}{h_{FE} (C_B + C_C)}$$

$$f_2 = \frac{h_{FE} f_P (C_B + C_C)}{C_{BE} \text{ or } C_C}$$

* f_T (unity gain frequency)

when the ^{want} gain tends to be unity..

we have $|A_I| = \left| \frac{h_{FE}}{1 + j^w \left(\frac{f}{f_P} \right)} \right|$

$$2) A_I = \frac{h_{FE}}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}$$

$$A_I = 1, \frac{f}{f_B} \gg 1, f = f_T$$

$$1 = \frac{h_{FE}}{\frac{f_T}{f_B}} \Rightarrow \frac{f_T}{f_B} = h_{FE}$$

$$\therefore \boxed{f_T = h_{FE} f_B}$$

① The following data for the parameters of

BJT $I_c = 2\text{mA}$, $V_{ce} = 10\text{V}$ at room temp

calculate $h_{FE} = 15$, $f_T = 15\text{MHz}$, $C_{b'e} = 3\text{pF}$

g_m , $\gamma_{b'e}$, f_B , f_α and C_{ble}

② If short circled $A_I = 50$ CE amplifier at frequency of 5MHz , $f_B = 1\text{MHz}$, calculate

f_T , h_{FE}

~~$$Q) g_m = \frac{I_c}{V_T} = \frac{2 \times 10^{-3}}{26 \times 10^{-3}} = 0.076$$~~

$$\gamma_{b'e} = \frac{h_{FE}}{g_m} = \frac{15}{0.076} = 197.3$$

$$C_{ble} = \frac{g_m}{2\pi f_T} = \frac{0.076}{2\pi \times 15 \times 10^6} = 8.06 \times 10^{-10}$$

$$f_B = \frac{1}{2\pi(197.36)(8.06 \times 10^{-10} + 3 \times 10^{-12})}$$

$$= 196830245.7$$

$$f_Q = \frac{h_{fe} f_B (C_e + C_c)}{C_{be}}$$

$$f_Q = \frac{(15)(196830245.7)(8.06 \times 10^{-10} + 3 \times 10^{-12})}{8.06 \times 10^{-10}}$$

$$f_Q = 296344614.9$$

Derive, A_I (current gain), voltage gain, I_{fp}
 Resistance, o/p. Resistance of Darlington pair.

Ques: Given

$$A_I = 50$$

$$f = 5 \times 10^6 \text{ Hz}$$

$$f_B = 10^6 \text{ Hz}$$

$$A_I = \frac{h_{fe}}{\sqrt{1 + \left(\frac{f}{f_B}\right)^2}}$$

$$50 = \frac{h_{fe}}{\sqrt{1 + \left(\frac{5 \times 10^6}{10^6}\right)^2}}$$

$$50 = \frac{h_{FE}}{\sqrt{1+25}}$$


$$50\sqrt{25} = h_{FE}$$

$$h_{FE} = 254.950$$

$$\begin{aligned}f_T &= h_{FE} f_B \\&= (254.950)(10^6)\end{aligned}$$

$$f_T = 254950 \text{ mA}$$

* Darlington pair

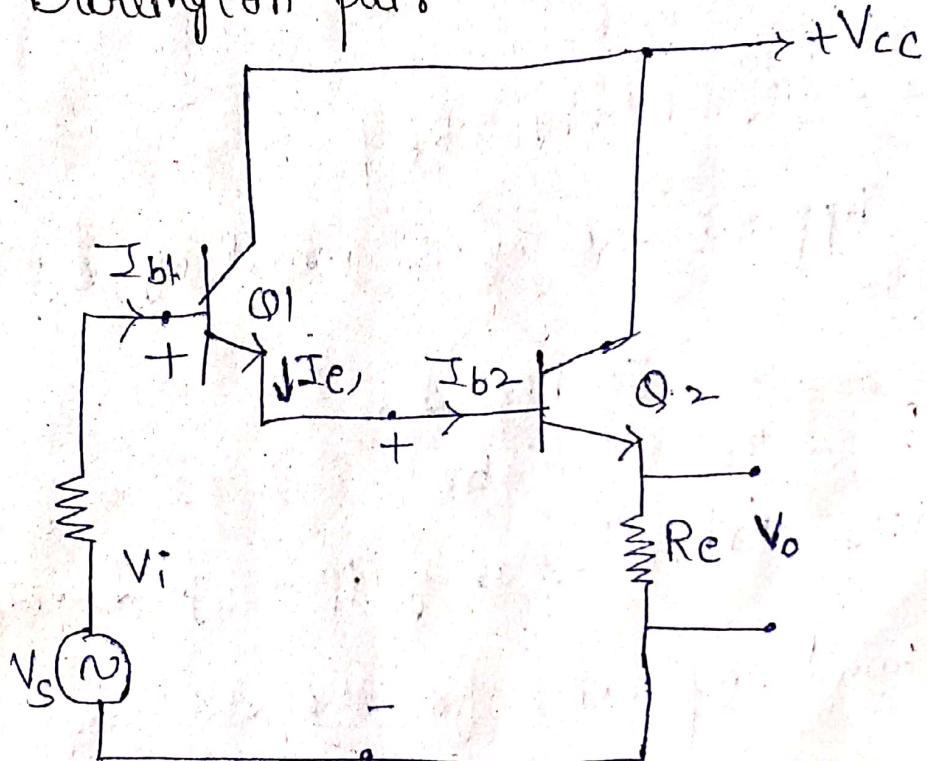

A single stage Emitter follower (Common Collector Amplifier) can produce current gain and input impedance i.e.; large in comparison to CB & CE configuration.

To increase that current gain and input

impedance further, we can connect Emitter followers in cascade such a cascaded condition is known as Darlington pair.

The purpose of darlington dt is to ↑ the current gain & i/p impedance

$$Z_{i2} = \text{Input impedance} = \frac{V_{b2}}{I_{b2}}$$

of second stage

$$Z_{i2} = \frac{h_{ie} I_{b2} + (1+h_{fe}) I_{b2} R_e}{I_{b2}}$$

$$Z_{i2} = h_{ie} + (1+h_{fe}) R_e$$

From Approximate hybrid model of CE amplifier

$$A_{I2} = \frac{I_{e2}}{I_{b2}} = \frac{(1+h_{fe}) I_{b2}}{I_{b2}}$$

$$A_{I2} = 1+h_{fe} \rightarrow \text{using Approx hybrid model}$$

The load impedance for the 1st stage is


Z_{L1}

$$Z_{L1} = Z_{i2} || \infty = Z_{i2}$$

Since the condition $h_{oe} Z_L > 10 \cdot 1$, we cannot use the Approximate hybrid model there whose the analysis of 1st stage.

Therefore Exact hybrid model have to used.

other
conditions

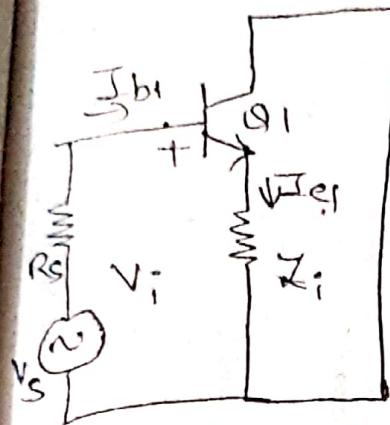

First stage of i/p impedance inverter

$$Z_{i1} = h_{ie} + h_{re} A_I \times Z_{i2}$$

$$h_{re} = 1 - h_{fe}$$

$$h_{re} \ll 1$$

$$h_{re} \approx 1$$

$$Z_{i1}^o = h_{ie} + A_I Z_{i2}$$

$$Z_{i1}^o = h_{ie} + A_I [h_{ie} + (1 + h_{fe}) R_E]$$

$$A_I = \frac{I_{c1}}{I_{b1}} = \frac{-h_{fe}}{1 + h_{oc} Z_{i2}} = \frac{(1 + h_{fe})}{1 + h_{oc} [h_{ie} + (1 + h_{fe}) R_E]}$$

$$A_I = \frac{1 + h_{fe}}{1 + h_{ie} h_{oc} + h_{oc} (1 + h_{fe}) R_E} \rightarrow \textcircled{2}$$

$$Z_{i1}^o = h_{ie} + \frac{(1 + h_{fe}) [h_{ie} + (1 + h_{fe}) R_E]}{1 + h_{ie} h_{oc} + h_{oc} (1 + h_{fe}) R_E}$$

$$(1 + h_{fe}) R_E \gg h_{ie}$$

$$h_{oc} (1 + h_{fe}) R_E \gg h_{ie} h_{oc}$$

$$Z_{i1}^o = h_{ie} + \frac{(1 + h_{fe})(1 + h_{fe}) R_E}{1 + h_{oc} (1 + h_{fe}) R_E}$$

$$Z_{i1}^o = h_{ie} + \frac{(1 + h_{fe})^2 R_E}{(1 + h_{oc} (1 + h_{fe})) R_E}$$

$$Z_{i1}^o \approx (1 + h_{fe})^2 R_E$$

$$Z_{i1}^o \approx h_{fe}^2 R_E$$

The overall current gain

$$A_I = \frac{I_{e2}}{I_{b1}}$$

$$A_I = \frac{I_{e2}}{I_{b2}} \times \frac{I_{b2}}{I_{b1}} \quad | I_{b2} = I_e$$

$$A_I = \frac{I_{e2}}{I_{b2}} \times \frac{I_{e1}}{I_{b1}}$$

$$A_I = A_{I_2} \times A_I$$

$$A_I = (1+h_{fe})^2$$
$$R_i = h_{fe} R_e$$

$$A_I = \frac{(1+h_{fe})(1+h_{fe})}{1+h_{fe}h_{oe} + (1+h_{fe})h_{oe}R_e}$$

More than two stages of darlington connection is not used practically because the reverse saturation current at the final stage will be very high which will make the Amplifier stage unstable.

* Gain Bandwidth products:-

(2M) Gain Bandwidth product for voltage:- (GBWVp)

It is the product of Amplifier B.W and the gain in which the B.W is measured.

→ The GBWVp is given by

$$A_{VS(\text{low})} \times f_H = \frac{h_{FE} R_L}{R_S + h_{IE}} \times \frac{1}{2\pi R_{EQ} C_{EQ}}$$


~~A_{VS}~~ \rightarrow overall voltage gain

* Note: $A_{VS} = \frac{h_{FE} R_L}{R_S + h_{IE}}$

$$f_H = \frac{1}{2\pi R_{EQ} C_{EQ}} \quad h_{FE} = g_m \gamma_{b'e}$$

where $R_{EQ} = \gamma_{b'e} \| (\gamma_{bb'} + R_S)$ and $h_{IE} = \gamma_{bb'} + \gamma_{b'e}$

$$C_{EQ} = C_E + C_C [1 + g_m R_L]$$

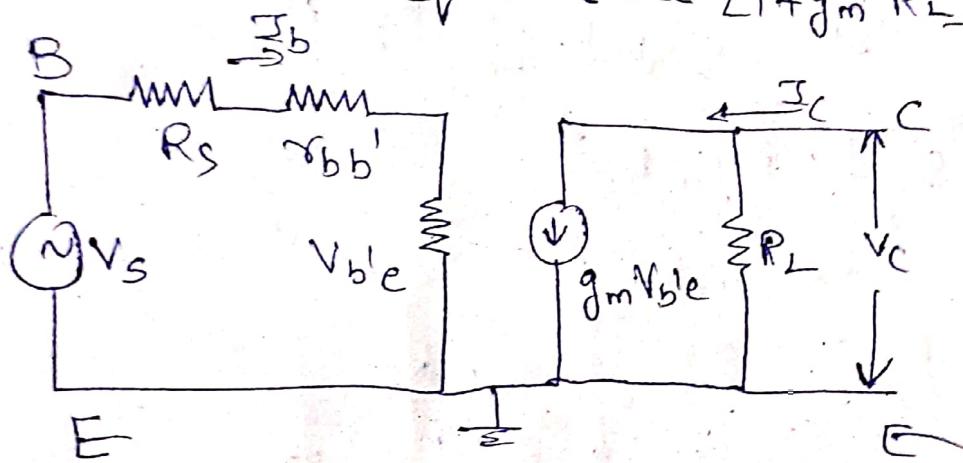

$$\gamma_{b'e} \| (\gamma_{bb'} + R_s) = \frac{\gamma_{b'e} (\gamma_{bb'} + R_s)}{\gamma_{b'e} + \gamma_{bb'} + R_s}$$

$$= \frac{h_{FE} R_L}{R_S + h_{IE}} \times \frac{1}{2\pi C_{EQ} \left[\frac{\gamma_{b'e} (\gamma_{bb'} + R_s)}{\gamma_{b'e} + \gamma_{bb'} + R_s} \right]}$$

$$= \frac{h_{FE} R_L}{R_S + h_{IE}} \times \frac{R_S + h_{IE}}{2\pi C_{EQ} \gamma_{b'e} (\gamma_{bb'} + R_s)}$$

$$= \frac{h_{fe} R_L}{R_s + r_{bb}'}$$

$$= \frac{g_m \times h_{fe} (r_{bb}' + R_s)}{R_s + r_{bb}'}$$

$$= \frac{g_m \cancel{h_{fe}} R_L}{R_s + r_{bb}'}$$

$$= \frac{g_m \times h_{fe} (r_{bb}' + R_s)}{R_s + r_{bb}'}$$

$$= \frac{g_m}{2\pi C_{eq}} \cdot \frac{R_L}{(R_s + r_{bb}')}$$

$$= \frac{g_m}{2\pi [C_e + C_C (1 + g_m R_L)]} \cdot \frac{R_L}{R_s + r_{bb}'}$$

$$\leftarrow C_C [1 + g_m R_L]$$

$$= C_C g_m R_L$$

$$= \frac{g_m}{2\pi [C_e + C_C g_m R_L]} \cdot \frac{R_L}{R_s + r_{bb}'}$$

$$\text{where } f_T = \frac{g_m}{2\pi C_e}$$

$$g_m = f_T 2\pi C_e$$

$$= \frac{f_T 2\pi C_e}{2\pi [C_e + C_C (f_T 2\pi C_e)]} \cdot \frac{R_L}{R_s + r_{bb}'}$$

$$= \frac{\cancel{f_T 2\pi C_e}}{2\pi C_e [1 + f_T C_e R_L]} \cdot \frac{R_L}{R_s + r_{bb}'}$$

$$A_{VS(\text{low})} \times f_H = \frac{f_T}{R_s + R_L + r_{bb}}$$

$$= \frac{f_T 2\pi C_e}{2\pi C_c f_T 2\pi C_e R_s + r_{bb}} \cdot \frac{R_L}{R_s + r_{bb}}$$

$$= \frac{2\pi C_e \cdot f_T}{2\pi C_c [1 + 2\pi C_c f_T R_s]} \cdot \frac{R_L}{R_s + r_{bb}}$$

$$\boxed{A_{VS(\text{low})} \times f_H = \frac{f_T}{[1 + 2\pi C_c f_T R_s]} \left(\frac{R_L}{R_s + r_{bb}} \right)}$$

* Grain Bandwidth ^{product} for current.

The GBWIP is given by

$$A_{IS(\text{low})} \times f_H = \frac{h_{fe} R_s}{R_s + r_{thie}} \times \frac{R_L}{2\pi R_E C_E}$$

$$A_{IS(\text{low})} \times f_H = \left(\frac{f_T}{1 + 2\pi f_T C_E R_S} \right) \left(\frac{R_s}{R_s + r_{bb}} \right)$$


UNIT-2 Feedback Amplifiers:

* Block diagram of feedback Amplifier

which strengthens the
Amplifier \rightarrow weak signals to high
signals

Feedback Amplifier \rightarrow The o/p of the
amplifier is connected back to the i/p.
is known as feed back

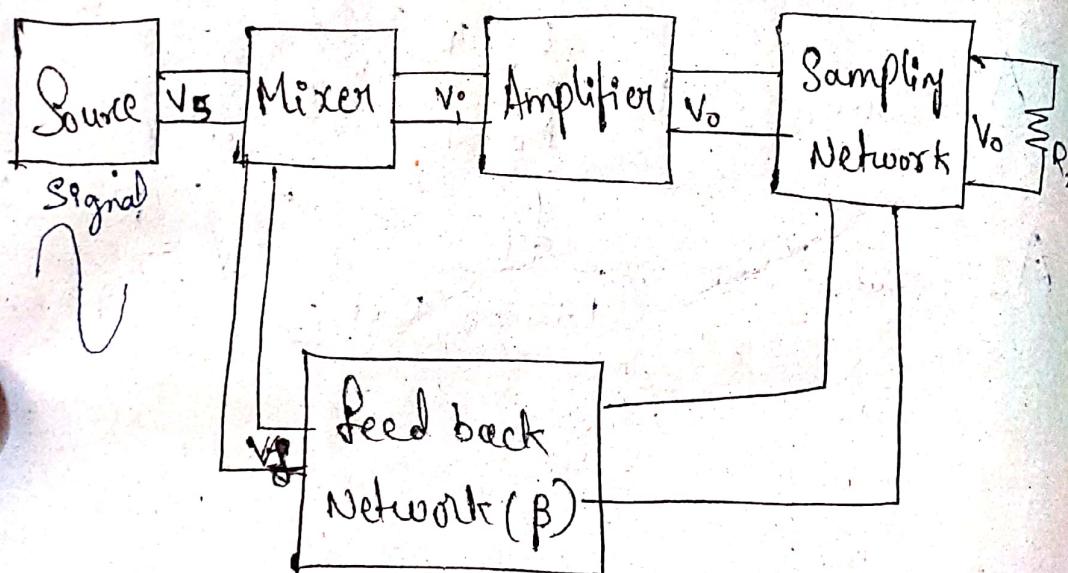Purposes - To reduce the noise and distortion



$A_v / A_T / A$ gain of open loop

$$A_v = \frac{V_o}{V_s}$$

$$A_f = \frac{V_o}{V_s} \quad (\text{gain in feed / closed loop})$$

$$\text{Feed back ratio } \beta = \frac{V_f}{V_o}$$

Types of Feed back amplifiers

1. Negative feed back

2. positive feed back

* Positive feed back amplifier:-

If source signal & feed back signal both are in phase it is called positive feed back amplifier.

* Negative feed back amplifier:-

out of phase with each other

* positive feed back:-

$$V_i^o = V_s + V_f$$

$$\beta = \frac{V_f}{V_o}$$

$$\beta = \frac{V_f}{V_o}$$

$$V_s = V_i^o - V_f$$

$$V_f = \beta V_o$$

$$= V_i^o - \beta V_o$$

$$V_s = V_i^o - \beta A V_i^o$$

$$\frac{V_s}{V_o} = \frac{V_f(1 - \beta A)}{V_o}$$

$$\frac{1}{A_f} = \frac{1 - \beta A}{A}$$

$$A_f = \frac{A}{1 - \beta A}$$

If $A\beta = 1$

$$A_f = \frac{A}{1+A}$$

$$A_f = \frac{A}{0} = \infty$$

If Gain $\rightarrow \infty$ then ckt will be acts as an oscillator.

Disadvantages:-

\rightarrow B.W decreases, Gain increases, noise decreases and Distortion increases.

* Negative feed back

\rightarrow If Source signal and feed back signal out of phase is known as negative feed back amplifier.

$$V_o = V_s - V_f$$

$$V_s = V_i + V_f$$

$$= V_i + \beta V_o$$

$$= V_i + \beta A V_i$$

$$\frac{V_s}{V_o} = \frac{V_i(1+\beta A)}{V_o}$$

$$\frac{1}{A_f} = \frac{1+A\beta}{A}$$

$$A_f = \frac{A}{1+A\beta}$$

If $A\beta = 1$

$$A_f = \frac{A}{2}$$

Gain \rightarrow finite

Advantages:

- B.W increases
- Gain ~~decreases~~ finite
- Noise decreases
- Distortion decrease

* Sensitivity:

We know that $\text{ve feed back gain } \frac{v_u - u_v}{v_u}$

given by $A_f = \frac{A}{1+A\beta} \rightarrow ①$

diff eq ① w.r.t A

$$\begin{aligned}\frac{\partial A_f}{\partial A} &= \frac{\partial}{\partial A} \left[\frac{A}{1+A\beta} \right] \\ &= \frac{1}{(1+A\beta)^2}\end{aligned}$$
$$\begin{aligned}u &= \frac{(1+A\beta \times 1) - (A)(\beta)}{(1+A\beta)^2} \\ v &= \frac{1+A\beta - A\beta}{(1+A\beta)^2}\end{aligned}$$

$$\frac{\partial A_f}{\partial A} = \frac{1}{(1+A\beta)^2}$$

$$= \frac{1}{(1+A\beta)} \cdot \frac{1}{(1+A\beta)} \times \frac{A}{A}$$

$$\frac{\partial A_f}{\partial A} = \frac{A}{(1+A\beta)} \cdot \frac{1}{1+A\beta} \cdot \frac{1}{A}$$

$$\frac{\partial A_f}{\partial A} = A_f \cdot \frac{1}{(1+AB)} \cdot \frac{1}{A}$$

$$\frac{\partial A_f}{A_f} = \frac{\partial A/A}{1+AB}$$

$$\frac{\partial A_f/AB}{\partial A/A} = \frac{1}{1+AB}$$

$$S = \frac{1}{1+AB}$$

$$D_S = 1+AB$$

- ① Calculate the gain of a -ve feedback amplifier, with an internal gain 100 and feedback collector 1/10.

$$A_f = \frac{A}{1+AB}$$

Internal Gain $A = 100$

$$\beta = \frac{1}{10} = 0.1$$

$$A_f = \frac{100}{1+100(0.1)} = 9.090$$

- ② An amplifier with -ve feed back has a voltage gain of 100 if it is found that without feedback an input signal of 50mV is

required to produce a gain output, ~~without feedback~~
 whereas with feedback, the o/p signal must
 be 0.6V for the same o/p calculate the
 value of A & B.

$$\log \frac{6}{10}$$

$$A_f = 100$$

$$V_i = 50 \text{ mV}$$

$$V_s = 0.6 \text{ V} \quad V_o = A_f V_s = 60 \text{ V}$$

$$A_f = \frac{V_o}{V_s} = \frac{1200}{1 + (200) \left(\frac{V_f}{60} \right)} \Rightarrow V_f$$

$$\therefore V_o = (100)(0.6) = 100 = 0.55$$

$$V_o = 60 \text{ V} \quad 9.16 \text{ mA}$$

$$\beta = \frac{V_f}{V_o} = \frac{\cancel{50 \times 10^3} \pm 1200}{\cancel{60}} = 0.33 \times 10^{-4} = 0.83 \text{ mA}$$

$$A = \frac{60}{50 \times 10^3} = 1200$$

- ③ An amplifier has a open loop gain of 100 and feed back ratio of 0.04. If the open loop gain changes by 10%. Due to temperature, find the percentage change in gain of the amplifier with feedback.

$$\beta = 0.04$$

$$A = 100$$

$$\frac{\Delta A}{A} = 10\%$$

$$\frac{\Delta A_f}{A_f} = ?$$

$$\frac{\Delta A_f}{A_f} = \frac{\Delta A}{A} \times \frac{1}{1+A\beta}$$

$$= \frac{10}{100} \times \frac{1}{1+(100)(0.04)}$$

$$= 0.02$$

~~2M~~ Characteristics of 've' feedback amplifiers

1. Stability of Gain $S = \frac{1}{1+A\beta}$
2. Reduction in forward gain $A_f = \frac{A}{1+A\beta}$
3. Reduction in Noise
4. Reduction in distortion
5. Increase in o/p impedance
6. Decrease in o/p impedance
7. Increase in bandwidth

Reduction in distortion,

If D is the distortion of an amplifier
then distortion with feedback is given
by

$$D_f = \frac{D}{1+A\beta}$$

① If Amplifier has a midgain of 125
an B.W of 250kHz

(i) If 4% -ve feedback is introduced
find the new B.W & Gain.

(ii) If B.W is restricted to 1MHz find
~~Sol:~~ the feedback ratio.

$$\text{Ques: } A = 125$$

$$\text{B.W} = 250\text{kHz}$$

$$\cancel{\beta} = 0.4$$

$$A_f = \frac{A}{1+AB} = \frac{125}{1+(125)(0.4)} = 2.450$$

$$\cancel{B} = \cancel{250\text{kHz}}$$

$$\begin{aligned} \text{B.W}_f &= \text{BW} (1+AB) \\ &= 250 \times 10^3 (1 + 125(0.4)) \\ &= 12750 \cancel{\text{kHz}} = \end{aligned}$$

$$\begin{aligned} \text{B.W}_f &= \text{BW} (1+AB) \\ &\approx 250 \times 10^3 (1 + 125(10^6)) \\ &= 3.125 \times 10^3 \text{ Hz} \end{aligned}$$

$$1\text{MHz} = 250 \times 10^3 (1+AB)$$

$$\frac{1 \times 10^6}{250 \times 10^3} = 1+AB$$

Topologies

* Classifications of -ve feedback amplifiers
 -ve feedback amplifiers are classified into
 4 types

(1) Voltage Series feedback


(2) Voltage Shunt feedback

(3) Current Series feedback


(4) Current shunt feedback

(1) Voltage Series feedback / shunt Series

Shunt (o/p)

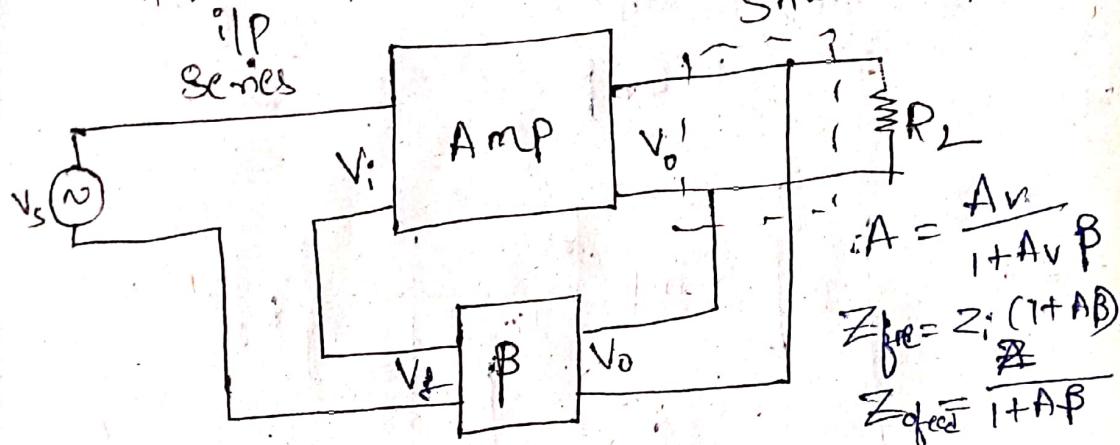


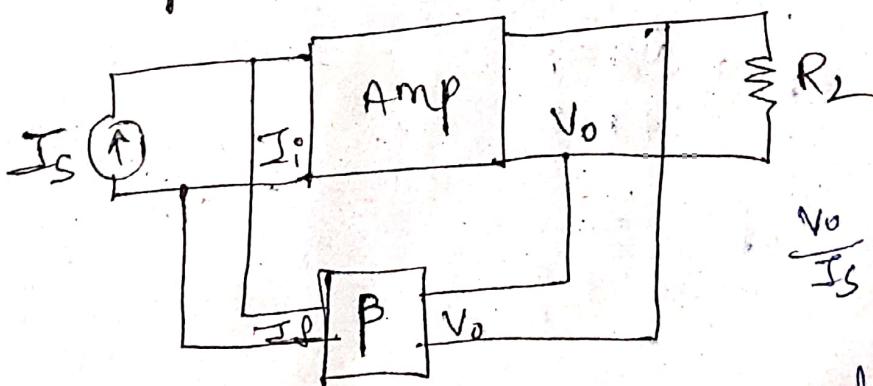(2) Voltage Shunt feedback / Trans resistance



$\frac{v_o}{I_s}$ (i/p Shunt) \rightarrow current divide
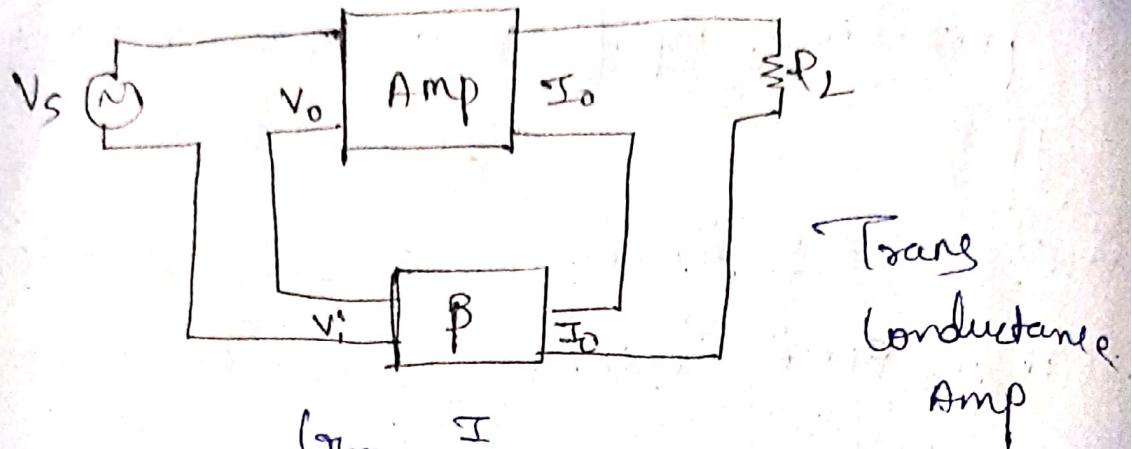
$$R_{m\beta} = \frac{R_m}{1 + R_m\beta}$$




$$G_m = \frac{I}{V}$$

$$Z_{if} = Z_i (1 + G_m \beta)$$

$$Z_{o\text{ feed}} = Z_o (1 + G_m \beta)$$

$$G_{mif} = \frac{G_m}{1 + G_m \beta}$$

(4)

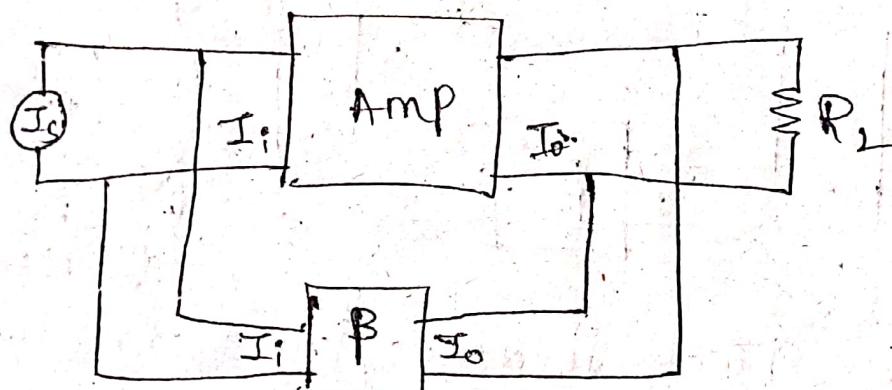

$$Z_{if} = \frac{Z_i}{1 + A_I \beta}$$

$$Z_{o\text{ f}} = \frac{Z_o}{1 + A_I \beta}$$

Bandwidth of a feedback amplifier

Lower cut off Frequency:

$$A_f = \frac{A}{1 + AB}$$

$$A_{fL} = \frac{A_L}{1 + A_L B}$$

$$A = \frac{A_{mid}}{1 - j\left(\frac{f_L}{f}\right)}$$

$$A_{fL} = \frac{\frac{A_{mid}}{1 - j\left(\frac{f_L}{f}\right)}}{1 + B\left(\frac{A_{mid}}{1 - j\left(\frac{f_L}{f}\right)}\right)}$$

$$A_{fL} = \frac{A_{mid}}{1 - j\left(\frac{f_L}{f}\right) + B A_{mid}}$$

divide with $1 + AB$

$$A_{fL} = \frac{\frac{A_{mid}}{1 + A_{mid}B}}{\frac{1 - j\left(\frac{f_L}{f}\right) + B A_{mid}}{1 + A_{mid}B}}$$

$$A_{f_L} = \frac{A f_m}{1 - j \left(\frac{f_L}{f} \right)} \quad \boxed{A f_m = \frac{A_m}{1 + A_m \beta}}$$

$$A_{f_L} = \frac{A f_m}{1 - j \left(\frac{f_L}{f(1 + A_m \beta)} \right)}$$

$$A_{f_L} = \frac{A f_m}{1 - j \left(\frac{f_{2f_L}}{f} \right)}$$

$$\boxed{f_{2f_L} = \frac{f_L}{1 + A_m \beta}}$$

higher cut off frequency

$$A_f = \frac{A}{1 + A \beta}$$

$$A_{f_h} = \frac{A}{1 + A_h \beta}$$

$$A = \frac{A_m i_d}{1 - j \left(\frac{f}{f_h} \right)}$$

$$A_{f_h} = \frac{A_m i_d}{1 - j \left(\frac{f}{f_h} \right)}$$

$$1 + \beta \left(\frac{A_m i_d}{1 - j \left(\frac{f}{f_h} \right)} \right)$$

$$A_{fh} = \frac{\text{Amid}}{1 - j\left(\frac{f}{f_h}\right) + \beta \text{Amid}}$$

divide with $1 + \text{Amid}$

$$A_{fh} = \frac{\frac{\text{Amid}}{1 + \text{Amid} \beta}}{\frac{1 - j\left(\frac{f}{f_h}\right) + \beta \text{Amid}}{1 + \text{Amid} \beta}}$$

$$A_{fh} = \frac{Af_m}{1 - j\left(\frac{f}{f_h}\right)}$$

$$A_{fh} = \frac{Af_m}{1 - j\left[\frac{f}{f_h(1 + \text{Amid} \beta)}\right]}$$


$$A_{fh} = \frac{Af_m}{1 - j\left(\frac{f}{f_h f}\right)}$$

$$f_h f = f_h (1 + \text{Amid} \beta)$$


$$B.W = f_{hf} - f_{Lf}$$


$$B.W = f_h (1 + \text{Amid} \beta) - \frac{f_L}{1 + \text{Amid} \beta}$$

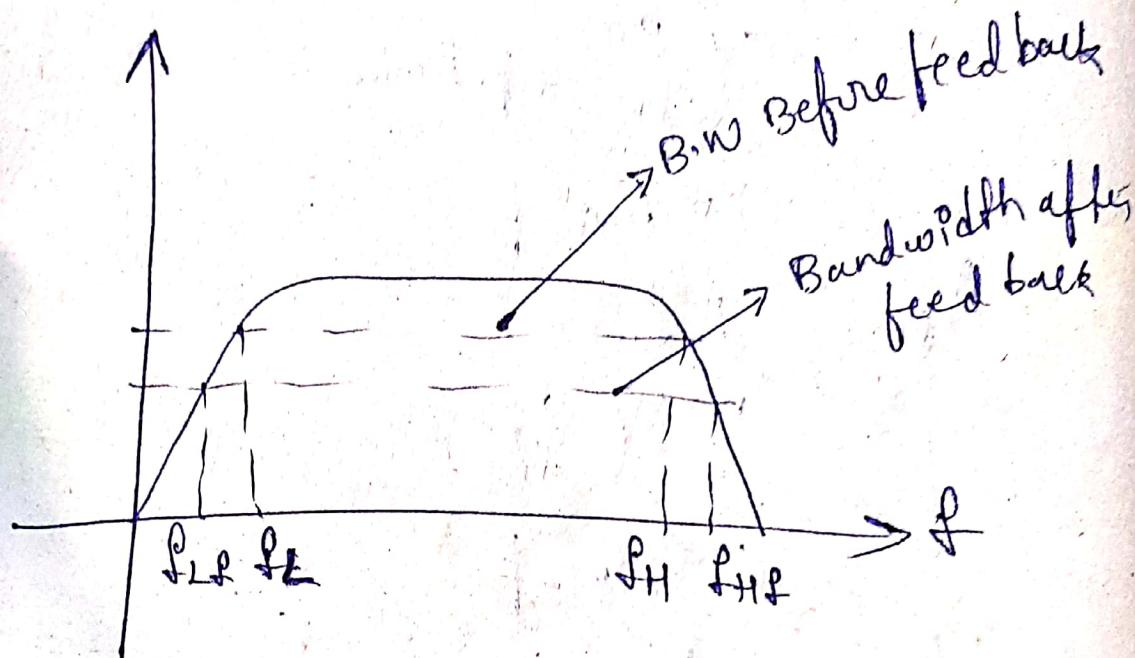Bandwidth is the frequency at which the gain starts to drop when frequency increases. So if lowering the gain by using feedback moves that point to higher frequency then the B.W. \uparrow .



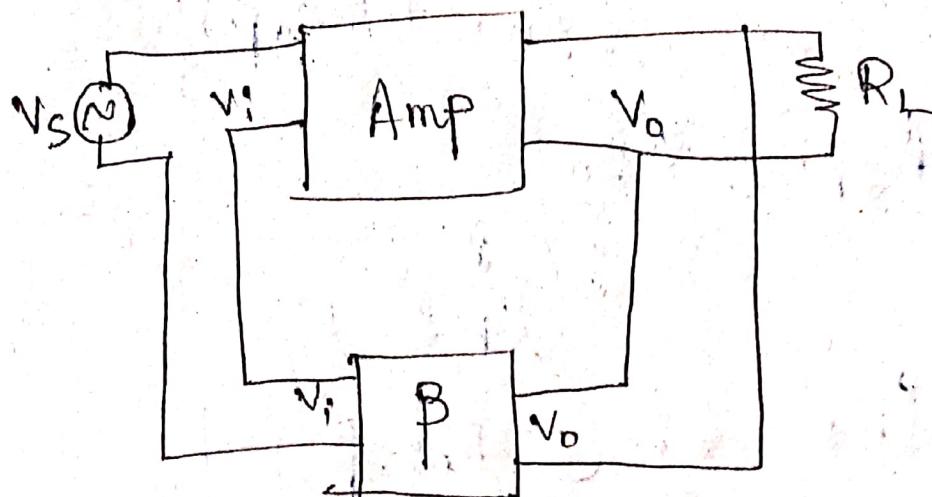* Voltage Series E_f Feedback Amplifier:-



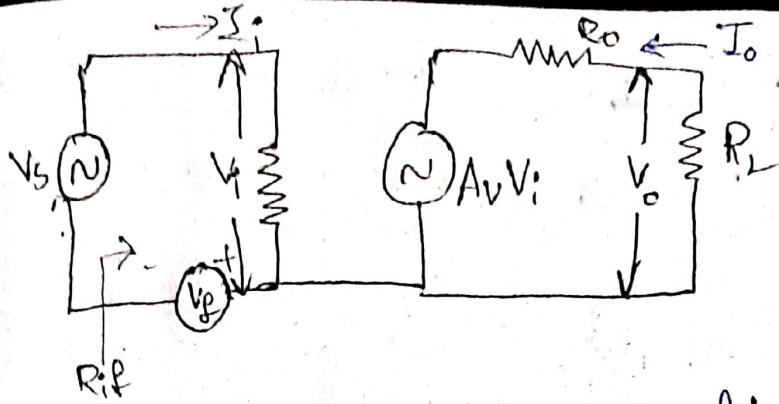

Input Resistance with feedback (R_{if})

$$R_{if} = \frac{V_s}{I_i}$$

$$V_i = V_s - V_f$$

$$V_s = V_i + V_f$$

$$= V_i + \beta V_o$$

$$= V_i + \beta A_v V_i$$

$$\frac{V_s}{I_i} = \frac{V_i}{I_i} (1 + \beta A_v)$$

$$R_{if} = R_i (1 + \beta A_v)$$

Output Resistance with feedback (R_{of}):

$$R_{of} = \frac{V_o}{I_o} \Big|_{V_s=0}$$

$$V_o = I_o R_o + A_v V_i$$

$$V_s = V_i + V_f$$

$$V_i = -V_f$$

$$V_i = -\beta V_o$$

$$V_o = I_o R_o - A_v \beta V_o$$

$$V_o + A_v \beta V_o = I_o R_o$$

$$V_o (1 + A_v \beta) = I_o R_o$$

$$\frac{V_o}{I_o} = \frac{R_o}{1 + A_v \beta}$$

$$R_{of} = \frac{R_o}{1 + A_v \beta}$$

$$A_{if} = \frac{A_v}{1 + A_v \beta}$$

- ① A voltage series -ve feed back amplifier has voltage gain without feed back of gain 500, ifp resistance $3k\Omega$, o/p resistance $20k\Omega$ and feed back ratio 0.01 calculate A_v , ifp R_{in}'s, o/p R_{out}'s, of the Amplifiers with feed back.

$$R_i = 3k\Omega$$

$$R_o = 20k\Omega$$

$$A_v = 500$$

$$\beta = 0.01$$

$$R_{if} = R_i(1 + \beta A_v)$$

$$= 3 \times 10^3 (1 + 500(0.01))$$



$$= 18k\Omega$$

$$R_{o,f} = \frac{R_o}{1 + A_v \beta} = \frac{20 \times 10^3}{1 + (500)(0.01)}$$

$$R_{o,f} = 3333.3 = 3.3 k\Omega$$

$$A_f = \frac{500}{1 + (500)(0.01)} = 83.33$$

* Voltage shunt feedback Amplifier

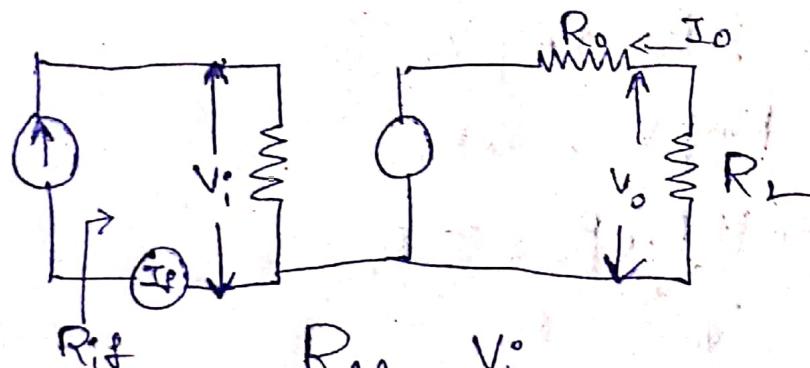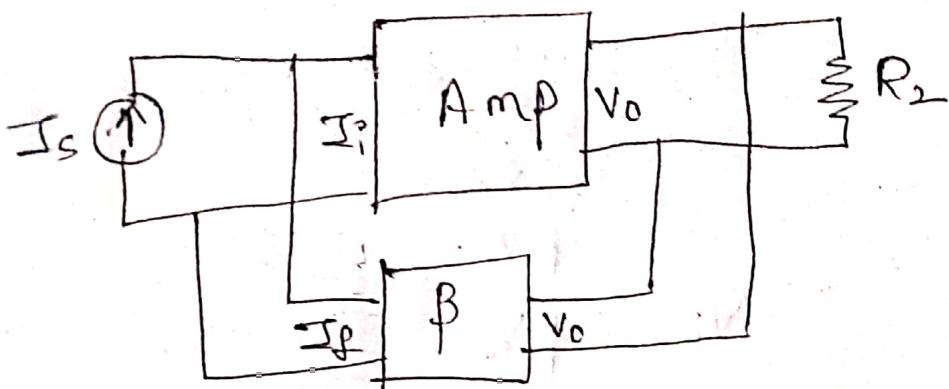

$$R_{if} = \frac{V_i}{I_s}$$

$$I_i = I_s - I_f$$

$$I_s = I_i + I_f$$

$$I_s = I_i + \beta V_o$$

$$= I_i + \beta R_m I_i$$

$$\frac{I_s}{V_i} = \frac{I_i}{V_i} (1 + R_m \beta)$$

$$\frac{1}{R_{if}} = \frac{1 + R_m \beta}{R_i}$$

$$R_{if} = \frac{R_i}{1 + R_m \beta}$$

* O/p Resistance with feedback

$$R_{of} = \left. \frac{V_o}{I_o} \right|_{I_s=0}$$

$$V_o = I_o R_o + R_m I_i$$

$$I_s = I_i + I_f$$

$$I_i = -I_f$$

$$= -\beta V_o$$

$$V_i = -\beta V_o$$

$$V_o = I_o R_o - R_m \beta V_o$$

$$V_o + R_m \beta V_o = I_o R_o$$

$$V_o (1 + R_m \beta) = I_o R_o$$

$$\frac{V_o}{I_o} = \frac{R_o}{1 + R_m \beta}$$

$R_{of} = \frac{R_o}{1 + R_m \beta}$

① A Voltage shunt -ve feed back amplifier
Gain of the AHP without feed back

Prop Constant $3k\Omega$ ilp Impedance $2k\Omega$
 $\rightarrow R_m$

O/p impedance $20k\Omega$, feed back ratio 0

0.05 Calculate gain, o/p impedance

D/P impedance of the amp with feedback

Ques: $R_m = 3 \text{ k}\Omega$

$$R_i = 2 \text{ k}\Omega, R_o = 20 \text{ k}\Omega$$

$$\beta = 0.05$$

$$Z_{if} = \frac{R_i}{1 + R_m \beta} = \frac{2 \times 10^3}{1 + (3 \times 10^3)(0.05)}$$

$$Z_{if} = 3.99 \times 10^{-3}$$

$$Z_{of} = \frac{20 \times 10^3}{1 + (3 \times 10^3)(0.05)}$$


$$Z_{of} = 132.45$$

$$A_m = \frac{R_m}{1 + R_m \beta}$$


$$A_m = \frac{3 \times 10^3}{1 + (3 \times 10^3)(0.05)}$$

$$A_m = 19.867$$

Current Series feedback Amplifier:

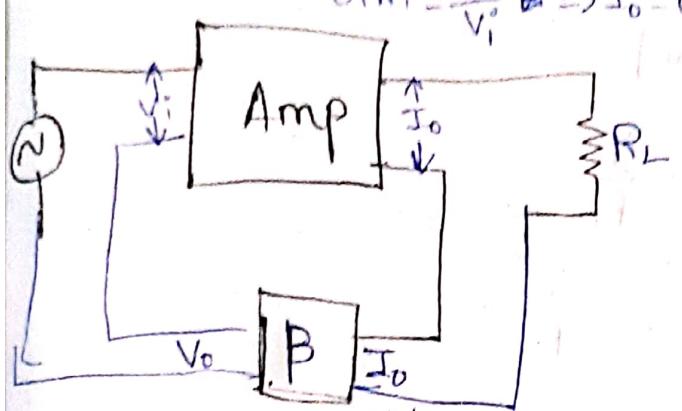

$$G_{mfp} = \frac{G_m}{1 + G_m \beta}$$

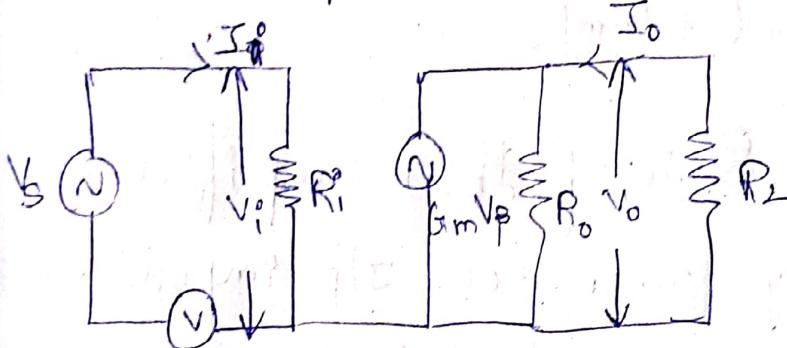

$$R_{if} = \frac{V_s}{I_i}$$

$$V_i^o = V_s - V_f$$

$$V_f = V_i^o + V_o$$

$$V = V_i^o + \beta I_o$$

$$= V_i^o + G_m \beta V_o$$

$$\frac{V_s}{I_i} = \frac{V_i^o (1 + G_m \beta)}{I_i}$$

$$R_{if} = R_i (1 + G_m \beta)$$

$$R_{of} = \frac{V_o}{I_o}$$

$$I_o = \frac{V_o}{R_o} - G_{mfp} V_i^o \rightarrow @$$

$$V_i^o = -V_f$$

$$V_i^o = -\beta I_o$$

$$I = -I_o$$

Current flowing in opp. direction

$$V_i = \beta I_o$$

$$I_o = \frac{V_o}{R_o} - G_{mB} \beta I_o$$


$$I_o + G_{mB} \beta I_o = \frac{V_o}{R_o}$$

$$I_o (1 + G_{mB}) = \frac{V_o}{R_o}$$

$$\frac{V_o}{I_o} = R_o (1 + G_{mB})$$

$$R_{of} = R_o (1 + G_{mB}).$$

* Current

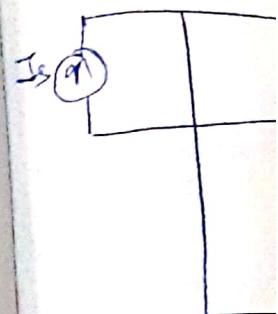

① A Current Series feedback amplifier has a proportionality factor 500, I/p impedance 3k Ω , o/p impedance 30k Ω , feed back ratio 0.01 calculate Gain o/p ~~impedance~~, o/p impedance with feed back.

$$G_m = 500$$

$$Z_i = 3k\Omega, Z_o = 30k\Omega$$

$$\beta = 0.01$$


$$R_{of} = 30 \times 10^3 (1 + (500)(0.01))$$

$$R_{of} = 180k\Omega$$


$$Gain = \frac{G_m}{1 + G_m \beta} = \frac{500}{1 + (500)(0.01)} = 83.33$$

* Current shunt feedback amplifier
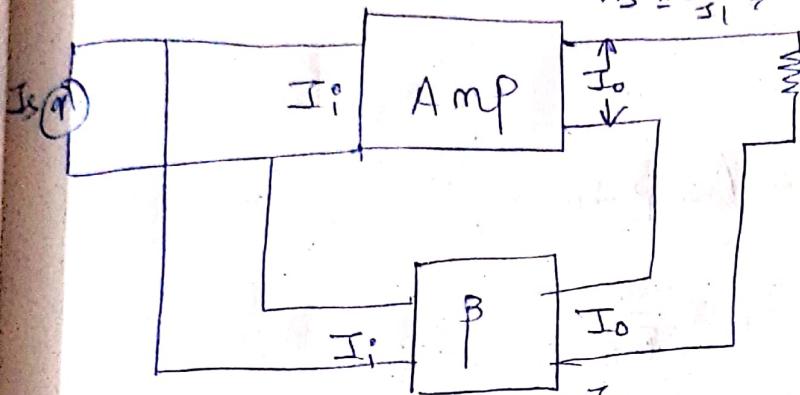
$$A_S = \frac{I_o}{I_i} \Rightarrow A_I I_i = I_o$$



$$I_f = \beta I_o$$

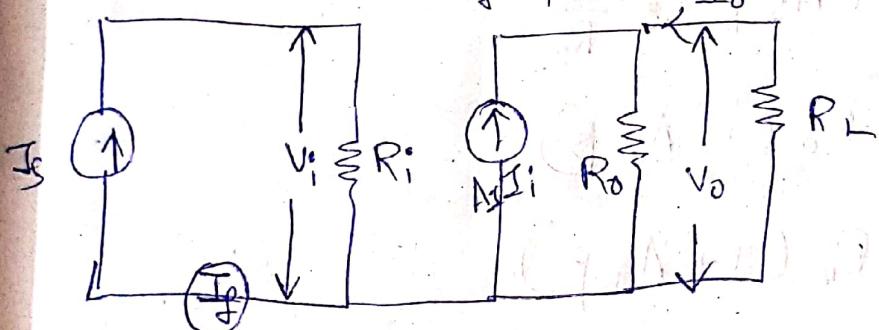

$$R_{if} = \frac{V_i}{I_f}$$

$$I_s = I_i + \beta I_o$$

$$I_i = I_s - I_f$$

$$I_s = I_i [1 + A_I \beta]$$

$$I_f = I_i + I_o$$

$$\frac{1}{R_{if}} = \frac{1}{R_i} + A_I \beta$$

$$R_{if} = \frac{R_i}{1 + A_I \beta}$$

$$R_{of} = \frac{V_o}{I_o} \quad |_{I_S = 0}$$

33

$$I_o = \frac{V_o}{R_o} = A_I R_i$$

$$I_i = -I_f$$

$$= -\beta I_o$$

$$\boxed{I_i = -I_o}$$

$$I_i = \beta I_o$$

$$I_o = \frac{V_o}{R_o} = A_I \beta I_o$$

$$I_o + A_I \beta I_o = \frac{V_o}{R_o}$$

$$I_o (1 + A_I \beta) = \frac{V_o}{R_o}$$

$$\frac{V_o}{I_o} = R_o (1 + A_I \beta)$$

$$R_{of} = R_o (1 + A_I \beta)$$

① A current shunt feed back amplifier of current gain 100, i_{lp}^{imp} , $2k\Omega$ o/p imp, $15k\Omega$ feedback ratio 0.05 calculate i_{lp} , o_{lp}^{imp} and gain with feed back.

Given: $A_I = 100$, $Z_i = 2k\Omega$, $Z_o = 15k\Omega$

$$\beta = 0.05$$

$$R_{if} = \frac{R_i}{1 + A_I \beta} = \frac{2 \times 10^3}{1 + (100)(0.05)} = 333.333\Omega$$

$$R_{if} = \cancel{333.333}\Omega$$

$$R_{of} = 15 \times 10^3 \\ = 90k$$

$$A_{if} = \frac{A_I}{1 + A_I \beta}$$

* Method

The following

obtain N

Rules

Rule 1. Identify

(i) Find Δ

\rightarrow If the

from the

Then it

\rightarrow If

from the

source

(ii) Find

\rightarrow short

feedback

is voltage

\rightarrow open

$$R_{of} = 15 \times 10^3 \cdot (1 + (100)(0.05))$$

$$= 90 \text{ k}\Omega$$

$$A_{if} = \frac{A_I}{1 + A_I \beta} = \frac{100}{1 + (100)(0.05)}$$

$$= 16.66$$

* Method of Analyzing feedback amplifier

The following rules may be applied to obtain Network Topology.

Rules

We 1. Identify the feedback Topology.

(i) Find the type of Mixing in Network

→ If the feedback Signal is subtracted from the applied voltage Signal Source.

Then it is Series Mixing.

→ If the feedback Signal is subtracted from the applied Current Signal Source, Then it is shunt Mixing.

(ii) Find the type of Sampler

→ short the o/p side i.e., $V_o = 0$, if

feedback Signal becomes zero, then it is voltage Sampler.

→ open the o/p side i.e., $I_o = 0$, if

feedback Signal becomes zero, then of current Sampler.

Q. (Rule-2):-

(i) To find the o/p ckt

→ For voltage Sampling set $V_o = 0$, i.e., short ckt the o/p node.

→ For current Sampling set $I_o = 0$, i.e., open the o/p loop.

(ii) To find the o/p ckt

→ For shunt comparison set $V_o = 0$, i.e., short the o/p node.

→ For Series comparison set $I_o = 0$, i.e., open the o/p loop.

3. Replace each active device by its

model namely the h-parameter model for low frequencies and hybrid π -model

for a transistor at high frequencies

4. Using Thevinin's Source if X_p (feedback Signal) is a voltage and a nodal source if X_p is a current.

5. Indicate X_f and X_o on the ckt obtain on carrying out steps 1, 3 & 4.


Evaluate $\beta = \frac{X_f}{X_o}$

6. Evaluate gain(A) by applying KVL & KCL to the equivalent ckt ^{after step 3} to the ~~equivalent ckt~~

7. Finally from A & β find A_f , R_{if} and R_{of} .

→ Linear elements are R, L, C

→ The graph does not start from zero

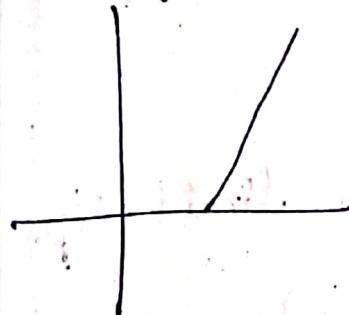

It starts linearly increasing with time.


→ The non linear elements are diode, FET, Transistor.

→ The transistor has high voltage gain and high current gain compare to FET.

→ In Transistor we have CB, CE, CC from these three we use CE compare to CB and CC.

→ Amplifiers are used in both Transistors and FET.

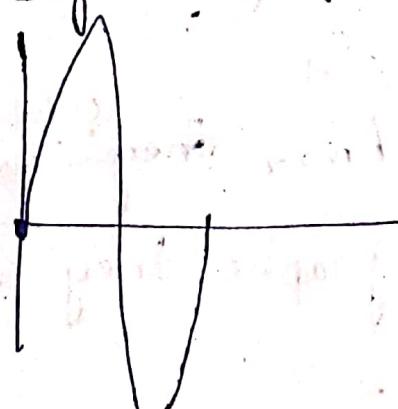Amplification → which strengthens the weak Signal to high signal.



The signal not only sinusoidal wave but Signal is an information..

→ For AC Supply we use 220V

→ For Transistor we take o/p in mV.

$$1V - 100V$$

$$100 - 1000V$$


→ For FET we take up to limit o/p.

→ Cascade (Multiplying the Signals we get the high o/p). cascode

→ ~~Band~~ RMS (Root mean Square) and Arg.

→ In America they use AC for 50Hz and 110V

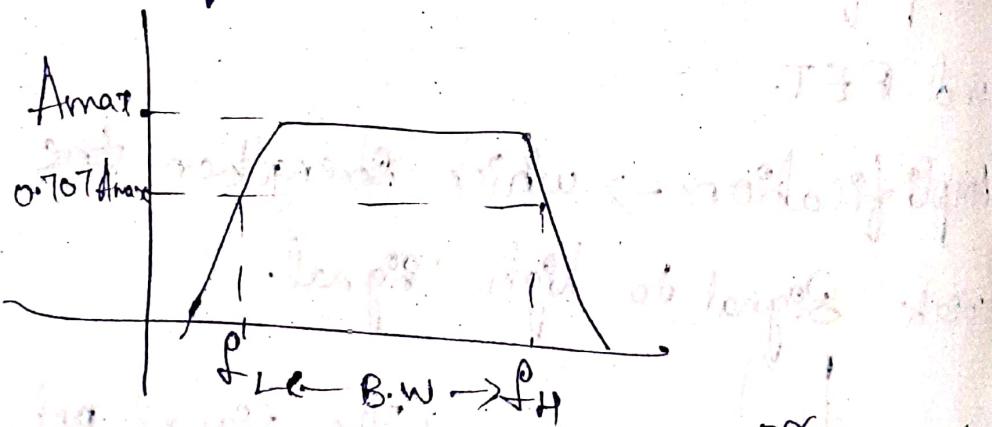→ Bandwidth is the difference between higher frequency and lower frequency



→ Instead of $0.707 A_{max}$ they can calculate $\frac{A_{max}}{\sqrt{2}}$. For some graphs they take $\sim 3dB$ (decibels).


→ We calculate the $\log A_v$ for the gain output.

→ we know that $P = VI$

$$= V \cdot \frac{V}{R} = \frac{V^2}{R}$$

$$= \frac{V^2}{2} = \left(\frac{V}{\sqrt{2}}\right)^2$$

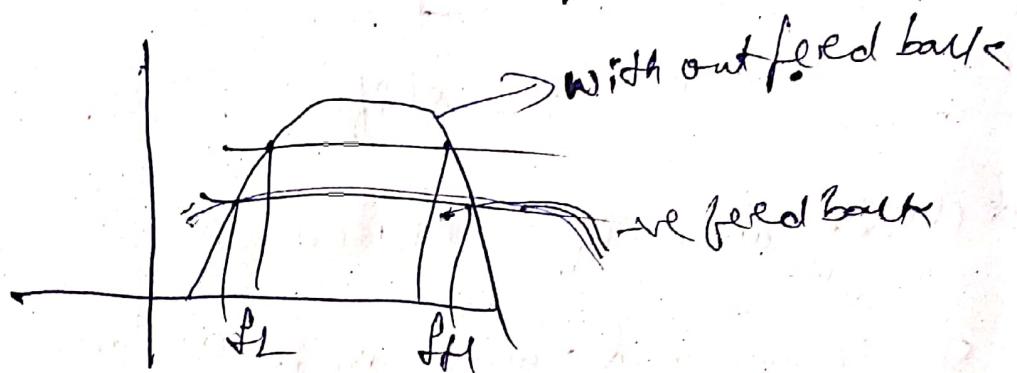→ In Negative feedback the gain decreases
 $A_f < A$ with -ve feedback.




→ $A = \frac{A}{1 + AB}$ when AB reaches to 1

then it becomes zero the gain will become infinite (Maximum) in the feedback.

→ In RC the gain will decrease.

* oscillator ckt

+ve. Feed back

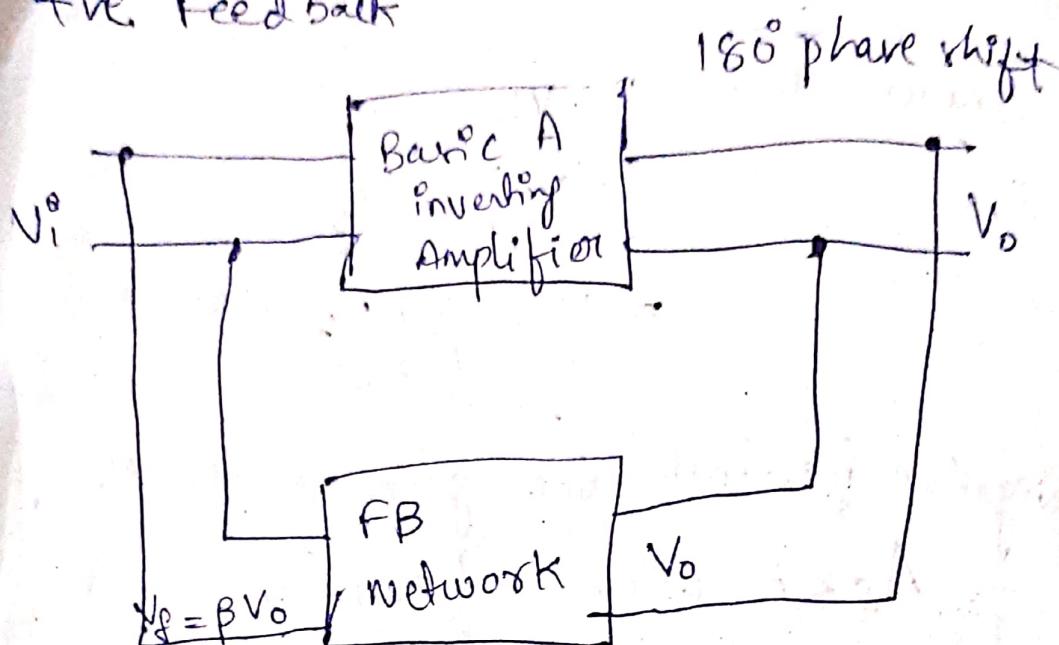


- 180° phase shift

* classification of oscillators

1. Sinusoidal and non-sinusoidal oscillators
2. feedback and non-feedback oscillators.
3. ckt components of ~~are~~ RLC tuned oscillators and crystal oscillators
- 4) Range of operating frequency.
 - Audio frequency oscillators ($20 \rightarrow 20\text{kHz}$)
 - RFO (Radio frequency oscillator) $\rightarrow 20\text{kHz} \rightarrow 30\text{MHz}$
 - VHF (Very high frequency) $\rightarrow 30 - 300\text{MHz}$
 - UHF (Ultra high frequency) $\rightarrow 300\text{MHz} \rightarrow 3\text{GHz}$

5. MNFO (Microwave Frequency oscillator) $> 3 \text{ GHz}$

* RC phase shift oscillator

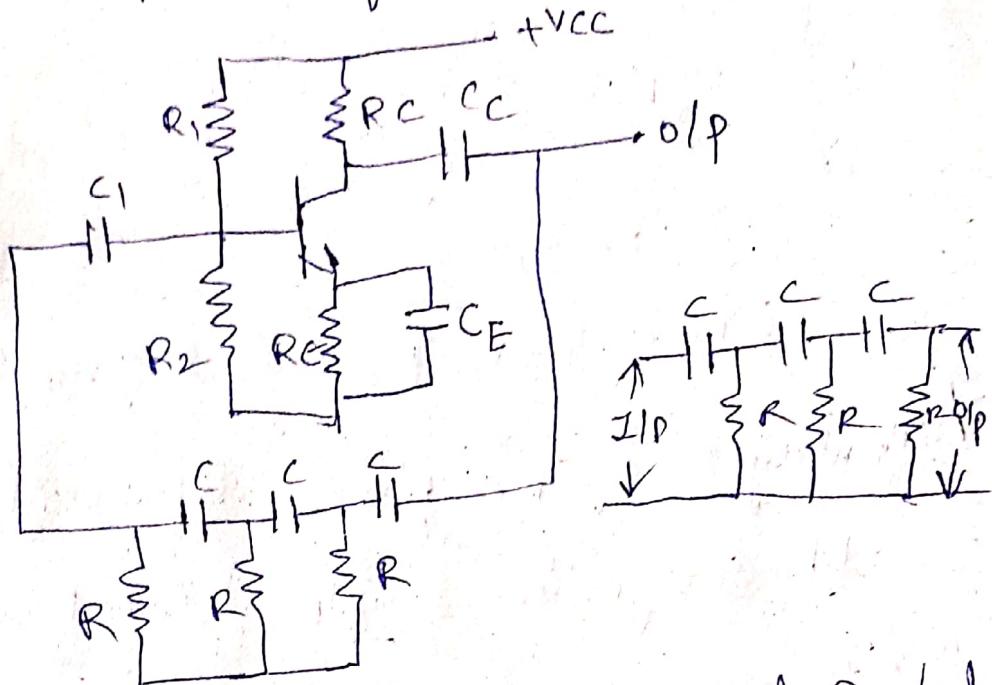

→ It consists of CE amplifier and RC feed back.

→ feedback resistance ^{n/w} consist of Resistor & capacitor.

→ Ladder phase shift oscillator feed back
n/w must introduce a phase shift of 180° .
to obtain total phase shift around 360° .

→ one RC phase shift n/w produces 60° total
phase shift = 180° ($\because 60 \times 3$)

→ O/p gain is -ve. O/p of amplifier produces
 180° . O/p of an amplifier is given to
fb n/w phase shift around a loop is 180°

* * Oscillators: UNIT 3

→ due to 3 RC N/w

$$f = \frac{1}{2\pi R C \sqrt{6}} \text{ Hz}$$

$$f = \frac{1}{2\pi R C \sqrt{6+4k}}$$

where $k = R_c / R \rightarrow$ is very small


Advantages of RC phase shift oscillator

→ Ckt design is simple it can produce audio frequency (less frequency) range.

→ produces sinusoidal o/p waveform.

→ It is a fixed frequency oscillator

* FET phase shift oscillator

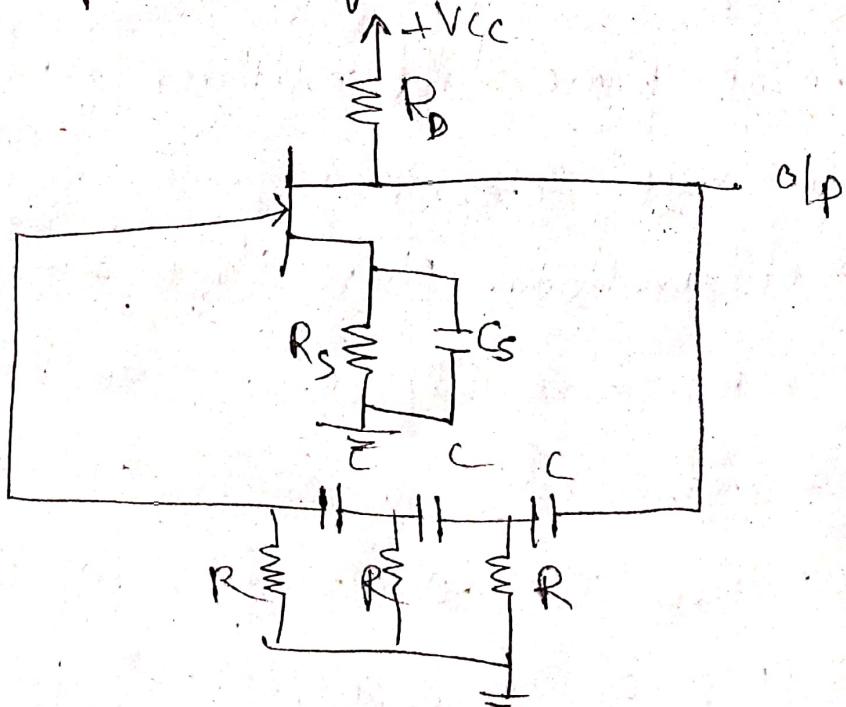

→ FET amplifier is self bias with capacitor by passed source Resistance R_s and bias Resistance R_D

→ The important parameters of FET are
 g_m, R_D .

$$|A| = g_m R_2 \text{ where } R_2 = R_D \parallel R_s$$

$$\text{with FB } |A| = 291K \quad |\beta| = 1/2$$

Problems

① In a RC phase shift oscillator, the phase shift network uses the R each of $4.7k\Omega$ and C each of $0.47\mu F$. Find the frequency

Sol: $R = 4.7k\Omega$

$$C = 0.47\mu F$$

$$F = \frac{1}{2\pi R C \sqrt{6}}$$

$$= \frac{1}{2\pi \times 4.7 \times 10^3 \times 0.47 \times 10^{-6} \sqrt{6}}$$

$$f = 29.413 Hz$$

② For an RC phase shift oscillator, the feed back network uses $R = 6k\Omega$ & $C = 1500\text{pF}$. The transistorized amplifier used as a collector resistance of $18k\Omega$ calculate the frequency of oscillations.

$$\text{Sol: } R = 6 \text{ k}\Omega$$

$$C = 1500 \text{ pF}$$

$$R_C = 18 \text{ k}\Omega$$

$$k = \frac{R_C}{R} = \frac{18 \text{ k}}{6 \text{ k}} = 3$$

$$f = \frac{1}{2\pi R C \sqrt{6+4k}}$$

$$f = \frac{1}{2\pi \times 6 \times 10^3 \times 1500 \times 10^{-12} \sqrt{6+4(3)}}$$

$$f = 4.168 \text{ kHz}$$