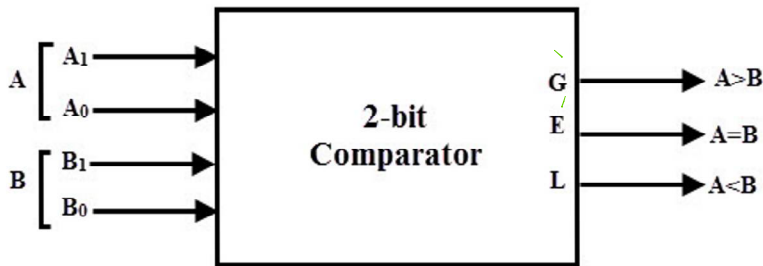


2-Bit Magnitude Comparator

A comparator used to compare two binary numbers each of two bits is called a 2-bit Magnitude comparator. It consists of four inputs and three outputs to generate less than, equal to and greater than between two binary numbers.



← i/ps → ← o/p →

A		B				
A1	A0	B1	B0	A>B	A<B	A=B
0	0	0	0	0	0	1
0	0	0	1	0	1	0
0	0	1	0	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	0	1	0	0	1
0	1	1	0	0	1	0
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	0	1	1	0	1	0
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	0	1

A > B

① $A_1 = 1, B_1 = 0 \Rightarrow A_1 > B_1$
 $A_1 = 0, B_1 = 0 \Rightarrow A_1 = B_1$

② $A_1 = 1, B_1 = 1, A_0 = 1, B_0 = 0 \Rightarrow A > B$
 $A_1 = 1, B_1 = 1, A_0 = 0, B_0 = 1 \Rightarrow A < B$
 $A_1 = 1, B_1 = 1, A_0 = 1, B_0 = 1 \Rightarrow A = B$

$$A > B = A_1 \bar{B}_1 + (A_1 = B_1) \cdot A_0 \bar{B}_0$$

$$= A_1 \bar{B}_1 + (A_1 \odot B_1) \cdot A_0 \bar{B}_0$$

A < B

① $A_1 = 0, B_1 = 1 \Rightarrow A < B = \bar{A}_1 B_1$

②

$$\left. \begin{array}{l} A_1 = 0 \\ B_1 = 0 \end{array} \right\} \rightarrow A_1 = B_1$$

$$\left. \begin{array}{l} A_1 = 1 \\ B_1 = 1 \end{array} \right\} \rightarrow A_1 = B_1$$

$$A_1 = B_1$$

$$\nrightarrow A_0 = 0 \ \& \ B_0 = 1 \Rightarrow A < B$$

$$(A_1 = B_1) \quad \bar{A}_0 B_0$$

$$(A_1 \odot B_1) \quad \bar{A}_0 B_0$$

$$A < B = \bar{A}_1 B_1 + (A_1 \odot B_1) \bar{A}_0 B_0$$

③

$$A = B$$

$$A_1 = B_1 \Rightarrow A_1 \odot B_1$$

$$A_0 = B_0 \Rightarrow A_0 \odot B_0$$

$$A = B \Rightarrow (A_1 \odot B_1) (A_0 \odot B_0)$$

A > B

	B ₁ B ₀	00	01	11	10
A ₁ A ₀	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

$\rightarrow A_0 \bar{B}_1 \bar{B}_0$
 $\rightarrow A_1 A_0 \bar{B}_0$
 $\rightarrow A_1 \bar{B}_1$

$$A > B \Rightarrow A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 + A_1 A_0 \bar{B}_0 \checkmark$$

		B1B0			
		00	01	11	10
A1A0	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	00	0	0	0	1

$$A_1 = B_1$$

$$A_0 = B_0$$


$$(A_1 \odot B_1) (A_0 \odot B_0) \Rightarrow A = B$$

		B1B0			
		00	01	11	10
A1A0	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	00	0	0	1	0

$$\bar{A}_1 \bar{A}_0 B_0$$

$$\bar{A}_1 B_1$$

$$\bar{A}_0 B_1 B_0$$

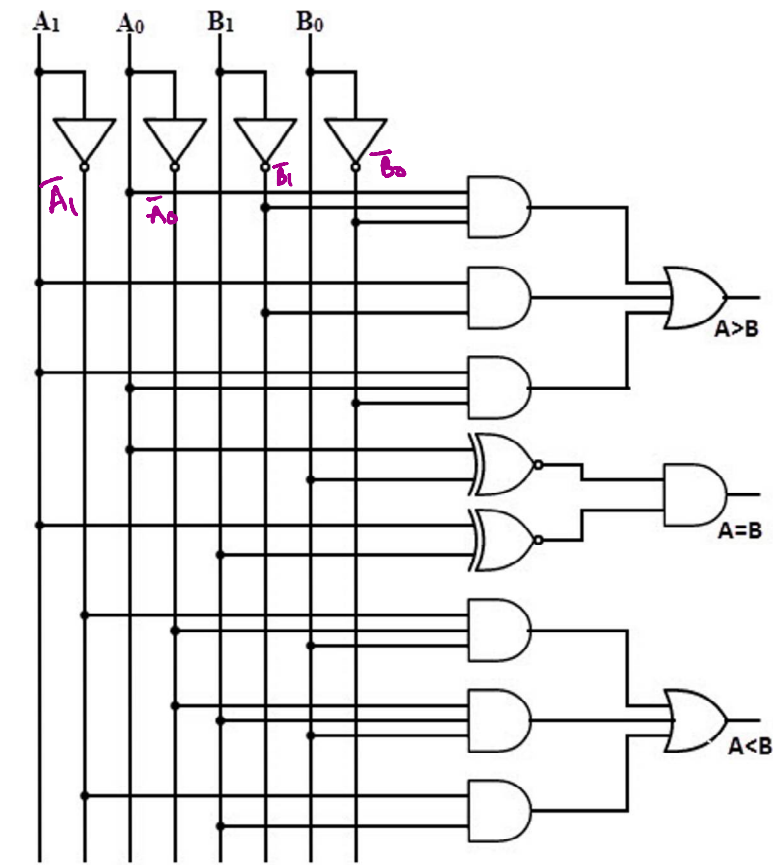

A) In a 2-bit comparator the condition of $A > B$ can be possible in the following cases:

1. If $A_1 = 1$ and $B_1 = 0 \longrightarrow A_1 \bar{B}_1$
2. If $A_1 = B_1$ and $A_0 = 1$ and $B_0 = 0 \Rightarrow (A_1 \odot B_1) A_0 \bar{B}_0$

$$A > B \Rightarrow A_1 \bar{B}_1 + (A_1 \odot B_1) A_0 \bar{B}_0$$

B) Similarly the condition for $A < B$ can be possible in the following cases:

1. If $A_1 = 0$ and $B_1 = 1$
2. If $A_1 = B_1$ and $A_0 = 0$ and $B_0 = 1 \Rightarrow \bar{A}_1 B_1$
 $\Rightarrow (A_1 \odot B_1) \bar{A}_0 B_0$

$$A < B \Rightarrow \bar{A}_1 B_1 + (A_1 \odot B_1) \bar{A}_0 B_0$$


C) The condition of $A=B$ is possible only when all the individual bits of one number exactly coincide with corresponding bits of another number.

$$\underline{A = B \Rightarrow (A_1 \odot B_1) (A_0 \odot B_0)}$$

2 bit Comparator

$$A < B \Rightarrow \bar{A}_1 B_1 + (A_1 \odot B_1) \bar{A}_0 B_0$$
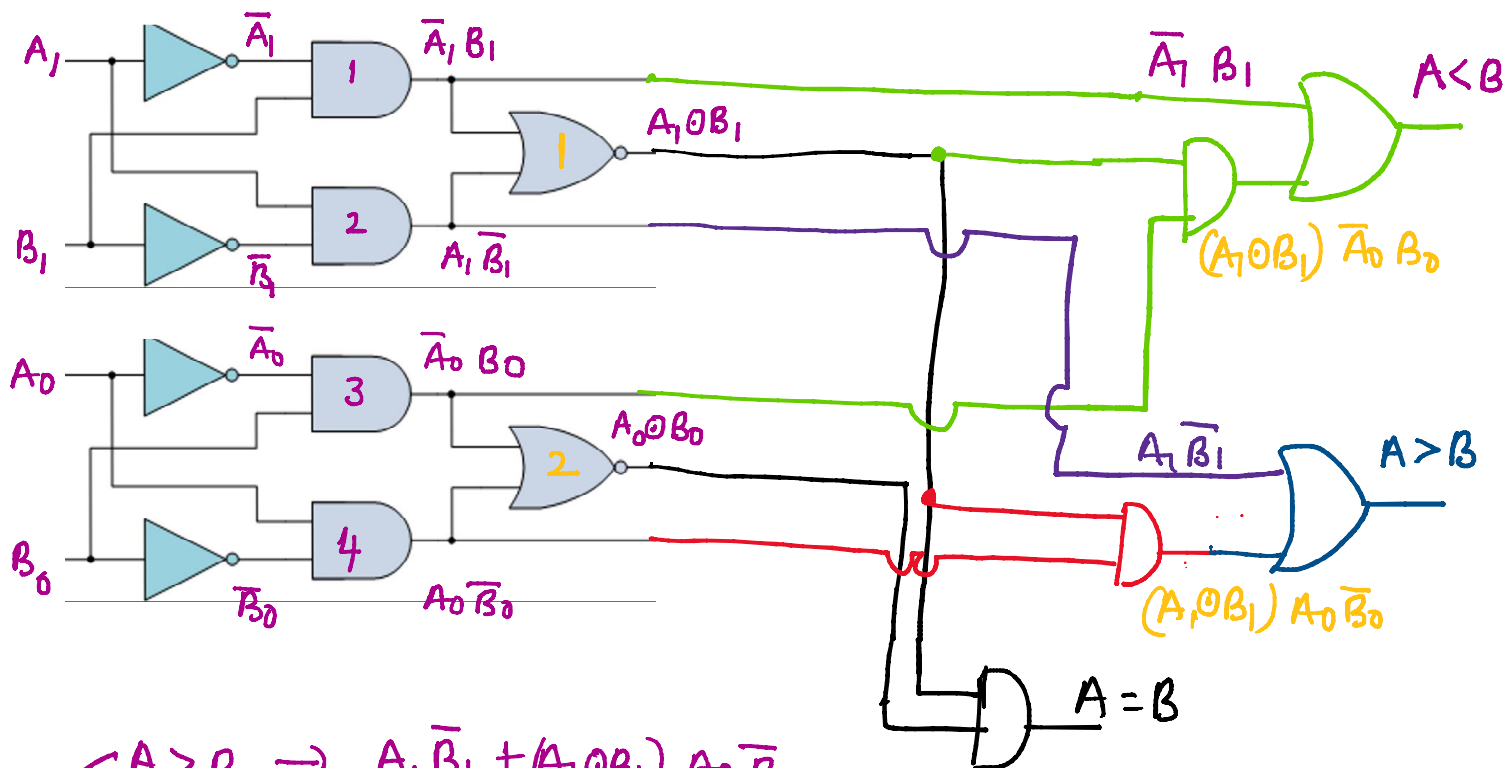
$$A = B \Rightarrow (A_1 \odot B_1) (A_0 \odot B_0)$$



$$\checkmark A > B \Rightarrow A_1 \bar{B}_1 + (A_1 \odot B_1) A_0 \bar{B}_0$$

