


$$|A_v| = \left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + \left( \frac{f}{f_H} \right)^2}}$$

Case - (1),  $f = 0$ ,  $|A_v| = 1$

Case - (2),  $f = f_H$ ,  $|A_v| = \frac{1}{\sqrt{2}}$


Case - (3),  $f \gg f_H$ ,  $|A_v| = \text{Low}$

Case - (4),  $f \gg f_H$ ,  $|A_v| = \text{very low}$

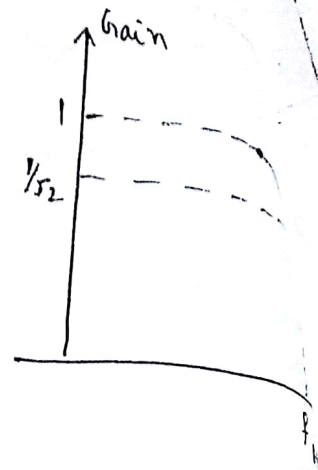

→ The freq at which has  $1/\sqrt{2}$  times of maximum value then it is upper cut off frequency.

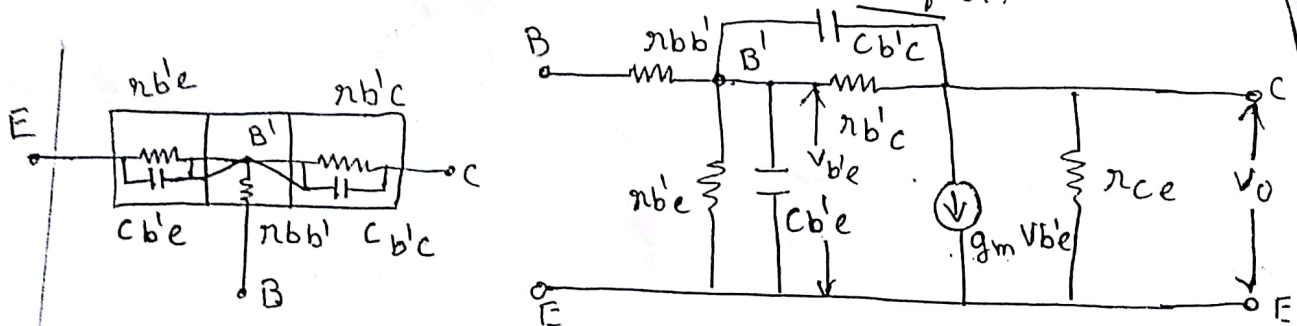High frequency response of BJT Amplifier:-



→ Forward biased PN junction exhibits a capacitive effect called diffusion capacitance.  $c_{be} \rightarrow$  diffusion capacitance of Emitter junction. Value = 100 pF

→ Reverse biased PN junction exhibits a capacitive effect called Transition capacitance.  $c_{bc} \rightarrow$  Transition capacitance of collector junction. Value = 3 pF

→  $r_{bb'}$  - Base spreading resistance. Its typical value is 100  $\Omega$ . It is a base series resistance between the external base terminal B and internal base region B'.

$r_{b'e}$  - resistance between the virtual base  $B'$  and the emitter terminal  $E$ . Typical value is  $1k\Omega$ .

Input resistance from base to emitter with the output shorted is simply  $r_{bb'} + r_{b'e}$  and this is the same as  $h_{ie}$ . Hence  $h_{ie} = r_{bb'} + r_{b'e}$ .

$r_{b'c}$  - resistance between the virtual base  $B'$  and the collector terminal  $C$ . It has a large value  $= 4M\Omega$ .


$r_{ce}$  - output resistance with typical value of  $80k\Omega$ .

$r_{ce} \gg R_L$ , if a load  $R_L$  is connected  $r_{ce}$  can be neglected.

$g_m v_{b'e}$  - It is a current generator. It is also known as collector current ' $I_c$ '. Where  $g_m$  is transconductance. Which is a ratio of o/p current to input voltage.


$$\therefore g_m = \frac{I_c}{v_{b'e}} \Rightarrow I_c = g_m v_{b'e}$$

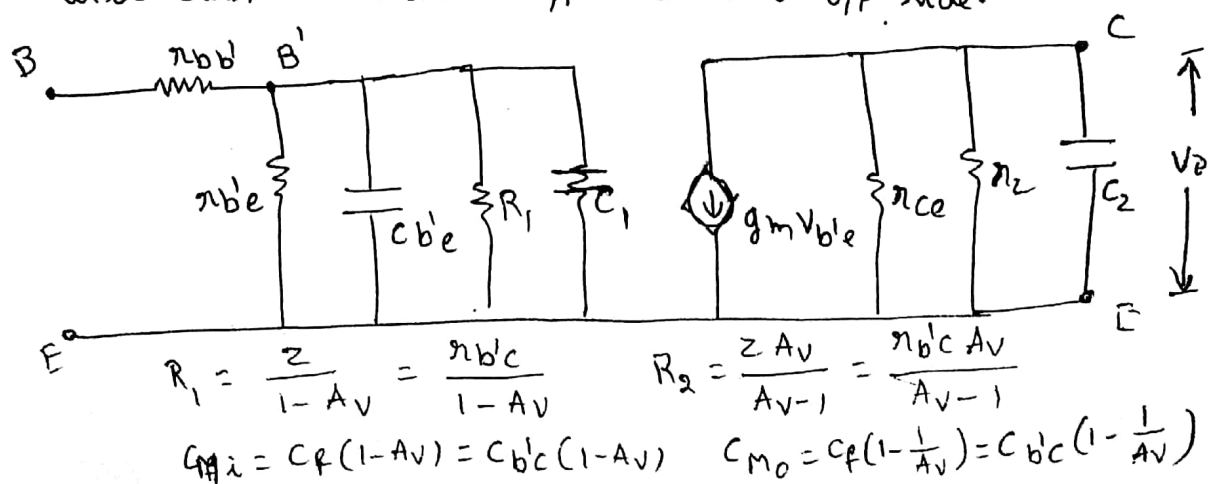→ The above circuit can be modified by Miller's theorem i.e., separate i/p and o/p capacitance, resistor will exist between i/p side and o/p side.



CE short circuit current gain at high frequency:-

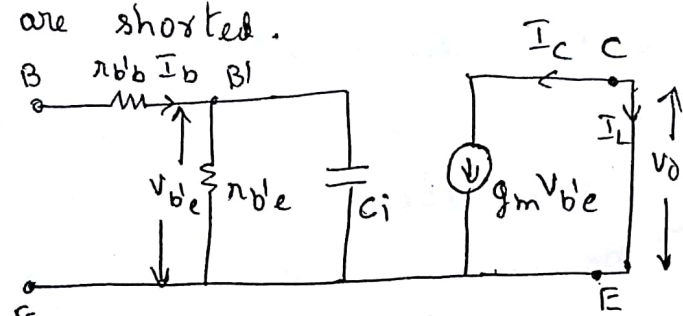Short circuited current gain means the o/p terminals are shorted.



→  $r_{ce}$  becomes zero, neglected.

→  $r_{be} || R_1 \approx r_{be}$

→  $C_i = C_{be} + C_1$

$$A_i = \frac{-I_c}{I_b} = \frac{-g_m V_{be}}{I_b} = \frac{I_L}{I_b} \quad (I_L = -I_c) = C_{be} + C_{bc}(1 - A_v)$$

from the circuit  $I_b = \frac{V_{be}}{r_{be}} + \frac{V_{be}}{1/s\omega C_i} = V_{be} \left[ \frac{1}{r_{be}} + s\omega C_i \right]$

$$\therefore A_i = \frac{-g_m V_{be}}{V_{be} \left[ \frac{1}{r_{be}} + s\omega C_i \right]} = \frac{-g_m r_{be}}{1 + s\omega C_i r_{be}}$$

$$g_m r_{be} = \frac{I_c}{V_{be}} \times r_{be} = \frac{I_c}{I_b} = \beta$$

$$\therefore A_i = \frac{-\beta}{1 + s2\pi f C_i r_{be}} = \frac{-\beta}{1 + s \frac{f}{f_\beta}}$$

where  $f_\beta = \frac{1}{2\pi r_{be} C_i}$

$$|A_i| = \frac{\beta}{\sqrt{1 + \left(\frac{f}{f_\beta}\right)^2}} \quad \text{at } f = f_\beta \Rightarrow |A_i| = \frac{\beta}{\sqrt{2}}$$

$\therefore f_\beta \rightarrow \beta$  cut off frequency.

→ It is the frequency at which the CE short circuit current gain drops by 3dB or  $1/\sqrt{2}$  times from its value at low frequency.

→  $f_\alpha$ : It is the frequency at which the CB short circuit current gain drops by 3dB or  $1/\sqrt{2}$  times from its value at low frequency.

$$f_\alpha = \frac{1}{2\pi r_{be}(1+h_{fe})C_{be}} = \frac{1+h_{fe}}{2\pi r_{be}C_{be}}$$

$f_\alpha = \frac{f_\beta}{1+h_{fe}}$   
 $f_\beta = f_\alpha(1+h_{fe})$



Unity Gain frequency:-  $f_T$  - Transition freq

It is the frequency, at which CE short circuit current gain becomes unity. Hence it is called unity gain frequency or Bandwidth.

$$|A_i| = \frac{\beta}{\sqrt{1 + \left(\frac{f_T}{f_\beta}\right)^2}} = 1$$

$$\therefore f = f_T \Rightarrow |A_i| = 1$$

The ratio of  $f_T/f_\beta$  is quite large compared to 1, so  $f_T/f_\beta \gg 1 \Rightarrow f_T \gg f_\beta$

$$1 = \frac{\beta}{f_T/f_\beta} = \frac{\beta f_\beta}{f_T}$$

$$\therefore f_T = \beta f_\beta$$

Where  $f_T$  is the product of low frequency current gain  $h_{fe}$  or  $\beta$  and  $\beta$  cut off frequency or CE bandwidth.

$$\therefore f_T = h_{fe} \times \frac{1}{2\pi r_{b'e}(C_{b'e} + C_{b'c})}$$

$$= \frac{g_m r_{b'e}}{2\pi r_{b'e}(C_{b'e} + C_{b'c})} = \frac{g_m}{2\pi (C_{b'e} + C_{b'c})}$$

$$\left[ \begin{aligned} \therefore h_{fe} &= \frac{I_C}{I_B} \\ &= \frac{I_C}{V_{be}/\eta} \\ &= g_m r_b \end{aligned} \right]$$

since  $C_{b'c} \ll C_{b'e}$  <sup>3PF</sup>  ~~$C_{b'c}$~~  <sup>100PF</sup>

$$\therefore f_T = \frac{g_m}{2\pi C_{b'e}}$$


$$\therefore C_{b'e} = \frac{g_m}{2\pi f_T}$$

substituting  $f_\beta = \frac{f_T}{\beta}$  in  $A_i$ , then

$$A_i = \frac{-\beta}{1 + j \frac{\beta f}{f_T}}$$


→ This equation shows the dependence of transistor's short circuit current gain on the transistor's gain at low frequency  $\beta$  and the high frequency characteristics  $f_T$ .
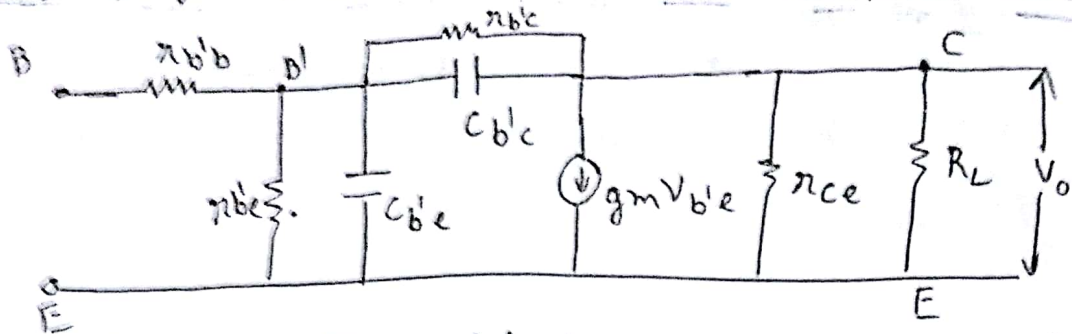
## High frequency Current Gain with Resistive Load:-



① Hybrid  $\pi$ -model for a single Transistor with Resistive Load

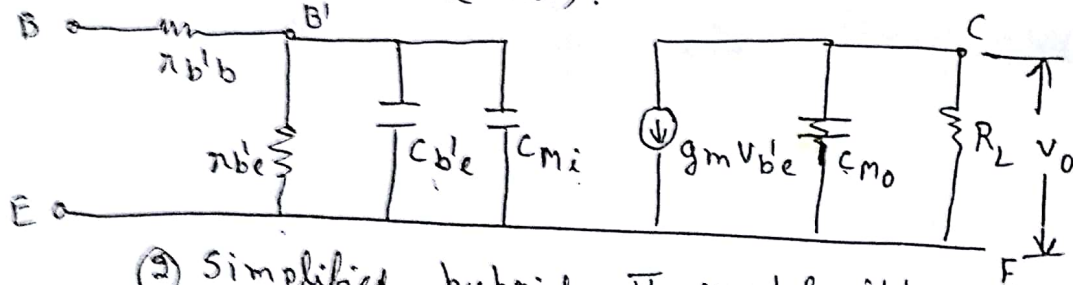- In the o/p circuit  $r_{ce}$  is parallel with  $R_L$ . For high freq amplifiers  $R_L$  is small as compared to  $r_{ce}$  (80k $\Omega$ ) and hence we can neglect  $r_{ce}$ .
- Using miller's theorem, we can split  $r_{b'c}$  and  $C_{b'c}$ . But  $r_{b'c}$  is neglecting here because it is high value (4M $\Omega$ ) comparing to  $r_{b'e}$  (1k $\Omega$ ).



② Simplified hybrid  $\pi$  model with Resistive Load

At input circuit:


where  $C_{mi} = C_{b'c} (1 - A_v)$

where  $A_v = \frac{V_o}{V_i} = \frac{-g_m V_{b'e} R_L}{V_{b'e}} = -g_m R_L$

$\therefore C_{mi} = C_{b'c} (1 + g_m R_L)$  — (1)

→ As  $C_{b'e}$  and  $C_{mi}$  are in parallel, the total capacitance is  $C_{eq} = C_{b'e} + C_{b'c} (1 + g_m R_L)$  — (2)

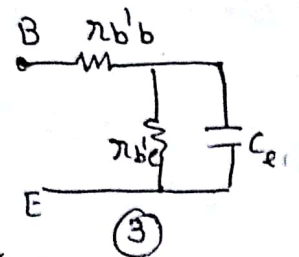
→ Due to this i/p capacitance of the circuit is increased.



At output circuit:-

$$C_{M0} = C_{b'c} \left(1 - \frac{1}{A_v}\right) \approx C_{b'c} \quad \text{--- (3)} \quad [\because A_v \gg 1]$$

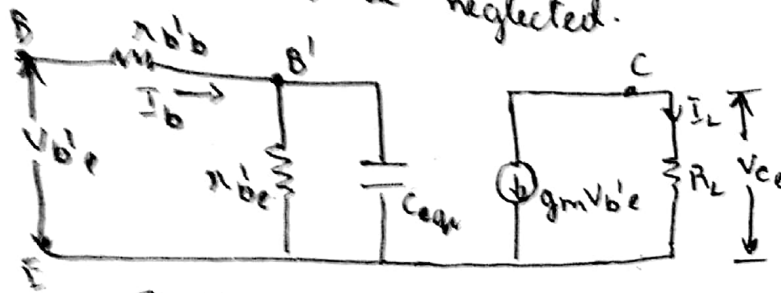→ As i/p capacitance  $C_{b'e} + C_{b'c}(1 + g_m R_L)$  is very high comparing with output capacitance  $C_{b'c}$ . Hence o/p capacitance is negligible in comparing with the i/p. So, we may be neglected.



$$z = r_{b'e} \parallel C_{eq}$$

$$z = r_{b'e} \times \frac{1}{1 + j\omega r_{b'e} C_{eq}}$$

$$z = \frac{r_{b'e}}{1 + j\omega r_{b'e} C_{eq}}$$

(4) Simplified hybrid  $\pi$ -Model

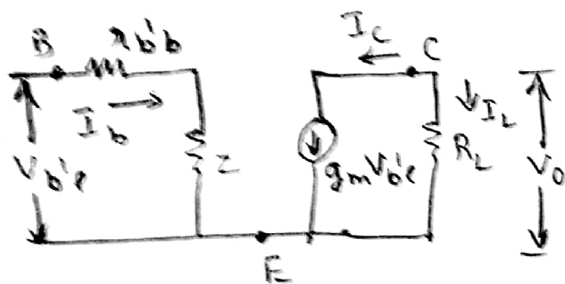


fig-(5)

∴ The current gain for the circuit

$$A_i = \frac{I_c}{I_b} = \frac{-g_m v_{b'e}}{I_b} = -g_m z$$

$$\therefore A_i = \frac{-g_m r_{b'e}}{1 + j\omega r_{b'e} C_{eq}} = -\beta \quad \left[ \because z = \frac{v_{b'e}}{I_b} \right]$$

$$\text{Let } f_H = \frac{1}{2\pi r_{b'e} C_{eq}}$$

$$\therefore A_i = \frac{-\beta}{1 + j\left(\frac{f}{f_H}\right)} \quad \text{--- (5)}$$

$$\therefore |A_i| = \frac{\beta}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}} \quad \text{--- (6)}$$

$$\text{if } f = f_H, \text{ then } |A_i| = \frac{\beta}{\sqrt{2}} \quad \text{--- (7)}$$

→ The  $f_H$  is the frequency at which the transistor's gain drops by 3dB or  $1/\sqrt{2}$  times from its value at low frequency.



$$\therefore f_H = \frac{1}{2\pi \tau_{b'e} C_{eq}} = \frac{1}{2\pi \tau_{b'e} [C_{b'e} + C_{b'c}(1 + g_m R_L)]}$$

At  $R_L = 0$ ,  $f_H = \frac{1}{2\pi \tau_{b'e} (C_{b'e} + C_{b'c})} = f_\beta$  — (9)

→ From eqn-(9) says that maximum possible value for  $f_H$  is  $f_\beta$ . As  $R_L$  increases,  $C_{eq}$  increases, then decreasing  $f_H$  as shown in fig (6).

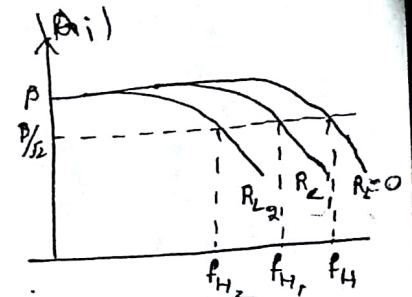


Fig-(6)

Relation between high frequency  $\pi$  and  $h$ -parameters — <sup>Low freq</sup>


Let us see how we can obtain all the resistive components in the hybrid- $\pi$  model from the  $h$ -parameters in the CE configuration.

① Transconductance:-

It is defined as the ratio of output current to the input voltage.

$$g_m = \frac{I_C}{V_{b'e}}$$
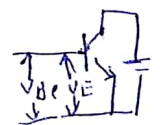
$$r_e = \frac{V_{b'e}}{I_E} \quad V_{b'e} = V_{b'e}$$



We know that  $I_C = \alpha I_E$  then  $g_m = \frac{\alpha I_E}{V_{b'e}}$  — (1)

but the emitter resistance  $r_e = \frac{V_{b'e}}{I_E}$  — (2)

$$\therefore g_m = \frac{\alpha V_{b'e}}{r_e \times V_{b'e}} = \frac{\alpha}{r_e}$$

$$r_e = \frac{V_T}{I_E}$$

The dynamic emitter resistance  $r_e$  is given as  $r_e = \frac{V_T}{I_E}$  where  $V_T = \frac{kT}{q}$

where  $k$  = boltzmann constant =  $1.36 \times 10^{-23} \text{ J/}^\circ\text{K}$

$$g_m = \frac{I_C}{V_{b'e}} = \frac{I_C}{V_T / I_E} = \frac{I_C I_E}{V_T}$$

$$r_e = \frac{V_T}{I_E}$$

$$g_m r_e = \frac{I_C I_E}{V_T} \times \frac{V_T}{I_E} = I_C$$

$$g_m r_e = \beta$$


$$g_m \tau_{b'e} = \beta$$

$T = 300^\circ K$ ,  $q = 1.6 \times 10^{-19} C$ ,  $V_T = \frac{T}{11,600} = 26 mV$   
 $\therefore g_m = \frac{I_C}{V_T} = \frac{I_C}{26 \times 10^{-3}} = \frac{1.3 \times 10^{-3}}{26 \times 10^{-3}} = 50 mS$

Note:-

Transconductance  $\propto$  collector current ( $I_C$ )  
 $\propto \frac{1}{Temp}$

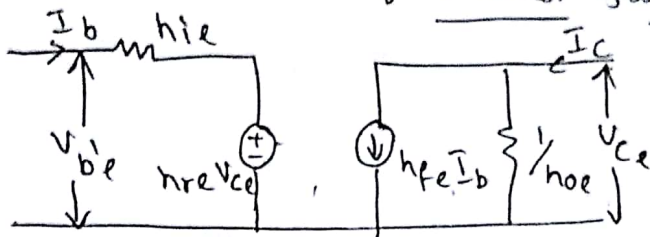② Input Resistance of emitter junction ( $r_{be}$ ):-




It can be obtained by low frequency h-parameter model.

$$v_{be} = h_{ie} I_b + h_{re} v_{ce} \quad \text{--- (1)}$$


$$I_C = h_{fe} I_b + h_{oe} v_{ce} \quad \text{--- (2)}$$

$$\therefore h_{fe} = I_C / I_b \big|_{v_{ce}=0} \quad \text{--- (3)}$$

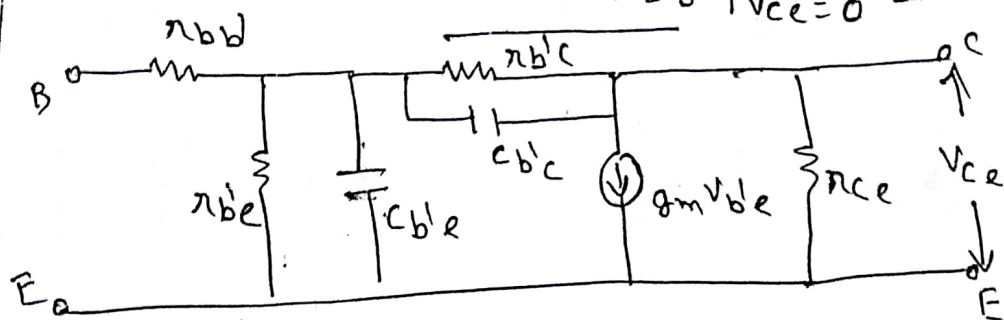

At low frequency, the hybrid  $\pi$  model when  $v_{ce}$  i.e short circuited at output side,  $r_{ce}$  can be neglected

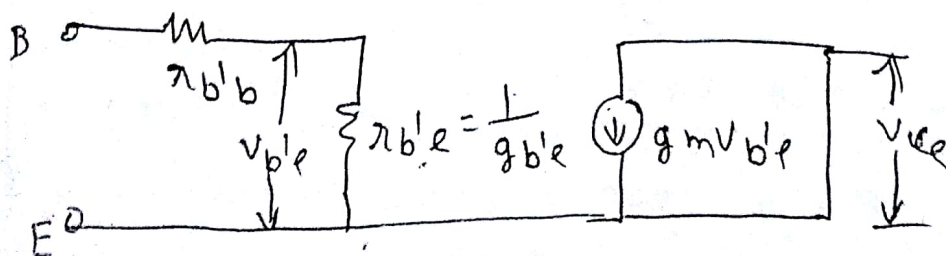$\rightarrow r_{bc} \gg r_{be}$ ,  $\therefore r_{bc}$  is neglected.





By looking at the o/p circuit, the collector current

$$I_c = g_m V_{b'e}$$

$$I_c = g_m I_b r_{b'e}$$

$$\frac{I_c}{I_b} = g_m r_{b'e}$$

from eqn (3)  $\frac{I_c}{I_b} = h_{fe}$



$$\therefore h_{fe} = g_m r_{b'e}$$

We know that  $r_{b'e} = \frac{h_{fe}}{g_m} = \frac{50}{50 \times 10^{-3}} = 1 \text{ k}\Omega$

$$\therefore \text{Input conductance } g_{b'e} = \frac{g_m}{h_{fe}}$$

Note:-  $g_{b'e} = \frac{g_m}{h_{fe}} = \frac{I_c}{V_T \cdot h_{fe}} \therefore g_{b'e} \propto I_c$   
 $\propto \frac{1}{\text{Temp.}}$

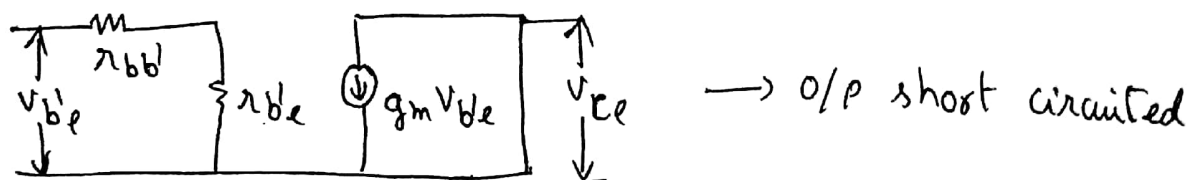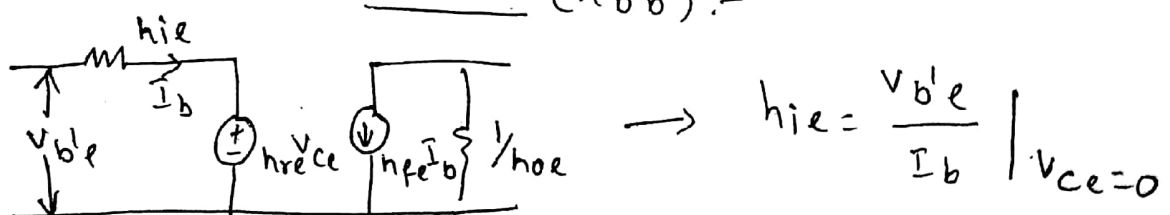③ Base Spreading Resistance ( $r_{bb'}$ ):-



$$h_{ie} = r_{bb'} + r_{b'e}$$


$$r_{bb'} = h_{ie} - r_{b'e}$$

$$= 1100 - 1000 = 100 \Omega$$

curve (4) Resistance of collector junction ( $r_{b'c}$ ) or feedback resist

eqn ①  $V_{b'e} = h_{ie} I_b + h_{re} V_{ce}$  — ①

$$h_{re} = \frac{V_{b'e}}{V_{ce}} \quad | \quad I_b = 0$$

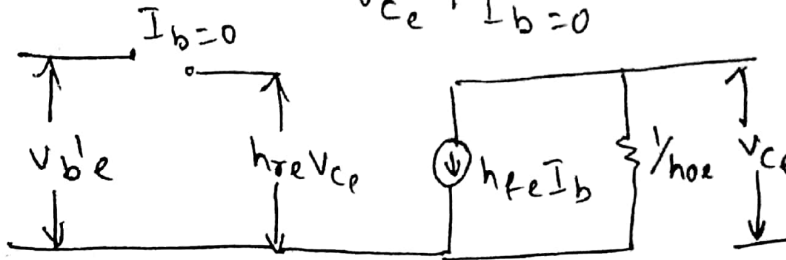

$$\therefore V_{b'e} = h_{re} V_{ce}$$



$$V_{b'e} = \frac{V_{ce} \times r_{b'e}}{r_{b'e} + r_{b'c}}$$

$$\frac{V_{b'e}}{V_{ce}} = \frac{r_{b'e}}{r_{b'e} + r_{b'c}}$$

$$\therefore h_{re} = \frac{r_{b'e}}{r_{b'e} + r_{b'c}}$$

$$\therefore h_{re} (r_{b'e} + r_{b'c}) = r_{b'e}$$

$$r_{b'c} = \frac{r_{b'e} - h_{re} r_{b'e}}{h_{re}} = 4 \text{ M}\Omega \approx 3.999 \text{ M}\Omega$$

$$r_{b'c} = \frac{r_{b'e} (1 - h_{re})}{h_{re}} = \frac{r_{b'e}}{h_{re}} \quad [\because 1 - h_{re} \approx 1]$$


$$\therefore r_{b'c} = \frac{r_{b'e}}{h_{re}}$$

$$(or) g_{b'c} = \frac{h_{re}}{r_{b'e}} = h_{re} g_{b'e}$$
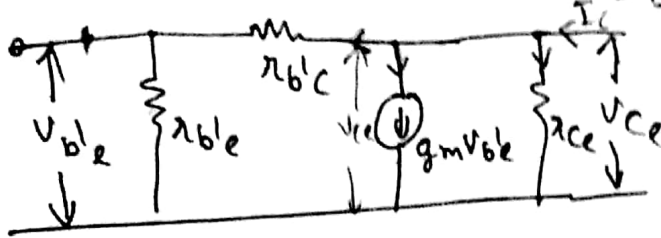
### ⑤ Output Resistance ( $r_{ce}$ ):-

eqn (2)  $I_c = h_{fe} I_b + h_{oe} V_{ce}$

$\therefore h_{oe} = I_c / V_{ce} \mid I_b = 0$



$$I_c = \frac{V_{ce}}{r_{ce}} + g_m V_{be} + \frac{V_{ce}}{r_{b'e} + r_{b'c}}$$

~~$\therefore V_{be} = \frac{V_{ce} r_{b'c}}{r_{b'e} + r_{b'c}}$~~

$$= V_{ce} \left[ \frac{1}{r_{ce}} + \frac{g_m r_{b'c}}{r_{b'e} + r_{b'c}} + \frac{1}{r_{b'e} + r_{b'c}} \right]$$

X  $\therefore h_{oe} = \frac{I_c}{V_{ce}} = g_{ce} + \frac{g_m r_{b'c}}{r_{b'e} + r_{b'c}} + \frac{1}{r_{b'e} + r_{b'c}}$

$$= g_{ce} + \frac{h_{fe} + 1}{r_{b'e} + r_{b'c}}$$

$\left[ \because g_m r_{b'e} = h_{fe} \right]$

$$= g_{ce} + \frac{h_{fe}}{r_{b'c}}$$

$\left[ \because h_{fe} \gg 1 \right]$

$\left[ r_{b'c} \gg r_{b'e} \right]$

$\therefore h_{oe} = g_{ce} + g_{b'c} h_{fe}$

$g_{ce} = h_{oe} - g_{b'c} h_{fe} = \frac{1}{r_{ce}}$

$h_{oe} = \frac{I_c}{V_{ce}} = g_{ce} + h_{fe} g_{b'e} h_{re} + g_{b'c}$

$$= g_{ce} + g_{b'e} h_{fe} \frac{g_{b'c}}{g_{b'e}} + g_{b'c}$$

$\therefore g_{ce} = h_{oe} - g_{b'c} (1 + h_{fe})$

$\left[ \because g_m = \frac{h_{fe}}{r_{b'e}} = h_f \right]$   
 $\left[ h_{re} = \frac{V_{b'e}}{V_{ce}} \right]$   
 $\left[ r_{b'c} \gg r_{b'e} \right]$



## ⑥ Diffusion capacitance ( $C_{b'e}$ ):-

It is also represented as  $C_{\pi}$  in hybrid- $\pi$  model.  $C_{b'e}$  is determined from a measurement of  $f_T$ , the frequency at which the CE short-circuit current gain drops to unity. It is given by

$$C_{b'e} = \frac{g_m}{2\pi f_T}$$

$$\because f_T = \frac{g_m}{2\pi C_{b'e}}$$

## ⑦ Transition capacitance ( $C_{b'c}$ ):-

It is also represented as  $C_{\mu}$  in hybrid- $\pi$  model.  $C_{\mu} = C_{b'c}$  is measured as a CB o/p capacitance with i/p open ( $I_E = 0$ ), and is usually specified by manufacturer as  $C_{ob}$  (open circuit base capacitance).

## Relation between Low freq h-parameters and High freq $\pi$ Parameters.

$$g_m = \frac{I_C}{V_T} = 50 \text{ mA/V}$$

$$r_{b'e} = \frac{h_{fe}}{g_m} = 1 \text{ k}\Omega = \frac{1}{g_{b'e}}$$


$$r_{bb'} = h_{ie} - r_{b'e} = 100 \Omega$$

$$r_{b'c} = \frac{1}{g_{b'c}} = \frac{r_{b'e}}{h_{re}}$$


$$g_{ce} = \frac{1}{r_{ce}} = h_{oe} - (1 + h_{fe})g_{b'c}$$

$$C_{b'e} = \frac{g_m}{2\pi f_T}$$

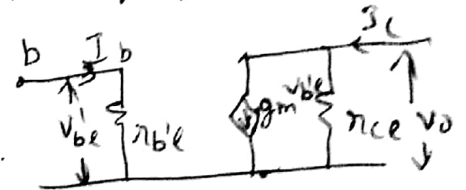Hybrid  $\pi$  model on  
→ Low freq Small signal



→  $r_e$  model

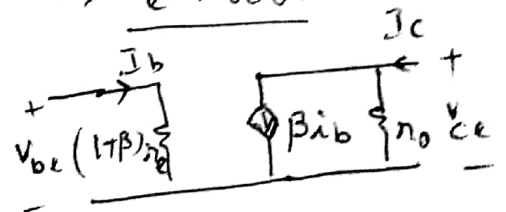

VCCS —  $g_m v_{b'e}$   
CCCS —  $\beta I_b$

### 3.10 Gain Bandwidth Product

#### 3.10.1 Gain Bandwidth Product for Voltage

The gain bandwidth product for voltage gain is given as

$$\begin{aligned}
 |A_{vs \text{ low}} f_H| &= |A_{vso} f_H| = \frac{-h_{fe} R_L}{R_s + h_{ie}} \times \frac{1}{2\pi R_{eq} C_{eq}} \\
 &= \frac{-h_{fe} R_L}{R_s + h_{ie}} \times \frac{1}{2\pi C_{eq} \left[ \frac{r_{b'e} (r_{bb'} + R_s)}{r_{b'e} + r_{bb'} + R_s} \right]} \\
 &= \frac{-h_{fe} R_L}{R_s + h_{ie}} \times \frac{1}{2\pi C_{eq} \left[ \frac{r_{b'e} (r_{bb'} + R_s)}{(R_s + h_{ie})} \right]}
 \end{aligned}$$

$$\begin{aligned}
 \therefore h_{ie} &= r_{b'e} + r_{bb'} \\
 &= \frac{-h_{fe} R_L}{2\pi C_{eq} r_{b'e} (r_{bb'} + R_s)} \\
 &= \frac{-g_m r_{b'e} R_L}{2\pi C_{eq} r_{b'e} (r_{bb'} + R_s)} \quad \because h_{fe} = g_m r_{b'e} \\
 &= \frac{-g_m R_L}{2\pi C_{eq} (r_{bb'} + R_s)} \quad \dots (1)
 \end{aligned}$$

This equation can be further simplified as follows.

$$\begin{aligned}
 |A_{vso} \times f_H| &= \frac{g_m}{2\pi [C_e + C_C (1 + g_m R_L)]} \times \frac{R_L}{R_s + r_{bb'}} \\
 \therefore C_{eq} &= C_e + C_C (1 + g_m R_L) \\
 &= \frac{g_m}{2\pi [C_e + C_C + g_m R_L]} \times \frac{R_L}{R_s + r_{bb'}} \quad \because g_m R_L \gg 1 \\
 &= \frac{R_L}{R_s + r_{bb'}} \times \frac{2\pi f_T C_e}{2\pi [C_e + C_C (2\pi f_T C_e) R_L]} \\
 \therefore g_m &= 2\pi f_T C_e \\
 &= \frac{R_L}{R_s + r_{bb'}} \times \frac{2\pi C_e f_T}{2\pi C_e [1 + 2\pi f_T C_C R_L]} \\
 &= \frac{R_L}{R_s + r_{bb'}} \times \frac{f_T}{1 + 2\pi f_T C_C R_L} \\
 \therefore |A_{vso} \times f_H| &= \frac{R_L}{R_s + r_{bb'}} \times \frac{f_T}{1 + 2\pi f_T C_C R_L} \quad \dots (2)
 \end{aligned}$$