


## UNIT - II

### Operational Amplifier and Applications


Operational amplifier is having so many applications and it can be classified based on characteristics of operational amplifier.

1. Linear op. Amplifier

2. Non-linear op. Amplifier

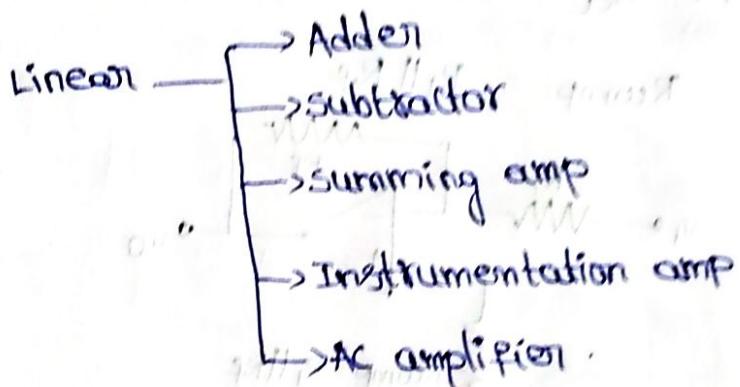

#### Non-linear

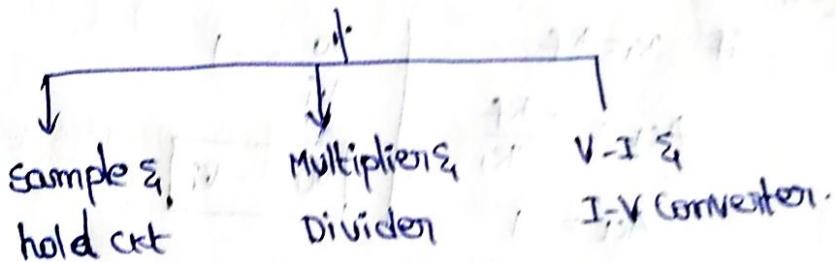


#### \* Basic Applications of op-Amplifier:

We are having 3 types of basic op. Amplifier

1. scalar / Inverter

2. summing inverter

3. Adder / subtractor

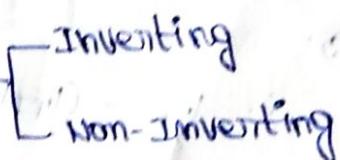

## 1. scalar / inverter ckt:-

scalar!:-


$$A_{CL} = -\frac{R_F}{R_1}$$

$$\text{Let us assume } K = -\frac{R_F}{R_1}$$

when  $R_{comp}$  is added to the non-inverting terminal  
the 'K' is acts as scalar ckt.

$$\text{i.e. } A_{CL} = -K \quad \therefore (R_1 + R_F)$$

$$R_{comp} = R_1 \parallel R_F$$

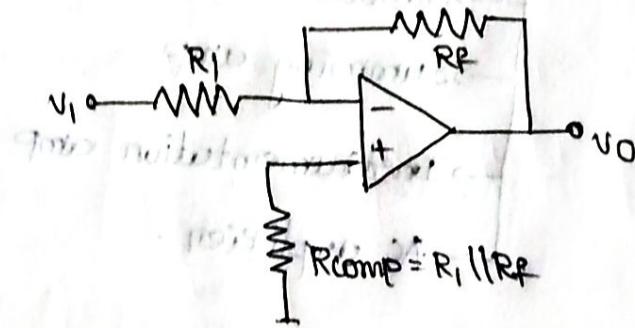

inverter!:-

$$\text{if } R_1 = R_F$$

$$A_{CL} = -\frac{R_F}{R_1}$$

$$A_{CL} = -1$$

$$\frac{V_O}{V_I} = -1$$

$$V_O = -V_I$$


## 2. Summing Amplifier!

This circuit is used to design the op signal is equal to summation of all the ip signals.

$$\text{V}_O = -(V_1 + V_2 + V_3 + \dots) \text{ for inverting}$$

$$V_O = V_1 + V_2 + V_3 + \dots \text{ for non-inverting}$$

### i) Inverting summing amplifier:-

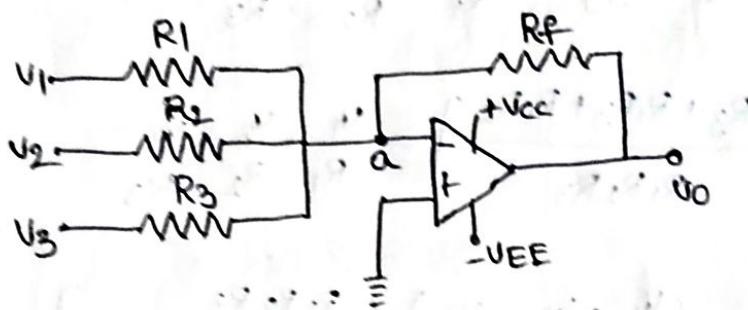

Apply KCL at node 'a'

$$\frac{Va - V_1}{R_1} + \frac{Va - V_2}{R_2} + \frac{Va - V_3}{R_3} = \frac{V_O - Va}{R_F}$$

$V_A \cdot K \cdot T \Rightarrow V_A = 0$  [from virtual ground concept]


$$-\left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] = \frac{V_O}{R_F}$$

$$-R_F \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] = V_O$$

Assume  $R_1 = R_2 = R_3 = R_f$

$$\therefore V_O = -(V_1 + V_2 + V_3)$$
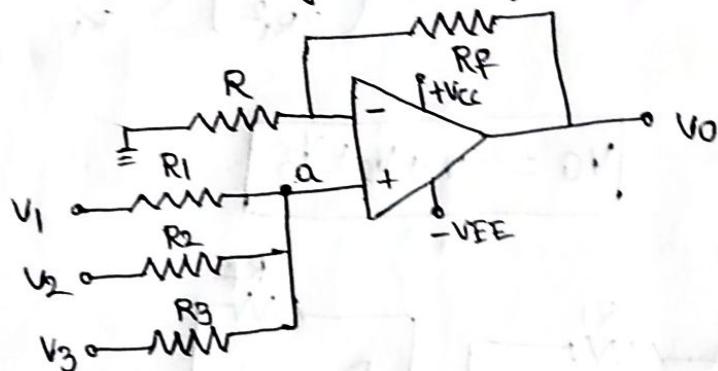
### ii) Non-inverting summing Amplifier:-



Apply KCL at node 'a'

$$\frac{Va - V_1}{R_1} + \frac{Va - V_2}{R_2} + \frac{Va - V_3}{R_3} = 0$$

$$\frac{Va}{R_1} - \frac{V_1}{R_1} + \frac{Va}{R_2} - \frac{V_2}{R_2} + \frac{Va}{R_3} - \frac{V_3}{R_3} = 0$$

$$V_A \left[ \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$V_A \left[ \frac{R_2 R_3 + R_1 R_3 + R_1 R_2}{R_1 R_2 R_3} \right] = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

$$V_A = \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right) \left( \frac{R_1 R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2} \right)$$

$$A_{CL} = 1 + \frac{R_F}{R}$$

$$\frac{V_O}{V_i} = 1 + \frac{R_F}{R}$$

$$V_O = \left( 1 + \frac{R_F}{R} \right) V_A \quad [ \because V_i = V_A ]$$

if  $R_1 = R_2 = R_3 \Rightarrow V_O = \left( 1 + \frac{R_F}{R} \right) \left[ \frac{V_1 + V_2 + V_3}{R_1 + R_2 + R_3} \right]$


$$R_F = 2R$$

$$V_O = \left( 1 + \frac{2R}{R} \right) \left[ \frac{\frac{R_1}{R}}{R_1^2 + R_2^2 + R_3^2} \right] \left[ \frac{V_1 + V_2 + V_3}{R_1} \right]$$

$$= (1+2) \left( \frac{R_1^2}{3R^2} \right) \left( \frac{V_1 + V_2 + V_3}{R_1} \right)$$

$$V_O = V_1 + V_2 + V_3$$

3. Adder :-

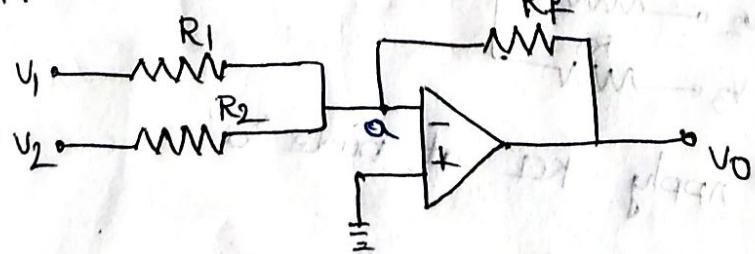

$$\frac{V_A - V_1}{R_1} + \frac{V_A - V_2}{R_2} = \frac{V_O - V_A}{R_f}$$

$$V_A = 0$$


$$-\left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} \right] = \frac{V_o}{R_f}$$

$$-R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = V_o$$

$$R_1 = R_2 = R_3 = R_f$$

$$\therefore V_o = -(V_1 + V_2)$$

Subtractor:-

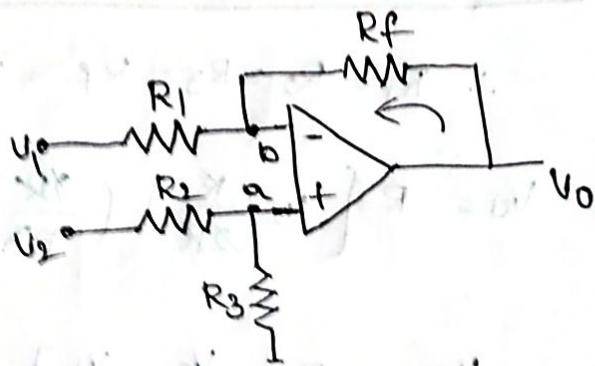

Apply KCL at node 'b'

$$\frac{V_b - V_1}{R_1} + \frac{V_b - V_o}{R_f} = 0$$

At node 'a'

$$\frac{V_a - V_2}{R_2} + \frac{V_a}{R_3} = 0 \quad \text{--- (1)}$$

From eq (1) ...

$$\frac{V_b}{R_1} - \frac{V_1}{R_1} + \frac{V_b}{R_f} - \frac{V_o}{R_f} = 0$$

$$V_b \left[ \frac{1}{R_1} + \frac{1}{R_f} \right] = \frac{V_1}{R_1} + \frac{V_o}{R_f}$$

$$V_b = \left( \frac{V_1}{R_1} + \frac{V_o}{R_f} \right) \left( \frac{R_1 R_f}{R_1 + R_f} \right) \quad \text{--- (2)}$$

From eq (2)

$$V_a \left[ \frac{1}{R_2} + \frac{1}{R_3} \right] = \frac{V_2}{R_2} \quad \text{--- (3)}$$

$$V_a = \frac{V_2}{R_2} \left[ \frac{R_2 R_3}{R_2 + R_3} \right] = V_2 \left[ \frac{R_3}{R_2 + R_3} \right]$$

From eq (3)

$$V_O = R_F \left[ V_B \left( \frac{1}{R_1} + \frac{1}{R_F} \right) - \frac{V_1}{R_1} \right]$$

$$\therefore V_A = V_B$$

$$V_O = R_F \left[ V_2 \cdot \left( \frac{R_3}{R_2 + R_3} \right) \left( \frac{R_1 + R_F}{R_1 R_F} \right) - \frac{V_1}{R_1} \right]$$

$$\therefore R_1 = R_2 = R_3 = R_F = R$$



$$V_O = R \left[ V_2 \left( \frac{R}{2R} \right) \left( \frac{2R}{R^2} \right) - \frac{V_1}{R} \right]$$

$$V_O = R \left[ \frac{V_2}{R} - \frac{V_1}{R} \right]$$


$$V_O = \frac{R}{R} (V_2 - V_1)$$

$$V_O = V_2 - V_1$$

Adder-subtractor using op-amp :-

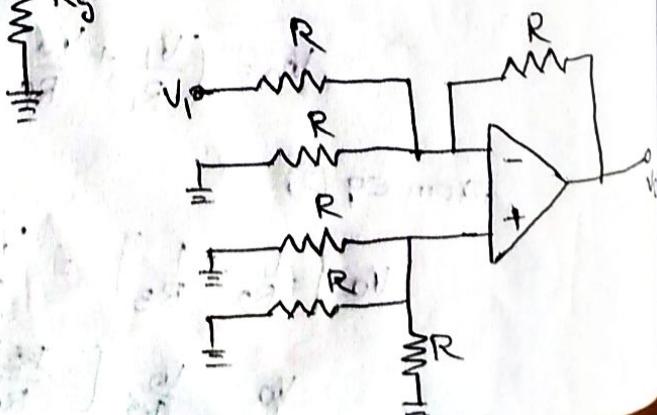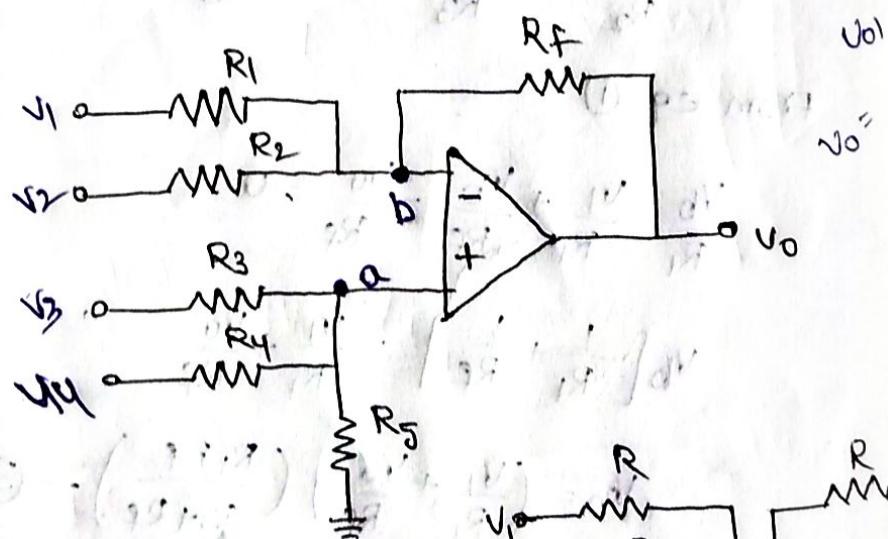

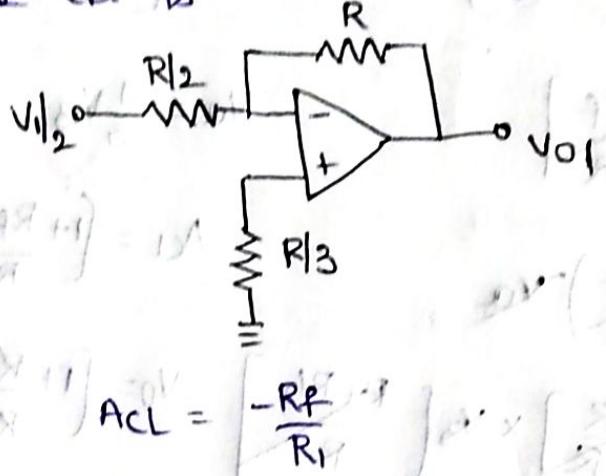case-i:- when  $v_1$  is active and remaining one inactive  
then the circuit is



$R_{13}$

$R_{13}$

$R_{13}$

$$A_{CL} = -\frac{R_f}{R_i}$$



$$\frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

$$V_o = \left[ \frac{R_f}{R_i} \right] V_i \quad \text{--- (1)}$$



$$V_o = -\left[ \frac{R}{R_{12}} \right] \left[ \frac{V_1}{2} \right]$$

$$V_{01} = -V_1$$

case-ii:- when  $v_2$  is active.

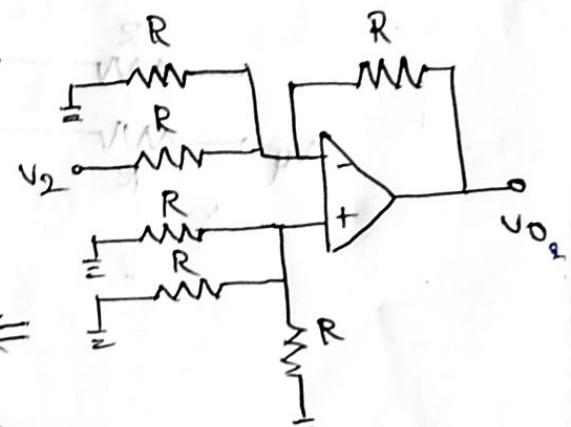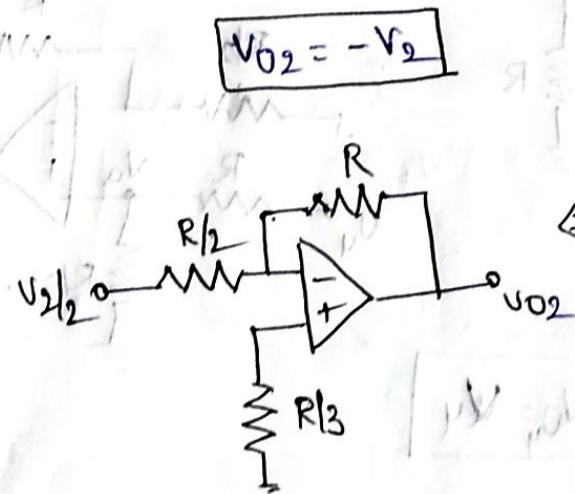

case-iii:-  $v_3$  is active

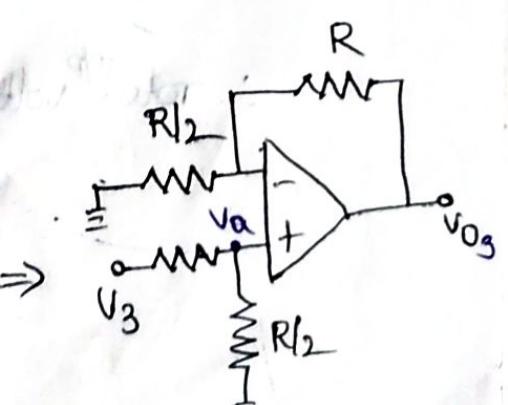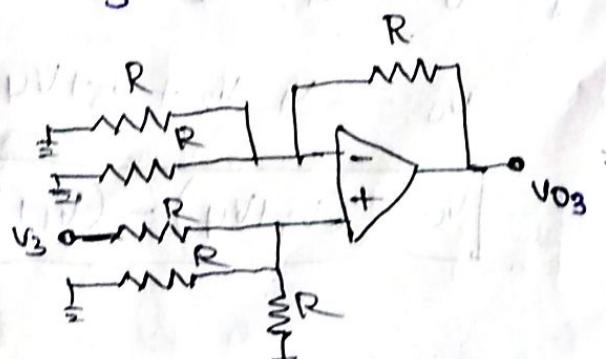

$$V_3 = V_a \left[ \frac{R}{R+R/2} \right] \Rightarrow V_a = V_3 \left[ \frac{R+R/2}{R} \right]$$

$$\frac{V_0}{V_a} = \left[ 1 + \frac{R_f}{R} \right]$$

$$V_a = \frac{1}{3} V_3$$

$$A_{CL} = \left( 1 + \frac{R_f}{R} \right) = \frac{V_0}{V_3}$$

$$V_0 = \left( 1 + \frac{R_f}{R} \right) V_a$$

$$= \left( 1 + \frac{R}{R} \right) \times V_3 \left[ \frac{R+R/2}{R} \right]$$



$$V_0 = \left[ 1 + \frac{R}{R/2} \right] \frac{V_3}{3}$$

$$= 2 \times V_3 \left[ \frac{2R+R}{2R} \right]$$

$$V_0 = (1+2) \times \frac{V_3}{3}$$

$$V_0 = V_3$$

Case 4:-  $V_4$  is active.

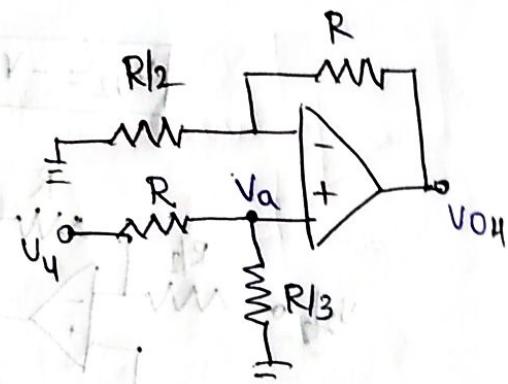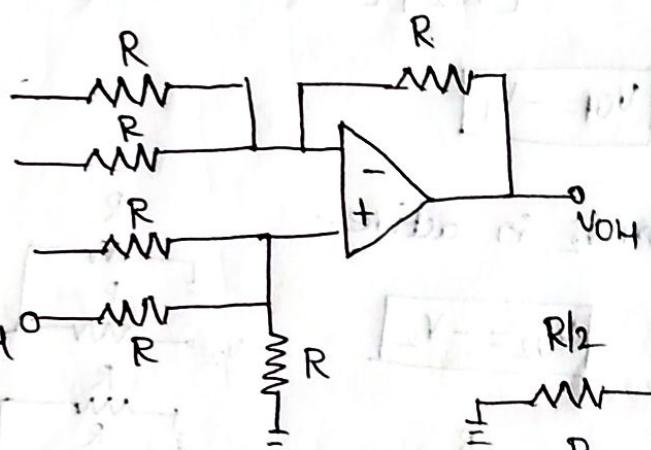

Similarly,

$$V_0 = V_4$$


$$\text{Total op voltage } V_0 = V_{01} + V_{02} + V_{03} + V_{04}$$

$$V_0 = -V_1 - V_2 + V_3 + V_4$$

$$V_0 = (V_3 + V_4) - (V_1 + V_2)$$

# ① Adder of Inverting Op-Amp

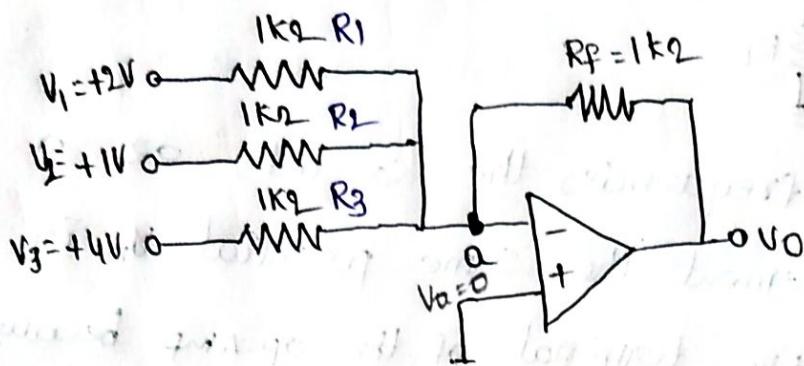Problem:- Find the  $V_o$  of the given circuit.



Sol:-

given that,

$$V_1 = +2V$$

$$V_2 = +1V$$

$$V_3 = +4V$$

$$R_1 = R_2 = R_3 = R_f = 1k\Omega$$

$$V_o = ?$$

formula:-

$$V_o = -R_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] \quad (1)$$

Substitute the values in eq (1)

$$V_o = -1 \times 10^3 \left[ \frac{2}{1 \times 10^3} + \frac{1}{1 \times 10^3} + \frac{4}{1 \times 10^3} \right]$$

$$= -\frac{1 \times 10^3}{1 \times 10^3} [2 + 1 + 4]$$

$$\therefore V_o = -7V$$

$$A_{CL} = -\frac{R_f}{R_{in}}$$


$$\frac{V_o}{V_{in}} = -\frac{R_f}{R_{in}}$$

$$V_o = -R_f \times \frac{V_{in}}{R_{in}}$$

$$V_o = -R_f \times \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right]$$

② Adder of non-inverting op-amp :-

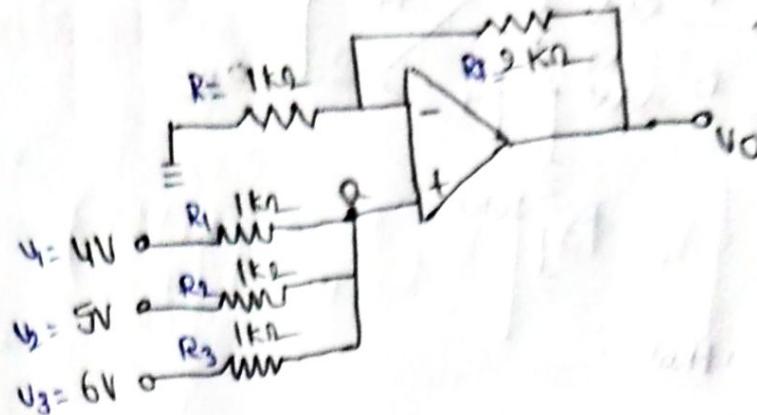problem:- Find the  $V_o$  of the given circuit.



Sol:-

given that,

$$V_1 = 4V$$

$$V_2 = 5V$$

$$V_3 = 6V$$

$$R_f = 2k\Omega$$

$$R = 1k\Omega$$

$$R_1 = R_2 = R_3 = 1k\Omega$$

$$V_o = ?$$

$$A_{CL} = 1 + \frac{R_f}{R}$$

$$\frac{V_o}{V_{in}} = \left(1 + \frac{R_f}{R}\right)$$

$$V_{in} = V_2$$

$$V_o = \left(1 + \frac{R_f}{R}\right) V_2$$

$$V_o = \left[ \frac{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) + 1} \right] V_2$$

formula:-

$$V_o = \left(1 + \frac{R_f}{R}\right) \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right] \left[ \frac{R_1 R_2 R_3}{R_2 R_3 + R_1 R_3 + R_1 R_2} \right]$$

Substitute the values in eq ①


$$V_o = \left(1 + \frac{2}{1}\right) \left[ \frac{4}{1} + \frac{5}{1} + \frac{6}{1} \right] \left[ \frac{1 \times 1 \times 1}{1 + 1 + 1} \right]$$

$$= 3 \times [4 + 5 + 6] \times \frac{1}{3}$$

$$= 15V$$

$$\therefore V_o = 15V$$

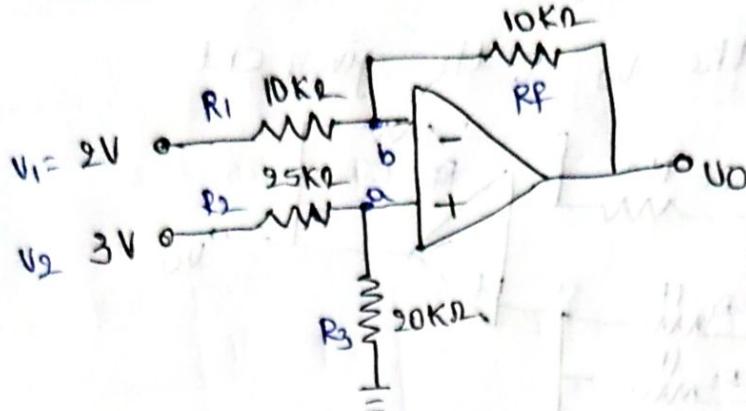③ Subtractor: - Find  $V_O$  of the given ckt.



Sol:- Given that,

$$V_1 = 2V$$

$$V_2 = 3V$$

$$R_1 = 10k\Omega$$

$$R_2 = 25k\Omega$$

$$R_3 = 20k\Omega$$


$$R_F = 10k\Omega$$

$$V_O = ?$$

Method 1:-

Case i): if  $V_1$  is active,  $V_2$  is inactive.

$$A_{CL} = -\frac{R_F}{R_{in}}$$

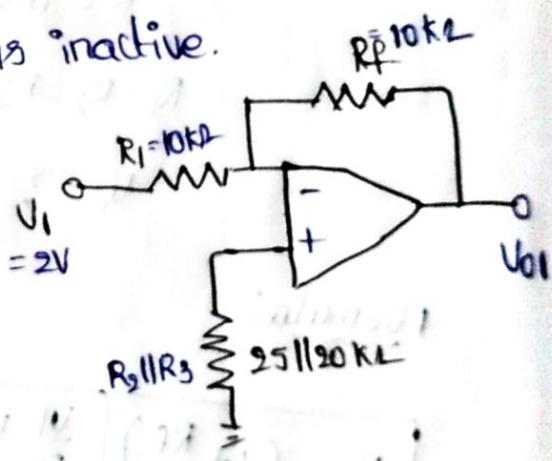

$$\frac{V_O}{V_{in}} = -\frac{R_F}{R_{in}}$$

$$V_{O1} = -\frac{R_F}{R_1} (V_1) \quad \text{--- ①}$$

Substitute the values in eq ①

$$V_{O1} = -\frac{10 \times 10^3}{10 \times 10^3} \times 2$$

$$V_{O1} = -2V$$

Case iii) :- If  $V_2$  is active,  $V_1$  is inactive.

$$A_{CL} = \left(1 + \frac{R_F}{R}\right)$$

$$\frac{V_{O2}}{V_{in}} = \left(1 + \frac{R_F}{R}\right)$$

$$\text{where } V_{in} = V_a$$

$$V_{O2} = \left(1 + \frac{R_F}{R}\right) V_a$$

$$\therefore V_{O2} = \left(1 + \frac{R_F}{R}\right) \times \frac{V_2}{R_2} \times \left[ \frac{R_2 R_3}{R_2 + R_3} \right] \quad \boxed{2}$$

$$\frac{V_a - V_2}{R_2} - \frac{V_a}{R_3} = 0$$

$$V_a \left[ \frac{1}{R_2} + \frac{1}{R_3} \right] = \frac{V_2}{R_2}$$

$$V_a = V_2 \times \left[ \frac{R_2 R_3}{R_2 + R_3} \right]$$

Sub. values in eq ②

$$V_{O2} = \left(1 + \frac{10 \times 10^3}{10 \times 10^3}\right) \times \frac{3}{25 \times 10^3} \left( \frac{25 \times 10^3 \times 20 \times 10^3}{(25+20) \times 10^3} \right)$$

$$= (1+1) \times \frac{3}{25} \times \frac{20}{45}$$

$$= 2 \times 3 \times \frac{20}{45} \times \frac{4}{3} = \frac{8}{3}$$

$$\therefore V_{O2} = \frac{8}{3} V$$

Total voltage


$$V_o = V_{O1} + V_{O2} \quad \boxed{3}$$

Sub values in eq ③

$$V_o = -2 + \frac{8}{3}$$

$$= -2 + \frac{8}{3} = \frac{2}{3}$$

$$V_o = 0.66 V$$

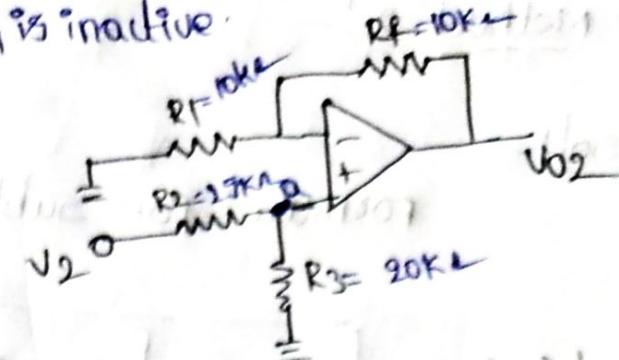

### Method 2:-

Sol:-

formula for subtractor,

$$V_0 = R_F \left[ V_2 \times \left( \frac{R_3}{R_2 + R_3} \right) \times \left( \frac{R_1 + R_F}{R_1 R_F} \right) - \frac{V_1}{R_1} \right]$$

—①

sub values in eq ①

$$V_0 = 10 \times 10^3 \left[ 3 \times \frac{20 \times 10^3}{25 \times 10^3 + 20 \times 10^3} \times \frac{\frac{10 \times 10^3 + 10 \times 10^3}{10 \times 10^3 \times 10 \times 10^3}}{10 \times 10^3} - \frac{2}{10 \times 10^3} \right]$$

$$= 10 \times 10^3 \left[ \frac{3 \times 20 \times 10^3}{(25+20) \times 10^3} \times \frac{(10+10) \times 10^3}{10 \times 10^3 \times 10 \times 10^3} - \frac{2}{10 \times 10^3} \right]$$

$$= \frac{10 \times 10^3}{(10 \times 10^3)} \left[ \frac{3 \times 20 \times 20}{45 \times 10} - \frac{2}{1} \right]$$


$$= \frac{10 \times 3 \times 40}{30 \times 45} - 2 = \frac{8}{3} - 2 = \frac{8}{3}$$

$$= 0.66 \text{ V}$$

$$\therefore V_0 = 0.66 \text{ V}$$

Q) Adder-subtractor

problem:- Find  $V_{O1}$  of given ckt

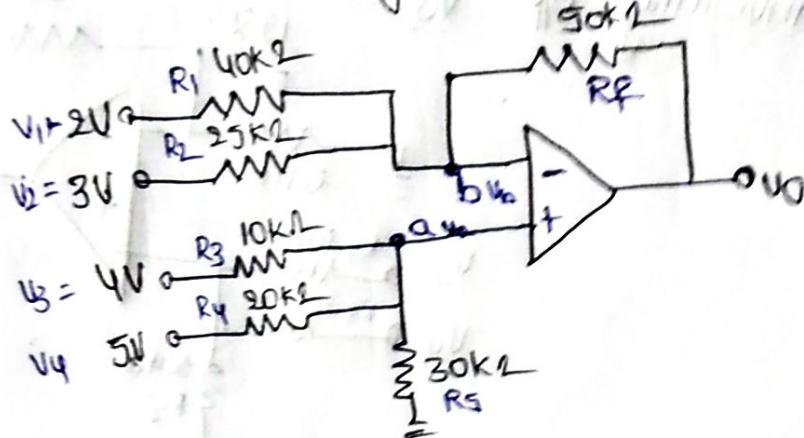

Sol:-

Given that,

$$V_1 = 2V$$

$$R_1 = 40k\Omega$$

$$V_2 = 3V$$

$$R_2 = 25k\Omega$$

$$V_3 = 4V$$

$$R_3 = 10k\Omega$$

$$V_4 = 5V$$

$$R_4 = 20k\Omega$$

$$V_5 = 5V$$


$$R_5 = 30k\Omega$$

$$R_f = 50k\Omega$$

$$\therefore V_{O1} = ?$$

→ If  $V_a$  is inactive  $V_b$  is active then the op-amp is

inverting op  $V_{O1}$

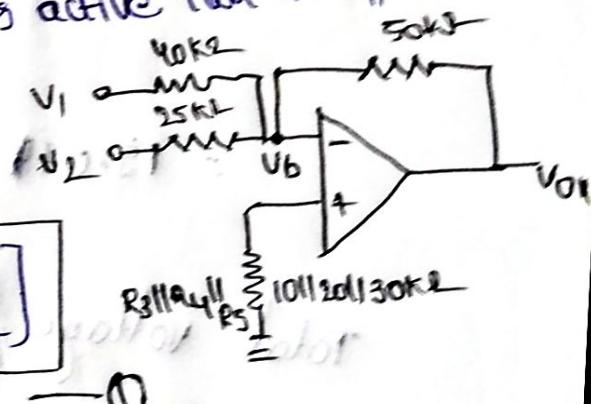

$$\therefore V_{O1} = -R_f \left[ \frac{V_1}{R_1} + \frac{V_2}{R_2} \right]$$


Sub values in eq(1)

$$V_{O1} = -50 \times 10^3 \left[ \frac{2}{40 \times 10^3} + \frac{3}{25 \times 10^3} \right]$$

$$= -\frac{50 \times 10^3}{125} \left[ \frac{2}{40} + \frac{3}{25} \right] = -8.2V$$

$$V_{O1} = -8.2V$$

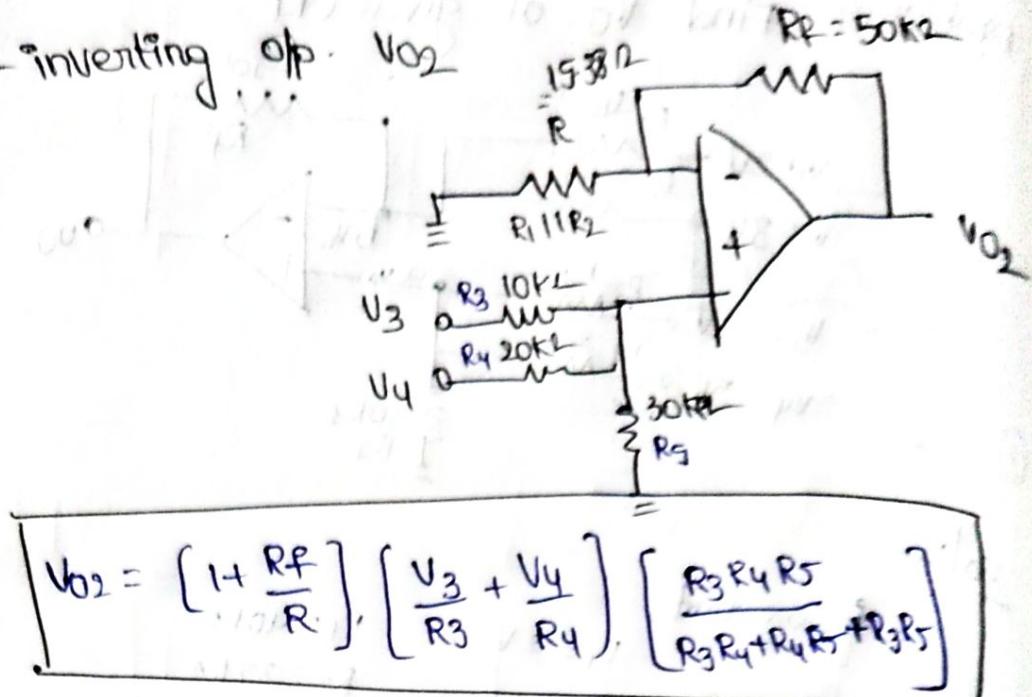→ if  $V_a$  is active,  $V_b$  is inactive then the op-amp is non-inverting op-amp.  $V_{o2}$



Sub values in eq ②

$$V_{o2} = \left[ 1 + \frac{50}{15.30} \right] \times \left[ \frac{4}{10 \times 10^3} + \frac{5}{20 \times 10^3} \right] \left[ \frac{10 \times 20 \times 30 \times 10^{-3}}{(10 \times 20) + (20 \times 30) + (10 \times 30)} \right]$$


$$= 15.071$$

Total Voltage,  $V_o = V_{o1} + V_{o2}$

$$\therefore V_o = -28.2 + 15.071$$

$$V_o = 6.87 \text{ V}$$

(2)

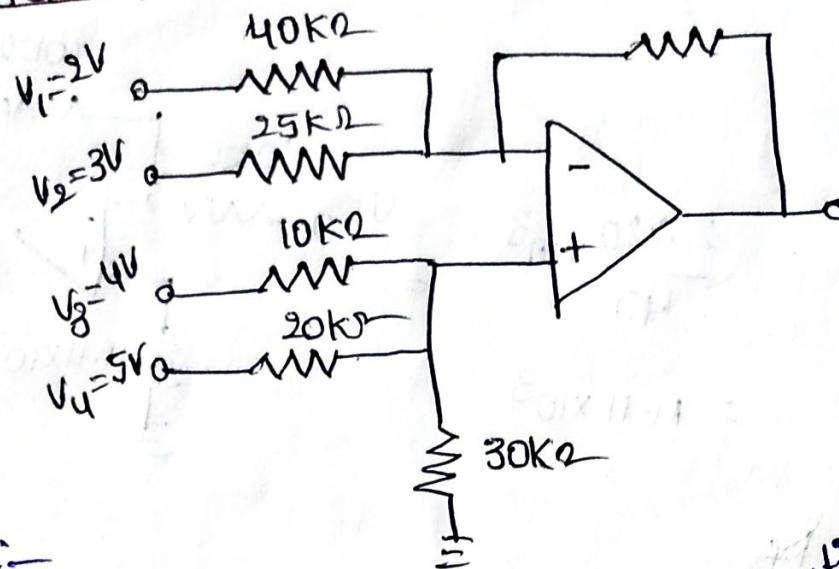
Method 2:

$$R = 50\text{k}\Omega$$

Find  $V_0$ .Sol:-

Case (i) :-  $V_1$  is active,  $V_2, V_3, V_4$  inactive
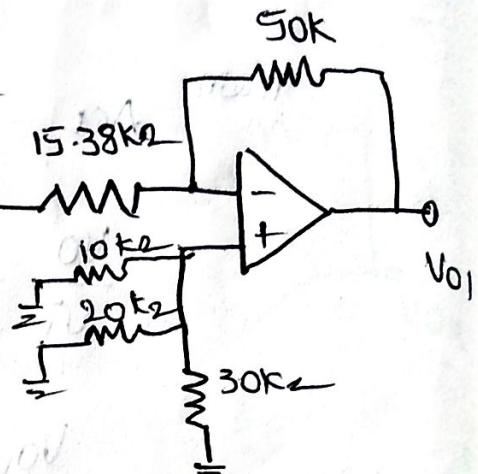
$$V_{O1} = \left( -\frac{R_F}{R_1} \right) \times \frac{V_1}{2}$$




$$= -\frac{50 \times 10^3}{15.38 \times 10^3} \times \frac{2}{2}$$

$$V_{O1} = -3.25 \text{ V}$$

Case (ii) :-  $V_2$  is active,  $V_1, V_3, V_4$  inactive

$$V_{O2} = -\left[ \frac{R_F}{R} \right] \times \frac{V_2}{2}$$
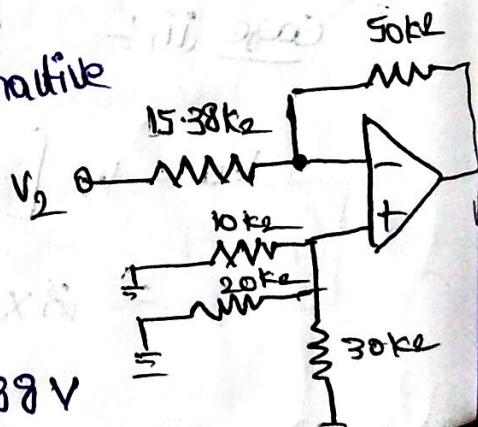
$$= -\frac{50}{15.38} \times \frac{3}{2} = -4.88 \text{ V}$$



$$V_{O2} = -4.88 \text{ V}$$

case (iii):  $V_3$  is active

$$V_a = \left( \frac{R_2}{R_1 + R_2} \right) \times V_3$$


$$V_{o1} = \left( \frac{12}{10+12} \right) \times 4$$

$$V_a = 2.18 \text{ V}$$

$$V_{o3} = \left( 1 + \frac{R_f}{R} \right) \times V_a$$

$$V_{O3} = \left[ 1 + \frac{50}{15.3} \right] \times 2.18$$

$$V_{O3} = 9.2 \text{ V}$$

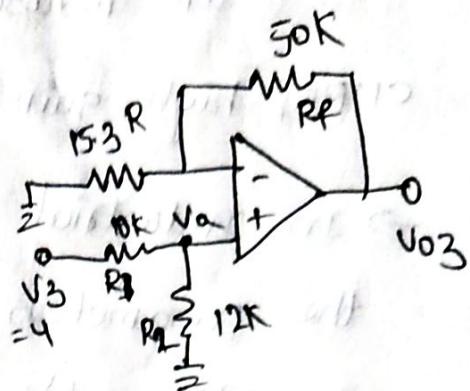

case (iv):  $V_4$  is active

$$V_a = \left( \frac{R_2}{R_1 + R_2} \right) \times V_4$$


$$V_{o1} = \left[ \frac{7.5}{20+7.5} \right] \times 5$$

$$V_a = 1.36 \text{ V}$$

$$V_{o4} = \left( 1 + \frac{R_f}{R} \right) V_a$$

$$V_{o4} = \left[ 1 + \frac{50}{15.3} \right] \times 1.36$$

$$V_{o4} = 5.80 \text{ V}$$

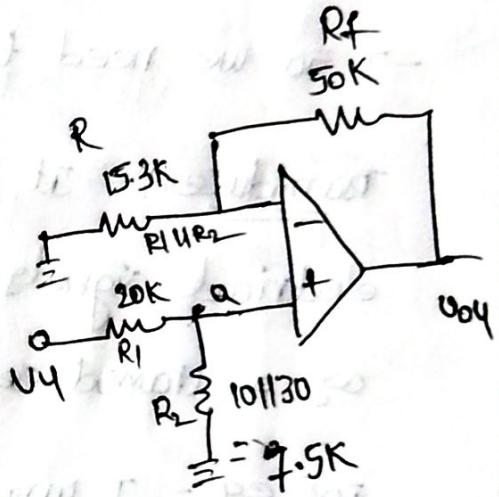

$$V_o = V_{o1} + V_{o2} + V_{o3} + V_{o4}$$

$$= -3.25 - 4.88 + 9.20 + 5.80$$

$$V_o = 6.87 \text{ V}$$

Method 2:

## \* Instrumentation Amplifier:-

In industrial applications we need high CMRR, high gain and high input impedance amplifier.


→ In industrial application we are measuring the parameters like ~~temp~~ temperature, humidity etc.

→ These type of measurement parameters we can't directly apply to the input of the amplifiers.

→ So we need transducers.

Transducer:- It convert any parameter into the electrical signals. Normally we use bridge circuits e.g. a. transducer.

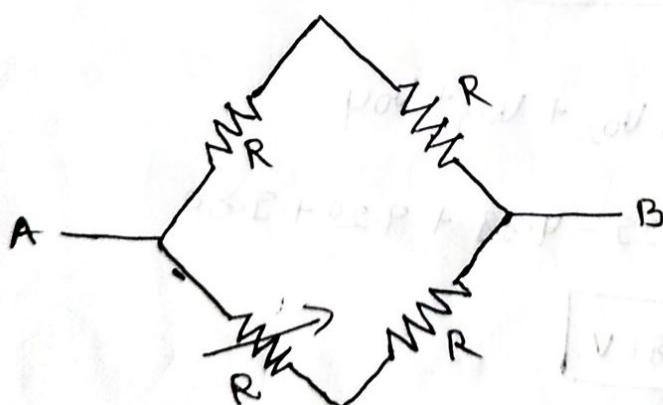
for eg:- I want to convert the temp into the electrical signals.



RTD (Resistance Thermo Detector)

→ It detects the temperature and vary the resistance, the temperature also varies then we find the two voltages at A & B.

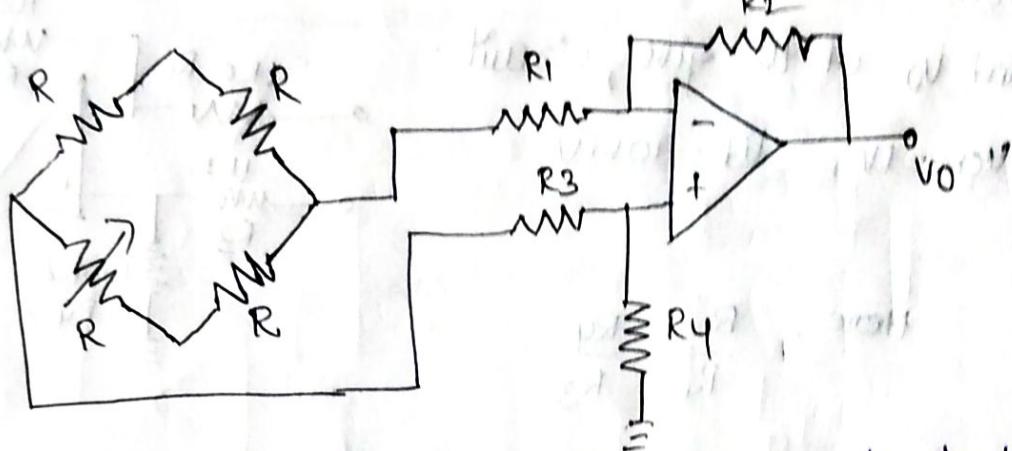
that voltages are 2 differential voltages.



1. To achieve high CMRR we need to eliminate the common mode signals.

2. To achieve high input impedance check the resistance values in differential amp in the bridge circuit.

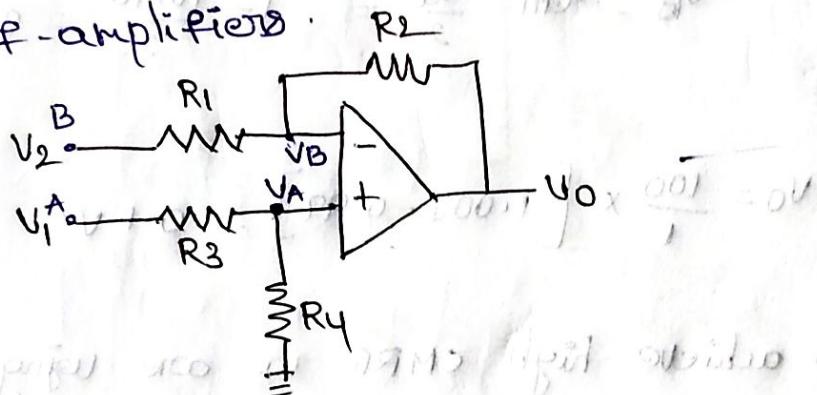3. To achieve high gain we have to eliminate mismatching b/w the transistors that are used in diff.-amplifiers.



$$V_0 = \left( \frac{R_4}{R_3 + R_4} \right) V_A \left[ 1 + \frac{R_2}{R_1} \right] - \left( \frac{R_2}{R_1} \right) V_B$$

$$\text{Assume } \frac{R_2}{R_1} = \frac{R_3}{R_4}$$

$$\text{then } V_0 = \frac{R_2}{R_1} [V_A - V_B]$$

$$V_d = V_A - V_B \Rightarrow V_0 = \frac{R_2}{R_1} \times V_d$$

$$V_0 = A_d V_d + A_{CM} V_{CM}$$

$$V_A = V_{CM} + \frac{V_d}{2}$$

$$V_B = V_{CM} - \frac{V_d}{2}$$


problem!

Find  $V_o$  of the given circuit.

$$V_{CM} = 1V, V_d = 10mV$$

Sol.
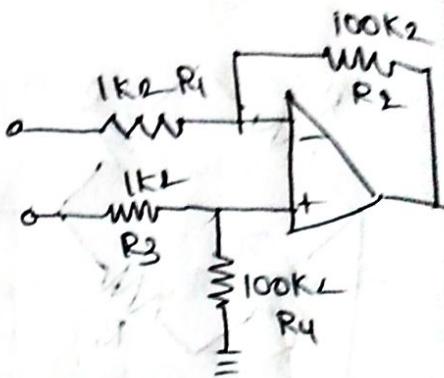
$$\text{Here, } \frac{R_2}{R_1} = \frac{R_4}{R_3}$$



then

$$V_o = \frac{R_2}{R_1} [V_A - V_B] \quad \text{--- (1)}$$

where

$$V_A = V_{CM} + \frac{V_d}{2}$$

$$V_A = 1 + \frac{10 \times 10^{-3}}{2} = 1.005$$

$$V_B = V_{CM} - \frac{V_d}{2} = 1 - \frac{10 \times 10^{-3}}{2} = 0.99V$$


$$V_o = \frac{100}{1} \times [1.005 - 0.99] = 10.1V$$

→ To achieve high CMRR we are using monolithic IC's.


In monolithic IC's all resistors are fabricated permanently but the  $\text{ilp}$  impedance is less by using Monolithic IC's.

→ To achieve high  $\text{ilp}$  impedance we can use buffers before the differential amplifier.

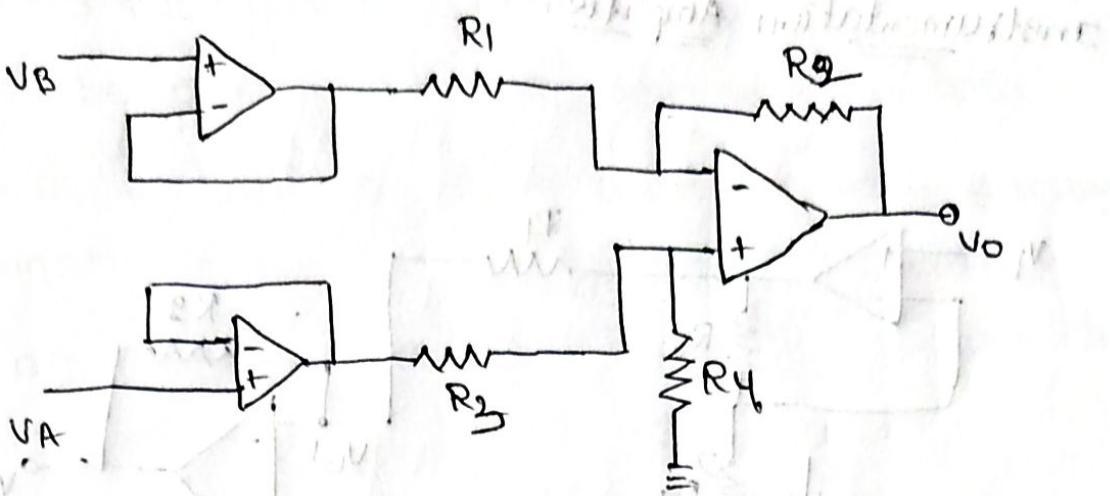→ we are using buffers along with the monolithic IC's.




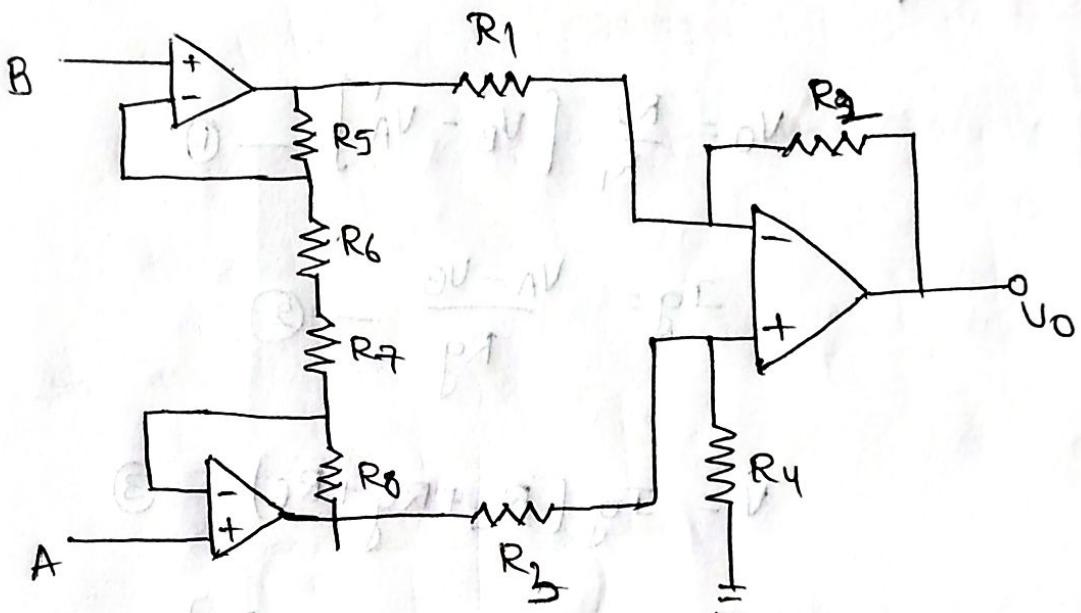- By using this above ckt we get fixed gain.
- To change this gain we can use non-inverting op. Amplifiers instead of buffers.



- The problem by using above ckt  
we have to match the  $R_5, R_6, R_7, R_8$
- To overcome this problem we are inserting  
a register  $R_g$ .

# Instrumentation Amplifier

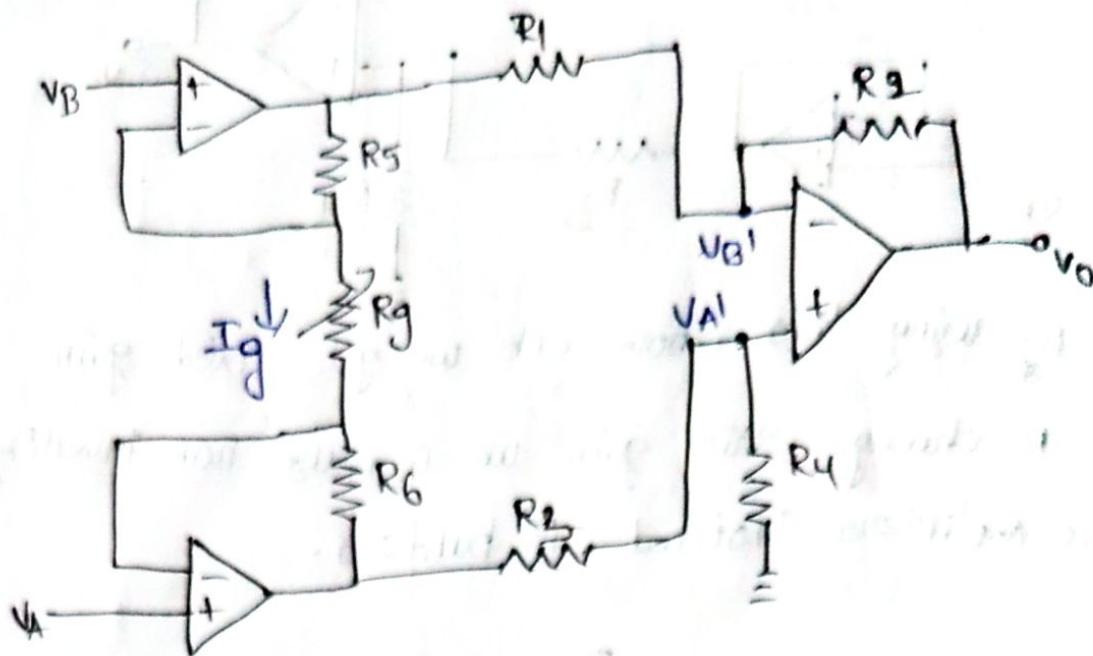

$$V_O = \frac{R_2}{R_1} [V_B' - V_A'] \quad \text{--- (1)}$$

$$I_g = \frac{V_A - V_B}{R_g} \quad \text{--- (2)}$$

$$V = I_g (R_5 + R_g + R_6) \quad \text{--- (3)}$$

$$V_B' - V_A' = I_g (R_5 + R_g + R_6)$$

sub (2), (3)

$$V_B' - V_A' = \left( \frac{V_A - V_B}{R_g} \right) (R_5 + R_g + R_6) \quad \text{--- (4)}$$

sub (4) in (1)

$$V_O = \frac{R_2}{R_1} \left[ \frac{V_A - V_B}{R_g} \right] [R_5 + R_g + R_6]$$

where  $R_5 = R_6 = R$

$$\therefore V_O = \frac{R_2}{R_1} \left[ \frac{V_A - V_B}{R_g} \right] (2R + R_g)$$


## AC Amplifier:-

The op-amp is designed for both AC & DC applications. If we want op-amp as a frequency response, we can use the AC amplifiers. In this AC amplifiers, we can use 1 capacitor to block the DC components.

1. Inverting AC amplifier

2. Non-Inverting AC amplifier.

1. Inverting AC amplifier:-

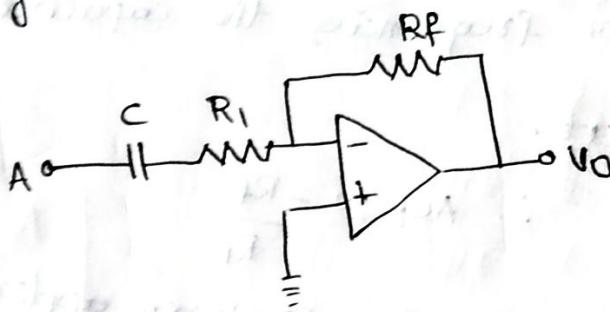

In inverting op-amp,

$$ACL = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$

In inverting AC op-amp,

$$ACL = \frac{V_o}{V_i} = \frac{-R_f}{R_1 + j\omega C}$$

$$= \frac{-R_f}{R_1 + \frac{1}{j\omega C}} = \frac{-R_f}{R_1 \left(1 + \frac{1}{j\omega R_1 C}\right)}$$

$$= -\frac{R_f}{R_1} \times \frac{1}{1 + \frac{1}{j\omega R_1 C}}$$

where,  $\omega = 2\pi f$

Block diagram

$$\frac{V_o}{V_{in}} = -\frac{R_f}{R_i} \times \frac{1}{1 + \left( \frac{1}{j\pi R_i C} \right)}$$

At low frequencies, the effect of capacitor is negligible.

At high frequencies, the capacitor works as a short circuit.

$$\therefore \frac{V_o}{V_{in}} = -\frac{R_f}{R_i} \times \frac{1}{1 + \frac{f_i}{j\omega}} = -\frac{R_f}{R_i} \left[ \frac{1}{1 - \frac{j\omega}{f_i}} \right]$$


At higher frequencies the capacitor works as a short circuit.

a short ckt.

$$\therefore A_{CL} \approx -\frac{R_f}{R_i}$$


→ It is used for low frequency applications.

### 2. Non-inverting AC amplifier:-

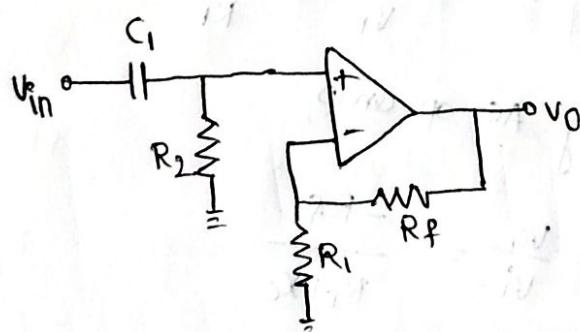


This  $R_2$  is provided to eliminate the dc components by, using this ckt i/p impedance of the op.Amp is decreased.

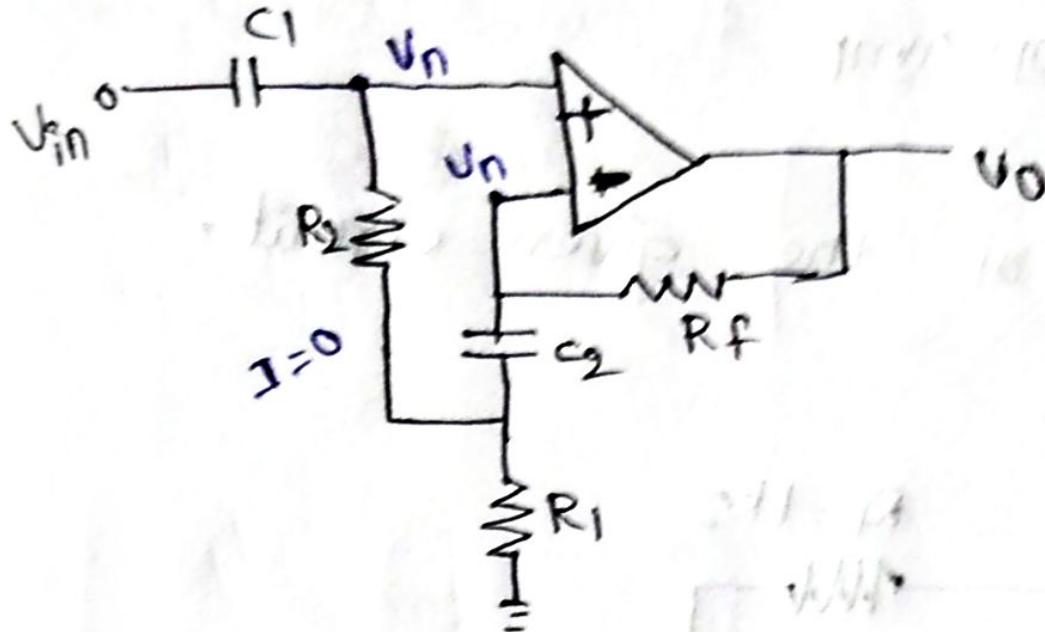→ To achieve high i/p impedance place a capacitor b/w the resistors of  $R_2 \& R_f$ .



→ At higher frequencies, the ~~is~~ acts as a short ckt element. Some potential ~~Un~~ is applied at +ve terminal of the op-amp because of this no current flows through the  $R_2$ .

## \* V-I Convertors (Voltage - Current)

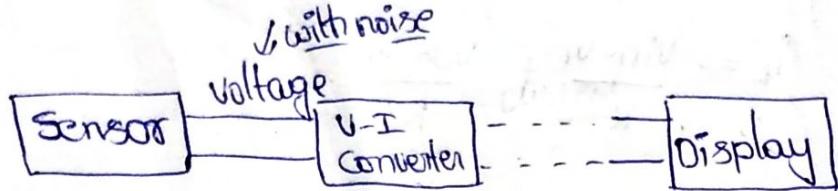

without distortion then the current will display.

There are 2 types:


1) Floating node V-I converter

2) Ground Load V-I converter

$$\text{v}_{in} \xrightarrow{\text{v}_{in}} \frac{I}{R} \xrightarrow{\text{v}_{in}} I = \frac{\text{v}_{in}}{R}$$

$$I = \frac{\text{v}_{in}}{R + R_{RL}}$$

1) Floating node V-I converter:

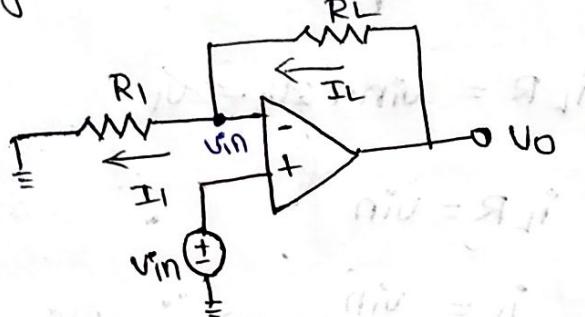

$$\text{where } I_I = I_L$$


$$\frac{\text{v}_{in}}{R_I} = I_L$$

$$\text{v}_{in} \propto I_L$$

when  $R_I$  is fixed this circuit will acts as

V-I converter.

2) Ground Load V-I converter:

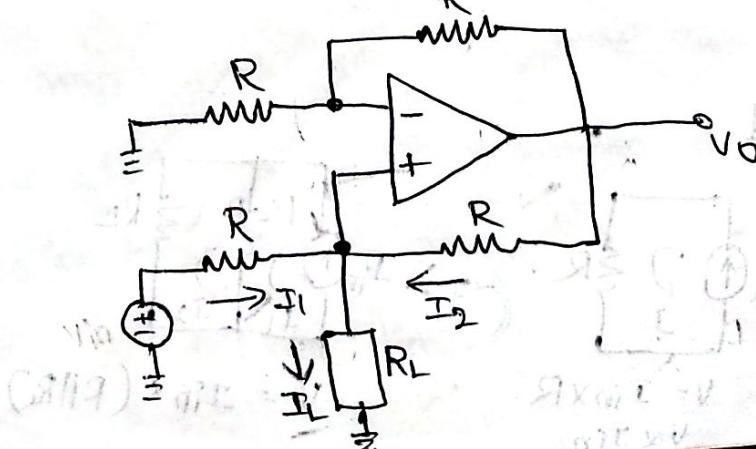

$$i_L = i_1 + i_2$$

$$i_L = \frac{V_{in} - V_1}{R} + \frac{V_O - V_1}{R}$$

$$i_{LR} = V_{in} + V_O - 2V_1 \quad \text{--- ①}$$

$$V_O = \left(1 + \frac{R_F}{R_1}\right) V_1$$

$$V_O = \left(1 + \frac{R}{R}\right) V_1$$

$$V_O = 2V_1 \quad \text{--- ②}$$

diode  
LED  
ZENER DIODE.

Sub ② in eq ①

$$i_{LR} = V_{in} + 2V_1 - 2V_1$$

$$i_{LR} = V_{in}$$

$$i_L = \frac{V_{in}}{R} \Rightarrow i_L \propto V_{in}$$

when 'R' is fixed this ckt acts V-I converter.

→ I to V converters:-


when we want to store the data then the op should integrate of voltage. but the data storage should take the voltages to store the op. we use the I-V converters.

Normal Method




$$V = I_{in} \times R$$

$$V \propto I_{in}$$

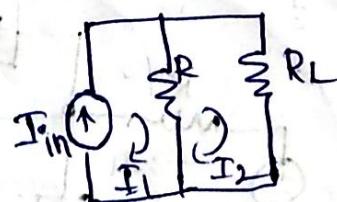

$$V_o = I_{in} \times (R || R_L)$$


By using Op-Amp

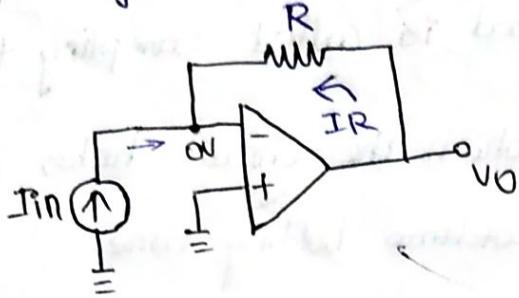

$$I_{in} = I_R$$

$$I_{in} = \frac{V_O}{R}$$


$$V_O = I_{in} \times R$$

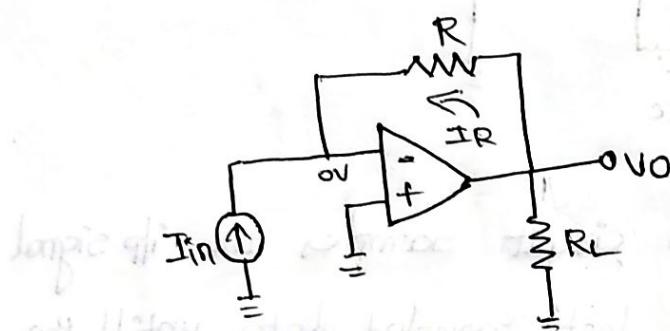

→ for ideal op-amp,  $R_L$  does not effect.

so,  $V_O = 0$

\* sample & hold circuit :-

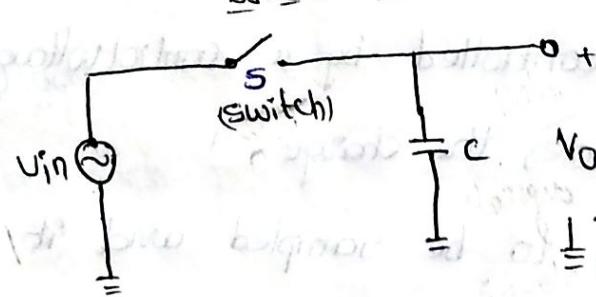


The sample and hold circuit is an electronic circuit which creates the samples of voltage given to it as input and after these, it holds these

Samples for definite time.

→ The time during which the circuit generates the sample of the input signal is called Sampling time.

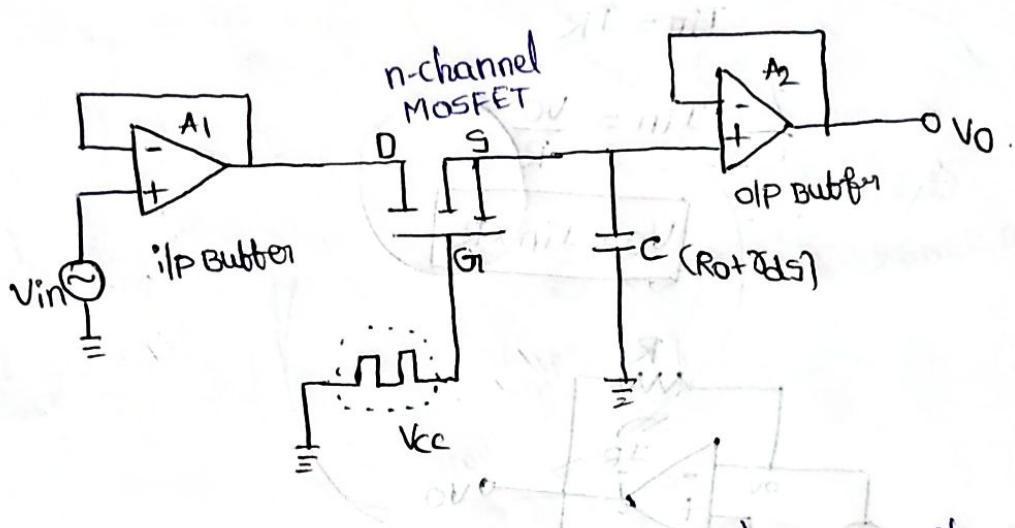→ The time during which the circuit holds the sampled value is called holding time.



→ A sample and hold circuit samples the i/p signal and holds on to its last sampled data until the i/p is sampled again.




→ This type of circuit used in A → D converters and PCM system (pulse code modulated).

→ In this circuit n-channel MOSFET works as a switch and it is controlled by a control voltage ( $V_c$ ). The capacitor 'C' stores the charge.

→ The i/p voltage ( $V_i$ ) to be sampled and it is applied to the drain of the MOSFET and  $V_c$  is applied at the Gate terminal of MOSFET.

→ When  $V_c$  is 1 the FET turns 'ON' and the capacitor charges to the instantaneous value of i/p ( $V_i$ ) with  $(R_o + R_{ds})$  where  $R_o \rightarrow$  o/p Resistance of  $A_1$

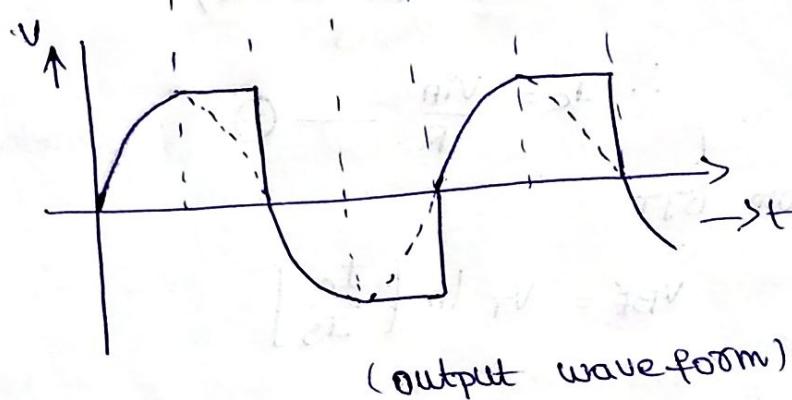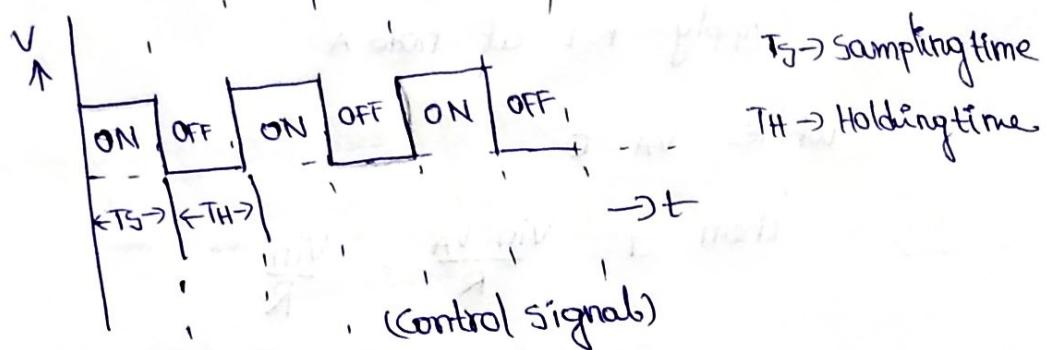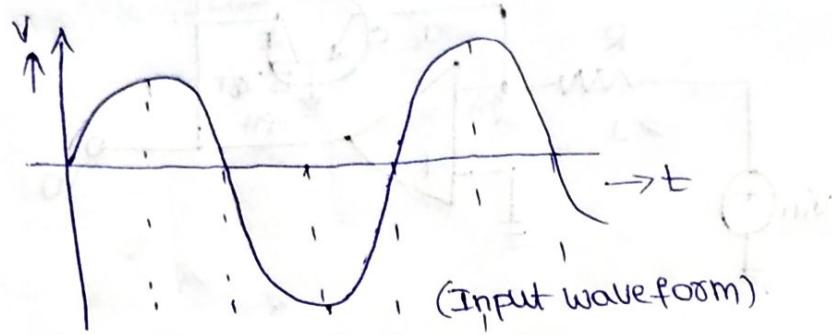$R_{ds} \rightarrow$  on resistance of MOSFET



### \* Log Amplifiers:-

→ In log amplifiers, BJT is used as a diode with base and collector shorted. i.e  $V_{CB} = 0$ .


→ For such BJT, the base-emitter voltage  $V_{BE}$  is

$$V_{BE} = V_T \ln \left( \frac{I_C}{I_S} \right)$$

where  $I_C$  = Collector Current

$I_S$  = Emitter saturation current.
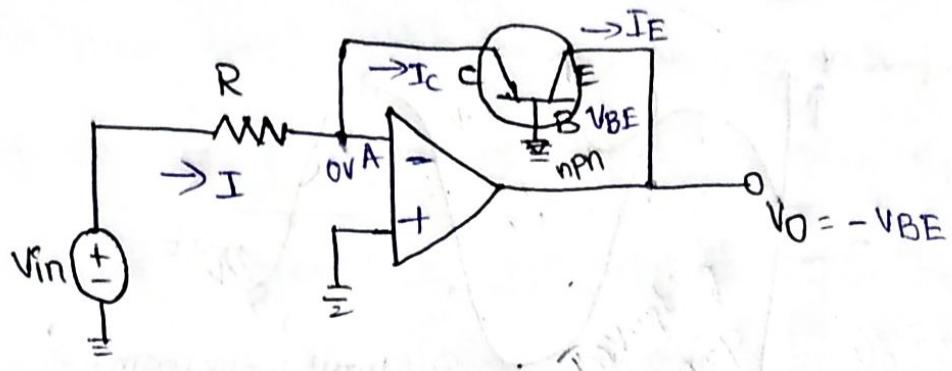
$$I_C = I_S \left[ e^{\frac{V_{BE}}{V_T}} \right]$$



Apply KCL at node A

where  $V_A = 0$

$$\text{then } I = \frac{V_{in} - V_A}{R} = \frac{V_{in}}{R}$$

(loop current)

$$I = I_C \text{ (At node A)}$$

$$\therefore I_C = \frac{V_{in}}{R} \quad \text{--- (1)}$$

From BJT

$$V_{BE} = V_T \ln \left[ \frac{I_C}{I_S} \right]$$

where  $V_0 = -V_{BE}$

$$= -V_T \ln \left[ \frac{I_C}{I_S} \right]$$

From eq (1)

$$V_0 = -V_T \ln \left[ \frac{V_{in}/R}{I_S} \right]$$


$$= -V_T \ln \left[ \frac{V_{in}}{R I_S} \right]$$

where  $R I_S = V_{ref}$

$$\therefore V_0 = -V_T \ln \left[ \frac{V_{in}}{V_{ref}} \right]$$

$$\therefore V_0 \propto \ln(V_{in})$$

## Anti-log amplifiers:-

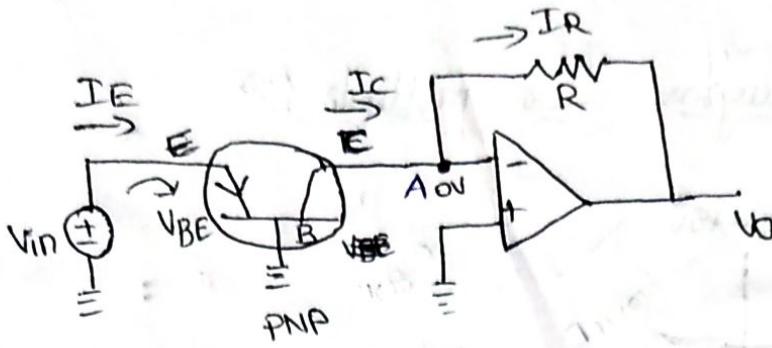

From virtual ground method,  $V_A = 0V$

$$\therefore V_{CB} = 0V$$

From node A,

$$I_C = I_R \Rightarrow I_R = \frac{V_A - V_0}{R} = -\frac{V_0}{R}$$

where,  $I_C = I_S e^{\frac{V_{BE}}{V_T}}$

$$\therefore -\frac{V_0}{R} = I_S e^{\frac{V_{BE}}{V_T}}$$

$$V_0 = -R I_S e^{\frac{V_{BE}}{V_T}} \quad \text{where } V_{BE} = V_{in}$$

$$\therefore V_0 = -R I_S e^{\frac{V_{in}}{V_T}}$$


where  $R I_S = V_{ref}$

$$\therefore V_0 = -V_{ref} e^{\frac{V_{in}}{V_T}}$$

$$V_0 \propto e^{\frac{V_{in}}{V_T}}$$

\* Multiplexer:-

Schematic diagram for multiplier:-

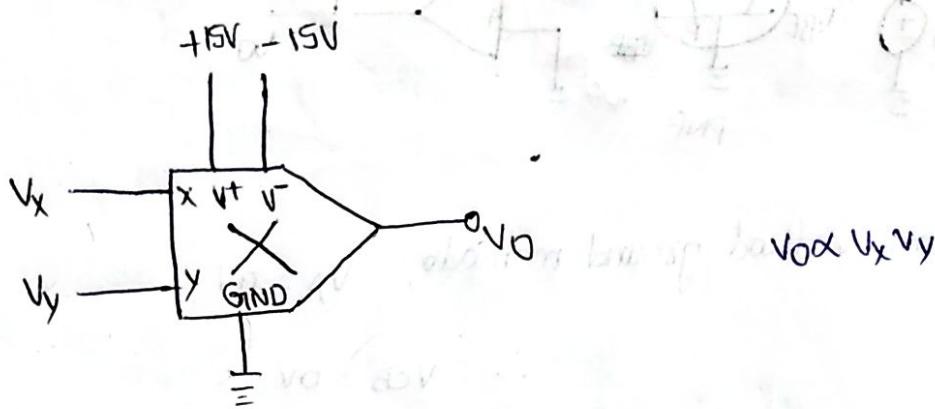


$$\text{where, } V_o = \frac{V_x V_y}{V_{\text{ref}}}$$

for practical  $V_{\text{ref}} = 10V$

Classification:-

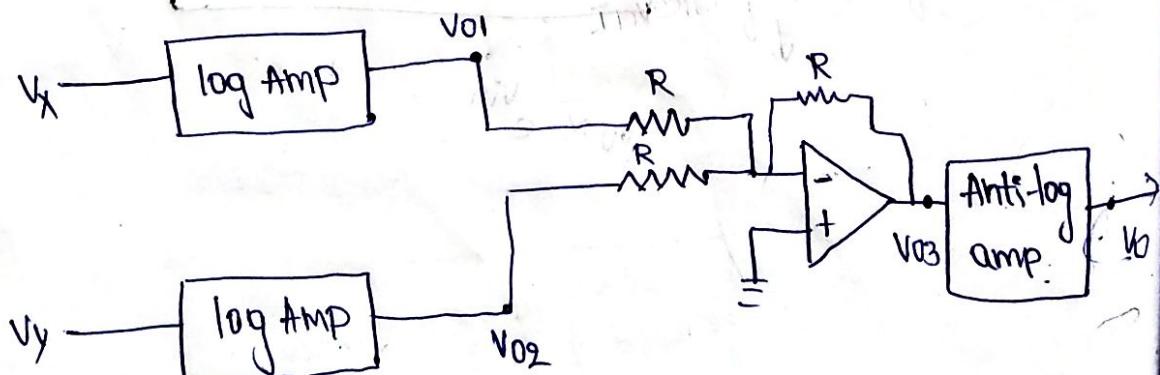1. one quadrant multiplier, both ilps are +ve or -ve
  2. Two quadrant Multiplier, one ilp is +ve other +ve or -ve
  3. Four quadrant Multiplier, ilps are +ve, +ve, -ve, -ve
- \* Designing a multiplier by using a log Amplifier:-



$$V_o = \frac{V_x V_y}{V_{\text{ref}}}$$

from the CKT.

$$V_{O1} = -V_T \ln \left[ \frac{V_X}{V_{\text{ref}}} \right] \quad \text{from log amplifier} \quad \textcircled{1}$$

$$V_{O2} = -V_T \ln \left[ \frac{V_Y}{V_{\text{ref}}} \right] \quad \textcircled{2}$$

$$V_{O3} = -[V_{O1} + V_{O2}]$$

$$= - \left[ -V_T \ln \left( \frac{V_X}{V_{\text{ref}}} \right) - V_T \ln \left( \frac{V_Y}{V_{\text{ref}}} \right) \right]$$

$$= V_T \ln \left[ \frac{V_X}{V_{\text{ref}}} \right] + V_T \ln \left[ \frac{V_Y}{V_{\text{ref}}} \right]$$

$$= V_T \left[ \ln \left( \frac{V_X}{V_{\text{ref}}} \right) + \ln \left( \frac{V_Y}{V_{\text{ref}}} \right) \right] \quad (\log a + \log b \\ = \log ab)$$

$$= V_T \ln \left[ \frac{V_X \cdot V_Y}{V_{\text{ref}}^2} \right]$$

$$V_{O3} = V_T \ln \left[ \frac{V_X V_Y}{V_{\text{ref}}^2} \right] \quad \textcircled{3}$$

$$V_O = -V_{\text{ref}} \times e^{\frac{V_{O3}}{V_T}} \quad \text{from Anti log amp} \quad \textcircled{4}$$

$$= -V_{\text{ref}} \times \frac{\frac{V_X V_Y}{V_{\text{ref}}^2}}{V_T}$$

$$= -V_{\text{ref}} \times \frac{V_X V_Y}{V_{\text{ref}}^2}$$

$$V_O = -\frac{V_X V_Y}{V_{\text{ref}}}$$

We want to change the sign then voltage

follower is used at the output terminal then,

$$V_O = \frac{V_X V_Y}{V_{\text{ref}}}$$

## \* Applications of Multiplier:-

1. frequency doubling
2. squaring a signal
3. detecting phase angle difference b/w 2 signals
4. multiplying 2 signals

## \* Frequency doubling:-

$$V_x = V_x \sin wt$$

$$V_0 = \frac{V_x V_y}{V_{\text{ref}}} \quad \text{--- (1)}$$

$$V_y = V_y \sin(wt + \theta)$$

$$V_0 = \frac{V_x V_y}{V_{\text{ref}}} \sin wt \cdot \sin(wt + \theta)$$

$$= \frac{V_x V_y}{V_{\text{ref}}} \cdot \sin wt \left[ \sin wt \cos \theta + \cos wt \sin \theta \right]$$

$$= \frac{V_x V_y}{V_{\text{ref}}} \left[ \sin^2 wt \cos \theta + \cos wt \sin wt \sin \theta \right]$$

$$[\text{Using identity } \sin^2 a = 1 - \cos^2 a]$$

$$\cos 2a = 2 \cos^2 a - 1$$


$$\sqrt{\cos^2 a} = \frac{1}{2} + \frac{1}{2} \cos 2a$$

$$\begin{aligned} \sin^2 a &= 1 - \frac{1}{2} - \frac{1}{2} \cos 2a \\ &= \frac{1}{2} [1 - \cos 2a] \end{aligned}$$

$$\therefore V_0 = \frac{V_x V_y}{V_{\text{ref}}} \left[ \frac{\cos \theta}{2} (1 - \cos 2wt) + \frac{\sin \theta \sin 2wt}{2} \right]$$

$$V_0 = \frac{V_x V_y \cos \theta}{2} - \frac{V_x V_y \cos \theta \cos 2wt}{V_{\text{ref}}} + \frac{V_x V_y \sin \theta \sin 2wt}{2 V_{\text{ref}}}$$

\* Squaring circuit:-

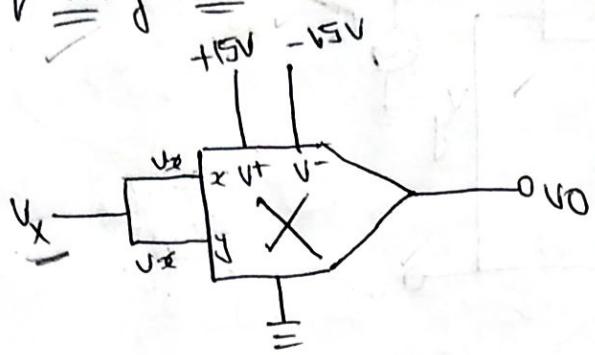

$$\therefore V_O = \underline{V_x V_y} \quad \text{where } V_y = V_x$$

$$V_O = \frac{V_x \times V_x}{V_{ref}}$$

$$V_O = \frac{V_x^2}{V_{ref}}$$

\* Phase angle detection:-

$$V_x = V_{m_x} \sin \omega t$$

$$V_y = V_{m_y} \sin(\omega t + \theta)$$

$$V_O = \frac{V_{m_x} V_{m_y}}{V_{ref}} \times \sin \omega t \times \sin(\omega t + \theta)$$

From Frequency doubling,

$$V_O = \frac{V_{m_x} V_{m_y}}{2V_{ref}} \cos \theta + \frac{V_{m_x} V_{m_y}}{V_{ref}} \cos \theta \cos 2\omega t +$$



phase angle.

detection

$$\frac{V_{m_x} V_{m_y}}{2V_{ref}} \sin \theta \sin 2\omega t$$

\* Dividers:-

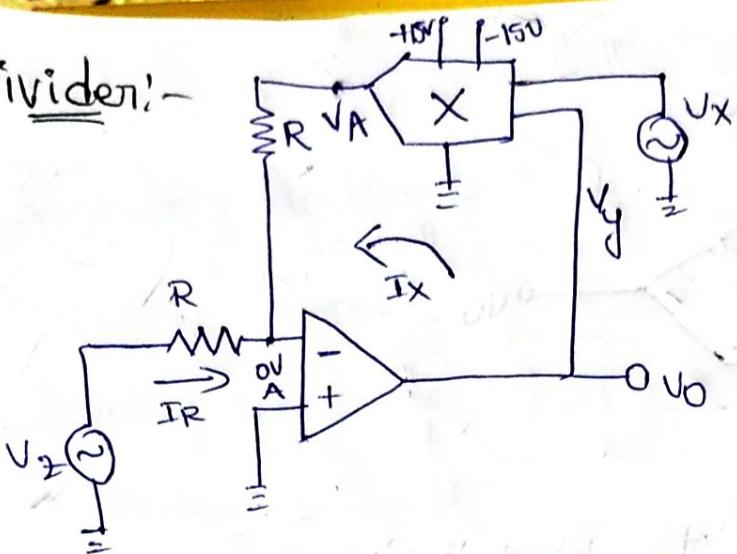


fig:- Divider circuit using multiplier and op-Amp

$$i_R = -\frac{i_X}{A} \quad \text{--- ①}$$

$$N_A = -\frac{V_x V_y}{V_{ref}}$$

$$I_X = -\frac{V_A}{R} = +\frac{V_x V_y}{V_{ref}} \times \frac{1}{R} \quad \text{--- ②} \quad (V_y = V_0)$$

$$I_R = \frac{V_2}{R} \quad \text{--- ③}$$


From ①

$$-\frac{V_x V_0}{V_{ref} R} = \frac{V_2}{R}$$

$$V_0 = -\frac{V_2}{V_x} \times V_{ref}$$

where  $V_2, V_x$  are inputs.

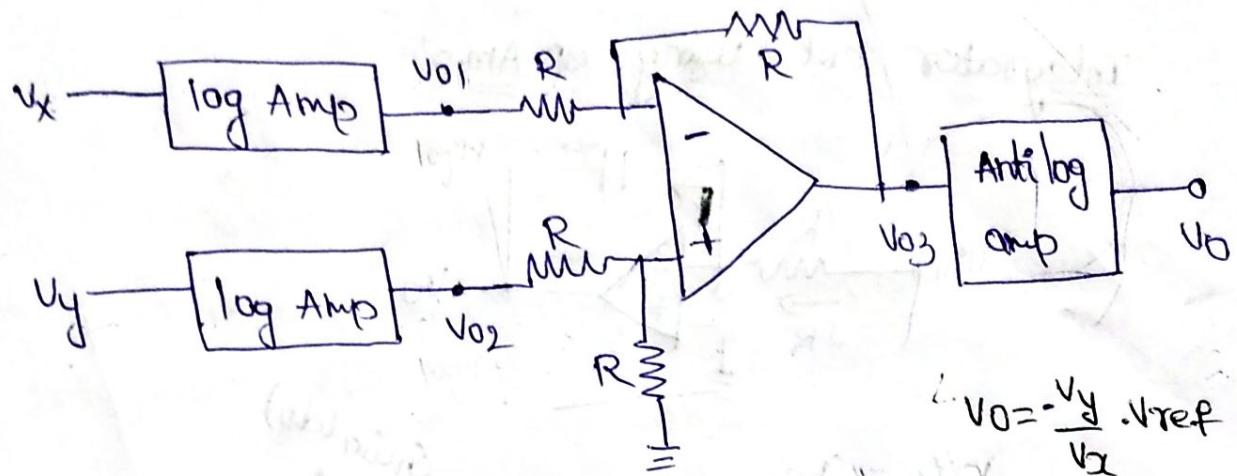\* Designing a divider by using log & anti-log amplifier.



$$V_O = -\frac{V_y}{V_x} \cdot V_{ref}$$

$$V_{O1} = (\ln V_x) \cdot V_{ref}$$

$$V_{O2} = (\ln V_y) \cdot V_{ref}$$

$$V_{O3} = V_{O2} - V_{O1}$$


$$= (\ln V_y - \ln V_x) \cdot V_{ref} \Rightarrow \left[ \ln \left( \frac{V_y}{V_x} \right) \right] V_{ref}$$

$$V_{O3} = V_{ref} \ln \left( \frac{V_y}{V_x} \right)$$

apply anti-log

$$V_O = -V_{ref} - \frac{V_y}{V_x}$$

Finding square root

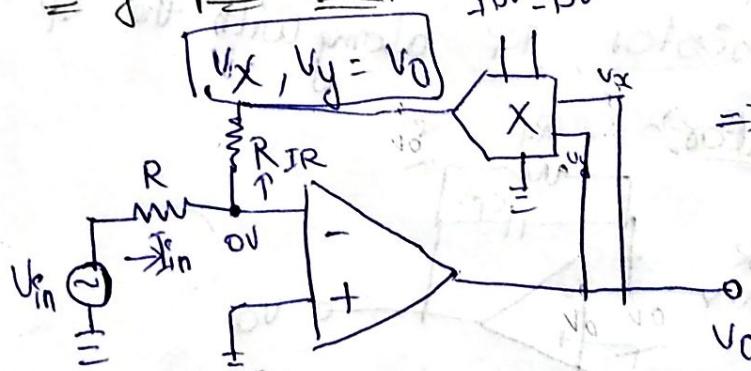

$$I_{in} = I_R$$

$$\frac{V_{in}}{R} = -\frac{V_x V_y}{V_{ref} \cdot R}$$


$$\frac{V_{in}}{R} = -\frac{V_O^2}{V_{ref} \cdot R}$$

$$V_O^2 = -V_{in} \cdot V_{ref}$$

$$V_O = \sqrt{|V_{in}| \cdot V_{ref}}$$
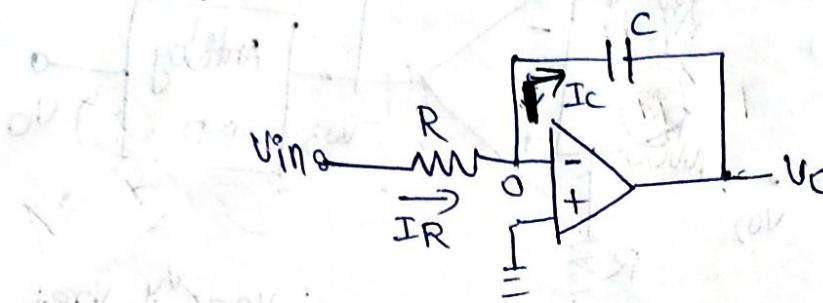
# \* Integrator and Differentiator using OP Amplifier

Integrator can be used using OP Amplifier




$$I_R = I_C$$

$$\frac{V_{in}}{R} = C \cdot \frac{dV_o}{dt}$$

$$\frac{dV_o}{dt} = \frac{1}{RC} \cdot V_{in}$$

$$V_o = \frac{1}{RC} \int V_{in} dt$$



Gain (dB)

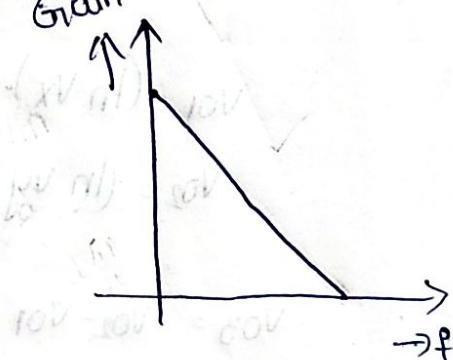

→ operational amplifier it maintains some input offset voltage ( $V_{ios}$ ) but due to this  $V_{ios}$ , the gain of this integrator is affected.

→ To eliminate this effect we can add a feed back resistor  $R_f$  along with the CF

practical Integrator:

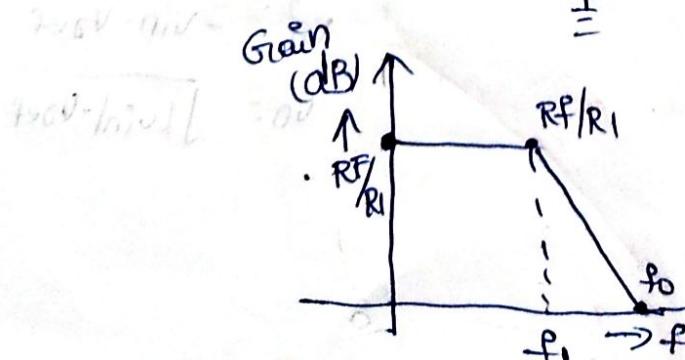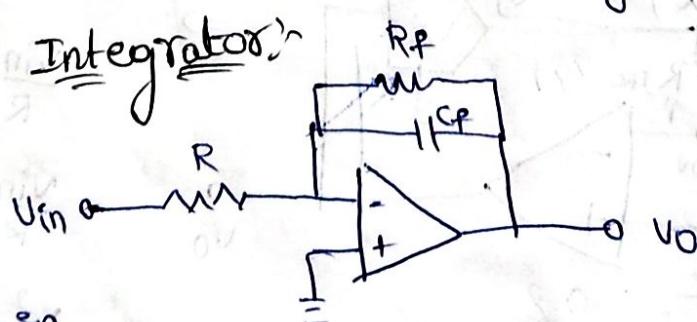

$$f_1 = \frac{1}{2\pi R_F C_F}$$

$$f_0 = \frac{1}{2\pi R C_F}$$

for proper integration.


$$f_l < f_a < f_0$$

$f_l \rightarrow$  Lower cut off frequency

$f_a \rightarrow$  i/p frequency

$f_0 \rightarrow$  zero dB frequency.

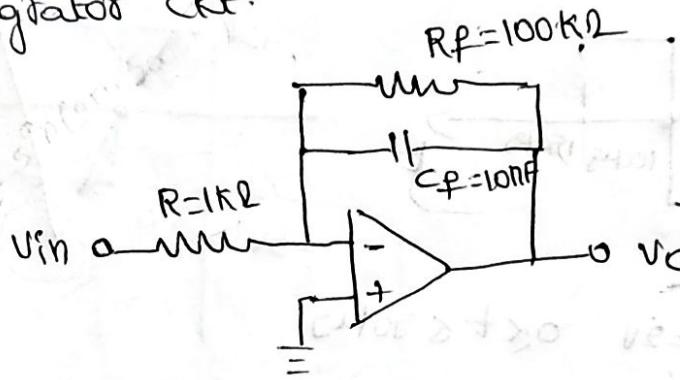- ① find lower cut off frequency for the given Integrator ckt.



Sol:- given that,

$$R = 1k\Omega$$

$$R_f = 100k\Omega$$

$$C_f = 10nF$$

Lower cut off frequency  $f_l = ?$

Formula:-

$$f_l = \frac{1}{2\pi R_f C_f}$$

$$f_l = \frac{1}{2\pi \times 100 \times 10^3 \times 10 \times 10^{-9}} = 159.23 \text{ Hz}$$

$$f_0 = \frac{1}{2\pi R C_f} = \frac{1}{2\pi \times 10^3 \times 10 \times 10^{-9}} = 15.92 \text{ kHz}$$

i)  $V_{in} = \sin(2\pi \times 5000t)$

$$V_o = (0), V_o = -\frac{1}{R_f C_f} \int V_{in}(t) dt$$



$$= -\frac{1}{10^3 \times 10 \times 10^{-9}} \int \sin(2\pi \times 5000t) dt$$

$$= -10^5 \left[ -\frac{\cos(2\pi \times 5000t)}{9\pi \times 5000} \right]$$

$$V_o = \frac{3.183}{31.83} \cos(2\pi \times 5000t)$$

The amplitude of OP signal depends upon

$R, C_f \approx V_{in}$  also.

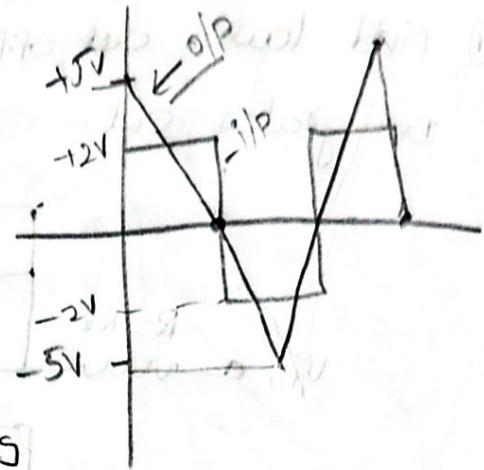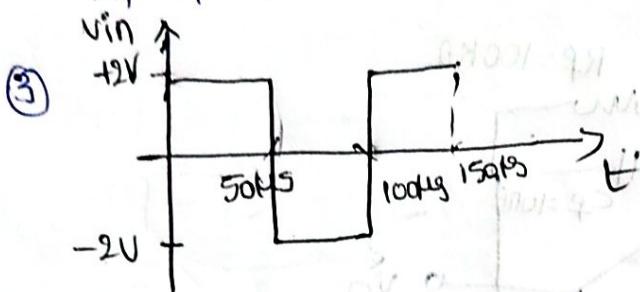

$$V_1(t) = 2V \quad 0 < t \leq 50\mu s$$

$$V_2(t) = -2V \quad 50\mu s \leq t \leq 100\mu s$$

Total time period = 100μs.

$$f = \frac{1}{T} = \frac{1}{100 \times 10^{-6}} = 10 \text{ kHz}$$


$$V_{o1} = -\frac{1}{RC_f} \int_{0}^{50\mu s} V_{in}(t) dt \quad V_{o2} = -\frac{1}{RC_f} \int_{50\mu s}^{100\mu s} V_{in}(t) dt$$

$$= -10^5 \int_{0}^{50\mu s} 2V dt \quad = -10^5 \int_{50\mu s}^{100\mu s} -2V dt$$


$$= -10^5 [2[t]_{0}^{50\mu s}] \quad = +10^5 \times 2 [100 - 50] \times 10^{-6}$$

$$= -10^5 \times 2 [50 - 0] = -10^5 \times 100 \times 10^{-6}$$

$$= -10V$$

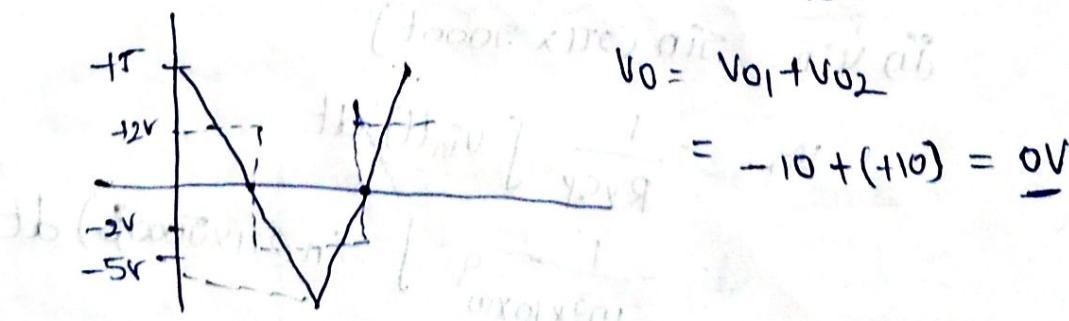
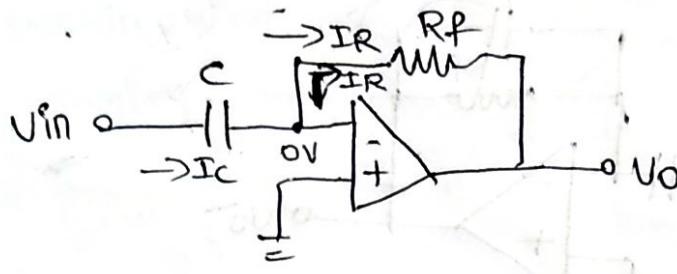
## \* Differentiator circuit using op-amp



$$I_c = IR$$

$$C \frac{dV_{in}}{dt} = \frac{U_o}{R_f}$$

$$R_f \frac{dV_{in}}{dt} = U_o$$


$$U_o = R_f \frac{dV_{in}}{dt}$$

$$\therefore A = -\frac{R_f}{R}$$


Drawbacks:

- \* High sensitive to frequency
- \* Low input impedance because of frequency is high.

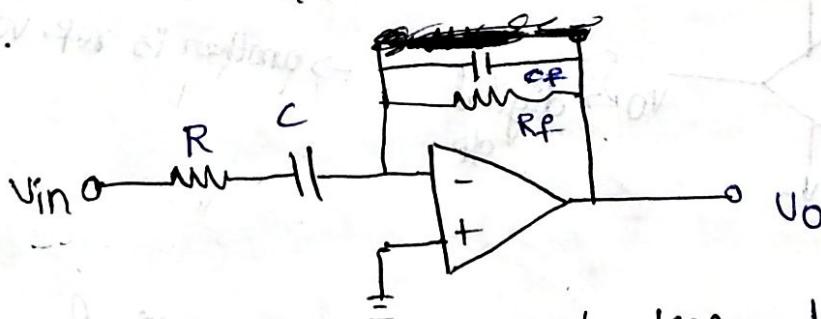To overcome this we are connecting input resistance  $R_i$ , feedback capacitance  $C_f$  to the ideal differentiator.




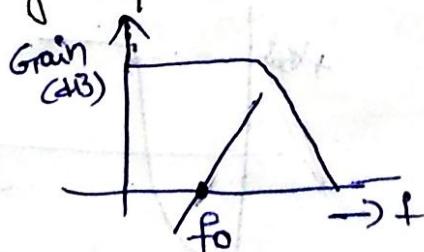Frequency response of ideal differentiator




The ideal differentiator frequency response limited by the open loop gain.

## Practical differentiator

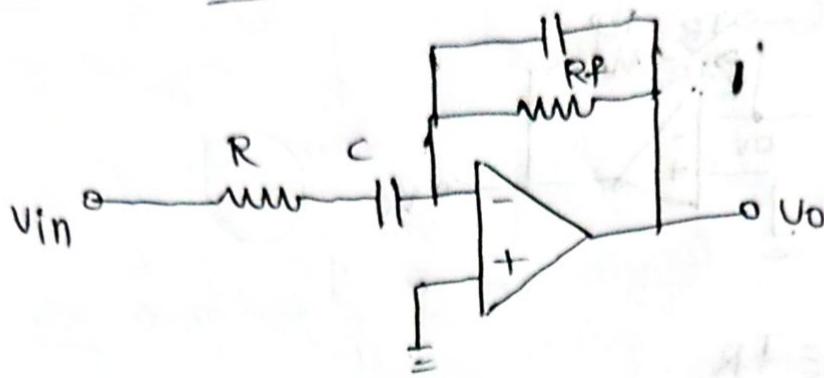


$$f_1 = \frac{1}{2\pi RC}, \quad f_2 = \frac{1}{2\pi R_f C_f}$$

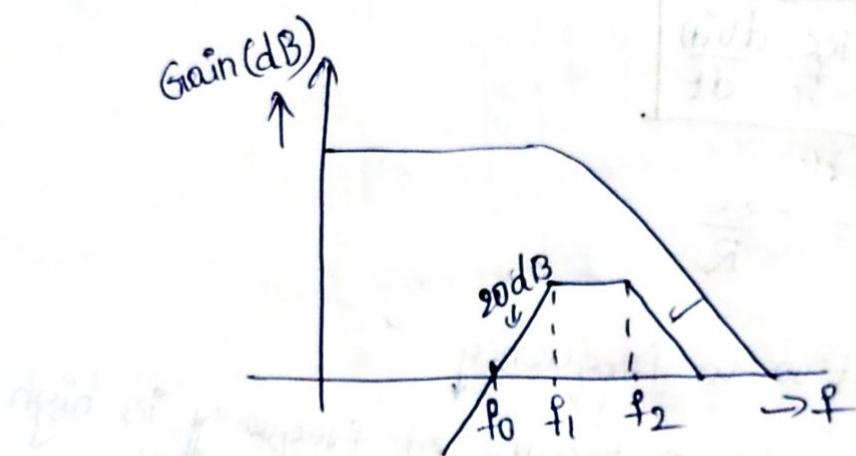
Frequency response for practical differentiator.




## \* comparator

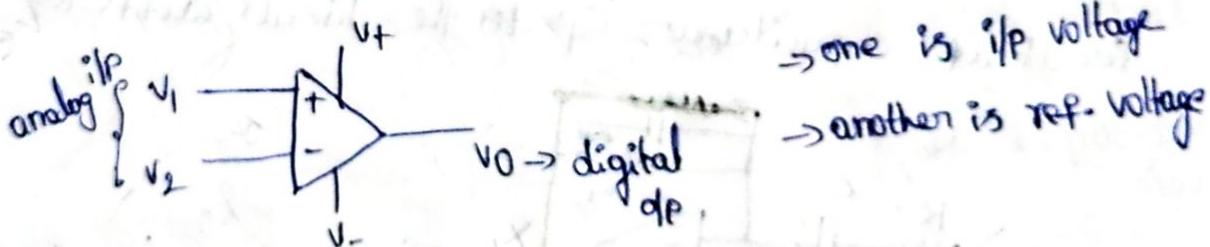

## Ideal

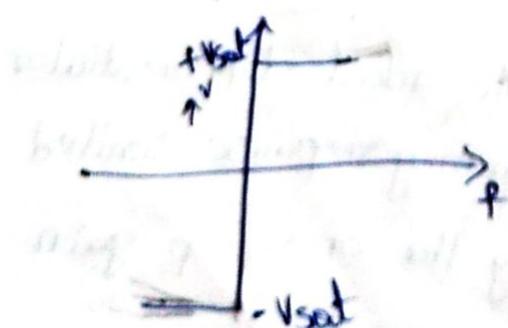

## practical

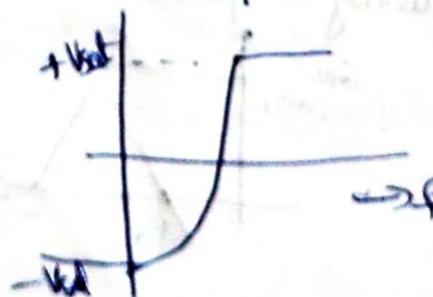


There are basically two types of comparators:-





1. Non-inverting comparator.

2. Inverting comparator.

\* Non-inverting comparator! -

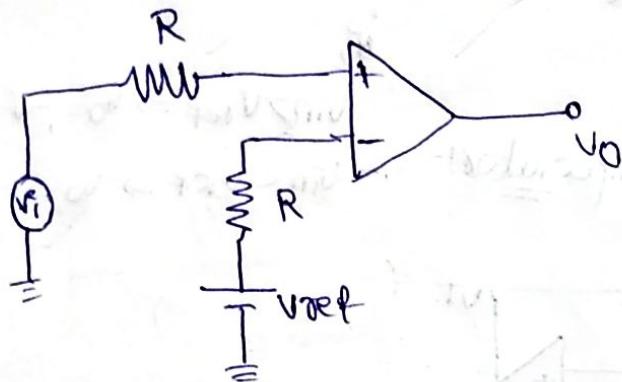

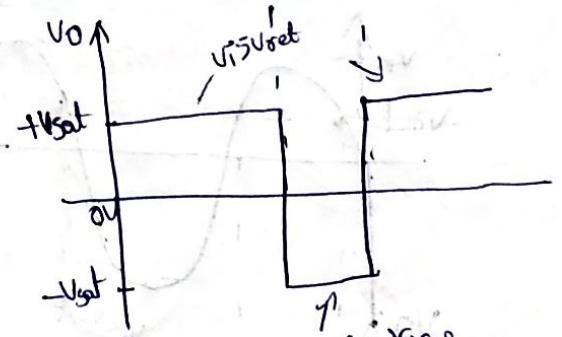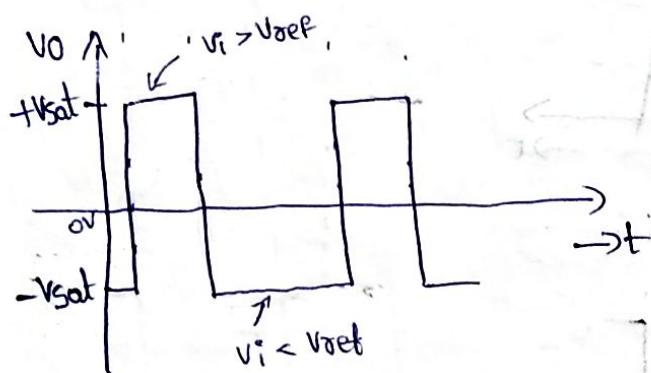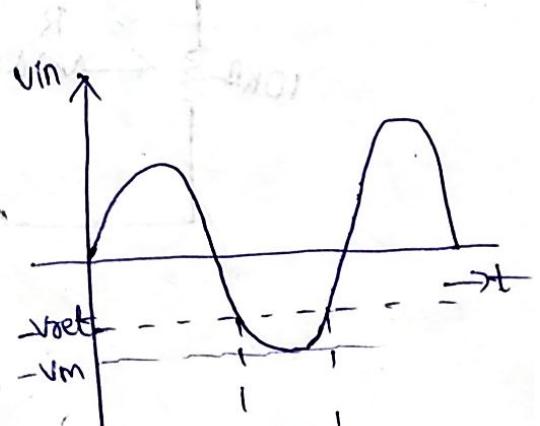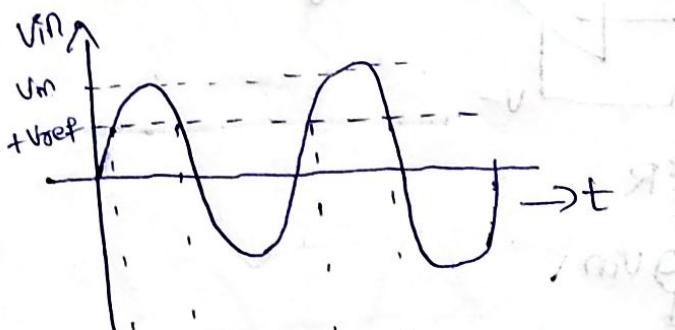
if,  
 $V_{in} > V_{ref} \Rightarrow V_O = +V_{sat}$   
 $V_{in} < V_{ref} \Rightarrow V_O = -V_{sat}$




For some applications instead of  $V_{ref}$ , we are

using a potentiometer of  $10\text{ k}\Omega$  is added to the inverting terminal.

Practical Non-inverting Comparator:-

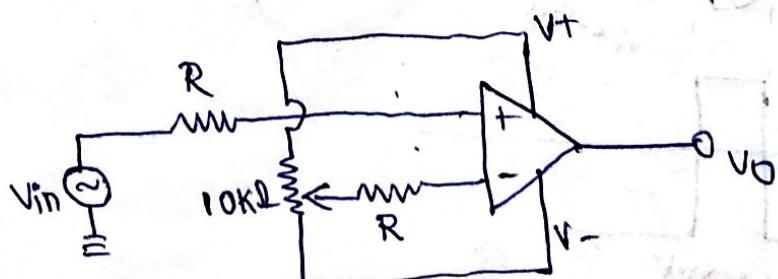




## \* Inverting Comparator

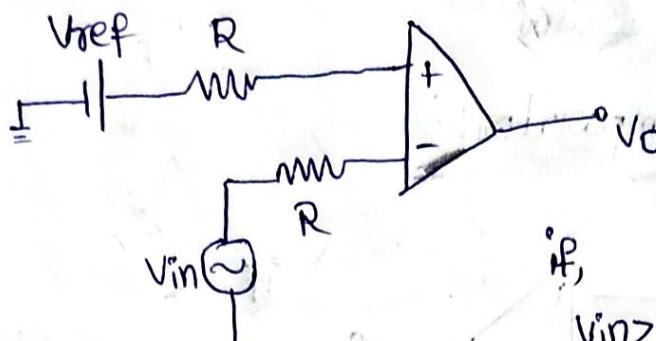

Practical Inverting Comparator:-

$$V_{in} > V_{ref} \Rightarrow V_o = -V_{sat}$$
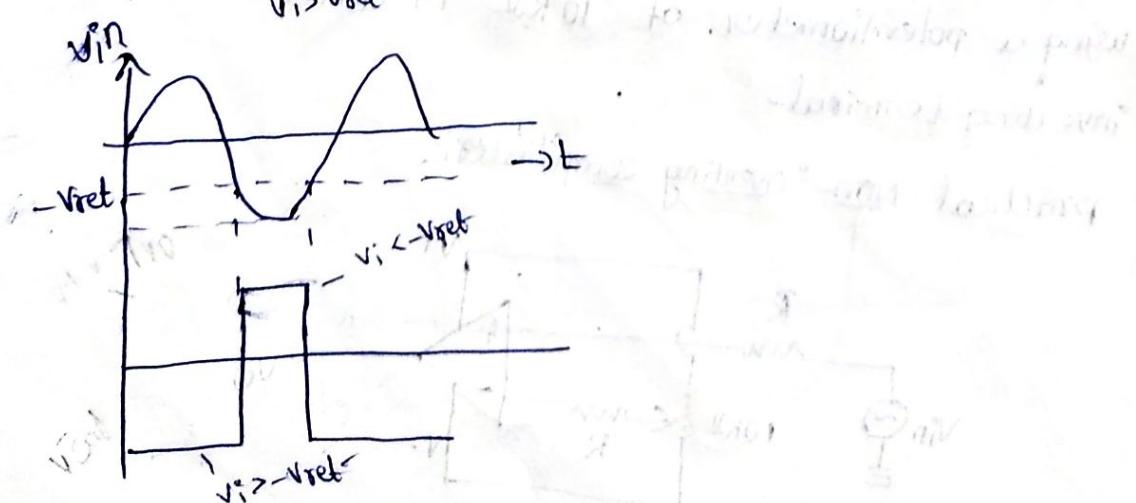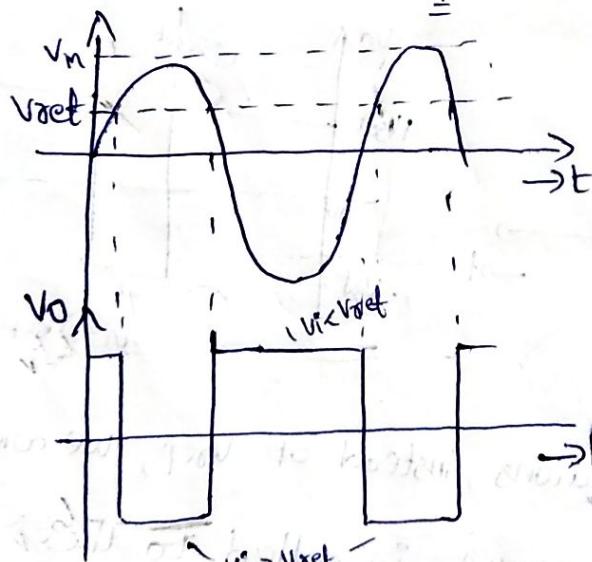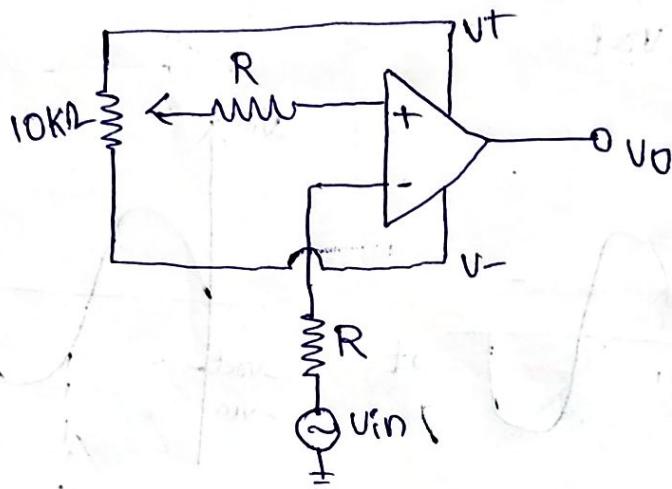
$$V_{in} < V_{ref} \Rightarrow V_o = +V_{sat}$$



## \* Applications of Comparator -



1. zero frequency detector

2. window Detector

3. Time marker generator

4. phase meter.

### ① zero frequency detector:-

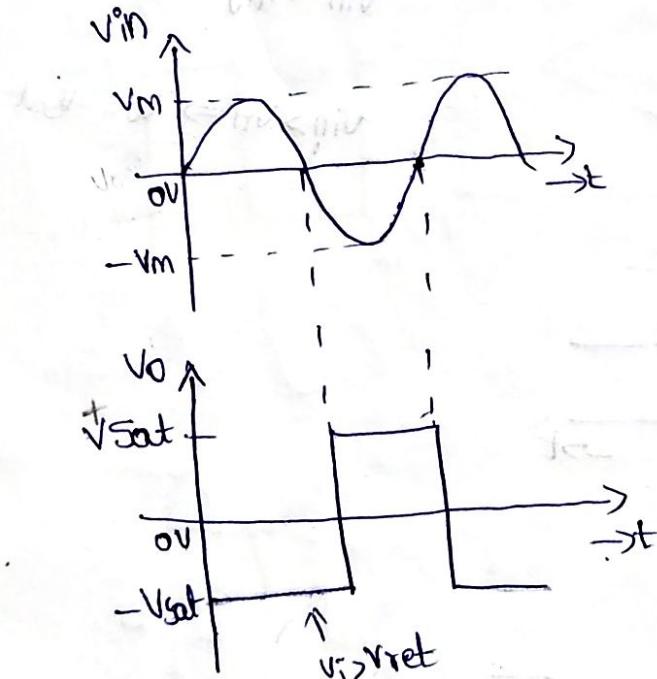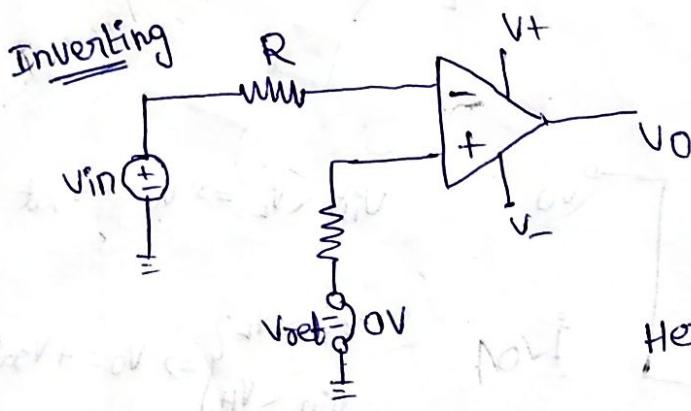


$$\text{Here } V_{\text{ref}} = 0V$$

$$V_{\text{in}} > V_{\text{ref}} \Rightarrow V_o = -V_{\text{sat}}$$

$$V_{\text{in}} < V_{\text{ref}} \Rightarrow V_o = +V_{\text{sat}}$$


### Non-Inverting

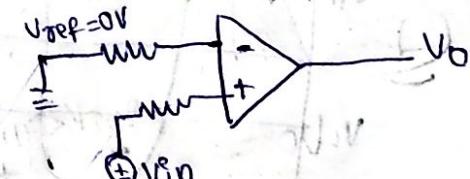

$$\text{if } V_{\text{in}} > V_{\text{ref}} \Rightarrow V_o = +V_{\text{sat}}$$


$$V_{\text{in}} < V_{\text{ref}} \Rightarrow V_o = -V_{\text{sat}}$$

### ② window Detector:-

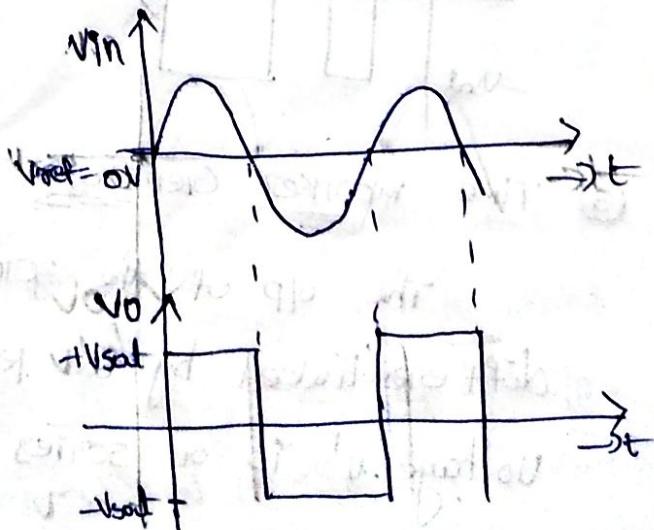

② Window Detector:- In this comparator, we are using two comparators. In some applications, when it is required to have a high to low o/p when the input is specific band. It can be designed by combination of Inverting and non-inverting comparators.

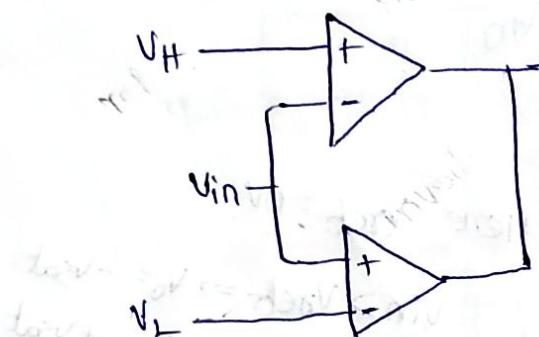
$$V_L < V_{in} < V_H \Rightarrow V_0 = V_{sat}$$



$$V_{in} < V_L \Rightarrow V_0 = -V_{sat}$$

$$\begin{cases} V_{in} > V_H \\ V_{in} < V_H \end{cases} \Rightarrow V_0 = +V_{sat}$$


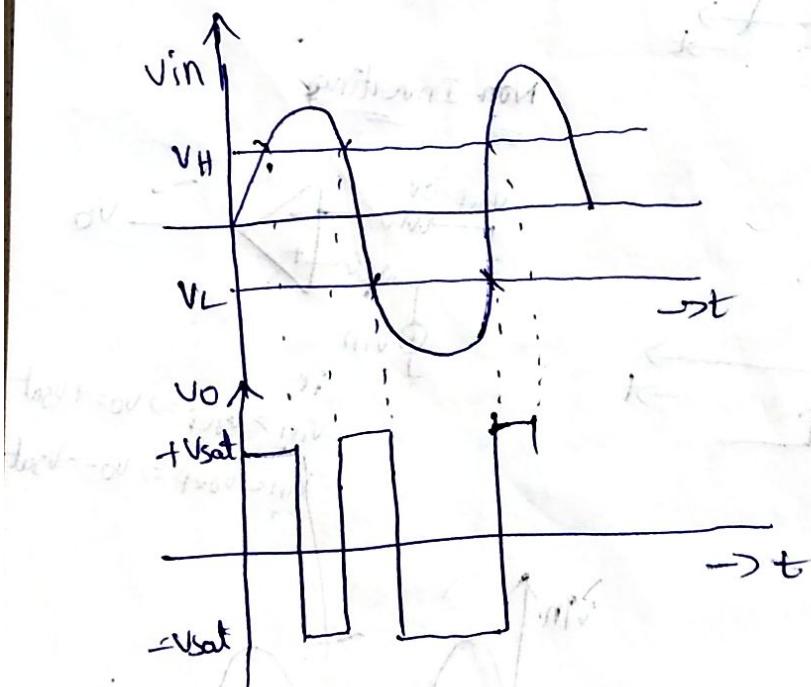
$$V_{in} > V_H \Rightarrow V_0 = -V_{sat}$$



③ Time marker Generator-

The o/p of the zero-crossing detector is differentiated by an RC circuit, so that the voltage  $V'$  is a series of positive and negative

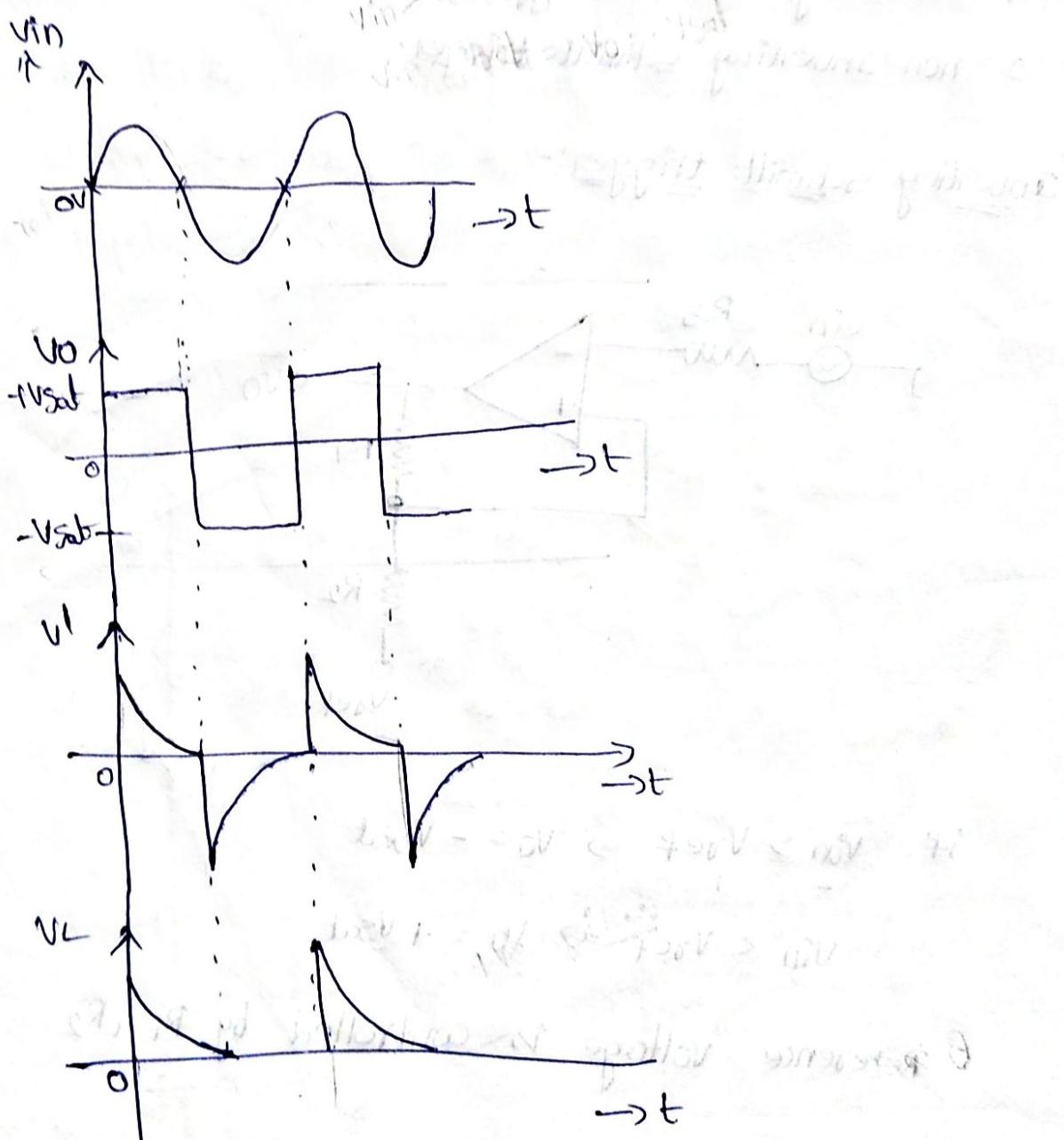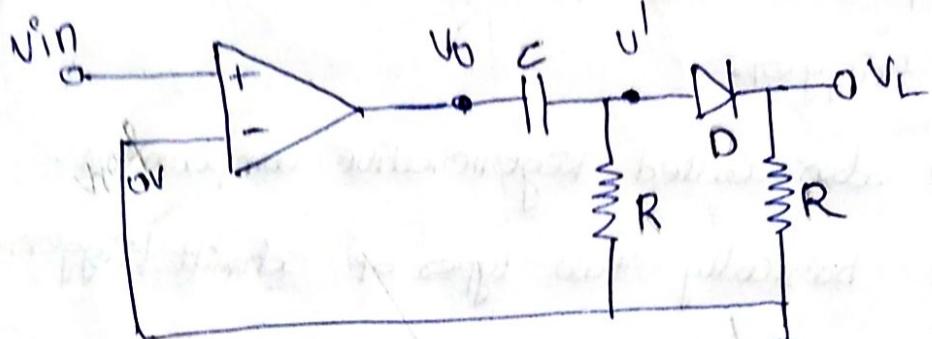pulses. The negative portion is clipped off after passing through the diode D the op is  $V_L$ .



(ii) phase detector (phase meter) :- By using time marker generator. Both voltages are converted into spikes and the time interval b/w the pulse spikes of one ip. The time interval is proportional to phase difference.

## Schmitt trigger:-

→ A Comparator with positive feedback is called Schmitt trigger.


→ It is also called Regenerative comparator.

There are basically two types of schmitt triggers.

1. Inverting schmitt trigger.

2. non-inverting schmitt trigger.

## Inverting schmitt trigger:-

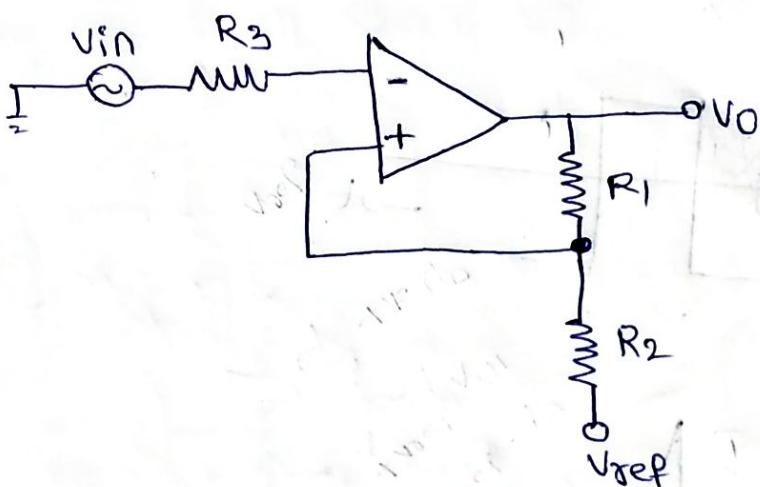

$$\text{if } V_{in} > V_{ref} \Rightarrow V_o = -V_{sat}$$

$$V_{in} < V_{ref} \Rightarrow V_o = +V_{sat}$$

Reference voltage is controlled by  $R_1 \& R_2$

$$+V_{ref} = \frac{V_o \times R_2}{R_1 + R_2} = \frac{+V_{sat} \times R_2}{R_1 + R_2} = +\beta V_{sat}$$

$$-V_{ref} = \frac{V_o \times R_2}{R_1 + R_2} = \frac{-V_{sat} \times R_2}{R_1 + R_2} = -\beta \cdot V_{sat}$$

→ At  $+V_{ref}$ ,  $V_0 = +V_{sat}$ . This is called upper threshold voltage ( $+V_{ref} = V_{UT}$ ).

→ At  $-V_{ref}$ ,  $V_0 = -V_{sat}$ . This is called lower threshold voltage ( $-V_{ref} = V_{LT}$ )

$$V_{in} > V_{UT} \Rightarrow V_0 = +V_{sat}$$

$$V_{LT} < V_{in} < V_{UT} \Rightarrow$$

$$V_{in} < V_{LT} \Rightarrow V_0 = -V_{sat}$$




$V_0 = \text{previous state}$



→ The difference b/w  $V_{UT}$  &  $V_{LT}$  is called as width of hysteresis. Denoted by  $H$ .

→ Hysteresis is also called as dead band. or


$$H = V_{UT} - V_{LT} = \frac{+V_{sat} R_2}{R_1 + R_2} + \left( \pm \frac{V_{sat} R_2}{R_1 + R_2} \right) \text{ dead zone.}$$
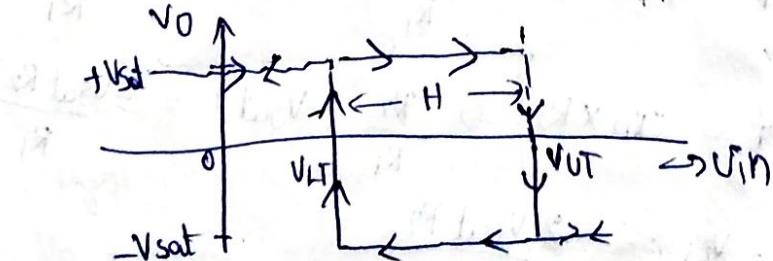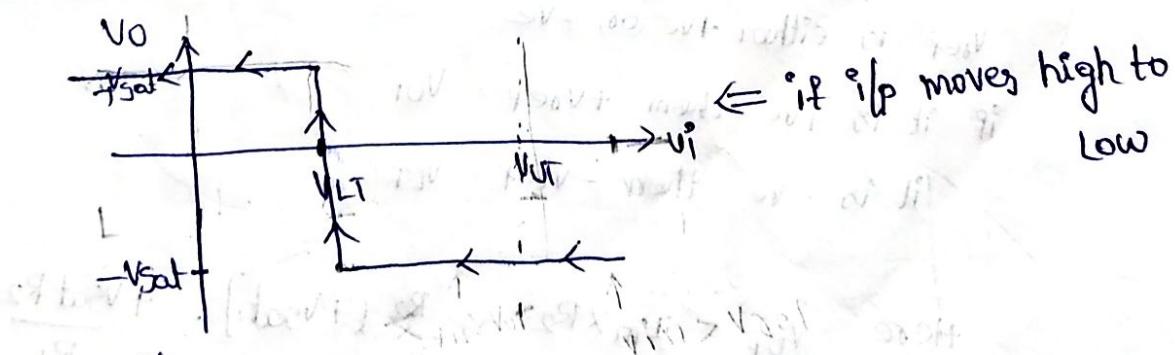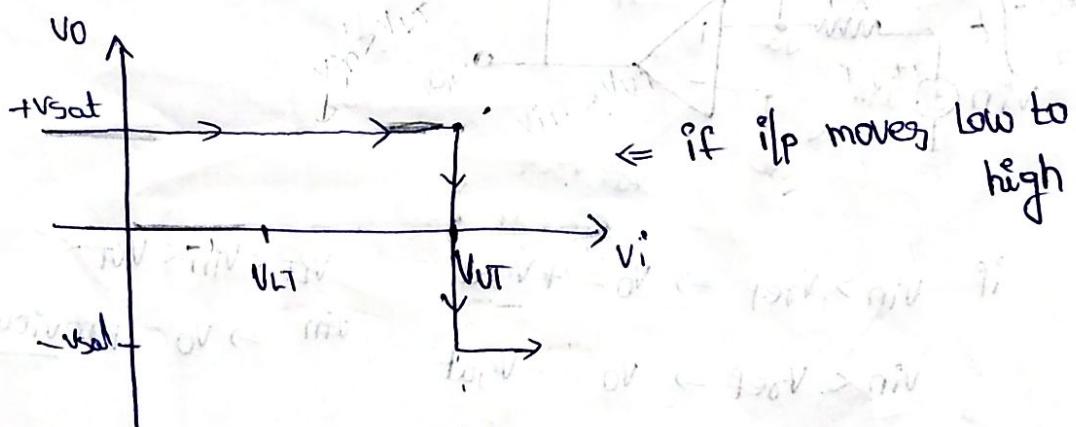
$$H = \frac{2 V_{sat} R_2}{R_1 + R_2} \quad \left[ \because H = V_{UT} - V_{LT} \right]$$



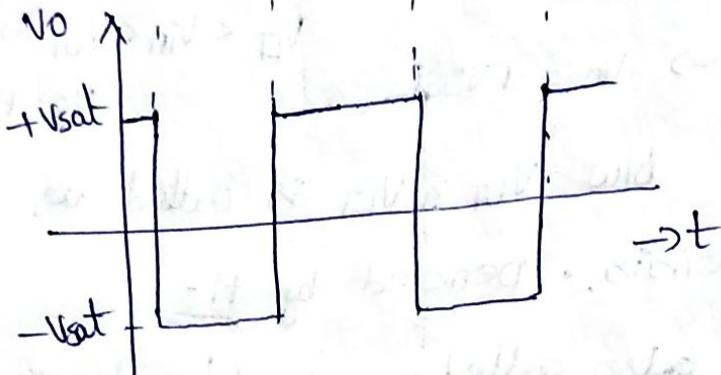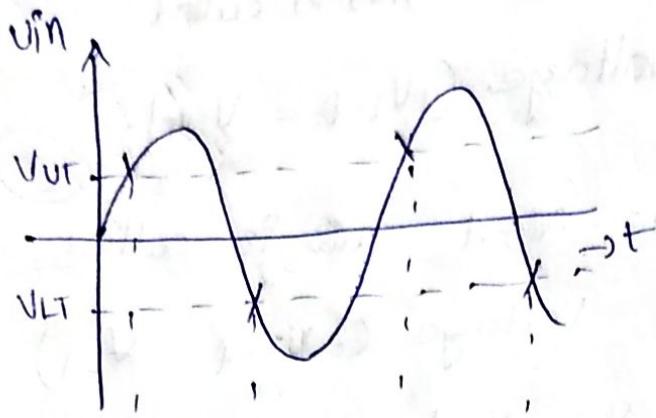

Non-Inverting Schmitt trigger!

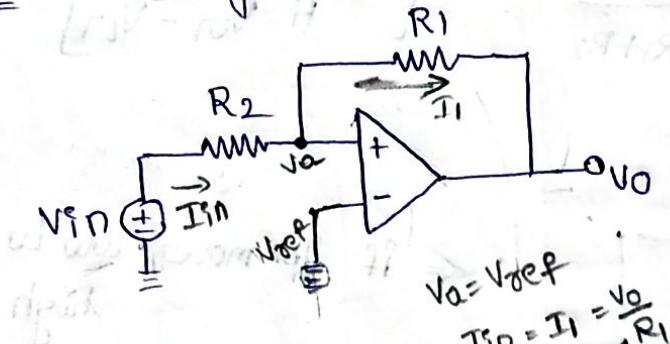

$$V_o = V_{def}$$

$$I_{in} = I_1 = \frac{V_o}{R_1}$$

if  $V_{in} > V_{ref} \Rightarrow V_O = +V_{sat}$

$V_{in} < V_{ref} \Rightarrow V_O = -V_{sat}$

$$V_{LT} < V_{in} < V_{UT}$$

~~if~~  $\Rightarrow V_O = \text{previous state}$

$V_{ref}$  is either +ve or -ve






if it is +ve then  $+V_{ref} = V_{UT}$

if it is -ve then  $-V_{ref} = V_{LT}$

$$\text{Here } V_{UT} = I_{in} \times R_2 \Rightarrow \frac{R_2}{R_1} (+V_{sat}) = +\frac{V_{sat} R_2}{R_1}$$

$$V_{LT} = I_{in} \times R_2 \Rightarrow \frac{R_2}{R_1} (-V_{sat}) = -\frac{V_{sat} R_2}{R_1}$$
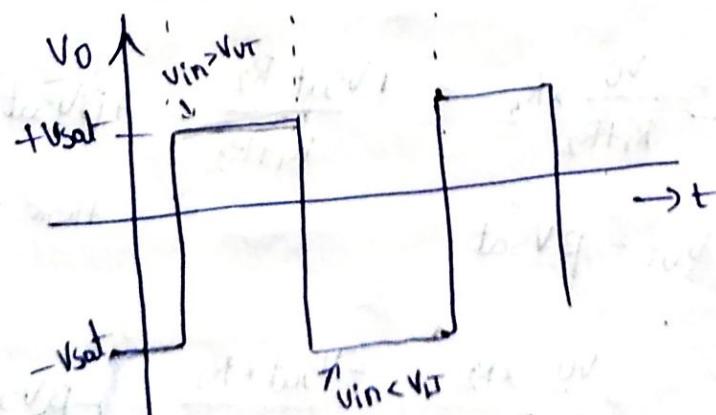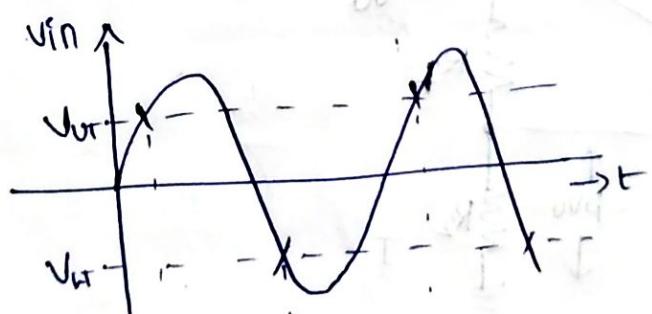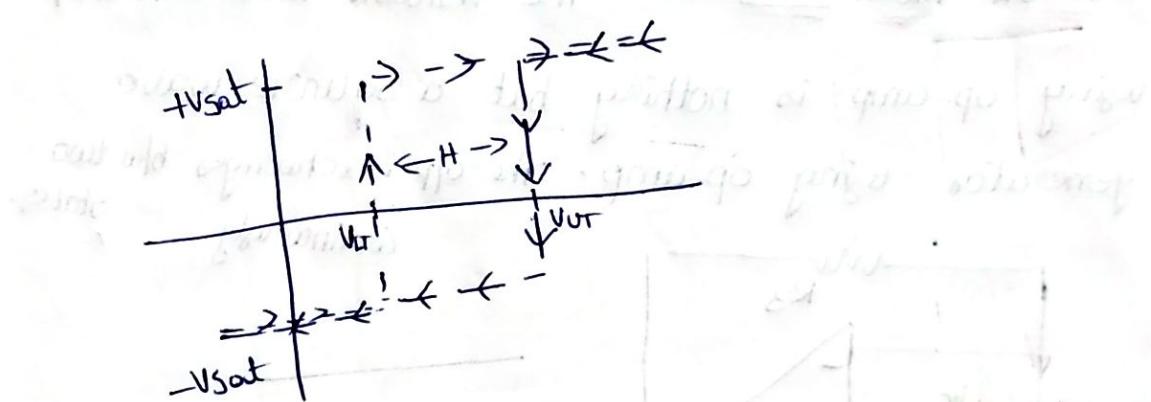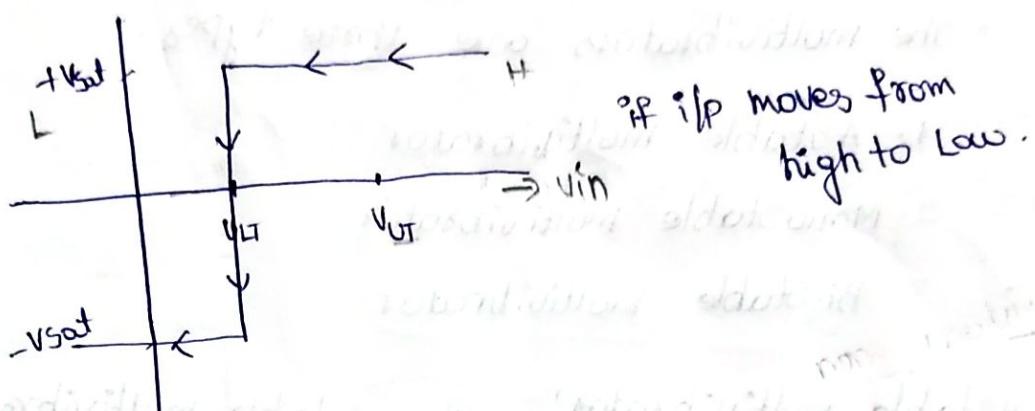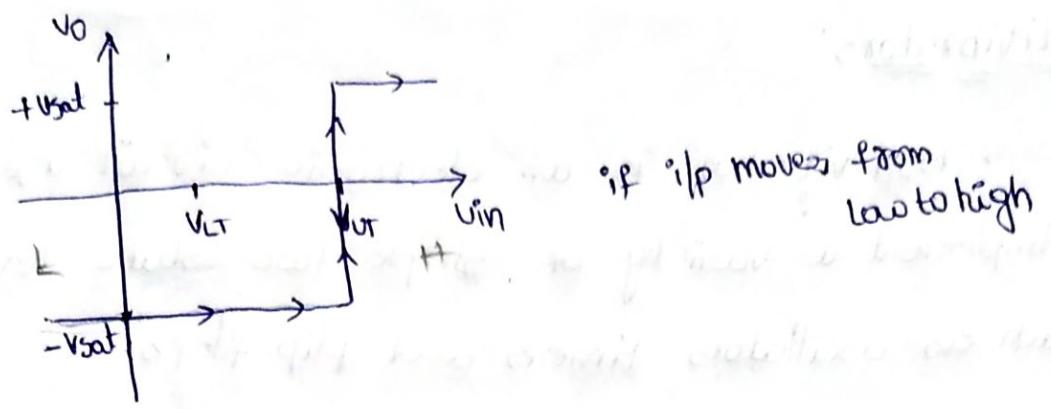
$$t = V_{UT} - V_{LT} = \frac{2 V_{sat} R_2}{R_1}$$




Hysteresis:- The output changes its states whenever i/p voltage exceeds certain voltage levels. i.e  $V_{LT} \neq V_{UT}$ .

## Multivibrators:-

- Multivibrator is an electronic circuit used to implement a variety of simple two-state devices such as oscillators, timers and flip-flops.
- The multivibrators are three types.
  1. Astable multivibrator
  2. Monostable multivibrator
  3. Bi-stable multivibrator.
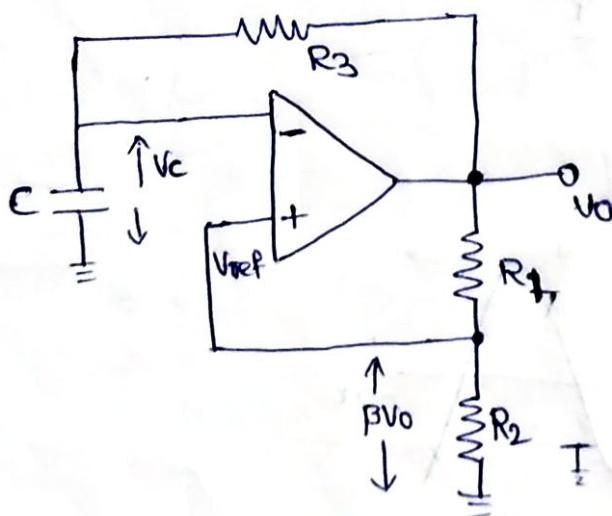
### 1. Astable multivibrator:- The Astable multivibrator

using op-amp is nothing but a square wave generator using op-amp. The o/p is changes b/w two states continuously



$$+V_{ref} = V_{UR} = \frac{V_0}{R_1 + R_2} \Rightarrow +\frac{V_{sat} R_2}{R_1 + R_2} = +\beta V_{sat}$$

$$\therefore V_{UR} = \beta V_{sat}$$

$$\text{Here } \beta = \frac{R_2}{R_1 + R_2}$$

$$-V_{ref} = V_{LT} = \frac{V_0}{R_1 + R_2} = -\frac{-V_{sat} \times R_2}{R_1 + R_2} = -\beta V_{sat}$$

Because of negative feedback, the output will be high.

$$V_{LT} = -\beta V_{sat}$$

→ if  $V_C < V_{LT} \Rightarrow V_O = +V_{sat}$  then


capacitor charges upto  $\beta V_{sat} (V_{LT})$ .

→  $V_C > V_{LT} \Rightarrow V_O = -V_{sat}$  then, [if  $V_C < V_{LT} \Rightarrow V_O = -V_{sat}$ ]

capacitor discharges upto  $-\beta V_{sat} (V_{LT})$

→  $V_C > V_{LT} \Rightarrow V_O = +V_{sat}$  then

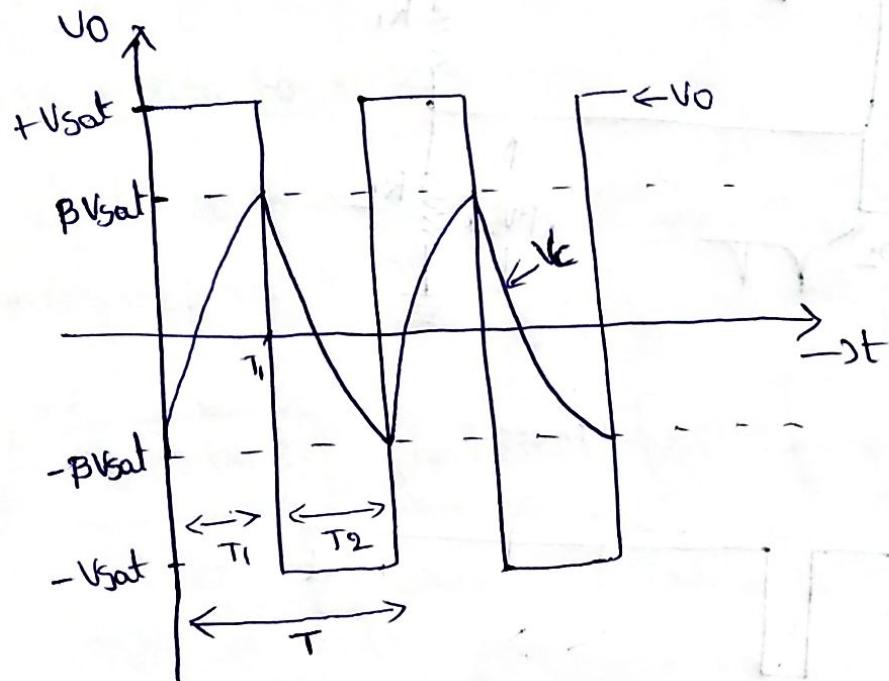capacitor charges upto  $\beta V_{sat} (V_{LT})$



The time period of waveform is



$$\therefore T = 2RC \ln \left[ \frac{1+\beta}{1-\beta} \right]$$

$$\left[ \text{Here, } \beta = \frac{R_2}{R_1+R_2} \right]$$
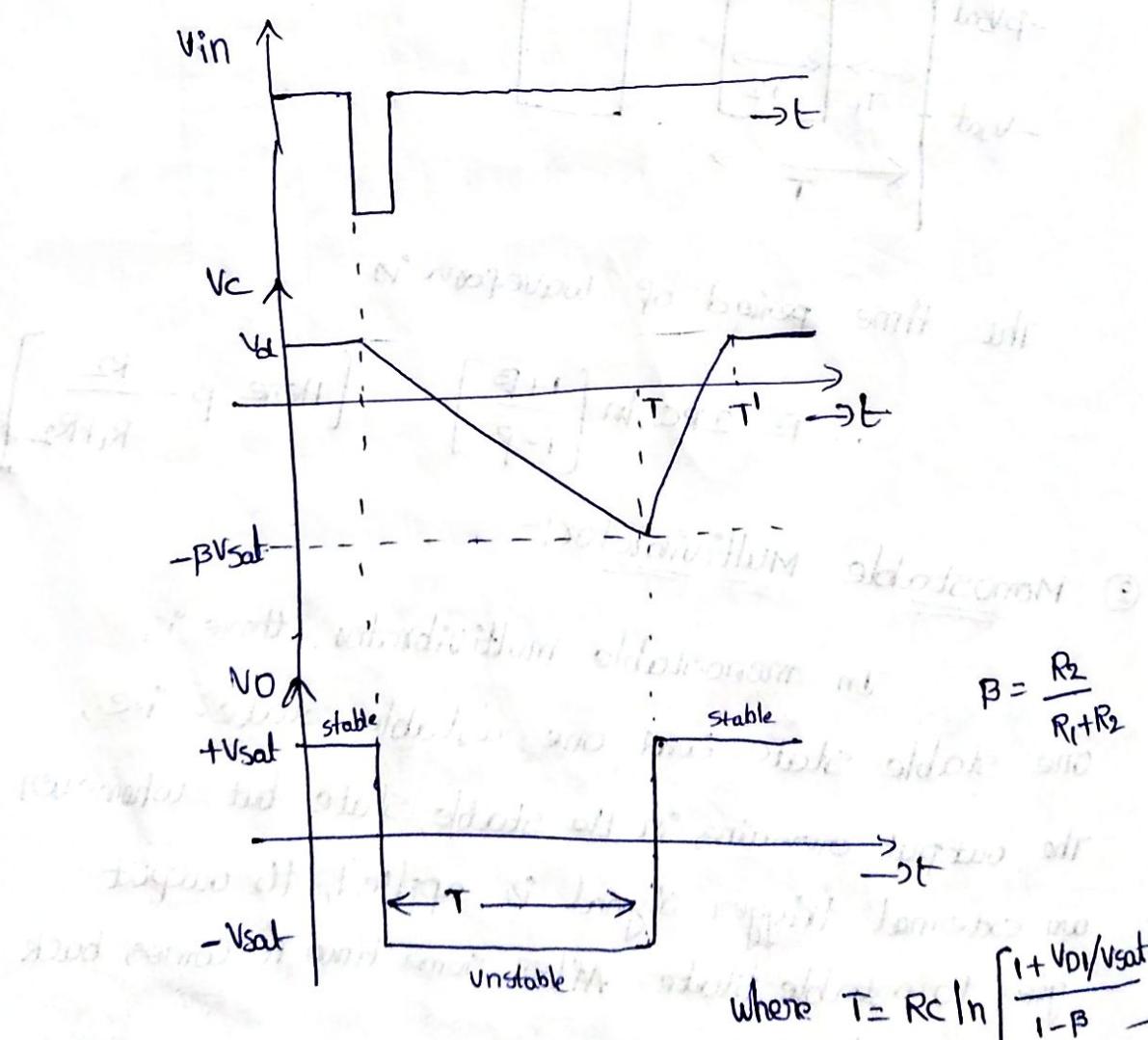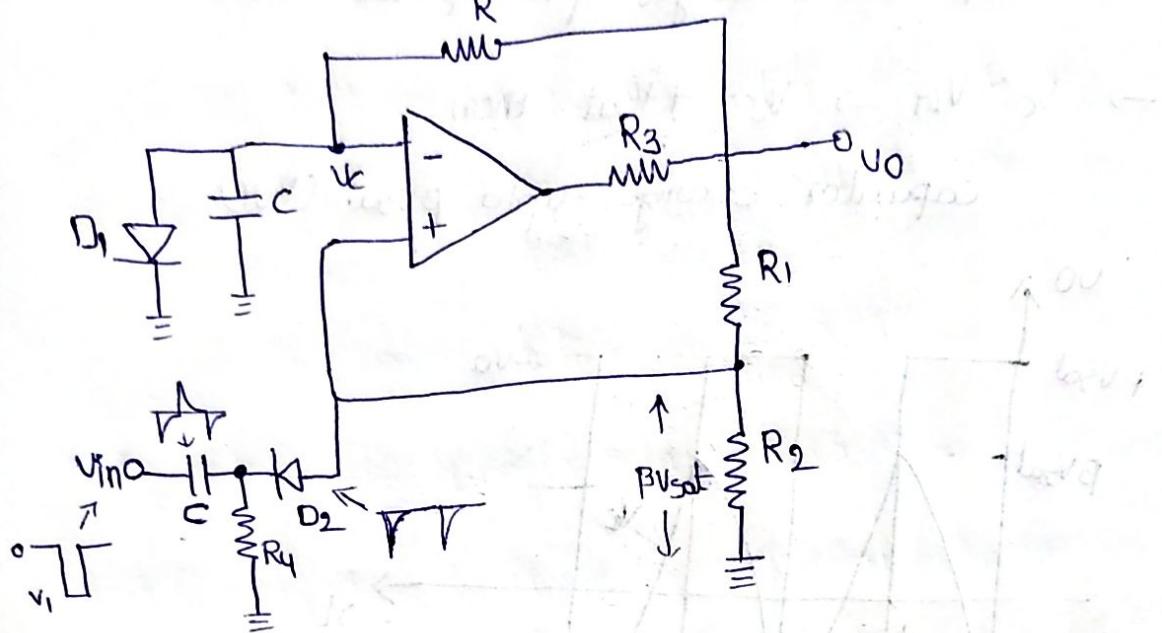
## ② Monostable Multivibrator:-

In monostable multivibrator, there is one stable state and one metastable state. i.e., the output remains in the stable state but whenever an external trigger signal is applied, the output goes to metastable state. After some time it comes back into stable state.


- The time required to come back into the stable state depends on the passive components like  $R$  &  $C$ .
- It is used in timer applications.



Bistable multivibrator:- It has two stable states. The output used to be in any one of the two stable states. Whenever an external trigger signal is applied the output goes from one stable state to another stable state. If no triggering action is applied, then it remains in the new stable state. It is used in flip-flop circuits.
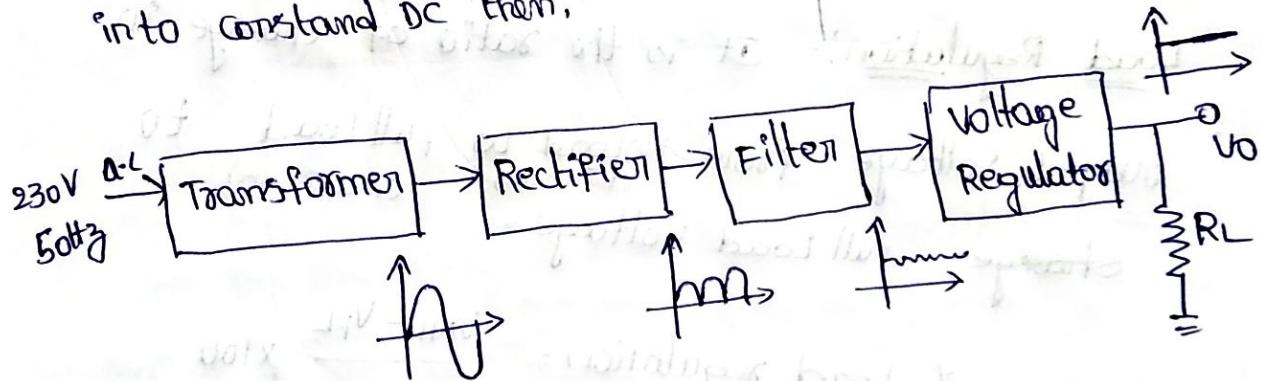
### \* Introduction to voltage Regulator:-

If the AC power supply converted into constant DC then,



→ if we are giving the AC power supply to transformer,

the o/p is AC signal.

→ the o/p of transformer AC signal is i/p of Rectifier.

It will convert AC into pulsating D.C or Ripples.

→ The o/p of Rectifier is i/p of filter. Then it will convert pure D.C. but any changes in i/p or load then o/p will change [distorted].

→ To maintain constant o/p [DC], voltage regulator is used. It gives the o/p as constant DC.

Voltage Regulator:- The voltage regulator is an electronic component of power supply, to make the output voltage constant irrespective of the changes in the load or line voltages [i.e. voltages]

Line Regulation:- It is the ratio of change in output voltage to change in input voltage.

$$\% \text{ Line regulation} = \frac{\Delta V_o}{\Delta V_{in}} \times 100$$

Ideally the line regulation is 0%.

Load Regulation:- It is the ratio of change in output voltage from No Load to full load to change in full load voltage.

$$\% \text{ Load regulation} = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100$$

Ideally the load regulation is 0%.

Voltage Regulator has four components.

1. Reference Voltage circuit

2. Error amplifier

3. pass transistor

4. Feed back network.

Depending on the connection of components the voltage regulators are classified as 2 types.

1. series voltage Regulator [  $T_0$  & Load connected in series]
2. shunt voltage Regulator [  $T_0$  & Load connected in parallel].

Depending on the operation, It is classified as:

1. Series or Linear Regulator
2. switching Regulator.

### 1. Series or Linear Regulator:

- In this regulators, the transistor connected in series b/w the unregulated dc ilp and the load.
- Linear regulators may have fixed output voltage [i.e +ve or, -ve].
- IC 723 is a Linear voltage regulator

### 2 switching Regulator:

- In switching Regulators, the transistor as a high frequency on/off switch.
- The transistor does not conduct current continuously.
- This gives improved efficiency over series regulator.

### IC 723 [General purpose Regulator]

#### Features:

- series voltage Regulator provides +ve & -ve voltage.

- provides current upto 150 mA


- with external resistor current upto 10 A

- ilp voltage between 9 to 40V.

- olp voltage between 2 to 37V

- Load and Line regulation is 0.01%


## Block diagram of IC 723:

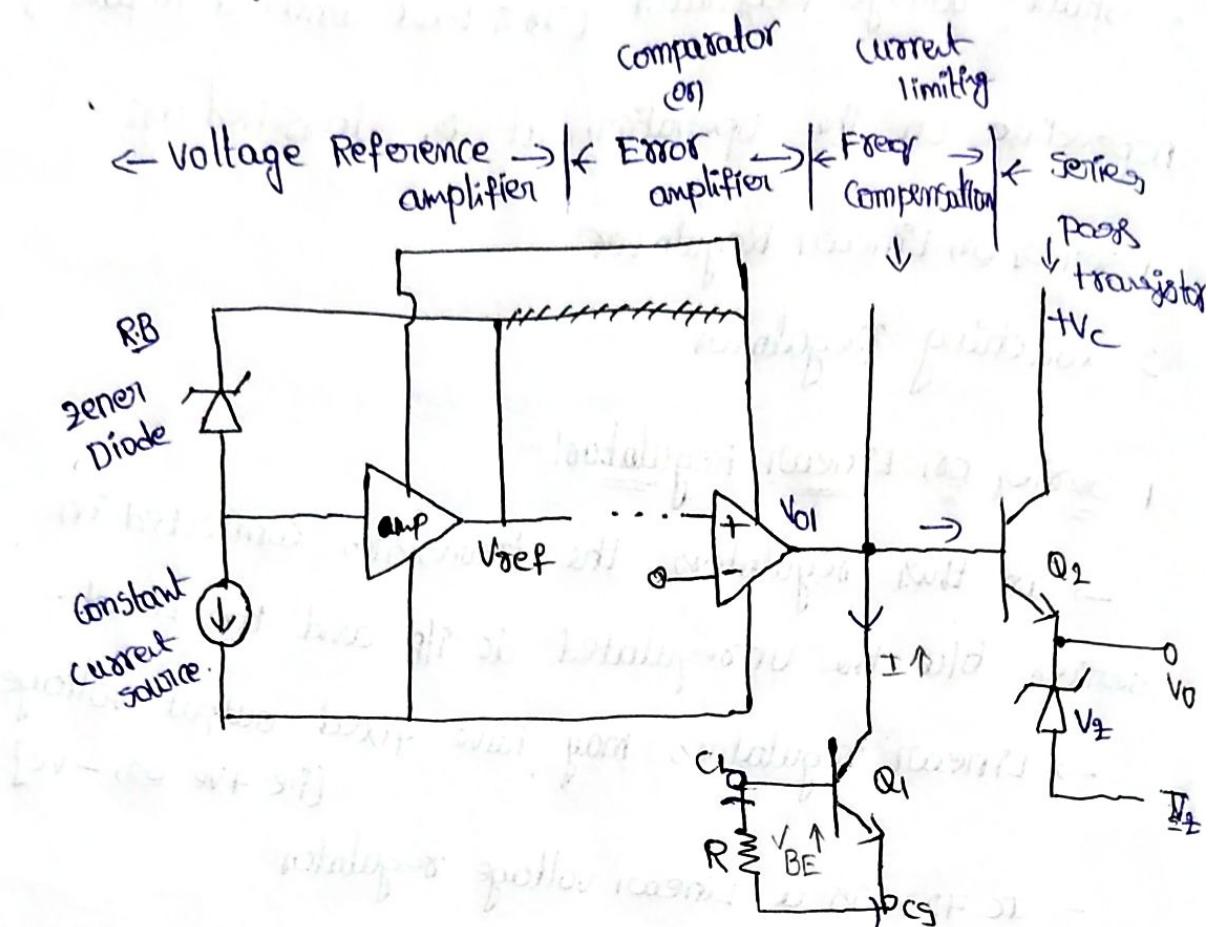

current  
Freq - in limit - OFF  
exceed - ON

- In IC 723, It has 4 blocks,
- In voltage Reference amplifier, Zener Diode is compared with Constant current source. It operates Reverse Bias.
- The output of voltage ref. amp gives to non-inverting input of the error amplifier.
- The inverting input is connected to total opv voltage.
- The output of error amplifier is connected to series pass transistor  $Q_2$ .
- Transistor  $Q_1$  acts as current limitter. It acts as ON/OFF switch.

# PIN Diagram of IC 723:-

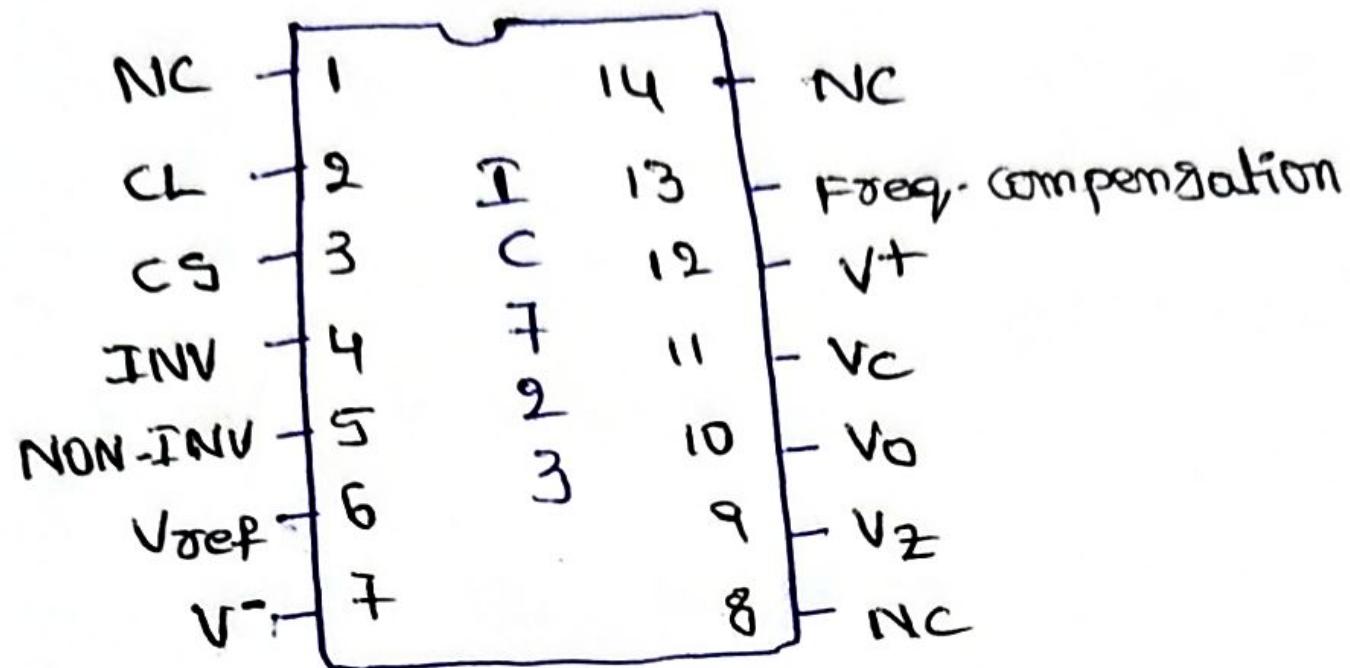

Dual - in - line package