

Multiplexer

Multiplexer


A multiplexer is a combinational circuit that has 2^n input lines and a single output line. Simply, the multiplexer is a multi-input and single-output combinational circuit. The binary information is received from the input lines and directed to the output line. On the basis of the values of the selection lines, one of these data inputs will be connected to the output.

Unlike encoder and decoder, there are n selection lines and 2^n input lines. So, there is a total of 2^N possible combinations of inputs. A multiplexer is also treated as **Mux**.

2×1 Multiplexer:

In 2×1 multiplexer, there are only two inputs, i.e., A_0 and A_1 , 1 selection line, i.e., S_0 and single outputs, i.e., Y . On the basis of the combination of inputs which are present at the selection line S_0 , one of these 2 inputs will be connected to the output. The block diagram and the truth table of the 2×1 multiplexer are given below.

Block Diagram:

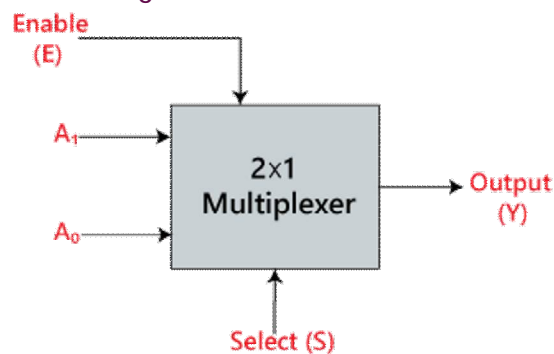


Truth Table:

INPUTS	Output
S_0	Y
0	A_0
1	A_1

The logical expression of the term Y is as follows:

$$Y = S_0' \cdot A_0 + S_0 \cdot A_1$$

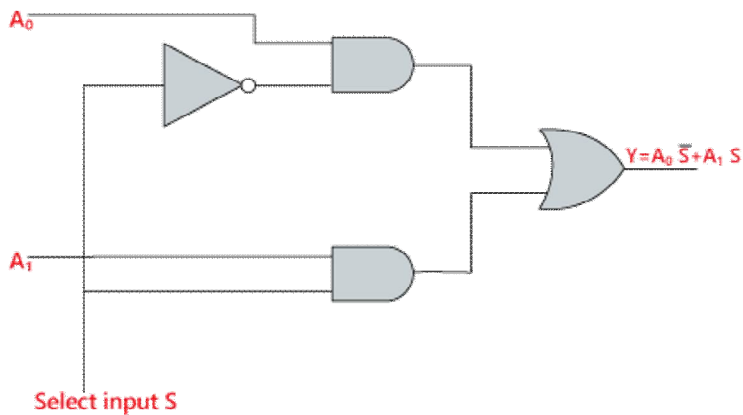
Logical circuit of the above expression is given below:



4×1 Multiplexer:

In the 4×1 multiplexer, there is a total of four inputs, i.e., A_0 , A_1 , A_2 , and A_3 , 2 selection lines, i.e., S_0 and S_1 and single output, i.e., Y . On the basis of the combination of inputs that are present at the selection lines S_0 and S_1 , one of these 4 inputs are connected to the output. The block diagram and the truth table of the 4×1 multiplexer are given below.

Block Diagram:

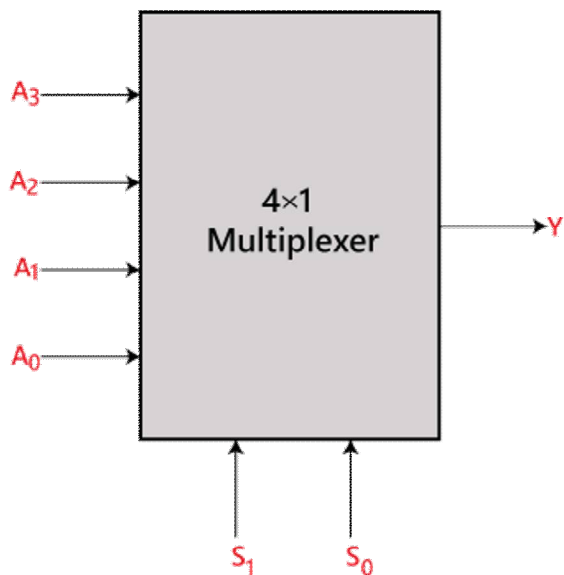


Truth Table:

INPUTS		Output
S ₁	S ₀	Y
0	0	A ₀
0	1	A ₁
1	0	A ₂
1	1	A ₃

The logical expression of the term Y is as follows:

$$Y = S_1' S_0' A_0 + S_1' S_0 A_1 + S_1 S_0' A_2 + S_1 S_0 A_3$$

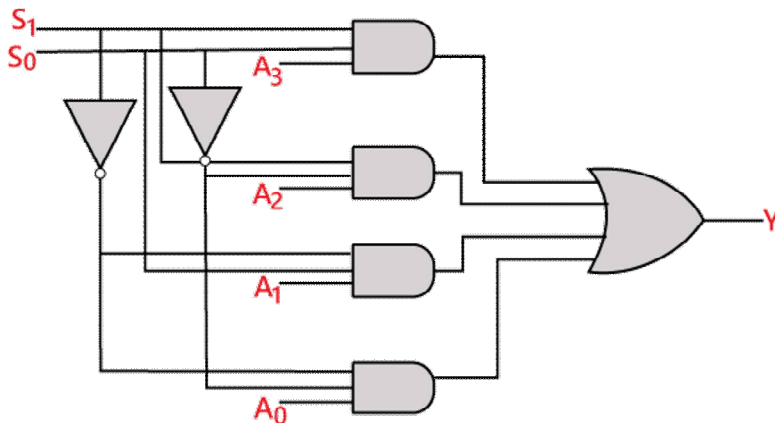
Logical circuit of the above expression is given below:




8 to 1 Multiplexer

In the 8 to 1 multiplexer, there are total eight inputs, i.e., A₀, A₁, A₂, A₃, A₄, A₅, A₆, and A₇, 3 selection lines, i.e., S₀, S₁ and S₂ and single output, i.e., Y. On the basis of the combination of inputs that are present at the selection lines S₀, S₁, and S₂, one of these 8 inputs are connected to the output. The block diagram and the truth table of the 8 × 1 multiplexer are given below.

Block Diagram:

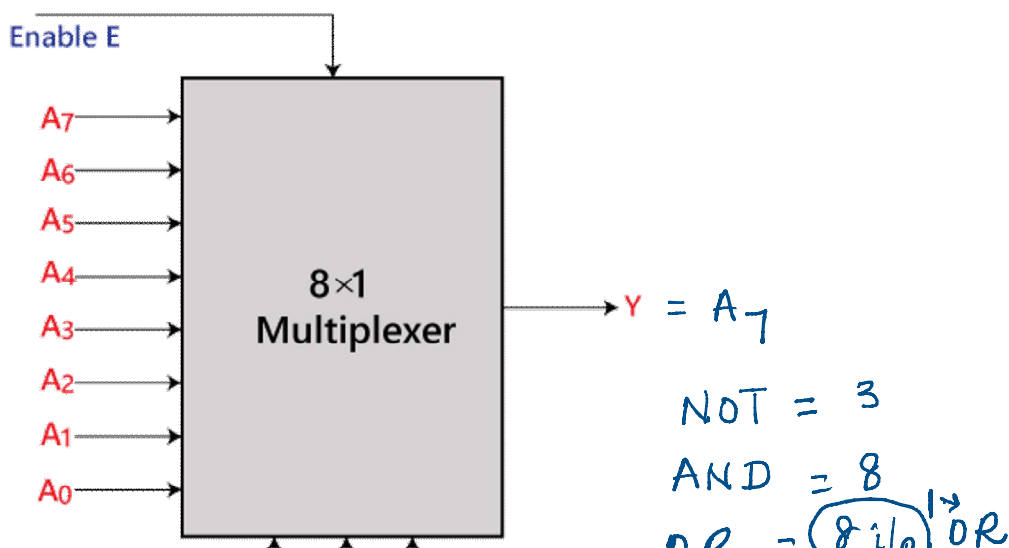

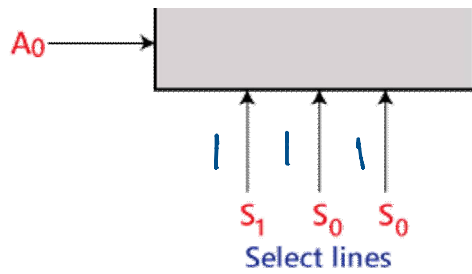

$$\text{AND} = 8$$

$$\text{OR} = \frac{8!}{p!} \text{OR}$$


Truth Table:

INPUTS			Output
S_2	S_1	S_0	Y
0	0	0	A_0
0	0	1	A_1
0	1	0	A_2
0	1	1	A_3
1	0	0	A_4
1	0	1	A_5
1	1	0	A_6
1	1	1	A_7

The logical expression of the term Y is as follows:

$$Y = S_0' \cdot S_1' \cdot S_2' \cdot A_0 + S_0 \cdot S_1' \cdot S_2' \cdot A_1 + S_0' \cdot S_1 \cdot S_2' \cdot A_2 + S_0 \cdot S_1 \cdot S_2' \cdot A_3 + S_0' \cdot S_1' \cdot S_2 \cdot A_4 + S_0 \cdot S_1' \cdot S_2 \cdot A_5 + S_0' \cdot S_1 \cdot S_2 \cdot A_6 + S_0 \cdot S_1 \cdot S_2 \cdot A_7$$

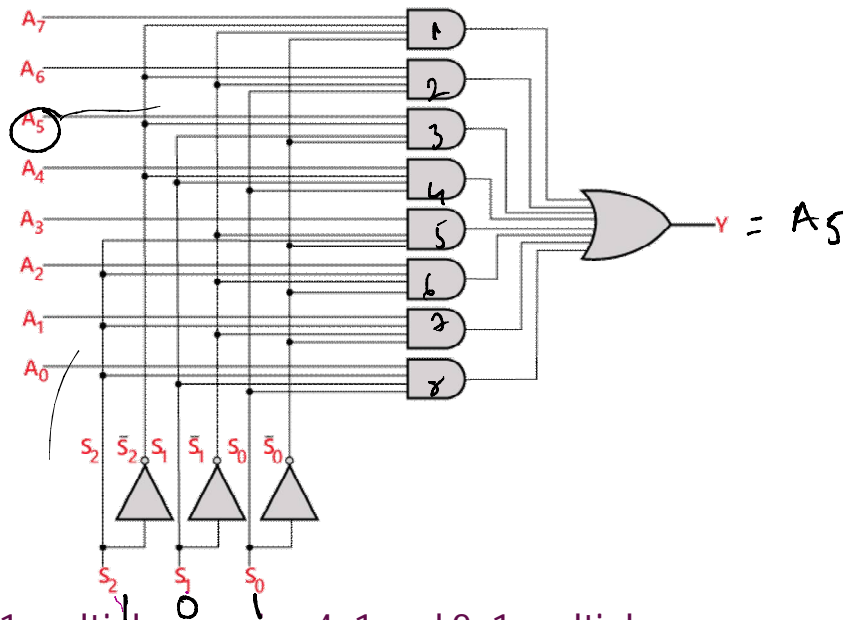Logical circuit of the above expression is given below:




8 × 1 multiplexer using 4 × 1 and 2 × 1 multiplexer

We can implement the 8 × 1 multiplexer using a lower order multiplexer. To implement the 8 × 1 multiplexer, we need two 4 × 1 multiplexers and one 2 × 1 multiplexer. The 4 × 1 multiplexer has 2 selection lines, 4 inputs, and 1 output.

The 2×1 multiplexer has only 1 selection line.

For getting 8 data inputs, we need two 4×1 multiplexers.

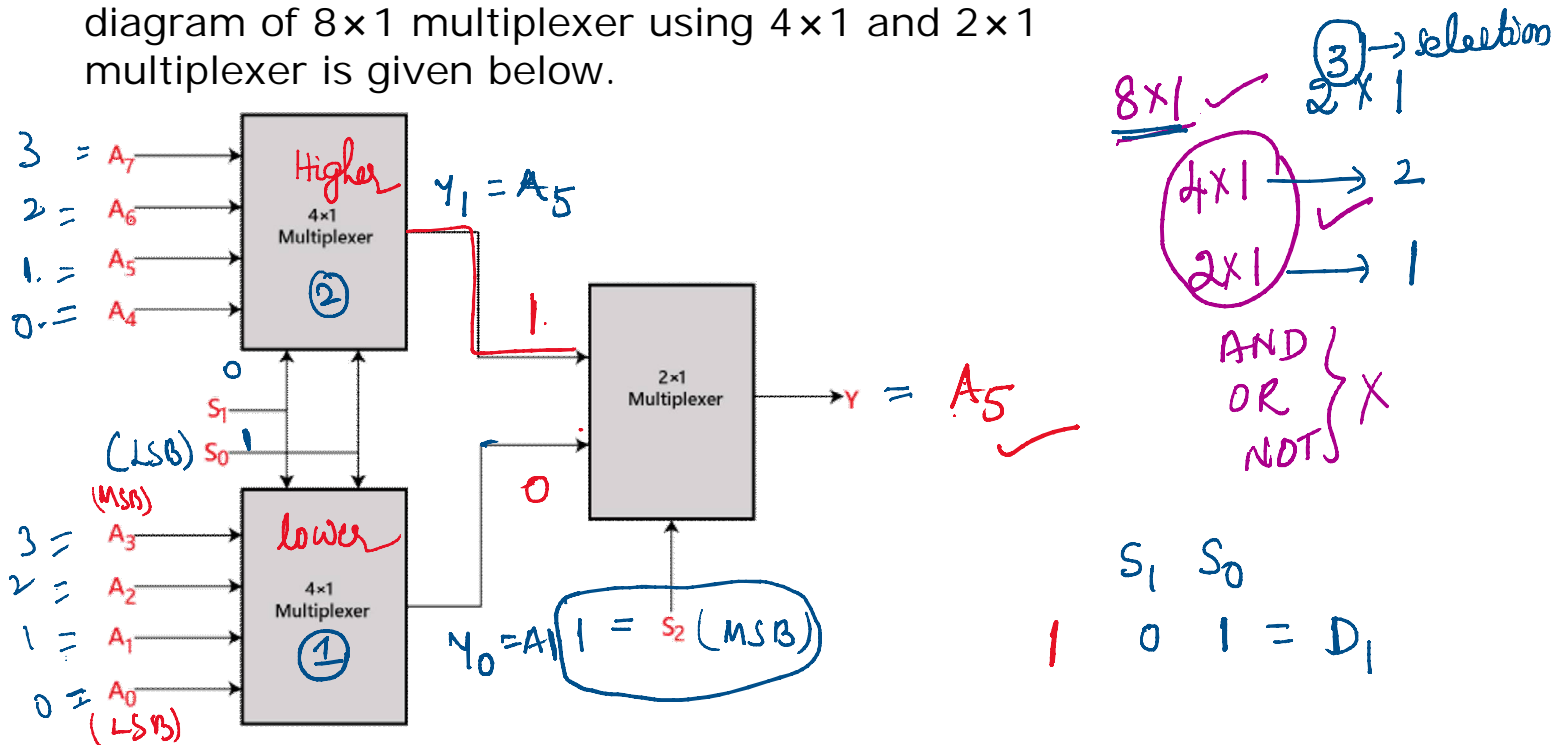
The 4×1 multiplexer produces one output. So, in order to get the final output, we need a 2×1 multiplexer. The block diagram of 8×1 multiplexer using 4×1 and 2×1 multiplexer is given below.



16 to 1 Multiplexer

In the 16 to 1 multiplexer, there are total of 16 inputs, i.e., A_0, A_1, \dots, A_{15} , 4 selection lines, i.e., S_0, S_1, S_2 , and S_3 and single output, i.e., Y . On the basis of the combination of inputs that are present at the selection lines S^0, S^1 , and S_2 , one of these 16 inputs will be connected to the output. The block diagram and the truth table of the 16×1

Block Diagram:

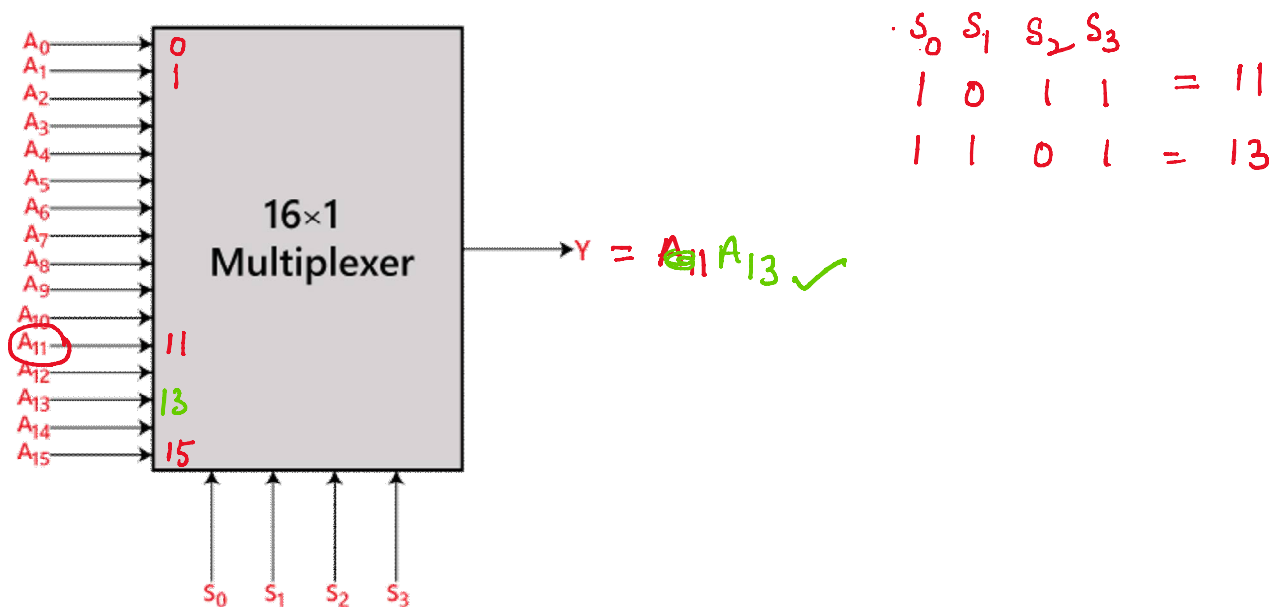


Truth Table:

INPUTS				Output
S ₀	S ₁	S ₂	S ₃	Y
0	0	0	0	A ₀
0	0	0	1	A ₁
0	0	1	0	A ₂
0	0	1	1	A ₃
0	1	0	0	A ₄
0	1	0	1	A ₅
0	1	1	0	A ₆
0	1	1	1	A ₇
1	0	0	0	A ₈
1	0	0	1	A ₉
1	0	1	0	A ₁₀
1	0	1	1	A ₁₁
1	1	0	0	A ₁₂
1	1	0	1	A ₁₃
1	1	1	0	A ₁₄
1	1	1	1	A ₁₅

The logical expression of the term Y is as follows:


$$Y = A_0 \cdot S_0' \cdot S_1' \cdot S_2' \cdot S_3' + A_1 \cdot S_0' \cdot S_1' \cdot S_2' \cdot S_3 + A_2 \cdot S_0' \cdot S_1' \cdot S_2 \cdot S_3' + A_3 \cdot S_0' \cdot S_1' \cdot S_2 \cdot S_3 + A_4 \cdot S_0' \cdot S_1 \cdot S_2' \cdot S_3' + A_5 \cdot S_0' \cdot S_1 \cdot S_2' \cdot S_3 + A_6 \cdot S_0' \cdot S_1 \cdot S_2 \cdot S_3' + A_7 \cdot S_0' \cdot S_1 \cdot S_2 \cdot S_3 + A_8 \cdot S_0 \cdot S_1' \cdot S_2' \cdot S_3' + A_9 \cdot S_0 \cdot S_1' \cdot S_2' \cdot S_3 + A_{10} \cdot S_0 \cdot S_1' \cdot S_2 \cdot S_3' + A_{11} \cdot S_0 \cdot S_1' \cdot S_2 \cdot S_3 + A_{12} \cdot S_0 \cdot S_1 \cdot S_2' \cdot S_3' + A_{13} \cdot S_0 \cdot S_1 \cdot S_2' \cdot S_3 + A_{14} \cdot S_0 \cdot S_1 \cdot S_2 \cdot S_3' + A_{15} \cdot S_0 \cdot S_1 \cdot S_2 \cdot S_3$$

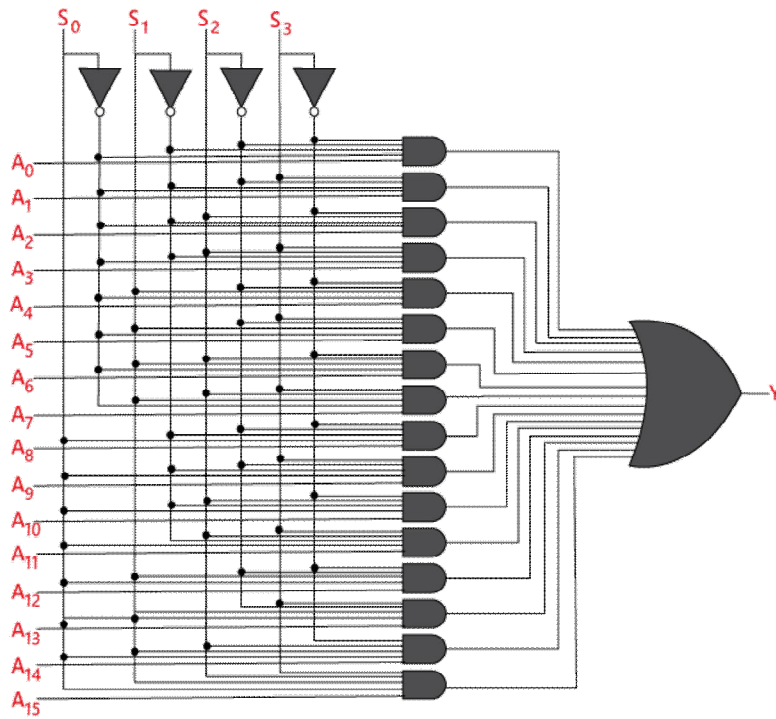
Logical circuit of the above expression is given below:



16x1 multiplexer using 8x1 and 2x1 multiplexer

We can implement the 16x1 multiplexer using a lower order multiplexer. To implement the 8x1 multiplexer, we need two 8x1 multiplexers and one 2x1 multiplexer. The 8x1 multiplexer has 3 selection lines, 4 inputs, and 1 output. The 2x1 multiplexer has only 1 selection line. For getting 16 data inputs, we need two 8x1 multiplexers. The 8x1 multiplexer produces one output. So, in order to get the final output, we need a 2x1 multiplexer. The block diagram of 16x1 multiplexer using 8x1 and 2x1 multiplexer is given below.

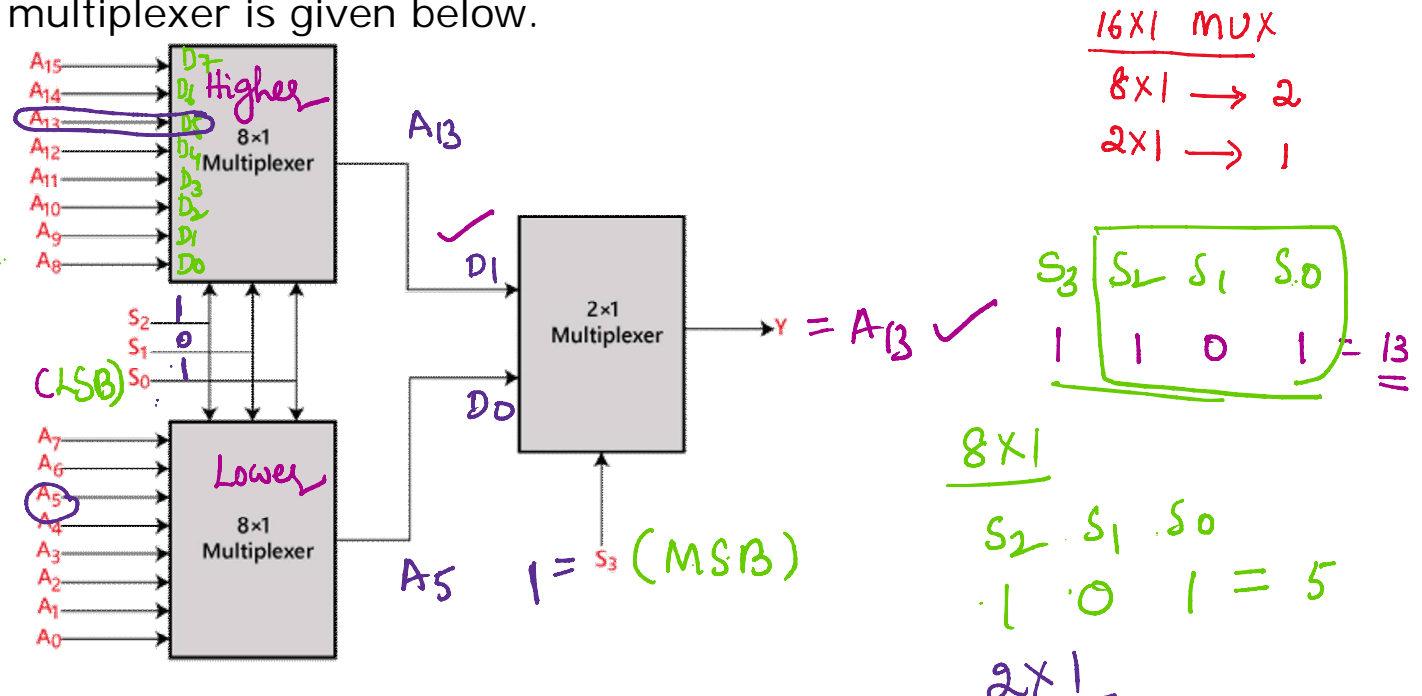

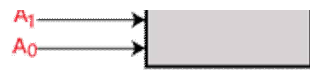

2×1

S_3	Y
0	$D_0 = A_5$
1	$D_1 = A_{13}$