
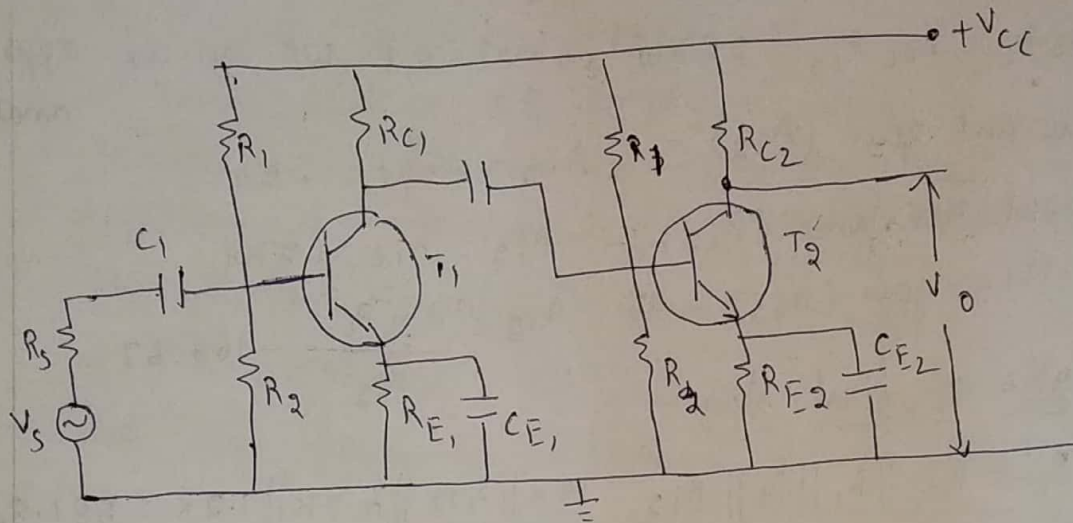


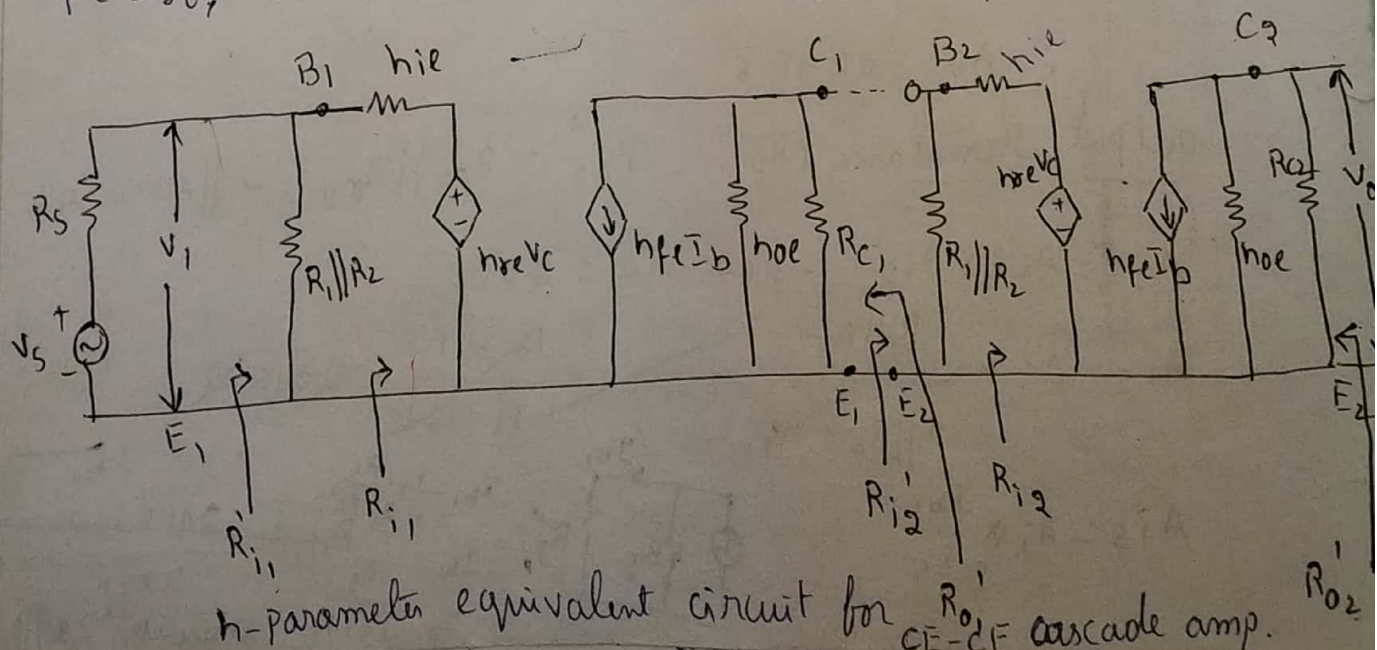Two stage RC coupled CE-CE Cascade Amplifier:-



CE-CE Cascade amplifier

→ Assuming all capacitors arbitrarily large and act as a short circuit for ac signal we can draw h-parameter equivalent circuit for CE-CE cascade amplifier, as shown in fig. Calculate R_i , A_i , A_v , R_o' , A_{vs} and A_{is} if circuit parameters are $R_S = 1K$, $R_{C1} = 15K$, $R_{E1} = 100\Omega$, $R_{C2} = 4K$, $R_{E2} = 330\Omega$ with $R_1 = 200K$ and $R_2 = 20K$ for first stage and $R_3 = 47K$ and $R_4 = 4.7K$ for second stage. Assume that $h_{ie} = 1.2K\Omega$, $h_{fe} = 50$, $h_{re} = 2.5 \times 10^{-4}$ and $h_{oe} = 25 \times 10^{-6} A/V$.



Analysis of second stage:-

$$h_{oe} R_L = h_{oe} R_{C2} = 25 \times 10^{-6} \times 4 \times 10^3 = 0.1 \quad \text{We can use approximate analysis}$$

(i) current gain (A_{i2}):- $A_{i2} = -h_{fe} = -50$

(ii) Input resistance (R_{i2}):- $R_{i2} = h_{ie} = 1.2 \text{ K}\Omega$

(iii) voltage gain (A_{v2}):- $A_{v2} = \frac{A_{i2} R_L}{R_{i2}} = -166.67$

Analysis of first stage:-

$$R_L' = R_{C1} \parallel R_1 \parallel R_2 \parallel R_{i2} = 15 \text{ K}\Omega \parallel 47 \text{ K}\Omega \parallel 4.7 \text{ K}\Omega \parallel 1.2 \text{ K}\Omega = 881.8 \Omega$$

$\therefore h_{oe} R_L' = 0.022 < 0.1$ so we can use approximate Analysis

(i) current gain (A_{i1}):- $A_{i1} = -h_{fe} = -50$

(ii) Input resistance (R_{i1}):- $R_{i1} = h_{ie} = 1.2 \text{ K}\Omega$

(iii) voltage gain (A_{v1}):- $A_{v1} = \frac{A_{i1} R_L'}{R_{i1}} = -36.74$

over all gain (A_v) $A_v = A_{v1} \times A_{v2} = 6123.45$

overall voltage gain (A_{vs}):- $A_{vs} = \frac{A_v \times R_{i1}'}{R_{i1}' + R_s}$

$$R_{i1}' = R_1 \parallel R_2 \parallel R_{i1} = 1.13 \text{ K}\Omega$$


$$\therefore A_{vs} = 3248.6$$

output Resistance (R_o):- $R_{o2}' = R_{o2} \parallel R_{C2} = \infty \parallel 4 \text{ K}\Omega = 4 \text{ K}\Omega$

$$A_I = A_{i1} \times A_{i2} = -50 \times -50 = 2500$$

$$A_{is} = A_i \times \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{i1}} = 2500 \times \frac{18.18 \text{ K}\Omega}{19.38 \text{ K}\Omega} = 2345.2$$
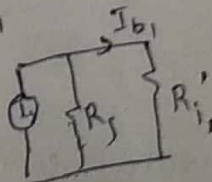
$$A_{is} = A_i \times \frac{I_{b1}}{I_s}$$



$$I_{b1} = I_s \times \frac{R_s}{R_s + R_{i1}} = \frac{200 \text{ K}\Omega \times 20 \text{ K}\Omega}{220 \text{ K}\Omega} = 18.18 \text{ K}\Omega$$

where $R_{i1}' = R_1 \parallel R_2 \parallel R_{i1}$

Analysis of first stage (CE amplifier):-

(i) Current gain (A_{i1}):- $A_{i1} = -h_{fe} = -50$

(ii) Input resistance (R_{i1}):- $R_{i1} = h_{ie} = 1.1 \text{ k}\Omega$

(iii) Voltage gain (A_{V1}):- $A_{V1} = \frac{A_{i1} R_{L1}}{R_{i1}} = \frac{-50 \times 21.56}{1.1 \text{ k}} = -0.98$

where $R_{L1} = R_{i2} = 21.56 \Omega$.

overall voltage gain (A_V) = $A_{V1} \times A_{V2} = -0.98 \times 136.36 = -133.63$

overall i/p resistance (R_i) = $R_{i1} \parallel R_B = R_{i1} \parallel R_3 \parallel R_4 = 986.1 \Omega$

$$A_{Vs} = \frac{V_o}{V_s} = \frac{V_o}{V_i} \times \frac{V_i}{V_s} = A_V \times \frac{R_i}{R_i + R_s} = -66.35$$

$$A_{is} = \frac{I_o}{I_s} = \frac{I_o}{I_{c2}} \times \frac{I_{c2}}{I_{e2}} \times \frac{I_{e2}}{I_{c1}} \times \frac{I_{c1}}{I_{b1}} \times \frac{I_{b1}}{I_s}$$

$$\frac{I_o}{I_{c2}} = -1 ; \frac{I_{c2}}{I_{e2}} = -A_{i2} ; \frac{I_{e2}}{I_{c1}} = -1 ; \frac{I_{c1}}{I_{b1}} = -A_{i1}$$

$$\frac{I_{b1}}{I_s} = \frac{R_B}{R_B + R_{i1}}$$

$$\therefore A_{is} = -1 \times -A_{i2} \times -1 \times -A_{i1} \times \frac{R_B}{R_B + R_{i1}} = -43.9$$

o/p Resistance (R_o):- $R_o = R_{o2} \parallel R_L = \infty \parallel 3 \text{ k} = 3 \text{ k}$

Direct coupling:-

- No coupling element
- It ~~allow~~ affecting the biasing conditions of next stage
- This unwanted change in the o/p is called drift. It is serious problem in the Direct coupled amplifiers.
- DC amplification ~~was~~ done.
- It is used in amplification of slow varying parameters and where DC amplification is required.
- It is simple circuit.

Comparison between various cascading methods:-

RC coupled:-

- Coupling elements are Resistors and capacitors.
- It blocks dc
- Frequency response is Flat at middle frequencies.
- Light weight circuit and simple circuit.
- Used in all audio small signal amplifiers, record players, tape recorders ~~players~~, public address systems, radio receivers and television receivers.

Transformer coupled:-

- Coupling component is impedance matching transformer.
- It blocks dc.
- Frequency response is not uniform, high at resonant frequency and low at other frequencies.
- It is used in impedance matching.
- It is Bulky and heavy.
- It is used in amplifiers where impedance matching is an important criteria.
- It is used in the o/p stage of the public address system to match the impedance of loudspeaker.
- Used in the RF amplifier stage of the receiver as a tuned voltage amplifier.