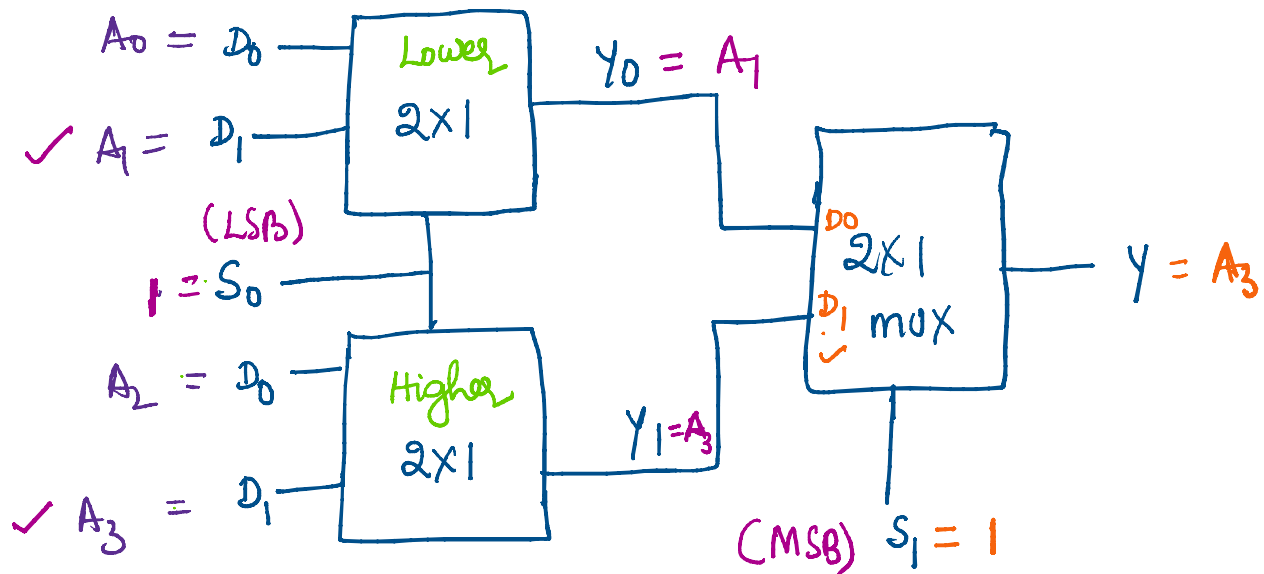


Higher order Multiplexer Design

4x1 multiplexer using 2x1 multiplexer



Required	Available	S_1	S_0	Y
↓	↓	1	1	=
4x1 mux	2x1			


$$\text{No. of multiplexers required} = \frac{\text{Required mux i/p}}{\text{Available mux i/p}} = \frac{4}{2} = 2$$

No. of 2x1 mux required to design 16x1 mux = —

8x1 mux using 2x1 mux

8x1 mux using 2x1 mux

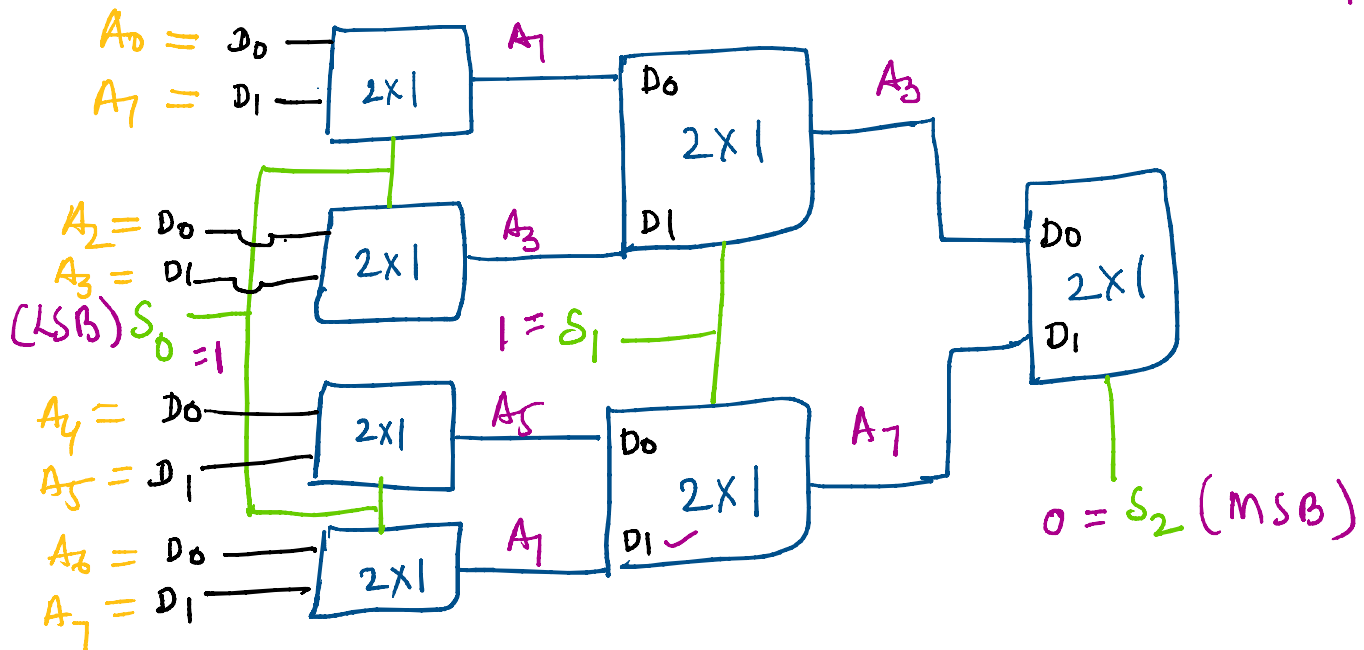No. of mux Required in first stage = $\frac{\text{Required mux i/p}}{\text{Available mux i/p}} = \frac{8}{2} = 4$



16x1 mux using 2x1 mux

first stage = $\frac{16}{2} = 8$

