

Prob. Tutorial problems - Determine the output voltage in each of the following cases for the open-loop D.A shown in Fig.

(a) $V_{in1} = 5 \mu V$ dc $V_{in2} = -7 \mu V$ dc

(b) $V_{in1} = 10 mV$ rms $V_{in2} = 20 mV$ rms.

The op-amp is a $\mu 741$ with the following

specification $A = 200000$ $R_i = 2 M\Omega$.

$R_o = 75 \Omega$ $+V_{cc} = +15 V$ $-V_{EE} = -15 V$ and

output voltage swing $= \pm 14 V$.

(a) $V_o = 200000 [5 \times 10^{-6} + 7 \times 10^{-6}] = 2.4 V$ dc.

Assume that output offset voltage is zero.

(b) $V_o = 200000 [10 \times 10^{-3} - 20 \times 10^{-3}]$
 $= -2000 V$ rms.

The theoretical value of out voltage is $V_o = -2000 V$ rms. The op-amp saturates at $\pm 14 V$. The actual o/p is clipped as shown in Fig. This non sinusoidal waveform is unacceptable in amplifier applications.

(2) For the $\mu A 741$ op-amp $PSRR = 70 dB$ min what is the numerical value of $PSRR$.

$$PSRR = 20 \log \frac{\Delta V_{io}}{\Delta V_o} = 70$$

$$\frac{\Delta V_{io}}{\Delta V} = ? \text{ Antilog}(3.5) \dots$$

- ③ The output voltage of a certain op-amp ckt changes by 20V in 4 μ sec.. what is its slew rate.

$$SR = \frac{20}{4} \frac{V}{\mu\text{sec}} = 5V/\mu\text{sec}$$

- ④ For the 741C opamp, the supply voltage rejection ratio is 150 μ V/V. cal the change in this op-amp's ΔV_{io} if the supply voltages varies from $\pm 10V$ to $\pm 12V$.

$$150 = \frac{\Delta V_{io}}{2}$$

$$\Delta V_{io} = 300 \mu\text{V}.$$


- ⑤ The 714C op-amp is used in a particular application. The change in the op-amp's input offset voltage V_{io} caused by variation in the supply voltages is 60 μ V. Determine the change in the supply voltages. Assume that $SVRR$ for 714C is 104 dB.

Tutorial problems

⑥ An op-amp with a slew rate of $10\text{V}/\mu\text{s}$ is used as an inverting amplifier with gain -4 . It has a 250kHz square wave as the i/p with an amplitude of 0.5V_p and -1V dc average voltage.

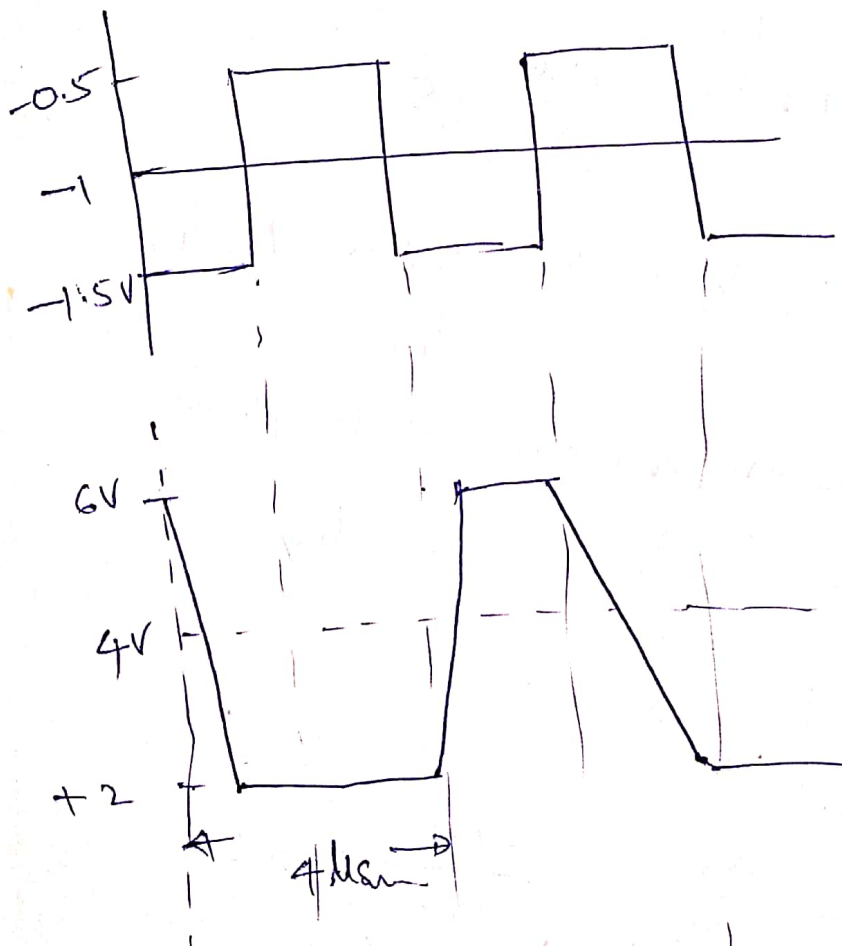- (a) Find the time t it takes to reach max output voltage.
(b) Draw the o/p waveform.

$$(a) \quad t = \frac{\Delta V}{S} = \frac{4\text{V}_{\text{p-p.}}}{10\text{V}/\mu\text{s}} = 0.4\mu\text{s}$$



② The o/p voltages of an op-amp are $V_1 = 1005 \text{ mV}$, $V_2 = 995 \text{ mV}$. The op-amp parameters are $\text{CMRR} = 100 \text{ dB}$, $A_d = A_o = 2 \times 10^5$. Determine the

- The differential voltage V_d
- The common-mode voltage V_c
- $|A_c|$ and
- The o/p voltage.

Soln. $20 \log \text{CMRR} = 100 \text{ dB}$

$$\log \text{CMRR} = 5$$

$$\text{CMRR} = \frac{A_d}{A_c} = 10^5$$

$$(a) \quad V_d = V_1 - V_2 = 1005 \text{ mV} - 995 \text{ mV} = 10 \text{ mV}$$

(b) The common mode voltage is

$$V_c = \frac{V_1 + V_2}{2} = 1000 \text{ mV}$$

$$(c) \quad \left| \frac{A_d}{A_c} \right| = 10^5$$

$$A_c = \frac{A_d}{10^5} = \frac{2 \times 10^5}{10^5} = \pm 2$$

$$|A_c| = 2$$

(d) The output voltage


$$V_o = A_d V_d + A_c V_c$$

$$= 2 \times 10^5 \times 10 \mu\text{V} \pm 2 \times 995 \mu\text{V}$$

$$= 2.002 \text{ V} = \underline{1.998 \text{ V}}$$

⑧ Determine the closed loop i/p resistance at the noninverting terminal of a NI amplifier with $A_{OL} = 10^5$, $R_c = 10 \text{ k}\Omega$, $R_f = 10 \text{ k}\Omega$
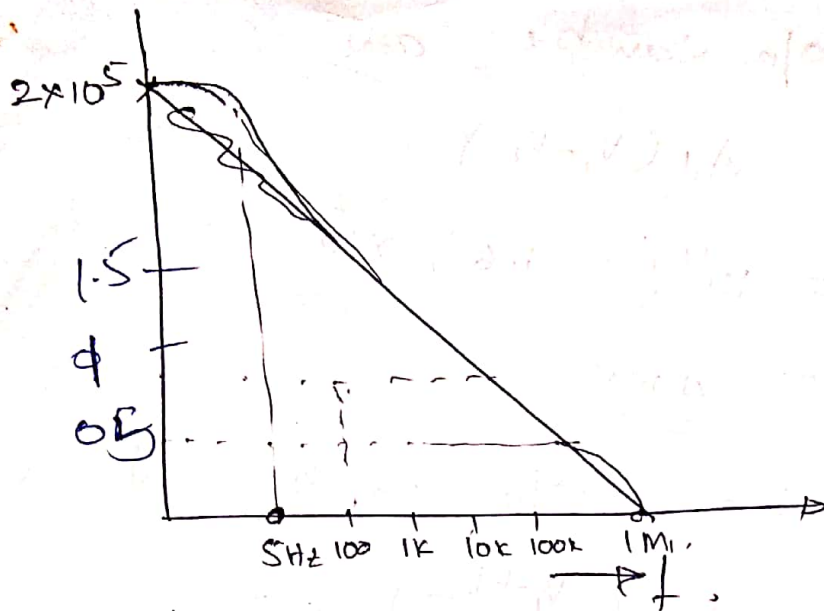
$$R_{if} = \frac{R_i(1+A_{OL})}{1+R_f/R_i} = \frac{10^4(1+10^5)}{2} = 450 \text{ m}\Omega$$



Probs.

- ① An op-amp has a differential gain of 80dB and CMRR of 95dB. If $V_1 = 2\text{mV}$ and $V_2 = 1.6\text{mV}$, the cal the differential and common mode output values.

$A_d = 80\text{dB}$ and $\text{CMRR} = 95\text{dB}$.

$$A_d \text{ in dB} = 20 \log A_d.$$

$$80 = 20 \log A_d.$$

$$A_d = A_d \log 4$$

$$= 10^4.$$

$$\text{CMRR in dB} = 20 \log \text{CMRR}.$$

$$95 = 20 \log \text{CMRR}$$

$$\text{CMRR} = A_d \frac{9.5}{20}$$

$$= A_d \log 4.75.$$

$$= 10^{4.75}.$$

$$= 5.6234 \times 10^4$$

Differential o/p can be cal as.

$$\begin{aligned}V_d &= A_d (V_1 - V_2) \\&= 10^4 (2 - 1.6) \times 10^{-6} \\&= \underline{\underline{4 \text{ mV}}}.\end{aligned}$$

And Common Mode o/p can be cal as

$$\begin{aligned}V_c &= A_c \left(\frac{V_1 + V_2}{2} \right) \\CMRR &= \frac{A_d}{A_c}.\end{aligned}$$

$$A_c = 0.1778.$$

$$\begin{aligned}V_c &= 0.1778 \left(\frac{2 + 1.6}{2} \right) \times 10^{-6} \\&= 0.32 \text{ } \mu\text{V}.\end{aligned}$$

- ② An op-amp has 7 kHz sine wave i/p signal. Find the largest amplitude that the o/p of the amp can have without distortion with I_{CO} of 8 mA and C of 27 pF

$$S = \frac{I}{C} = \frac{8 \times 10^{-6}}{27 \times 10^{-12}} = 0.2962 \text{ V}/\mu\text{s}.$$

$$f_m = \frac{S}{2\pi V_m} = 7 \text{ kHz}.$$

$$V_m = \frac{0.2962 \times 10^6}{2\pi \times 7 \times 10^3} = 6.736 \text{ V}.$$

j) A Square wave of peak to peak amplitude of 750 mV has to be amplified to a p-p amplitude of 3.8 V, with a rise time of 4.5 μ sec or less. Can IC 741 op-amp be used

The IC 741 has a slew rate of 0.5V/ μ sec
According to definition,

$$S = \frac{\Delta V}{\Delta t}$$

Now rise time is the time required by the o/p to rise from 10% to 90% of its final value.

$$\Delta V = (0.9 - 0.1) \times 3.8 = 3.04 \text{ V}$$

This happens in 4.5 μ sec i.e.
 $\Delta t = 4.5 \text{ } \mu$ sec.

$$S = \frac{3.04}{4.5} = 0.675 \text{ V}/\mu\text{sec}$$

The slew rate of IC 741 is 0.5V/ μ sec which is too low compared to what is required

The i/p signal V_i to an op-amp is $\sin 1.13 \times 10^5 t$ is to be amplified to the maximum extent. How much maximum gain can be had by using op-amp with slew rate of $0.4 \text{ V}/\mu\text{sec}$.

- ④ The common mode i/p to a certain diff. A. having differential gain of 125 is $4 \sin 200\pi t$. Determine the common mode o/p if CMRR is 60dB.

$$60 = 20 \log \left| \frac{A_d}{A_c} \right| \Rightarrow \frac{A_d}{A_c} = 1000$$

$$A_d = 125.$$

$$A_c = 0.125.$$

The common mode o/p is

$$V_{ocm} = A_c V_{cm}$$

$$= 0.125 \times 4 \sin 200\pi t$$

$$V_{ocm} = 0.5 \sin 200\pi t \text{ V.}$$

- ⑤ For an op-amp having a slew rate of $3 \text{ V}/\mu\text{sec}$ what is the max closed loop voltage gain that can be used when the i/p signal varies by 0.4 V in $12 \mu\text{sec}$.

$$V_o = A V_i$$

$$\frac{dV_o}{dt} = A \cdot \frac{dV_i}{dt}$$

$$S = A \cdot \frac{dV_i}{dt}$$

$$A = \frac{S}{\frac{dV_i}{dt}}$$

$$= \frac{S}{\frac{0.4}{12 \times 10^{-6}}} = \frac{3 \times 10^6}{0.4}$$

$$= \frac{36}{0.4} = \frac{36 \times 10}{4} = \frac{360}{4} = 90$$

- ⑦ The 741 IC is used as an inverting op. with a gain of 50. The sinusoidal o/p signal has a variable freq and maximum amplitude of 20mV peak. What is the maximum freq of the o/p at which the o/p will be undistorted. Assume that the amplitude is initially nulled.
- The Slewrate of 741 IC is $0.5 \text{ V}/\mu\text{s}$.

$$S = 2\pi f_m V_m.$$

$$V_m = 20 \text{ mV (o/p)}$$

$$\text{gain} = 50.$$

$$\text{Gain} = \frac{V_m(\text{o/p})}{V_m(\text{i/p})} = 50$$

$$V_m(\text{o/p}) = 50 \times 20 \times 10^{-3} = 1 \text{ V}.$$

$$0.5 \times 10^{-6} = 2\pi f_m \times 1.$$

$$f_m = \underline{\underline{79.577 \text{ kHz}}}$$

- ⑧ How fast can the o/p of an op-amp change by 10V if its Slewrate is $1 \text{ V}/\mu\text{s}$.