


Johnson counter

The **Johnson counter** is similar to the **Ring counter**. The only difference between the **Johnson counter** and the **ring counter** is that the outcome of the last flip flop is passed to the first flip flop as an input. But in **Johnson counter**, the inverted outcome Q' of the last flip flop is passed as an input. The remaining work of the **Johnson counter** is the same as a **ring counter**. The **Johnson counter** is also referred to as the **Creeping counter**.

In Johnson counter

- No. of states in Johnson counter = No. of flip-flop used(n)
- Number of used states = $2n$

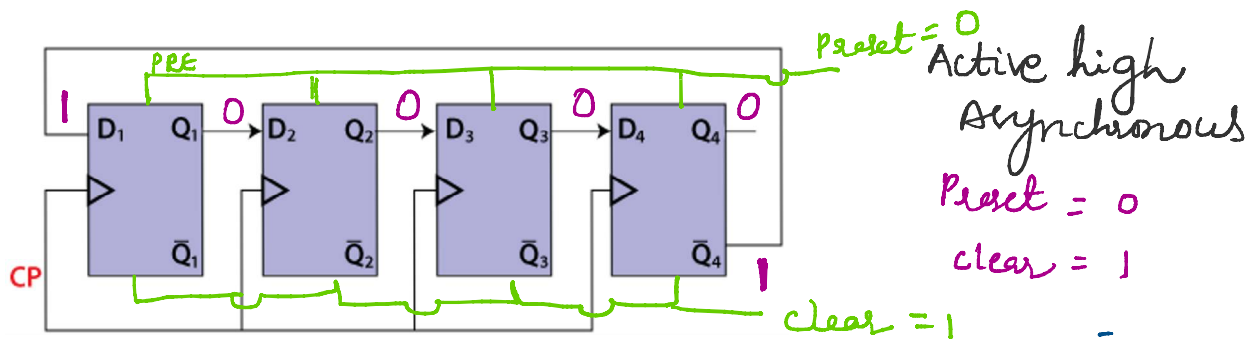
Below is the diagram of the 4-bit Johnson counter. Like Ring counter, four D flip flops are used in the 4-bit Johnson counter, and the same clock pulse is passed to all the input of the flip flops.



$D_1 = \overline{Q_4}$	clock	Q_1	Q_2	Q_3	Q_4
1	No clock	0	0	0	0

→ Asynchronous i/p

First Clock pulse

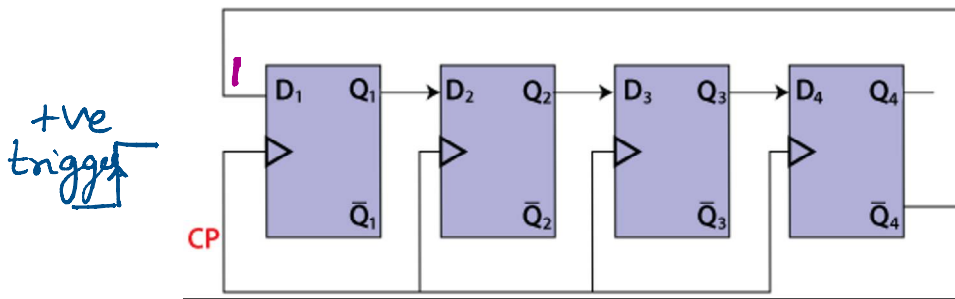

$$D_1 = \overline{Q_4} = 1 \rightarrow Q_1 = 1$$


$$D_2 = Q_1 = 0 \rightarrow Q_2 = 0$$

$$D_3 = Q_2 = 0 \rightarrow Q_3 = 0$$

$$D_4 = Q_3 = 0 \rightarrow Q_4 = 0$$


clock	D1 = $\overline{Q_4}$	Q1	Q2	Q3	Q4
No clock	1	0	0	0	0
1st	1	1	0	0	0

Second Clock pulse

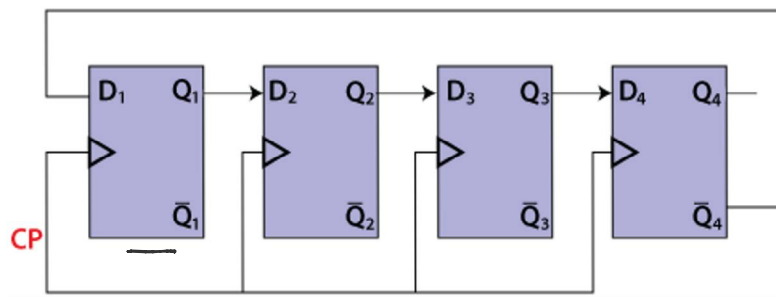


clock	D1 = $\overline{Q_4}$	Q1	Q2	Q3	Q4
1st	1	1	0	0	0
2nd	1	1	1	0	0

Third Clock pulse

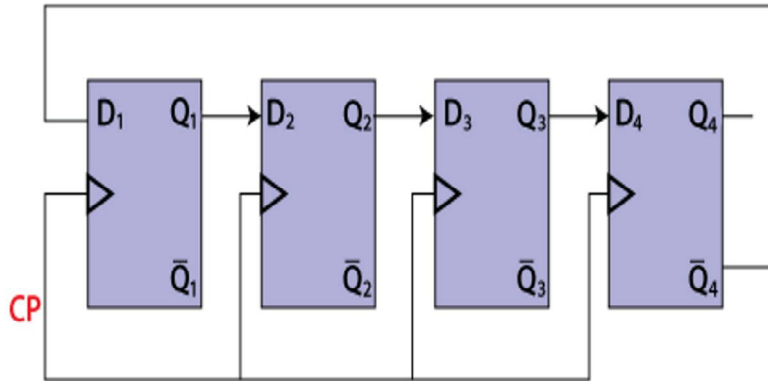


clock	D1 = $\overline{Q_4}$	Q1	Q2	Q3	Q4
2nd		1	1	0	0
3rd					0

Fourth Clock pulse

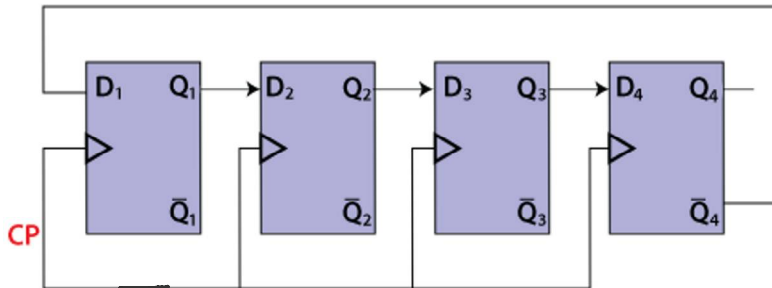

clock	D1 = $\overline{Q_4}$	Q1	Q2	Q3	Q4
3rd	1	1	1	1	0
4th	0	1	1	1	1


Fifth Clock pulse

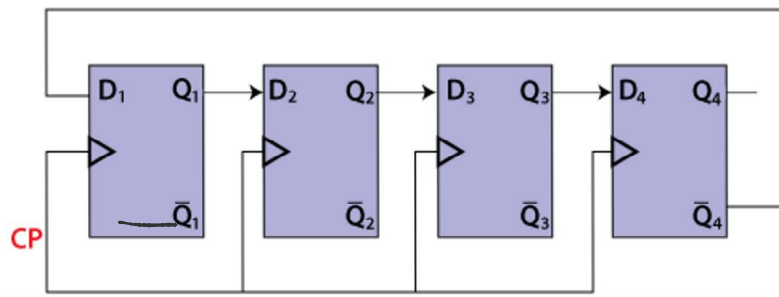

clock	D1 = $\overline{Q_4}$	Q1	Q2	Q3	Q4
4 th	0	1	1	1	1
5 th	0	0	1	1	1

$\overline{Q_4}$


Sixth Clock pulse

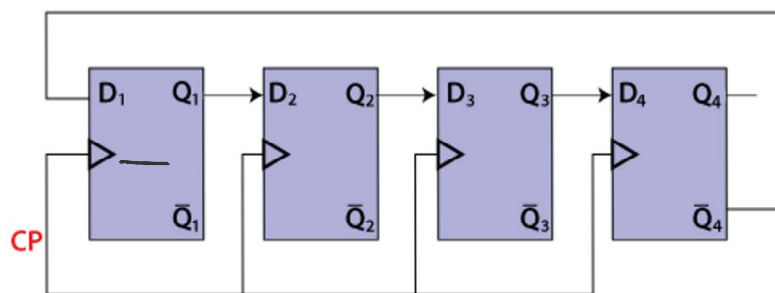

clock	D1 = $\overline{Q_4}$	Q1	Q2	Q3	Q4
5 th	0	0	1	1	1
6 th	0	0	0	1	1


$\overline{Q_4}$

Seventh Clock pulse

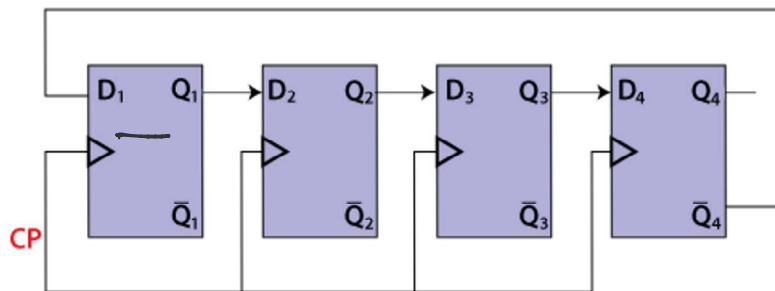

clock	D1 = $\overline{Q_4}$	Q1	Q2	Q3	Q4	$\overline{Q_4}$
6 th	0	0	0	1	1	
7 th	0	0	0	0	1	0

Eighth Clock pulse

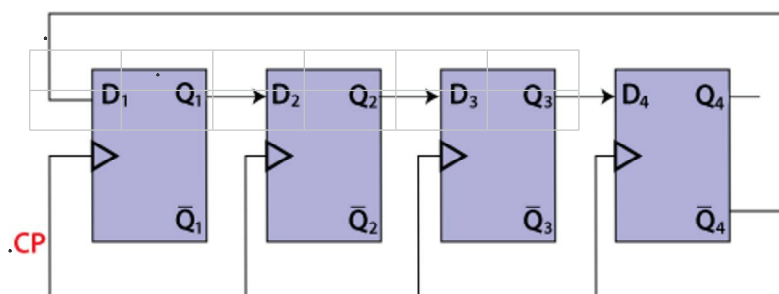


clock	D1 = $\overline{Q_4}$	Q1	Q2	Q3	Q4	$\overline{Q_4}$
7 th	0	0	0	0	1	
8 th	1	0	0	0	0	1

$D_1 = \overline{Q_4}$

No. of Clock pulses	clock	Q1	Q2	Q3	Q4
No clock		0	0	0	0
1	$\overline{\uparrow}$	1	0	0	0
2	$\overline{\uparrow}$	1	1	0	0
3	$\overline{\uparrow}$	1	1	1	0
4	$\overline{\uparrow}$	1	1	1	1
5 th	$\overline{\uparrow}$	0	1	1	1
6 th	$\overline{\uparrow}$	0	0	1	1
7 th	$\overline{\uparrow}$	0	0	0	1
8 th	$\overline{\uparrow}$	0	0	0	0
9 th	\uparrow	1	0	0	0
10 th	$\overline{\uparrow}$	1	1	0	0
11 th	\uparrow	1	1	1	0

$\overline{Q_4} = 1$
 $Q_4 = 1$
 $\overline{Q_4} = 1$

John
 2^n
 8 states
 n flip flop

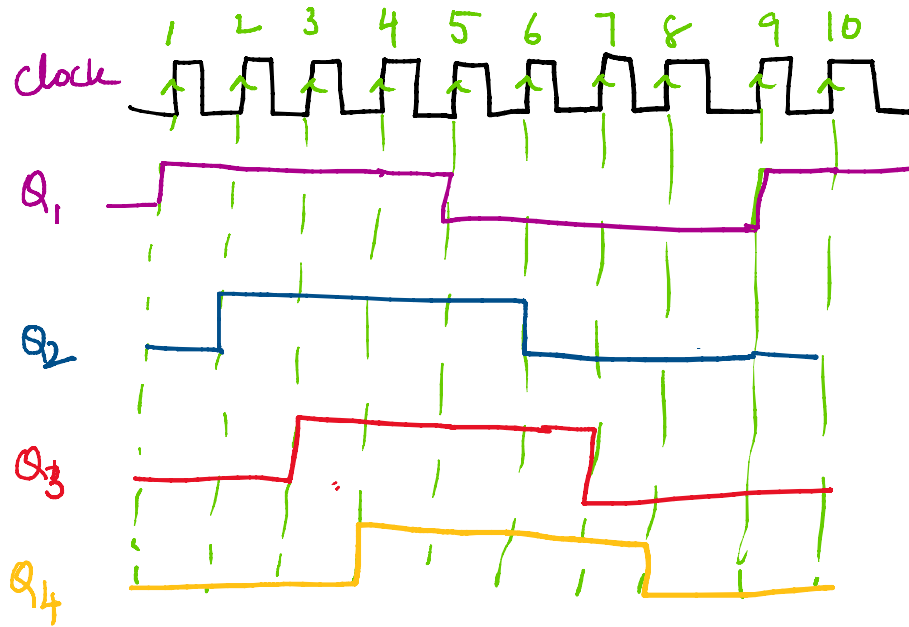

The above table state that

- The counter produces the output 0000 when there is no clock input passed(0).
- The counter produces the output 1000 when the 1st clock pulse is passed to the flip flops.
- The counter produces the output 1100 when the 2nd clock pulse is passed to the flip flops.
- The counter produces the output 1110 when the 3rd clock pulse is passed to the flip flops.
- The counter produces the output 1111 when the 4th clock pulse is passed to the flip flops.
- The counter produces the output 0111 when the 5th clock pulse is passed to the flip flops.
- The counter produces the output 0011 when the 6th clock pulse is passed to the flip flops.
- The counter produces the output 0001 when the 7th clock pulse is passed to the flip flops.

Timing diagram

