


Timing Considerations


Timing Issues

- For correct operation of a synchronous sequential circuit, several timing issues need to be considered.
 - Some of these issues relate to the properties of flip-flops.
 - Some of these issues relate to circuits external to the flip-flops.
- All these taken together determines the maximum speed with which the circuit can operate.
 - Typically specified in terms of the clock frequency.

Some Definitions



- Clock width (t_w):** Minimum time duration for which the clock signal needs to be high in order that the flip-flops it feeds work properly.
- Setup time (t_{setup}):** Amount of time the input to a flip-flop must be stable *before* the clock transitions high (for positive-edge triggered), or transitions low (for negative-edge triggered).
- Hold time (t_{hold}):** Amount of time the input to a flip-flop must be stable *after* the clock transitions high (for positive-edge triggered), or transitions low (for negative-edge triggered).
- Propagation delays (t_{p-lh} and t_{p-hl}):** Delay between clocking event (low-to-high or high-to-low transition) and change in the output.

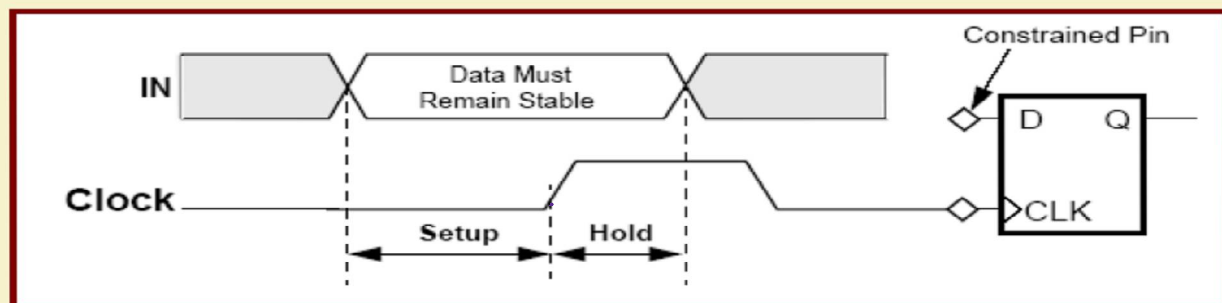

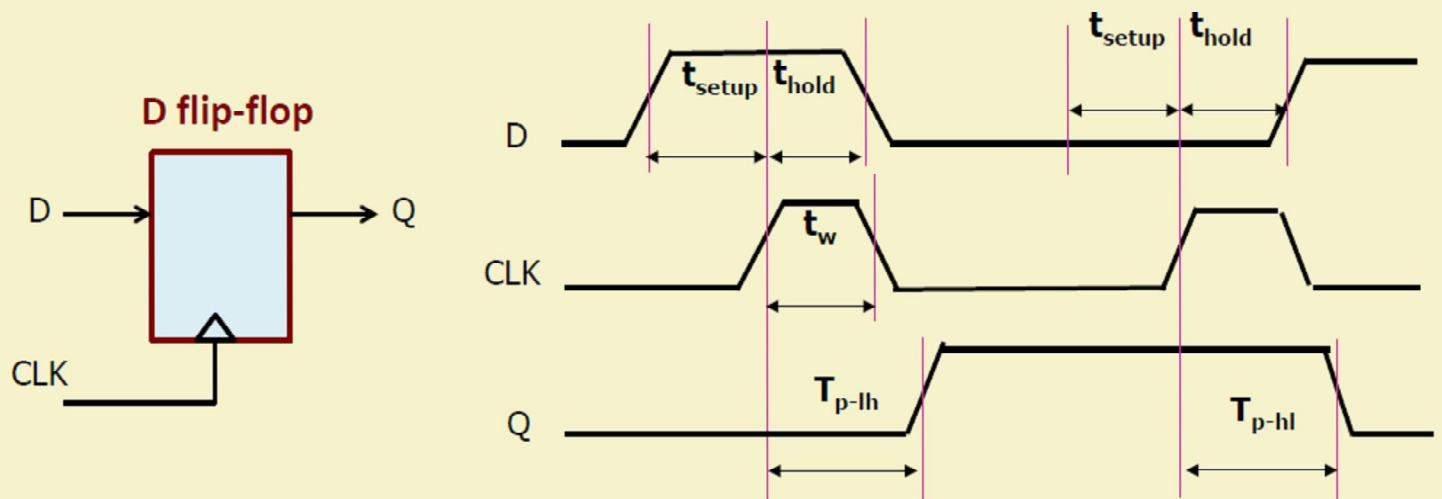

Cascading Flip-flops

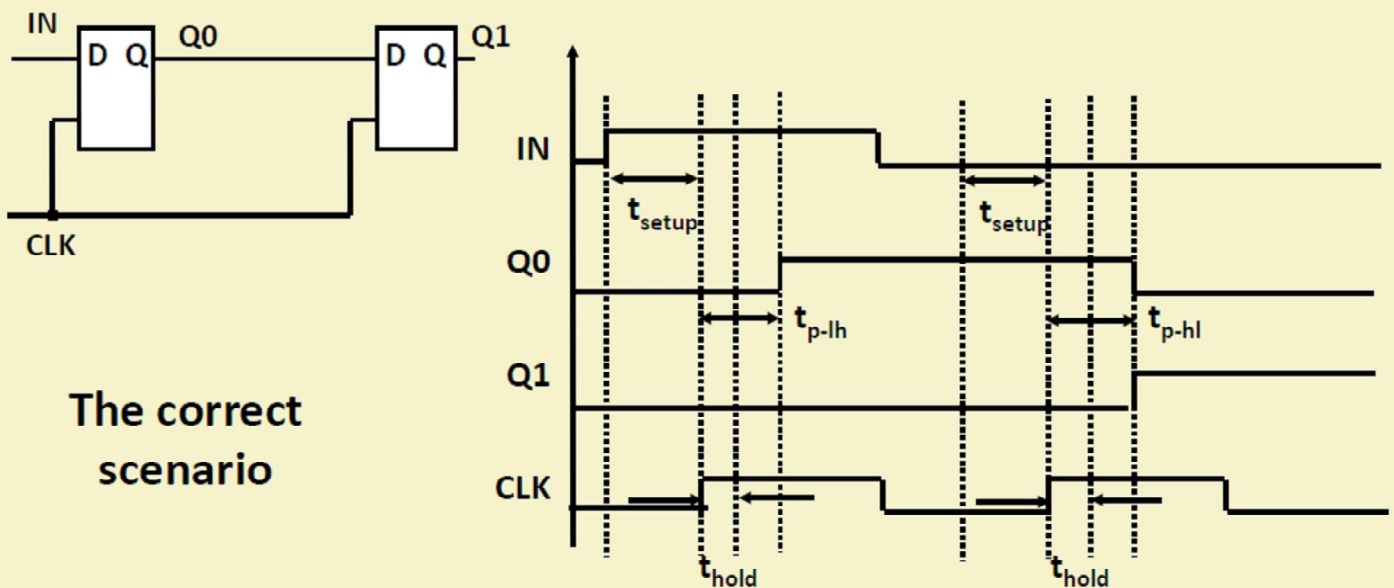 - Suppose that the flip-flop propagation delay exceeds the hold time.
- Second stage can commit its input before Q0 changes.



Edge-triggered Clocking

- Edge-triggered operation (either positive or negative edge triggered)
 - Data leaving at time t must arrive at the next flip-flop *one setup time before* $t+T$, where T is the clock period.
- Clocking relationships are relatively simple:
 - Delay from each input flip-flop to each output flip-flop of a combinational block should be less than $(T - t_{setup})$.
- Ideally, the clock signal should arrive *all* flip-flops at *exactly* the same time.
 - In practice, clock skew exists.

Example 1

- Given a clock signal of frequency f Hz, how to generate another clock of frequency $f/2$ Hz.
 - Frequency division.

Example 2

- Given a clock signal of frequency f Hz, how to generate another clock of frequency $f/2^k$ Hz, for some integer k .
 - Frequency division by some power of 2.