

⇒ Number Systems

1. Binary - base = 2

2. Decimal - 10
- 8

3. Octal

4. Hexa Decimal - 16

0 - 0 - 0000

1 - 2^0 - 0001

2 - 2^1 - 0010

3 - $2^1 2^0$ - 0011

4 - 2^2 - 0100

5 - $2^2 2^0$ - 0101

6 - $2^2 2^1$ - 0110

7 - $2^2 2^1 2^0$ - 0111

8 - 2^3 - 1000

9 - 1001

10 - 1010

11 - 1011

12 - 1100

13 - 1101

14 - 1110

15 - 1111

16 - 10000

17 - 10001

18 - 10010

19 - 10011

20 - 10100 (11100)

21 - 10101 (11101)

22 - 10110 (11100)

23 - 10111 (11101)

24 - 11000 (11100)

25 - 11001 (11101)

26 - 11010 (11100)

27 - 11011 (11101)

28 - 11100 (11100)

29 - 11101 (11101)

30 - 11110 (11100)

31 - 11111 (11101)

1. Binary to decimal conversion

$$(010111.1)_2 = (?)_{10}$$

$$1 \times 2^0 + 1 \times 2^1 + 1 \times 2^2 + 0 \times 2^3 + 0 \times 2^4 + 1 \times 2^5.$$

$$1 + 2 + 4 + 16 = 23$$

(MSB) $(10101)_2 = (?)_{10}$ least significant bit (LSB)

Most Significant bit $1 + 2^2 + 2^4 = 16 + 4 + 1 = 21$

$$(10100)_2 \Rightarrow 2^2 + 2^4 = 16 + 4 = 20$$

$$(10101.1011)_2 = (?)_{10}$$

After binary decimal

$$1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} + 1 \times 2^{-4} = \frac{1}{2} + 0 + \frac{1}{8} + \frac{1}{16}$$

$$1 + 2^{-2} + 2^{-4} = 16 + 4 + 1 = 21 \\ = 21.51875$$

2. Decimal to Binary

$$\begin{array}{r} 2 | 25 \\ 2 | 12 \\ 2 | 6 \\ 2 | 3 \\ 2 | 1 \\ 0 \end{array} \quad (25)_{10} = (?)_2 = 11001$$

$$(25.65)_{10} = (?)_2$$

After the decimal point

$$\left\{ \begin{array}{l} 0.65 \times 2 = 1.3 \\ 0.3 \times 2 = 0.6 \\ 0.6 \times 2 = 1.2 \\ 0.2 \times 2 = 0.4 \\ 0.4 \times 2 = 0.8 \\ 0.8 \times 2 = 1.6 \end{array} \right. \quad \begin{array}{l} 1 \\ 0 \\ 1 \\ 0 \\ 0 \\ 1 \end{array}$$

Number left to the decimal

$$11001.101001...$$

$$11001 \dots$$

$$11001 \dots$$

$$11001 \dots$$

$$(25 \cdot 25)_{10} = (?)_2$$

$$\begin{array}{r} 0.25 \times 2 = 0.5 \\ 0.5 \times 2 = 1 \end{array}$$

↓ ↓

11001.11

$$0.125$$

$$\begin{array}{r} 0.125 \times 2 = 0.25 \\ 0.25 \times 2 = 0.5 \\ 0.5 \times 2 = 1 \end{array}$$

↓ ↓ ↓

0.001

3. Octal to Decimal

$$(2516)_8 = (?)_{10}$$

$$6 \times 8^0 + 1 \times 8^1 + 5 \times 8^2 + 2 \times 8^3$$

$$6 + 8 + 320 + 1024 = 1358$$

$$\rightarrow (124)_8 = (?)_{10}$$

$$4 \times 8^0 + 2 \times 8^1 + 1 \times 8^2$$

$$64 + 16 + 4 = 84$$

$$\rightarrow (124.241)_8 = (?)_{10}$$

↓
84

$$2 \times 8^{-1} + 4 \times 8^{-2} + 1 \times 8^{-3}$$

$$0.25 + 0.0625 + 0.00195\ldots$$

$$84.31445$$

4. Decimal to Octal

$$\rightarrow (55)_{10} = (?)_8$$

$$\begin{array}{r} 8 \overline{)55} \quad 7 \\ 8 \overline{)6} \quad 6 \end{array} = (67)_8$$

$$\rightarrow (255)_{10} = (?)_8$$

$$\begin{array}{r} 8 \overline{)255} \quad 7 \\ 8 \overline{)31} \quad 7 \\ 8 \overline{)3} \quad 3 \\ 0 \end{array} = (377)_8$$

$$(55.8)_{10} = (?)_8$$

$$0.8 \times 8 = 6.4 - 6$$

$$0.4 \times 8 = 3.2 - 3$$

$$0.2 \times 8 = 1.6 - 1$$

$$0.6 \times 8 = 4.8 - 4$$

$$0.2 \times 8 = 1.6 - 1$$

$$0.25)_{10}$$

$$0.25 \times 8 = 2.$$

5. Hexadecimal to Decimal

0-9, A, B, C, D, E, F

$$\rightarrow (27CD)_{16} = (?)_{10}$$

$$D \times 16^0 + C \times 16^1 + 7 \times 16^2 + 2 \times 16^3$$

$$13 + 192 + 1792 + 8192 = 10189$$

$$\rightarrow (45269)_{16} = (?)_{10}$$

$$9 \times 16^0 + 6 \times 16^1 + 2 \times 16^2 + 5 \times 16^3 + 4 \times 16^4$$

$$9 + 96 + 512 + 20480 + 486432$$

$$\rightarrow (27C.4A6)_{16} = (?)_{10}$$

$$C \times 16^0 + 7 \times 16^1 + 2 \times 16^2 + 4 \times \frac{1}{16} + 10 \times \frac{1}{16^2} + 6 \times \frac{1}{16^3}$$

$$192 + 112 + 512 + 0.25 + 0.0310 + 0.001464$$

$$\rightarrow (0.2456)_{16} = (?)_{10}$$

$$2 \times \frac{1}{16} + 4 \times \frac{1}{16^2} + 5 \times \frac{1}{16^3} + 6 \times \frac{1}{16^4}$$

$$0.125 + 0.0156 + 0.00122 + 0.00009155$$

6. Decimal to Hexadecimal

$$\rightarrow (55)_{10} = (?)_{16} \rightarrow (255)_{10} = (?)_{16}$$

$$16 \overbrace{55}^3 \rightarrow (37)_{16} \quad 16 \overbrace{255 \text{ } 15}^{15} \rightarrow (FF)_{16}$$

$$\rightarrow (165)_{10} = (?)_{16}$$

$$16 \overbrace{165 \text{ } 5}^{10} \rightarrow (A5)_{16}$$

$$\rightarrow (165.125)_{10} = (?)_{16}$$

$$0.125 \times 16 = 2$$

$$(A5.2)_{16}$$

$$\rightarrow (0.65)_{10} = (?)_{16}$$

$$0.65 \times 16 = 10.4$$

$$0.4 \times 16 = 6.4$$

$$0.4 \times 16 = 6.4$$

$$= (0.A66)_{16}$$

7. Binary to Hexadecimal

$$\rightarrow 1010101101001$$

$$0001|0101|0011|01001$$

$$\rightarrow 0101|101|0110|1001 = 5D6B$$

$$\rightarrow 1010110.1101101$$

$$0101|0110.110|1010 = 56DA$$

Reverse process for Hexadecimal to Binary

$$\begin{array}{r} 1111111 \\ 11110\text{ (skip)} \leftarrow 001001 \leftarrow \\ \hline 000001 \end{array}$$

8. Binary to Octal

$$\rightarrow 10|101|101|101 = (555)_8$$

$$\rightarrow 001|111|011|001|001 = (17311)_8$$

$$\rightarrow 01|010|110 \cdot 110|110|100 = (126.664)_8$$

← Binary
Hexadecimal to Octal
Binary →

Complements

1's complement:

Interchange zeros and ones

$$011010 \rightarrow 100101$$

2's complement = 1's complement + 1

$$\rightarrow 011010 \rightarrow 2^S \rightarrow 100101 \text{ in arithmetic addition}$$
$$\begin{array}{r} & 1 \\ & + 1 \\ \hline 100101 \end{array}$$

1+1=0 with carry 1

$$\rightarrow 1001 \rightarrow 0110$$

$$\begin{array}{r} + 1 \\ \hline 0111 \end{array}$$

$$\rightarrow 00000001 \rightarrow \underline{\underline{000}}$$
$$\begin{array}{r} 1111110 \\ + 1 \\ \hline 1111111 \end{array}$$

$$\rightarrow 100000 \rightarrow \underline{\underline{000}}.011111$$
$$\begin{array}{r} + 1 \\ \hline 100000 \end{array}$$

$\rightarrow 01011010$

For any number, to find the 2's complement
scan the bits from Right side until the 1 comes
and complement the remaining

$$01011010 \rightarrow 10100110$$

$$\rightarrow 100101 \rightarrow 011011$$

$$\begin{array}{r} \text{1's complement} \\ +5 = 101 \\ +3 = 011 \\ \hline 1000 = 8 \end{array}$$

$$\begin{array}{r} \text{1's complement} \\ +16 = 10000 \\ +17 = 10001 \\ \hline 100001 = 33 \end{array}$$

$$\begin{array}{r} \text{1's complement} \\ +16 = 10000 \\ +14 = 01110 \\ \hline 11110 = 30 \end{array}$$

$$\begin{array}{r} \text{1's complement} \\ -5 = 101 \\ -3 = 011 \\ \hline 010 \end{array} \quad \begin{array}{l} \text{In arithmetic subtraction} \\ \text{carry is 2} \end{array}$$

1's complement addition

$$\begin{array}{r} 101 \\ +100 \text{ (1's complement of 3)} \\ \hline 001 \\ \text{carry} \\ \text{should} \\ \text{be added} \end{array}$$

$$\begin{array}{r} \text{1's complement} \\ -7 = 111 \\ -2 = 010 \\ \hline 100 \end{array}$$

$$1+1+1=1 \text{ with carry 1}$$

$$\begin{array}{r} 25 = 1101 \\ -17 = 10001 \\ \hline 01101 \end{array}$$

$$\begin{array}{r} 11001 \\ 01110 \\ \hline 01101 \end{array}$$

$$\begin{array}{r} 1 \\ 1000 \\ \hline 1000 = 8 \end{array}$$

$$\begin{array}{r}
 3 \quad 011 \quad 011 \\
 -5 \quad \underline{101} \quad 010 \\
 \hline
 & 101 \\
 & 010 \\
 & \underline{-2}
 \end{array}$$

If there is no carry then its result is negative and it is in its 1's complement form

$$\begin{array}{r}
 2 \quad 010 \quad 010 \\
 -7 \quad 111 \quad \underline{000} \\
 \hline
 & 010
 \end{array}$$

NO carry complement \Rightarrow 101

$$\begin{array}{r}
 17 \quad 10001 \quad 10001 \\
 -25 \quad 11001 \quad \underline{00110} \\
 \hline
 & 10111
 \end{array}$$

\Rightarrow 01000
= -8

2's complement addition

$$\begin{array}{r}
 5 \quad 101 \quad 101 \\
 -3 \quad 011 \quad \underline{100} \quad (2\text{'s complement}) \\
 \hline
 & 010 = 2
 \end{array}$$

→ carry should be neglected in

2's complement addition

$$\begin{array}{r}
 7 \quad 111 \quad 111 \\
 -2 \quad 010 \quad \underline{0110} \\
 \hline
 & 101 = 5
 \end{array}$$

$$\begin{array}{r}
 25 \quad 11001 \quad 11001 \\
 -17 \quad 10001 \quad \underline{01111} \\
 \hline
 & 01000 = 8
 \end{array}$$

$$\begin{array}{r}
 3 \quad 011 \quad 011 \\
 -5 \quad 101 \quad \underline{011} \\
 \hline
 & 110
 \end{array}$$

If there is no carry then Result is in negative and in its 2's complement form

$$\begin{array}{r}
 2 \quad 0 \mid 0 \quad 0 \mid 0 \\
 -7 \quad 1 \mid 1 \mid 0 \quad 0 \mid 0 \mid 1 \\
 \hline
 0 \mid 1 \rightarrow 101 = 5 \text{ No carry} \Rightarrow -5
 \end{array}$$

$$\begin{array}{r}
 17 \quad 1 \mid 0 \mid 0 \mid 0 \mid 1 \quad 1 \mid 0 \mid 0 \mid 0 \\
 -25 \quad 1 \mid 1 \mid 0 \mid 0 \mid 1 \quad 0 \mid 0 \mid 1 \mid 1 \mid 1 \\
 \hline
 \text{borrowed } 1 \quad 1 \mid 0 \mid 0 \mid 0 \mid 0 \quad = -8
 \end{array}$$

$$\begin{array}{r}
 80 \quad 1 \mid 0 \mid 1 \mid 0 \mid 0 \mid 0 \quad 1 \mid 0 \mid 1 \mid 0 \mid 0 \mid 0 \\
 -70 \quad 1 \mid 0 \mid 0 \mid 0 \mid 1 \mid 0 \quad 0 \mid 1 \mid 1 \mid 1 \mid 0 \mid 0 \\
 \hline
 \text{borrowed } 1 \quad 0 \mid 0 \mid 0 \mid 1 \mid 0 \mid 0 \quad \Rightarrow \\
 \text{Neglected } 1 \quad 80 - 80 = 0 \Rightarrow 10
 \end{array}$$

$$\begin{array}{r}
 70 \quad 1 \mid 0 \mid 0 \mid 0 \mid 1 \mid 0 \quad 1 \mid 0 \mid 0 \mid 1 \mid 1 \mid 0 \\
 -80 \quad 1 \mid 0 \mid 1 \mid 0 \mid 0 \mid 0 \quad 0 \mid 1 \mid 1 \mid 0 \mid 0 \mid 0 \\
 \hline
 \text{borrowed } 1 \quad 1 \mid 1 \mid 0 \mid 1 \mid 1 \mid 0 \quad \Rightarrow \\
 0 \mid 0 \mid 0 \mid 1 \mid 0 \mid 0 \quad 32 + 8 = -10
 \end{array}$$

$$\begin{array}{r}
 126 \quad 1 \mid 1 \mid 1 \mid 1 \mid 1 \mid 0 \quad 1 \mid 1 \mid 1 \mid 1 \mid 1 \mid 0 \\
 -86 \quad 0 \mid 0 \mid 1 \mid 0 \mid 1 \mid 0 \quad 0 \mid 1 \mid 0 \mid 1 \mid 0 \mid 0 \\
 \hline
 \text{borrowed } 1 \quad 0 \mid 1 \mid 0 \mid 0 \mid 0 \quad \Rightarrow \\
 32 + 8 = 40
 \end{array}$$

$$\begin{array}{r}
 86 \quad 1 \mid 0 \mid 1 \mid 0 \mid 1 \mid 0 \quad 1 \mid 0 \mid 1 \mid 0 \mid 1 \mid 0 \\
 -126 \quad 1 \mid 1 \mid 1 \mid 1 \mid 1 \mid 0 \quad 0 \mid 0 \mid 0 \mid 0 \mid 1 \mid 0 \\
 \hline
 \text{borrowed } 1 \quad 1 \mid 0 \mid 1 \mid 0 \mid 0 \mid 0 \quad \Rightarrow \\
 (64 + 16 + 8) \quad 32 + 8 = 40 \\
 -40 \text{ (No carry)}
 \end{array}$$

Representation of Negative numbers

$$+14 = 0 \cdot 0001110 \quad (8\text{ bits})$$

$$-14 = 1 \cdot 0001110 \quad \text{sign magnitude (S.M)}$$

$$-14 = 111.10001 \rightarrow 1's \text{ complement}$$

$$-14 = 11110010 \rightarrow 2's \text{ complement}$$

$$+0 = 0 \cdot 0000000$$

$$-0 = 1 \cdot 0000000 \quad \text{sign magnitude}$$

$$-0 = 11111111 \rightarrow 1's \text{ complement}$$

$$-0 = 00000000 \rightarrow 2's \text{ complement}$$

If the no. of bits $n=8$, only $(n-1)=7$ bits are only assigned and one bit is fixed for sign

$n=8$ +127 to -127 \rightarrow in sign mag. and 1's

-128 to +127 \rightarrow in 2's complement

2's complement is preferred over 1's complement and sign magnitude because of the following reason

In order to represent +0 and -0 in sign magnitude we need two separate representations, whereas in 2's complement only one representation is sufficient to represent +0 and -0, that means we can represent one extra number in 2's complement compared to 1's complement and sign magnitude

$n=4$

-7 to +7 \rightarrow sign magnitude and 1's complement
-8 to +7 \rightarrow 2's complement

For 'n' bits,

- $(2^{n-1} - 1)$ to $+ (2^{n-1} - 1)$ sign magnitude and
1's complement
 -2^{n-1} to $+ (2^n - 1)$ in 2's complement

whenever the MSB is 1, that indicates it is a
negative number

$$1001 = -7 \quad 111001 = -1$$

$$11001 = -7 \quad 1111001 = -1$$

Represent +42 in 2's complement

a) 0 0101010

$$\begin{array}{r} 1010110 \\ \hline 64 \quad 16 \quad 4 \end{array}$$

$$\begin{array}{r} 1001010 \\ \hline 16 \quad 4 \end{array}$$

b) 1 0101011

c) 1 1010110

$$\begin{array}{r} 0101010 \\ \hline 32 \quad 8 \quad 2 \end{array}$$

d) None

$\rightarrow -15$

1 0001111

0 1110001

most significant bit is 1, so it is a negative number

so add 1 to get positive number by subtracting

add 1 to get positive number by subtracting

Weighted and non-weighted codes:

8 4 2 1	2 4 2 1
0 0 0 0 -0	0 0 0 0 -0
0 0 0 1 -1	0 0 0 1 -1
0 0 1 0 -2	0 0 1 0 -2
0 0 1 1 -3	0 0 1 1 -3
0 1 0 0 -4	0 1 0 0 -4
0 1 0 1 -5	0 1 0 1 -5
0 1 1 0 -6	0 1 1 0 -6
0 1 1 1 -7	0 1 1 1 -7
1 0 0 0 -8	1 1 1 0 -8
1 0 0 1 -9	1 1 1 1 -9

6 4 -3 2

0 0 0 0 -0
0 1 1 0 -1
0 0 0 1 -2
1 0 1 0 -3
0 1 0 0 -4
1 0 1 1 -5
1 0 0 0 -6
1 1 1 0 -7
1 0 0 1 -8
1 1 1 1 -9

Self complementary code

9's complement is obtained by subtracting that particular number from 9 or 99 or 999...

based on the number of digits.

$$3 \rightarrow 93 = 6 \quad 25 \rightarrow \underline{99}$$

A code is said to be self complementary code, if 9's complement is obtained, by interchanging 1's and 0's

2421 — self complementary code

64-32 is also a self complementary code

8421 is not a self complementary code

BCD → Binary coded Decimal Number.

If a number is to be represented in BCD form then it should be represented in 4-bit form.

85 89 125
0010 0101 1000 1001 0001 0010 0101

8421 — BCD code

Non-weighted codes

Excess-3 (Gray) → by adding 3 to Binary

Binary	Excess-3
0000	0011
0001	0100
0010	0101
0011	0110
0100	0111

Boolean Algebra

Properties

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

$$1) A \cdot 0 = 0$$

$$2) A \cdot 1 = A$$

$$3) A \cdot A = A$$

$$4) A \cdot \bar{A} = 0$$

$$5) \bar{\bar{A}} = A$$

$$6) A + 0 = A$$

$$7) A + A = A$$

$$8) A + \bar{A} = 1$$

$$9) A + 1 = 1$$

$$10) (A+B)(A+C) = A+BC$$

$$11) (A+\bar{A}B) = (A+\bar{A}) \cdot (A+B)$$

$$\Rightarrow 11. (A+B) = A+B$$

$$12) (\bar{A}+AB) = \bar{A}+B$$

$$13) A+B = B+A$$

$$14) A(B+C) = AB+AC$$

$$1) AB + A(B+C) + B(B+C)$$

$$= AB + AB + AC + B \cdot B + BC$$

$$= AB + B + AC + BC$$

$$= AB + B + BC + AC$$

$$= AB + B(1+C) + AC$$

$$= AB + AC + B$$

$$= (A+1)B + AC$$

$$= B + AC$$

$$2) \bar{A}B + A\bar{B} + AB$$

$$= \bar{A}B + A(\bar{B}+B)$$

$$= (A+B)(\bar{A}+\bar{B})$$

$$= A+B$$

$$\begin{aligned}
 3. & a'bc + ab'c + abc' + abc \\
 & a'bc + ab'c + ab \\
 & (\cancel{c(a'b + ab')} + ab) \\
 & a'bc + ab + ab'c \\
 & (\bar{a}c + a)b + ab'c \\
 & (a+c)b + ab'c \\
 & ab + bc + ab'c \\
 & ab + c(b + ab') \\
 & ab + c(a + b) = ab + ac + bc
 \end{aligned}$$

$$\begin{aligned}
 & a'bc + abc + ab'c + abc' + abc \\
 & bc(\bar{a}' + a) + ac(b' + b) + ab(c' + c)
 \end{aligned}$$

$$\begin{aligned}
 & bc + acab \\
 4. & a + a'b + \underline{a'b'c} + a'b'c'd + a'b'c'd'e + \dots \\
 & \left[a + a'(b + b'c + b'c'd + \dots) \right] \\
 & \left[a + a'(b + b'(c + c'd + c'd'e + \dots)) \right] \\
 & a + a'b + a'b'c + a'b'c'd + a'b'c'd'e + \dots \\
 & a + b + a'b'c + a'b'c'd + a'b'c'd'e + \dots \\
 & a + b + b'c + a'b'c'd + \dots \\
 & a + b + c + a'b'c'd + \dots \\
 & a + b + b'c'd + c + \dots \\
 & a + b + c + c'd + \dots \\
 & a + b + c + d + a'b'c'd'e + \dots \\
 & a + b + c + d + e + \dots
 \end{aligned}$$

$$5. (x+y)(x+y+z) + x'y' + x'z'$$

$$x + xy + x'yz + xy + yz + x'y' + z'z$$

$$x + xy + x'yz + yz + x'y' + z'z$$

$$x(1+y) + yz(1+x) + x'y' + x'z'$$

$$x + yz + x'z' + x'y'$$

$$x + z' + yz + x'y'$$

$$x + y' + z' + y$$

$$x + 1 + z'$$

$$= 1 + z'$$

$$\Rightarrow 1$$

$$6. \underline{a'b'c' + a'b'c + a'bc + ab'c + abc}$$

$$a'b' + c' + a'bc + ab'c + abc$$

$$a'b' + c' + a'bc + ac$$

$$\times \underline{a'b' + c'(1+a'b+a)}$$

$$a'b' + c'$$

$$a'b' + a'bc + ac$$

$a'b' + ac + bc \rightarrow$ Irredundant expression

$$a'b'c' + a'c' + ac$$

$$(or) a'b'c' + c$$

$$c + a'b'$$

Consensus Theorem

$$xy + x'z + yz = xy + x'z$$

Proof: $xy + x'z + yz(x + x')$

$$\underline{xy + x'z + xyz + x'yz}$$

$$xy + x'z$$

$$\Rightarrow \underline{xy + x'z} + \underline{yz} = \underline{xy + x'z}$$

$$\rightarrow xy + x'y' + yz = xy + x'y' + x'z \text{ (prove)}$$

$$xy + yz + x'y' + x'z$$

$$= xy + x'y' + x'z$$

$$\rightarrow xy + x'y'z' + wxz' = xy + y'z'$$

$$xz' + xy + y'z' + wxz' \Rightarrow xy + y'z' + xz' \\ = xy + y'z'$$

$$\rightarrow a'c' + abd + bc'd + ab'd' + abc'd' = a'c' + abd + abd' + ac'd$$

$$(a'c' + abd + c'b'd + b'c'd')$$

$$(a'c' + abd + ab'd + abc'd')$$

$$a'c' + abd + ab'd + abc' + abc$$

$$a'c' + abd + ad'c + abc'd'$$

$$abd + (abc) + tab'd$$

$$a'c' + ad + adc$$

$$a'c' + ad + c'd + adc$$

$$a'c' + ad + c'd + ad'c$$

$$a'c' + ad + c'd + adc$$

$$a'c' + abd + bc'd + ab'd' + abc'd' = a'c' + abd + ab'd' + ac'd$$

$$a'c' + abd + ad'(b' + bc)$$

$$a'c' + abd + ad'(b' + c)$$

$$a'c' + abd + ab'd' + ac'd'$$

$$\rightarrow ab'c + a'b'c' + bc$$

$$ab'c + bc + ac + a'b'c'$$

$$ab'c + bc + ac + a'b'c'$$

$$c(a+b) + ac + a'b'c'$$

$$ac + bc + a'b'c'$$

$$ac + \cancel{bc} + a'b'c' + a'b$$

$$ac + bc + a'b$$

$$ac + a'b$$

$$\rightarrow ab'c + a'b'c' + ab$$

$$\underline{ab'c + ab + a'b'c'} \quad ab'c + b(a'c' + a)$$

$$ab'c + ab + ac + a'b'c' \quad ab'c + bc' + ab$$

$$a(c+b) + ac + a'b'c' \quad a(b + b'c) + bc'$$

$$\underline{ac + ab + a'b'c'} \quad a(b+c) + bc'$$

$$\underline{ab + ac + a'b'c' + a} \quad ab + ac + bc'$$

$$act + bc'$$

$$\rightarrow ab'c + abc + a'c$$

$$a'b'c + \cancel{c}(ab + a')$$

$$a'b'c + c(b + a')$$

$$a'b'c + bc + a'c \quad ab + bc + a'c$$

$$a'b'c + bc$$

$$c(a'b' + b)$$

$$ac + bc$$

$$1. AB'C' + A'B'C' + A'BC' + A'B'C$$

$$B'C'(A+A') + A'BC' + A'B'C$$

$$B'C' + A'BC' + A'B'C$$

$$A'BC' + B'C' + A'C' + A'B'C$$

$$A'C' + B'(C'+A'C)$$

$$A'C' + B'(C'+A')$$

$$A'B' + A'C' + B'C'$$

$$2. ABC + A'BC + AB'C + ABC' + AB'C' + A'BC' + A'B'C'$$

$$BC + AB'C + ABC' + ABC' + A'BC' + A'B'C'$$

$$BC + AB'C + ABC' + A'BC' + B'C'$$

$$BC + AB'C + B'C'$$

$$BC + AB'C + C'$$

$$BC + AB' + C'$$

$$B + AB' + C'$$

$$A + B + C'$$

$$3. AB'C(BD + CDE) + AC'$$

$$AB'CD(B + CE) + AC'$$

$$AB'CD + AC'$$

$$A(B'CDE + C')$$

$$A(B'DE + C')$$

$$AB'DE + CA$$

DeMorgan's Laws

$$\overline{ABC} = \overline{A} + \overline{B} + \overline{C}$$

$$\overline{A+B+C} = \overline{A} \cdot \overline{B} \cdot \overline{C}$$

4. $AB(C+BD')(AB)'$

$$AB(C+BD')(A'+B')$$

$$(ABC+ABD')(A'+B')$$

$$AB(C+D')(A'+B')$$

$$AB(AC+B'C+A'D'+D'B') = 0$$

5. $A'B'C + A'B'C + A'B'C'D'$

$$A'B'C + A'B'C'D'$$

$$A'B'C + A'B'D'$$

$$A'B'(C+D')$$

6. $AB'C + (B'+C')(B'+D') + (A+C+D)'$

$$AB'C + B' + B'D' + C'B' + C'D' + A'C'D'$$

$$AB'C + B' + C'B' + C'D' + A'C'D'$$

$$AB'C + B' + C'B' + C'D'$$

$$B'(AC+I)$$

$$B' + C'B' + C'D'$$

$$B' + C'D'$$

30/7/19

Minterm: A minterm is a product term which contains all the 'n' variables in complemented or uncomplemented form.

In Minterm 0 is represented in ^{td} (SOP) $1 \rightarrow$ uncomplemented form

Sum of products: sum of product terms

Eg: $x'y'z + xyz' + xyz$ Min terms

Maxterm: A max term is a sum term which contains all the 'n' variables either in complemented or uncomplemented form. $0 \rightarrow$ Uncomplemented form $1 \rightarrow$ complemented form

Product of sum (POS): product of sum terms

Eg: $(x+y+z)(x'+y'+z')(x''+y''+z)$ Maxterm

abs. val.	Minterm	Maxterm
0 0 0	$a'b'c'$	$a+b+c$
0 0 1	$a'b'c$	$a+b+c'$
0 1 0	$a'b c'$	$a+b'c$
1 0 0	$a b'c'$	$a'+b+c$
0 1 1	$a'b c$	$a+b'+c$
1 1 0	$a b c'$	$a'+b'+c$
0 0 1	$a b'c'$	$a'+b+c$
1 1 1	$a b c$	$a'+b'+c'$

canonical SOP: Here, each product term should contain all the variables.

$x'y + xz' + yz$ (Not a canonical form)

$$= x'y(z+z') + xz'(y+y') + yz(x+x')$$

$$= x'yz + x'yz' + xy'z' + xy'z + x'yz + x'zy$$

$$= x'yz + x'yz' + xy'z' + xy'z + x'yz$$

canonical form

converting
into
canonical
form

Canonical POS : Each sum term should contain all the variables.

$(x+y)(x+z)(y'+z) \rightarrow$ Not a canonical form

$$(x+y+z-z)(x+y'+yy')(y'+z+xx') \quad \left. \begin{array}{l} \text{converting} \\ \text{into} \\ \text{canonical} \\ \text{form} \end{array} \right\}$$


$$\begin{aligned} A+BC &= (A+B)(A+C) \\ &= (x+y+z)(x+y+z') \\ &\quad + (x+y+z)(x+z'+y') \\ &\quad + (y'+z+x)(y'+z+x') \end{aligned}$$

canonical form


Logic Gates:

Basic gates : AND, OR, NOT

1. NOT (Inverter)

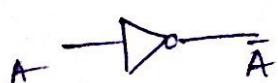


A	Y	\bar{A}
0	1	1
1	0	0

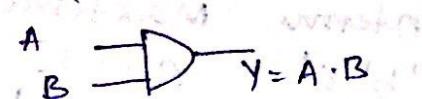

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


3. OR

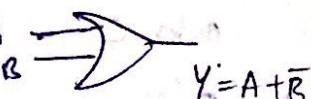

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1


Universal Gates : NAND, NOR

1. NAND

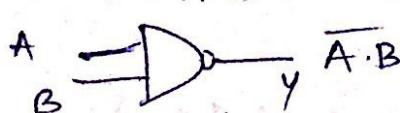

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

2. NOR

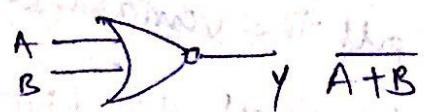

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

When all the inputs in AND gate is high the output is high


when at least one inputs in OR gate is high the output is high

The output of NAND gate is high, when atleast one input is low


The output of NOR gate is high, when all the inputs are low.

→ NAND as universal gate


1) NOT

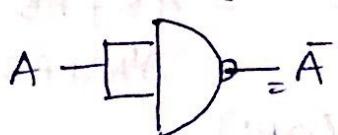


2) AND

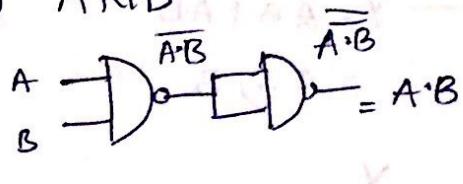

3) OR

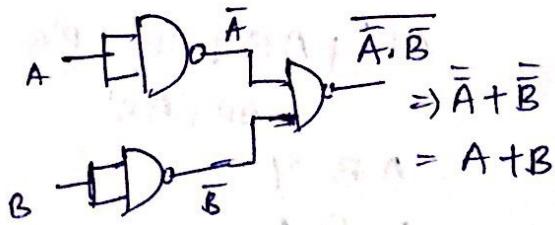


4) NOR

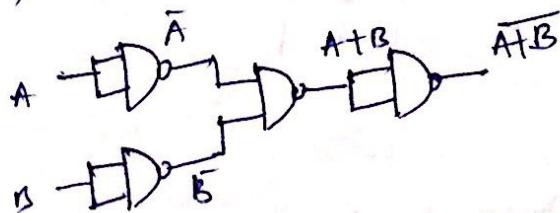



→ NOR as universal gate

1) NOT

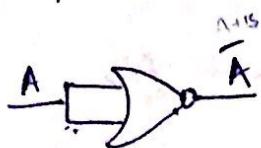


2) AND

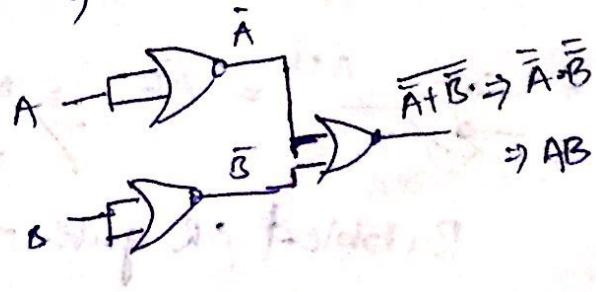

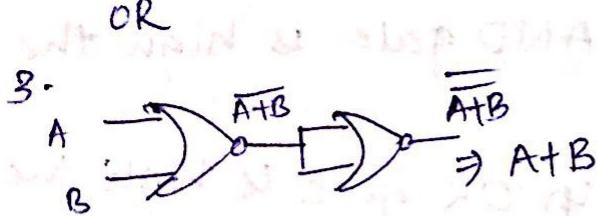

4. NAND

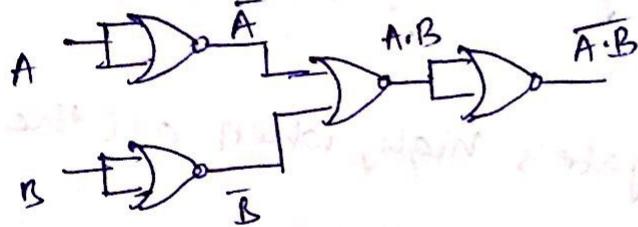

Ex-OR gate

$$Y = \overline{\overline{AB} + A\overline{B}} \\ = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Ex-NOR gate



$$Y = \overline{\overline{A}\overline{B} + A\overline{B}} \\ = \overline{A'B} + AB \\ = A'B' + AB \\ (A'B)'(AB')' \\ (A+B')(A'+B) \\ AA' + AB + A'B' + B'B \\ = AB + A'B'$$

AB Y

0	0	1
0	1	0
1	0	0
1	1	1


NAND-OR \rightarrow NAND-NAND

$$Y = AB + CD$$

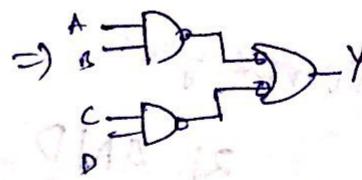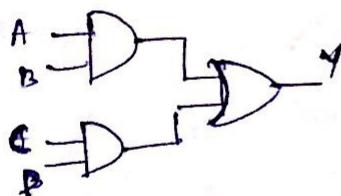

$$\overline{A+B} = \overline{AB} \Rightarrow \overline{A} \Rightarrow \overline{AB}$$



Bubbled OR gate = NAND gate

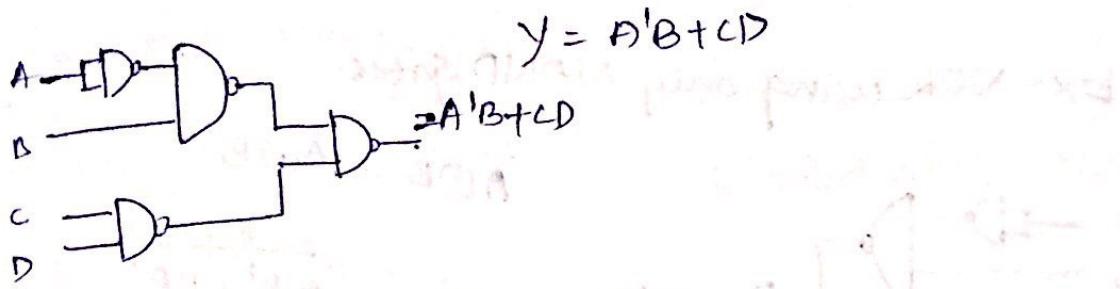



OR-AND \rightarrow NOR-NOR

$$F = (A+B)(C+D)$$

Bubbled
AND gate = NOR gate

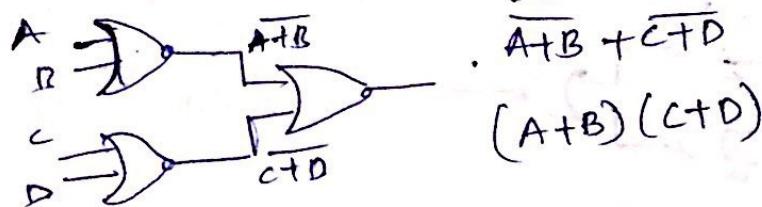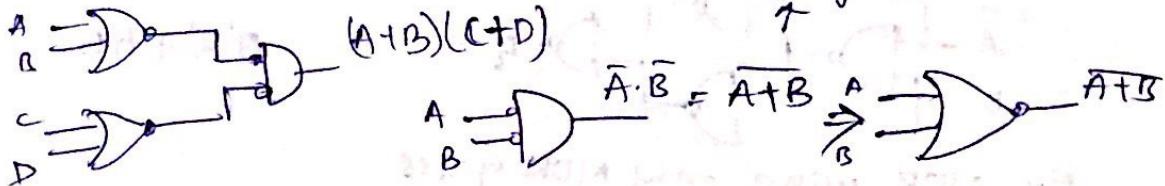

Ex-OR gate using only NAND gate

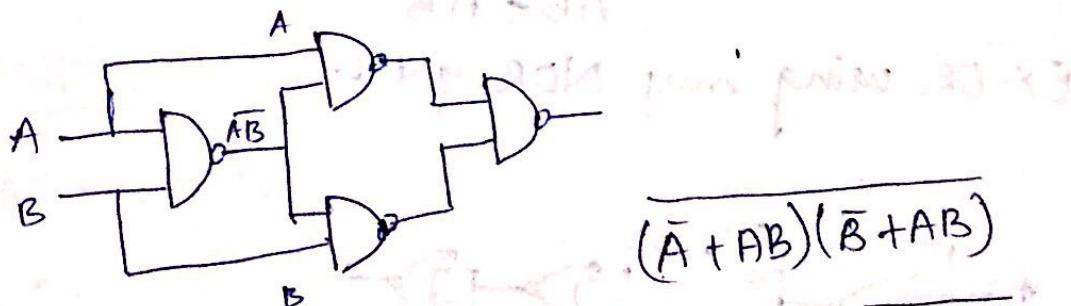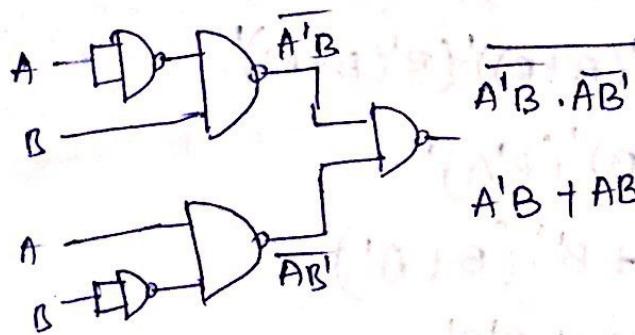


$$\overline{A \cdot \overline{AB}} \Rightarrow \overline{A} + AB$$

$$\overline{\overline{AB} \cdot B} = \overline{B} + AB$$

$$(\overline{A} + AB)' + (\overline{B} + AB)'$$

$$AB' + A'B$$

Ex-NOR using only NAND Gates.

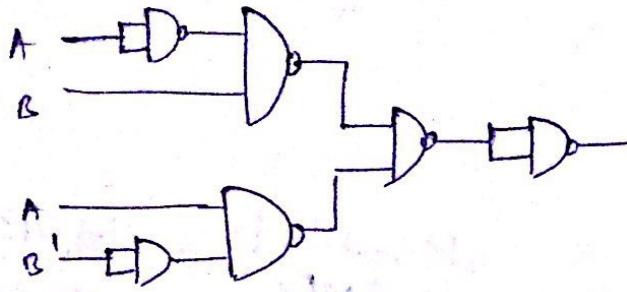


$$\overline{A \oplus B} = A \odot B$$

$$\overline{AB' + BA'}$$


$$(AB)'(BA')'$$

$$(A'B)(B'A)$$

$$A'B' + AB$$

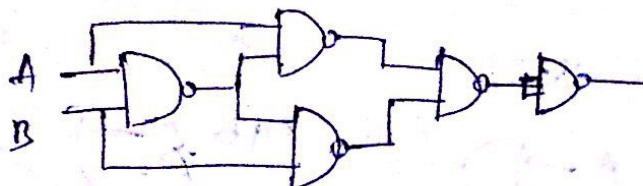

Ex-NOR using only NOR gates

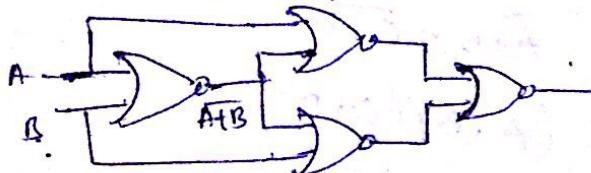

$$\overline{A + \overline{A+B}} \Rightarrow (A') \cdot (\overline{A+B})' = B'(A+B)$$

$$\Rightarrow A'(A+B) + B'(A+B)$$


$$\Rightarrow (A'(A+B))' (B'(A+B))'$$

$$(A'B)' (B'A)'$$

$$(A+B')(B+A')$$


$$AB + A'B'$$

Ex-OR using only NOR gates.

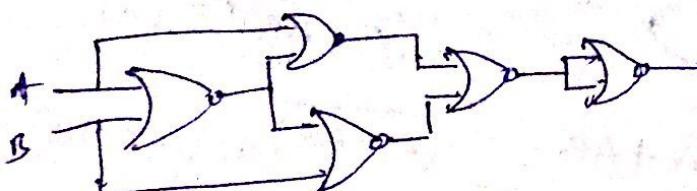


Multilevel NOR/NAND

1) NOR $F = (A + B(C + D))(B + D')$

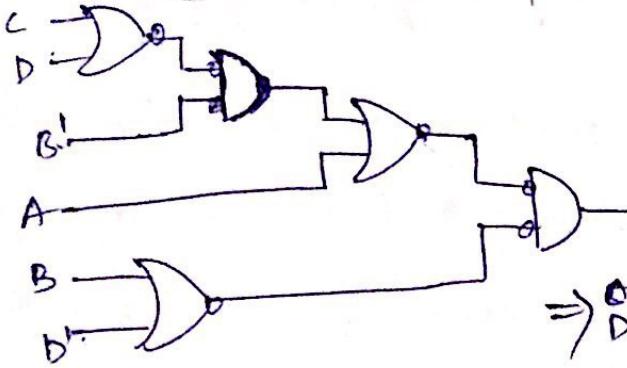


Bubbled AND = NDR

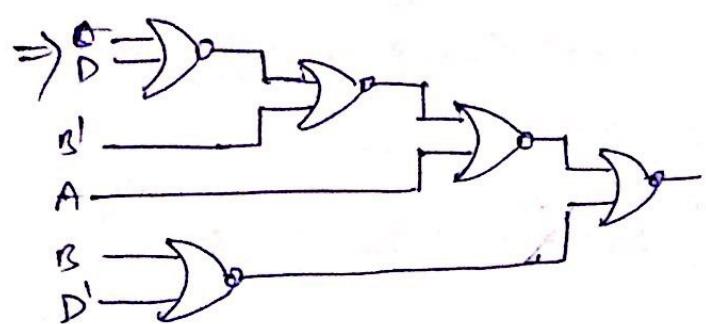

3-level NOR



$$(AB' + CD')(A' + B)$$

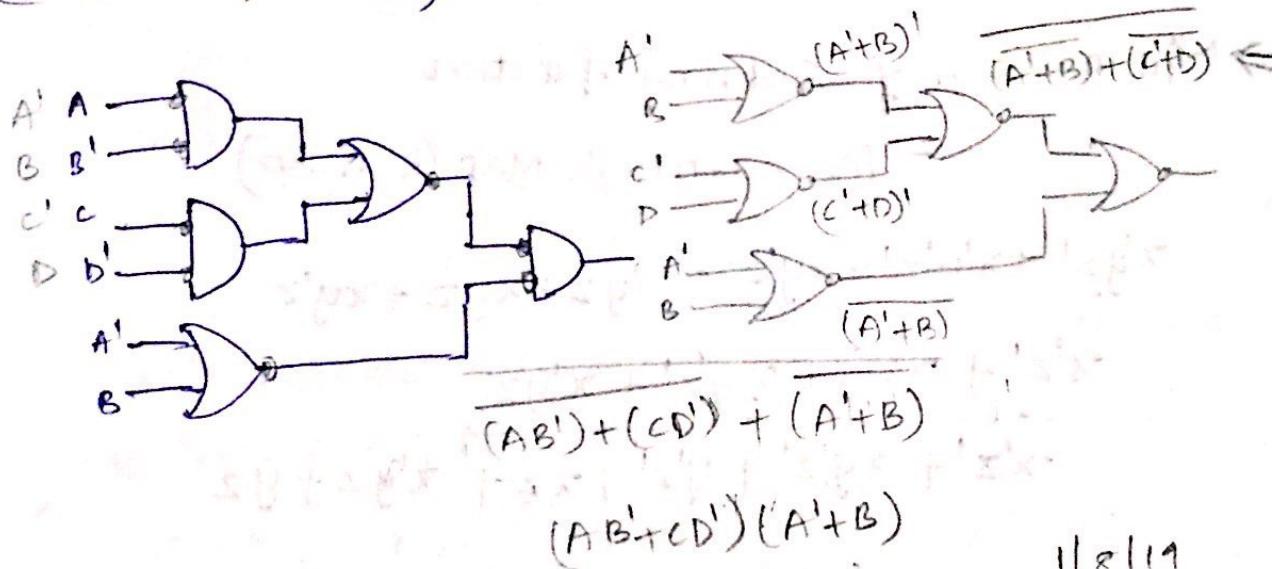

11/8/19

2) NAND


$$A(B + CD) + B'$$

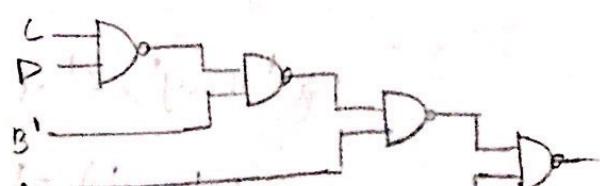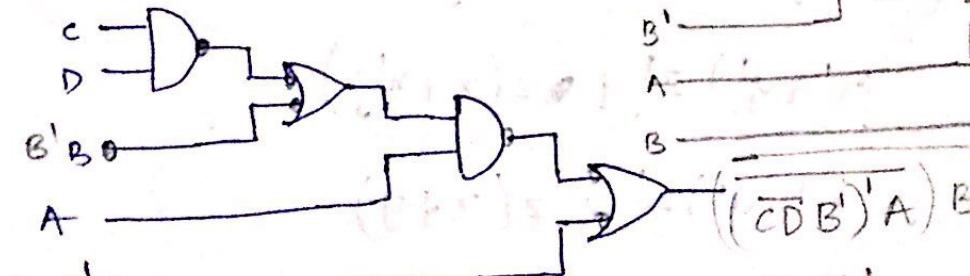

$$\begin{aligned} & ((CDB')' A) B \\ \rightarrow & (CDB')' A + B' \\ \rightarrow & A + (ED)A + B' \end{aligned}$$

Multi-level NAND

$$(AB' + CD')(A' + B)$$

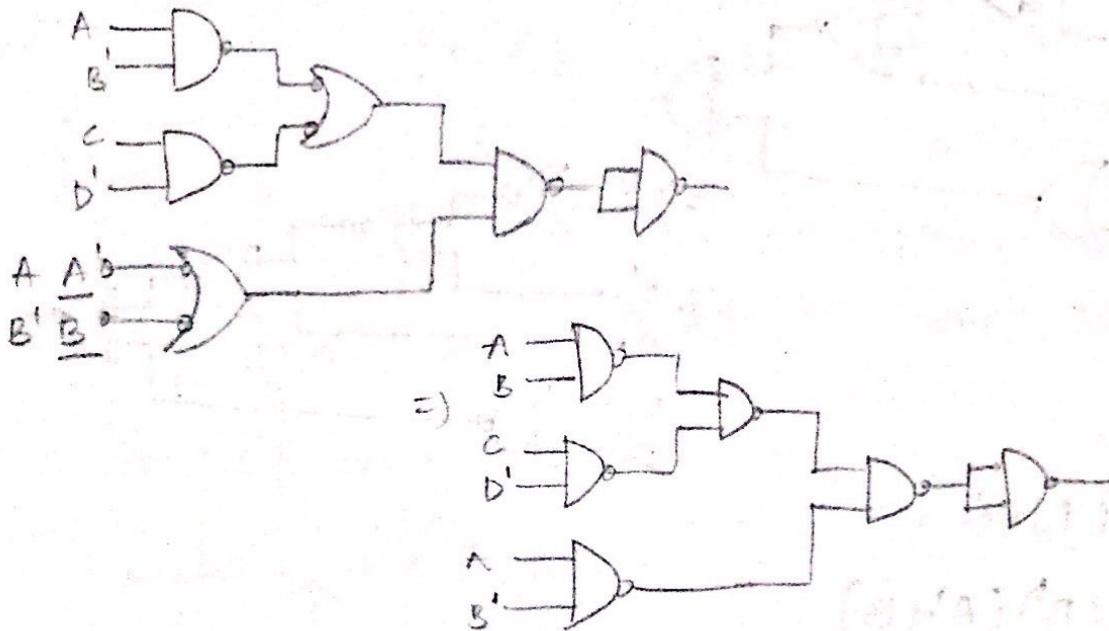

⇒ Minimisation of Switching function

- The Karnaugh Map (K-map)

$$\cancel{x'yz'} + \cancel{x'y'z'} + \cancel{xy'z'} + \cancel{x'yz} + \cancel{xyz} + \cancel{x'y'z}$$

$$\cancel{x'z'} + \cancel{xz} + \cancel{xy'z'} + \cancel{x'yz}$$

$$\cancel{x'z'} + \cancel{xy'z'} + \cancel{y'z'} + \cancel{xz} + \cancel{x'yz} + \cancel{yz}$$

1 + + +

$$\cancel{y'z'} + \cancel{yz} + \cancel{x'z'} + \cancel{xz}$$

$$(x' + xy)z' + xz + x'yz$$

$$(x' + y)z' + z(x + xy)$$

$$(x' + y)z' + z(x + y)$$

$$\textcircled{1} \rightarrow x'z' + y'z' + xz + zy$$

$$\textcircled{2} - x'z' + xy' + yz$$

$\textcircled{2}$ & $\textcircled{3}$ \rightarrow Minimal

$$\textcircled{3} - x'y + y'z' + xz$$

Expressions.

$\textcircled{1}, \textcircled{2}, \textcircled{3} \rightarrow$ Redundant expressions

An irredundant expression need not be minimal
A minimal expression may not be unique

K-Map

No. of cells = 2^n where $n =$ No. of variables.

$$n=4 \Rightarrow 2^4 = 16 \text{ cells.}$$

		AB	00	01	11	10
		CD	00	01	11	10
CD	00	0	9	12	8	
	01	1	5	13	9	
	11	3	7	15	11	
	10	2	6	14	10	

In 'n' variable K-map each cell will be adjacent to ' 2^n ' other cells.

$$5 \rightarrow 1, 4, 13, 7 ; 0 \rightarrow 1, 4, 2, 8 ; 9 \rightarrow 8, 13, 11, 1$$

Cell combinations will be in powers of 2 $\Rightarrow 2^n = 2, 4, 8$

2 cells \rightarrow pair ; 4 cells \rightarrow quad ; 8 cells \rightarrow octet

We can form a pair if they are adjacent.

Min terms in the K-map are represented

say 1

pair

		AB	00	01	11	10
		CD				
		00				
		01		1 1		
		11				
		10			1 1	

when two adjacent cells are given
The changing variable
should be eliminated.

1. $BC'D$
2. ACD'

quad

		AB	00	01	11	10
		CD	2 1			
		00	1	1	1	
		01	1	1	1	
		11	1	1	1	1
		10	1		1	1

In quad, each cell should
be adjacent to two other cells
which are considered.

1. BD
2. $A'B'$
3. AC

octet

		AB	00	01	11	10
		CD	1 1	1 1	1 1	1 1
		00	1	1	1	1
		01	1	1	1	1
		11				
		10				

1's at four corners can also
form a quad

$\rightarrow C'$

Among the collection of
octet each cell should be
adjacent to 3 other cells

A collection of 2^m cells results in a product term
which contains $(m-n)$ variables, where n is the
no. of variables.

$$2^1 = \text{pair} \Rightarrow 4-1 = 3$$

$$2^2 = \text{quad} \Rightarrow 4-2 = 2$$

$$2^3 = \text{octet} \Rightarrow 8-3 = 1$$

	AB	CD	00	01	11	10
CD	00	00	1	1		1
00	01	11	1			
01	11	1				
11	10					

First obtain
then quads, if any rema
make it apart

$$F = A'C' + B'C' + A'B'D'$$

	AB	CD	00	01	11	10
CD	00	00				
00	01	11	1	1	1	1
01	11	1				
11	10					

$$BD + B'C$$

Each minterm must be covered atleast once.

Always try to combine less no. of subcubes

Each sub cube must be as large as possible.

$$\rightarrow F(ABCD) = \sum(0, 1, 2, 3, 4, 6, 8, 9, 10, 11)$$

	AB	CD	00	01	11	10
CD	00	00	1	1		1
00	01	11	1			
01	11	1				
11	10					

$$B' + A'D'$$

$$\rightarrow = \sum(0, 1, 5, 7, 8, 10, 14, 15)$$

	AB	CD	00	01	11	10
CD	00	00	1			
00	01	11	1	1		
01	11	1				
11	10					

$$= A'B'C' + A'BD + ABC + ABC' \\ = A'C'D + BCD + ACD' + B'C'D'$$

$$\rightarrow = \sum(0, 1, 2, 3, 4, 6, 7, 8, 9, 11, 15)$$

	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$\begin{array}{l} A'B' + CD + A'D' + B'C \\ \downarrow \\ \text{Redundant} \end{array}$$

$$\rightarrow = \sum(0, 1, 4, 6, 8, 9, 12, 13, 14)$$

	AB	00	01	11	10
CD	00	1	1	1	1
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$$B'C' + BD' + AC'$$

$$\rightarrow = \sum(0, 1, 2, 3, 11, 12, 14, 15)$$

	AB	00	01	11	10
CD	00	1	1	1	1
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$$A'B' + ACD + ABD'$$

$$\rightarrow = \sum(0, 1, 2, 4, 5, 6, 8, 9, 12, 14)$$

	AB	00	01	11	10
CD	00	1	1	1	1
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$$C' + A'D' + BD'$$

6/8/19

Don't cares

Represented by d φ x

If it is useful in simplification consider it or
else don't care (neglect it) it.

It is considered as minterm

Note: All minterms must be covered, don'tcares
may or may not be considered.

1	1		d
d	.	.	.
d	.	.	d
1	.	.	d

Here without quad; also all minterms can be covered in pair so the answer is only 1 pair

1 pair

1	1		d
d	.	.	.
1	.	.	d

1 quad, 1 pair ✓

2 pairs

$$\rightarrow f(abcd) = \sum(1, 3, 5, 8, 9, 11, 15) + d(2, 12)$$

	f	1	1
1	1	d	1
1	.	1	1
d	.	.	.

3 quads

1 pair

$$\rightarrow f(abcd) = \sum(1, 3, 7, 11, 15) + d(0, 2, 5)$$

d	.	.	.
1	d	.	.
1	1	1	1
d	.	.	.

2 quads

$$= \Sigma (0, 2, 4, 9, 12, 15) + d (1, 5, 7, 10)$$

1	1	1
d	d	1
d	d	1
1	1	d

4 pairs


Essential Prime Implicants

All the adjacent cell are combined wherever it is possible but a pair in quad or a quad in a octet are not considered.

Now whatever the ^{combinations} (subcubes) formed are called prime implicants.

If each minterm is covered by more than one prime implicant then it is non-essential prime implicants.

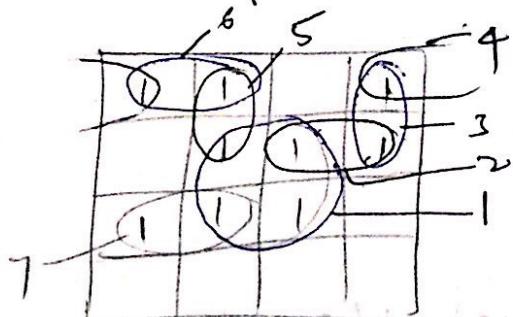If any of minterms are not covered by more than one prime implicant, then it is essential prime implicant.



7, 1 - Essential prime implicant

2, 3, 4, 5, 6 - non-essential prime implicants

Essential Prime implicant:

7/8/19

If prime implicant of a function F is said to be Essential Prime implicant if it covers atleast any minterm which is not covered by ^{any} other prime implicants.

Procedure to find the Minimal expression

1. Identify all the essential prime implicants and include them in the Minimal expression.
2. If the essential prime implicant covers all the minterms then the expression will be unique.
3. otherwise choose minimum no. of additional prime implicants so that all the minterms are covered.

1. $f(a, b, c, d) = \sum(4, 5, 8, 12, 13, 14, 15)$

ab\cd	00	01	11	10
00	.	1	1	1
01	.	1	1	.
11	.	.	1	.
10	.	1	.	.

$$ab + b\bar{c} + a\bar{c}d'$$


2. $\sum(0, 5, 7, 8, 9, 10, 11, 14, 15)$

ab\cd	00	01	11	10
00	1	.	.	1
01	.	1	.	1
11	.	1	1	1
10	.	1	1	1

5PI


9 EPI
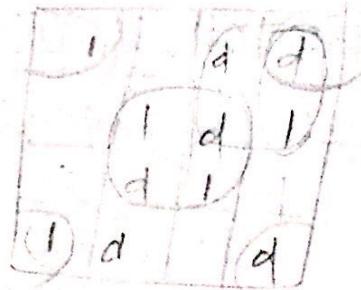
$$3. = \sum(0, 2, 5, 9, 15) + d(6, 7, 8, 10, 12, 13)$$



- 3 quads
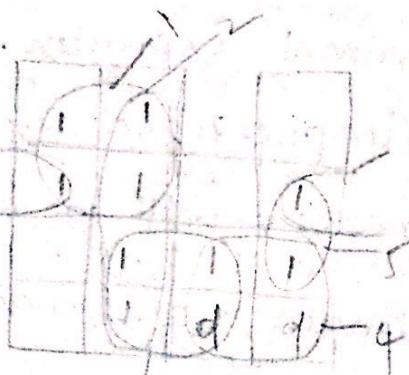
$$4. = \sum(0, 1, 4, 5, 6, 7, 9, 11, 15) + d(10, 14)$$




6 PI

1 epi

$1+3+5 \Rightarrow$ minimal expression
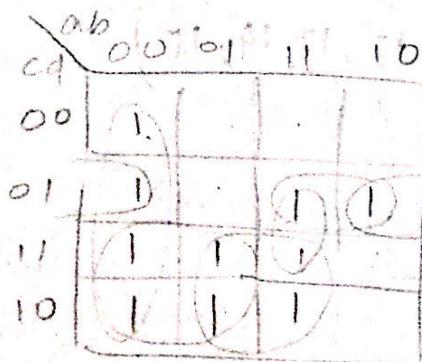
$$= \sum(0, 1, 2, 3, 6, 7, 9, 13, 14, 15).$$




6 PI

2 epi

$$a'b' + bc + c'da$$

$$\underline{8|8|19}$$
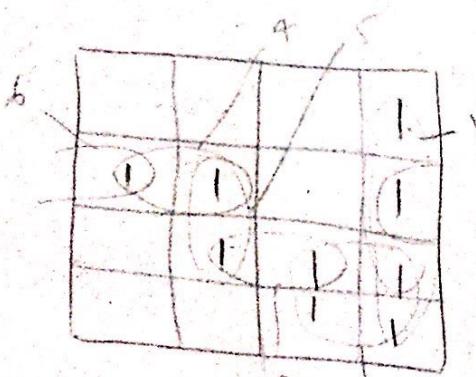
$$= \sum(1, 5, 7, 8, 9, 10, 11, 14, 15) = (1) + (2)$$



In the minimal expression all the essential prime implicants must be covered.

$$= \sum (1, 2, 3, 8, 9, 10, 11, 14) + d(7, 15)$$

			D
	1	1	1
B	d	d	1
	1	1	1

5 pvi

4 epi

	D	1	1	1
	1	1	1	1
D	1	1	1	1
	1	1	1	1

6 quads

3 epi

Product of Sums

A	B	00	01	11	10
C	D	00	0	0	0
00	0	0	0	0	0
01	0	0	0	0	0
11	0	0	0	0	0
10	0	0	0	0	0

$$(A+B)(A'+C+D) \cdot (C'+D+A) \cdot (A'+B'+C+D')$$

$$f(ABCD) = \prod (0, 4, 8, 12, 14, 15)$$

A	B	00	01	11	10
C	D	00	0	0	0
00	0	0	0	0	0
01	0	0	0	0	0
11	0	0	0	0	0
10	0	0	0	0	0

$$(C+D) \cdot (A'+B'+C')$$

$$= \pi(0, 1, 2, 3, 8, 9, 10, 11)$$

	AD CD	00 01 11 10	
00	0		0
01	0		0
11	0		0
10	0		0

$$\rightarrow = \sum(4, 5, 6, 7, 12, 13, 14, 15)$$

If the max terms are given then the remaining cells are contain maxterms.

In K-map cells are adjusted such that one variable changes when considered with adjacent cell.

Five variable K-map

$$2^5 = 32 \Rightarrow \text{cells}$$

		V=0			
wx		00	01	11	10
yz	00	0	4	12	8
01	1	5	13	9	
11	3	7	15	11	
10	2	6	14	10	

		V=1			
wx		00	01	11	10
yz	00	16	20	28	24
01	17	21	29	25	
11	19	23	31	27	
10	18	22	30	26	

For each cell in 5 variable K-map, each will be adjacent to other 5 cells.

$$+ (vwxyz) = \sum(4, 5, 6, 7, 13, 15, 20, 21, 22, 23, 25, 27, 29)$$

		V=0			
wx		00	01	11	10
yz	00	1	.	.	.
01	1	1	.	.	.
11	1	1	1	.	.
10	1	1	1	1	.

		V=1			
wx		00	01	11	10
yz	00	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$$w'x + xz + vwz$$

$$= \sum_{v=0}^1 (1, 2, 6, 7, 9, 12, 14, 15, 17, 22, 23, 25, 29, 30, 31)$$

	$w'x$	00	01	10	11	10
$y'z$	00
00	00
01	01	1	1	1	1	1
11	11	1	1	1	1	1
10	10	1	1	1	1	1

$w'y'z'$

$y'z'x'$

$y'z'w'$

xy

$$= \sum (0, 1, 2, 4, 5, 9, 11, 13, 15, 16, 18, 22, 23, 26, 29, 30, 31)$$

7 (Redundant)

	00	01	11	10	00
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1



	00	01	11	10	00
00	1	1	1	1	1
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

$$= \sum (0, 2, 3, 4, 5, 6, 7, 11, 15, 16, 18, 19, 23, 27, 31)$$

	$w'x$	00	01	11	10	$w'x$	00	01	11	10
$y'z$	00	1	1	1	1	00	1	1	1	1
00	00	00
01	01	1	1	1	1	01	1	1	1	1
11	11	1	1	1	1	11	1	1	1	1
10	10	1	1	1	1	10	1	1	1	1

$y'z + w'xv' + w'x'z'$
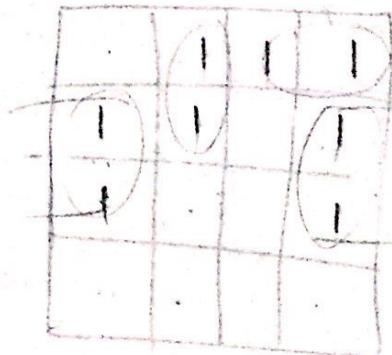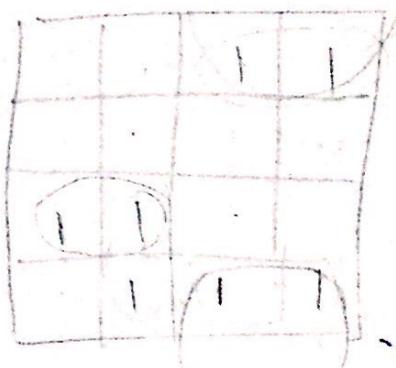
$$= \sum (3, 6, 7, 8, 10, 12, 14, 17, 19, 20, 21, 24, 25, 27, 29)$$



3 quads
3 pairs

Quine MC cluskey

or

14|8|19

Tabulation Method

Step

1. Arrange all minterms in groups, such that all terms in the same group have the same no. of 1's in their binary representation.

Start with the least no. of ones and continue with groups of increasing no. of 1's

The no. of ones in the term is called the index of the term.

Step

2. Compare every term of the lowest index group with each term in the successive group. Whenever possible, combine the two terms being compared. Repeat this by comparing each term in a group of index i with every term in the group of index $i+1$, until all possible combinations are completed.

Step 3: The terms generated in step-2 are now compared in the same fashion. The process continues until no further combinations are possible. The remaining unchecked terms constitutes the set of prime implicants of the function.

$$\rightarrow f(wxyz) = \sum (0, 1, 2, 5, 7, 8, 9, 10, 13, 15)$$

①	or	(0, 1) (1) ✓	2^3	2^2	2^1	2^0
		(0, 2) (2) ✓	8	4	2	1
		(0, 8) (8) ✓	w	x	y	z
		(1, 5) (4) ✓				
		(1, 9) (8) ✗				
		(2, 10) (8) ✗				
		(8, 9) (1) ✓				
		(8, 10) (2) ✗				
		(5, 7) (2) ✓				
		(5, 13) (8) ✗				
		(9, 13) (4) ✗				
		(7, 15) (8) ✗				
		15 ✗				
		(13, 15) (4) ✗				

Weight of the variable, that is being eliminated when the terms are combined

Minterms are combined such that their difference is power of 2's

also have equal weights
 $(0, 1)$ & $(8, 9)$ are combined because the difference b/w 0, 8 and 1, 9 is same and is equal to 8

If the combinations selected contain the terms which are not in increasing order then that combination already exists

These can not be further combined

In ① ②, ③ columns the unchecked terms are the prime implicants.

$$A = 0, 1, 8, 9 \quad (1, 8) \rightarrow 0 - wxyz'z = wy$$

$$B = 0, 2, 8, 10 \quad (2, 8) \rightarrow 2 - wx'y'z = x'z$$

$$C = 1, 5, 9, 13 \quad (4, 8) \rightarrow 9 - wxyz'z = y'z$$

$$D = 5, 7, 13, 15 \quad (2, 8) \rightarrow 15 - wxyz'z = xz$$

	0	1	2	5	7	8	9	10	13	15
A	x	x				x	x			
B		x	(x)			x		(x)		
C			x	x			x		x	
D				x	(x)				x	(x)

$$F = B + D + A$$

$$= B + D + C$$

$$\rightarrow f(wxyz) = \sum (13, 15, 17, 18, 19, 20, 21, 23,$$

$$(25, 27, 29, 31) + d(1, 2, 12, 24)$$

1	(1, 17), (16)		
2	(2, 18), (16)		
3	(2, 13), (1)	(25, 27) (2)	
4	(17, 19), (2)	(25, 29) (4)	
5	(17, 21), (4)	(15, 31) (16)	
6	(17, 25), (8)	(23, 31) (8)	
7	(18, 19), (1)	(27, 31) (4)	
8	(20, 21), (1)	(29, 31) (2)	
9	(24, 25), (1)		
10	(13, 15), (12)		
11	(13, 29), (16)		
12	(19, 23), (4)		
13	(19, 27), (8)		
14	(21, 23), (2)		
15	(21, 29), (2)		

$17, 19, 21, 23$ (2, 4) ✓
 $17, 19, 25, 27$ (2, 8) ✗
 $17, 21, 25, 29$ (4, 8) ✓

$13, 15, 29, 31$ (2, 16)
 $19, 23, 27, 31$ (4, 8) ✓
 $21, 23, 29, 31$ (2, 8) ✓
 $25, 27, 29, 31$ (2, 4) ✓

$17, 19, 21, 23, 25, 27, 29, 31$ (2, 4, 8)

$\frac{20 \mid 8 \mid 19}{(1, 17) \quad (2, 18) \quad (12, 13) \quad (18, 19) \quad (20, 21) \quad (24, 25) \text{ B}}$
 $\text{G} \quad \text{E} \quad \text{D} \quad \text{C}$
 $(13, 15, 29, 31) \text{ A} \rightarrow \text{prime implicants}$

$$(1, 17) = w'x'y'z$$

	13	15	17	18	19	20	21	23	25	27	29	31
A	x	x									x	x
B											x	
C							x	x				
D				x	x							
E	x											
F			x									
G			x									

$$f(vwxyz) = \sum (0, 1, 2, 8, 9, 15, 17, 21, 24, 25, 27, 31)$$

0 ✓
 1 ✓
 2 ✓
 8 ✓
9 ✓
 17 ✓
24 ✓
21 ✓
25 ✓
15 ✓
27 ✓
31 ✓

0, 1, 8, 9 (1, 8.) C
 1, 9 (8) ✓
 1, 17 (16) ✓
 8, 9 (1) ✓
 8, 24 (16) ✓
 9, 25 (16) ✓
 17, 21 (4) G
 17, 25 (8) ✓
24, 25 (1) ✓
25, 27 (2) F
15, 21 (16) E
27, 31 (4) D

$w \oplus y \oplus z = c$
 $w \oplus y = c$
 $vwyz = D$


	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓	✓
	0	1	2	8	9	15	17	21	24	25	27	31
A			x	x					x		x	
B		x			x		x			x		
C	x	x		x	x						x	x
D											x	x
E						x						
F										x	x	
G							x		x			
H		x		x								

21/8/19

	10	11	18	19	26
C			X	X	X
D				X	
E	X	X			
F	X	X		X	
G			X		X
H		X			
I		X			


Here all the minterms of D are covered in C so the row D can be eliminated. When G and H columns are considered H can be eliminated because in order to cover the elements of H E, F, G and I should be taken.

Digital circuits

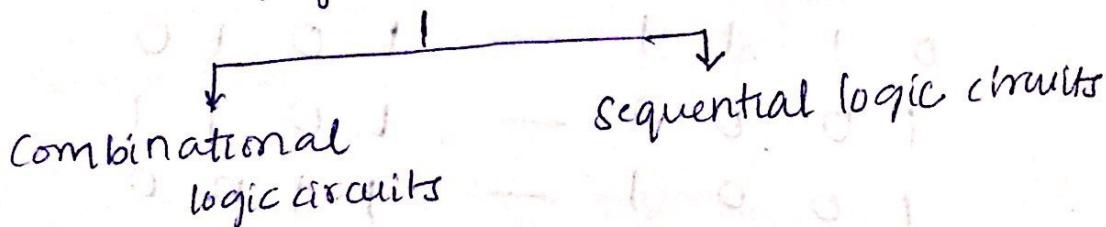

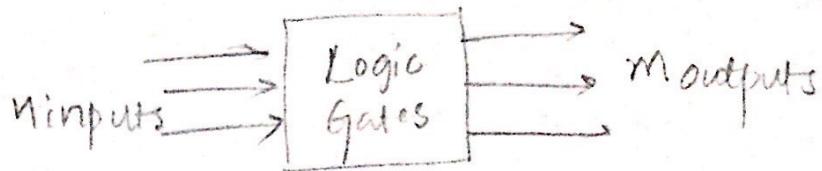- a) Code converters
- b) Adders.
- c) Subtractors
- d) Decoders
- e) Comparators
- f) Encoders
- g) Multiplexers
- h) Demultiplexers

Any combinational logic circuit will have n inputs and m outputs



1. Code converters: combinational code converters

Converts one code in to other codes.

BCD to Excess-3 code converter.

B_3	B_2	B_1	B_0		E_3	E_2	E_1	E_0
0	0	0	0	—	0	0	1	1
0	0	0	1	—	0	1	0	0
0	0	1	0	—	0	1	0	1
0	0	1	1	—	0	1	1	0
0	1	0	0	—	0	1	1	0
0	1	0	1	—	1	0	0	0
0	1	1	0	—	1	0	0	1
0	1	1	1	—	1	0	1	0
1	0	0	0	—	1	0	1	1
1	0	0	1	—	1	1	0	0

$$E_3 = f(B_3, B_2, B_1, B_0) + \text{fd}(10-15)$$

$$= \Sigma(5, 6, 7, 8, 9)$$

\downarrow
 $E_3 = 1$ at $5, 6, 7, 8, 9$

Since the inputs are 4 the no. of possible ways are 16 . We are considering only upto 9 , so the remaining are taken as don't care.

$$E_2 = f() = \sum(1, 2, 3, 4, 9) + d(10-15)$$

$$E_1 = f() = \sum(0, 3, 4, 7, 8) + d(10-15)$$

$$E_0 = f() = \sum(0, 2, 4, 6, 8) + d(10-15)$$

E_2

B_3B_2	00	01	11	10
00		d	1	
01	1	d	1	
11	1	d	d	
10	1	d	d	

E_2

B_3B_2	00	01	11	10
00		1	d	
01	1	.	d	1
11	1	.	d	d
10	1	.	d	d

$$E_3 = B_3 + B_2B_0 + B_2B_1$$

$$B_2'B_0 + B_2'B_1 + B_1'B_0'B_2$$


E_1

B_3B_2	00	01	11	10
00	0	1	d	1
01	.	.	1	
11	1	1	d	d
10	.	.	1	1

E_0

B_3B_2	00	01	11	10
00	1	1	d	1
01	.	.	d	-
11	.	.	d	d
10	1	1	d	d

$$B_0'B_1 + B_0B_1$$

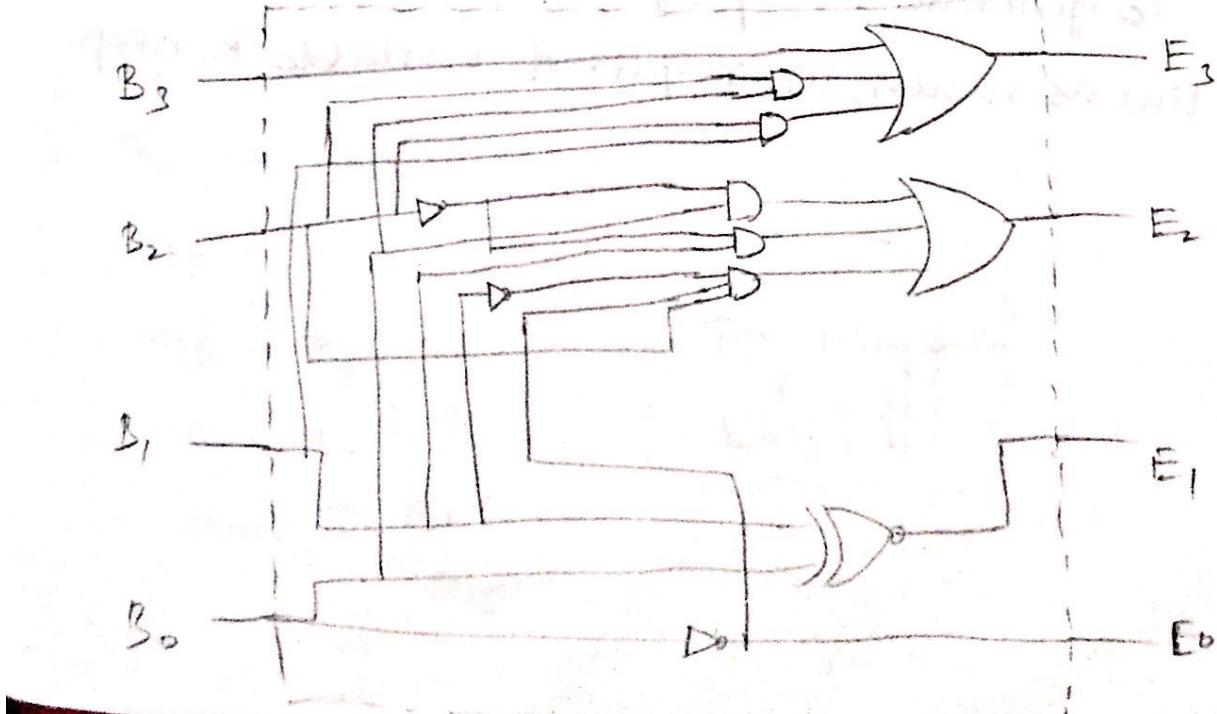

22/8/19

Binary to Gray code converter

Gray code is the mirror image code, first take the mirror image and add zeros above and ones below continue the process.

0 0 0 0
0 0 0 1
0 0 1 1
0 0 1 0
0 1 1 0
0 1 1 1
0 1 0 1
0 1 0 0
1 1 0 0
1 1 0 1
1 1 1 1
1 1 1 0
1 0 1 0
1 0 1 1
1 0 0 1
1 0 0 0

To generate the gray code take a zig-zag line as shown, in required variable K-map.

0	4	12	8
1	5	13	9
3	7	14	11
2	6	15	10

Truthtable

B_3	B_2	B_1	B_0		G_3	G_2	G_1	G_0
0	0	0	0	—	0	0	0	0 - 0
0	0	0	1	—	0	0	0	1 - 1
0	0	1	0	—	0	0	1	1 - 3
0	0	1	1	—	0	0	1	0 - 2
0	1	0	0	—	0	1	1	0 - 6
0	1	0	1	—	0	1	1	1 - 7
0	1	1	0	—	0	1	0	1 - 5
0	1	1	1	—	0	1	0	0 - 4
1	0	0	0	—	1	1	0	0 - 12
1	0	0	1	—	1	1	0	1 - 13
1	0	1	0	—	1	1	1	1 - 14
1	0	1	1	—	1	1	1	1 - 15
1	1	0	0	—	1	0	1	0 - 10
1	1	0	1	—	1	0	1	1 - 11
1	1	1	0	—	1	0	0	1 - 9
1	1	1	1	—	1	0	0	0 - 8

$$G_3 = \Sigma(8, 9, 10, 11, 12, 13, 14, 15) \rightarrow \text{For these inputs}$$

$$G_2 = \Sigma(4, 5, 6, 7, 8, 9, 10, 11) \rightarrow \text{the outputs are 1's}$$

$$G_1 = \Sigma(2, 3, 4, 5, 10, 11, 12, 13)$$

$$G_0 = \Sigma(1, 2, 5, 6, 9, 10, 13, 14)$$

$$G_3 = B_3$$

$$G_2 = B_3 \oplus B_2$$

$$G_1 = B_2 \oplus B_1$$

$$G_0 = B_1 \oplus B_0$$

G_3

		$B_3 B_2$	$B_3 B_1$	$B_3 B_0$	
		00	01	11	10
$B_1 B_0$	00	.	1	1	1
01	.	.	1	1	1
11	.	.	1	1	1
10	.	.	1	1	1

 G_2

		$B_3 B_2$	$B_3 B_1$	$B_3 B_0$	
		00	01	11	10
$B_1 B_0$	00	.	1	1	1
01	.	.	1	1	1
11	.	.	1	1	1
10	.	.	1	1	1

 B_3


		$B_3 B_2 G_1$	$B_3 B_1 G_1$	$B_3 B_0 G_1$	
		00	01	11	10
$B_1 B_0$	00	.	1	1	1
01	.	1	1	1	1
11	1	.	1	1	1
10	1	1	.	1	1

 $B_2 B_1' + B_1 B_2'$

		$B_3 B_2 G_0$	$B_3 B_1 G_0$	$B_3 B_0 G_0$	
		00	01	11	10
$B_1 B_0$	00
01	1	1	1	1	1
11	1	1	1	1	1
10	1	1	1	1	1

 $B_1' B_0 + B_1 B_0'$
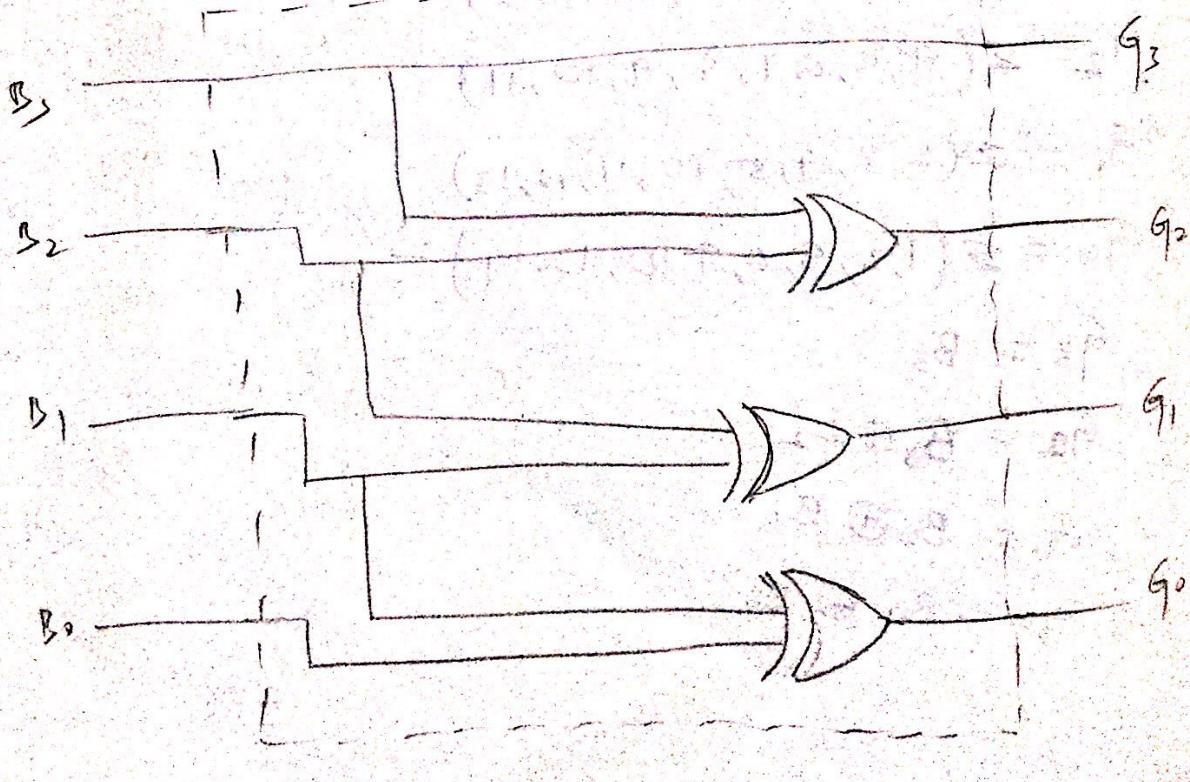
$$G_3 = B_3; G_2 = B_3 \oplus B_2; G_1 = B_2 \oplus B_1; G_0 = B_1 \oplus B_0$$



Gray to Binary code converter

$$B_2 = \sum (4, 5, 6, 7, 12, 13, 14, 15)$$

$G_1 G_0$	00	01	10	11
00	1		1	
01		1		1
11		1	1	
10	1			1

$$G_3' G_2 + G_3 G_2'$$

$$G_3 \oplus G_2$$

$$B_1 = \sum (2, 3, 5, 4, 13, 14, 11, 10)$$

$G_1 G_0$	00	01	11	10
00	0	1		1
01	1		1	
11	1		1	
10	1			1

$G_1 G_0$	00	01	11	10
00	1	1	1	1
01	1		1	1
11		1	1	
10	1			1

$$G_3' G_2 G_1' + G_1 G_3' G_2'$$

$$+ G_3 G_2 G_1 + G_3 G_2' G_1'$$

$$G_3' (G_2 \oplus G_1) + G_3 (\overline{G_1 + G_2})$$

$$\underline{G_3 \oplus (G_1 \oplus G_2)}$$

$$G_3' G_2 G_1 G_0' + G_3 G_2' G_1 G_0$$

$$+ G_3' G_2' G_1' G_0 + G_3 G_2' G_1' G_0$$

$$+ G_3' G_2 G_1 G_0 + G_3 G_2' G_1 G_0$$

$$+ G_3' G_2' G_1 G_0' + G_3 G_2 G_1 G_0'$$

$$G_0' G_1' (G_3 \oplus G_2) + G_0 G_1 (\overline{G_2 \oplus G_3}) + G_1 G_0 (G_2 \oplus G_3)$$

$$+ G_0' G_1 (\overline{G_2 \oplus G_3})$$

$$(G_3 \oplus G_2) (G_0' G_1' + G_0 G_0) + (\overline{G_2 \oplus G_3}) (G_0 G_1 + G_0' G_1)$$


$$(G_1 \oplus G_2) (\overline{G_0 \oplus G_1}) + (\overline{G_2 \oplus G_3}) (G_0 \oplus G_1)$$

$$= G_0 \oplus G_1 \oplus G_2 \oplus G_3$$

Adders:


Half Adder: It is a combinational logic circuit, it consists two inputs and two outputs. Two outputs are sum and carry.

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


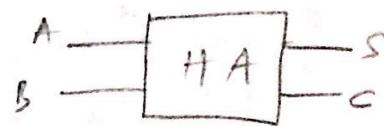


$$S = A \oplus B$$

$$C = AB$$

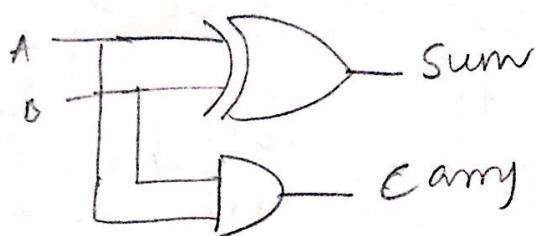

Half adder using only NAND gates.

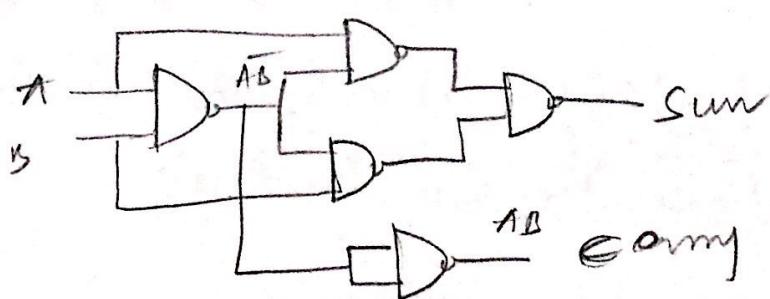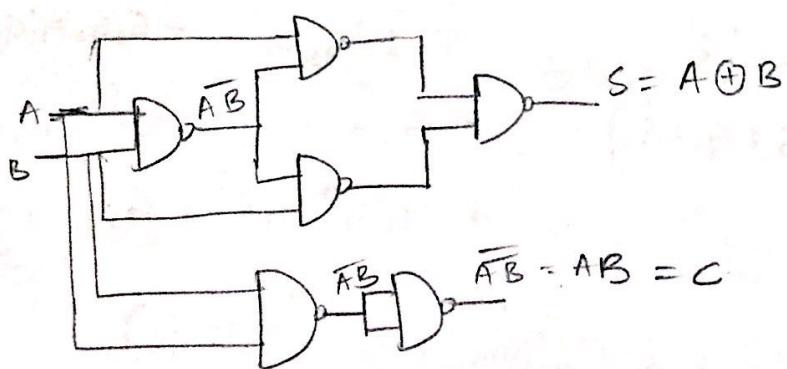


Half subtractor: It is a combinational logic circuit, consists two inputs & two outputs. Two outputs are Difference and carry.

A	B	D	B	A		D
0	0	0	0			
0	1	0	1			
1	0	1	0			
1	1	0	0			

$D = A \oplus B$

$B = A'B$

Half subtractor using only NAND gates.

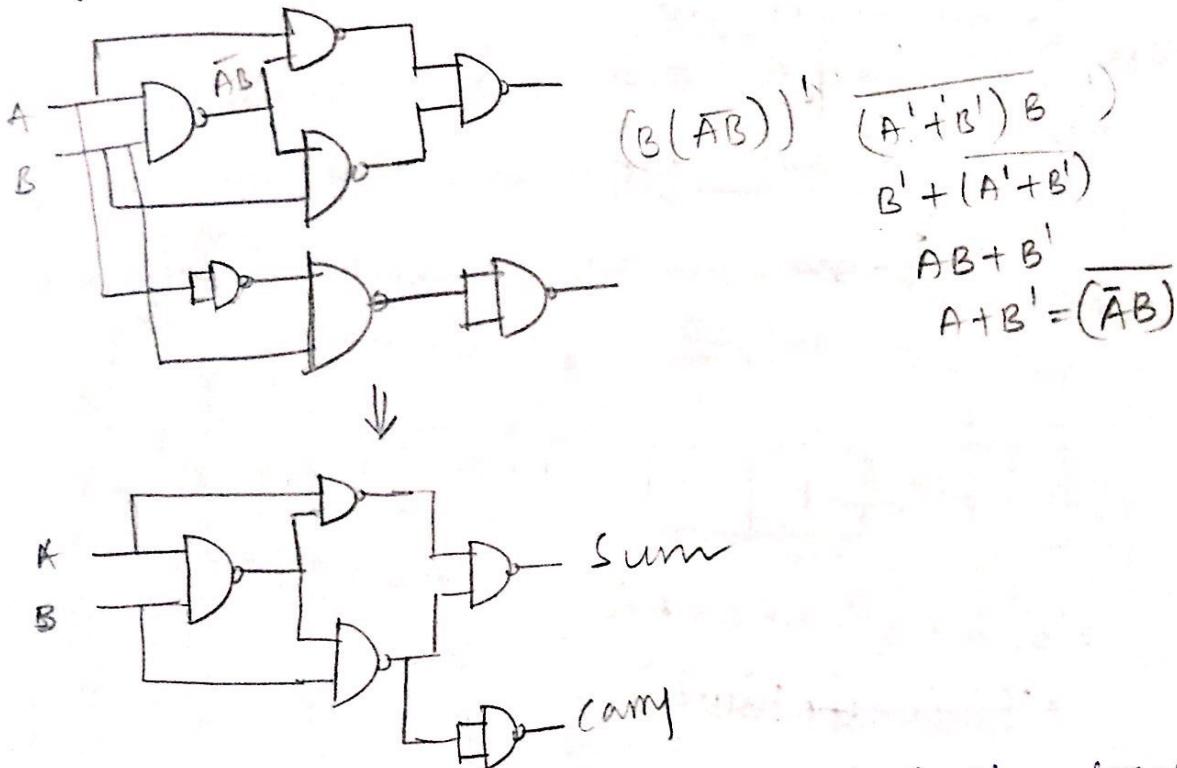

Full adder: It is a combinational logic circuit that consists three inputs and two outputs. Two outputs are sum and carry.

A B C S

0 0 0 0 0

0 0 1 1 0

0 1 0 1 0

0 1 1 0 1

1 0 0 1 0

1 0 1 0 1

1 1 0 0 1

1 1 1 1 1

A B	00	01	11	10
C	0	2	6	4
0	0	1	3	7
1	1	0	5	6

Sum

A B	00	01	11	10
C	0	1	-	1
0	1	1	1	-
1	1	0	1	1

Carry

A B	00	01	11	10
C	0	1	1	1
0	1	0	1	0
1	1	1	0	1

$$A'B'C + A'BC' + ABC + A'BC'$$

$$A'(B \oplus C) + A(B \oplus C)$$



$$A \oplus B \oplus C$$

$$AB + BC + AC$$

Carry	A B	00	01	11	10
C	0	0	1	1	0
0	1	0	0	1	0
1	1	1	0	1	1

23/8/19

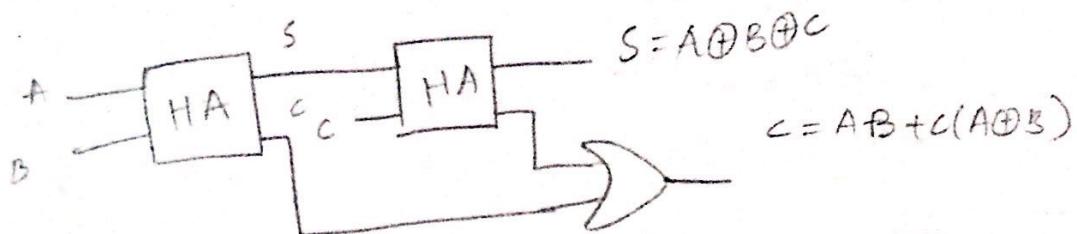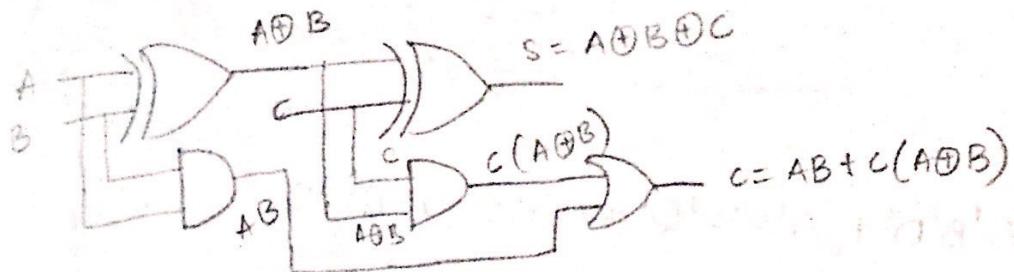Full Adder using two Half Adders and one OR gate



Full subtractor: It is a combinational logic circuit which consists three inputs and two outputs which are Difference and Borrow.


A	B	C	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

AB		00	01	11	10
C		0	1	1	1
0	0	0	1	1	1
1	1	1	1	1	1

$$D = A \oplus B \oplus C$$

AB		00	01	11	10
C		0	1	1	1
0	0	0	1	1	1
1	1	1	1	1	1
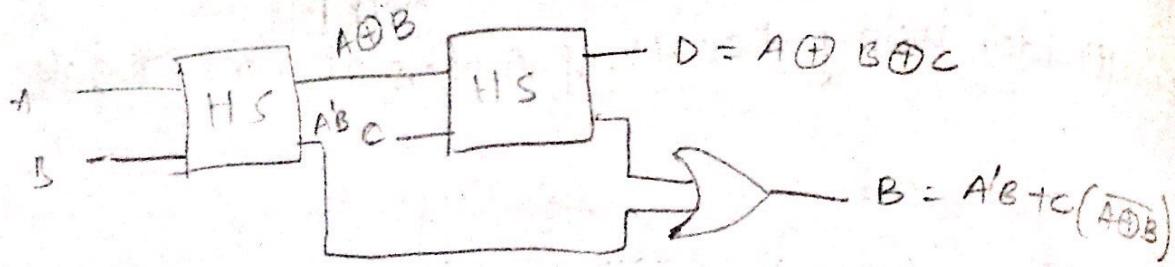
$$\begin{aligned} D &= A'B + A'B'C + ABC \\ &= A'B + C(A \oplus B) \end{aligned}$$



$$f = A'B'D' + A'B'C'D' + A'BD + ABC'D$$

$$A'B'D' + BD(A' + C')$$

$$A'B'D' + A'BD + BDC'$$

$\backslash AB$	00	01	11	10
CD	00	1		
01		1	1	
11		1		
10	1			

$$\rightarrow \pi(1, 3, 5, 7, 13, 15)$$


$\backslash AB$	00	01	11	10
CD	00			
01	D	D	D	
11	D	D	D	
10				

$$(A + D')(B' + D)$$

4-bit Binary Parallel Adder

27/8/19

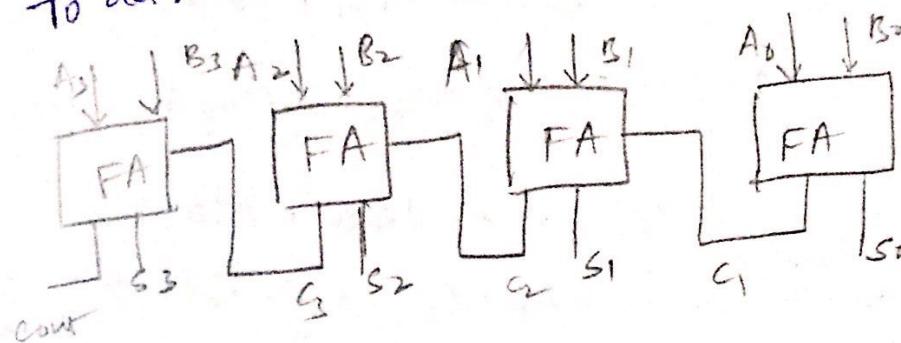To add 2 bits and a carry full adder is required.



but it's
a slow
process

Magnitude Comparator (n-2)

A ₁ A ₀	B ₁ B ₀	A > B	A = B	A < B
0 0	0 0	0	1	0
0 0	0 1	0	0	1
0 0	1 0	0	0	1
0 0	1 1	0	0	1
0 1	0 0	1	0	0
0 1	0 1	0	1	0
0 1	1 0	0	0	1
0 1	1 1	0	0	1
1 0	0 0	1	0	0
1 0	0 1	1	0	0
1 0	1 0	1	0	0
1 0	1 1	1	0	0
1 1	0 0	1	0	0
1 1	0 1	1	0	0
1 1	1 0	1	0	0
1 1	1 1	1	0	0

For this 3-K-maps are required to write the expressions for the outputs. Instead of that it can be done using only one K-map.

A, A_0	B, B_3	00	01	11	10
00	$A = B$	$A > B$	$A > B$	$A > B$	
01	$A < B$	$B = B$	$A > B$	$A > B$	
11	$A < B$	$A < B$	$A = B$	$A < B$	
10	$A < B$	$A < B$	$A > B$	$A = B$	

$$A > B \Rightarrow A_1 B_1' + A_0 B_1' B_0' + A_1 B_0'$$

$$A < B \Rightarrow A_1' B_1 + A_1' A_0 B_0 + A_0' B_1 B_0$$

$$A = B \Rightarrow A_1' A_0' B_1' B_0' + A_1' A_0 B_1' B_0$$

$$+ A_1 A_0 B_1 B_0 + A_1 A_0' B_1 B_0'$$

$$\Rightarrow A_1' B_1' (\overline{A_0 \oplus B_0}) + A_1 B_1 (A_0 B_0 + A_0 B_0')$$

$$= A_1' B_1' (\overline{A_0 \oplus B_0}) + A_1 B_1 (\overline{A_0 \oplus B_0})$$

$$= (\overline{A_1 \oplus B_1}) (\overline{A_0 \oplus B_0})$$

$$= (A_1 \ominus B_1) (A_0 \ominus B_0)$$

4-bit magnitude comparator.

$$\text{No. of cells} = 2^{2n} \Rightarrow n=4 \Rightarrow 2^8$$

$$A = A_3 A_2 A_1 A_0$$

$$A_3 > B_3 \Rightarrow A > B$$

$$B = B_3 B_2 B_1 B_0$$

$$A_3 = B_3 ; A_2 > B_2 \Rightarrow A > B$$

$$A_2 = B_2 ; A_1 > B_1 \Rightarrow A > B$$

$$A_1 = B_1 ; A_0 > B_0 \Rightarrow A > B$$

$$A_0 \odot B_3 = x_3$$

Output will be higher (1) when
both the inputs are equal


$$A_2 \odot B_2 = x_2$$

in XNOR gate

$$A_1 \odot B_1 = x_1$$

$$A_0 \odot B_0 = x_0$$

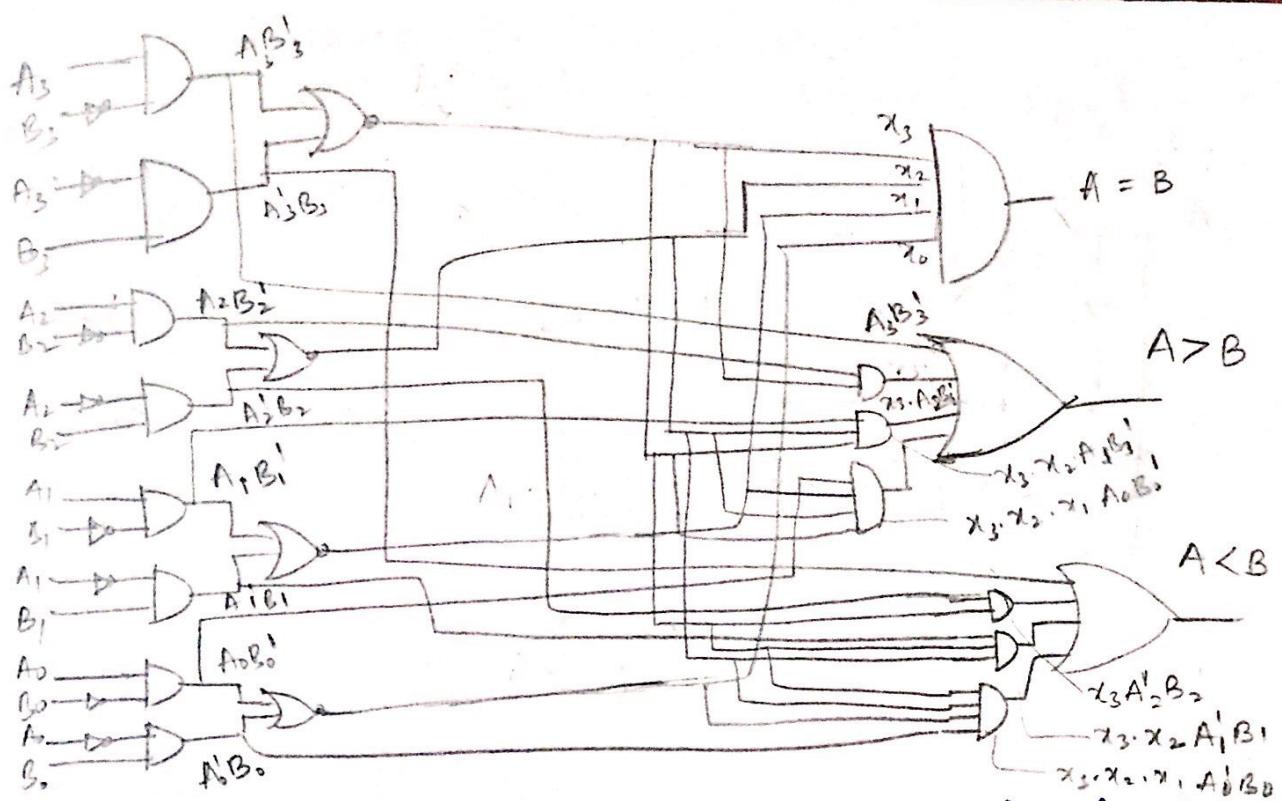Output will be higher (1) when all the inputs
are higher(1) in AND gate



A_3	B_3	$F \Rightarrow A_3B_3'$
0	0	0
0	1	0
1	0	1
1	1	0

A_2B_2' is further checked only when A_3 is equal to B_3
 $\Rightarrow x_3 \cdot A_2B_2'$
 similarly $x_3 \cdot x_2 \cdot A_1B_1'$

$$A > B \Rightarrow A_3B_3' + x_3 \cdot A_2B_2' + x_3 \cdot x_2 \cdot A_1B_1' + x_3 \cdot x_2 \cdot x_1 \cdot A_0B_0'$$


$$\Rightarrow A < B : A_3'B_3 + x_3 \cdot A_2'B_2 + x_3 \cdot x_2 \cdot A_1'B_1 + x_3 \cdot x_2 \cdot x_1 \cdot A_0B_0$$

Decoder :

$$A_1B_1 + x_1 \cdot A_0B_0 \\ A_0'A_1 + A_0A_1(A_0B_0) \Rightarrow A_0'A_1A_0B_0 +$$


It is a combinational logic circuit, which consists of n inputs and m outputs.

$$m \leq 2^n$$

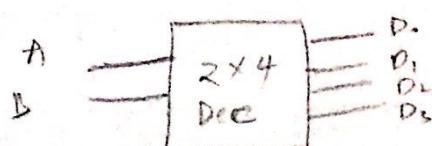


Block Diagram
 $2 \times 4 \Rightarrow 2$ inputs
 4 outputs

Logic diagram

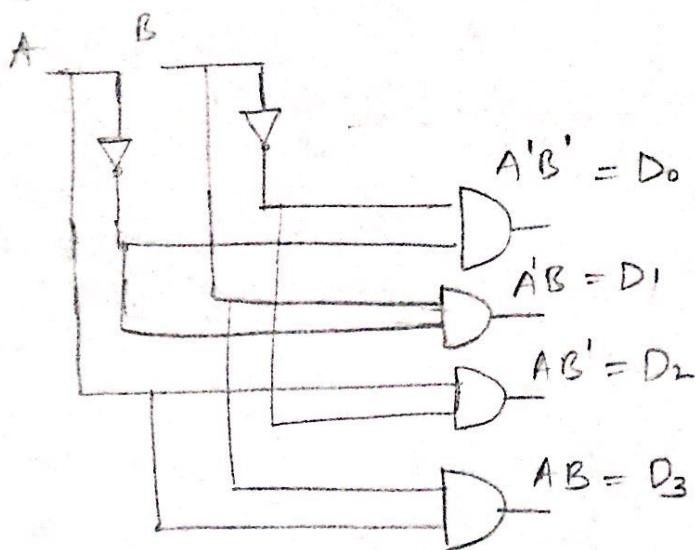


3x8 decoder

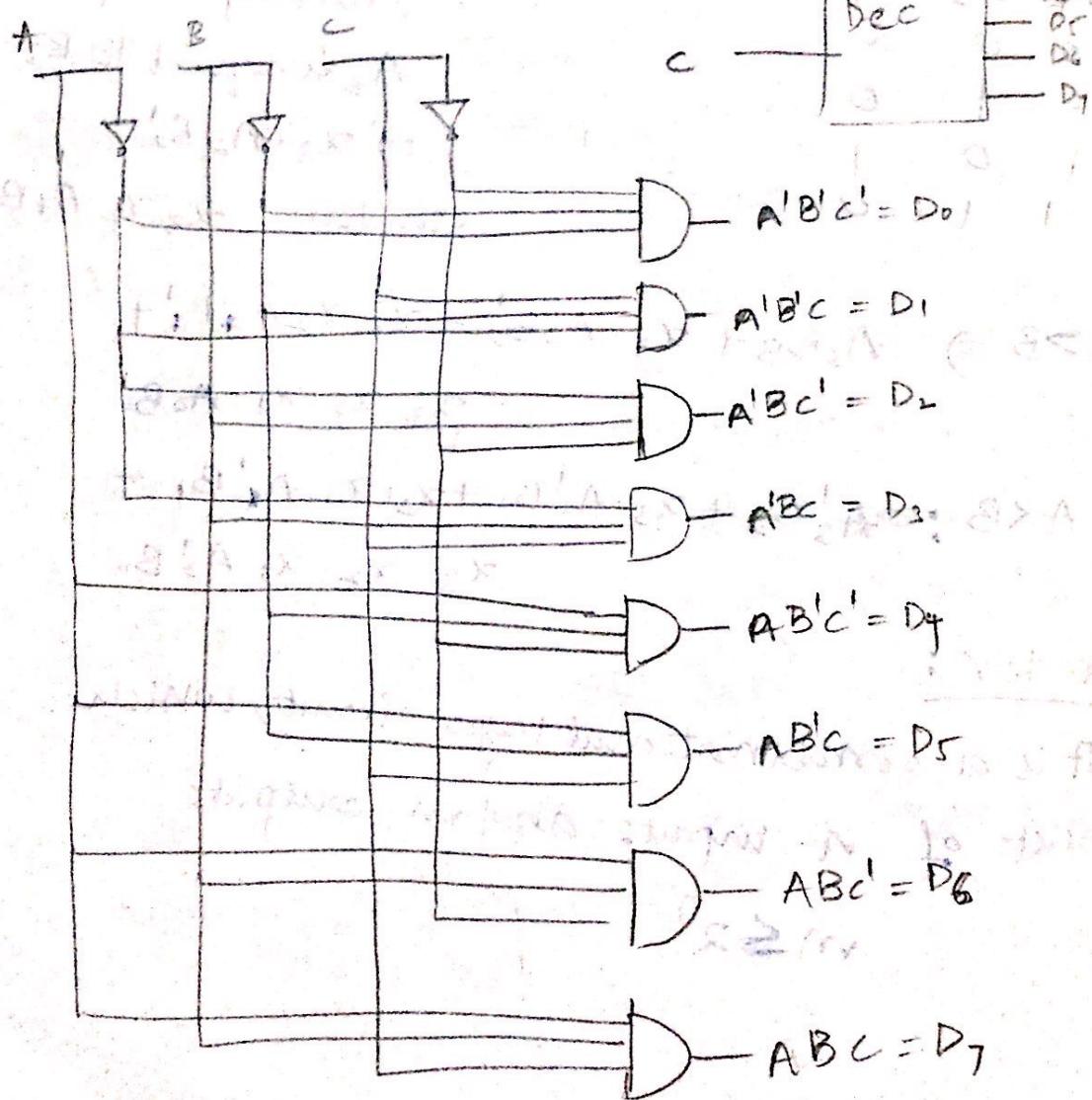


Boolean Function Implementation

$$f(A, B, C) = \Sigma(1, 2, 4, 7) \rightarrow \text{connect a OR gate to } D_1, D_2, D_4 \text{ and } D_7$$

$$f(A, B, C) = \Sigma(0, 3, 4, 7)$$

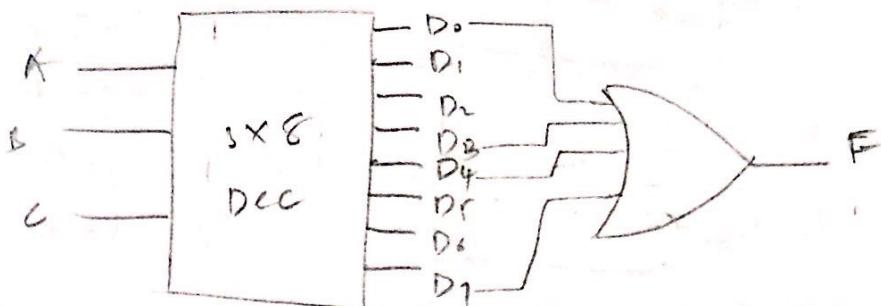

Implement full adder using a decoder


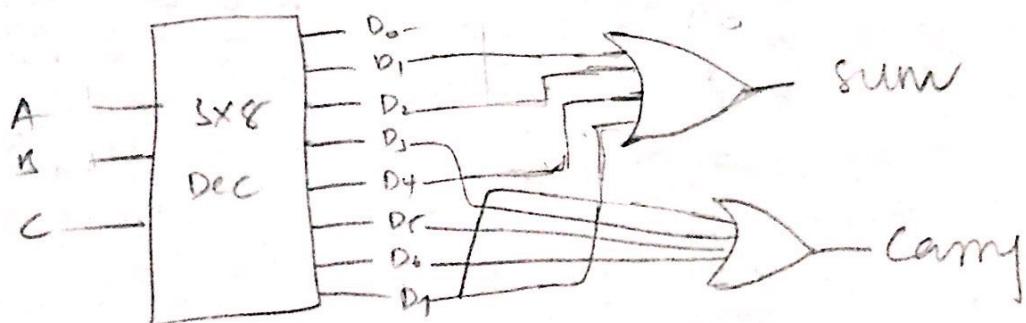



$$f(A, B, C) = \Pi(1, 2, 4, 7)$$

$$\nexists f(A, B, C) = \Sigma(0, 3, 5, 6) \rightarrow \text{Implement } \bar{F}$$

Implement 4x16 decoder using TWO 3x8


decoder and one inverter.

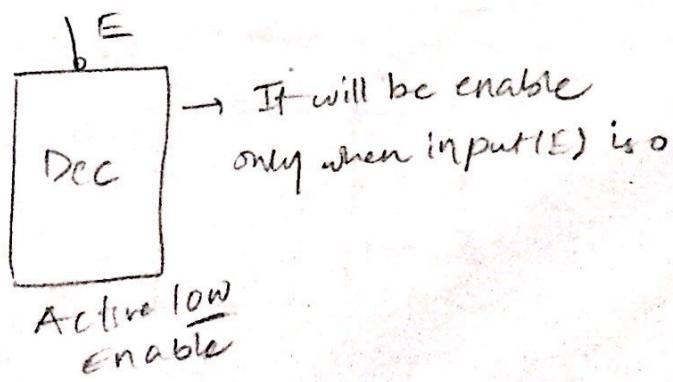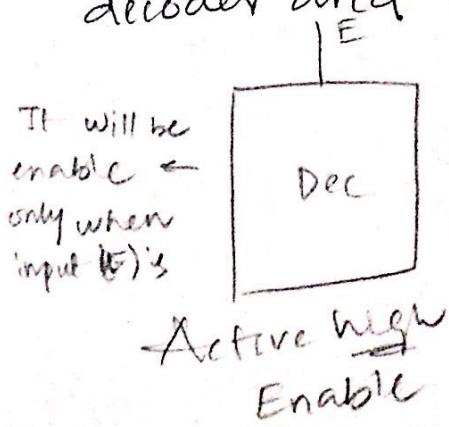

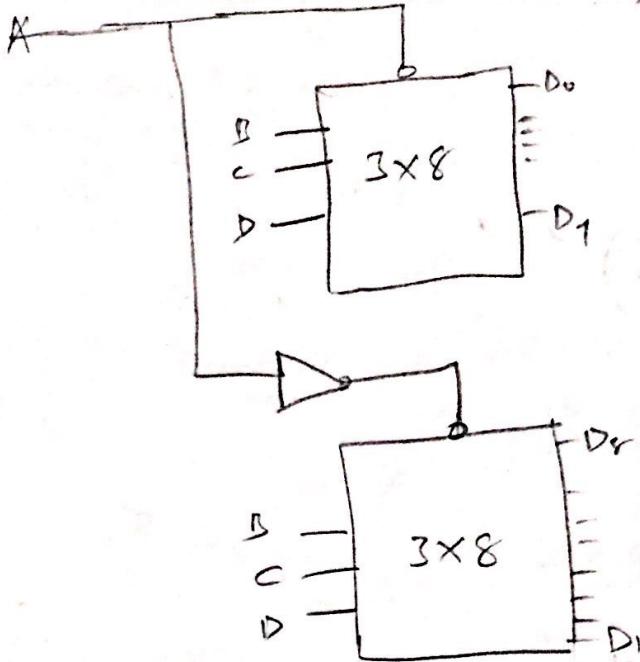

A	B	C	D	D_0	D_1	D_8	D_9	D_{10}	D_{11}	D_{12}	D_{13}	D_{14}	D_{15}
0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	1
0	0	1	0	0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	1	1	0	0	0	0	0	1
0	1	0	0	0	0	0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	1	1	0	0	0	0	1
0	1	1	0	0	0	0	0	0	1	0	0	0	0
0	1	1	1	0	0	0	1	1	1	0	0	0	1
1	0	0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1
1	0	1	0	0	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0	0	1
1	1	0	0	0	0	0	0	0	0	1	0	0	0
1	1	0	1	0	0	0	0	0	1	1	0	0	1
1	1	1	0	0	0	0	0	0	0	0	1	0	0
1	1	1	1	0	0	0	0	1	1	1	1	0	1

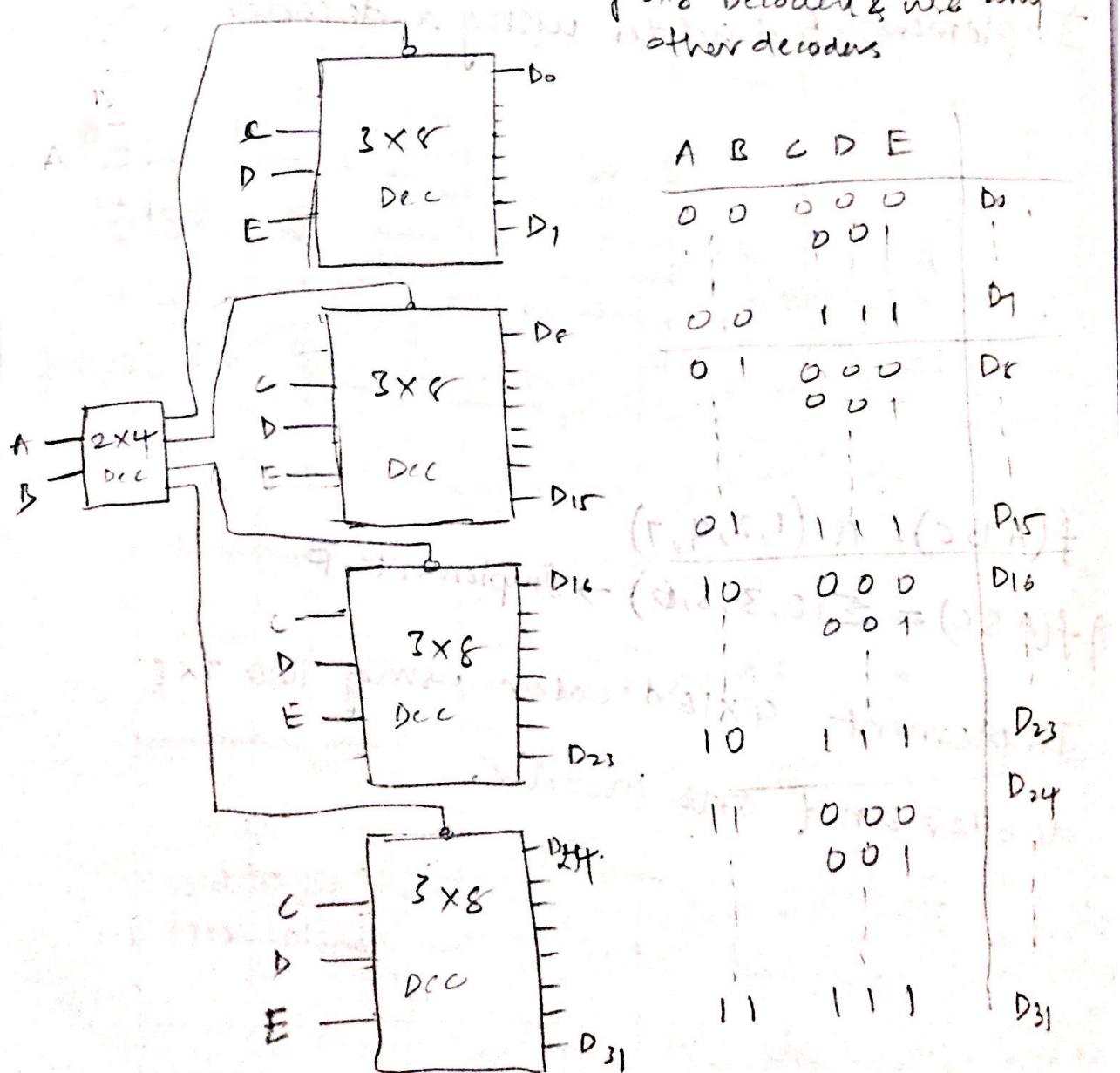→ Implement 5x32 Decoder using 3x8 Decoders & use any other decoders



Decimal Decoders


3/9/19

B_3	B_2	B_1	B_0	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	D_8	D_9
0	0	0	0	1	0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	0	0	0	0	0
0	1	0	1	0	0	0	0	0	1	0	0	0	0
0	1	1	0	0	0	0	0	0	0	1	0	0	0
0	1	1	1	0	0	0	0	0	0	0	1	0	0
1	0	0	0	0	0	0	0	0	0	0	0	1	0
1	0	0	1	0	0	0	0	0	0	0	0	0	1

B_3B_2	00	01	11	10	
B_1B_0	00	D_0	D_4	d	D_8
	01	D_1	D_5	d	D_9
	11	D_3	D_7	d	d
	10	D_2	D_6	a	d

10 to 15 should be taken as don't cares


BCD to seven segment decoder

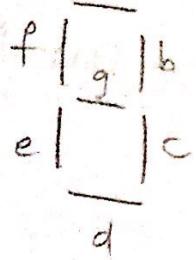

	B_3	B_2	B_1	B_0	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	r	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	1	0	1	1

Encoder (Opposite of Decoder)

2^n -inputs ; n -outputs.

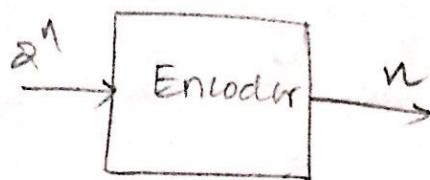

8x3 Encoder:

D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	C	B	A
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$C = D_4 + D_5 + D_6 + D_1$$


$$B = D_2 + D_3 + D_6 + D_7$$

$$A = D_1 + D_3 + D_5 + D_7$$

Disadvantages:

If two inputs are high simultaneously, we will get wrong output.

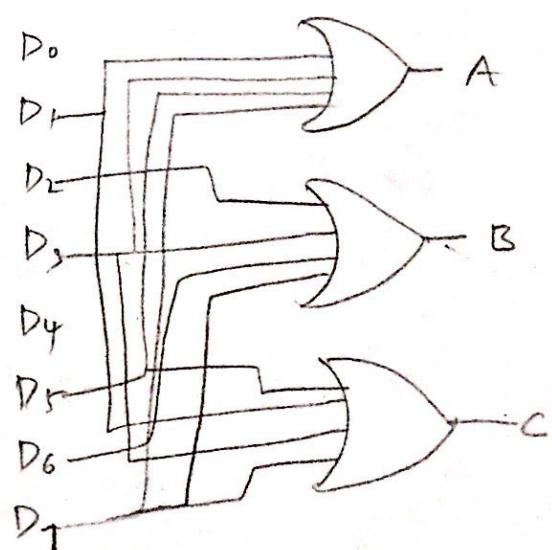If all inputs are low the output is not mentioned.



To overcome the disadvantages of Encoder

Priority Encoder, uncd -

4x2 Encoder

V = Valid bit

D ₀	D ₁	D ₂	D ₃	Y ₁ , Y ₀	V
0	0	0	0	X X	0
1	0	0	0	0 0	1
X	1	0	0	0 1	1
X	X	1	0	1 0	1
X	X	X	1	1 1	1

If D₂ and D₃ both inputs are in then the D₃ output will come because the priority will be given to D₃ as 3 is greater than 2.

		Y ₁				
		00	01	11	10	
D ₀ , D ₁		00	0	0	0	0
00		01	1	1	1	1
01		11	1	1	1	1
11		10	1	1	1	1
10						

$$Y_1 = D_2 + D_3$$

		Y ₀				
		00	01	11	10	
D ₀ , D ₁		00	1	1	1	0
00		01	1	1	1	1
01		11	1	1	1	1
11		10	1	1	1	1
10						

$$D_2' + D_3$$

		V				
		00	01	11	10	
D ₀ , D ₁		00	0	1	1	1
00		01	1	1	1	1
01		11	1	1	1	1
11		10	1	1	1	1
10						

$$V = D_0 + D_1 + D_2 + D_3$$

If XX10 is considered for Y, X may be 0 or 1


$$\begin{array}{l} 0010-2 \\ 0110-6 \\ 1010-10 \\ 1100-12 \end{array} \left. \right\} \rightarrow 1$$

Multiplexer


(mux = many inputs to single output)
(parallel to series converter)

Multiplexer will have 2^n inputs and one output

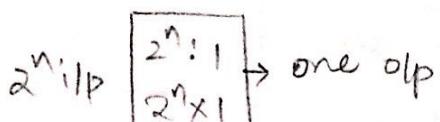
n - no. of selection inputs. Multiplex is commonly known as mux.



↑ n selection inputs.

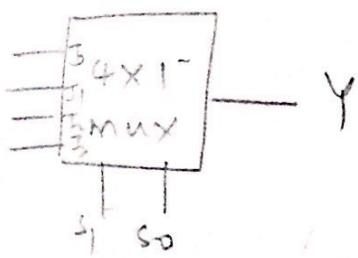


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

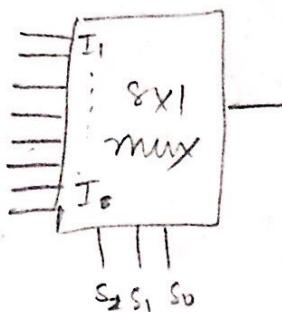

S_2	S_1	S_0	Y
0	0	0	I_0
0	0	1	I_1
0	1	0	I_2
0	1	1	I_3
1	0	0	I_4
1	0	1	I_5
1	1	0	I_6
1	1	1	I_7


4|9|19

4x1 mux Logic diagram

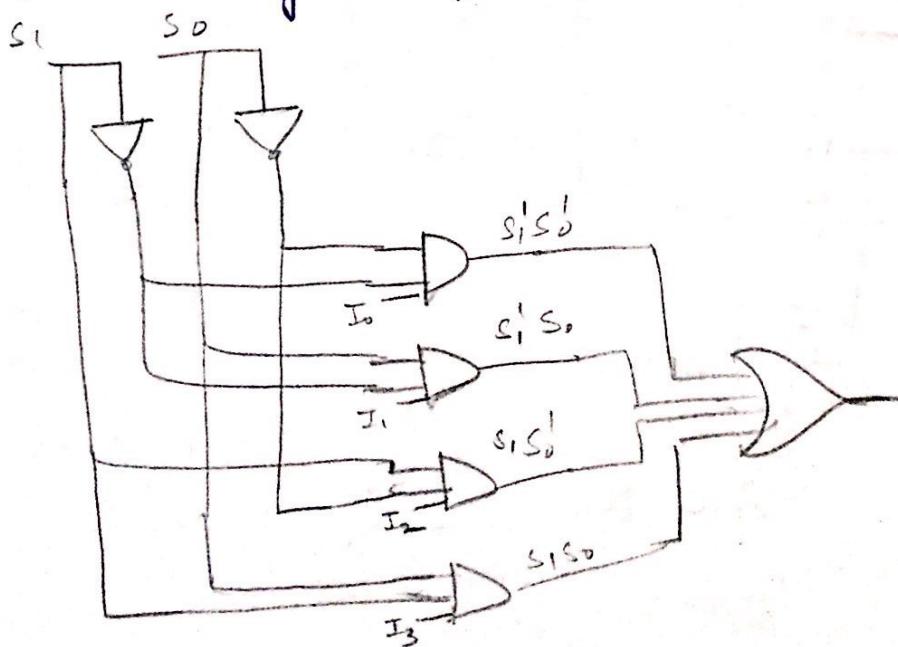


Boolean Function Implementation

$$f(A B C) = \sum(1, 3, 5, 6)$$

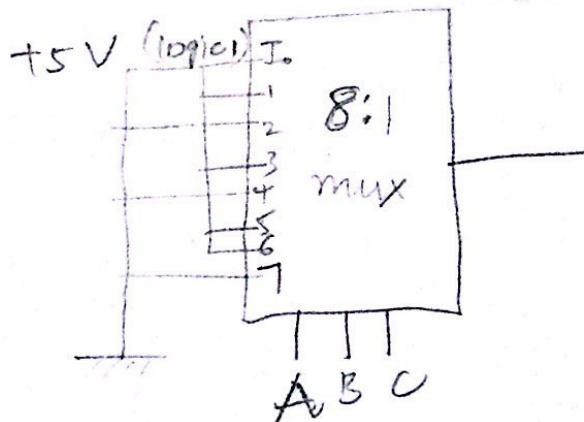

First find the size of mux
connect the given numbers
to logic 1 and remain
to the ground (logic 0)
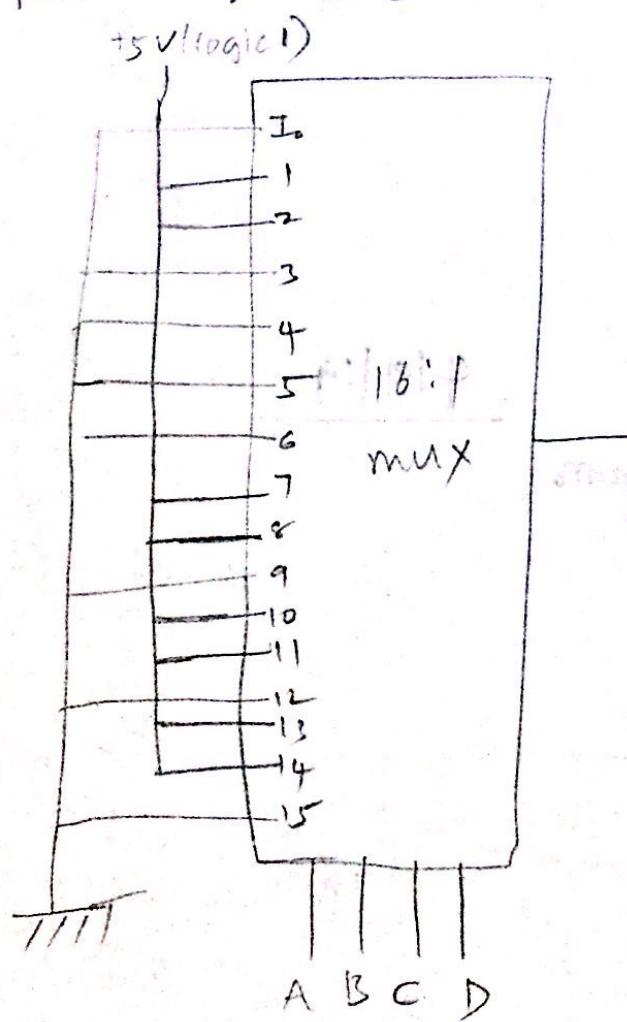
$$\rightarrow f(A B C D) = \sum(1, 2, 7, 8, 10, 11, 13, 14)$$



Case(i): Implementing n-variable Boolean Function with

$2^n \times 1$ mux

Case(ii): Implementing n-variable Boolean Function with


$2^{n-1} \times 1$ mux

$2^{n-1} \times 1$ mux

(Normal 3,5,6,8) \geq (Simplified)


$$\rightarrow f(ABC) = \Sigma(1, 2, 6, 7)$$

A	B	C	f
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

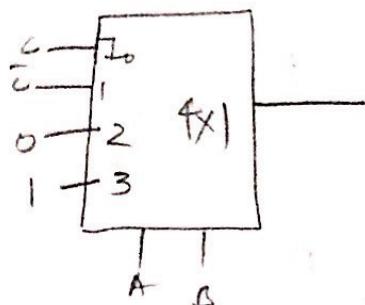

$$\rightarrow f(ABCD) = \Sigma(1, 2, 4, 6, 7, 8, 13, 14)$$

A	B	C	D	f
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0
1	1	1	1	1

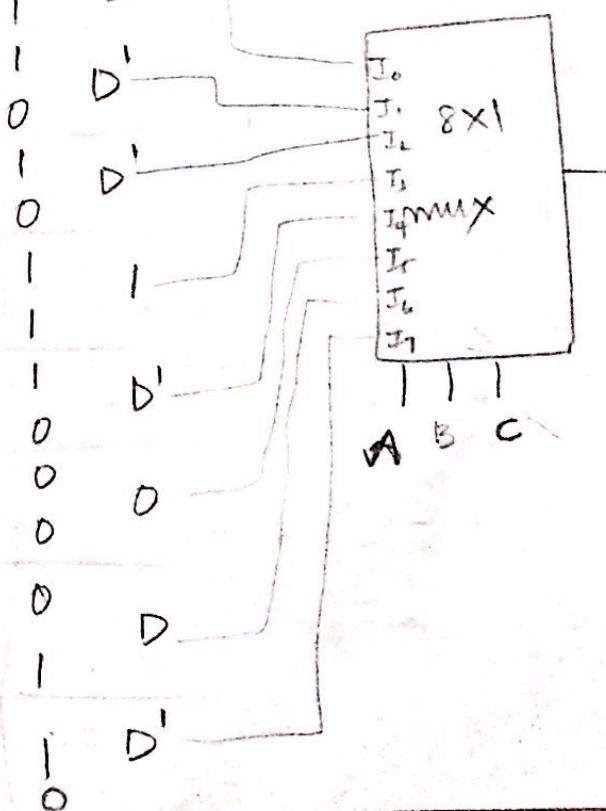

5/9/19


iii) Implementing 'n' variable Boolean function with
 $2^{n-2} \times 1$ mux

$$f(ABCD) = \sum(1, 2, 7, 8, 13, 14, 15)$$



A	B	C	D	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Represent F in terms of C and D

Now, A & B are the selection inputs.

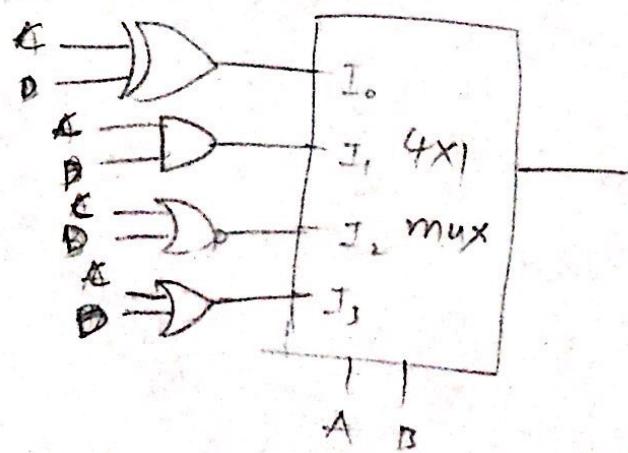


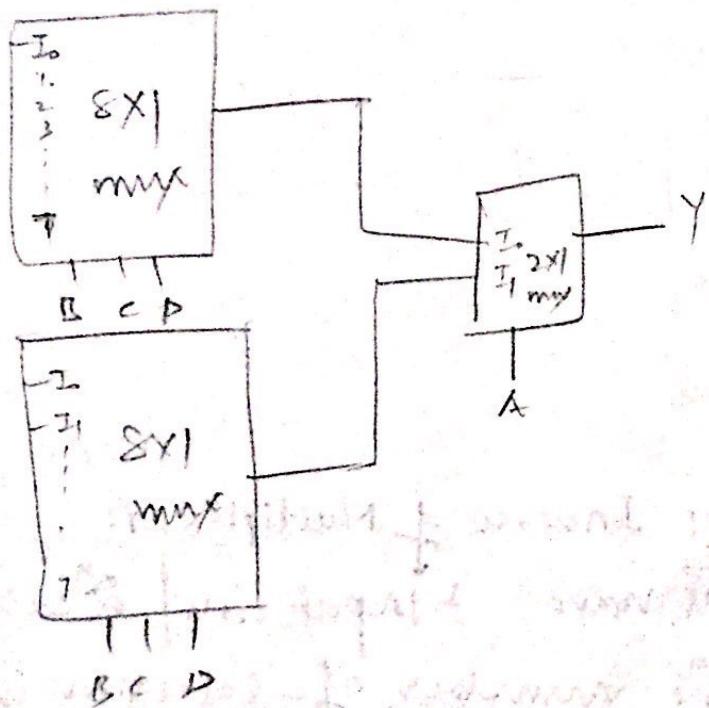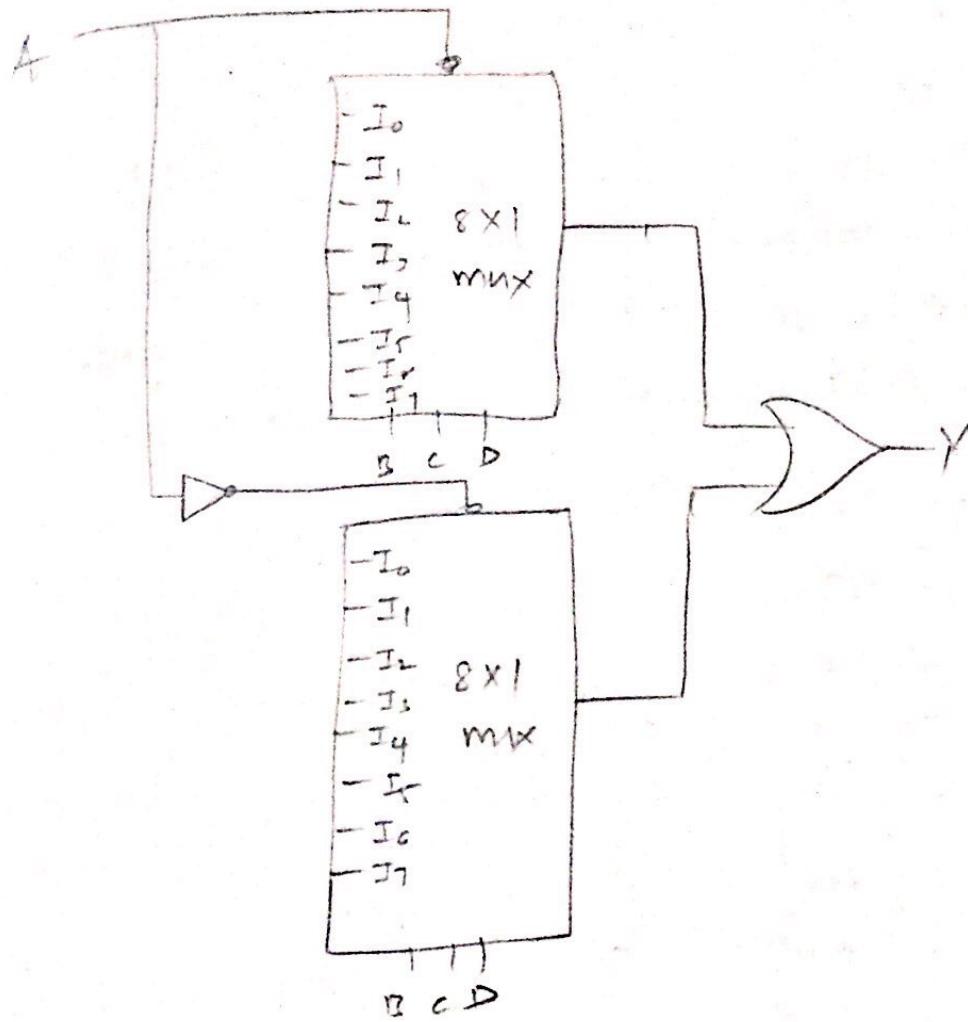Implement 16×1 mux using two 8×1 muxes and one or gate



When enable inputs are not given then the mux will be enabled.

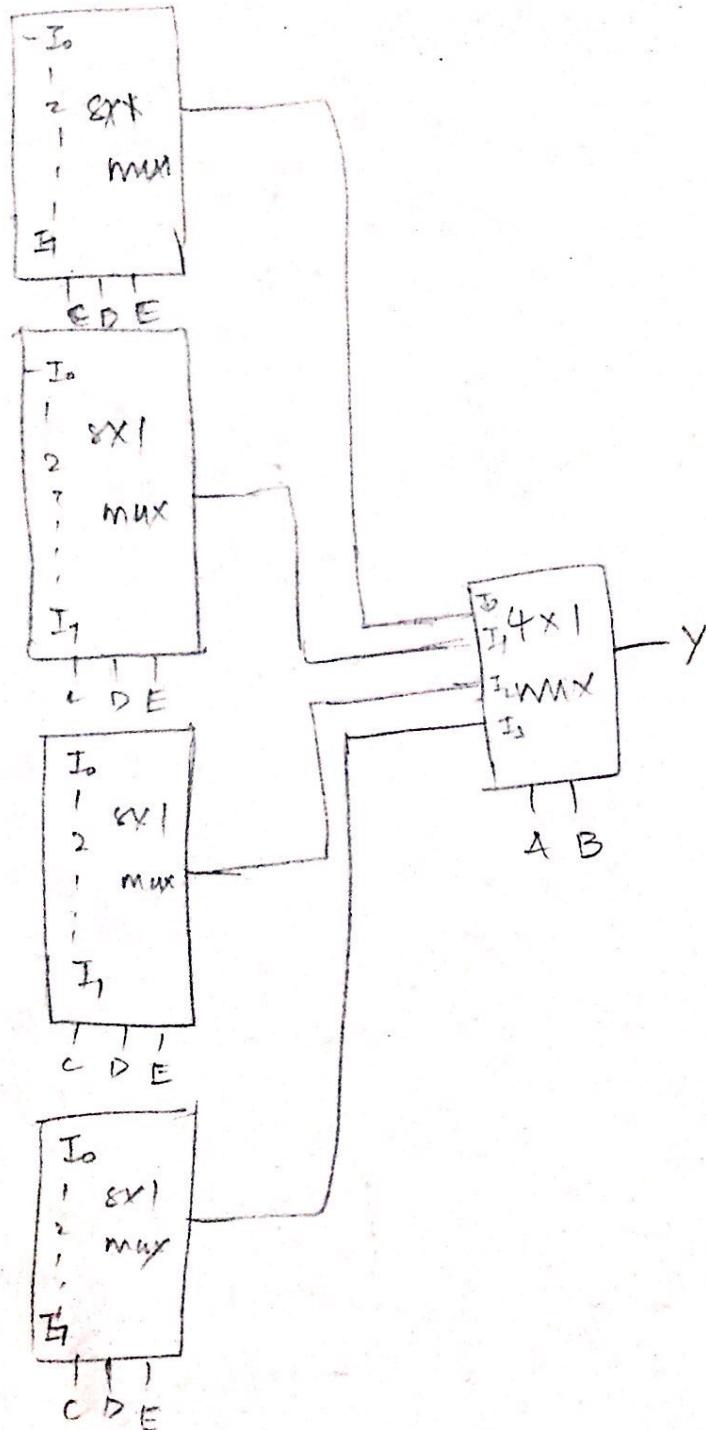Implement 32×1 mux using 4 8×1 mux
and any another mux




Demultiplexers: Inverse of Multiplexer.

Here it will have 1 input and 2^n outputs.

where n is the number of selection inputs.


$$1 \times 2^n$$

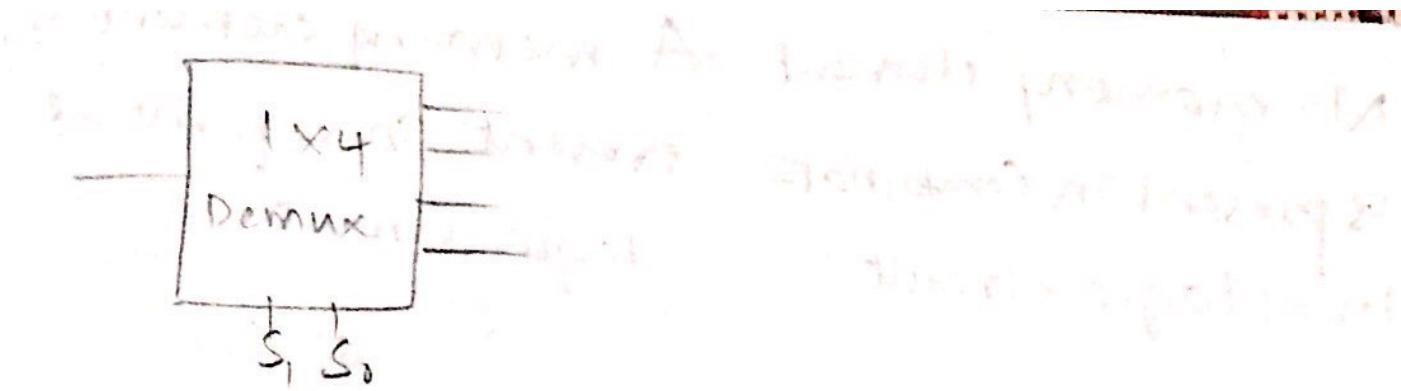

Hazards

Getting momentary erroneous output is called as hazard. To avoid hazards we need to consider all the prime implicants.

$$f(x,y,z) = \Sigma(2,3,5,7)$$

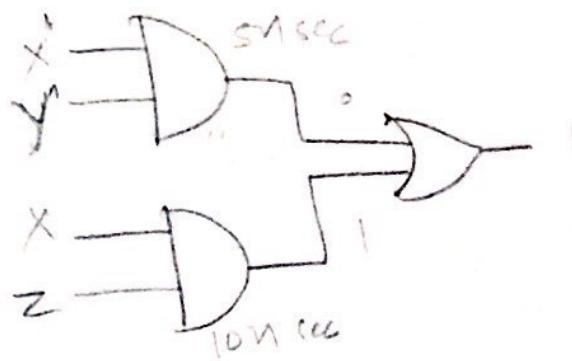

$x'y$	00	01	11	10
z	1	0	0	0
y	0	1	1	0
f	1	1	1	0

$$x'y + xz$$

