

- In a network topology, only geometrical structure of a network is considered.
- Basically, a network is an interconnection of various elements which are either active or passive.
- In the network topology, only geometrical patterns is considered but not diff. network elements.

* Elements in network topology :

1. Node! It is defined as the pt at which two or more elements are having common connection.
2. Branch! It is a line connecting a pair of nodes, the line representing a single element and series of connected elements.
3. loop! When there is more than 1 path b/w 2 nodes then it is a circuit or loop.
4. Mesh: It is a loop which does not contain any other loops in it.
5. Linear graph: It is defined as collection of nodes and branches. The nodes are joined together by branches.


* Graphs :

1. Oriented graph: If every branch of a graph has a direction or each element in the connected

graph is given direction, it is called oriented or directed graph.

→ Otherwise.


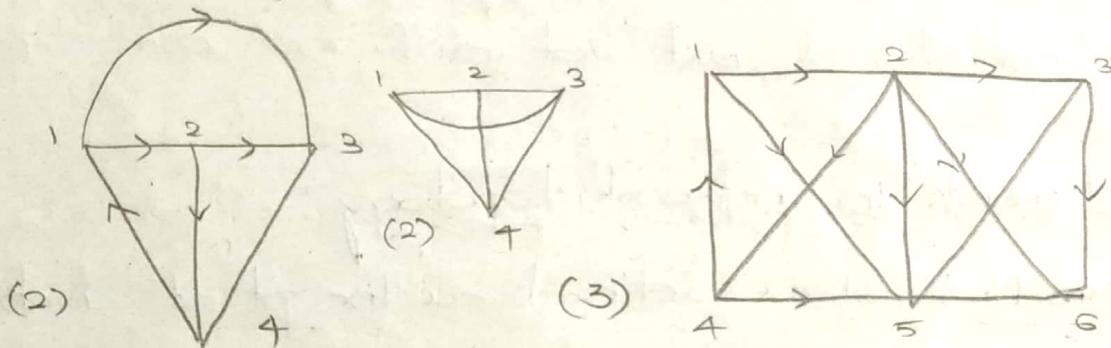
2. Planar graph: A graph is said to be planar if it can be drawn on a plane surface such that no 2 branches cross each other.




3. Non-planar graph: A non-planar graph is a graph drawn on 2D plane such that 2 or more branches intersect each other at a pt other than a node.

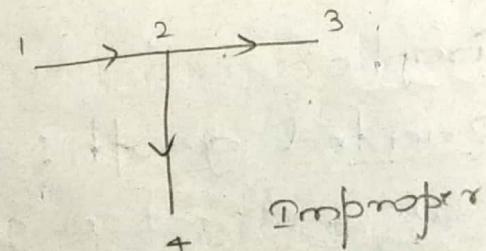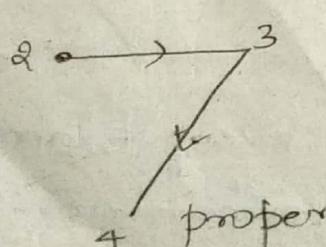4. Sub graph: It is a subset of branches & nodes of a graph. There are 2 types of subgraphs.

- If the subgraph contains branches & nodes less in no. then it is called proper subgraph.
- If the subgraph contains branches & nodes less in no. & all nodes resp. is called improper subgraph.



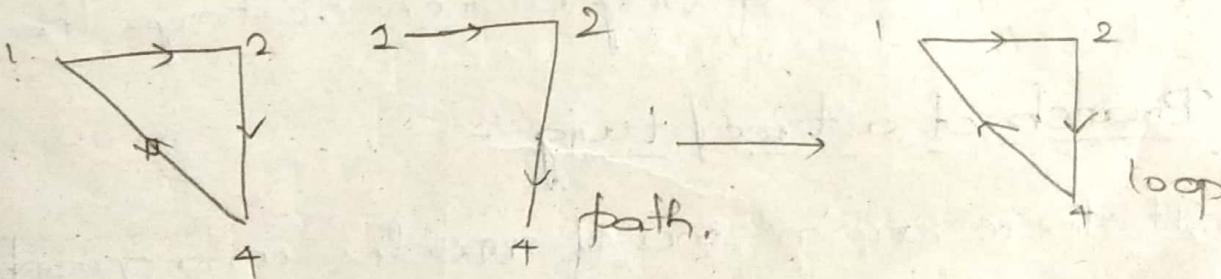
5. Path: A path is an improper subgraph.
- At terminating node, only 1 branch is incident, at the remaining nodes 2 branches are incident
6. connected graph: A graph is said to be connected if there exists a path b/w any pair of nodes.
7. loop or circuit: It is a connected subgraph of connected graph at each node of which are incident exact at 2 branches.
- If 2 terminals of a path are made to coincide it results a loop or circuit.
- There are atleast 2 branches in a loop.
- There are exactly 2 paths b/w any pair of nodes in a loop.
- The max. no. of possible branches is = to the no. of nodes.



- A node & branch are incident if the node is a terminal of branch.
- Nodes can be incident to 1 or more elements.
- The no. of branches incident on the node indicate the degree of node.

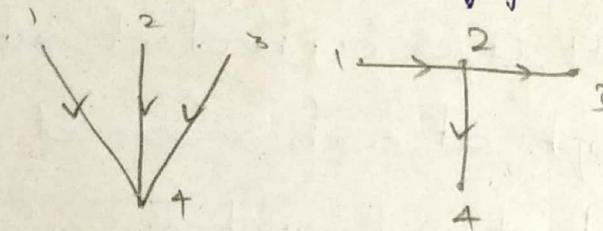8. Tree! A tree is a connected subgraph of network which consists of all the nodes of original graph but no closed path.

→ Tree contains all the nodes of graph, there exists only 1 path b/w any pair of nodes.



→ If 'n' is the no. of nodes of graph there are $n-1$ branches in the tree.

→ The tree does not contain any loop.

→ Every connected graph has at least 1 tree.

→ The min. terminal nodes in a tree are two.

→ A tree is a set of branches with every node connected to every other node in such a way that removal of any branch destroys the property.

9. Branch of a tree / twig! -


→ If there are 'n' no. of nodes in a graph then the tree of graph contains $n-1$ twigs.

10. Cotree!

→ The left over branches after forming a tree constitute a cotree.

→ Branch of cotree is called chord / link.

- A set of branches forming a complement of tree is called cotree.
- The no. of branches of a cotree is $b - (n - 1)$ where b is no. of branches of graph.
- If there exists 'm' no. of nodes vertices then rank of a graph $\approx m - 1$
- * Incidence matrix :
- An oriented graph can be completely explained or represented with the help of a matrix known as incidence matrix.
- The incidence matrix gives information abt the branches incident on which nodes, orientation at the node (whether towards/away from node).
- Types :
 - (i) complete incidence (A_a)
 - (ii) Reduced incidence (A)

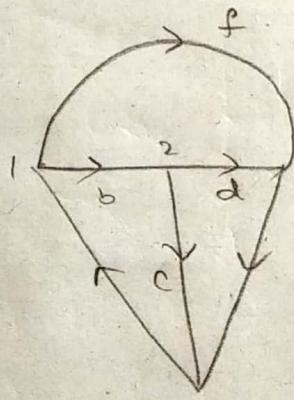

$a_{hk} = +1, 0, -1$
 $+1 \Rightarrow$ leaving
 $-1 \Rightarrow$ entering

	a	b	c	d	e	f
1	-1	+1	0	0	0	+1
2	0	-1	+1	+1	0	0
3	0	0	0	-1	+1	-1
4	+1	0	-1	0	-1	0

Proofs of (i) :-


- The sum of entries in any column is zero
- The rank of complete incidence matrix of

connected graph is $n-1$.

→ The determinant of a loop of complete incidence matrix is always zero.

→

$$\begin{array}{c|ccccc} & a & b & c & d & e \\ \hline 1 & -1 & 0 & 0 & 1 & -1 \\ 2 & 1 & -1 & 0 & 0 & 0 \\ 3 & 0 & 1 & -1 & 0 & 1 \\ 4 & 0 & 0 & 1 & -1 & 0 \end{array}$$

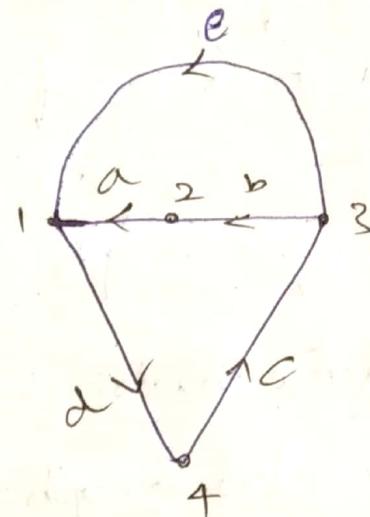

(ii) Reduced incidence matrix :

→ When any 1 row from the complete incidence matrix is eliminated by using mathematical manipulation then it is called reduced incident matrix.

29/7/19


monday

$$A^2 = \begin{bmatrix} -1 & +1 & 0 & 0 & 0 \\ 0 & -1 & +1 & +1 & 0 \\ 0 & 0 & 0 & -1 & -1 \end{bmatrix}$$

$$A^{T_2} = \begin{bmatrix} -1 & 0 & 0 \\ +1 & -1 & 0 \\ 0 & +1 & 0 \\ 0 & +1 & -1 \\ 0 & 0 & -1 \end{bmatrix}$$

$$\det(AA^T) = 8$$

→ The no. of possible trees is $\det |AA^T|$

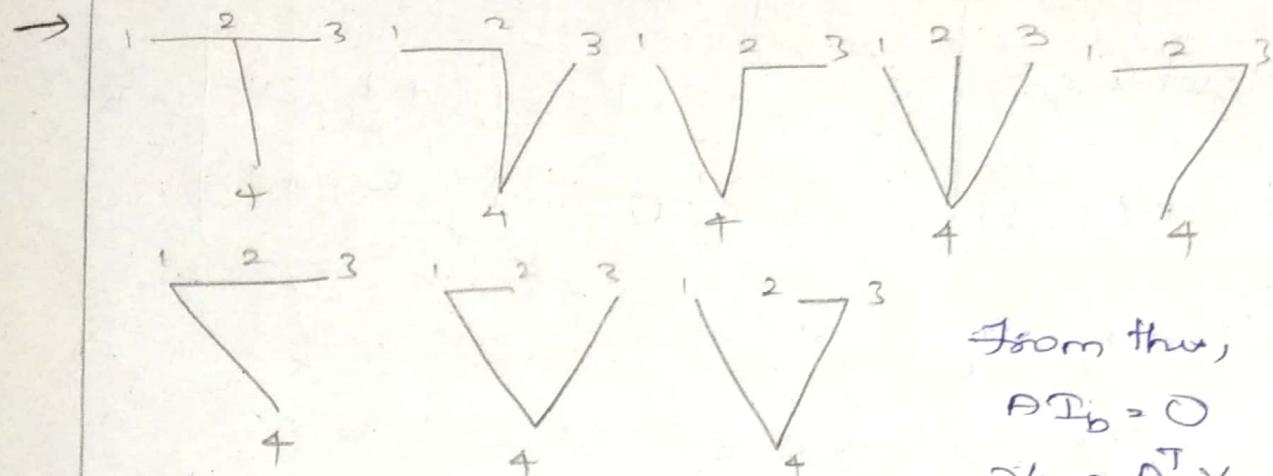

From this,


$$A \mathbf{I}_b = 0$$

$$\mathbf{v}_b = A^T \mathbf{v}_n$$

* loop/circuit matrix: $(B_a) l \times b$



$$b_{hk} = +1; -1; 0$$

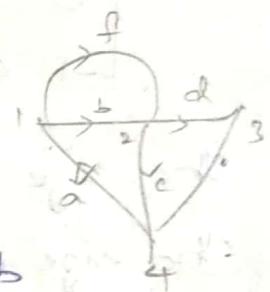- $b_{hk} = +1 \rightarrow$ if branch k is in loop & its orientation coincides with loop
- $-1 \rightarrow$ if branch k is in loop & its orientation does not coincide with loop orientation
- $0 \rightarrow$ if the branch k is not in the loop.



* Fundamental circuit matrix / fundamental tie-set:
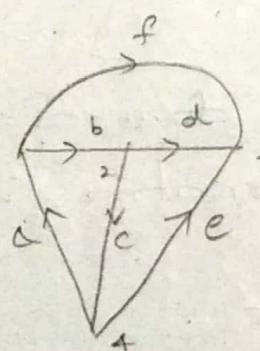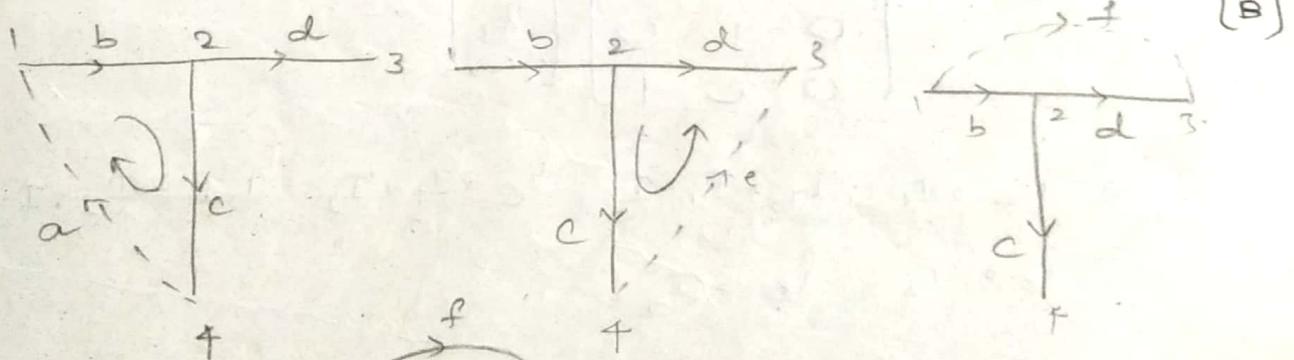
$$[B] = \begin{matrix} 1 & b & 2 & d & 3 \\ 1 & \rightarrow & 2 & \rightarrow & 3 \\ 1 & & & & \end{matrix}$$



$$\begin{aligned}
 & \text{tieset}(ab,c) \stackrel{\mathbb{I}_1}{=} \begin{bmatrix} a & b & c & d & e & f \\ +1 & +1 & +1 & 0 & 0 & 0 \end{bmatrix} \\
 & \text{tieset}(e,c,d) \stackrel{\mathbb{I}_2}{=} \begin{bmatrix} 0 & 0 & +1 & -1 & +1 & 0 \end{bmatrix} = B \\
 & \text{tieset}(f,b,d) \stackrel{\mathbb{I}_3}{=} \begin{bmatrix} 0 & +1 & 0 & -1 & 0 & +1 \end{bmatrix}
 \end{aligned}$$

$$\rightarrow B, B_T, B_L$$

bcd : aef

$$\begin{bmatrix} 1 & 1 & 0 & : & 1 & 0 & 0 \\ 0 & 1 & -1 & : & 0 & 1 & 0 \\ -1 & 0 & -1 & : & 0 & 0 & 1 \end{bmatrix}$$

\rightarrow The size of tie-set matrix is $b-(n-1) \times b$ [B]

\rightarrow The size of twig matrix $B_T = b-(n-1) \times n-1$

\rightarrow The size of link matrix $B_L = b-(n-1) \times b-(n-1)$

\rightarrow The branch current $i_b = B^T I_L$ (mesh analysis)

$$i_b = \begin{bmatrix} 1 & 0 & 0 \\ 1 & 0 & -1 \\ 1 & 1 & 0 \\ 0 & -1 & -1 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} \mathbb{I}_1 \\ \mathbb{I}_2 \\ \mathbb{I}_3 \end{bmatrix}$$

$$\Rightarrow i_a = \mathbb{I}_1; i_b = \mathbb{I}_1 - \mathbb{I}_3 \quad i_c = \mathbb{I}_1 + \mathbb{I}_2 \quad i_d = -\mathbb{I}_2 - \mathbb{I}_3$$

$$i_e = \mathbb{I}_2; i_f = \mathbb{I}_3$$

\rightarrow KVL equations can be formed from tie-set matrix using rows of tie-set matrix, we get

$$V_a + V_b + V_c = 0$$

$$V_b - V_{dl} + V_c = 0$$

$$-V_b - V_{dl} + V_f = 0$$

$$BV_b = 0$$

$$\rightarrow \sum_{k=1}^b V_{ik} = 0 \quad \therefore \sum_{k=1}^b b_{ik} V_{ik} = 0 \quad i = 1, \dots, l.$$

$$b_{ik} = +1; -1$$

23/7/2019

Tuesday

* Orthogonal relationship:

$$\rightarrow A_a B_a^T = A_a^T B_a = 0$$

$$\rightarrow AB^T = A^T B = 0$$

* Cut-set matrix


→ A connected graph can be separated into 2 parts by removing certain branches of graph. This is equal to cutting a graph into 2 parts. This is referred as cut-set.

→ A cut-set is a minimal set of branches of a connected graph such that after removal of these branches, graph gets separated into 2 distinct parts each of which a connected graph, if the condition that replacing any 1 branch from the cut-set makes the graph connected.

→ Cutset matrix is represented by Q_a .


→ The size of cutset matrix is $c \times b$

	a	b	c	d	e
f-cutset (a,b)	+1	-1	0	0	0
f-cutset (b,c,d)	0	+1	-1	-1	0
f-cutset (d,e)	0	0	0	+1	+1
f-cutset (a,c,e)	-1	0	+1	0	-1
f-cutset (b,c,e)	0	-1	+1	0	-1
f-cutset (a,c,d)	+1	0	-1	-1	0

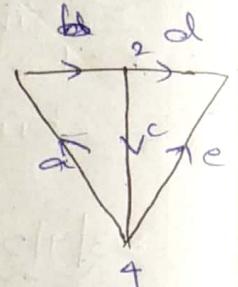

→

	a	b	c	d	e
f-cutset ₁ (b,a)	-1	+1	0	0	0
f-cutset ₂ (d,e)	0	0	0	+1	-1
f-cutset ₃ (c,a,e)	-1	0	+1	0	+1

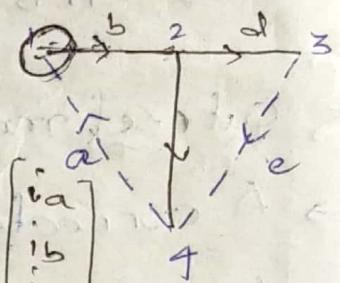

→ The above matrix is denoted by Q

→ The size of Q is $n-1 \times b$ (nodal analysis)

→ $Q \rightarrow Q_T : Q_L \rightarrow [u : Q_L]$

$$\begin{matrix} & b & d & c & : & a & e \\ & 1 & 0 & 0 & & -1 & 0 \\ & 0 & 1 & 0 & & 0 & -1 \\ & 0 & 0 & 1 & & -1 & +1 \end{matrix}$$

$$Q^T I_b = 0$$

→ The size of Q_T is $(n-1) \times (n-1)$

→ The size of Q_L is $(n-1) \times b-(n-1)$


$$V_b = Q^T V_f$$

→ We get KCL equations from this, i.e.,


$$\begin{aligned} -i_a + i_b &= 0 \\ i_d - i_e &= 0 \\ -i_a + i_c + i_e &= 0 \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\} \text{KCL}$$

→ $V_a = -V_1 - V_4$; $V_b = V_1$; $V_c = V_4$; $V_d = V_3$; $V_e = V_4 - V_3$

Q.

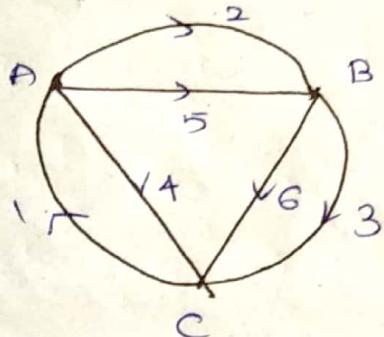

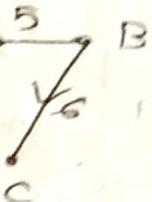find CIM, RIM, no. of possible trees, fundamental set, fundamental cut-set. Consider $A \xrightarrow{5} B$



26/7/2019

Friday

Sol: CIM: $n \times b$

$$\begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 \\ A & [-1 & +1 & 0 & +1 & +1 & 0] \\ B & [0 & -1 & +1 & 0 & -1 & +1] \\ C & [+1 & 0 & -1 & -1 & 0 & -1] \end{matrix}$$


$$\left(\begin{bmatrix} -1 & +1 & 0 & +1 & 0 \\ 0 & -1 & +1 & 0 & -1 \\ +1 & 0 & -1 & -1 & 0 \end{bmatrix} \right) \left(\begin{bmatrix} -1 & 0 & +1 \\ +1 & -1 & 0 \\ 0 & +1 & -1 \\ +1 & 0 & -1 \\ +1 & -1 & 0 \\ 0 & +1 & -1 \end{bmatrix} \right)$$

$$\Rightarrow \begin{pmatrix} 1+1+1+1 & -1-1 & -1-1 \end{pmatrix} \times$$

-1


$$\left[\begin{array}{cccccc} -1 & +1 & 0 & +1 & +1 & 0 \\ 0 & -1 & +1 & 0 & -1 & +1 \end{array} \right] \left[\begin{array}{c} -1 & 0 \\ +1 & -1 \\ 0 & +1 \\ +1 & 0 \\ +1 & -1 \\ 0 & +1 \end{array} \right] = 12.$$

No. of possible trees = 12

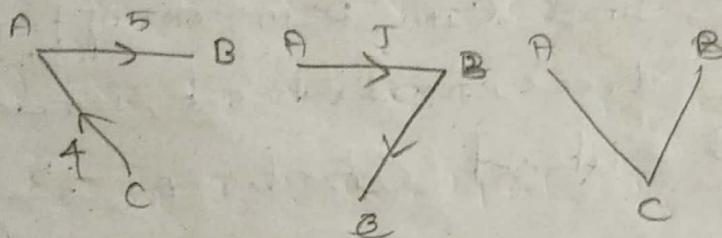

Fundamental tieset:-

Consider a tree

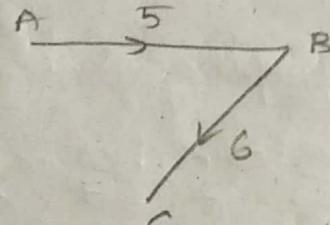

$$\begin{aligned}
 \text{tieset}(1, 5, 6) &= \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ +1 & 0 & 0 & 0 & +1 & +1 \end{bmatrix} \\
 \text{tieset}(2, 5, 6) &= \begin{bmatrix} 0 & +1 & 0 & 0 & -1 & 0 \end{bmatrix} \\
 \text{tieset}(3, 5, 6) &= \begin{bmatrix} 0 & 0 & +1 & 0 & 0 & -1 \end{bmatrix} \\
 \text{tieset}(4, 5, 6) &= \begin{bmatrix} 0 & 0 & 0 & +1 & -1 & -1 \end{bmatrix}
 \end{aligned}$$


$B_T : B_L$

$$\begin{matrix}
 5 & 6 & : & 1 & 2 & 3 & 4 \\
 1 & 1 & & 1 & 0 & 0 & 0 \\
 -1 & 0 & & 0 & 1 & 0 & 0 \\
 0 & -1 & & 0 & 0 & 1 & 0 \\
 -1 & -1 & & 0 & 0 & 0 & 1
 \end{matrix}$$

Fundamental cutset : Ω (2×6)

$$\text{CC}(5,1,2,4) \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ -1 & +1 & 0 & +1 & +1 & 0 \end{bmatrix}$$
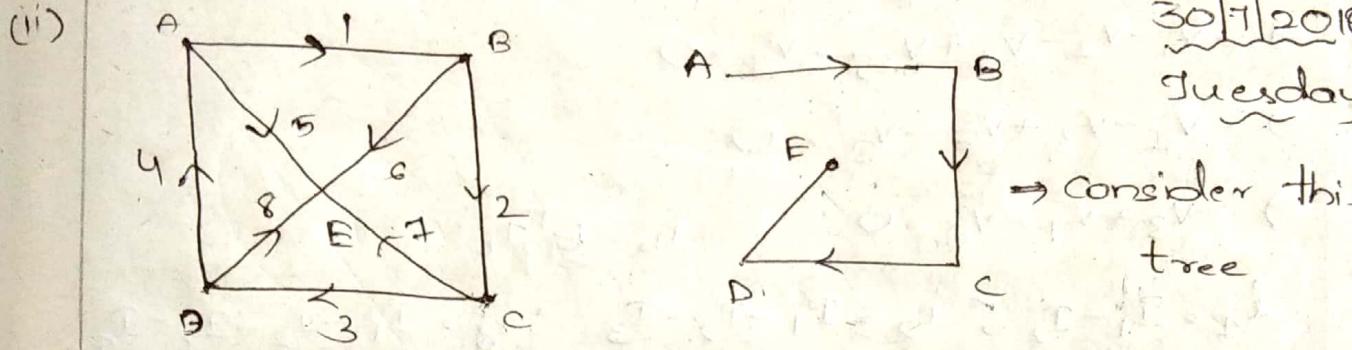
$$\text{CS}(6,1,3,4) \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ -1 & 0 & +1 & +1 & 0 & -1 \end{bmatrix}$$



CIM: $n \times b = 5 \times 8$ (Aa)

$$A \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ +1 & 0 & 0 & -1 & +1 & 0 & 0 & 0 \end{bmatrix}$$

$$B \begin{bmatrix} -1 & +1 & 0 & 0 & 0 & 0 & +1 & 0 & 0 \end{bmatrix}$$

$$C \begin{bmatrix} 0 & -1 & +1 & 0 & 0 & 0 & +1 & 0 \end{bmatrix}$$

$$D \begin{bmatrix} 0 & 0 & -1 & +1 & 0 & 0 & 0 & +1 \end{bmatrix}$$

$$E \begin{bmatrix} 0 & 0 & 0 & 0 & -1 & -1 & -1 & -1 \end{bmatrix}$$

RIM: $n-1 \times b = 4 \times 8$ (A)

$$\det |AA^T| = 45$$

Fundamental tieset : $b-(n-1) \times b$

$$(B) \quad 1 \quad 2 \quad 3 \quad 4 \quad 5 \quad 6 \quad 7 \quad 8$$

$$\text{I tieset } 1(4,1,2,3,8) \begin{bmatrix} +1 & +1 & +1 & +1 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$\text{II tieset } 2(5,1,2,3,8) \begin{bmatrix} -1 & -1 & -1 & 0 & +1 & 0 & 0 & -1 \end{bmatrix}$$

$$\text{III tieset } 3(6,1,2,3,8) \begin{bmatrix} 0 & -1 & -1 & 0 & 0 & +1 & 0 & -1 \end{bmatrix}$$

$$\text{IV tieset } 4(7,1,2,3,8) \begin{bmatrix} 0 & 0 & -1 & 0 & 0 & 0 & +1 & -1 \end{bmatrix}$$

$$B = B_T : B_L$$

$$B_T = b - (n-1) \times n-1 \rightarrow 4 \times 4$$

$$B_L = b - (n-1) \times b - (n-1) \rightarrow 4 \times 4$$

$$BV_b = 0$$

$$\rightarrow v_1 + v_2 + v_3 + v_4 = 0$$

$$\rightarrow -v_1 - v_2 - v_3 + v_5 - v_8 = 0$$


$$\rightarrow -v_2 - v_3 + v_6 - v_8 = 0$$

$$\rightarrow -v_3 + v_7 - v_8 = 0 \quad i_b = B^T \underline{I}_L$$

$$i_1 = I_1 - I_2 ; \quad i_2 = I_1 - I_2 - I_3 ; \quad i_3 = I_1 - I_2 - I_3 - I_4$$

$$i_4 = I_1 ; \quad i_5 = I_2 ; \quad i_6 = I_3 ; \quad i_7 = I_4 ; \quad i_8 = -I_2 - I_3 - I_4$$

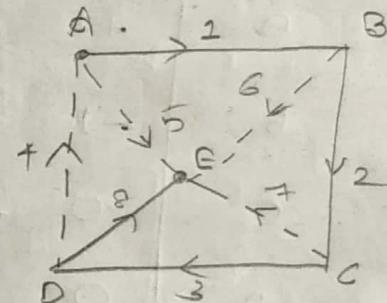Fundamental cutset: $\mathbb{Q} (n-1) \times b = 4 \times 8$



	1	2	3	4	5	6	7	8
v_1 , cutset 1(1, 4, 5)	+1	0	0	-1	+1	0	0	0
v_8 , cutset 2(8, 5, 6, 7)	0	0	0	0	+1	+1	+1	+1
v_2 , cutset 3(2, 4, 5, 6)	0	+1	0	-1	+1	+1	0	0
v_4 , cutset 4(3, 6, 5, 7)	0	0	+1	-1	+1	+1	+1	0

$$\Theta_T : \mathbb{Q}_L \rightarrow \mathbb{I} : \mathbb{Q}_L$$

$$\Theta_T \Rightarrow (n-1) \times (n-1) \Rightarrow 4 \times 4$$

$$\mathbb{Q}_L \rightarrow (n-1) \times b - (n-1) \Rightarrow 4 \times 4$$

$$Q I_b = 0$$

$$i_1 - i_4 + i_5 = 0; i_5 + i_6 + i_7 + i_8 = 0$$

$$i_2 - i_4 + i_5 + i_6 = 0; i_3 - i_4 + i_5 + i_6 + i_7 = 0$$

$$v_1 = V_1; v_2 = V_8; v_3 = V_8;$$

$$v_1 = V_1; v_2 = V_2; v_3 = V_3; v_4 = -V_1 - V_2 - V_3$$

$$v_5 = V_1 + V_2 + V_3 + V_4; v_6 = V_2 + V_3 + V_8; v_7 = V_3 + V_8$$

$$v_8 = V_8$$

2/8/2019 Part-2 Magnetic Circuits

Friday

- * Coupled circuits :
 - When energy transfer takes place from one to another without any electrical connection.
 - Coupled circuits are used in network analysis and synthesis. E.g. Transformer and gyrator.
 - The requirements for induction -
 - (i) Coil or conductor.
 - (ii) permanent magnet or electromagnet.
 - (iii) Relative motion b/w coil & magnet
(achieved by moving coil w.r.t. flux, moving magnet w.r.t. coil).
 - The phenomena of cutting flux lines by the conductor to get the induced emf is called electromagnetic induction.
 - Faraday 1st law : Whenever the no. of magnetic lines of force (flux) linking with a coil changes, an emf gets induced in that coil or conductor.

→ Faraday's 2nd law! The magnitude of induced emf is directly proportional to rate of change of flux linkages.

$$\text{Flux linkage} = N \times \phi$$

$$t = t_1, \phi_1 \rightarrow N\phi_1$$

$$t = t_2, \phi_2 \rightarrow N\phi_2$$

$$e \propto \frac{N\phi_2 - N\phi_1}{t_2 - t_1}$$

$$e \propto \frac{N\phi}{dt} \rightarrow e = kN \frac{d\phi}{dt} \rightarrow e = -N \frac{d\phi}{dt} \quad [k=1]$$

→

$$\phi \propto I$$

$$\phi = kI$$

$$e = -N \frac{d\phi}{dt}$$

$$e = -Nk \frac{dI}{dt} \rightarrow e = -\left(\frac{N\phi}{I}\right) \frac{dI}{dt} \rightarrow e = -L \frac{dI}{dt}$$

k = coefficient of self inductance.

→

$$\phi_{12} \propto I_1$$

$$\phi_{12} = kI_1 \rightarrow k = \frac{\phi_{12}}{I_1}$$

$$e = -N \frac{d\phi}{dt}$$


$$V_2 = -N_2 \frac{d\phi_{12}}{dt}$$

$$= -N_2 k \frac{dI_1}{dt}$$

$$V_2 = -\frac{N_2 \phi_{12} \frac{dI_1}{dt}}{I_1}$$

$$V_2 = -M_{12} \frac{dI_1}{dt} \quad \text{by}$$
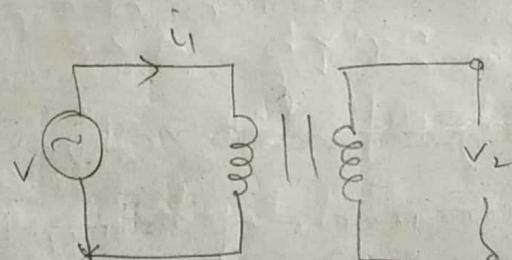
$$V_1 = -M_{21} \frac{dI_2}{dt} \quad [M_{12}, M_{21} \text{ are mutual inductances}]$$



$$\rightarrow M_{12} = M_{21} = M$$

$$N_1 \times M = \frac{N_2 \phi_{12}}{I_1} \times \frac{N_1 \phi_{21}}{I_2}$$

$$= \frac{N_2 k_1 \phi_1}{I_1} \times \frac{N_1 k_2 \phi_2}{I_2} \quad [\because \phi_{12} = k_1 \phi_1; \phi_{21} = k_2 \phi_2]$$

$$= k_1 k_2 \frac{N_1 \phi_1}{I_1} \frac{N_2 \phi_2}{I_2}$$

$$M^2 = k_1 k_2 H L_2$$

$$M = \sqrt{k_1 k_2} \sqrt{H L_2}$$

$$M = k \sqrt{H L_2}$$

$\Rightarrow k = \frac{M}{\sqrt{H L_2}}$ \rightarrow coefficient of coupling.

- Q. When one of magnetically coupled coils has a current of 3A. The resultant fluxes ϕ_{11} & ϕ_{12} are 0.3 mWb & 0.5 mWb. If $N_1 = 600$, $N_2 = 1200$ find H , L_2 , M , k .

Sol:

$$I_1 = 3A$$

$$\phi_{11} = 0.3 \text{ mWb}$$

$$\phi_{12} = 0.5 \text{ mWb}$$

$$N_1 = 600$$

$$N_2 = 1200$$

$$\phi_r = \phi_{11} + \phi_{12}$$

$$\rightarrow 0.3 + 0.5 = 0.8 \text{ mWb}$$

$$L_2 = \frac{N_1 \phi_r}{I_1} = \frac{600 \times 0.8 \times 10^{-3}}{3} = \frac{0.6 \times 0.8}{3}$$

$$= 0.2 \times 0.8$$

$$= 0.16 \text{ Henry}$$

$$k = \frac{\phi_{12}}{\phi_r} = \frac{0.5}{0.8} = 0.625$$

$$M = +200 \frac{N_2 \phi_{12}}{I}$$

$$= 200 \text{ mH}$$

$$M = k \sqrt{L_1 L_2}$$

$$L_2 = \frac{M^2}{k^2 I} \Rightarrow L_2 = \frac{(200 \times 10^{-3})^2}{(0.625)^2 \times 0.16}$$

$$= 640 \text{ mH}$$

- Q. If a coil of $L_1 = 100 \text{ mH}$ is magnetically coupled to another coil of $L_2 = 400 \text{ mH}$ with the coefficient of coupling is 0.6. The second coil has 1500 turns, $I = 4 \sin 200t \text{ Amp}$. Determine the voltage at the coil and flux ϕ_1 .

Sol:

$$L_1 = 100 \text{ mH}, L_2 = 400 \text{ mH}$$

$$k = 0.6, I = 4 \sin 200t \text{ Amp}$$

$$N_2 = 1500$$

$$M = k \sqrt{L_1 L_2}$$

$$= 0.6 \sqrt{100 \times 10^{-3} \times 400 \times 10^{-3}}$$

$$= 0.6 \sqrt{0.1 \times 0.4}$$

$$= 0.6 \sqrt{0.04}$$

$$= 0.6 \sqrt{4 \times 10^{-2}} = 0.6 \times 10^{-1} \times 2$$

$$= 0.12 \times 10^{-1}$$

$$= 0.12 = 120 \text{ mH}$$

$$V_2 = M \frac{d\phi}{dt} = 120 \times 10^{-3} \times \frac{d}{dt} (4 \sin 200t)$$

$$= 120 \times 10^{-3} \times 4 \times 200 \times 4 \cos 200t$$





$$= 96 \cos 200t$$

$$M = \frac{N_2 \phi_{12}}{I_1}$$

$$M = \frac{N_2 K \phi_1}{I_1} \Rightarrow \phi_1 = \frac{MI_1}{N_2 K}$$

$$\phi_1 = 0.5333 \sin 200t \text{ mWb.}$$

* Dot convention:

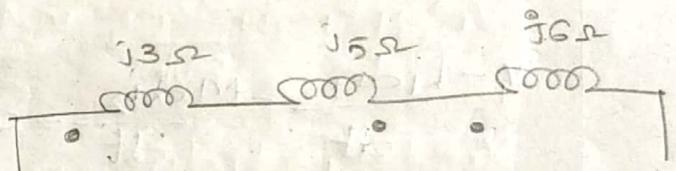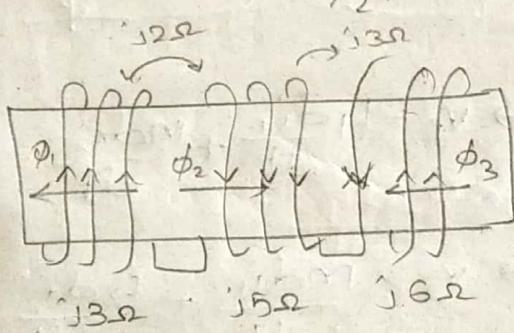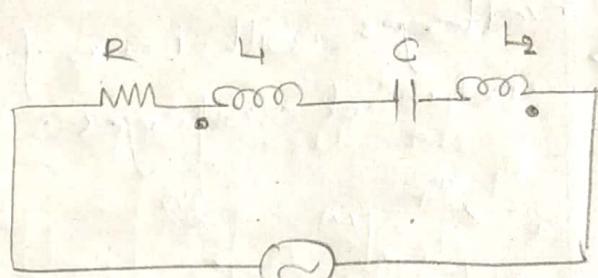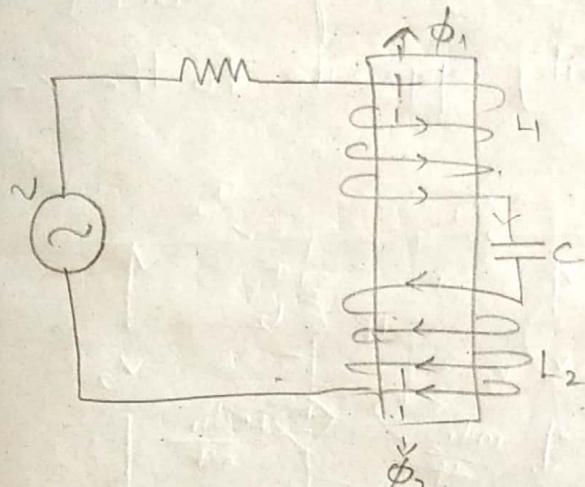


- The signs of mutually induced voltage depends on the winding of coils.
- But it is very inconvenient to supply the information about winding of coils. Hence, dot conventions are used for indicating direction of coil windings.
- If a positive current enters into the dots of both the coils ^{or out of both coils} then mutually induced emf of both the coils add to the self induced voltages. Hence mutually induced voltages will have same polarity.

as that of self induced voltage.

6/8/2019


Tuesday

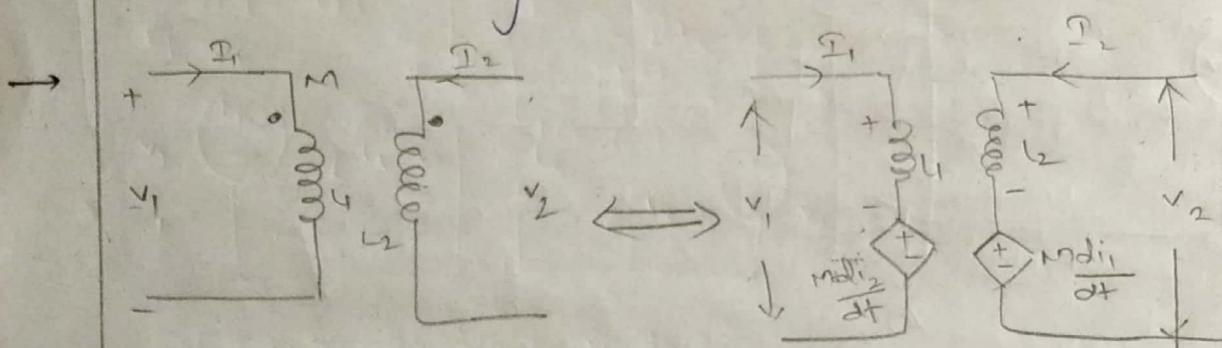- If the current enters into or out of the dot in 1st coil & in the other coil current flows out of or into the dot then the mutually induced voltages will have polarity opposite to the self induced voltage.



$$v_1 - L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = 0 \Rightarrow v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

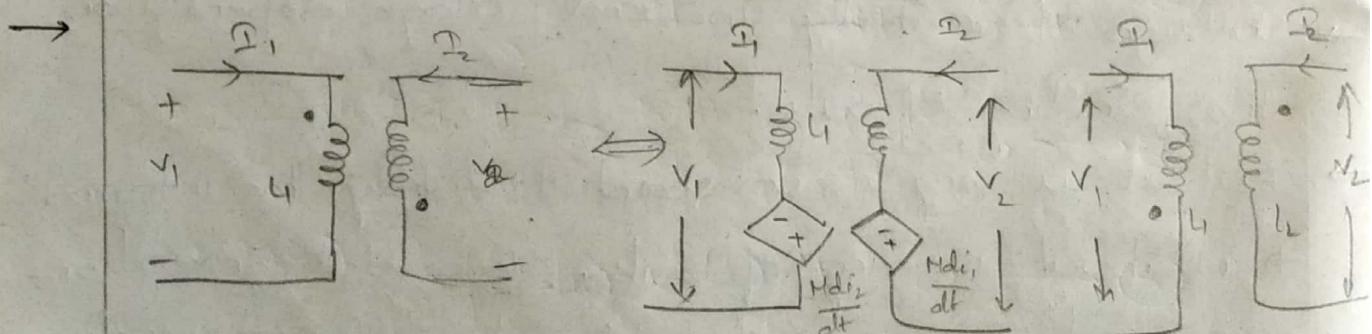
$$v_2 - L_2 \frac{di_2}{dt} - M \frac{di_1}{dt} = 0 \Rightarrow v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



$$v_1 - L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = 0 \Rightarrow v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 - L_2 \frac{di_2}{dt} + M \frac{di_1}{dt} = 0 \Rightarrow v_2 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

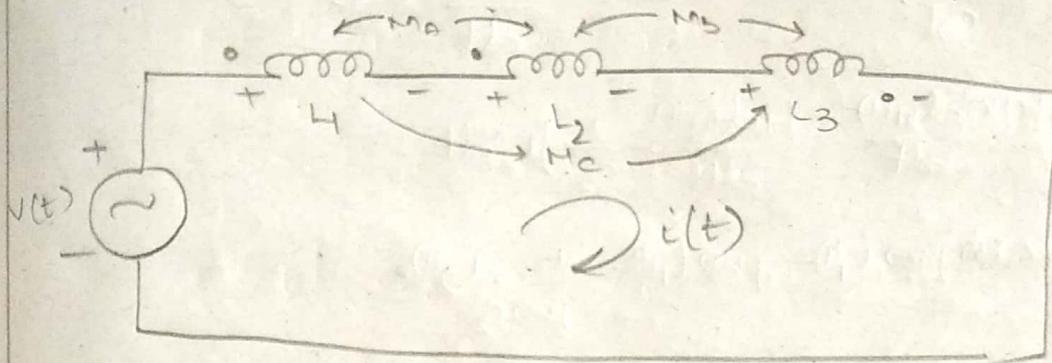a. Write the eq. for the figure showing network.




$$V(t) - L_1 \frac{di(t)}{dt} - M_A \frac{di(t)}{dt} - L_2 \frac{di(t)}{dt} + M_B \frac{di(t)}{dt} - L_3 \frac{di(t)}{dt} \\ + M_C \frac{di(t)}{dt} - M_A \frac{di(t)}{dt} + M_B \frac{di(t)}{dt} + M_C \frac{di(t)}{dt} + \\ \frac{M_B di(t)}{dt} = 0.$$

$$V(t) = (L_1 + L_2 + L_3 + 2M_A - 2M_B - 2M_C) \frac{di(t)}{dt}$$

$$\text{Effective inductance} = L_1 + L_2 + L_3 + 2M_A - 2M_B - 2M_C$$

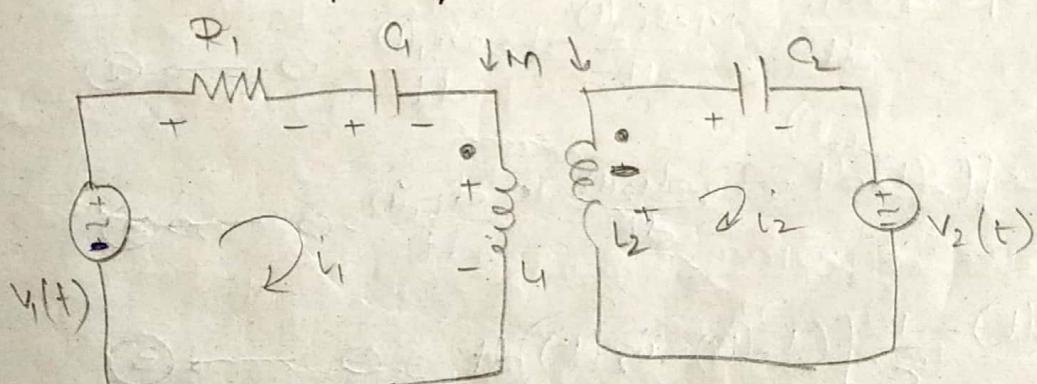b. Write the loop equations for the network.



~~$$V_1 - i_1 R_1 - \frac{1}{C_1} \int i_1 dt - L_1 \frac{di_1}{dt} + M \frac{di_2}{dt} = 0$$~~

$$V_1 i_1 R_1 - \frac{1}{j\omega C_1} - j\omega L_1 i_1 + j\omega M i_2 = 0$$


$$V_1 = \left(R_1 + \frac{1}{j\omega C_1} + j\omega L_1 \right) I_1 - j\omega I_2$$

$$Q = \frac{Q}{V} = \frac{i_1 t}{C_1 V}$$

$$-L_1 \frac{di_2(t)}{dt} - \frac{1}{C_2} \int i_2(t) dt - v_2 + M \frac{di_1(t)}{dt} = 0$$

$$v_2 = M \frac{di_1(t)}{dt} - L_1 \frac{di_2(t)}{dt} - \frac{1}{C_2} \int i_2(t) dt$$
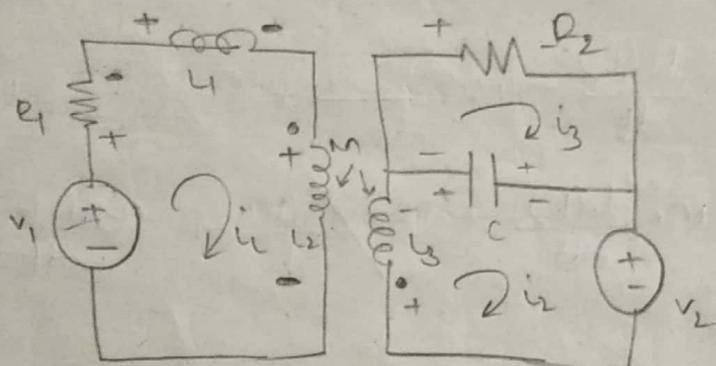
$$v_2 = M j \omega i_1(t) - j \omega L_1 i_2(t) - \frac{1}{j \omega C_2} i_2(t)$$



$$v_1 + i_1 R_1 - L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_1 - i_1 R_1 - L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = R_2 \frac{di_2}{dt}$$

$$v_1 - i_1 R_1 - L_1 \frac{di_1(t)}{dt} - M \frac{di_2(t)}{dt} - L_2 \frac{di_1(t)}{dt} = 0 \rightarrow \textcircled{1}$$

$$-v_2 - \frac{1}{C} \int (i_2(t))^{i_3(t)} dt - L_3 \frac{di_2(t)}{dt} - M \frac{di_1(t)}{dt} = 0 \rightarrow \textcircled{2}$$

$$-R_2 i_3(t) - \frac{1}{C} \int (i_3(t) - i_2(t)) dt = 0 \rightarrow \textcircled{3}$$

9/8/2019

Friday

series aiding \rightarrow series (cumulative coupling)

series opposing \rightarrow series (differential coupling)

* Series aiding:

$I_1 = I_2 = I$ since it is in series.

$$V_1 = -L_1 \frac{dI_1}{dt} = -L_1 \frac{dI}{dt}$$


$$V_2 = -L_2 \frac{dI_2}{dt} = -L_2 \frac{dI}{dt}$$

$$V_3 = -M \frac{dI_2}{dt} = -M \frac{dI}{dt}$$

$$V_4 = -M \frac{dI_1}{dt} = -M \frac{dI}{dt}$$

$$V = V_1 + V_2 + V_3 + V_4$$
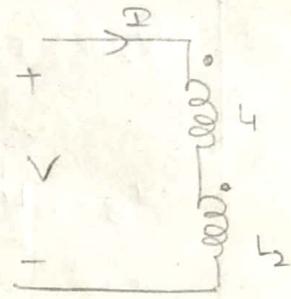
$$= -(L_1 + L_2 + 2M) \frac{dI}{dt} \Rightarrow L_{\text{eff}} = L_1 + L_2 + 2M$$




→ Two coils are connected in series and the current through the 2 coils is in same direction in order to produce flux in the same direction. Such coupling is termed as series aiding.

* Series opposing:

→ Two coils are connected in series and the current through the 2 coils are in opposite in order to produce fluxes in opposite direction. Such coupling is termed as series opposing.

$$I_1 = I_2 = I$$
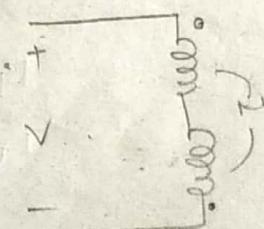
$$V_1 = -L_1 \frac{dI_1}{dt} = -L_1 \frac{dI}{dt}$$



$$V_2 = -L_2 \frac{dI_2}{dt} = L_2 \frac{dI_1}{dt}$$

$$V_3 = M \frac{dI_2}{dt} = M \frac{dI}{dt}$$


$$V_4 = M \frac{dI_1}{dt} = M \frac{dI}{dt}$$

$$V_1 + V_2 + V_3 + V_4 \rightarrow V$$

$$V = -(L_1 + L_2 - 2M) \frac{dI}{dt}$$

$$L_{\text{eff}} = L_1 + L_2 - 2M$$

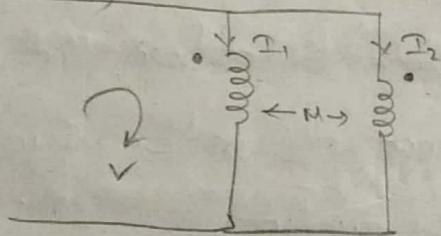- parallel aiding → parallel (cumulative coupling)
 * parallel opposing → parallel (differential coupling)
 * parallel aiding!



$$I = I_1 + I_2$$

$$V - L_1 \frac{dI_1}{dt} - L_2 \frac{dI_2}{dt} = 0$$

$$V = j\omega L_1 I_1 + j\omega M I_2 \rightarrow (1)$$

$$V = j\omega L_2 I_2 + j\omega M I_1 \rightarrow (2)$$

$$(1) \rightarrow (2)$$

$$\Rightarrow j\omega L_1 I_1 + j\omega M I_2 = j\omega L_2 I_2 + j\omega M I_1 \rightarrow (3)$$

$$I = I_1 + I_2 \Rightarrow I_2 = I - I_1 \rightarrow (4)$$

Sub (4) in (3)

$$j\omega L_1 I_1 + j\omega M(I - I_1) = j\omega L_2(I - I_1) + j\omega M I_1$$

$$L_1 I_1 + M I - M I_1 = L_2 I - L_2 I_1 + M I_1$$

$$L_1 I_1 + M I - M I_1 + L_2 I_1 - M I_1 = L_2 I$$

$$\Rightarrow \frac{I_1 - (L_2 - M)I}{L_1 + L_2 - 2M} \quad \textcircled{5}$$

From eq (4), we get $I_2 = I - I_1$

$$\Rightarrow I_2 = I - \frac{(L_2 - M)I}{L_1 + L_2 - 2M}$$

$$\Rightarrow \mathcal{D} = \frac{I(L_1 + L_2 - 2M) - (L_2 - M)I}{L_1 + L_2 - 2M}$$

$$\Rightarrow \frac{IL_1 + I\cancel{L_2} - 2MI - L_2\cancel{I} + MI}{L_1 + L_2 - 2M}$$

$$\Rightarrow I_2 = \frac{(L_1 - M)I}{L_1 + L_2 - 2M} \quad \textcircled{6}$$

Sub (5) & (6) in eq (1)

$$V = j\omega \left[4 \left(\frac{(L_2 - M)I}{L_1 + L_2 - 2M} \right) + j\omega M \left(\frac{(L_1 - M)I}{L_1 + L_2 - 2M} \right) \right] \\ = \frac{j\omega I}{L_1 + L_2 - 2M} \left[\frac{4L_2 - L_1M + ML_1 - M^2}{L_1 + L_2 - 2M} \right]$$


$$V = j\omega \left[\frac{4L_2 - M^2}{L_1 + L_2 - 2M} \right] I$$

$$L_{eff} = \frac{4L_2 - M^2}{L_1 + L_2 - 2M}$$

Two coils connected in \parallel^{el} such that fluxes produced by the coils act in same direction such connection is called parallel aiding

* Parallel opposing!

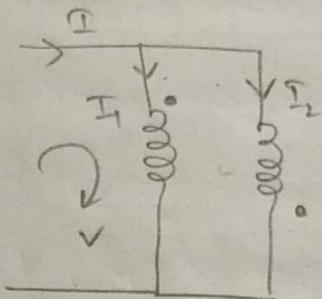Two coils connected in Π el such that fluxes produced by the coils act in opposite direction. Such connection is called parallel opposing.



$$I = I_1 + I_2$$

$$V - L_1 \frac{dI}{dt} = 0$$

$$V = j\omega L_1 I_1 - j\omega M I_2 \rightarrow \textcircled{1}$$

$$\textcircled{1} - \textcircled{2} \quad V = j\omega L_2 I_2 - j\omega M I_1 \rightarrow \textcircled{2}$$

$$\cancel{j\omega [L_1 I_1 - M I_2]} \Rightarrow j\omega [L_2 I_2 - M I_1] \rightarrow \textcircled{3}$$

$$I_2 \Rightarrow I_2 = I_1 \rightarrow \textcircled{4}$$

Sub $\textcircled{4}$ in $\textcircled{3}$,

$$L_1 I_1 - M I_1 + M I_1 = L_2 I_1 - L_2 I_1 - M I_1$$

$$\cancel{M I_1} \Rightarrow I_1 [L_1 + M + M + L_2] = (L_2 + M) I_1$$

$$\Rightarrow I_1 = \frac{(L_2 + M) I_1}{L_1 + L_2 + 2M}$$

$$I_2 = \frac{(L_1 + M) I_1}{L_1 + L_2 + 2M}$$

$$V =$$

- Q. Two coils with coeff of coupling is 0.6 bho them that are connected in series so as to magnetize in (i) same direction (ii) opposite direction. The total inductance in same direction is 1.5H, and in opposite direction is 0.5H.

Sol: $L_{\text{cumulative}} = 1.5 \text{ H}$

$$L_{\text{differential}} = 0.5 \text{ H}$$

$$\Rightarrow L_1 + L_2 + 2M = 1.5$$

$$L_1 + L_2 - 2M = 0.5$$

(+)

$$\underline{\underline{L_1 + L_2 = 1}}$$

$$L_1 + L_2 + 2M = 1.5$$

$$L_1 + L_2 - 2M = 0.5$$

(-)

$$\underline{\underline{M = 0.25}}$$

$$k = \frac{M}{\sqrt{L_1 L_2}} \rightarrow L_1 L_2 = \frac{M^2}{k^2} = \frac{\left(\frac{1}{4}\right)^2}{(0.6)^2} = 0.1736$$

$$L_1 L_2 = 0.1736$$


$$L_1 = \frac{0.1736}{L_2}$$

$$\frac{0.1736}{L_2} + L_2 + 2(0.25) = 1.5$$

$$L_2 = 0.78 \text{ H}$$

$$\text{Hence } L_1 = \frac{0.1736}{0.78} = 0.22 \text{ H}$$

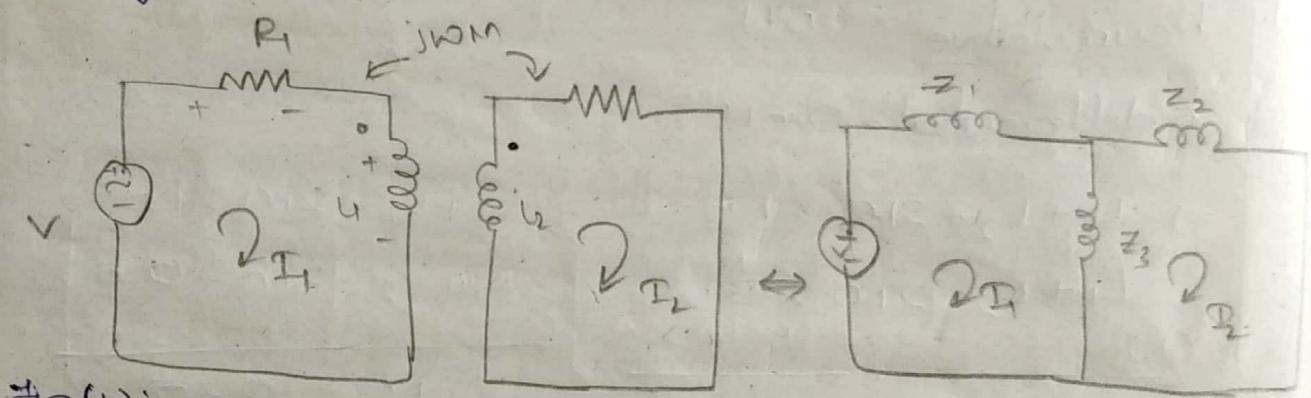- * Conductively coupled silent T circuit:
- For easy circuit analysis, it is desirable to replace magnetically coupled circuit with an equivalent network called conductively coupled circuit.
- In this circuit, no magnetic couplings are involved, the dot connection is not needed.
- It can be analysed by general network simplification techniques such as mesh analysis, nodal analysis.



Fig(1):

$$V = (R_1 + j\omega L_1)I_1 - j\omega M I_2 \quad (1)$$

$$(R_2 + j\omega L_2)I_2 - j\omega M I_1 = 0 \quad (2)$$

$$\begin{bmatrix} R_1 + j\omega L_1 & -j\omega M \\ -j\omega M & R_2 + j\omega L_2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V \\ 0 \end{bmatrix}$$

Fig(2)

$$V = (z_1 + z_2)I_1 - z_2 I_2 \quad (1)$$

$$-z_2 I_1 + (z_2 + z_3) I_2 \quad (2)$$

$$\begin{bmatrix} z_1 + z_2 & -z_2 \\ -z_2 & z_2 + z_3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} v \\ 0 \end{bmatrix}$$

$$z_1 + z_2 = R_1 + j\omega L_1$$

$$z_2 = j\omega M$$

$$z_2 + z_3 = R_2 + j\omega L_2$$

$$\Rightarrow z_1 = R_1 + j\omega L_1 - z_2$$


$$= R_1 + j\omega L_1 - j\omega M$$

$$= R_1 + j\omega (L_1 - M)$$


$$\Rightarrow z_3 = R_2 + j\omega L_2 - z_2$$

$$= R_2 + j\omega L_2 - j\omega M$$


$$= R_2 + j\omega (L_2 - M)$$

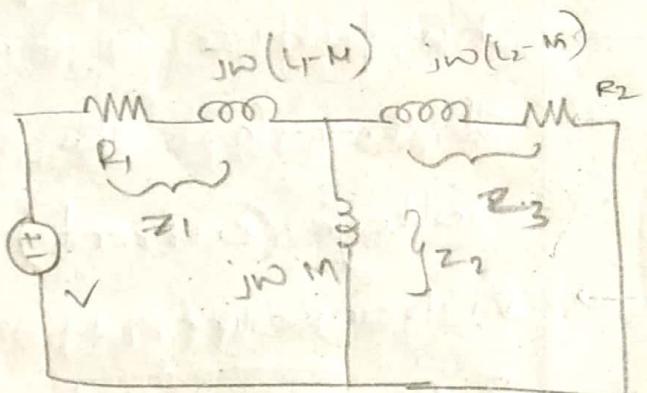


Q.

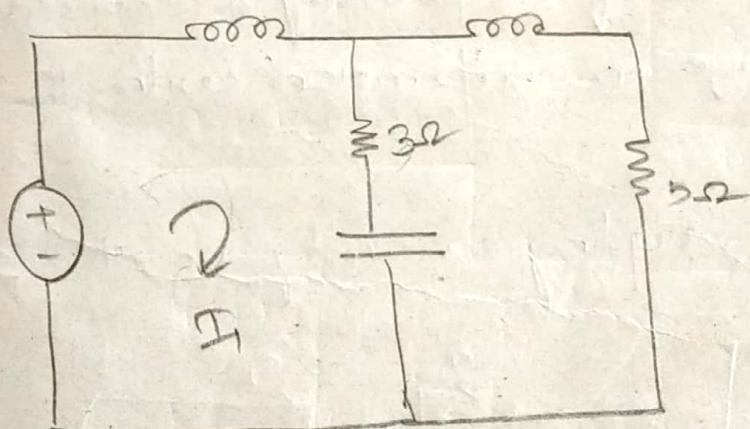

Dot connection for multiple inductors:

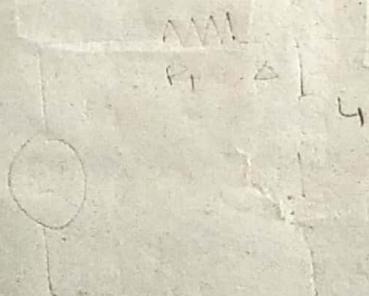

- * Ideal transformer :-
- Transfer of energy from 1 circuit to another circuit through mutual induction is widely used in power systems.
- This purpose is served by transformer.
- It transfers the energy at one voltage to another voltage (current) without change in transformer.
- A transformer is a static piece of apparatus having 2 or more windings or coils arranged on a common magnetic core.
- Ideal transformer is characterized by assuming zero resistance (zero power dissipation in the primary & secondary windings).
- The self inductances of the primary & secondary are extremely large in comparison with the load impedance.
- The coefficient of coupling is unity i.e., $K = 1$.

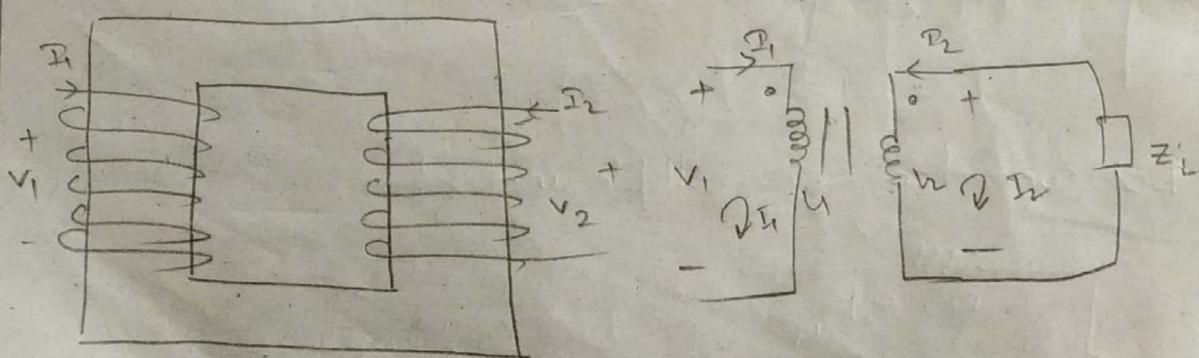

$$\frac{N_2}{N_1} \rightarrow a ; K = 1$$

$$v = L \frac{di}{dt} \rightarrow ①$$

$$v = N \frac{d\phi}{dt} \rightarrow ②$$

$$① - ②$$

$$\Rightarrow L \frac{di}{dt} = N \frac{d\phi}{dt} \Rightarrow L = N \frac{d\phi}{di} \quad \therefore L = \frac{N^2}{R}$$

$$\frac{L_2}{L_1} = \frac{N_2^2}{N_1^2} = \alpha^2$$

$$I = \frac{v}{R} = \frac{\text{emf}}{\text{Resistance}}$$

$$\phi = \frac{\text{mmf}}{\text{Reluctance}} = \frac{NI}{R}$$

w.r.t. that, $v_1 = N_1 \frac{d\phi}{dt}$

$$v_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_2}{v_1} = \frac{N_2}{N_1} = \alpha$$

from the figure,

$$v_1 = j\omega L_1 I_1 - j\omega M I_2 \rightarrow (1)$$

$$0 = -j\omega M I_1 + (j\omega L_2 + z_L) I_2 \rightarrow (2)$$

$$\Rightarrow I_2 = \frac{j\omega M I_1}{j\omega L_2 + z_L} \rightarrow (3)$$

Sub (3) in (1)

$$v_1 = j\omega L_1 I_1 - j\omega M \left[\frac{j\omega M I_1}{j\omega L_2 + z_L} \right]$$

$$= I_1 j\omega L_1 + \frac{I_1 \omega^2 m^2}{z_L + j\omega L_2}$$

$$Z_{in} = \frac{V_1}{I_1}$$

$$\Rightarrow Z_{in} \rightarrow j\omega L_1 + \frac{\omega^2 M^2}{Z_L + j\omega L_2}$$

we know that, $\alpha = 1 \rightarrow M = \sqrt{4L_2}$

$$Z_{in} = j\omega L_1 + \frac{\omega^2 L_1 L_2}{Z_L + j\omega L_2}$$

$$\Rightarrow \frac{j\omega L_1 (Z_L + j\omega L_2) + \omega^2 L_1 L_2}{Z_L + j\omega L_2}$$

$$= \frac{j\omega L_1 Z_L - \omega^2 L_1 L_2 + \omega^2 L_1 L_2}{Z_L + j\omega L_2}$$

$$Z_{in} = \frac{Z_L L_1 j\omega}{Z_L + j\omega L_2}$$

$$j\omega L_2 \gg Z_L$$

$$Z_{in} = \frac{Z_L L_1 j\omega}{j\omega L_2}$$

$$Z_{in} = \frac{Z_L L_1}{L_2}$$

$$Z_{in} = \frac{Z_L}{\alpha^2}$$

Consider eq(2),

$$j\omega M I_1 - (j\omega L_2 + Z_L) I_2$$


$$\frac{I_1}{I_2} \rightarrow \frac{Z_L + j\omega L_2}{j\omega M}$$

$$\frac{I_1}{I_2} \rightarrow \frac{j\omega L_2}{j\omega M}$$

$$\rightarrow \frac{L_2}{M} = \frac{L_2}{\sqrt{4L_2}} = \sqrt{\frac{L_2}{4}} = a$$

$$\therefore a = \frac{N_2}{N_1} = \sqrt{\frac{L_2}{4}} = \frac{I_1}{I_2}$$

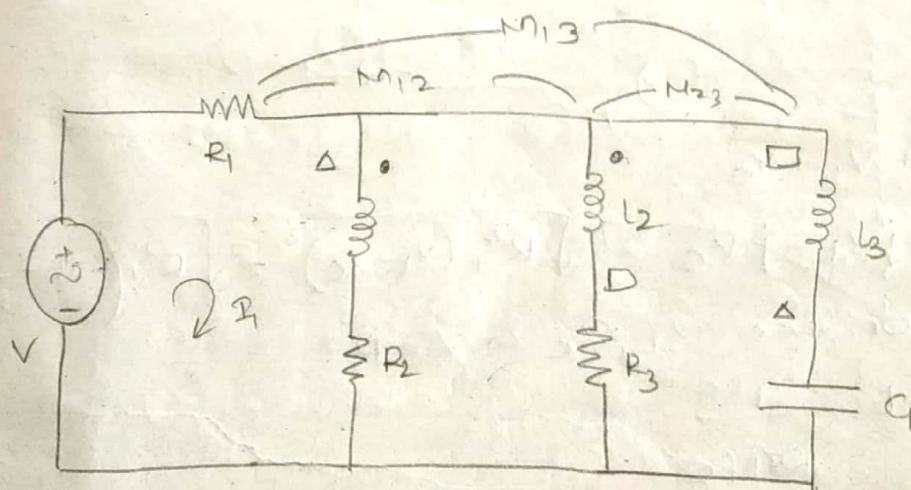- Q. An amplifier of output resistance 193.6Ω is to feed a loud speaker with an impedance of 4Ω . (i) Calculate the desired turns ratio for an ideal transformer to connect the 2 systems. (ii) An RMS current of 20mA at 500Hz is flowing in the primary. Calculate the RMS value of current in secondary winding. (iii) What is the power delivered to the load?




$$V - R_1 I_1 - j\omega L_1 (I_1 - I_2) - R_2 (I_1 - I_2) - j\omega M_{12} (I_2 - I_3) + j\omega M_{13} I_2$$

$$+ j\omega m (I_3 - I_2) = 0$$

* Resonance :

- It is defined as a phenomena in which applied voltage and resulting current are in phase.
- An AC circuit is said to be in resonance if it exhibits unity power factor condition.
- There are 2 types of resonance .
 - (i) Series resonance or resonance
 - (ii) parallel resonance or anti-resonance.
- The reactances are cancelled if the inductive and capacitive reactances are in series.
- The susceptances get cancelled if the inductive & capacitive reactances are in parallel.

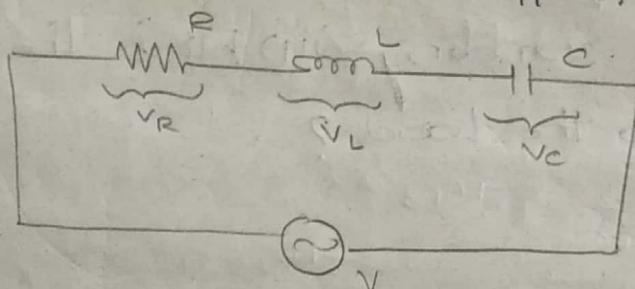

$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$

$$Z = R + jX_L - jX_C = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{R^2 + (WL - \frac{1}{WC})^2}$$


At resonance $X_L = X_C$ & $Z = R$

$$\Rightarrow 2\pi f L = \frac{1}{2\pi f C}$$

$$\Rightarrow f_0^2 = \frac{1}{(2\pi)^2 LC}$$

$$\Rightarrow f_0 = \frac{1}{2\pi\sqrt{LC}}$$

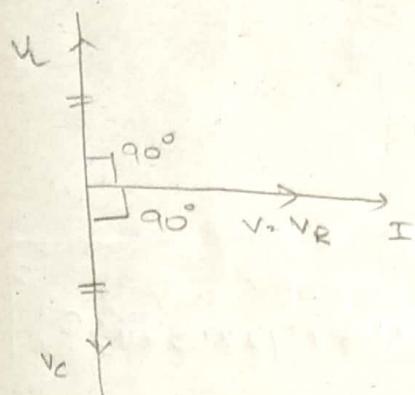
$$\rightarrow X_L > X_C \quad \rightarrow X_L < X_C \quad \rightarrow X_L > X_C$$



$$\cos\phi = \cos 0^\circ = 1$$

$$Y = \bar{V}_R$$


RC circuit

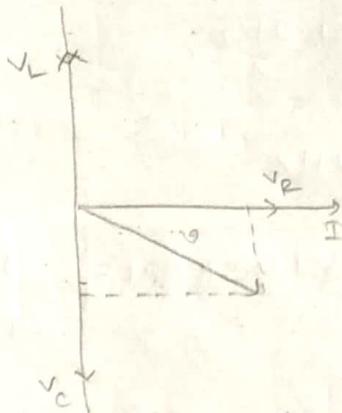

$$\cos(-\phi), \text{ leading}$$

$$V = \bar{V}_R + (\bar{V}_C - \bar{V}_L)$$

resistive circuit

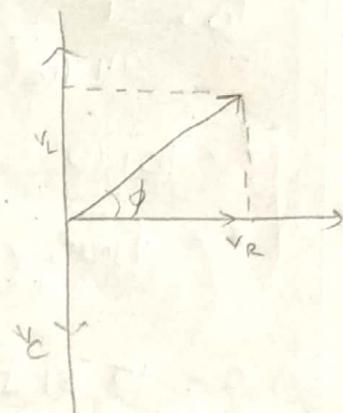

$$\cos\phi, \text{ lagging}$$

$$V = \bar{V}_R + (\bar{V}_L - \bar{V}_C)$$

RL circuit

- Q. Determine the value of capacitive reactance and impedance for the circuit. $R = 50\Omega$, $L = +j25$, $C = -jX_C$

Sol: $X_C = 25$

$$Z = R = 50\Omega$$

- Q. Determine f_0 where $R = 10\Omega$, $L = 0.5mH$, $C = 10\mu F$

Sol: $f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow \frac{1}{2\pi\sqrt{0.5 \times 10^{-3} \times 10 \times 10^{-6}}} \Rightarrow \frac{1}{2\pi\sqrt{10^{-8} \times 0.5}} = \frac{10^8}{\pi} \text{ Hz} \cdot \frac{1}{2\pi \times 10^{-4} \times \sqrt{0.5}} \Rightarrow 2.25 \text{ kHz}$

- Q. $f_0 = 5 \text{ kHz}$, $\omega L = 1 \text{ rad/s}$, $R = 2\Omega$ find $C = ?$

Sol: $f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow 5 \times 10^3 = \frac{1}{2\pi\sqrt{C \times 10^{-3}}} \Rightarrow C = \frac{1}{(2\pi)^2 \times 10^6 \times 10^{-3}} \Rightarrow C = 7.95 \times 10^{-10} \text{ F}$

- Q. Determine the impedance, f_0 , $10\text{Hz} \uparrow f_0$, $10\text{Hz} \downarrow f_0$

$$R = 10\Omega, 0.1\text{H} = L, C = 10\mu F$$

Sol: At f_0 , $Z = R = 10\Omega$

At $f = f_0 + 10$,

$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 159.2 \text{ Hz}$$

$$f = f_0 + 10 = 169.2 \text{ Hz}$$

$$\Rightarrow Z = \sqrt{R^2 + \left(2\pi \times 169.2 \times 0.1 - \frac{1}{2\pi \times 169.2 \times 10 \times 10^{-6}}\right)^2}$$


$$\Rightarrow Z = 15.81 \Omega$$

At $f = f_0 - 10$

$$f = 159.2 - 10 = 149.2 \text{ Hz}$$

$$\Rightarrow Z = \sqrt{R^2 + \left(2\pi \times 149.2 \times 0.1 - \frac{1}{2\pi \times 149.2 \times 10^{-6} \times 10}\right)^2}$$

$$\Rightarrow Z = 16.28 \Omega$$

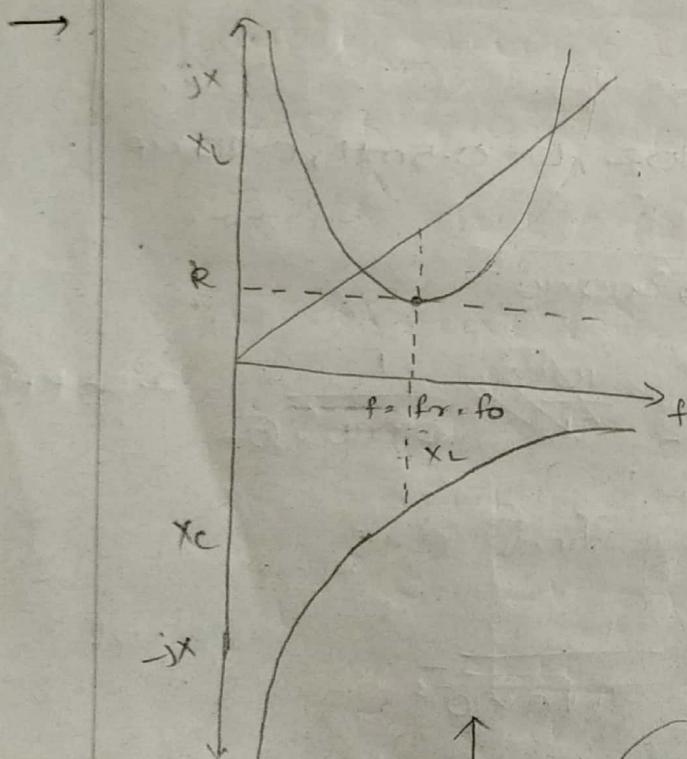

$$X_L = 2\pi f L$$



$$f = 0, X_L = 0$$



$$f \rightarrow \infty, X_L \rightarrow \infty$$

$$X_C = \frac{1}{2\pi f C}$$

$$f = 0, X_C = \infty$$

$$f \rightarrow \infty, X_C = 0$$

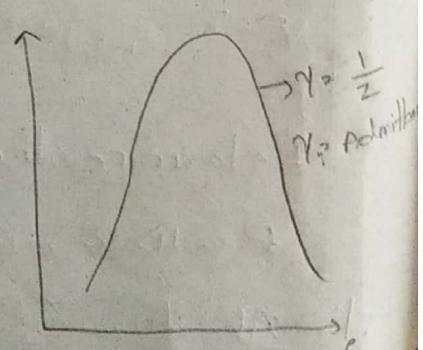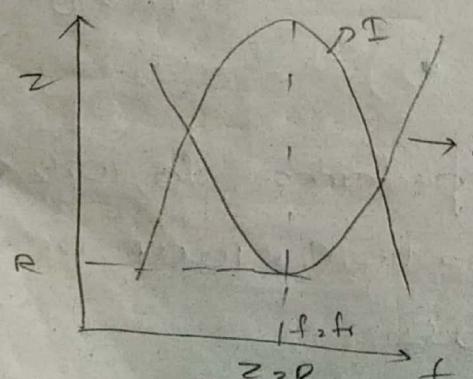

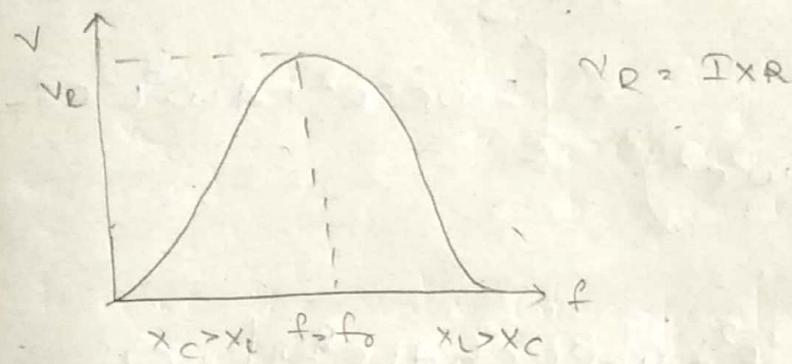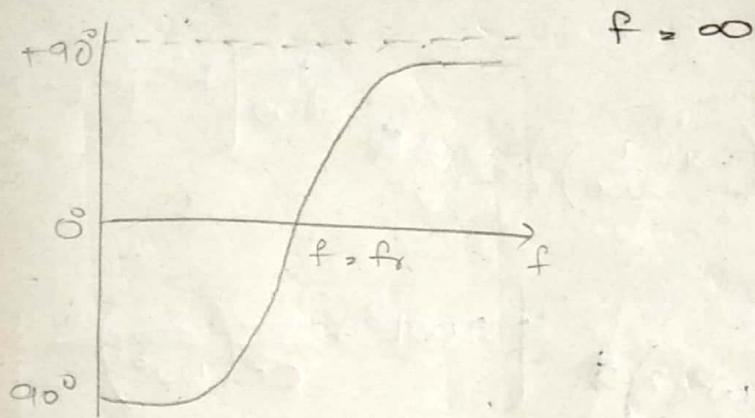


16/8/2019

For a resistor, C, L -

$$V_R = I \times R$$

$$V_C = I \times \frac{1}{\omega C} = I \times \frac{1}{2\pi f C}$$
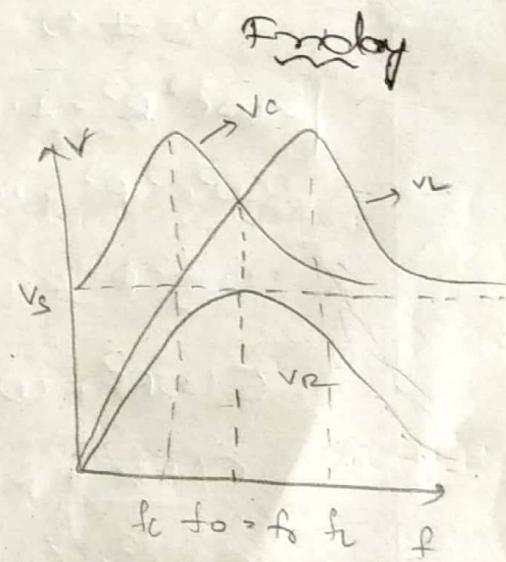
$$V_L = I \times \omega L = I \times 2\pi f L$$



$$X_C = I \times \frac{1}{\omega C}$$

$$\Rightarrow \frac{V_s}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} \omega C$$

$$V_C^2 = \frac{V_s^2}{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 \omega^2 C^2}$$

$$\frac{dV_C^2}{d\omega} = 0 \quad \text{To get max. value}$$

$$0 = v_s^2 \cdot \frac{-1}{\left(\left(R^2 + \left(\omega_L - \frac{1}{\omega_C} \right)^2 \right) \omega^2 C^2 \right)} \cdot \frac{d}{d\omega} \left[R^2 + \left(\omega_L - \frac{1}{\omega_C} \right)^2 \right] / \omega^2$$

$$\Rightarrow \frac{-v_s^2}{\left(\left(R^2 + \left(\omega_L - \frac{1}{\omega_C} \right)^2 \right) \omega^2 C^2 \right)} \cdot \left[2\omega L^2 + \frac{1}{C^2} \left(\frac{2}{\omega^3} \right) \right],$$

$$\frac{-v_s^2}{\left(\left(R^2 + \left(\omega_L - \frac{1}{\omega_C} \right)^2 \right) \omega^2 C^2 \right)^2} \cdot \left[2\omega C^2 R^2 + 4\omega^3 L^2 C^2 - 4LC^3 \omega \right] = 0$$

$$\Rightarrow -v_s^2 \left[2\omega C^2 R^2 + 4\omega^3 L^2 C^2 - 4LC^3 \omega \right] = 0$$

$$v_s \neq 0$$

$$2\omega C^2 R^2 + 4\omega^3 L^2 C^2 - 4LC^3 \omega = 0$$

$$\omega^3 C^2 R^2 + \omega^3 L^2 C^2 - 2LC^3 \omega = 0$$

$$\omega C^2 R^2 + \omega^2 L^2 C^2 - 2LC^3 \omega = 0$$

$$C\omega R^2 + \omega^2 L^2 - 2LC^3 \omega = 0$$

$$C\omega R^2 + 2\omega^2 L^2 - 2LC^3 \omega = 0$$

$$C2L^2 \omega^2 + R^2 \omega C - 2LC^3 \omega = 0$$

$$2L^2 \omega^2 = 2LC - R^2 \omega$$

$$\omega^2 = \frac{2LC}{2L^2} - \frac{R^2 \omega}{2L^2}$$

$$\omega^2 = \frac{C}{L} - \frac{R^2 \omega}{2L^2}$$

$$\omega = \sqrt{\frac{C}{L} - \frac{R^2 \omega}{2L^2}} \times$$

$$2L^2C\omega^2 + R^2\omega C - 2L = 0$$

$$2\omega R^2C^2 + 4\omega^3 L^2C^2 - 4LC\omega = 0$$

$$2R^2C^2 + 4\omega^2 L^2C^2 - 4LC = 0$$

$$R^2C + 2C\omega^2 L^2 - 2L = 0$$

$$\omega^2 = \frac{2L - R^2C}{2CL^2}$$

$$\omega^2 = \frac{1}{LC} - \frac{R^2}{2L^2}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$2\pi f_C = \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$f_C = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}}$$

$$f_C = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R^2C}{2L}}$$

$$f_C = f_0 \sqrt{1 - \frac{R^2C}{2L}}$$

→

$$V_L = I \times \omega L$$

$$= \frac{V_S \omega L}{\sqrt{R^2 + (\omega_C - \frac{1}{\omega_C})^2}}$$

$$V_L^2 = \frac{V_S^2 \omega^2 L^2}{\sqrt{R^2 + (\omega L - \frac{1}{\omega_C})^2}}$$

$$\frac{dV_L^2}{d\omega} = 0$$

* Quality factor:

→ Figure of merit is called quality factor.


→ $Q = \frac{\text{max. energy stored per cycle}}{\text{max. energy dissipated per cycle}} \times 2\pi$

$$\rightarrow E_L = \frac{1}{2} L I_m^2$$

$$P_D = I^2 R$$

$$\Rightarrow \left(\frac{I_m}{\sqrt{2}} \right)^2 R = \frac{I_m^2 R}{2}$$
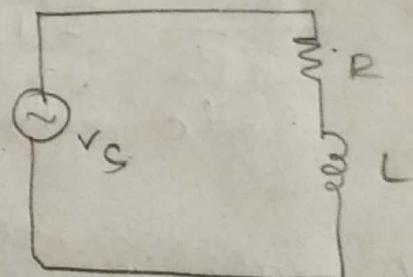
$$P_D \text{ per cycle} \Rightarrow \frac{I_m^2 R}{2f}$$



$$\rightarrow Q = \frac{2\pi \times \frac{1}{2} L I_m^2}{I_m^2 R / 2f}$$


$$\Rightarrow \frac{\pi \times 2f \times L}{R} = \frac{\omega L}{R} = \text{Quality factor of Inductor}$$

$$\rightarrow E_C = \frac{1}{2} C V_m^2 = \frac{1}{2} C \left(\frac{I_m}{\omega C} \right)^2$$

$$P_D = I^2 R$$

$$= \left(\frac{I_m}{\sqrt{2}} \right)^2 R \cdot \frac{I_m^2 R}{2}$$
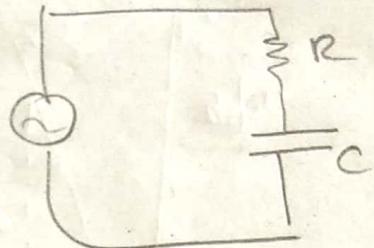
$$P_D \text{ for cycle} = \frac{I_m^2 R}{2f}$$



$$Q = \frac{2\pi \times \frac{1}{2} C V_m^2}{\frac{I_m^2}{2f}} = \frac{1}{\omega CR} \text{, quality factor of capacitor}$$

$$\rightarrow Q = \frac{1}{\omega CR} ; Q = \frac{\omega L}{R}$$

$$Q \times Q = \frac{\omega L}{R} \times \frac{1}{\omega CR}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} \text{ - quality factor of LCR circuit.}$$

\rightarrow The series resonance circuit acts like a voltage amplifier.

$$V_{in} > V_s$$

$$V_L = I \times j \times L \quad \left[\because \text{At resonance, } I = \frac{V_s}{R} \right]$$


$$= \frac{V_s}{R} \omega L (+90^\circ)$$

$$V_L = V_s Q_0 < 90^\circ$$

$$\text{Why } V_C = I \times -j \times C$$

$$= \frac{V_s}{R} \times \frac{1}{\omega C} < -90^\circ$$


$$= V_s Q_0 < -90^\circ$$

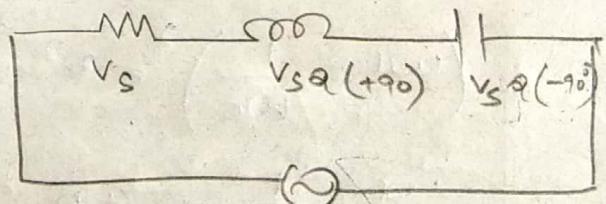

A/8/2019

Monday

* Bandwidth of series resonant circuit:

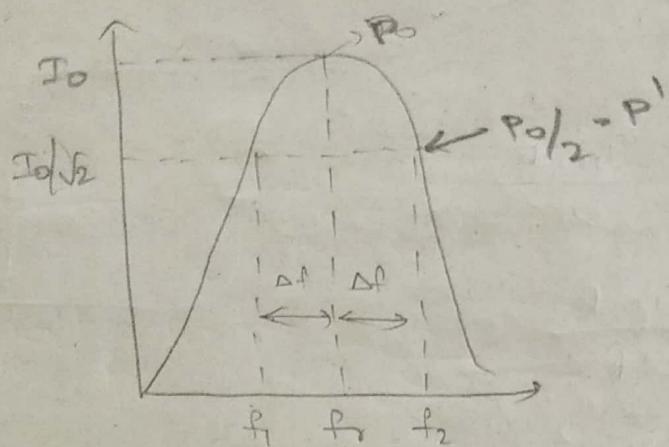

$$\text{Bandwidth} = f_2 - f_1 \rightarrow 2\Delta f$$

$$P' = \frac{P_0}{2}$$

$$= \frac{I_0^2}{2} R = \left(\frac{I_0}{\sqrt{2}}\right)^2 R$$

$$I_0 = \frac{V}{R}$$

$$\frac{I_0}{\sqrt{2}} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}} = \frac{V}{Z}$$

$$\frac{V}{R\sqrt{2}} = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$2R^2 = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

$$\omega L - \frac{1}{\omega C} = \pm R$$

$$\omega_L - \frac{1}{\omega_C} = \pm R \rightarrow \textcircled{1}$$

$$\omega_1 L - \frac{1}{\omega_1 C} = -R \longrightarrow ②$$

$$① + ②$$

$$(\omega_1 + \omega_2)L - \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} \right) \frac{1}{C} = 0$$

$$(\omega_1 + \omega_2)L - \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right) \frac{1}{C} = 0$$

$$\omega_1 \omega_2 = \frac{1}{LC}$$

$$f_1 f_2 = \frac{1}{4\pi^2 LC} = f_r^2 \quad \left[\because f_r = \frac{1}{2\pi\sqrt{LC}} \right]$$

$$\boxed{\Rightarrow f_r = \sqrt{f_1 f_2}}$$

$$① - ②$$

$$(\omega_2 - \omega_1)L + \left(\frac{1}{\omega_1} - \frac{1}{\omega_2} \right) \frac{1}{C} = 2R$$

$$\omega_2 - \omega_1 + \left(\frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right) \frac{1}{LC} = \frac{2R}{L}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$\omega_r^2 = \frac{1}{LC}$$

$$\Rightarrow \omega_2 - \omega_1 = \frac{R}{L}$$

$$f_2 - f_1 = \frac{R}{2\pi L}$$

$$f_1 = f_r - \Delta f$$

$$= f_r - \frac{R}{4\pi L}$$

$$f_2 = f_r + \Delta f$$

$$= f_r + \frac{R}{4\pi L}$$

Selectivity:

$$\text{Selectivity} = \frac{f_r}{Bw}$$

$$\Rightarrow \frac{f_r}{f_2 - f_1} = \frac{f_r}{R/2\pi L} \Rightarrow \frac{2\pi f_r L}{R} = \frac{\omega L}{R}$$

$$\text{Quality factor} = \frac{f_r}{Bw}$$

- Q. A series RLC circuit consists of resistance $1\text{k}\Omega$, $L = 100\text{mH}$, $C = 10\text{pF}$. Find Resonant frequency f_r , I_o , Q-factor, f_1 , f_2

$$R = 1\text{k}\Omega = 10^3 \Omega \quad V = 100\text{V}$$

$$L = 100 \times 10^{-3} = 0.1\text{H}$$

$$C = 10 \times 10^{-12} = 10^{-11}\text{F}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{10^{-1} \times 10^{-11}}} = \frac{1}{2\pi \times 10^{-5}} = \frac{10^5}{2\pi}$$

$$I_o = \frac{V}{R} = \frac{100}{10^3} = 0.1\text{A} \quad > 159235.6\text{Hz}$$

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10^3} \sqrt{\frac{10^{-1}}{10^{-11}}} = \frac{10^5}{10^3} = 100$$

$$f_1 = f_r - \frac{R}{4\pi L} = 159235.6 - \frac{10^3}{4\pi \times 10^{-1}}$$

$$> 159235.6 - \frac{10^4}{4\pi}$$

$$= 159235.6 - 795.77 = 158439.83$$

$$f_2 = f_r + \frac{R}{4\pi L} \rightarrow 159235.6 + 795.77 \\ \rightarrow 160031.37$$

Q. A series RLC circuit with $R = 8\Omega$, B.W. = 50Hz, Determine the value of L and C so that the circuit resonates at 250Hz

Sol: BW $\Rightarrow \frac{R}{2\pi L}$

$$50 = \frac{R}{2\pi L} \Rightarrow 2\pi L = \frac{8}{50} \\ \Rightarrow L = \frac{8}{2\pi \times 50} = 0.025 \text{ H}$$

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$250 = \frac{1}{2\pi\sqrt{0.025 \times C}}$$

$$\sqrt{0.025 \times C} = \frac{1}{2\pi \times 250}$$

$$0.025 \times C = \frac{1}{4\pi^2 \times 250 \times 250}$$

$$C = \frac{1}{4\pi^2 \times 250 \times 250 \times 0.025} = 1.62113 \times 10^{-5} \text{ F}$$

Q. A max. current of 0.1A flows through the circuit when a capacitor value is 5μF with a fixed frequency & voltage of 5V. Determine the frequency at which the circuit resonates, the BW, Q, the value of R at resonance.
 $L = 0.1H$

$$D_o \rightarrow \frac{V}{R}$$

$$R_o \rightarrow \frac{V}{I_o} \rightarrow \frac{5}{0.1} \rightarrow 50\Omega$$

$$\begin{aligned} Q &= \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{50} \sqrt{\frac{0.1}{5 \times 10^{-6}}} \\ &= \frac{1}{50} \sqrt{\frac{10^6 \times 10^{-1}}{5}} \\ &= \frac{1}{50} \sqrt{\frac{105}{5}} \approx 2.828 \end{aligned}$$

$$\begin{aligned} f_r &= \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 5 \times 10^{-6}}} \\ &\rightarrow \frac{1}{2\pi\sqrt{5 \times 10^{-7}}} \approx 225.07 \text{ Hz} \end{aligned}$$

$$BW = \frac{R}{2\pi L} = \frac{50}{2\pi \times 10^{-1}} = \frac{500}{2\pi} \approx 79.57 \text{ Hz}$$

Q. $R = 10\Omega$, $L = 60\text{mH}$, $f = 25\text{Hz}$ are present in series RLC circuit. The P.F of the circuit is 45° leading. At what frequency the circuit resonates.

Sol:

$$R = 10\Omega$$

$$L = 60\text{mH}$$

$$f = 25\text{Hz}$$

$$\tan \phi = \frac{x_C - x_L}{R}$$

$$\tan 45^\circ = \frac{x_C - x_L}{10}$$

$$x_C - x_L = 10$$

$$\cos \phi = R/Z$$

$$\frac{1}{\sqrt{2}} = \frac{10}{Z} \Rightarrow Z = 10\sqrt{2}$$

Q. A series RLC circuit has $R = 4\Omega$, $L = 25\text{mH}$.

(a) Calculate 'C' if $\alpha = 50$.

(b) Calculate ω_1 , ω_2 & BW .

(c) Calculate Avg power at $\omega_0 = \omega_1, \omega_2$ take

$$V_m = 100\text{V}$$

Sol: $R = 4\Omega$, $L = 25\text{mH}$

(i) $\alpha = 50$

$$\alpha = \frac{1}{R} \sqrt{\frac{L}{C}} \Rightarrow 50 = \frac{1}{4} \sqrt{\frac{25 \times 10^{-3}}{C}}$$

$$\Rightarrow C =$$

(ii) $\omega_1 = \omega_r - \frac{R}{2L}$; $\omega_2 = \omega_r + \frac{R}{2L}$

$$\alpha = \frac{\omega_r L}{R}$$

$$50 \times \frac{1}{\omega_r} = \omega_r L \Rightarrow \omega_r = \frac{50 \times 4}{25 \times 10^{-3}} = \frac{200 \times 10^3}{25}$$

$$\Rightarrow \omega_r = \frac{200000}{25} =$$

$$\Rightarrow \omega_r = 8 \times 10^3 \text{ Hz}$$

$$\omega_1 = 8 \times 10^3 - \frac{4 \times 10^3}{2 \times 25} = 10^3 \left[8 - \frac{2}{25} \right]$$


$$\omega_1 = 8 \times 10^{-3} - 8$$

$$= 8(10^{-3} - 1)$$

20/8/2019

Tuesday

* Parallel Resonance:

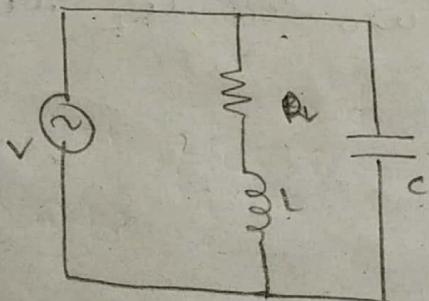

$$Z = R \pm jX_L$$

$$Y = G \pm jB \mp$$

$$Z_1 = R + jX_L$$

$$\gamma_1 = \frac{1}{Z_1} = \frac{1}{R + jX_L} = \frac{R - jX_L}{R^2 + X_L^2}$$

$$Z_2 = \frac{+}{jX_C} - jX_C$$

$$\gamma_2 = \frac{1}{Z_2} = \frac{j}{jX_C} = \frac{1}{X_C}$$

$$\gamma = \gamma_1 + \gamma_2$$

$$= \frac{R - jX_L}{R^2 + X_L^2} + \frac{j}{X_C}$$

$$\gamma_T = \frac{R}{R^2 + X_L^2} - \frac{jX_L}{R^2 + X_L^2} + \frac{j}{X_C}$$

$$Y_T = \frac{R}{R^2 + X_L^2} + j \left[\frac{X_L}{R^2 + X_L^2} - \frac{1}{X_C} \right]$$

$$G = \frac{R}{R^2 + X_L^2}; B = \frac{X_L}{R^2 + X_L^2} - \frac{1}{X_C} = 0$$

$$\Rightarrow \frac{X_L}{R^2 + X_L^2} = \frac{1}{X_C}$$

$$\Rightarrow X_L X_C = R^2 + X_L^2$$

$$\Rightarrow R^2 + X_L^2, \omega_{\text{ar}} \frac{1}{\omega_{\text{ar}}}$$

$$\Rightarrow R^2 + X_L^2 = \frac{L}{C}$$

$$\Rightarrow R^2 + \omega_{\text{ar}}^2 L^2 = \frac{L}{C}$$

$$\Rightarrow \omega_{\text{ar}}^2 L^2 = \frac{L}{C} - R^2 \Rightarrow \omega_{\text{ar}}^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$\Rightarrow \omega_{\text{ar}} = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$f_{\text{ar}} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

far = frequency at resonance
in ||| e |||

$$\frac{1}{LC} \gg \frac{R^2}{L^2}$$

or = anti resonance

$$Y = \frac{R^2}{R^2 + X_L^2}$$

$$Z = \frac{R^2 + X_L^2}{R} = \frac{L}{RC}$$

$$\rightarrow R^2 + X_L^2 = \frac{L}{C}$$

$$R^2 \left[1 + \frac{\omega_{\text{ar}}^2 C^2}{R^2} \right] = \frac{L}{C}$$

$$R^2 (1 + \omega^2) = \frac{L}{C}$$

$$\rightarrow R(1+Q^2) = \frac{1}{CR}$$

$$\rightarrow P(1+Q^2) = Z_{ar}$$

→ Z_{ar} is also called dynamic resistance.

$$f_{ar} = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R^2C}{L}}$$

$$Q \times Q = \frac{\omega_0 L}{R} \times \frac{1}{\omega_0 C}$$

$$Q^2 = \frac{L}{R^2 C}$$

$$f_{ar} = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{1}{Q^2}}$$

→ If $Q \uparrow$ (very large) then $f_{ar} = f_r$.

→ Parallel resonance circuit acts like a current amplifier.

→ Series resonance circuit acts like a voltage amplifier.

$$V \cdot P_{Zar} = I \times \frac{L}{CR}$$

$$I_c = \frac{V}{X_C} = V \omega_{arc}$$

$$= \frac{IL}{RC} \times \omega_{arc} C$$

$$= I_x \left(\frac{\omega_{al}}{R} \right)$$

$$I_c = I Q$$

Hence, current is amplified $\approx Q$ times across the capacitor.

$$P = I_e^2 R$$


$$P = I^2 Z_{ar}$$

$$I^2 Z_{ar} = I_e^2 R$$

$$I_e^2 = \frac{I^2 \cdot \frac{1}{RC}}{R} \Rightarrow I_e^2 = I^2 \cdot \frac{L}{R^2 C}$$

$$\Rightarrow I_e = \sqrt{I^2 \frac{L}{R^2 C}}$$
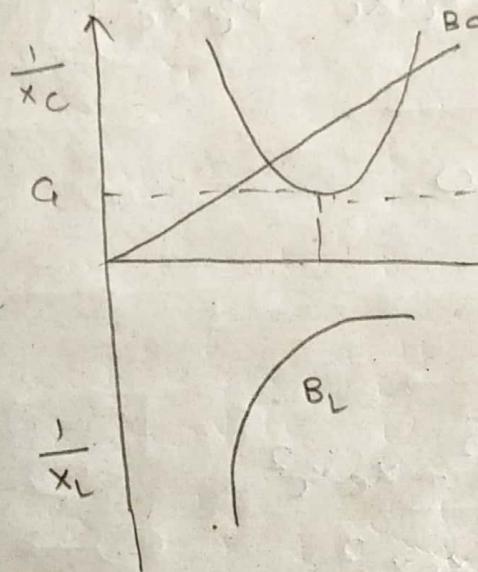
$$\Rightarrow I_e = I \times \frac{1}{R} \int \frac{L}{C} \Rightarrow I_e = I \times Q.$$




X_C




$$B_C = \frac{1}{X_C} = \omega C$$

$$B_L = \frac{1}{X_L} = \frac{1}{\omega L}$$

$$\gamma = G \pm jB$$

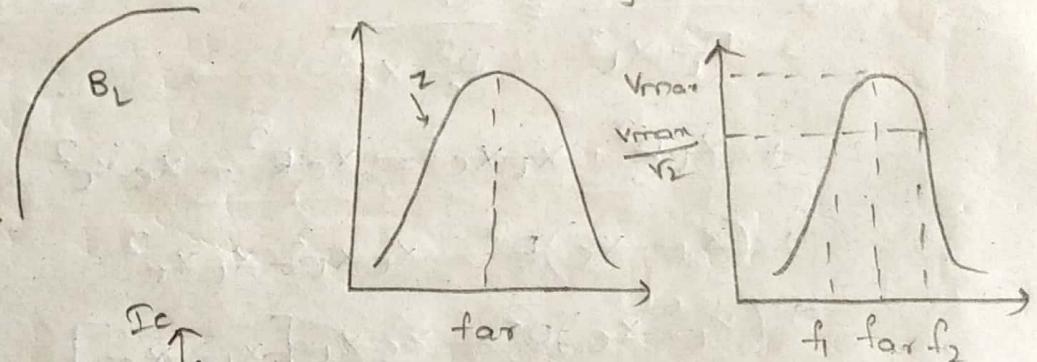

$$Q = \frac{f_1}{f_2 - f_1}$$

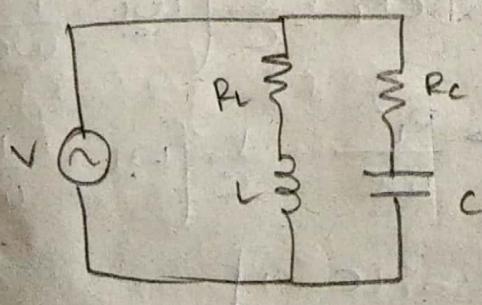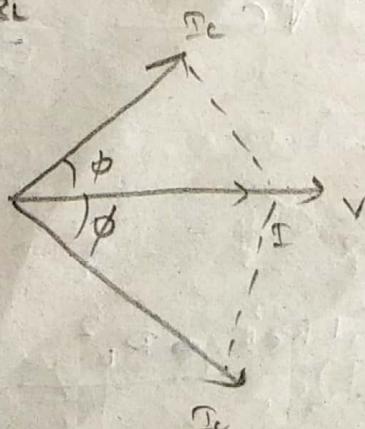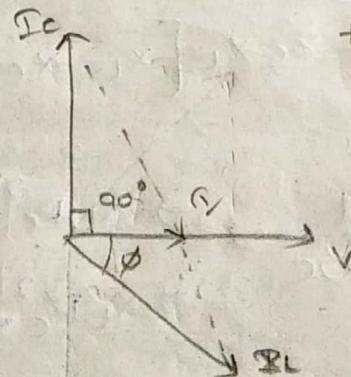

$$Z_1 = R_L + jX_L$$

$$\gamma_1 = \frac{1}{Z_1} = \frac{R_L - jX_L}{R_L^2 + X_L^2}$$

$$Z_2 = R_C - jX_C$$

$$\gamma_2 = \frac{1}{Z_2} = \frac{1}{R_C - jX_C} = \frac{R_C + jX_C}{R_C^2 + X_C^2}$$

$$\gamma = \gamma_1 + \gamma_2$$

$$= \frac{R_L}{R_L^2 + X_L^2} + \frac{R_C}{R_C^2 + X_C^2} - j \left[\frac{X_L}{R_L^2 + X_L^2} - \frac{X_C}{R_C^2 + X_C^2} \right]$$

$$B = 0$$

$$\rightarrow \frac{X_L}{R_L^2 + X_L^2} - \frac{X_C}{R_C^2 + X_C^2} = 0$$

$$\Rightarrow \frac{X_L}{R_L^2 + X_L^2} = \frac{X_C}{R_C^2 + X_C^2}$$

$$\rightarrow X_L R_L^2 + X_L X_C^2 = X_C R_C^2 + X_C X_L^2$$

$$\rightarrow (X_L - X_C) R^2 = X_C X_L^2 - X_L X_C^2$$

$$\rightarrow (X_L - X_C) R^2 = X_C X_L [X_L - X_C]$$

$$\rightarrow R^2 = X_C X_L$$

$$\rightarrow R^2 = \frac{X_L R_L^2 + X_L X_C^2}{X_C R_C^2 + X_C X_L^2} = \frac{X_L R_C^2 + X_C X_L^2}{X_C R_L^2 + X_C X_L^2}$$

$$\rightarrow R = \sqrt{\frac{L}{C}}$$

$$\Rightarrow X_L R_C^2 + X_C X_L^2 = X_C X_L \left[\frac{X_L}{X_C} - 1 \right]$$

for

$$\Rightarrow X_L R_C^2 + X_C X_L^2 = \frac{L}{C} \left[\omega_L - \frac{1}{\omega_C} \right]$$

$$\Rightarrow \frac{\omega_L R_C^2 + R_L^2}{\omega_C} = \frac{L}{C} \left[\omega_L - \frac{1}{\omega_C} \right]$$

$$\Rightarrow \frac{\omega_{ar}^2 L R_C^2 C + R_L^2}{\omega_{ar} C} = \frac{L [\omega_{ar}^2 LC - 1]}{\omega_{ar} \omega_C^2}$$

$$\rightarrow \omega_{ar}^2 R_c^2 LC - R_L^2 = \frac{1}{C} [\omega_{ar}^2 LC - 1]$$

$$\rightarrow \omega_{ar}^2 R_c^2 L C^2 - R_L^2 C = \omega_{ar}^2 L^2 C - L$$

$$\rightarrow \omega_{ar}^2 R_c^2 L C^2 + \omega_{ar}^2 L^2 C = R_L^2 C - L$$

$$\rightarrow \omega_{ar}^2 R_c [R_c^2 - L] = R_L^2 C - L$$

$$\rightarrow \omega_{ar}^2 = \frac{1}{LC} \left[\frac{R_L^2 C - L}{R_c^2 C - L} \right]$$

$$\rightarrow \omega_{ar}^2 = \frac{1}{LC} \left[\frac{\frac{R_L^2 - L/C}{C}}{\frac{R_c^2 - L/C}{C}} \right]$$

$$\rightarrow \omega_{ar} = \sqrt{\frac{1}{LC} \left[\frac{R_L^2 - L/C}{R_c^2 - L/C} \right]}$$

$$\rightarrow 2\pi f_{ar} = \sqrt{\frac{1}{LC} \left[\frac{R_L^2 - L/C}{R_c^2 - L/C} \right]}$$

$$\rightarrow f_{ar} = \frac{1}{2\pi} \sqrt{\frac{1}{LC} \left[\frac{R_L^2 - L/C}{R_c^2 - L/C} \right]}$$

$$\rightarrow f_{ar} = \frac{1}{2\pi\sqrt{LC}} \sqrt{\left(\frac{R_L^2 - L/C}{R_c^2 - L/C} \right)}$$

Q. Find the value of C such that the circuit resonates at $\omega_{ar} = 5000$ rad/sec

Sol:

$$\omega_{ar} = \frac{1}{\sqrt{LC}} \sqrt{\left(\frac{R_L^2 - L/C}{R_c^2 - L/C} \right)}$$

$$5000 = \frac{1}{\sqrt{0.6 \times 10^{-3} \times C}} \sqrt{\frac{25 - 0.6 \times 10^3 / C}{16 - 0.6 \times 10^3 / C}}$$


Solving this, we get a quadratic equation
in terms of 'c':

$$C_1 = 20.66 \mu F$$

$$C_2 = 121 \mu F$$

- Q. In \parallel L-C circuit find the resonant freq.
given $L = 1mH, R_L = 2\Omega, C = 10\mu F$.

29/8/2019

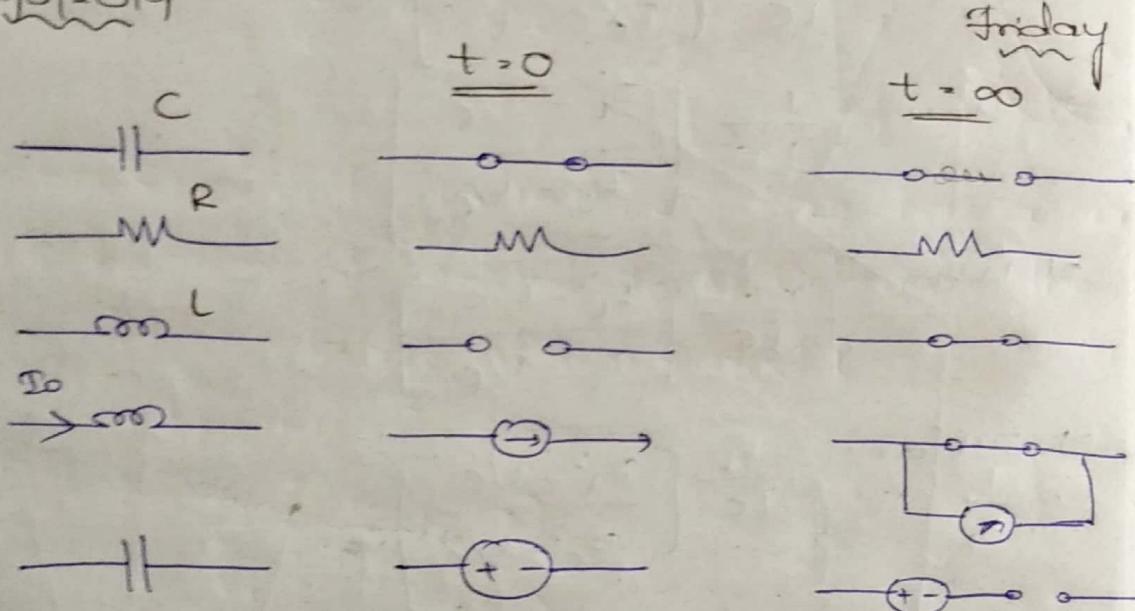

* Transient analysis:

DC Step input


$$V - R_i(t) - L \frac{di(t)}{dt} = 0$$

$$\frac{di(t)}{dt} + \frac{R_i(t)}{L} \cdot \frac{V}{L}$$

$$\frac{dx}{dt} + P x, \text{ & then soln } x(I.F) = \int Q(I.F) dt$$

$$e^{\int \frac{R}{L} dt} = e^{\frac{Rt}{L}}$$
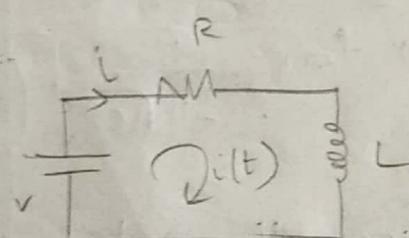
$$i(t) e^{\frac{Rt}{L}} = \int \frac{V}{L} e^{\frac{Rt}{L}} dt + C$$



$$i(t)e^{Rt/L} = \frac{V}{L} \int e^{Rt/L} dt + C$$

$$i(t) e^{Rt/L} = \frac{V}{L} \left(e^{Rt/L} \right) \cancel{\frac{dt}{R/L}} + C$$

$$\boxed{i(t) = \frac{V}{R} + Ce^{-Rt/L}}$$

$$i(t) = \frac{V}{R} + Ce^{-Rt/L} \quad \rightarrow (1)$$

$$t \rightarrow 0^- \rightarrow i(0^-) = 0$$

$$t \rightarrow 0^+ \rightarrow i(0^+) = 0$$

$$i(0^-) = \frac{V}{R} + Ce^{-R(0)/L}$$

$$0 \rightarrow \frac{V}{R} + C \Rightarrow C = -\frac{V}{R} \rightarrow (2)$$


Sub (2) in (1),

$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-Rt/L}$$

$$i(t) = \frac{V}{R} \left[1 - e^{-Rt/L} \right]$$

$$\boxed{\tau = \frac{L}{R}}$$

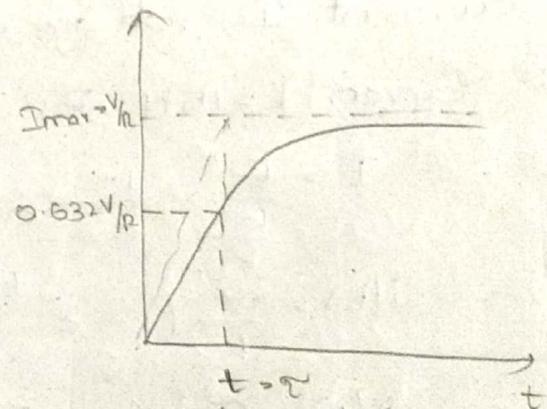$t \rightarrow 0^-$ just b4 switching
 $t \rightarrow 0^+$ just aft switching
 $t \rightarrow \infty$ steady state.



$$\text{If } t = \tau \rightarrow \frac{L}{R}$$

$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-Rt/L} \times \cancel{V_R}$$

$$= 0.632 \frac{V}{R}$$

$$i(t) = 63.2 \frac{V}{R}$$

$$V_R = R i(t) = R \times \frac{V}{R} \left(1 - e^{-Rt/L} \right)$$

$$= V \left(1 - e^{-Rt/L} \right)$$

$$V_L = L \frac{di(t)}{dt} = L \frac{V}{R} \left(-e^{-Rt/L} \right) \times \left(-\frac{R}{L} \right)$$

$$v_L = v e^{-\tau_L t}$$



$$P_R = V_R i(t)$$

$$= v(1 - e^{-t/\tau}) \frac{v}{R} (1 - e^{-t/\tau})$$

$$= \frac{v^2}{R} (1 - e^{-t/\tau})^2$$

$$P_L = v_L \times i(t) = v e^{-t/\tau} \frac{v}{R} (1 - e^{-t/\tau})$$
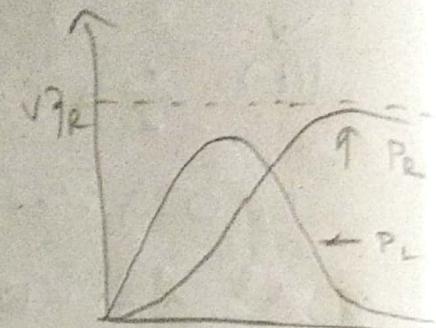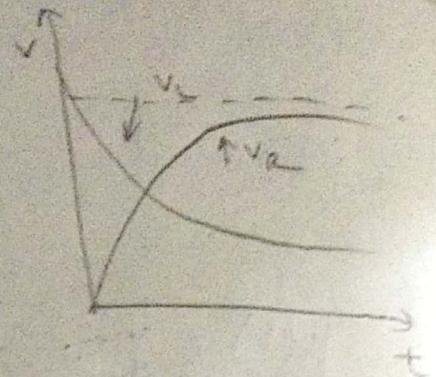
$$= \frac{v^2}{R} (e^{-t/\tau} - e^{-2t/\tau})$$



Q Series RL circuit, $L = 15 \text{ H}$, $R = 30 \Omega$ has a const voltage 60V applied at $t = 0$. Determine the current I , voltage across R and L.

Sol: Given $L = 15 \text{ H}$, $R = 30 \Omega$

$$\tau = \frac{L}{R} = \frac{15}{30} = \frac{1}{2}$$

$$i(t) = \frac{v}{R} (1 - e^{-t/\tau})$$

$$i(t) = \frac{60}{30} (1 - e^0) = 0 \text{ at } t = 0$$

$$i(t) = 2(1 - e^{-2t})$$

$$v_R = 60(1 - e^{-2t})$$



$$v_L = 60(e^{-2t})$$

Q. In a network of figure, the switch is initially at position 1. On the steady state having reached the switch is changed to position 2. Find $i(t)$.

At position 1,

$$i(0^-) \rightarrow \frac{V}{R_1}$$

then the eq. ckt is

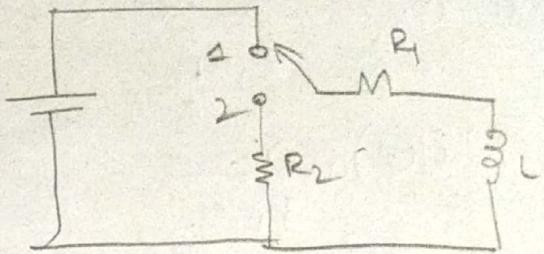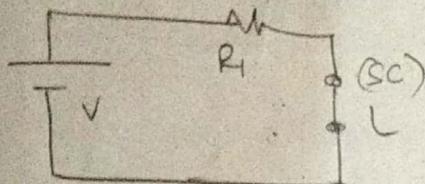


Since, the inductor does not accept sudden changes in current,

$$i(0^+) \rightarrow \frac{V}{R_1} \quad (\text{At position 2})$$

Writing KVL for adj. fig.,
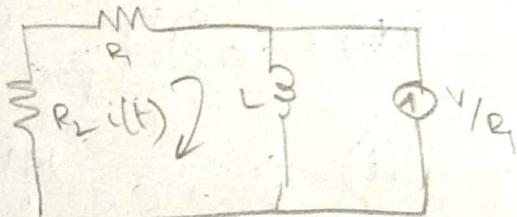
$$-R_2 i(t) - R_1 i(t) - L \frac{di(t)}{dt} = 0$$



$$\frac{di(t)}{dt} + \left(\frac{R_1 + R_2}{L} \right) i(t) = 0$$

$$i(t) \rightarrow C e^{-\left(\frac{R_1 + R_2}{L} \right) t} \rightarrow ①$$

$$t=0 \rightarrow i(0) = C e^{-\left(\frac{R_1 + R_2}{L} \right)(0)}$$


$$\Rightarrow \frac{V}{R_1} = C \rightarrow ②$$

② in ①


$$i(t) = \frac{V}{R_1} e^{-\left(\frac{R_1 + R_2}{L} \right) t}$$

- Q. A switch is closed at t=0. A steady state having previously attained. Find the current $i(t)$.

$$i(0^-) = \frac{V}{R_1 + R_2}$$

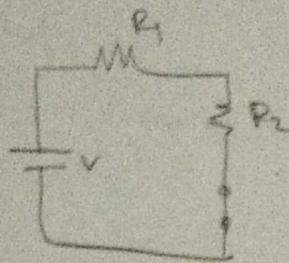


$$i(0^+) = \frac{V}{R_1 + R_2}$$

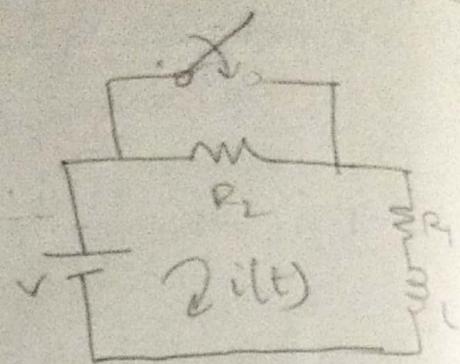

$$V - R_1 i(t) - \frac{L di(t)}{dt} > 0$$

$$\frac{di(t)}{dt} + \frac{R_1}{L} i(t) = \frac{V}{L}$$
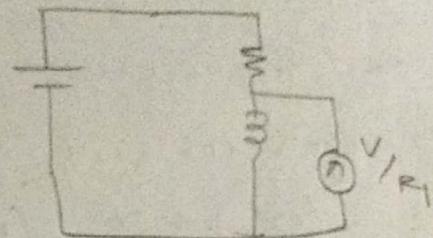
$$i(t) \rightarrow \frac{V}{R_1} \left(1 - e^{-\frac{R_1 t}{L}} \right)$$



$$i(t) = C e^{-\frac{R_1 t}{L}} \int \frac{V}{L} e^{\frac{R_1 t}{L}} dt + C e^{-\frac{R_1 t}{L}}$$

$$i(t) = \frac{V}{R_1} + C e^{-\frac{R_1 t}{L}}$$

At $t = 0$,

$$i(0) = \frac{V}{R_1} + C e^{-\frac{R_1 (0)}{L}}$$

$$\frac{V}{R_1 + R_2} = \frac{V}{R_1} + C \Rightarrow C = \frac{V}{R_1 + R_2} - \frac{V}{R_1}$$


$$i(t) = \frac{V}{R_1} + \left(\frac{V}{R_1 + R_2} - \frac{V}{R_1} \right) e^{-\frac{R_1 t}{L}}$$



- Q. Steady state is reached with switch closed, the switch is open at $t = 0$. Find $v_L(t)$, $I_L(t)$

Sol: At $t = 0^-$

$$i(0^-) = \frac{15}{100} = 0.15 \text{ A}$$

$$v_L(0^-) = 0 \text{ V}$$

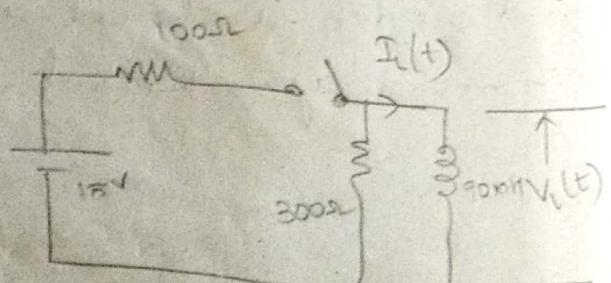

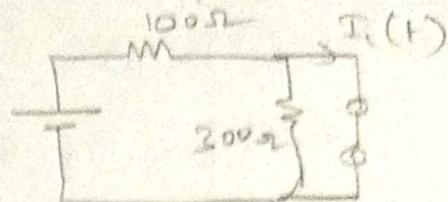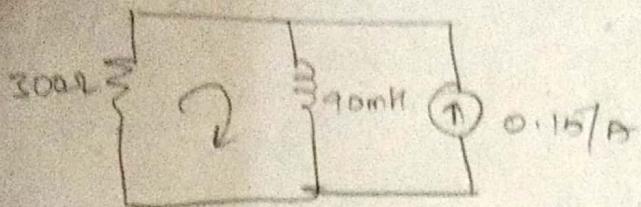

$$300i(t) + 90 \times 10^{-3} \frac{di}{dt} i(t) = 0$$

$$\frac{d}{dt} i(t) + \frac{300}{90 \times 10^{-3}} i(t) = 0$$

$$i(t) = C e^{-3.33 \times 10^3 t}$$

At $t=0$
 $i(0) = C e^{-3.33 \times 10^3 \cdot 0} = C$

$$C = 0.15 \text{ A}$$

$$i(t) = 0.15 e^{-3.33 \times 10^3 t}$$


$$V_L(t) = L \frac{di(t)}{dt}$$

$$= 90 \times 10^{-3} \frac{d}{dt} 0.15 e^{-3.33 \times 10^3 t}$$

$$= -450 e^{-3.33 \times 10^3 t}$$

At $t=0$, $V_L(t) = -450 \text{ V}$

Q.

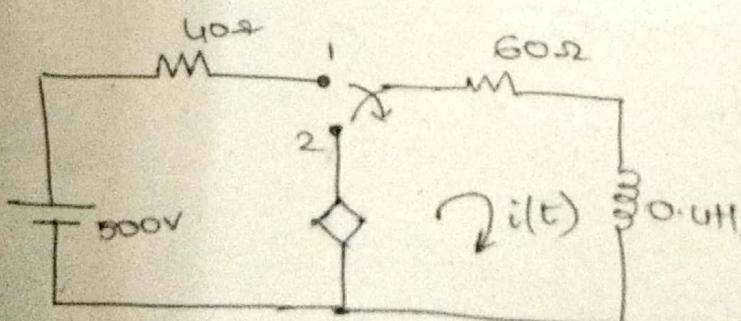

26/8/2019
Monday

Find $i(t)$ when switch is changed from ① to ② at $t=0$.

$$t=0^-$$

$$i(0^-) = \frac{500}{100} = 5 \text{ A}$$

$$i(0^+) = 5A$$

when position of switch
is changed from 1 to 2,

Applying KVL,

$$10i(t) - 60i(t) - 0.4 \frac{di(t)}{dt} = 0$$



$$\frac{di(t)}{dt} + \frac{50}{0.4} i(t) = 0$$

$$i(t) = Ce^{-pt}$$

$$= C e^{-125t}$$

$$\text{At } t=0, C=5$$

$$i(t) = 5e^{-125t} \quad (t>0)$$

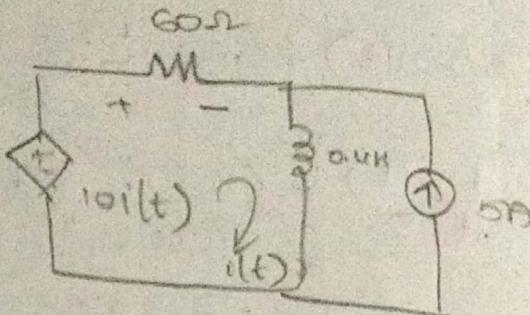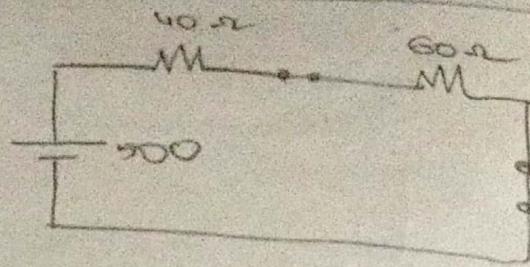

RC circuit:

$$V - Ri(t) - \frac{1}{C} \int i(t) dt = 0$$

$$0 - R \frac{di(t)}{dt} - \frac{1}{C} i(t) = 0$$

$$\frac{di(t)}{dt} + \frac{1}{RC} i(t) = 0 \rightarrow (1)$$

$$i(t) = Ce^{-pt} = Ce^{-t/RC}$$

$$t=0^+ \rightarrow i(0^+) = \frac{V}{R}$$


$$RC = \tau$$

$$\frac{V}{R} = Ce^{-0/RC} \rightarrow C = \frac{V}{R}$$


$$\rightarrow i(t) = \frac{V}{R} e^{-t/RC}$$

$$V_R = Ri(t) = Ve^{-t/RC}$$
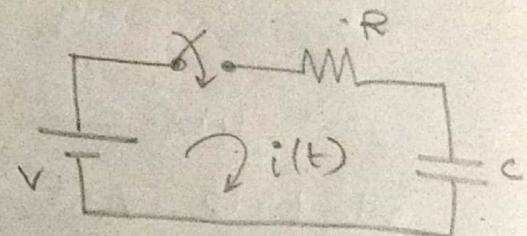
$$V_C = \frac{1}{C} \int_0^t i(t) dt = \frac{1}{C} \int_0^t \frac{V}{R} e^{-t/RC} dt$$


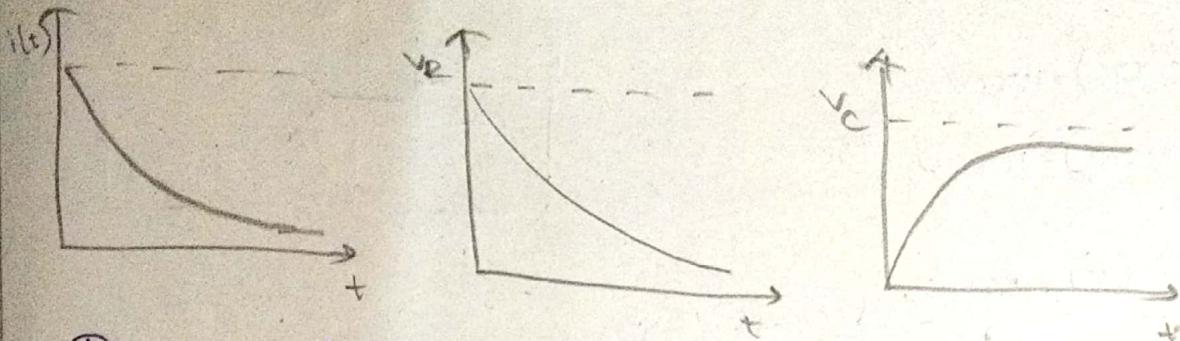
$$v_c = \frac{V}{RC} \left[e^{-t/RC} - e^0 \right] = V \left[1 - e^{-t/RC} \right]$$



$$P_R = v_R \times i(t)$$


$$= V e^{-t/RC} \times \frac{V}{R} e^{-t/RC}$$

$$= \frac{V^2}{R} e^{-2t/RC}$$

$$P_C = v_c \times i(t)$$

$$= V (1 - e^{-t/RC}) \times \frac{V}{R} e^{-t/RC}$$
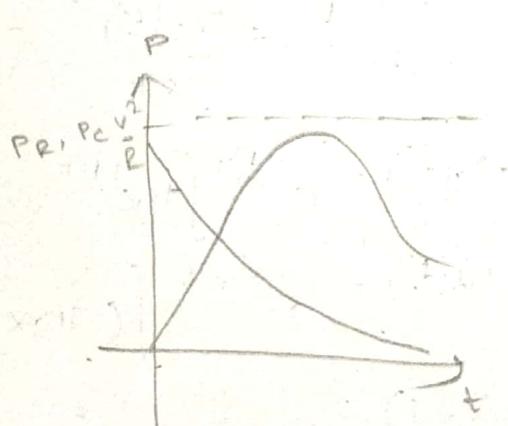
$$= \frac{V^2}{R} [e^{-t/RC} - e^{-2t/RC}]$$



- Q. A series RC circuit consists of 10Ω Resistor, 0.1F capacitor. A constant voltage of 20V is applied at $t=0$. Apply Obtain the current eq, v_R , v_c .

Sol: $i(t) = ?$



- Q. The switch in the circuit of figure moved from position 1 to 2 at $t=0$. Find $v_c(t)$.

Sol:

$t > 0^-$


$$v_c(0^-) = 100V$$

$$v_c(0^+) = 100V$$

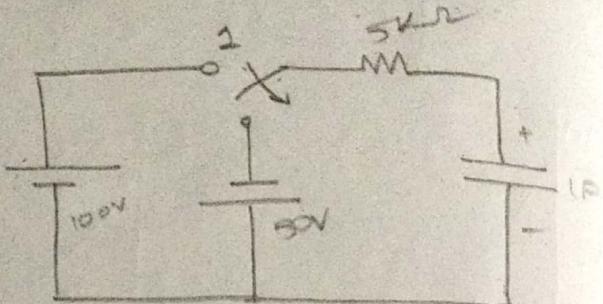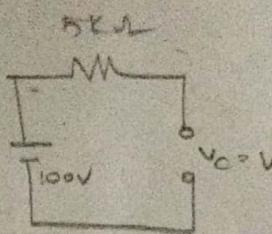

$$\frac{v_c(t) + 50}{5k} + \frac{d}{dt} v_c(t) = 0$$
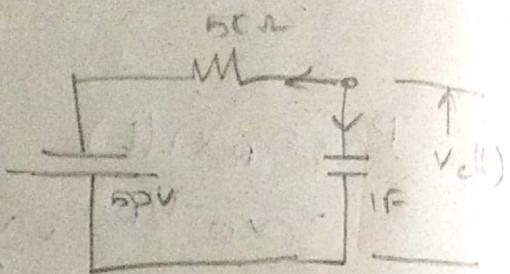
$$\frac{d v_c(t)}{dt} + \frac{v_c(t)}{5k} = -10 \times 10^{-3}$$



$$v_c(t) = e^{-Pt} \int e^{+Pt} + C e^{-Pt}$$

$$v_c(t) = e^{-\frac{1}{5k}t} \int (-10 \times 10^{-3}) e^{\frac{t}{5k}} + C e^{-\frac{t}{5k}}$$

$$v_c(t) = -0.25 \times 10^{-5} e^{-t/5k} + C e^{-t/5k}$$

$$v_c(t) = 50 + C e^{-t/5k}$$

$$t \rightarrow 0 \Rightarrow 100 = 50 + C$$


$$\therefore C = 50$$

$$v_c = 50 (1 + e^{-t/5k})$$

21/8/2019

Tuesday

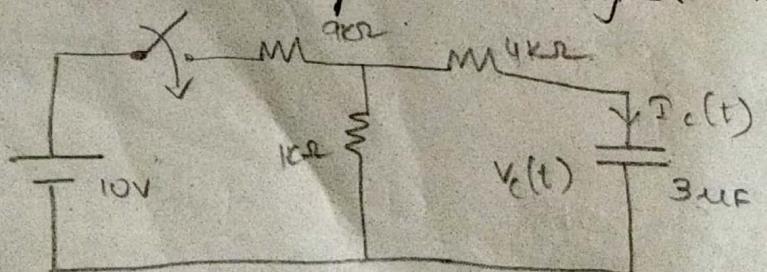- Q. In a network, the switch is closed at $t=0$, the capacitor is initially unchanged. Find $v_c(t)$ & $i_c(t)$



$$At = 0^+$$

$$V_C(0^+) = 0$$

$$I_C(0^+) = ?$$



$$I_T(0^+) = \frac{10V}{\left(\frac{4 \times 1 \times 10^9}{5 \times 10^3} + 9k\right) + 9k}$$

$$= \frac{10}{\frac{4}{5} \times 10^3 + 9 \times 10^3}$$

$$= \frac{10}{(6.8 + 9) \times 10^3}$$

$$\Rightarrow \frac{10}{9.8 \times 10^3} = \frac{1}{9.8 \times 10^2} = \frac{10^{-2}}{9.8} = 1.02 \text{ mA}$$
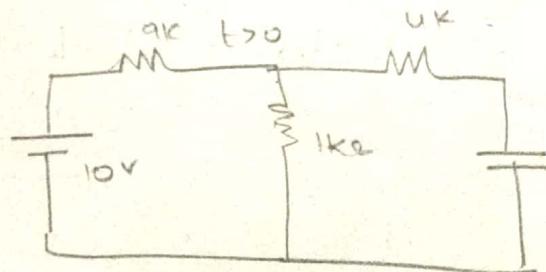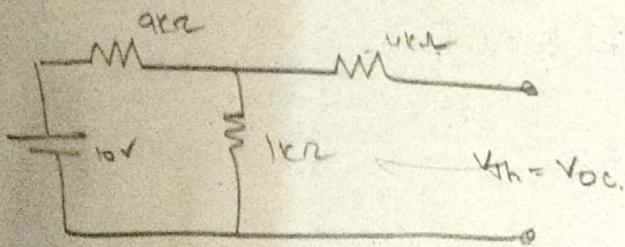
$$I_C(0^+) = I_T(0^+) \times \frac{1k}{5k} = \frac{1.02 \text{ mA}}{5} = 0.204 \text{ mA}$$



$$10 - 10kI = 0$$

$$\Rightarrow \frac{10}{10k} = 1 \text{ mA}$$


$$V_{TH} = V_{OC} = 1k \times 1 \text{ mA} = 1V$$

$$R_{TH} = \frac{9 \times 1k}{(9+1)k} + 4k = 4.9k\Omega$$

$$V_C(t) = e^{-Pt}$$

$$\frac{V_C(t) - 1}{4.9k} + 3 \times 10^{-6} \frac{d}{dt} V_C(t) = 0$$
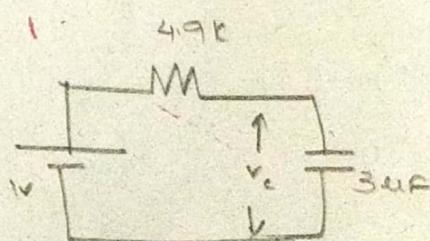
$$\frac{dV_C(t)}{dt} + \frac{V_C(t)}{4.9 \times 10^3 \times 3 \times 10^{-6}} = -\frac{1}{4.9 \times 3 \times 10^{-6}}$$



$$v_c(t) = e^{-Pt} \int e^{Pt} dt + ce^{-Pt}$$

$$= e^{-68.02t} \int 68.02 e^{68.02t} dt + ce^{-68.02t}$$

$$= e^{-68.02t} e^{68.02t} \times \frac{68.02}{68.02} + ce^{-68.02t}$$

$$= 1 + ce^{-68.02t}$$

$$\text{At } t=0^+ \rightarrow c=1$$


$$\Rightarrow v_c(t) = 1 - e^{-68.02t}$$

$$i(t) = C \frac{d v_c(t)}{dt} \rightarrow 3 \times 10^{-6} \frac{d}{dt} (1 - e^{-68.02t})$$

$$i(t) = 2.04 \times 10^{-4} e^{-68.02t}$$

- a. For the network, the switch is opened for long time and closes at $t=0$. Find $v_c(t)$.


Sol:

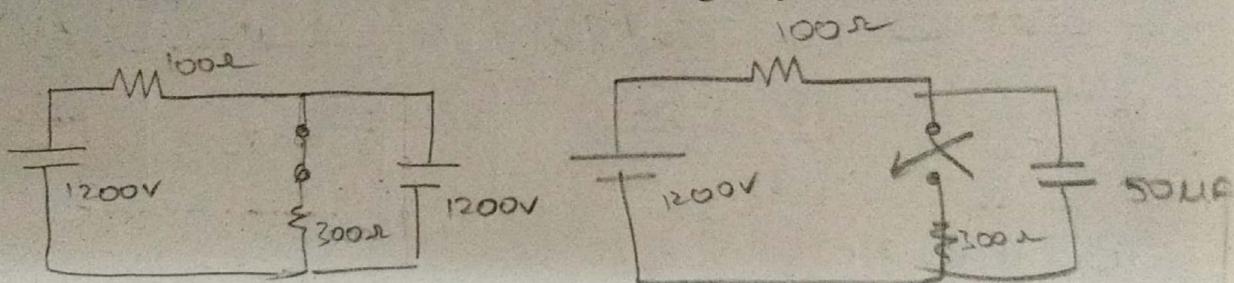

$$v_c(0^+) = 1200V$$

$$I_c(0^+) = \frac{1200}{100} = 12A$$
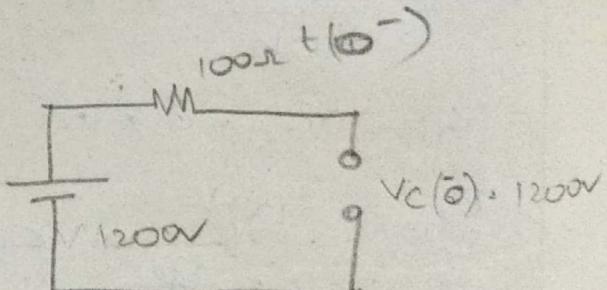
$$\frac{v_d(t) - 1200}{100} + \frac{v_c(t)}{300} + 50 \times 10^{-6} \frac{d v_c(t)}{dt} = 0$$



$$\Rightarrow \frac{v_c(t) - 1200}{100} + \frac{v_c(t)}{300} = -50 \times 10^{-6} \frac{d v_c(t)}{dt}$$

$$\Rightarrow \cancel{\frac{v_c(t)}{100}} + \frac{v_c(t)}{300} - 12 = -50 \times 10^{-6} \frac{d v_c(t)}{dt}$$

$$(-50 \times 10^{-6} \frac{d}{dt} v_c(t)) = 4 \times 10^{-3} v_c(t) - 12$$

$$\Rightarrow \frac{d}{dt} v_c(t) = \frac{4 \times 10^{-3}}{-50 \times 10^{-6}} v_c(t) - \frac{12}{-50 \times 10^{-6}}$$



$$\Rightarrow \frac{d}{dt} v_c(t) = -\frac{2 \times 10^3}{25} v_c(t) + \frac{12 \times 10^6}{50}$$

$$\Rightarrow \frac{d}{dt} v_c(t) + \frac{2 \times 10^3}{25} v_c(t) = \frac{12 \times 10^6}{50}$$

$$\Rightarrow \frac{d}{dt} v_c(t) + 800 v_c(t) = 24 \times 10^4$$

$$\Rightarrow v_c(t) = e^{-800t} \int)x$$

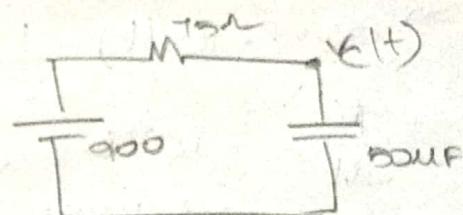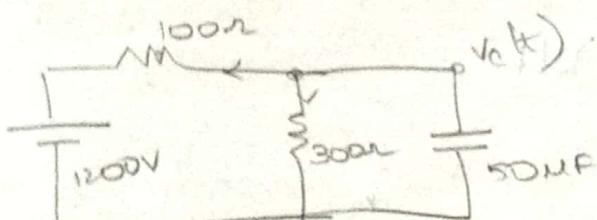
$$v_c(t) = 900 + 300 e^{-266.6 t} \quad \text{for } t > 0$$



$$v_{oc} = v_{Th} = \frac{1200}{400} \times 300 = 900 \text{ V.}$$

$$R_{Th} = \frac{100 \times 300}{400} = \frac{300}{4} = 75 \Omega$$

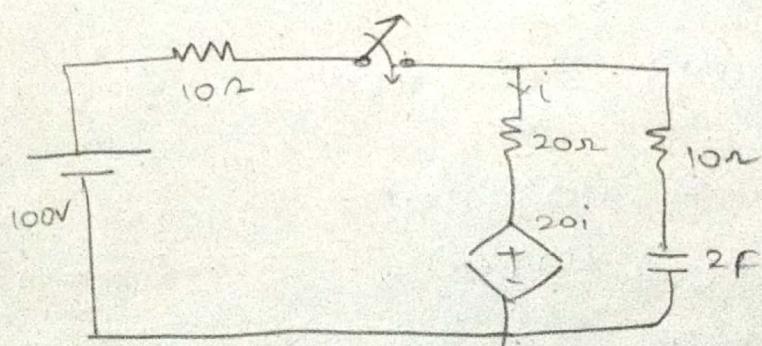- Q. Find the current $i(t)$ when the switch is opened at $t = 0$



$$100 - 10i(0^-) - 20i(0^-) = 0$$

$$100 = 50i(0^-)$$


$$i(0^-) = \frac{100}{50} = 2A$$

$$100 - 10i(0^-) \Rightarrow V_C(0^-)$$

$$100 - 10 \times 2 = V_C(0^-)$$

$$V_C(0^-) = 80V$$

$$i(0^-) = 2A, V_C(0^-) = 80V$$

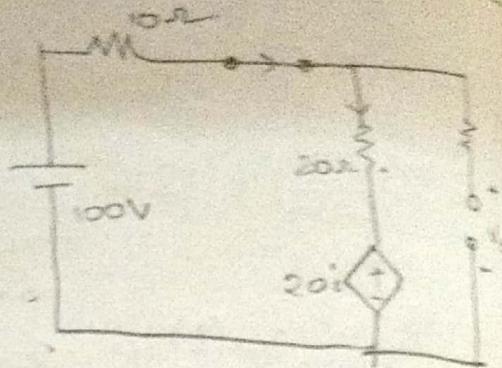

$$Y(20i(t) - 20i(t) - 10i(t))$$



$$-\frac{1}{2} \int i(t) dt - 80 = 0$$

$$\Rightarrow 80 = -10i(t) - \frac{1}{2} \int i(t) dt$$

$$\Rightarrow \frac{di}{dt} + 10^4 i = 0$$

$$\Rightarrow i = C e^{-1 \times 10^4 t}$$

At $t > 0^+$,

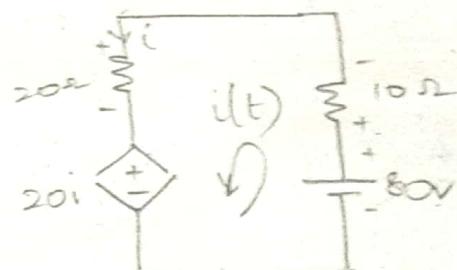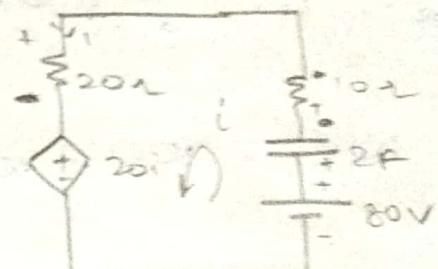

30/8/2019

Friday

Q1: $80 - 10i - 20i - 20i = 0$

$$80 = 50i$$

$$i(0^+) = \frac{80}{50} = 1.6A$$

put $t = 0$, $i(0) = 1.6A$

$$1.6 = C e^{-1 \times 10^4 (0)}$$


$$C = 1.6A$$

$$i = 1.6 e^{-1 \times 10^4 t}$$

* RC circuit:

$$V - Ri(t) - \frac{1}{C} \int i(t) dt =$$

$$\frac{d^2 i(t)}{dt^2} = 0$$

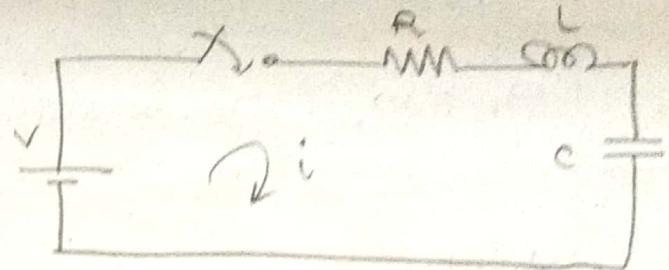

$$0 - R \frac{di(t)}{dt} - \frac{1}{C} i(t) - L \frac{d^2 i(t)}{dt^2} = 0$$

$$R \frac{di(t)}{dt} + \frac{1}{C} i(t) + L \frac{d^2 i(t)}{dt^2} = 0$$

$$L \frac{d^2 i(t)}{dt^2} + \frac{1}{C} i(t) + R \frac{di(t)}{dt} = 0$$

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

$$\omega_1, \omega_2 = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\left[\frac{d^2 i}{dt^2} + \alpha_1 \frac{di}{dt} + \alpha_2 i = 0 \right]$$

$$\omega_1, \omega_2 = -\frac{\alpha_1}{2} \pm \sqrt{\left(\frac{\alpha_1}{2}\right)^2 - \alpha_2}$$





→ Critical resistance R_{cr} is given by,

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$$

$$\frac{R_{cr}^2}{4L^2} = \frac{1}{LC}$$

$$\Rightarrow R_{cr} = 2 \sqrt{\frac{L}{C}}$$

Note!

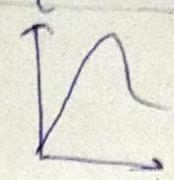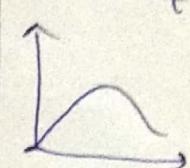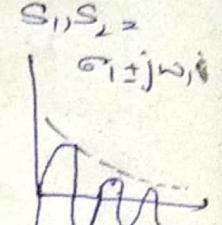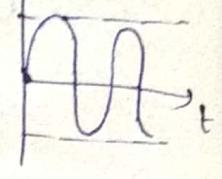Coeff of condition	Nature of roots	Descriptive name	Soln	Graph
$\alpha_1^2 > 4\alpha_2$	-ve, real & =	overdamped -ped	$i = k_1 e^{S_1 t} + k_2 e^{S_2 t}$	
$\alpha_1^2 = 4\alpha_2$	-ve, real & =	critically damped	$i = k_1 e^{S_1 t} + k_2 t e^{S_2 t}$	
$\alpha_1^2 < 4\alpha_2$	complex conj. real part -ve	under damped	$i = e^{\sigma_1 t} (k_1 \cos \omega_1 t + k_2 \sin \omega_1 t)$	$S_1, S_2 = \sigma \pm j\omega_1$ 
$\alpha = 0$ $\alpha_2 \neq b$	conjugate imaginary	oscillatory	$i = k_1 \cos \omega_1 t + k_2 \sin \omega_1 t$ $S_1, S_2 = \pm j\omega_1$	

→ Damping ratio is the ratio of actual resistance to the critical value of resistance.

$$\text{Damping ratio} = \frac{R}{R_{cr}} = \frac{R}{2\sqrt{LC}} = \xi$$

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$\omega_n = \frac{1}{\sqrt{LC}}$$

$$2\xi\omega_n = 2 \times \frac{R}{2\sqrt{LC}} \times \frac{1}{\sqrt{LC}} = \frac{R}{L}$$

$$\frac{d^2 i}{dt^2} + 2\zeta \omega_n \frac{di}{dt} + \omega_n^2 i = 0$$

$$s_1, s_2 = -\zeta \omega_n \pm \sqrt{(\omega_n)^2 - (\zeta^2 - 1)} = -\zeta \omega_n \pm \omega_n \sqrt{\zeta^2 - 1}$$

$$Q \cdot \omega_n \left(\frac{L}{R} \right) \Rightarrow \omega_n \times \frac{1}{2Q\omega_n} = \frac{1}{2Q}$$

$$\therefore 2Q = \frac{1}{Q}$$

$$\frac{d^2 i}{dt^2} + \frac{\omega_n}{Q} \frac{di}{dt} + \omega_n^2 i = 0.$$

$$i = k_1 e^{s_1 t} + k_2 e^{s_2 t}$$

$$= k_1 e^{(-\zeta \omega_n + \omega_n \sqrt{\zeta^2 - 1})t} + k_2 e^{(-\zeta \omega_n - \omega_n \sqrt{\zeta^2 - 1})t}$$

→ Damping ratio (ζ) varies from 0 to ∞
 $(\because R \rightarrow 0 \text{ to } \infty)$


→ $\zeta > 1$ - over damped case

$\zeta = 1$ - critically damped case

$\zeta < 1$ - under damped case

$\zeta = 0$ - oscillatory ($R = 0$)

→ Root locus is given by,

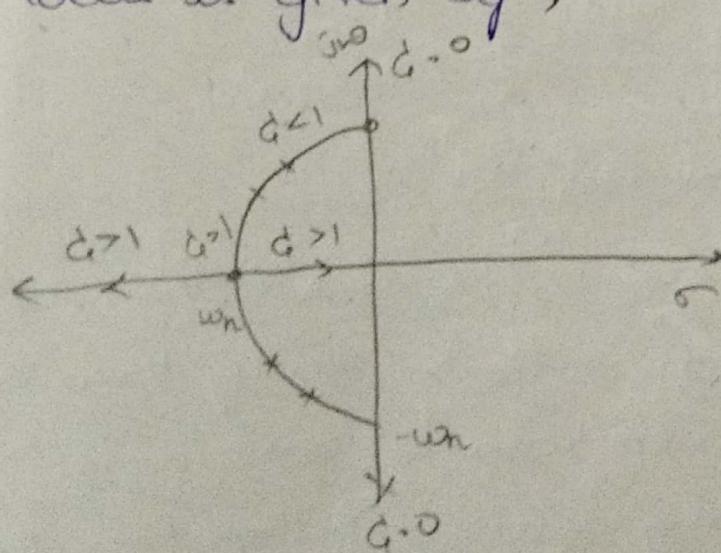

Two port network parameters

- Generally any network may be represented by a pair of terminals at which a signal may enter or leave the port.
- A port is defined as any pair of terminals into which energy is supplied or from which energy is withdrawn where network variables may be measured.
- A 2-port network is simply ~~a~~ inside a black box and network has only 2 pairs of accessible network terminals.
- Usually, 1 pair represents i/p and 2nd pair represents o/p.
- Such a network is common in electronics, communication, transmission and distribution.




2port network.

- 2ports containing no sources in their branches are called passive ports. Among them are power transmission lines & transformers.
- 2ports containing sources in their branches are called active ports. A voltage or current is

Two port network parameters

- Generally any network may be represented by a pair of terminals at which a signal may enter or leave the port.
- A port is defined as any pair of terminals at which energy is supplied or from which energy is withdrawn where network variables may be measured.
- A 2-port network is simply a inside a black box and network has only 2 pairs of accessible network terminals.
- Usually, 1 pair represents i/p and 2nd pair represents o/p.
- Such a network is common in electronics, communication, transmission and distribution.

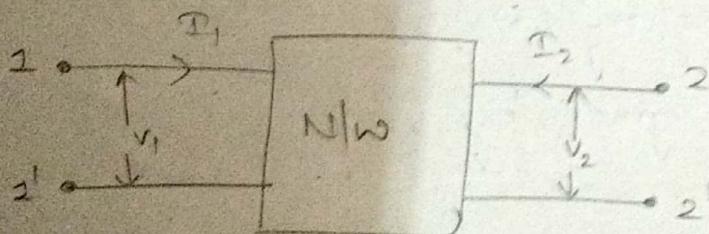

2port network

- 2 ports containing no sources in their branches are called passive ports. Among them are power transmission lines & transformers.
- 2 ports containing sources in their branches are called active ports. A voltage or current is

assigned to each of 2 ports.

→ Possible combinations with V_1, V_2, I_1, I_2 .

Parameters.	Expression	In terms of
1. Z parameters	$V_1 V_2$	$I_1 I_2$
2. Y parameters	$I_1 I_2$	$V_1 V_2$
3. Transmission	$V_1 I_1$	$V_2 I_2$
4. Inverse transmission	$V_2 I_1$	$V_1 I_2$
5. Hybrid	$V_1 I_2$	$I_1 V_2$
6. Inverse hybrid	$I_1 V_2$	$V_1 I_2$

* Z-parameters:

- These are also called open circuit parameters.
- Z_{11} - Input impedance when o/p port is open circuited and it is also called as driving point i/p impedance.
- Z_{21} - forward transfer impedance when o/p port is open circuited. It is also called as o.c forward transfer impedance.
- Z_{12} - Reverse transfer impedance when i/p port is o.c and is also called as o.c reverse transfer impedance.
- Z_{22} - o/p impedance when o/p port is o.c and is also called open circuit o/p impedance.

$$\rightarrow V_1, V_2 = f(I_1, I_2)$$

$$V_1 = aI_1 + bI_2$$

$$V_2 = cI_1 + dI_2$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$


$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

(*) Conditions for reciprocity:

\rightarrow A network is said to be reciprocal, if the ratio of excitation of 1 port to response at other port is same if excitation & response are interchanged.

Case - 1:

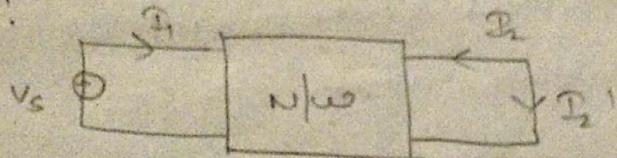

$$V_1 = V_s$$

$$V_2 = 0$$

$$V_1 = Z_{11}I_1 + Z_{12}I_2$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$V_s = Z_{11}I_1 - Z_{12}I_2$$


$$0 = Z_{21}I_1 - Z_{22}I_2$$

$$\Rightarrow I_1 = \frac{Z_{22}I_2}{Z_{21}}$$

$$\Rightarrow V_s = Z_{11} \left[\frac{Z_{22}}{Z_{21}} I_2 \right] - Z_{12}I_2$$

$$\Rightarrow \frac{V_s}{I_2} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{21}}$$

Case-2:

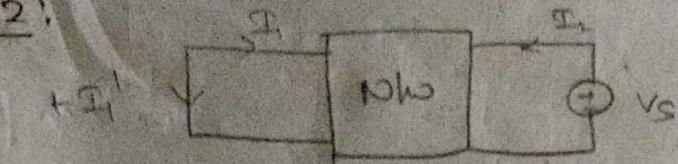

$$V_2 = V_S \quad V_1 > 0 \quad I_1 = -I_1'$$

$$\frac{V_S}{I_1'} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{12}}$$

$$\frac{V_S}{I_2'} = \frac{V_S}{I_1'} \text{ if } Z_{12} = Z_{21}$$

(c) Conditions for symmetry:

- For a nlc to be symmetrical, the voltage to current ratio at one port should be same as the voltage to current ratio at another port with one of the port open circuited.

case-1: If o/p is O.C

$$I_2 = 0$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$\rightarrow Z_{11} = V_1 / I_1$$

It is symmetrical, if $\frac{V_1}{I_1} = \frac{V_2}{I_2} \Rightarrow Z_{11} = Z_{22}$

case-2: If o/p is O.C

$$I_1 = 0$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$Z_{22} = V_2 / I_2$$

(d) Find the z parameters.

$$\text{put } I_2 = 0$$

$$V_1 = Z_1 I_1 + Z_2 (I_1 - I_2)$$

$$V_1 = (Z_1 + Z_2) I_1$$


$$Z_{11} = \frac{V_1}{I_1} = Z_1 + Z_2$$


$$\rightarrow V_2 = I_1 Z_2$$

$$Z_{21} = \frac{V_2}{I_1} = Z_2$$

$$\text{Now put } I_1 = 0 \Rightarrow Z_{22} = \frac{V_2}{I_2} = Z_2 + Z_3$$

$$Z_{12} = \frac{V_1}{I_2} = Z_1$$

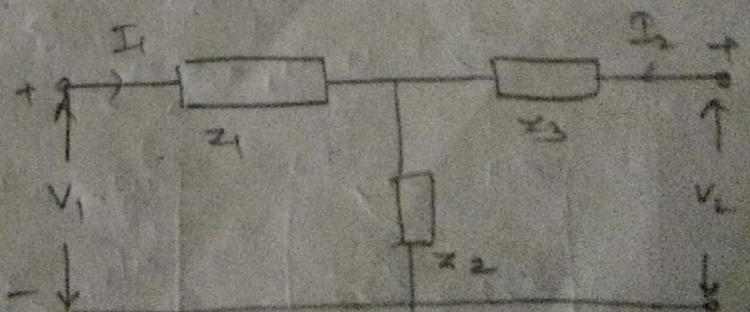

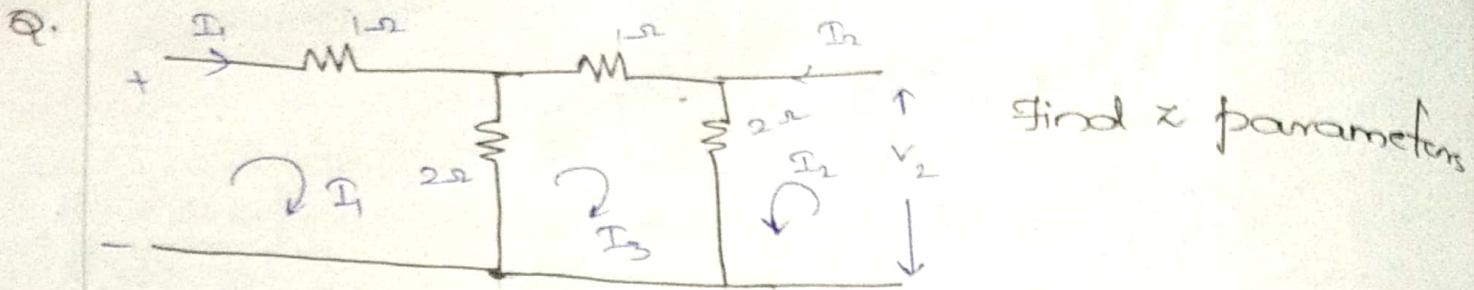

Find Z parameters

Sol:

$$v_1 = 3I_1 - 2I_3 \quad \dots (1)$$

$$v_2 = 2(I_2 + I_3) = 2I_2 + 2I_3 \quad \dots (2)$$

$$-2I_1 + 2I_2 + 5I_3 = 0 \quad \dots (3)$$

$$I_3 = \frac{2I_2 + 2I_1}{5}$$

$$\Rightarrow I_3 = 0.4I_2 + 0.4I_1 \quad \dots (4)$$

Sub (4) in (1) & (2)

$$\Rightarrow v_1 = 3I_1 - 2 \left[\frac{2}{5}I_1 + \frac{2}{5}I_2 \right]$$

$$\Rightarrow 3I_1 - \frac{4}{5}I_1 + \frac{4}{5}I_2$$

$$\Rightarrow v_1 = \frac{11}{5}I_1 + \frac{4}{5}I_2$$


$$v_2 = 2I_2 + 2 \left[\frac{2}{5}I_1 + \frac{2}{5}I_2 \right]$$

$$\Rightarrow 2I_2 + \frac{4}{5}I_1 - \frac{4}{5}I_2$$

$$\Rightarrow \frac{4}{5}I_1 + \frac{6}{5}I_2$$

$$\Rightarrow \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} 11/5 & 4/5 \\ 4/5 & 6/5 \end{bmatrix}$$

Q.

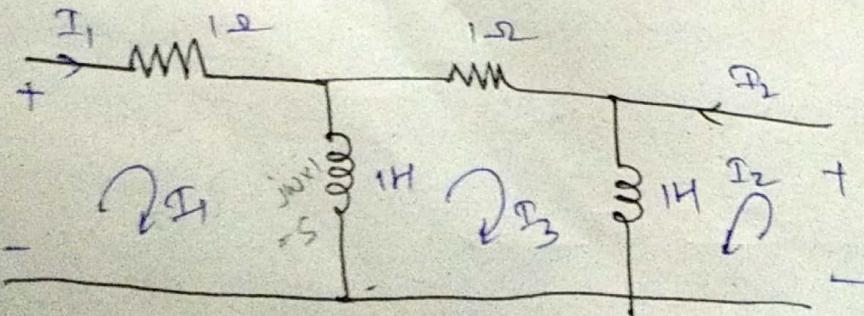

Find Z parameters

$$V_1 = I_1 + S I_1 - S I_3 \quad (1)$$

$$V_2 = S(I_2 + I_3) = S I_2 + S I_3 \quad (2)$$

$$2S I_3 + I_3 - S I_1 = 0 + S I_2 = 0$$

$$2S I_3 + I_3 + S(I_2 - I_1) = 0$$

$$(2S+1) I_3 + S(I_2 - I_1) = 0$$

$$I_3 = \frac{-S(I_2 - I_1)}{2S+1}$$

$$I_3 = \frac{S(I_1 - I_2)}{2S+1} \quad (3)$$

Sub (3) in (1) & (2),

$$V_1 = I_1 + S I_1 - S \left[\frac{S(I_1 - I_2)}{2S+1} \right]$$


$$= I_1 + S I_1 - \frac{S^2 I_1}{2S+1} + \frac{S^2 I_2}{2S+1}$$

$$= I_1 \left[1 + S - \frac{S^2}{2S+1} \right] + \frac{S^2 I_2}{2S+1}$$

$$= I_1 \left[\frac{2S+1+2S^2+S-S^2}{2S+1} \right] + \frac{S^2 I_2}{2S+1}$$

$$\text{Hence } V_2 = \frac{S^2}{2S+1} I_1 + \frac{S^2+S}{2S+1} I_2$$
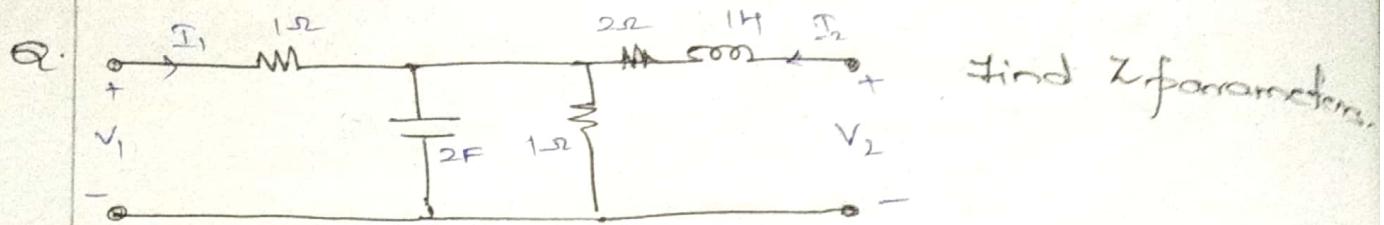
$$\therefore \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{S^2+3S+1}{2S+1} & \frac{S^2}{2S+1} \\ \frac{S^2}{2S+1} & \frac{S^2+S}{2S+1} \end{bmatrix}$$



For T circuit,

$$Z_{11} = Z_1 + Z_2$$

$$Z_{22} = Z_2 + Z_3$$

$$Z_{12} = Z_{21} = Z_2$$


$$Z_1 = 1$$

$$Z_2 = 2s \parallel 1/s$$

$$Z_3 = 2 + s$$

we get,
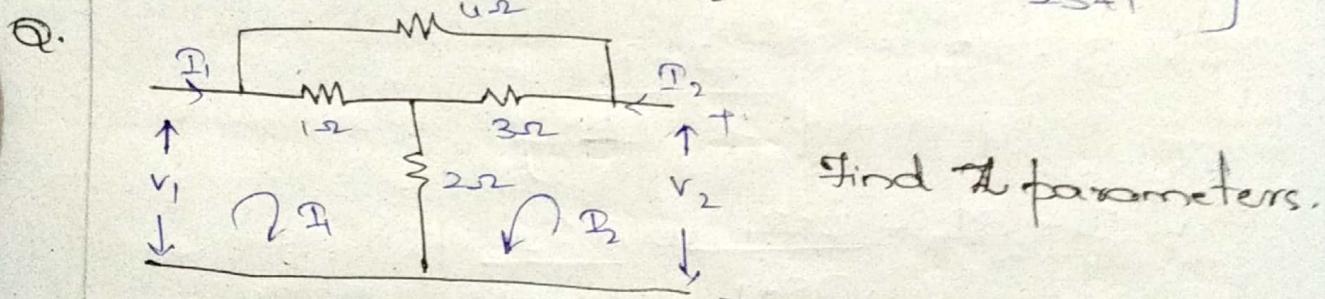
$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} \frac{2s+2}{2s+1} & \frac{1}{2s+1} \\ \frac{1}{2s+1} & \frac{2s^2+5s+3}{2s+1} \end{bmatrix}$$



* γ -parameters :

→ These are also called ^{Admittance} ~~impedance~~ parameters, short circuit parameters.

$$(I_1, I_2) = f(v_1, v_2)$$

$$I_1 = \gamma_{11} v_1 + \gamma_{12} v_2 \quad \text{--- (1)}$$

$$I_2 = \gamma_{21} v_1 + \gamma_{22} v_2 \quad \text{--- (2)}$$

Case-1:

short circuit at o/p port, $v_2 = 0$

$$I_1 = \gamma_{11} v_1$$

$$\gamma_{11} = I_1 / v_1 \quad / v_2 = 0$$

$$I_2 \rightarrow Y_{21} V_1$$

$$Y_{21} = \frac{I_2}{V_1} \quad / V_2 = 0$$

Case-2 :

Short circuit at o/p port, $V_1 = 0$


$$I_1 = Y_{12} V_2$$

$$Y_1 = \frac{I_1}{V_2} \quad / V_1 = 0$$

$$I_2 = Y_{22} V_2$$

$$Y_{22} = \frac{I_2}{V_2} \quad / V_1 = 0.$$


→ Equivalent circuit of γ parameters is

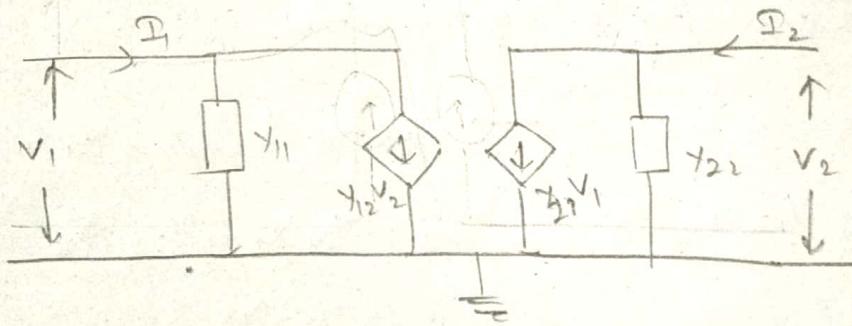

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

- Y_{11} is the driving pt admittance with o/p port sc.
- Y_{11} is also called short circuit i/p admittance.
- Y_{21} is the transfer admittance with o/p port sc.
- Y_{21} is also called short circuit transfer (forward) admittance
- Y_{12} is the transfer admittance with i/p port sc
- Y_{12} is also called SC reverse transfer admittance.
- Y_{22} is the SC driving pt admittance with i/p port sc.
- Y_{22} is also called SC o/p admittance.

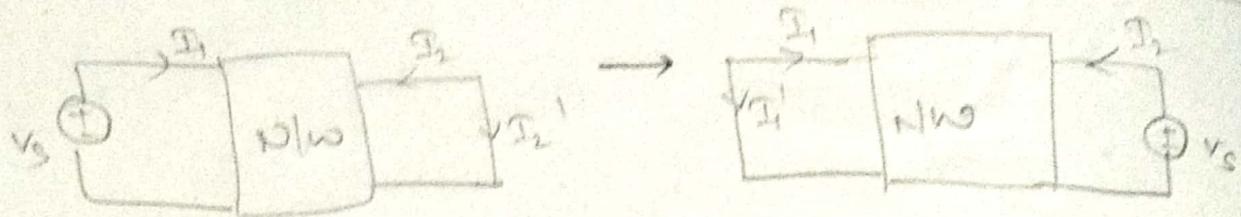

$$V_1 = V_S$$

$$V_2 = 0$$

$$I_2 = -I_2'$$

$$I_1 = Y_{11} V_S$$

$$-I_2' = Y_{21} V_S$$

$$\frac{V_S}{I_2'} = \frac{-1}{Y_{21}}$$

$$\rightarrow \frac{V_S}{I_2'} = \frac{V_S}{I_1} \rightarrow \frac{-1}{Y_{21}} = \frac{-1}{Y_{12}} \rightarrow Y_{21} = Y_{12}$$

Hence, reciprocity is applicable.

→ o/p port s.c., $V_2 = 0$

$$I_1 = Y_{11} V_S + Y_{12} V_2$$

$$I_1 = Y_{11} V_S$$

$$\frac{V_S}{I_1} = \frac{1}{Y_{11}}$$

→ i/p port s.c., $V_1 = 0$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$I_2 = Y_{22} V_S$$

$$\frac{V_S}{I_2} = \frac{1}{Y_{22}}$$

$$\rightarrow \frac{V_S}{I_1} = \frac{V_S}{I_2} \rightarrow \frac{1}{Y_{11}} = \frac{1}{Y_{22}} \rightarrow Y_{11} = Y_{22}$$


Hence, symmetry is applicable.

- Q. Test results of a 2-port networks are @
port 2 is sc, V_1 , $I_1 = 2.1 \angle 30^\circ A$,

$$I_2 = -1.1 \angle -20^\circ A$$

- (b) port 2 is sc $V_2 = 50 \angle 0^\circ$, $I_2 = +3 \angle -50^\circ$, $I_1 = -1.1 \angle -20^\circ A$

Q. Find the γ parameters for the network

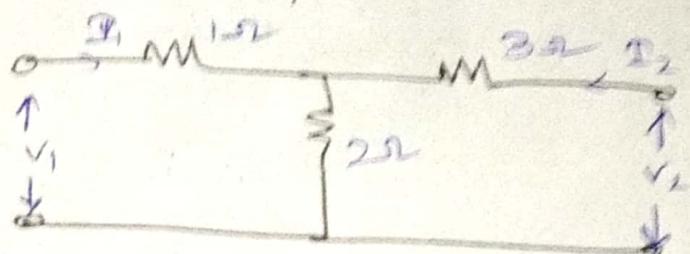

Case-1: S.C o/p port, $v_2 = 0$

$$\gamma_{11} = \frac{Z_1}{v_1}, \quad \gamma_{21} = \frac{Z_2}{v_1}$$

$$v_1 = ((3||2) + 1) Z_1$$

$$\gamma_{11} = \frac{Z_1}{v_1} = \frac{5}{11} \approx 0.45$$

$$Z_2 = -Z_1 \times \frac{2}{2+3}$$

$$Z_2 = -\frac{5}{11} v_1 \times \frac{2}{5}$$

$$Z_2 = -\frac{2v_1}{11}$$

$$\frac{Z_2}{v_1} = -\frac{2}{11} \approx -0.18 = \gamma_{21}$$