

NOR-SR latch


- ① Non clocked flip flops.
- ② They are not dependent on clock signal for their operation
- ③ Latch is a sequential device that checks all its inputs continuously and changes its outputs accordingly at any time independent of clock signal.

NOR gate truth table


A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

$Q = P.S \Rightarrow$ Present state



$Q_{t+1} = N.S =$ Next state

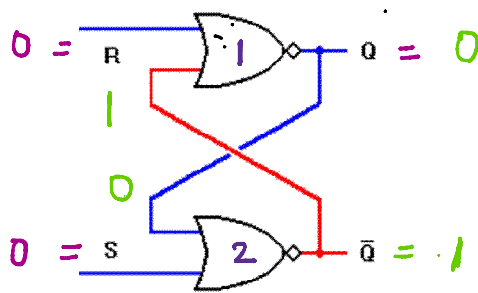

S	R	Q	Q_{t+1}	state
0	0	0	0	No change state
0	0	1	1	

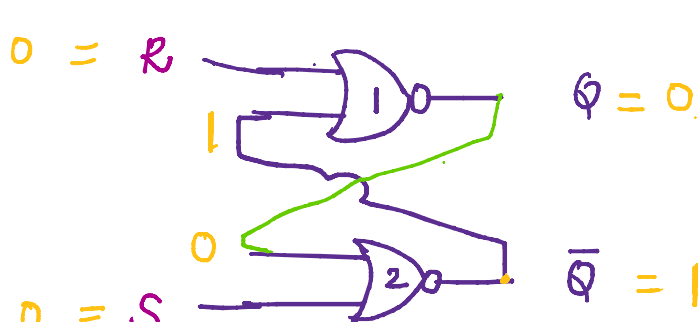


		P.S	N.S
S	R	Q	Q_{t+1}
0	0	0	0

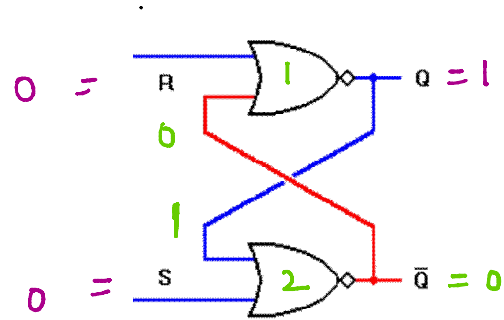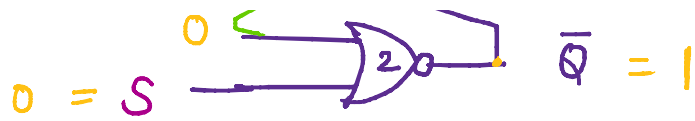



		P.S	N.S	
S	R	Q	Q_{t+1}	
0	0	1	1	

		P.S	N.S	
S	R	Q	Q_{t+1}	
0	0	0	0	} No change state
0	0	1	1	


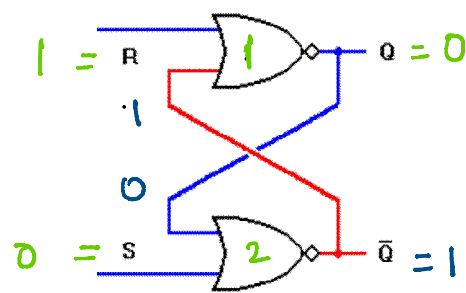


S	R	P.S Q	N.S Q_{t+1}	state
0	1	0	0	} Reset state
0	1	1	0	

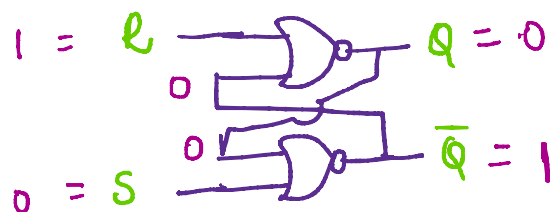


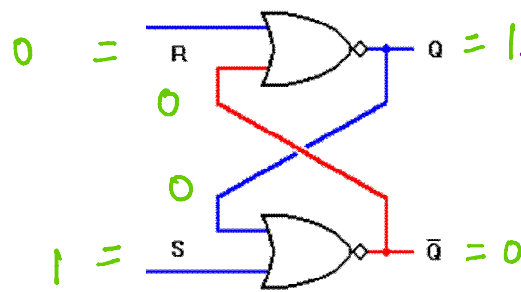

S	R	P-S Q	N-S Q_{t+1}	state
1	0	0	1	} set
1	0	1	1	

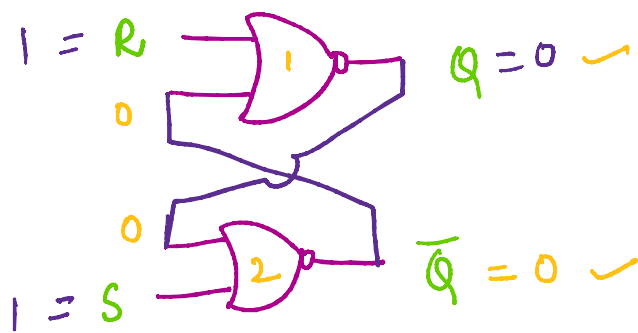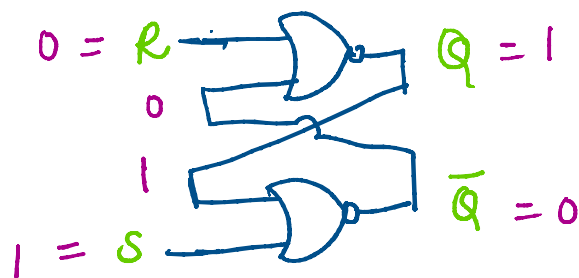


S	R	Q	Q_{t+1}	state
1	1	0	x	} Not used
1	1	1	x	

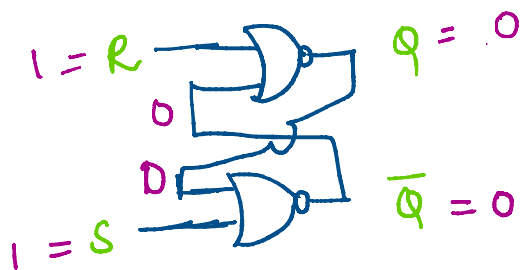

NOR gate S-R latch (b) Active high S-R latch

NOR gate S-R latch

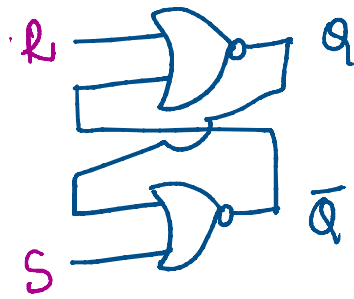

Truth table

			N-S	
S	R	PS Q	Q(t+1) Q(t)	State
0	0	0	0	No change
0	0	1	1	
0	1	0	0	Reset state
0	1	1	0	
1	0	0	1	Set state
1	0	1	1	
1	1	0	x	Not used
1	1	1	x	