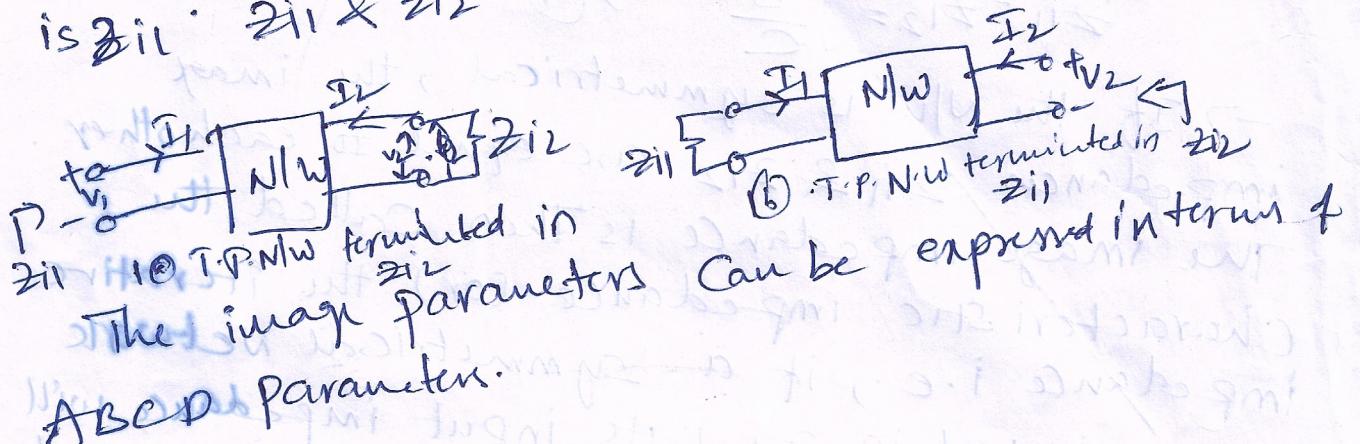


IMAGE PARAMETERS:-

The image impedance z_{11} & z_{12} of two port N are two values of impedance such that, if the port 1 of the network is terminated in z_{11} , the input impedance of the port 2-2' is z_{12} ; and if the port 2-2' is terminated in z_{12} , the input impedance at the port 1 is z_{11} . z_{11} & z_{12} are also known image parameters.



ABC D parameters.

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

if the N/w is terminated in z_{12} at 2-2'

$$V_2 = -I_2 z_{12}$$

$$\frac{V_1}{I_1} = \frac{A V_2 - B I_2}{C V_2 - D I_2} = \frac{-A I_2 z_{12} - B I_2}{-C I_2 z_{12} - D I_2}$$

$$I_1 = \frac{-A z_{12} - B}{-C z_{12} - D} = \frac{A z_{12} + B}{C z_{12} + D} \rightarrow ①$$

$$z_{11} = \frac{-A z_{12} - B}{-C z_{12} - D} = \frac{A z_{12} + B}{C z_{12} + D}$$

Similarly if the N/w is terminated in z_{11} at 1-1'

$$V_1 = -I_1 z_{11}$$

$$\frac{V_2}{I_2} = z_{12}$$

$$-z_{11} = \frac{V_1}{I_1} = \frac{A V_2 - B I_2}{C V_2 - D I_2} = \frac{A I_2 z_{12} - B I_2}{C I_2 z_{12} - D I_2}$$

$$-z_{11} = \frac{A z_{12} - B}{C z_{12} - D} \Rightarrow -C z_{11} z_{12} + D z_{11} = A z_{12} - B$$

$$z_{12} [A + C z_{11}] = B + D z_{11}$$

$$z_{12} = \frac{D z_{11} + B}{C z_{11} + A}$$

$$\rightarrow ②$$

Substitute z_{11} in the above equation.

$$z_{12} \left[C \left(\frac{-Az_2 + B}{Cz_{12} - D} \right) + A \right] = D \left[\frac{-Az_2 + B}{Cz_{12} - D} \right] + B$$

Solving eqn ① & ②.

$$z_{11} = \sqrt{\frac{AB}{CD}} \quad \& \quad z_{12} = \sqrt{\frac{BD}{AC}} \rightarrow ③$$

If the network is symmetrical, then $A=D$.

$$z_{11} = z_{12} = \sqrt{\frac{B}{C}} \rightarrow ④$$

→ If the N/w is symmetrical, the image impedances z_{11} & z_{12} are equal to each other. The image impedance is then called the characteristic impedance (or) the iterative impedance i.e., if a symmetrical Network is terminated in z_L , its input impedance will also be z_L . (or) its impedance transformation ratio is unity.

→ Since a reciprocal network can be described by two independent parameters, the image parameters z_{11} & z_{12} are sufficient to characterize reciprocal symmetric networks. z_{11} & z_{12} , the two image parameters do not completely define a network. A third parameter called image transfer constant is also used to describe reciprocal networks. This parameter may be obtained from the voltage & current ratios.

If the image impedance z_{12} is connected across the port 2-2, Then

$$V_1 = AV_2 - BI_2 \rightarrow ⑤$$

$$V_2 = -I_2 z_{12} \Rightarrow I_2 = \frac{V_2}{z_{12}} \rightarrow ⑥$$

$$V_1 \left[A + \frac{B}{z_{12}} \right] V_2 \rightarrow ⑦$$

$$I_1 = CV_2 - DI_2 \rightarrow ⑧$$

$$I_1 = -[(CZ_{12} + D)I_2] \rightarrow ⑨$$

from ⑧

$$\frac{V_1}{V_2} = \left[A + \frac{B}{Z_{12}} \right] = A + B \sqrt{\frac{AC}{BD}}$$

$$\frac{V_1}{V_2} = A + \frac{\sqrt{ABCD}}{D} = \frac{AD + \sqrt{ABCD}}{D} \rightarrow ⑩$$

From ⑨

$$\frac{-D}{I_2} = [CZ_{12} + D] = D + C \sqrt{\frac{BD}{AC}}$$

$$= D + \sqrt{\frac{ABCD}{A}} = \frac{AD + \sqrt{ABCD}}{A} \rightarrow ⑪$$

Multiply can ⑩ & ⑪

$$-\frac{V_1}{V_2} \times \frac{I_1}{I_2} = \frac{AD + \sqrt{ABCD}}{D} \times \frac{AD + \sqrt{ABCD}}{A}$$

$$-\frac{V_1}{V_2} \times \frac{I_1}{I_2} = \frac{(AD)^2 + ABCD + 2AD\sqrt{ABCD}}{AD}$$

$$= AD + BC + 2\sqrt{ABCD} = \boxed{[AD + BC]^2}$$

$$\sqrt{AD} + \sqrt{BC} = \sqrt{\frac{-V_1}{V_2} \times \frac{I_1}{I_2}}$$

$$\sqrt{AD} + \sqrt{AD-1} = \sqrt{\frac{-V_1}{V_2} \times \frac{I_1}{I_2}}$$

$\therefore AD - BC \neq 0$

Let $\cosh \phi = \sqrt{AD}$ $\sinh \phi = \sqrt{AD-1}$

$$\tanh \phi = \frac{\sqrt{AD-1}}{\sqrt{AD}} = \sqrt{\frac{BC}{AD}}$$

$$\phi = \tanh^{-1} \sqrt{\frac{BC}{AD}} \rightarrow e^\phi = \cosh \phi + \sinh \phi = \sqrt{\frac{V_1}{V_2} \times \frac{I_1}{I_2}}$$

$$\phi = \log \sqrt{\frac{-V_1}{V_2} \times \frac{I_1}{I_2}} = \frac{1}{2} \log e \left(\frac{-V_1}{V_2} \times \frac{I_1}{I_2} \right)$$

Since $V_1 = Z_{11} I_1$ $V_2 = -I_2 Z_{12}$


$$\phi = \frac{1}{2} \log e \left(\frac{Z_{11} I_1}{Z_{12} I_2} \times \frac{I_1}{I_2} \right) \Rightarrow \phi = \frac{1}{2} \log e \frac{Z_{11} \log \frac{I_1}{I_2}}{Z_{12}}$$

For symmetric reciprocal N.L.
 $Z_{11} = Z_{12}$
 All properties

$$\phi = \log e \left(\frac{I_1}{I_2} \right) \in R$$

T-Network :-

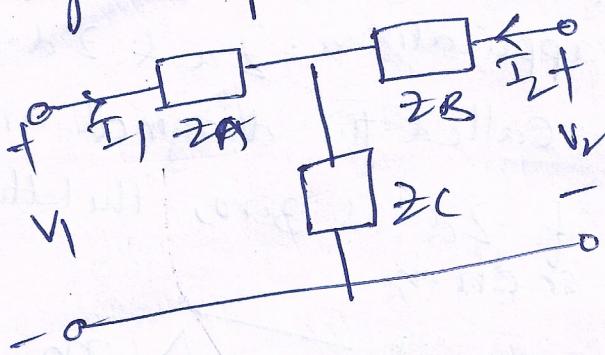Any two port N/w can be represented by an equivalent T network. The elements of the equivalent T network may be expressed in terms of Z-parameter.



$$V_1 = (Z_A + Z_C)I_1 + Z_C I_2$$

$$V_2 = Z_C I_1 + (Z_B + Z_C)I_2$$

$$Z_{11} = Z_A + Z_C \quad Z_{12} = Z_C$$

$$Z_{21} = Z_C \quad Z_{22} = Z_B + Z_C$$

$$Z_A = Z_{11} - Z_C = Z_{11} - Z_{12} = Z_{11} - Z_{21}$$


$$Z_B = Z_{12} = Z_{21}$$

$$Z_C = Z_{22} - Z_C = Z_{22} - Z_{21} = Z_{22} - Z_{12}$$

II-Network :-

Any two port N/w can be represented by an equivalent II N/w

$$\frac{V_1}{V_2} =$$

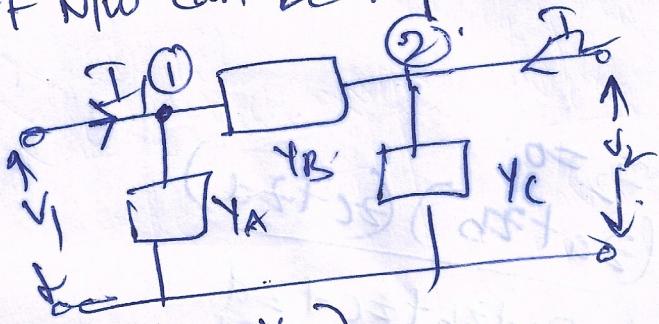

$$I_1 = Y_A V_1 + Y_B (V_1 - V_2)$$

$$I_1 = (Y_A + Y_B) V_1 - Y_B V_2 \quad \text{KCL at node 1}$$

$$I_2 = -Y_B V_1 + (Y_B + Y_C) V_2 \quad \text{KCL at node 2.}$$

$$Y_{11} = Y_A + Y_B$$

$$Y_{12} = Y_{21} = -Y_B$$

$$Y_{22} = Y_B + Y_C$$


$$Y_A = Y_{11} - Y_{12} = Y_{11} - Y_{12} = Y_{11} - Y_{21}$$

$$Y_B = Y_{12} = Y_{21}$$

$$Y_C = Y_{22} - Y_B = Y_{22} - Y_{12} = Y_{22} + Y_{21}$$

Lattice Networks:-

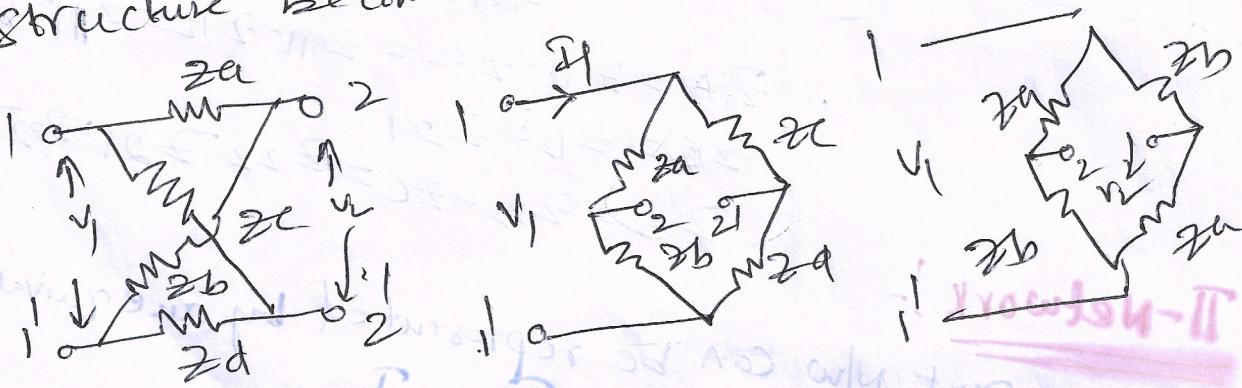one of the common four-terminal two-port N/w is the lattice (or) bridge N/w. Lattice N/w's are used in filter sections and are also used as attenuators. Lattice structures used in preference to ladder structures in some special applications. Z_a & Z_d are series arms & Z_b & Z_c are called the diagonal arms. It can be observed that, if Z_d is zero, the lattice structure becomes a Π -section.



$$Z_{11} = \frac{V_1}{I_1} \quad | \quad I_2 = 0 \\ V_1 = I_1 (Z_a + Z_b) (Z_c + Z_d)$$

$$\boxed{Z_{11} - \frac{V_1}{4} = \frac{(Z_a + Z_b)(Z_c + Z_d)}{Z_a + Z_b + Z_c + Z_d}}$$

i.e., $Z_a = Z_d$, $Z_b = Z_c$

$$\boxed{Z_{11} = \frac{Z_a + Z_b}{2}}$$

if N/w is symmetric

when $I_2 = 0$, V_2 is the voltage across $2-2'$

$$V_2 = V_1 \left[\frac{Z_b}{Z_b + Z_a} - \frac{Z_d}{Z_c + Z_d} \right]$$

$$= I_1 \frac{(Z_a + Z_b)(Z_c + Z_d)}{Z_a + Z_b + Z_c + Z_d} \left\{ \frac{-Z_b(Z_c + Z_d) - Z_d(Z_b + Z_a)}{(Z_a + Z_b)(Z_c + Z_d)} \right\}$$

$$\boxed{\frac{V_2}{Z_{22}}} = \frac{Z_b Z_c - Z_a Z_d}{Z_a + Z_b + Z_c + Z_d}$$

If the NW is symmetric $z_a = z_d, z_b = z_c$

$$z_{21} = \frac{z_b^2 - z_a^2}{2(z_a + z_b)} = \frac{(z_b - z_a)(z_a + z_b)}{2(z_a + z_b)}$$

$$\boxed{z_{21} = \frac{z_b - z_a}{2}}$$

when the top port is open, $I_1 = 0$:

$$z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$



$$V_1 = V_2 \left[\frac{z_c}{z_a + z_c} - \frac{z_d}{z_d + z_b} \right] \rightarrow \textcircled{1}$$

$$V_1 = V_2 = I_2 \frac{(z_a + z_c)(z_b + z_d)}{z_a + z_b + z_c + z_d} \rightarrow \textcircled{2}$$

$$\begin{aligned} V_1 &= I_2 \left[\frac{z_c(z_b + z_d) - z_d(z_a + z_c)}{(z_a + z_c)(z_d + z_b)} \right] \left[\frac{(z_a + z_c)(z_b + z_d)}{z_a + z_b + z_c + z_d} \right] \\ &= I_2 \left[\frac{z_c z_b + z_c z_d - z_c z_d - z_a z_d}{z_a + z_b + z_c + z_d} \right] \end{aligned}$$

$$z_{12} = \frac{V_1}{I_2} = \frac{z_c z_b - z_a z_d}{z_a + z_b + z_c + z_d}$$

If the network is symmetric

$$z_a = z_d \quad \& \quad z_b = z_c$$

$$\frac{V_1}{I_2} = \frac{z_b^2 - z_a^2}{2(z_a + z_b)} = \frac{(z_b - z_a)(z_b + z_a)}{2(z_a + z_b)} = \frac{z_b - z_a}{2} = \frac{z_c - z_d}{2}$$

$$z_{22} = \frac{V_2}{I_2} \Big|_{I_2=0}$$

$$\frac{V_2}{I_2} = \frac{(z_a + z_c)(z_b + z_d)}{z_a + z_b + z_c + z_d}$$

If the network is symmetric i.e., $z_a = z_d$; $z_b = z_c$

$$z_{22} = \frac{(z_a + z_b)(z_a + z_b)}{2(z_a + z_b)} = \frac{z_a + z_b}{2}$$

From the above equation.

$$z_{11} = z_{22} = \frac{z_a + z_b}{2}$$


$$z_{12} = z_{21} = \frac{z_b - z_a}{2}$$

$$\boxed{z_b = z_{11} + z_{12}}$$

$$\boxed{z_a = z_{11} - z_{12}}$$

Terminated Two-port Networks

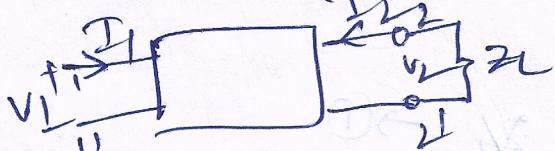② Driving-point impedance at the input port of a load terminated network:-



fig(1) Two port network

The output port. The input impedance of this Nw can be expressed in terms of parameters of the 2-port Nw.

In terms of Z parameters:-

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow ①$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow ②$$

The load at the $0/1$ port $2-2'$ imposes the following constraints on the port Voltage & Current.

$$V_2 = -Z_L I_2 \rightarrow ③$$

Substitute ③ in ②

$$-Z_L I_2 = Z_{21}I_1 + Z_{22}I_2$$

$$\Rightarrow I_2 = \frac{-Z_{21}}{Z_{22} + Z_L} I_1 \rightarrow ④$$

Substitute eqn ④ in ①

$$Z_{in} = \frac{V_1}{I_1} = Z_{11} + Z_{12} \left[\frac{-Z_{21}}{Z_{22} + Z_L} \right]$$

$$= Z_{11} + \frac{Z_{12} Z_{21}}{Z_{22} + Z_L} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22} + Z_L}$$

If the output port is open-circuited i.e. $Z_L = \infty$

$$Z_{in} = Z_L \left[\frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_L + Z_{22}} \right] = Z_{11}$$

If the output port is short-circuited i.e. $Z_L = 0$

$$Z_{in} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{22}} = \frac{1}{Y_{11}}$$

Fig shows a 2-port Nw connected to an ideal generator at the $0/p$ port and to a load impedance at

In terms of Y-parameters:-

If a load admittance Y_L is connected across the the output port

$$V_2 = -Z_L I_2$$

$$I_2 = -\frac{V_2}{Z_L} = -Y_L \frac{V_2}{Z_L} \rightarrow ①$$

$$I_1 = Y_{11} + Y_{12} V_2 \rightarrow ②$$

$$I_2 = Y_{21} + Y_{22} V_2 \rightarrow ③$$

Substitute eqn ① in ③

$$-V_2 Y_L = Y_{21} V_1 + Y_{22} V_2$$

$$V_2 = -\left(\frac{Y_{21}}{Y_L + Y_{22}}\right) V_1 \rightarrow ④$$

Substitute eqn ④ in ②

$$I_1 = Y_{11} V_1 - \frac{Y_{12} Y_{21} V_1}{Y_L + Y_{22}}$$

$$\frac{I_1}{V_1} = Y_{11} - \frac{Y_{12} Y_{21}}{Y_L + Y_{22}} = \cancel{\frac{Y_{12} Y_{11} Y_L + Y_{11} Y_{22} - Y_{12} Y_{21}}{Y_L + Y_{22}}}$$

$$\boxed{Z_{in} \frac{V_1}{I_1} = \frac{Y_L + Y_{22}}{Y_{11} Y_{22} - Y_{12} Y_{21} + Y_{11} Y_L}}$$


When o/p port is open-circuited i.e $Y_L = 0$

$$Z_{in} = \frac{Y_{22}}{Y_{11} Y_{22} - Y_{12} Y_{11}} = \frac{Y_{22}}{Y_{11}} = Z_{11} = \cancel{10 \Omega}$$

When o/p port is short-circuited i.e $Y_L = \infty$

$$Z_{in} = \frac{Y_{11} \left[1 + \frac{Y_{22}}{Y_{11}} \right]}{Y_{11} \left[\frac{Y_{11}}{Y_L} + Y_{11} \right]} = \frac{1}{Y_{11}}$$

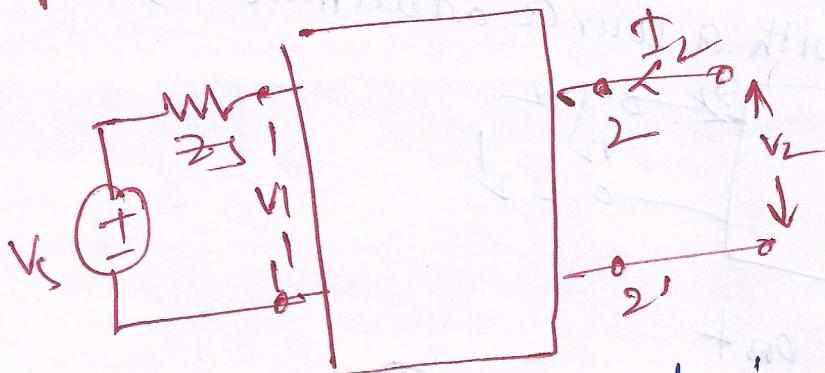(B) Driving point impedance at the output port with source impedance at the input port :-



Consider a 2-port N.H.s connected to a generator at the 1st port with a source impedance Z_S .

In terms of Z parameters:-

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \rightarrow ①$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \rightarrow ②$$

$$V_1 = V_s - I_1 Z_S \rightarrow ③$$

$$Z_{11}I_1 + Z_{12}I_2 = V_s - I_1 Z_S$$

$$-I_1 = \frac{Z_{12}I_2 - V_s}{Z_S + Z_{11}} \rightarrow ④$$

Substitute eqn ④ in ② we get.

$$V_2 = -Z_{21} \left[\frac{Z_{12}I_2 - V_s}{Z_S + Z_{11}} \right] + Z_{22}I_2$$

with no source voltage at the 1st port ($V_s = 0$), i.e. if the source V_s is short-circuited,

$$V_2 = \frac{-Z_{21}Z_{12}}{Z_S + Z_{11}} I_2 + Z_{22}I_2$$

the driving point impedance at the port 2 is $Z_D = Z_2$

$$\frac{V_2}{I_2} = \frac{Z_{21}Z_S + Z_{22}Z_{11} - Z_{21}Z_{12}}{Z_S + Z_{11}} \Rightarrow \frac{Z_2 + Z_{22}Z_S}{Z_S + Z_{11}}$$


If the 1st port is open $Z_S \rightarrow \infty$.

$$\frac{V_2}{I_2} = \frac{\Delta Z}{Z_S} + Z_{22} = Z_{22}$$

If the source impedance is zero with a short-circuited 1st port, the driving point impedance at the output port is given by $\frac{V_2}{I_2} = \frac{\Delta Z}{Z_S} = \frac{1}{Z_D}$.

Internals of Y-parameter:-

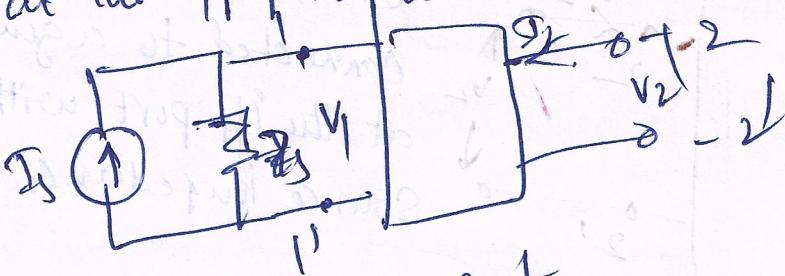Let us consider a two-port N/W connected to a current source at the 1st port with a source admittance y_s .



Eq at the port

$$I_1 = I_s - \frac{V_1}{Y_1} = I_s - V_1 Y_{11} \rightarrow ①$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \rightarrow ②$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \rightarrow ③$$

Substitute eqn ① & ②.

$$I_s - V_1 Y_{11} = Y_{11} V_1 + Y_{12} V_2$$

$$-V_1 = \frac{Y_{12} V_2 - I_s}{Y_{11} + Y_{11}} \rightarrow ④$$

Substitute eqn ④ in ③.

$$I_2 = Y_{21} \left[\frac{Y_{12} V_2 - I_s}{Y_{11} + Y_{11}} \right] + Y_{22} V_2$$

With no source curr at 1st ie if current source is open-circuited

$$I_2 = - \frac{Y_{21} Y_{12} V_2}{Y_{11} + Y_{11}} + Y_{22} V_2$$

Hence the driving point admittance at the 1st port is given as

$$\frac{I_2}{V_2} = \frac{Y_{22} V_2 + Y_{21} Y_{11} - Y_{11} Y_{12}}{Y_{11} + Y_{11}} = \frac{\Delta Y + Y_{22} Y_s}{Y_s + Y_{11}}$$


If the input is open circuited ie the source admittance is zero. $\frac{V_2}{I_2} = \frac{0 \cdot Y_{11}}{\Delta Y} = \frac{0 \cdot Y_{11}}{\Delta Y} = \Delta Y$

If the input is short circuited ie $Y_s = \infty, Z_s = 0$


$$\frac{V_2}{I_2} = \frac{Y_s (1 + Y_{11}/Y_{11})}{Y_{11} (\Delta Y/Y_s + Y_{12})} = \frac{1}{Y_{11}}$$

problems on Terminated 2-port N/w.

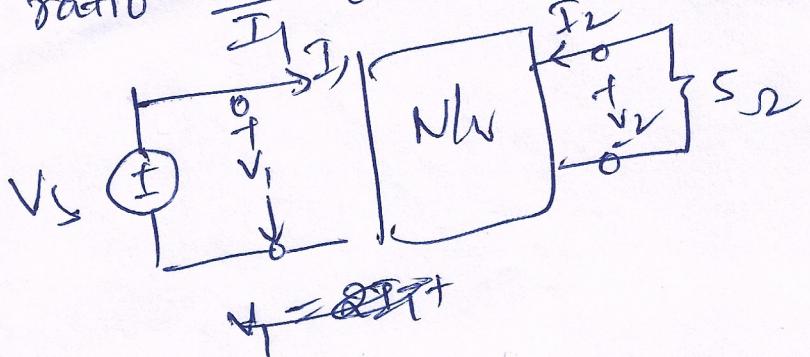1. The 2-parameters are $\bar{Z}_{11}=Z_{22}$, $\bar{Z}_{12} = \bar{Y}_2 Z_{22}$, $\bar{Z}_{22} = S_{22}$. Calculate the voltage ratio $\frac{V_2}{V_1}$, current ratio $\frac{-I_2}{I_1}$ and input impedance $\frac{V}{I_1}$



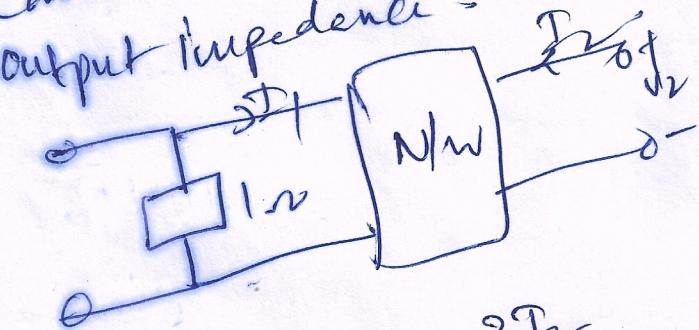2. The 4-parameters for a 2-port N/w $\bar{Y}_{11}=4\Omega$ $\bar{Y}_{12}=\bar{Y}_{21}=5\Omega$ $\bar{Y}_{22}=4\Omega$. If a resistor of 1Ω is connected across port-1 of the N/w then find the output impedance -



3. The $V_1 = 8V - 3I_1$
 $I_1 = 6V - 2I_2$
a load resistance of S_{22} is connected across the 0/V port. calculate the input impedance